

## UNIT-1

### Review of Number Systems & codes ①

There are four types of number systems in digital electronics

① Decimal number system (Base 10)

② Binary number system (Base 2)

③ Octal number system (Base 8)

④ Hexa-decimal number system (Base 16)

Base is also known as radix.

If the base of any number system describes the no. of distinct symbols and the highest digit/number in that number system.

Ex: In hexa decimal number system, there are 16 symbols they are

0, 1, 2, 3, 4, 5, 6, 7, 8, 9, A, B, C, D, E, F

\* List the first 20 numbers in hexa decimal number system

0, 1, 2, 3, 4, 5, 6, 7, 8, 9, A, B, C, D, E, F, 10, 11, 12, 13

\* List the first 15 numbers in Base 12 system

0, 1, 2, 3, 4, 5, 6, 7, 8, 9, A, B, 10, 11, 12

\* List the first 10 numbers in octal number system

0, 1, 2, 3, 4, 5, 6, 7, 10, 11

### Base Conversions!

To Convert  $( )_{10}$  to  $( )_8$  perform the successive division of the given decimal number with required base upto the coefficient is less than the base.

Ex Convert  $(48)_{10} = (?)_2$

2	48	
	24 - 0	
	12 - 0	
	6 - 0	
	3 - 0	
	1 - 1	

$$\rightarrow (48)_{10} = (110000)_2$$

\*Convert  $(71)_{10} = (?)_2$  \*Convert  $(524)_{10} = (?)_2$

2	71	
	35 - 1	
	17 - 1	
	8 - 1	
	4 - 0	
	2 - 0	
	1 - 0	

$$(71)_{10} = (1000111)_2$$

2	524	
	262 - 0	
	131 - 0	
	65 - 1	
	32 - 1	
	16 - 0	
	8 - 0	
	4 - 0	
	2 - 0	
	1 - 0	

$$(524)_{10} = (1000001100)_2$$

\*Convert  $(461)_{10} = (?)_2$  \*Convert  $(10.125)_{10} = (?)_2$

2	461	
	230 - 1	
	115 - 0	
	57 - 1	
	28 - 1	
	14 - 0	
	7 - 0	
	3 - 1	
	1 - 1	

$$(461)_{10} = (111001101)_2$$

2	10	
2	5 - 0	
2	2 - 1	
	1 - 0	

$$\begin{aligned}125 \times 2 &= 0.250 \\250 \times 2 &= 0.500 \\500 \times 2 &= 1.000\end{aligned}$$

$$(10.125)_{10} = (1010.001)_2$$

\* Convert  $(39.225)_{10} = (?)_2$

$$\begin{array}{r} 2 \mid 39 \\ 2 \mid 19-1 \\ 2 \mid 9-1 \\ 2 \mid 4-1 \\ 2 \mid 2-0 \\ 1-0 \end{array}$$

$$\begin{aligned} & 225 \times 2 = 0.450 \\ & 450 \times 2 = 0.900 \\ & 900 \times 2 = 1.800 \\ & 800 \times 2 = 1.600 \end{aligned}$$

(3)

$$(39.225)_{10} = (100111.0011)_2$$

\* Convert  $(63.525)_{10} = (?)_2$

$$\begin{array}{r} 2 \mid 63 \\ 2 \mid 31-1 \\ 2 \mid 15-1 \\ 2 \mid 7-1 \\ 2 \mid 3-1 \\ 1-1 \end{array}$$

$$\begin{aligned} & 525 \times 2 = 1.050 \\ & 050 \times 2 = 0.100 \\ & 100 \times 2 = 0.200 \\ & 200 \times 2 = 0.400 \\ & 400 \times 2 = 0.800 \end{aligned}$$

$$(63.525)_{10} = (111111.1000)_2$$

### Conversion of decimal to octal

\* Convert  $(25)_{10} = (?)_8$

$$\begin{array}{r} 8 \mid 25 \\ 3-1 \end{array}$$

$$(25)_{10} = (31)_8$$

\* Convert  $(125)_{10} = (?)_8$

$$\begin{array}{r} 8 \mid 125 \\ 8 \mid 15-5 \\ 1-7 \end{array}$$

$$(125)_{10} = (175)_8$$

\* Convert  $(93)_{10} = (?)_8$

$$\begin{array}{r} 8 \mid 93 \\ 8 \mid 11-5 \\ 1-3 \end{array}$$

$$(93)_{10} = (135)_8$$

\* Convert  $(154.125)_{10} = (?)_8$

$$\begin{array}{r} 8 \mid 154 \\ 8 \mid 19-2 \\ 2-3 \end{array}$$

$$(154.125)_{10} = (232.1)_8$$

\* Convert  $(23.225)_{10} = (?)_8$

$$\begin{array}{r} 8 \mid 23 \\ 2-7 \end{array}$$

$$(23.225)_{10} = (27.1681)_8$$

$$\begin{aligned} & 225 \times 8 = 1.800 \\ & 800 \times 8 = 6.400 \\ & 400 \times 8 = 3.200 \\ & 200 \times 8 = 1.600 \end{aligned}$$

→ Conversion from decimal to hexa decimal

\* Convert  $(31)_{10} = (?)_{16}$  \* Convert  $(49)_{10} = (?)_{16}$  (4)

$$16 \overline{)31} \\ \underline{1-F}$$

$$(31)_{10} = (1F)_{16}$$

$$16 \overline{)49} \\ \underline{3-1}$$

$$(49)_{10} = (31)_{16}$$

\* convert  $(62)_{10} = (?)_{16}$

$$16 \overline{)62} \\ \underline{3-E}$$

$$(62)_{10} = (3E)_{16}$$

\* convert  $(74)_{10} = (?)_{16}$

$$16 \overline{)74} \\ \underline{4-A}$$

$$(74)_{10} = (4A)_{16}$$

\* convert  $(70.250)_{10} = (?)_{16}$

$$16 \overline{)70} \\ \underline{4-6}$$

$$(70.250)_{10} = (46.4)_{16}$$

$$250 \times 16 = 4000$$

\*  $(92.150)_{10} = (?)_{16}$

$$16 \overline{)92} \\ \underline{5-6}$$

$$(92.150)_{10} = (5C.2666)_{16}$$

$$150 \times 16 = 2400$$

$$400 \times 16 = 6400$$

$$400 \times 16 = 6400$$

$$400 \times 16 = 6400$$

\* convert  $(10.125)_{10} = (?)_4$

$$4 \overline{)10} \\ \underline{2-2}$$

$$(10.125)_{10} = (22.02)_4$$

$$125 \times 4 = 0.500$$

$$500 \times 4 = 2.000$$

8 to 10 conversions

Binary to decimal conversion

$$\rightarrow (110000)_2 = (?)_{10}$$

$$1 \times 2^5 + 1 \times 2^4 + 0 \times 2^3 + 0 \times 2^2 + 0 \times 2^1 + 0 \times 2^0$$

$$\Rightarrow 32 + 16$$

$$\rightarrow (48)_{10}$$

$$\rightarrow (1000001100)_2$$

$$1 \times 2^9 + 0 + 1 \times 2^8 + 1 \times 2^7$$

$$512 + 8 + 4$$

$$(524)_{10}$$

$$\rightarrow (1000011)_2 \times 2^8$$

$$1 \times 2^6 + 0 + 1 \times 2^5 + 1 \times 2^4 + 1 \times 2^3$$

$$64 + 4 + 2 + 1$$

$$68 + 3$$

$$(71)_{10}$$

$$\rightarrow (11100101)_2$$

$$1 \times 2^8 + 1 \times 2^7 + 1 \times 2^6 + 1 \times 2^3 + 1 \times 2^2 + 1 \times 2^0$$

$$256 + 128 + 64 + 8 + 4 + 2 + 1$$

$$(461)_{10}$$

$$\rightarrow (1010.001)_2 = (?)_{10}$$

$$1 \times 2^3 + 1 \times 2^1 + 0 \times 2^{-1} + 1 \times 2^{-3}$$

$$8 + 2 + \frac{1}{2^3} \Rightarrow 10 + 0.125$$

$$(10.125)_{10}$$

$$\rightarrow (100111.001)_2 = (?)_{10}$$

$$1 \times 2^5 + 1 \times 2^4 + 1 \times 2^3 + 1 \times 2^0 + 1 \times 2^{-3} + 1 \times 2^{-4}$$

$$\Rightarrow 32 + 16 + 8 + 1 + \frac{1}{2^3} + \frac{1}{2^4}$$

$$\Rightarrow 39 + 0.125 + 0.0625 \Rightarrow (39.1875)_{10} \approx (39.1875)$$

$$\rightarrow (111111.1000)_2 = (?)_{10}$$

$$1 \times 2^5 + 1 \times 2^4 + 1 \times 2^3 + 1 \times 2^2 + 1 \times 2^1 + 1 \times 2^0 + 1 \times 2^{-1}$$

$$32 + 16 + 8 + 4 + 2 + 1 + 0.5 \Rightarrow (63.5)_{10}$$

(5)

## Octal to decimal conversion

$$*(31)_8 = (?)_{10}$$

$$8^1 \times 3 + 1 \times 8^0$$

$$24 + 1$$

$$\boxed{(25)_{10}}$$

$$*(175)_8 = (?)_{10}$$

$$1 \times 8^2 + 7 \times 8^1 + 5 \times 8^0$$

$$64 + 56 + 5$$

$$\boxed{(125)_{10}}$$

$$*(135)_8 = (?)_{10}$$

$$1 \times 8^2 + 3 \times 8^1 + 5 \times 8^0$$

$$64 + 24 + 5$$

$$\boxed{(93)_{10}}$$

$$*(24.1631)_8 = (?)_{10}$$

$$2 \times 8^1 + 4 \times 8^0 + 1 \times 8^{-1} + 6 \times 8^{-2}$$

$$3 \times 8^{-3} + 8^{-4} \times 1$$

$$16 + 4 + 0.125 + 0.09375 + 0.00585 + 0.00024$$

$$\boxed{(23.2248)_{10}}$$

$$*(232.1)_8 = (?)_{10}$$

$$2 \times 8^2 + 3 \times 8^1 + 2 \times 8^0 + 1 \times 8^{-1}$$

$$128 + 24 + 2 + 0.125$$

$$\boxed{154.125}$$

Ans: 154.125

## Hexadecimal to decimal

$$\rightarrow (1F)_{16} = (?)_{10}$$

$$1 \times 16^1 + 15 \times 16^0$$

$$16 + 15 \Rightarrow \boxed{(31)_{10}}$$

$$\rightarrow (31)_{16} = (?)_{10}$$

$$16^1 \times 3 + 16^0 \times 1$$

$$48 + 1 = \boxed{49}_{10}$$

$$*(5C.2666)_{16} = (?)_{10}$$

$$5 \times 16^1 + 12 \times 16^0 + 2 \times 16^{-1} + 6 \times 16^{-2} + 6 \times 16^{-3} + 6 \times 16^{-4}$$

$$80 + 12 + 0.125 + 0.0234 + 0.00144 + 0.00009$$

$$\Rightarrow (92.1498)_{10} \approx \boxed{(92.150)_{10}}$$

Base 4 to Base 10

$$x \left( \frac{1}{2} \cdot \frac{1}{2} \right)_4$$

$$2 \times 4^3 + 2 \times 4^0 + 0 + 2 \times 4^{-2}$$

$$8 + 2 + 0 + 2 \times \frac{1}{16}$$

$$10 + 0.125$$

$$(10.125)_{10}$$

(7)

### 2-8 Conversions:

In binary to octal conversion segment the given binary number as group and each group should contain 3 bit. Replace each group with its octal equivalent.

3-bit binary code

2	1	0
4	2	1
0	0	0 - 0
0	0	1 - 1
0	1	0 - 2
0	1	1 - 3
1	0	0 - 4
1	0	1 - 5
1	1	0 - 6
1	1	1 - 7

$$2^3 = 8$$

\* Convert  $(1011010)_2$  to (?)<sub>8</sub>

88

$$\begin{array}{|c|c|c|c|} \hline 0 & 0 & 1 & 1 \\ \hline 1 & 3 & 2 & \\ \hline \end{array}$$

$$(132)_8$$

\*  $(1110101101101)_2$  to (?)<sub>8</sub>

$$\begin{array}{|c|c|c|c|c|c|c|} \hline 0 & 0 & 1 & 1 & 0 & 1 & 0 & 1 & | & 1 & 0 & 1 \\ \hline 1 & 6 & 5 & 5 & 5 & 5 & 5 & | & 1 & \\ \hline \end{array}$$

$$(16555)_8$$

$$*(1110111110110.0110111)_2 = (?)_8$$

(8)

$$\begin{array}{r} 111|011|111|110|110.011|011|100 \\ +3 \quad +6 \quad 6 \cdot 3 \quad 3 \quad 4 \end{array}$$

$$(73+66.334)_8$$

Binary to hexadecimal:

4 bit  
binary  
code

$2^4$	$2^3$	$2^2$	$2^1$	$2^0$	
8	4	2	1		
0	0	0	0	-0	
0	0	0	1	-1	
0	0	1	0	-2	
0	0	1	1	-3	
0	1	0	0	-4	
0	1	0	1	-5	
0	1	1	0	-6	
0	1	1	1	-7	
1	0	0	0	-8	
1	0	0	1	-9	
1	0	1	0	-10 -A	
1	0	1	1	-11 -B	
1	1	0	0	-12 -C	
1	1	0	1	-13 -D	
1	1	1	0	-14 -E	
1	1	1	1	-15 -F	

$$2^4 = 16$$

Scanned with CamScanner

$$*(11001010)_2 = (?)_{16} \quad * (10) \quad (9)$$

$\begin{array}{r} 11001010 \\ \text{C} \quad \text{A} \end{array}$

$(CA)_{16}$

$$*(10101110101011)_2 = (?)_{16}$$

$\begin{array}{r} 0010101110101011 \\ \text{2} \quad \text{B} \quad \text{A} \quad \text{B} \end{array}$

$(2BAB)_{16}$

$$*(101101010.101010111)_2 = (?)_{16}$$

$\begin{array}{r} 0001001010.101010111 \\ \text{1} \quad \text{6} \quad \text{A} \quad \text{A} \quad \text{B} \quad \text{8} \end{array}$

$(16ABA8)_{16}$

0001 0000 0001 0001

### Octal to Binary conversion

\* In octal to binary conversion each digit of octal number should be replaced with its 3-bit binary equivalent

$$*(132)_8$$

$\begin{array}{r} 1 \mid 3 \mid 2 \\ 001 \quad 011 \quad 010 \end{array}$

$(001011010)_2$

$$*(16555)_8$$

$\begin{array}{r} 1 \mid 6 \mid 5 \mid 5 \mid 5 \\ 001 \quad 110 \quad 101 \end{array}$

$$*(75766.334)_8$$

$\begin{array}{r} 7 \mid 5 \mid 7 \mid 6 \mid 6 \cdot 3 \mid 3 \mid 4 \\ 111 \quad 011 \quad 111 \quad 110 \quad 110 \cdot 011 \quad 011 \quad 100 \end{array}$

$(1110111110110 \cdot 0110111)_2$

## Hexadecimal to binary:

\*  $(1011)_{16} = (?)_2$

1 | 0 | 1 | 1  
0001 0000 0001 0001

$$(0001000000010001)_2$$

\*  $(CA)_{16} = (?)_2$

C | A  
1100 | 1010

$$(11001010)_2$$

## Octal to hexadecimal conversion:

\* To convert Octal to hexadecimal convert the octal number to binary and then to hexadecimal.

→ Convert  $(145)_8 = (?)_{16}$ .

(a)  $(145)_8 = (?)_2$

1 | 4 | 5  
001 100 101

$$(001100101)_2$$

(b) 0000|0110|0101

0 6 5

$$(065)_{16} = (65)_{16}$$

$$\rightarrow (1372)_8 = (?)_{16}$$

(11)

$$(a) \quad (1372)_8 = (?)_2.$$

$$\begin{array}{r} 0\ 0\ 1\ | 3\ 0\ 1\ 1\ | 7\ 0\ 1\ 1\ | 2\ 0\ 1\ 0 \\ \text{---} \end{array}$$

$$(00101111010)_2$$

$$(b) \quad (00101111010)_2 = (?)_{16}.$$

$$\begin{array}{r} 0\ 0\ 1\ 0\ | 1\ 1\ 1\ 1\ | 1\ 0\ 1\ 0 \\ 2\ \ \ \ F\ \ \ \ A \\ \text{---} \end{array}$$

$$(2FA)_{16}$$

Hexadecimal to octal

$$\rightarrow (DAC)_{16} = (?)_8$$

$$(a) \quad (DAC)_{16} = (?)_2.$$

$$\begin{array}{r} D\ | \ A\ | C \\ 1101\ 1010\ 1100 \\ \text{---} \end{array}$$

$$(110110101100)_2.$$

$$(b) \quad (110|110|101|100)_2 = (?)_8$$

$$(6654)_8$$

$$\rightarrow (1A8)_{16} = (?)_8$$

$$(a) \quad (1A8)_{16} = (?)_2$$

$$\begin{array}{r} 1\ | \ A\ | 8 \\ 0001\ 1010\ 1000 \\ \text{---} \end{array}$$

$$(000110101000)_2$$

$$(b) \quad 000|110|101|000$$

$$(650)_8$$

#### \*Note

10 → successive division

γ → powers multiplication

γ → if powers relation exists then grouping and use bit code else

use intermediate (decimal / binary)

to convert

$$\begin{array}{r} 6\ 1\ 5\ 0 \\ 1\ 0\ 1\ 0 \\ \text{---} \end{array}$$

## Binary addition:

$$\rightarrow 8 \rightarrow 1 \ 0 \ 0 \ 0$$

$$4 \rightarrow 0 \ 1 \ 1 \ 1$$

$$15 \rightarrow \underline{1 \ 1 \ 1 \ 1}$$

$$\rightarrow 7 \ 0 \ 1 \ 1 \ 1$$

$$7 \ 0 \ 1 \ 1 \ 1$$

$$14 \ 1 \ 1 \ 1 \ 0$$

$$\rightarrow 15 \ 1 \ 1 \ 1 \ 1$$

$$15 \ 1 \ 1 \ 1 \ 1$$

$$\underline{1 \ 1 \ 1 \ 1 \ 0}$$

$$\rightarrow 5 \ 0 \ 1 \ 0 \ 1$$

$$5 \ 0 \ 1 \ 0 \ 1$$

$$10 \ 1 \ 0 \ 1 \ 0$$

$$\rightarrow 110 \ 10 \ 1$$

$$1 \ 0 \ 1 \ 0$$

$$1 \ 1 \ 1$$

$$0 \ 1 \ 1$$

$$\underline{1 \ 0 \ 0 \ 0 \ 0 \ 0}$$

## Binary subtraction:

$$8 \rightarrow 1 \ 0 \ 0 \ 0$$

$$4 \rightarrow 1 \ 0 \ 1 \ 0$$

$$-4 \underline{4}$$

$$0 \ 0 \ 0 \ 0$$

$$1 \ 0 \ 1 \ 0$$

$$0 \ 1 \ 0 \ 1$$

$$\underline{0 \ 1 \ 0 \ 1}$$

Here  $2 \rightarrow 10$

$$3 \rightarrow 0011$$

$$4 \rightarrow 10100$$

$$5 \rightarrow 0101$$

$$6 \rightarrow 0110$$

$$7 \rightarrow 0111$$

$$8 \rightarrow 1000$$

$$9 \rightarrow 1001$$

$$10 \rightarrow 1010$$

$$11 \rightarrow 1011$$

$$12 \rightarrow 1100$$

$$13 \rightarrow 1101$$

$$14 \rightarrow 1110$$

$$15 \rightarrow 1111$$

$$16 \rightarrow 10000$$

$$17 \rightarrow 10001$$

$$18 \rightarrow 10010$$

$$19 \rightarrow 10011$$

$$20 \rightarrow 10100$$

$$21 \rightarrow 10101$$

$$22 \rightarrow 10110$$

$$23 \rightarrow 10111$$

$$24 \rightarrow 11000$$

$$25 \rightarrow 11001$$

$$26 \rightarrow 11010$$

$$27 \rightarrow 11011$$

$$28 \rightarrow 11100$$

$$29 \rightarrow 11101$$

$$30 \rightarrow 11110$$

$$31 \rightarrow 11111$$

$$32 \rightarrow 100000$$

$$33 \rightarrow 100001$$

$$34 \rightarrow 100010$$

$$35 \rightarrow 100011$$

$$36 \rightarrow 100100$$

$$37 \rightarrow 100101$$

$$38 \rightarrow 100110$$

$$39 \rightarrow 100111$$

$$40 \rightarrow 101000$$

$$41 \rightarrow 101001$$

$$42 \rightarrow 101010$$

$$43 \rightarrow 101011$$

$$44 \rightarrow 101100$$

$$45 \rightarrow 101101$$

$$46 \rightarrow 101110$$

$$47 \rightarrow 101111$$

$$48 \rightarrow 110000$$

$$49 \rightarrow 110001$$

$$50 \rightarrow 110010$$

$$51 \rightarrow 110011$$

$$52 \rightarrow 110100$$

$$53 \rightarrow 110101$$

$$54 \rightarrow 110110$$

$$55 \rightarrow 110111$$

$$56 \rightarrow 111000$$

$$57 \rightarrow 111001$$

$$58 \rightarrow 111010$$

$$59 \rightarrow 111011$$

$$60 \rightarrow 111100$$

$$61 \rightarrow 111101$$

$$62 \rightarrow 111110$$

$$63 \rightarrow 111111$$

$$31(2) \rightarrow 011111$$

$$32(2) \rightarrow 100000$$

$$33(2) \rightarrow 100001$$

$$34(2) \rightarrow 100010$$

$$35(2) \rightarrow 100011$$

$$36(2) \rightarrow 100100$$

$$37(2) \rightarrow 100101$$

$$38(2) \rightarrow 100110$$

$$39(2) \rightarrow 100111$$

$$40(2) \rightarrow 101000$$

$$41(2) \rightarrow 101001$$

$$42(2) \rightarrow 101010$$

$$43(2) \rightarrow 101011$$

$$44(2) \rightarrow 101100$$

$$45(2) \rightarrow 101101$$

$$46(2) \rightarrow 101110$$

$$47(2) \rightarrow 101111$$

$$48(2) \rightarrow 110000$$

$$49(2) \rightarrow 110001$$

$$50(2) \rightarrow 110010$$

$$51(2) \rightarrow 110011$$

$$52(2) \rightarrow 110100$$

$$53(2) \rightarrow 110101$$

$$54(2) \rightarrow 110110$$

$$55(2) \rightarrow 110111$$

$$56(2) \rightarrow 111000$$

$$57(2) \rightarrow 111001$$

$$58(2) \rightarrow 111010$$

$$59(2) \rightarrow 111011$$

$$60(2) \rightarrow 111100$$

$$61(2) \rightarrow 111101$$

$$62(2) \rightarrow 111110$$

$$63(2) \rightarrow 111111$$

$$64(2) \rightarrow 010000$$

$$65(2) \rightarrow 010001$$

$$66(2) \rightarrow 010010$$

$$67(2) \rightarrow 010011$$

$$68(2) \rightarrow 010100$$

$$69(2) \rightarrow 010101$$

$$70(2) \rightarrow 010110$$

$$71(2) \rightarrow 010111$$

$$72(2) \rightarrow 011000$$

$$73(2) \rightarrow 011001$$

$$74(2) \rightarrow 011010$$

$$75(2) \rightarrow 011011$$

$$76(2) \rightarrow 011100$$

$$77(2) \rightarrow 011101$$

$$78(2) \rightarrow 011110$$

$$79(2) \rightarrow 011111$$

$$80(2) \rightarrow 100000$$

$$81(2) \rightarrow 100001$$

$$82(2) \rightarrow 100010$$

$$83(2) \rightarrow 100011$$

$$84(2) \rightarrow 100100$$

$$85(2) \rightarrow 100101$$

$$86(2) \rightarrow 100110$$

$$87(2) \rightarrow 100111$$

$$88(2) \rightarrow 101000$$

$$89(2) \rightarrow 101001$$

$$90(2) \rightarrow 101010$$

$$91(2) \rightarrow 101011$$

$$92(2) \rightarrow 101100$$

$$93(2) \rightarrow 101101$$

$$94(2) \rightarrow 101110$$

$$95(2) \rightarrow 101111$$

$$96(2) \rightarrow 110000$$

$$97(2) \rightarrow 110001$$

$$98(2) \rightarrow 110010$$

$$99(2) \rightarrow 110011$$

$$100(2) \rightarrow 110100$$

$$101(2) \rightarrow 110101$$

$$102(2) \rightarrow 110110$$

$$103(2) \rightarrow 110111$$

$$104(2) \rightarrow 111000$$

$$105(2) \rightarrow 111001$$

$$106(2) \rightarrow 111010$$

$$107(2) \rightarrow 111011$$

$$108(2) \rightarrow 111100$$

$$109(2) \rightarrow 111101$$

$$110(2) \rightarrow 111110$$

$$111(2) \rightarrow 111111$$

$$112(2) \rightarrow 010000$$

$$113(2) \rightarrow 010001$$

$$114(2) \rightarrow 010010$$

$$115(2) \rightarrow 010011$$

$$116(2) \rightarrow 010100$$

$$117(2) \rightarrow 010101$$

$$118(2) \rightarrow 010110$$

$$119(2) \rightarrow 010111$$

$$120(2) \rightarrow 011000$$

$$121(2) \rightarrow 011001$$

$$122(2) \rightarrow 011010$$

$$123(2) \rightarrow 011011$$

$$124(2) \rightarrow 011100$$

$$125(2) \rightarrow 011101$$

$$126(2) \rightarrow 011110$$

$$127(2) \rightarrow 011111$$

$$128(2) \rightarrow 100000$$

$$129(2) \rightarrow 100001$$

$$130(2) \rightarrow 100010$$

$$131(2) \rightarrow 100011$$

$$132(2) \rightarrow 100100$$

$$133(2) \rightarrow 100101$$

$$134(2) \rightarrow 100110$$

$$135(2) \rightarrow 100111$$

$$136(2) \rightarrow 101000$$

$$137(2) \rightarrow 101001$$

$$138(2) \rightarrow 101010$$

$$139(2) \rightarrow 101011$$

$$140(2) \rightarrow 101100$$

$$141(2) \rightarrow 101101$$

$$142(2) \rightarrow 101110$$

$$143(2) \rightarrow 101111$$

$$144(2) \rightarrow 110000$$

$$145(2) \rightarrow 110001$$

$$146(2) \rightarrow 110010$$

$$147$$

$$\begin{array}{r}
 & 0 & 1 & 2 & 2 & 2 \\
 * & 1 & 6 & 1 & 0 & 0 0 0 \\
 1 & 4 & 0 & 1 & 1 & 1 0 \\
 \hline
 \underline{2} & 0 & 0 & 0 & 1 & 0
 \end{array}
 \quad
 \begin{array}{r}
 & 1 & 8 & 9 & 0 & 2 & 0 & 2 \\
 * & 1 & 8 & 0 & 1 & 1 & 0 & 1 \\
 \hline
 5 & 0 & 0 & 1 & 0 & 1
 \end{array}$$

(13)

### Complements:

For any "base" system there exists two complements  
 1.  $\gamma$ 's complement  
 2.  $(\gamma-1)$ 's complement

\* To find  $\gamma$ 's complement the following formula is used i.e.,  $\gamma^n - N$

where  $\gamma$  - Base of number system  
 $n$  - no. of integer digits in the given number

$N$  - The number, for which  $\gamma$ 's complement to be calculated

\* To find  $(\gamma-1)$ 's complement the following formula is used i.e.,  $(\gamma^n - 1) - N$

### Complements in binary number system.

1's complement

→ Find 1's complement of 101

$$N = 101$$

$$n = 3, \gamma = 2$$

$$\text{Formula: } (\gamma^n - 1) - N$$

$$(2^3 - 1) - N$$

$$(8 - 1) - 101$$

$$7(111) - 101$$

$$111 - 101$$

$$\boxed{010}$$

$$\begin{array}{r}
 111 \\
 101 \\
 \hline
 010
 \end{array}$$

1's complement of 101 is 010

→ Find 1's complement of 1010

1's complement of 1010 is 01011

Simply replace  
1's with 0 & 0's  
with 1's

14

→ 100011

1's complement is 011100

→ 2's complement

2's complement can be calculated by adding 1 to 1's complement of number.

\* Find the 2's complement of following number

→ 1101

1's complement = 0010

Add 1 = 1

2's complement 0011

→ 1000

1's complement = 0111

Add 1 = 1

2's complement 1000

→ 10000

1's complement = 01111

Add 1 = 1

10000

→ 10110

1's complement = 01001

01010

By directly 01010

\* To find 2's complement directly there are two cases.

(i) if units place have zero then from right to left do not change the number until 1 is reached then next numbers are interchanged by 0's as 1 & 1's as 0

(ii) if units place have 1 then not exchange 1 kept it as 1 & then next numbers are interchanged by 0 as 1 & 1 as 0

(1) 1010

Ans 01010

(2) 111101

2's comp 000011

→ 10000

1's complement = 01111

11111  
10000

## 1's Complement Subtraction

(15)

If  $A - B$  is the required operation take the 1's complement of  $B$  & add it to  $A$ . After adding there are two cases

Case(1): Carry generated.

If carry generated after the addition of A and B's complement of B End-around the carry i.e., add carry to the LSB (least significant bit)

Case (ii): Carry not generated

If carry not generated after the addition, take the 1's Compliment of result again and put a '-' sign before the result.

Ex-:

$$\begin{array}{r} 9 \\ \times 4 \\ \hline 5 \end{array}$$

case (1)

$$\begin{array}{r}
 9 \rightarrow 1 \ 0 \ 0 \ 1 \\
 + 44 \rightarrow 1 \ 0 \ 1 \ 1 \\
 (+) \underline{\quad} \quad \quad \quad \\
 \text{Carry } 1 \ 0 \ 1 \ 0 \ 0 \\
 + \quad \quad \quad \quad \quad \\
 \hline
 5 \rightarrow 0 \ 1 \ 0 \ 1
 \end{array}$$

$$5 \rightarrow \overline{0101}$$

$$\begin{array}{r}
 * \cdot 8 \rightarrow 1^{\circ} 0^{\circ} 0^{\circ} \\
 3 \rightarrow 0^{\circ} 0^{\circ} 1^{\circ} 1^{\circ} \\
 \hline
 5 \rightarrow 0^{\circ} 1^{\circ} 0^{\circ} 1^{\circ}
 \end{array}$$

case(1):

$$\begin{array}{r}
 8 & 1 & 0 & 0 & 0 \\
 -3 & (+) & 1 & 1 & 0 & 0 \\
 \hline
 5 & & 1 & 0 & 1 & 0 & 0 \\
 \text{carry } 0^+ & & & & & & 1 \\
 \hline
 & & 0 & 1 & 0 & 1 &
 \end{array}$$

case(1)

$$\begin{array}{r}
 & 0 & 1 & 0 & 0 \\
 4 & . & 0 & 1 & 0 \\
 9 & 0 & 1 & 1 & 0 \\
 \hline
 & 1 & 0 & 1 & 0 \\
 \hline
 & 0 & 1 & 0 & 1 \rightarrow 1^{\text{st}} \text{ comp of}
 \end{array}$$

cause(s) :

$$\begin{array}{r}
 & 0 & 0 & 1.1 \\
 3 & 0 & 0 & 1.1 \\
 8(1^{\text{st}} \text{ comp}) & 0 & 1 & 1.1 \\
 \cdot & & & \\
 & \hline
 & 1 & 0.1 & 0
 \end{array}
 \rightarrow \text{carryout generated}$$

$$\begin{array}{r} * \quad 10 \rightarrow 10 \quad 10 \\ (-) \quad 7 \rightarrow 0 \quad 1 \quad 1 \quad 1 \\ \hline 3 \qquad \qquad \qquad 0 \quad 0 \quad 1 \quad 1 \end{array}$$

$$\begin{array}{r}
 10 \rightarrow 1010 \\
 \text{is comp of } 7 \quad (+) \overline{000} \\
 \hline
 10010 \\
 (+) \overline{\quad\quad\quad\quad\quad} \\
 \hline
 0011
 \end{array}$$

$$\begin{array}{r} 10 \\ \times 110 \\ \hline 100 \end{array}$$

$$\begin{array}{r} * \quad 15 \\ (-) \frac{11}{4} \\ \hline 1111 \\ 1011 \\ \hline 0100 \end{array}$$

$$\begin{array}{r}
 15 \quad 1111 \\
 \text{is composite} \quad (+) \overset{0}{\underset{1}{\mid}} \quad 100 \\
 \hline
 10011 \\
 \boxed{+1} \\
 \hline
 00100
 \end{array}$$

$$\begin{array}{r}
 11 \\
 \text{is of } 15 \\
 \hline
 -4
 \end{array}
 \quad
 \begin{array}{r}
 1^{\circ} 0 1.1 \\
 0 0 0 0 \\
 \hline
 1 0 1 1 \\
 \hline
 -0 1 0 0
 \end{array}$$

$$\begin{array}{r} * \\ \begin{array}{r} 101101 \\ 010110 \\ \hline \end{array} \end{array}$$

## case (i)

$$\begin{array}{r}
 101101 \\
 (+) \underline{101001} \\
 \hline
 \underline{1010110} \\
 + 1 \\
 \hline
 010111
 \end{array}$$

$$\begin{array}{r}
 010110 \\
 (+) \underline{010010} \\
 \hline
 101000 \\
 (-) \underline{010110} \\
 \hline
 000000
 \end{array}$$

## 2's Complement Subtraction:

(17)

If "A-B" is the required operation, takes the Two's Complement of "B" and Add it to "A". After addition there are two cases.

Case(1):

Carry generated. After adding Add 2's complement of "B" if carry is generated neglect carry. If carry is generated discard the

Case(2):

Carry is not generated. After adding "A" & 2's complement of "B" if carry is not generated take the 2's complement of result again and Put a (-) (minus) sign before it.

Ex:

$$* 8 \rightarrow 1000 \rightarrow 1000 \\ (-5) \rightarrow 0101 \rightarrow \begin{array}{r} (+) \\ 0101 \\ \hline 10011 \end{array}$$

discard the carry 0011

Ans. 3

$$5 \rightarrow 0101 \rightarrow 0101 \\ (-8) \rightarrow 1000 \rightarrow \begin{array}{r} (+) \\ 1000 \\ \hline 1101 \end{array}$$

Ans. -3

$$* 9 \rightarrow 1001 \rightarrow 1001$$

$$(-4) \rightarrow 0100 \rightarrow \begin{array}{r} (+) \\ 1100 \\ \hline 10101 \end{array}$$

discard 1

$$4 \rightarrow 0100 \rightarrow 0100$$

$$(-9) \rightarrow 1001 \rightarrow \begin{array}{r} (+) \\ 0111 \\ \hline 10101 \end{array}$$

2's -0101  $\rightarrow -5$

18

$$\begin{array}{r} \text{* } 23 \quad 0111 \rightarrow 1011 \\ \text{10} \quad | \quad | \quad | \quad | \\ \text{(+) } \underline{01010} \quad \text{(+) } \underline{10110} \\ \text{10110} \\ \text{discard } \boxed{01101} \end{array}$$

$$\begin{array}{r} \text{10} \quad 01010 \rightarrow 01010 \\ \text{23} \quad | \quad | \quad | \quad | \\ \text{(+) } \underline{10111} \quad \text{(+) } \underline{01001} \\ \text{10011} \\ \text{(-) } \underline{01101} \end{array}$$

$$\begin{array}{r} \text{* } 22 \quad 16 \quad 842 \\ \text{Q} \quad 01101 \rightarrow 00110 \\ \text{111101} \quad | \\ \text{001101} \quad | \\ \text{000011} \\ \text{010000} \\ -110000 \\ \hline \end{array}$$

$$\begin{array}{r} 111101 \rightarrow 111101 \\ \text{001101} \quad | \\ \text{110000} \\ \text{discard } \boxed{110000} \end{array}$$

### 9's Complement Subtraction:

If ' $A-B$ ' is the required operation take the 9's complement of B & add it to A. After adding there are two cases

case 1: carry generated.

If carry generated after the addition of A and 9's complement of B. End around the carry i.e., add carry to LSB

case 2: carry not generated

If carry not generated after the addition take the 9's complement of result again and put a '-' sign before the result.

$$* \quad \begin{array}{r} 8 \\ - 5 \xrightarrow{\text{9's comp}} \underline{4} \\ \hline 12 \\ \boxed{3} \end{array} \quad \begin{array}{r} 9 \\ - 5 \\ \hline 4 \end{array}$$

$\xrightarrow{\text{end around carry}}$

$$\begin{array}{r} 5 \\ - 8 \xrightarrow{\text{9's comp}} \underline{1} \\ \hline 6 \\ \boxed{-3} \end{array}$$

(19)

$$\begin{array}{r} 9 \\ - 6 \\ \hline 3 \end{array}$$

$$* \quad \begin{array}{r} 9 \\ - 4 \xrightarrow{\text{9's comp}} \underline{(+)5} \\ \hline 14 \\ \boxed{5} \end{array}$$

$$\begin{array}{r} 9 \\ - 4 \\ \hline 5 \end{array}$$

$$\begin{array}{r} 4 \\ - 9 \xrightarrow{\text{9's comp}} \underline{(+)0} \\ \hline 4 \\ \boxed{-5} \end{array}$$

$\frac{9}{4} \frac{5}{6}$

$$* \quad \begin{array}{r} 25 \\ - 19 \xrightarrow{\text{9's comp}} \underline{(+)80} \\ \hline 105 \\ \boxed{6} \end{array}$$

$$\begin{array}{r} 19 \\ - 25 \xrightarrow{\text{9's comp}} \underline{(+)74} \\ \hline 953 \\ \boxed{-6} \end{array}$$

$\frac{99}{25} \frac{25}{4}$   
 $\frac{99}{93} \frac{93}{6}$

$$* \quad \begin{array}{r} 84 \\ - 27 \xrightarrow{\text{9's comp}} \underline{(+)72} \\ \hline 156 \\ \boxed{57} \end{array}$$

$$\begin{array}{r} 99 \\ - 27 \rightarrow 27 \\ \hline (-)84 \rightarrow \underline{(+)15} \\ \hline 9's of 42 \boxed{-57} \end{array}$$

$\frac{99}{84} \frac{84}{15} \frac{99}{42} \frac{99}{57}$

$$* \quad \begin{array}{r} 459 \\ - 362 \xrightarrow{\text{9's of 42}} \underline{(+)634} \\ \hline 1096 \\ \boxed{097} \end{array}$$

$$\begin{array}{r} 999 \\ - 362 \rightarrow 362 \\ \hline 634 \\ \hline 902 \end{array} \quad \begin{array}{r} 362 \rightarrow 362 \\ -(459) \rightarrow \underline{(+)540} \\ \hline 902 \\ \boxed{-97} \end{array}$$

$\frac{999}{902} \frac{999}{97}$

## 10's Complement Subtraction

(20)

E.g "A - B" is the required operation, takes 10's complement of B and add it to A. After addition there are two cases:

Case(I): Carry generated

If carry generated after adding A & 10's complement of B, if carry generated then discard the carry.

Case(II): Carry not generated.

After adding A & 10's complement of B if carry not generated take 10's complement of result again and put a (-)minus sign before it.

$$\begin{array}{r}
 \text{PP} \\
 \text{PB} \\
 9 \rightarrow 9 \\
 (-) 3 \xrightarrow{\text{10's comp}} 7 \\
 \hline
 (+) \cancel{6} \\
 \boxed{7} \\
 \text{discard.}
 \end{array}$$

$$\begin{array}{r}
 \text{10's comp.} \\
 9 \\
 - 9 \\
 \hline
 0 \\
 + 1 \\
 \hline
 1
 \end{array}$$

$$\begin{array}{r}
 8 \rightarrow 8 \\
 (-) 4 \xrightarrow{\text{10's comp}} 6 \\
 \hline
 \cancel{8} \\
 \boxed{6}
 \end{array}$$

$$\begin{array}{r}
 \text{10's comp.} \\
 9 \\
 - 8 \\
 \hline
 1 \\
 + 1 \\
 \hline
 4
 \end{array}$$

$$\begin{array}{r}
 56 \rightarrow 56 \\
 - 43 \xrightarrow{\text{10's comp}} 43 \\
 \hline
 \cancel{56} \\
 \boxed{13}
 \end{array}$$

$$\begin{array}{r}
 \text{10's comp.} \\
 99 \\
 - 43 \\
 \hline
 56 \\
 + 1 \\
 \hline
 44
 \end{array}$$

$$\begin{array}{r}
 99 \\
 - 87 \\
 \hline
 12 \\
 + 1 \\
 \hline
 13
 \end{array}$$

$$\begin{array}{r}
 * \quad 546 \\
 - 304 \\
 \hline
 \end{array}
 \quad
 \begin{array}{r}
 \xrightarrow{\text{id est}} 540 \\
 \cancel{6} \quad 93 \\
 \hline
 \textcircled{*} 239
 \end{array}
 \quad
 \begin{array}{r}
 999 \\
 304 \\
 \hline
 693
 \end{array}$$

$$\begin{array}{r}
 304 \rightarrow 304 \\
 -546 \rightarrow 454 \\
 \hline
 41 \\
 \hline
 461 \\
 \hline
 454 \\
 \hline
 239
 \end{array}$$

(21)

## Binary codes:

Binary codes are classified into 6 types

1. Weighted codes
  2. Non-Weighted codes
  3. Sequential codes
  4. Reflective codes
  5. Alphanumeric codes
  6. Error Correcting & detecting codes

In weighted codes each place value is having a specific weight. Based on the weights, the codes are derived.

Ex: 8421, 2421, 5411 etc....

## Non-weighted codes.

These are the codes derived from weighted codes and no specific weight for place value

Ex: Gray Code, Parity, excess 3 code etc..

Sequential Codes:      4211 → not sequential

In Sequential Codes the weights are continuously increasing from LSB to MSB

Ex: 8421.

## Reflective codes.

In these codes zero is the 1's complement of 9, 1 is the 1's complement of 8  
(P.T.O)

(P.F.O)

2 is the 1's complement of 8<sup>x</sup> and so on.

Ex: 2 4 2 1

(22)

→ Write the 2421 code

2 4 2 1

0 0 0 0 0

1 0 0 0 1

2 0 0 1 0

3 0 0 1 1

4 0 1 0 0

5 1 1 0 1

6 1 1 0 0

7 1 1 0 1

8 1 1 1 0

9 1 1 1 1

Alphanumeric codes:

In Alphanumeric codes, each alphabet (Both uppercase lowercase), numbers and symbols are having specific binary representation.

Ex: ASCII code

American Standard Code for  
Information Interchange

## Error Correcting & Error detecting codes

By using some of the binary codes errors can be detected but not corrected they are called error detecting codes.

By using some of the binary codes errors can be detected & corrected they are called error correcting code.

Ex: Hamming code.

### BCD Codes (Binary Coded decimal)

In BCD code all the decimal digits from 0 to 9 are coded with binary numbers as shown below

	8	4	2	1
0 - 0	0	0	0	0
1 - 0	0	0	0	1
2 - 0	0	1	0	0
3 - 0	0	1	1	0
4 - 0	1	0	0	0
5 - 0	1	0	1	0
6 - 0	1	1	0	0
7 - 0	1	1	1	0
8 - 1	0	0	0	0
9 - 1	0	0	1	0

(24)

28  
6  
4  
5BCD addition

In BCD addition, after adding two BCD numbers, the result should be valid BCD number. If it is invalid add correction factor 6 (0110) to the invalid BCD number.

$$\begin{array}{r} * 5 \rightarrow 0.1\ 0.1 \\ 3 \rightarrow \\ \hline 8 \rightarrow \begin{array}{r} (+) 0 \\ 0.11 \\ \hline 1\ 0\ 0\ 0 \end{array} \end{array}$$

$$\begin{array}{r} * 5 \rightarrow 0.1\ 0.1 \\ 5 \rightarrow \\ \hline 10 \rightarrow \begin{array}{r} (+) 1 \\ 0.1\ 0.1 \\ \hline 1\ 0\ 1 \end{array} \end{array} \xrightarrow{\text{0} \rightarrow \text{invalid BCD}}$$

$$\begin{array}{r} +6 \rightarrow 0 \\ 0.1\ 1\ 0 \\ \hline 0001 \end{array}$$

$$\begin{array}{r} * 8 \rightarrow 1\ 0\ 0\ 0 \\ +6 \rightarrow \\ \hline 14 \rightarrow \begin{array}{r} 0.1\ 1\ 0 \\ \hline 1\ 1\ 1\ 0 \end{array} \end{array} \xrightarrow{\text{0} \rightarrow \text{invalid BCD}}$$

$$\begin{array}{r} +6 \rightarrow 0 \\ 0.1\ 1\ 0 \\ \hline 0001 \end{array}$$

$$\begin{array}{r} * 15 \rightarrow 0001\ 0101 \\ 12 \rightarrow \\ \hline 27 \rightarrow \begin{array}{r} + 0001\ 0010 \\ \hline 0010\ 0111 \end{array} \end{array}$$

$$\begin{array}{r} * 39 \rightarrow 0011\ 1001 \end{array}$$

$$\begin{array}{r} (7) 23 \rightarrow 0010\ 0011 \\ \hline 62 \end{array}$$

$$\begin{array}{r} 0110\ 0010 \\ 6\ 2 \\ \hline +6 \end{array} \quad \begin{array}{r} 0110 \\ \hline 0110\ 0010 \\ 6\ 2 \end{array}$$

$$\begin{array}{r}
 * \quad 2 \quad 8 \\
 + \quad 2 \quad 6 \\
 \hline
 5 \quad 4
 \end{array}
 \rightarrow
 \begin{array}{r}
 0010 \quad 1000 \\
 0010 \quad 0110 \\
 \hline
 0100 \quad 1110
 \end{array}
 \rightarrow \text{Invalid BC D}$$

(25)

$$\begin{array}{r}
 * \quad 4 \quad 5 \\
 + \quad 3 \quad 8 \\
 \hline
 8 \quad 3
 \end{array}
 \rightarrow
 \begin{array}{r}
 0100 \quad 0101 \\
 0011 \quad 1000 \\
 \hline
 0111 \quad 1101
 \end{array}
 \rightarrow \text{Invalid BC D}$$

$$\begin{array}{r}
 1000 \quad 0011 \\
 + \quad 8 \quad 3 \\
 \hline
 1111 \quad 0110
 \end{array}
 \begin{array}{r}
 +6 \\
 \hline
 1000 \quad 0011
 \end{array}
 \begin{array}{r}
 \hline
 8 \quad 3
 \end{array}$$

$$\begin{array}{r}
 * \quad 1 \quad 5 \quad 4 \\
 + \quad 1 \quad 3 \quad 8 \\
 \hline
 2 \quad 9 \quad 5
 \end{array}
 \rightarrow
 \begin{array}{r}
 0001 \quad 0101 \quad 0111 \\
 0001 \quad 0011 \quad 1000 \\
 \hline
 0010 \quad 1000 \quad 1111
 \end{array}$$

$$\begin{array}{r}
 0010 \quad 1000 \quad 0101 \\
 + \quad 2 \quad 9 \quad 5 \\
 \hline
 0010 \quad 1001 \quad 0101
 \end{array}
 \begin{array}{r}
 +6 \\
 \hline
 0010 \quad 1001 \quad 0101
 \end{array}
 \begin{array}{r}
 \hline
 2 \quad 9 \quad 5
 \end{array}$$

$$\begin{array}{r}
 * \quad 8 \quad 6 \quad 7 \\
 + \quad 5 \quad 4 \\
 \hline
 14 \quad 4 \quad 1
 \end{array}
 \rightarrow
 \begin{array}{r}
 1000 \quad 0110 \quad 0111 \\
 0101 \quad 0111 \quad 0100 \\
 \hline
 1101 \quad 1101 \quad 1011
 \end{array}$$

$$\begin{array}{r}
 0001 \quad 0100 \quad 0100 \quad 0001 \\
 + \quad 1101 \quad 1110 \quad 0001 \\
 \hline
 +6 \quad 1 \quad 1 \quad 0110
 \end{array}$$

$$\begin{array}{r}
 +6 \quad 1 \quad 1 \quad 0110 \\
 \hline
 1110 \quad 0100 \quad 0001
 \end{array}$$

$$\begin{array}{r}
 +6 \quad 0110 \\
 \hline
 0001 \quad 0100 \quad 0100 \quad 0001
 \end{array}$$

## BCD subtraction:

26 \*

If  $(A - B)$  is required operation, take the 9's complement of  $B$  and add it to  $A$ . After adding there are two cases.

### Case 1: Invalid BCD

If the sum is invalid BCD number validate it by adding 6 (0110). After addition of 6, the carry has to be end rounded.

### Case 2: Valid BCD

After addition, if the result is valid BCD, take the 9's complement of result once again & put (-)minus sign before it.

Ex:

①

$$\begin{array}{r}
 8 \rightarrow 100.0 \\
 -4 \xrightarrow{\text{q's of 4}} 010.1 \\
 \hline
 4 \\
 0100 + 60110 \\
 \hline
 10011 \\
 \downarrow \quad \downarrow \\
 + 11 \\
 \hline
 0100
 \end{array}$$

→ invalid BCD

$$\begin{array}{r}
 4 \rightarrow 0100 \\
 -8 \xrightarrow{\text{q's of 8}} 0001 \\
 \hline
 -4 \\
 0100 \\
 \hline
 0101
 \end{array}$$

→ valid BCD

q's of result → 0100

②

$$\begin{array}{r}
 9 \rightarrow 1001 \\
 -3 \xrightarrow{\text{q's of 3}} 0110 \\
 \hline
 6 \\
 0110 + 60110 \\
 \hline
 1010 \\
 \downarrow \quad \downarrow \\
 + 1 \\
 \hline
 0110
 \end{array}$$

→ invalid BCD

$$\begin{array}{r}
 8 \rightarrow 0011 \\
 -9 \xrightarrow{\text{q's of 9}} 0000 \\
 \hline
 -6 \\
 0011
 \end{array}$$

q's of result is -0110

\* 25 →

$$\begin{array}{r}
 13 \\
 -12 \\
 \hline
 0001\ 0010
 \end{array}$$

$$\begin{array}{r}
 9's \text{ of } 13 \\
 \xrightarrow{\quad} 0010\ 0101 \\
 (+) 1000\ 0110 \\
 \hline
 1010\ 1011
 \end{array}$$

$$\begin{array}{r}
 +6 \\
 \hline
 0110 \\
 \hline
 111 \\
 \hline
 1011\ 0001
 \end{array}$$

$$\begin{array}{r}
 +9\ 0110 \\
 \hline
 10001000 \\
 \hline
 +1 \\
 \hline
 00010010
 \end{array}$$

$$\begin{array}{r}
 99 \\
 -13 \\
 \hline
 86
 \end{array}$$

(27)

$$\begin{array}{r}
 99 \\
 -87 \\
 \hline
 12
 \end{array}$$

$$\begin{array}{r}
 13 \\
 -25 \\
 \hline
 -12
 \end{array}
 \rightarrow$$

$$\begin{array}{r}
 0001\ 0011\ 0001 \\
 0011\ 0101\ 0111 \\
 +0111\ 0100\ 0100 \\
 \hline
 10000111
 \end{array}$$

9's of result

$$\begin{array}{r}
 -0001\ 0010
 \end{array}$$

\* 257 →

$$\begin{array}{r}
 143 \\
 \hline
 114
 \end{array}$$

$$\begin{array}{r}
 0010\ 0101\ 0111 \\
 (+) 0001\ 0100\ 0011 \\
 \hline
 1010\ 1011\ 1010
 \end{array}$$

$$\begin{array}{r}
 +6 \\
 \hline
 1010\ 1011\ 0011
 \end{array}$$

$$\begin{array}{r}
 +6 \\
 \hline
 1011\ 0001\ 0011
 \end{array}$$

$$\begin{array}{r}
 +9\ 0110 \\
 \hline
 100010001010
 \end{array}$$

$$\begin{array}{r}
 +1 \\
 \hline
 000100010100
 \end{array}$$

$$\begin{array}{r}
 999 \\
 -143 \\
 \hline
 856
 \end{array}$$

$$\begin{array}{r}
 143 \rightarrow 0001 \quad 0100 \quad 0011 \\
 -257 \rightarrow 0111 \quad 0100 \quad 0010 \\
 \hline
 -114 \quad + \quad 111 \quad | \quad 1000 \quad 1000 \quad 0101 \\
 \hline
 1000 \quad | \quad 1000 \quad 0101
 \end{array}$$

(28) Bim  
Date 9/11/19

$$\begin{array}{r}
 999 \\
 257 \\
 \hline
 742
 \end{array}$$
  

$$\begin{array}{r}
 999 \\
 885 \\
 \hline
 114
 \end{array}$$

q's of 885 is -0001 0001 0100

### Gray Code:

Gray Code is a non weighted code, derived from binary code. In gray code there is only one bit change from one number to the immediate next number.

Q) Generate 4-bit gray code from single bit gray code.

Ans

$$\begin{array}{r}
 Q = 0 \quad \overline{Q} = 1 \\
 \hline
 \overline{Q} = 1 \quad Q = 0
 \end{array}$$

0 - 0	0 - 0 0	0 - 0 0 0
1 - 1	1 - 0 1	1 - 0 0 1
	<hr/>	<hr/>
2 - 1 0	2 - 0 1 1	2 - 0 0 1 1
	<hr/>	<hr/>
3 - 1 0	3 - 0 1 0	3 - 0 0 1 0
	<hr/>	<hr/>
4 - 1 1 0	4 - 0 1 1 0	
5 - 1 1 1	5 - 0 1 1 1	
6 - 1 0 1	6 - 0 1 0 1	
7 - 1 0 0	7 - 0 1 0 0	
	<hr/>	<hr/>
8 - 1 1 0 0		
9 - 1 1 0 1		
10 - 1 1 1 1		
11 - 1 1 1 0		
12 - 1 0 1 0		
13 - 1 0 1 1		
14 - 1 0 0 1		
15 - 1 0 0 0		

## Binary to Gray Code

29:

To convert given 4-bit binary to its equivalent 4-bit gray code, the following formula is used.

Let the given 4-bit binary number is  $(B_3 B_2 B_1 B_0)$  and its equivalent 4-bit gray code is  $(G_3 G_2 G_1 G_0)$ . Then

$$G_3 = B_3$$

$$G_2 = B_3 \oplus B_2$$

$$G_1 = B_2 \oplus B_1$$

$$G_0 = B_1 \oplus B_0$$

EX-OR truth table

A	B	y
0	0	0
0	1	1
1	0	1
1	1	0

→ Convert  $(111)_B = (?)_G$  →  $(101110)_B = (?)_G$

Ans,

$$\begin{array}{cccc} B_3 & \oplus & B_2 & \oplus \\ \downarrow & & \downarrow & \\ B_1 & & B_0 & \\ \downarrow & & \downarrow & \\ (1 & 0 & 0 & 0) & G \end{array}$$

$$\begin{array}{cccccc} 1 & 0 & 1 & 1 & 1 & 0 \\ \downarrow & \downarrow & \downarrow & \downarrow & \downarrow & \\ 1 & 1 & 1 & 0 & 0 & 1 \end{array}$$

$$(111001)_G$$

→  $(0111)_B = (?)_G$

Ans,

$$\begin{array}{cccc} 0 & 1 & 1 & 1 \\ \downarrow & \downarrow & \downarrow & \downarrow \\ 0 & 1 & 0 & 0 \end{array}$$

→  $(1001)_B = (?)_G$

$$\begin{array}{cccc} 1 & 0 & 0 & 1 \\ \downarrow & \downarrow & \downarrow & \downarrow \\ 1 & 1 & 0 & 1 \end{array}$$

→  $(1110)_B = (?)_G$

$$\begin{array}{cccc} 1 & 1 & 1 & 0 \\ \downarrow & \downarrow & \downarrow & \downarrow \\ 1 & 0 & 0 & 1 \end{array}$$

## Gray code to Binary code Conversion:

Let the given 4-bit gray code is  $(G_3 G_2 G_1 G_0)$  and its equivalent binary is  $(B_3 B_2 B_1 B_0)$ . Then

$$\mathcal{B}_3 = \mathcal{G}_3$$


$$B_2 = G_3 \oplus B_3, \quad B_3 \oplus G_2.$$

$$B_{\cdot 1} = B_{\cdot 2} \oplus G_1$$

$$B_0 = B_1 \oplus G_0$$

→ convert.
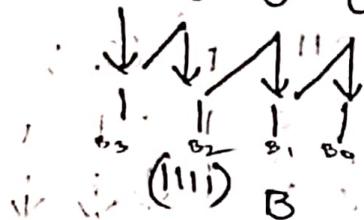
$$1^{G_3} \cdot 0^{G_2} \cdot 0^{G_1} \cdot 0^{G_0} G = (?) B$$



$$\rightarrow (1011)_B = (?)_{10}$$

1 0 1 1  
↓ ↗ ↗ ↗  
1 1 0 1

(1101)<sub>3</sub>

$$\rightarrow (011)_6 = (?)_3$$

(0 101)<sub>B</sub>

Excess-3 code

Excess-3 code is a non weighted code delivered from BCD code for every BCD number, 3 is added to get excess 3-code

BCD	Excess-3
0 - 0000	$\rightarrow 0011$
1 - 0001	$\rightarrow 0100$
2 - 0010	$\rightarrow 0101$
3 - 0011	$\rightarrow 0110$
4 - 0100	$\rightarrow 0111$
5 - 0101	$\rightarrow 1000$
6 - 0110	$\rightarrow 1001$
7 - 0111	$\rightarrow 1010$
8 - 1000	$\rightarrow 1011$
9 - 1001	$\rightarrow 1100$

Excess-3 addition:

In excess-3 addition after adding two excess-3 numbers there are two cases

Case(i): No carry

If there is no carry after excess-3 addition subtract (0011) 3 from the result to get final result.

Case(ii): Carry generated

After excess-3 addition if carry generated add 3 (0011) to both sum & carry.

Ex:

$$\begin{array}{r}
 3 \rightarrow 0110 \\
 (+) 4 \rightarrow (+) 0111 \\
 \hline
 7 \quad 1010 \\
 (1010) \quad 0011 \text{ (sub-3)} \\
 \hline
 1010
 \end{array}$$

(32)

$$\begin{array}{r}
 2 \rightarrow 0101 \\
 + 3 \rightarrow 0110 \\
 \hline
 85 \quad 1011 \\
 1000 \quad 0011 \text{ (Sub 3)} \\
 \hline
 1000
 \end{array}$$

$$\begin{array}{r}
 6 \rightarrow 1001 \\
 + 4 \rightarrow 1010 \\
 \hline
 13 \quad 0001\ 0011 \\
 0011\ 0011 \text{ Add 3} \\
 \hline
 0100\ 0110 \\
 \hline
 3
 \end{array}$$

$$\begin{array}{r}
 13 \rightarrow 0100\ 0110 \\
 + 12 \rightarrow 0100\ 0101 \\
 \hline
 25 \quad 1000\ 1011 \\
 \hline
 0101\ 1000 \\
 \hline
 2 \quad 5 \\
 - 0011 \text{ Sub(3)} \\
 \hline
 1000\ 1000
 \end{array}$$

$$\begin{array}{r}
 \text{Sub3} \\
 0011 \\
 \hline
 0101\ 1000 \\
 \hline
 2 \quad 5
 \end{array}$$

$$\begin{array}{r}
 38 \rightarrow 0110\ 1011 \\
 + 25 \rightarrow 0101\ 1000 \\
 \hline
 63 \quad 1100\ 0011 \\
 1001\ 0110 \\
 \hline
 0011\ 0011 \text{ Sub 3} \\
 \hline
 1001\ 0110
 \end{array}$$

$$\begin{array}{r}
 45 \rightarrow 0111\ 1000 \\
 + 36 \rightarrow 0110\ 1001 \\
 \hline
 81 \quad 1110\ 0001 \\
 1011\ 0100 \\
 \hline
 8 \quad 1 \\
 0011 \text{ Add 3} \\
 \hline
 1110\ 0100
 \end{array}$$

Sub3 0011

$$\begin{array}{r}
 1011\ 0100 \text{ ②} \\
 \hline
 193 \rightarrow 01100\ 0110 \\
 + 48 \rightarrow 01111\ 1011 \\
 \hline
 141 \quad 0001\ 0100 \\
 0100\ 0111\ 0100 \\
 \hline
 0100\ 0111\ 0100 \text{ Add(3)}
 \end{array}$$

## excess-3 Subtraction

(33)

In excess-3 subtraction if  $A-B$  is the required operation then take the  $q^1$ 's complement of  $B$  and add it to  $A$ . After addition there are two cases..

Case 1: Carry generated.

After addition if carry generated, end-around the carry and add to the sum to get the final answer.

Case 2: Carry not generated.

After addition if carry is not generated subtract 3 from the sum and once again take the  $q^1$ 's complement of the result and put (-) sign before the result.

\* Excess-3 is a selfcomplement code, because  $q^1$ 's complement of  $q^1$ 's complement is same.

Ex:

$$\begin{array}{r} 6 \rightarrow 1001 \\ - 3 \xrightarrow{\text{q's compl}} 1001 \\ \hline 3 & 10010 \\ 0110 & \boxed{+} \quad \text{(end-around)} \\ \hline 00110 \end{array}$$

$$\begin{array}{r} 00110 \\ + 0011 \\ \hline 0110 \end{array} \text{ Add } 3(0011)$$

$$\begin{array}{r} 3 \rightarrow 0110 \\ - 6 \xrightarrow{\text{q's compl}} 0110 \\ \hline -3 & 1100 \\ - 0110 & \hline 0011 \text{ Sub } 3(0011) \\ \hline \text{q's compl result} & 1001 \\ \hline - 0110 & \end{array}$$

$$\begin{array}{r} *5 \\ -4 \xrightarrow{\text{q's of 4}} \\ \hline 1 \end{array}$$

$\xrightarrow{(+)} 1 \quad 0 \quad 0 \quad 0 \quad 0 \quad 9$   
 $\hline 1 \quad 0 \quad 0 \quad 0 \quad 0 \quad 5$

$$\begin{array}{r} 0100 \\ \hline 0 \quad 0 \quad 0 \quad 1 \\ 0 \quad 0 \quad 1 \quad 1 \xrightarrow{\text{Add 3(0011)}} \\ \hline 0 \quad 1 \quad 0 \quad 0 \end{array}$$

$$\begin{array}{r} 4 \rightarrow 0 \quad 1 \quad 1 \quad 1 \quad 9 \\ -5 \rightarrow 0 \quad 1 \quad 1 \quad 1 \quad 4 \\ \hline -1 \quad 0 \quad 1 \quad 1 \quad 4 \\ \downarrow 0100 \quad 0 \quad 0 \quad 1 \quad 1 \xrightarrow{\text{Sub. 3(0011)}} \\ \hline 1 \quad 0 \quad 1 \quad 1 \\ \xrightarrow{\text{q's of 4}} 0 \quad 1 \quad 0 \quad 0 \end{array}$$

$$\begin{array}{r} * \quad 2 \quad 6 \rightarrow 0101 \quad 1001 \rightarrow 0101 \quad 100 \\ -1 \quad 4 \xrightarrow{\text{q's}} 0100 \quad 0111 \xrightarrow{\text{1's comp}} 1011 \quad 1000 \\ \hline 1 \quad 2 \quad 0001 \quad 0001 \quad 0001 \\ \downarrow 0100 \quad 0101 \quad \hline 0 \quad 0 \quad 0 \quad 1 \quad 0 \quad 0 \quad 1 \end{array}$$

$$\begin{array}{r} * \quad 1 \quad 4 \rightarrow 0100 \quad 0111 \\ -2 \quad 6 \xrightarrow{\text{q's}} 1010 \quad 0110 \\ \hline -12 \quad 1110 \quad 1101 \\ \hline 0011 \xrightarrow{\text{(Sub 3)}} 0100 \quad 0101 \\ \hline 1 \quad 1 \quad 1 \quad 0 \quad 1 \quad 0 \\ \hline 0 \quad 0 \quad 1 \quad 1 \\ \hline 1 \quad 0 \quad 1 \quad 1 \quad 0 \quad 1 \quad 0 \end{array}$$

$$\xrightarrow{\text{q's of result}} 0100 \quad 0101 \\ \hline 1 \quad 2$$

$$\begin{array}{r}
 255 \rightarrow 0101\ 1000\ 1000 \rightarrow 0101\ 1000\ 1000 \\
 (-) 163 \rightarrow 0100\ 1001\ 0110 \xrightarrow{(+)} 1011\ 0110\ 1001 \\
 \hline
 092 \qquad \qquad \qquad 100001110001
 \end{array}$$

$$\begin{array}{r}
 0011 \ 1100 \ 0101 \\
 + \underline{\quad\quad\quad} \\
 \hline
 0000 \ 1111 \ 0010
 \end{array}$$

Add3      001'1  
 (+)      111  
 00100101

$$\begin{array}{r}
 \text{(Add 3)} \quad 0011 \\
 & (-) \quad 0011 \\
 \hline
 0011 & 1000 & 010 \\
 & \overline{9} & \overline{2}
 \end{array}$$

$$\begin{array}{r}
 \rightarrow 163 \rightarrow 0100 & 1001 & 0110 \\
 (-) 255 \xrightarrow{15} \begin{array}{c} (+) \\ \hline -092 \end{array} & 1010 & 0111 & 0111 \\
 & \hline 1111 & 0000 & 1101 \\
 \text{(G)} \begin{array}{r} 0011 + 0011 \end{array} \begin{array}{c} (0) \\ \hline 1100 \end{array} & \begin{array}{c} 11 \\ 11 \\ \hline 0011 \end{array} & \begin{array}{c} 0011 \\ 0011 \\ \hline 1010 \end{array}
 \end{array}$$

isobsexual

$$\text{exult} \begin{pmatrix} -0.011 & 11.00 & 0.101 \end{pmatrix},$$

$$\begin{array}{r}
 * \quad \begin{array}{r} 2 \\ 3 \end{array} \quad \begin{array}{r} 17 \\ 8815 \end{array} \rightarrow 0110 \quad 1011 \quad 1000 \quad 999 \\
 - \quad \begin{array}{r} 1 \\ 9 \end{array} \quad \begin{array}{r} 6 \end{array} \rightarrow \begin{array}{r} 1011 \\ (A) \\ 1 \end{array} \quad \begin{array}{r} 0011 \\ 11 \end{array} \quad \begin{array}{r} 0110 \\ 1110 \end{array} \quad \begin{array}{r} 1 \\ 110 \end{array} \quad \begin{array}{r} 196 \\ 803 \end{array} \\
 \hline
 \begin{array}{r} 1 \\ 8 \end{array} \quad \begin{array}{r} 9 \end{array} \quad \begin{array}{r} 10001 \\ \hline 1110 \end{array} \quad \begin{array}{r} \rightarrow 1 \end{array}
 \end{array}$$

$$\begin{array}{r}
 0100 \quad 1011 \quad 1100 \\
 \hline
 & 000 & 110 & 1020^{\circ} & 111 & @1 \\
 (+) 0 & 011 & (-) 0 & 011 & (-) 0 & 11 \text{ Add. 3} \\
 \hline
 & 11 & & & & \\
 & 0100 & 1011 & 1100 & & \\
 \hline
 & & & & 9 &
 \end{array}$$

(36)

$$\begin{array}{r}
 196 \rightarrow .0100 \quad 1100 \quad 1001 \\
 -385 \\
 \hline
 -189 \\
 01001011 \\
 \hline
 1100 \\
 (-)0011 \quad (-)01011 \quad (-)001 \\
 \hline
 .1011 \quad 0100 \quad 0011 \\
 \hline
 0112 \quad (0100 \quad 1011 \quad 1100) \\
 \hline
 1 \quad 8 \quad 9
 \end{array}$$

↓

q's of result:

## Signed Binary numbers

(37)

In Signed binary numbers, one sign bit is allocated for representation of +ve numbers and -ve numbers. For +ve numbers sign bit is 0. For -ve numbers the sign bit is 1.

For Ex:

sign bit
0 0001 = +1
1 0001 = -1

- \* The signed binary numbers can be represented in three ways.

(1) Sign magnitude representation.

(2) 1's complement "

(3) 2's complement "

Note:

\*\*\* In all three representations, +ve numbers are having unique representation, where as -ve numbers having different representations.

Ex:-

+5	$\underline{-5}$
Sign magnitude 0 0000101	1 0000101
1's complement 0 0000101	1 1111010
2's complement 0 0000101	1 1111011

Ex:- using 2's Complement

$$= +7 = 00000111$$

$$+5 = 00000101$$

$$-5 = 11111011$$

$$-7 = 11111001$$

$$+2 = 00000010$$

$$-2 = 11111110$$

$$+12 = 00001100$$

$$-12 = 11110100$$

$$+7 \rightarrow 00000111$$

$$+5 \rightarrow 00000101$$

$$\begin{array}{r} + \\ +5 \\ \hline +12 \end{array} \quad 00001100$$

$$+7 \rightarrow 00000111$$

$$-5 \rightarrow 11111011$$

$$\begin{array}{r} (+) \\ +2 \\ \hline +12 \end{array} \quad 00000010$$

$$-7 \rightarrow 11111001$$

$$+5 \rightarrow 00000101$$

$$\begin{array}{r} (+) \\ -2 \\ \hline +12 \end{array} \quad 11111100$$

$$\begin{array}{r}
 \begin{array}{c}
 \begin{array}{c}
 -7 \\
 -5 \\
 \hline
 -12
 \end{array} & \rightarrow & 11111001
 \end{array} \\
 \begin{array}{c}
 \begin{array}{c}
 (+) \\
 \hline
 1
 \end{array} & \rightarrow & 11111011
 \end{array} \\
 \hline
 \begin{array}{c}
 \text{discard} \\
 \text{*}
 \end{array} & \text{---} & 11110100
 \end{array}$$

(30)

some above suction using its original

\* Using 1's complement.

- +7 → 00000111
- +5 → 00000101
- 7 → 11111000
- 5 → 11111010
- +2 → 00000010
- 2 ⇒ 11111101
- +12 → 00001100
- 12 → 11110011

$$\begin{array}{r}
 +7 \rightarrow 000000\ 111 \\
 +5 \rightarrow 000000\ 101 \\
 \hline
 +12 \quad 00001100
 \end{array}$$

$+7 \rightarrow 000000111$   
 $-5 \rightarrow \begin{array}{r} (-) \\ | \\ 11111010 \end{array}$   
 $+2 \rightarrow \begin{array}{r} 100000000 \\ \hline 100000000 \end{array}$   
 $\hline$   
 $0000000010$

$$\begin{array}{r}
 -4 \\
 +5 \\
 \hline
 -2
 \end{array}
 \rightarrow
 \begin{array}{r}
 11111000 \\
 \xrightarrow{(+)} 00000101 \\
 \hline
 11111101
 \end{array}$$

$\begin{array}{r} -7 \\ -5 \\ -12 \end{array}$	$\rightarrow$	$\begin{array}{ccccccc}   &   &   &   &   & 0 & 0 \\   &   &   &   &   & 0 & 1 \\   &   &   &   &   & 0 & 0 \end{array}$
		$\begin{array}{cccccc}   &   &   &   &   & 0 & 0 & 1 & 0 \\   &   &   &   &   & 0 & 1 & 0 & 0 \end{array}$
		$\rightarrow +1$

## ERROR DETECTING CODES:

(39)

Parity bit is an extra bit which is added to the original bit. Parity is of two types

1. Even Parity.
2. Odd Parity.

Even parity: For even parity the no. of 1's in the information should be even including parity bit.

Odd Parity: For odd parity the no. of 1's in information is odd including parity bit.

Ex: Generate Even and Odd Parity for given message

Message → 0 0 1 0 1 1 0

0 0 1 0 1 1 0 1 → even parity  
0 0 1 0 1 1 0 0 → odd parity.

Block Parity: In block parity the parity is taken for both rows & columns for group of messages.

Ex:

Even parity

0	0	1	0	1	0	0
0	0	1	0	1	0	0
0	0	1	0	1	1	
1	0	1	0	1	0	1
<hr/>						1
<hr/>						1 0 0, 0 0 1

+

## Error detection & correction codes

(40)

In the error detection & correction

Codes Hamming code is the best example  
By using hamming code, error can be detected and it can be corrected.

Hamming code generation:

To generate hamming code for  $m$  no. of message bits the following formula is used

$$2^P \geq m + p + 1$$

where  $P = \text{no. of parity bits}$

Generate Hamming code for 1011.

Ans:

$$\begin{matrix} 1 & 0 & 1 & 1 \\ m_1 & m_2 & m_3 & m_4 \\ m = 4 \end{matrix}$$

$$2^P \geq m + p + 1$$

$$2^P \geq 4 + p + 1 \quad [\because m = 4]$$

; if  $p = 0$

$$2^0 \geq 4 + 0 + 1$$

$$1 \geq 5$$

; if  $p = 3$

$$2^3 \geq 4 + 3 + 1$$

$$8 \geq 8$$

$$m = 4$$

$$p = 3$$

$$\text{Total} = \underline{7}$$

	1	2	3	4	5	6	7	(4)
$P_1$	$P_2$	$m_1$	$P_3$	$m_2$	$m_3$	$m_4$	0 0 1 - 1	
1, 3, 5, 7 0			1	0	1	1	0 1 0 - 2	
2, 3, 6, 7			1	0	1		0 1 1 - 3	
4, 5, 6, 7			1	0	1		1 0 0 - 4	
							1 0 1 - 5	
							1 1 0 - 6	
							1 1 1 - 7	

(011 0011)

	1	2	3	4	5	6	7	
$P_1$	$P_2$	$m_1$	$P_3$	$m_2$	$m_3$	$m_4$	0 0 1 - 1	
1, 3, 5, 7 0			0	0	1	0	0 0 1 0 - 2	
2, 3, 6, 7			1	0	0	0	1 0 0 1 - 2	
4, 5, 6, 7			1	0	1	0	1 0 1 0 - 1	
			1	0	1	0	1 1 1 0	

(010 1010)

	1	2	3	4	5	6	7	
$P_1$	$P_2$	$m_1$	$P_3$	$m_2$	$m_3$	$m_4$	0 0 1 - 1	
1, 3, 5, 7 0			1	0	0	1	0 0 1 0 - 2	
2, 3, 6, 7			0	1	0	1	1 0 0 1 - 2	
4, 5, 6, 7			1	0	0	1	1 0 1 0 - 1	
			1	0	0	1	1 1 1 0	

(0011 001)

10101 1 2 3 4 5 6 7 (15)

P<sub>1</sub> P<sub>2</sub> m<sub>1</sub> P<sub>3</sub> m<sub>2</sub> m<sub>3</sub> m<sub>4</sub>

1 1 0 1 0

4,5,6,7 1 1 0 0

2,3,6,7 1 0 1 1 0

4,5,6,7 1 0 1 0

(101010)

11101 1 2 3 4 5,6,7

P<sub>1</sub> P<sub>2</sub> m<sub>1</sub> P<sub>3</sub> m<sub>2</sub> m<sub>3</sub> m<sub>4</sub>

1 1 1 0

1,3,5,7 0 1 1 0

2,3,6,7 0 1 1 0

4,5,6,7 0 1 1 0

(0010110)

Error detection and correction:

→ original: 0101010  $\xrightarrow{\text{err}}$  0100010

1 2 3 4 5 6 7

0 1 0 0 0 1 0

C<sub>1</sub> → 1,3,5,7 0 0 0 0 0 → 0

C<sub>2</sub> → 2,3,6,7 1 0 0 0 1 → 0

C<sub>3</sub> → 4,5,6,7 0 0 1 0 → 1

C<sub>3</sub> C<sub>2</sub> C<sub>1</sub>

1 0 0 → 4

∴ There is an error in 4<sup>th</sup> position.  
the correct information is 0101010

$0101010 \xrightarrow{\text{odd}}$  0101000

(4.3)

1	2	3	4	5	6	7
0	1	0	1	0	0	0

$c_1 \rightarrow 1, 3, 5, 7 \rightarrow 0$

$c_2 \rightarrow 2, 4, 6, 8 \rightarrow 1$

$c_3 \rightarrow 4, 5, 6, 7 \rightarrow 1$

$c_3 \ c_2 \ c_1$

1 1 0  $\rightarrow 5$

∴ There is an error in 6<sup>th</sup> position.

The correct information is 0101010

$\Rightarrow 0101010 \xrightarrow{\text{odd}}$  0001010

1	2	3	4	5	6	7
0	0	0	1	0	1	0

$c_1 \rightarrow 1, 3, 5, 7 \rightarrow 0$

$c_2 \rightarrow 2, 3, 6, 7 \rightarrow 0$

$c_3 \rightarrow 4, 5, 1, 7 \rightarrow 1$

$c_3 \ c_2 \ c_1$

0 1 0  $\rightarrow 2$

∴ There is an error in 2<sup>nd</sup> position, The  
correct information is 0101010.

$\Rightarrow 0101010$

1	2	3	4	5	6	7
0	1	0	1	0	1	0

$c_1 \rightarrow 1, 3, 5, 7 \rightarrow 0$

$c_2 \rightarrow 2, 3, 6, 7 \rightarrow 1$

$c_3 \rightarrow 4, 5, 1, 7 \rightarrow 0$

$c_3 \ c_2 \ c_1$

0 0 0

No error.

# Logic Gates

(44)

(1) Basic gates  $\rightarrow$  AND, OR, NOT

(2) Universal gates  $\rightarrow$  NAND, NOR

(3) Special gates  $\rightarrow$  EX-OR, EX-NOR

## AND Gate



A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

$$Y = A \cdot B$$

$$= AB$$

## OR Gate



$$Y = A + B$$

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1

## NOT Gate




$$Y = \bar{A} = A'$$

A	Y
0	1
1	0

## NAND Gate

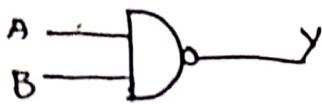4.5

NAND Gate is AND gate followed by NOT Gate



$$Y = \overline{A \cdot B}$$


$$= \overline{AB}$$

A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

Any boolean function can be purely implemented with this two gates (NAND, NOR)

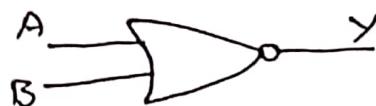
## NOR Gate

NOR Gate is OR Gate followed by NOT gate.



$$Y = \overline{(A+B)}$$

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0

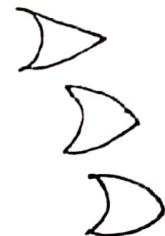

## Special gates

→ EX-OR: (Inequality gate)



$$Y = A \oplus B$$

$$= A\bar{B} + \bar{A}B$$

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0

Important  
Property:  $A \oplus 0 = A$   
 $A \oplus 1 = \bar{A}$

## Ex-NOR (equality gate)

A+G



A	B	Y
0	0	1
0	1	0
1	0	0
1	1	1

$$\begin{aligned} Y &= A \oplus B \\ &= AB + \overline{AB} \\ &= AB + \overline{A}\overline{B} \end{aligned}$$



To learn about other gates and their applications

# Logic Gates:

44

- (1) Basic gates  $\rightarrow$  AND, OR, NOT
- (2) Universal gates  $\rightarrow$  NAND, NOR
- (3) Special gates  $\rightarrow$  EX-OR, EX-NOR

## AND Gate

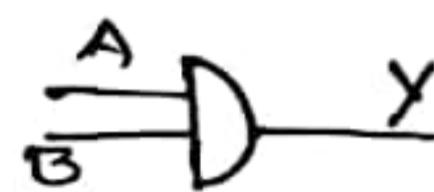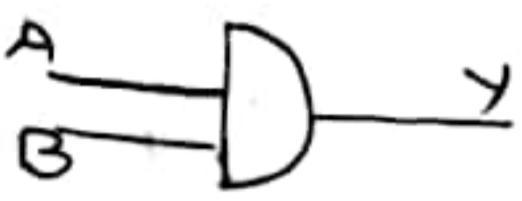

A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

$$Y = A \cdot B \\ = AB$$


## OR Gate



$$Y = A + B$$

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1

## NOT Gate

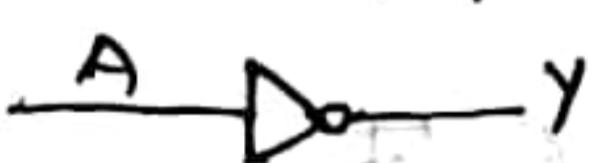


$$Y = \overline{A} = A'$$

A	Y
0	1
1	0

## NAND Gate :

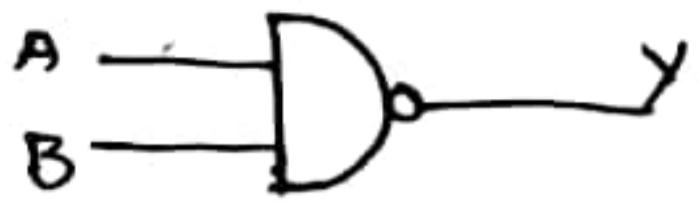(45)

NAND gate is AND gate followed by NOT gate



A	B	y
0	0	1
0	1	1
1	0	1
1	1	0

$$y = \overline{A \cdot B}$$

$$= \overline{AB}$$

Any boolean function can be purely implemented with these two gates (NAND, NOR)

## NOR Gate :

NOR gate is OR gate followed by NOT gate.



A	B	y
0	0	1
0	1	0
1	0	0
1	1	0

$$y = \overline{(A+B)}$$



## Special gates:

→ Ex-OR: (Inequality gate)



A	B	y
0	0	0
0	1	1
1	0	1
1	1	0

$$Y = A \oplus B$$

$$= A\bar{B} + \bar{A}B$$

Important:  
Property:  $A \oplus 0 = A$   
 $A \oplus 1 = \bar{A}$

## Ex-NOR (equality gate)

46



A	B	y
0	0	1
0	1	0
1	0	0
1	1	1

$$\begin{aligned}
 y &= A \oplus B \\
 &= AB + \overline{A}\overline{B} \\
 &= AB + \overline{A}\overline{B}
 \end{aligned}$$

To find complemented output of the above

A	B	C
0	0	0
0	1	1
1	0	1
1	1	0

Stop today

See you tomorrow

## MINIMIZATION TECHNIQUES

- Binary Logic is used in all of today's digital computers and devices, the cost of the circuits that implement it is an important factor.
- Finding simpler and cheaper, but equivalent, realizations of a circuit must be good. To reducing the overall cost of the design.
- 

Boolean theorems :-1. Complementation laws :-

Complement means, to change 0's to 1's and 1's to 0's.

$$\text{Law 1} : \overline{0} = 1$$

$$\text{Law 2} : \overline{1} = 0$$

$$\text{Law 3} : \overline{\overline{A}} = A \rightarrow \overline{A} = \overline{1}$$

$$\text{Law 4} : \overline{A} = \overline{1} \rightarrow A = 0$$

$$\text{Law 5} : \overline{\overline{A}} = A \quad (\text{Double complementation does not change the function}).$$

2. AND laws :-

$$\text{Law 1} : A \cdot 0 = 0$$

$$\text{Law 2} : A \cdot 1 = A$$

$$\text{Law 3} : A \cdot A = A$$

$$\text{Law 4} : A \cdot \overline{A} = 0$$

3. OR laws :-

$$\text{Law 1} : A + 1 = 1$$



$$\text{Law 2} : A + 0 = A$$

$$\text{Law 3} : A + A = A$$

$$\text{Law 4} : A + \overline{A} = 1$$

#### 4. Commutative laws:-



Law 1 :-  $A+B = B+A$

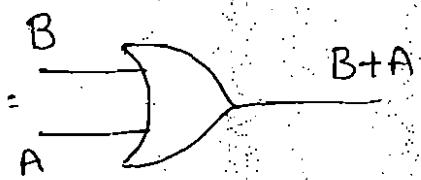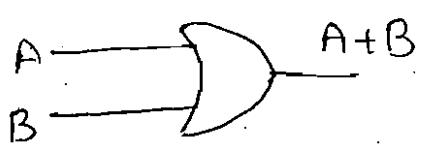

A	B	$A+B$
0	0	0
0	1	1
1	0	1
1	1	1

A	B	$B+A$
0	0	0
0	1	1
1	0	1
1	1	1

Law 2 :-  $A \cdot B = B \cdot A$

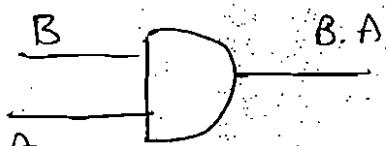
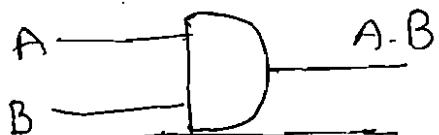


A	B	$A \cdot B$
0	0	0
0	1	0
1	0	0
1	1	1

A	B	$B \cdot A$
0	0	0
0	1	0
1	0	0
1	1	1

#### 5. Associate laws:-



Law 1:  $(A+B)+C = A+(B+C)$

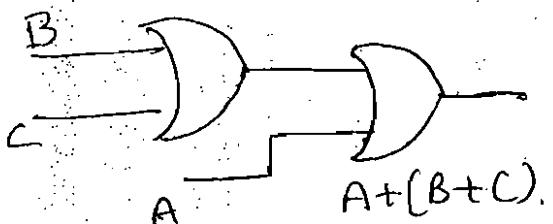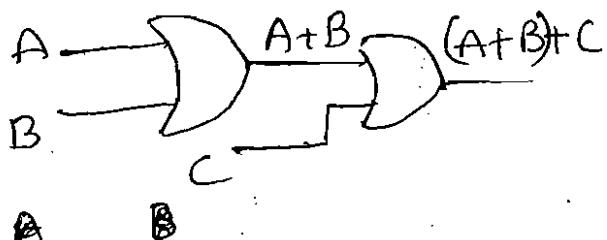

A	B	C	$A+B$	$(A+B)+C$
0	0	0	0	0
0	0	1	0	1
0	1	0	1	1
0	1	1	1	1
1	0	0	1	1
1	0	1	1	1
1	1	0	1	1
1	1	1	1	1

A	B	C	$B+C$	$A+(B+C)$
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	1	1
1	0	0	0	0
1	0	1	1	1
1	1	0	1	1
1	1	1	1	1

Law 2:  $(A \cdot B)C = A(B \cdot C)$ .

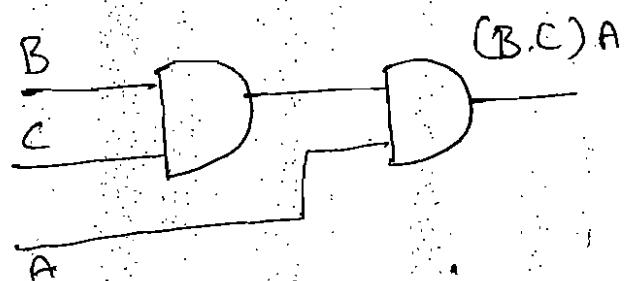
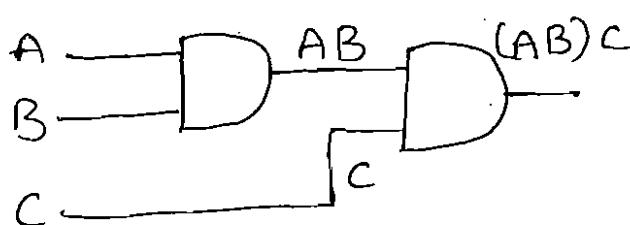


A	B	C	$AB$	$(AB)C$
0	0	0	0	0
0	0	1	0	0
0	1	0	0	0
0	1	1	0	0
1	0	0	0	0
1	0	1	0	0
1	1	0	1	0
1	1	1	1	1

A	B	C	$B \cdot C$	$A(B \cdot C)$
0	0	0	0	0
0	0	1	0	0
0	1	0	0	0
0	1	1	1	0
1	0	0	0	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

## 6. Distributive Laws:-



Law 1 :  $A(B+C) = AB+AC$

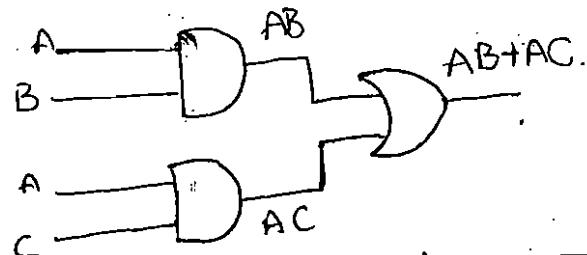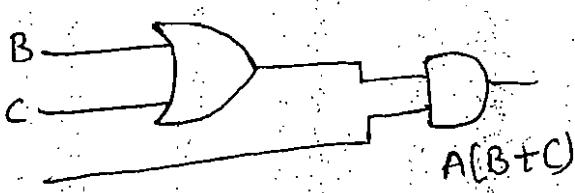

A	B	C	$(B+C)$	$A(B+C)$
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	1	0
1	0	0	0	0
1	0	1	1	1
1	1	0	1	1
1	1	1	1	1

A	B	C	AB	AC	$AB+AC$
0	0	0	0	0	0
0	0	1	0	0	0
0	1	0	0	0	0
0	1	1	0	0	0
1	0	0	0	0	0
1	0	1	0	1	1
1	1	0	1	0	1
1	1	1	1	1	1

Law 2 :  $A+BC = (A+B)(A+C)$

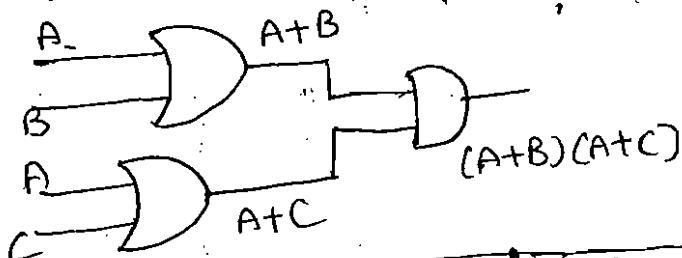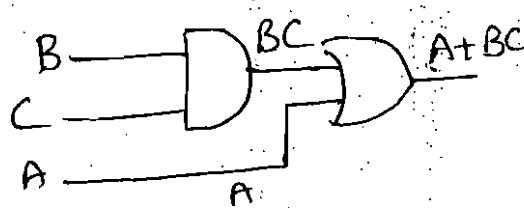


A	B	C	$BC$	$A+BC$
0	0	0	0	0
0	0	1	0	0
0	1	0	0	0
0	1	1	1	1
1	0	0	0	1
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

A	B	C	$A+B$	$A+C$	$(A+B)(A+C)$
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	1	0	0
0	1	1	1	1	1
1	0	0	1	1	1
1	0	1	1	1	1
1	1	0	1	1	1
1	1	1	1	1	1

## 7. Redundant Literal Rule :-


Law 1:  $A(\bar{A} + B) = AB$ .

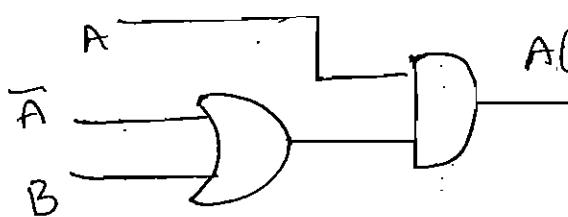

$$= A(\bar{A} + B)$$

$$= A \cdot \bar{A} + AB$$

$$= \underline{AB}$$

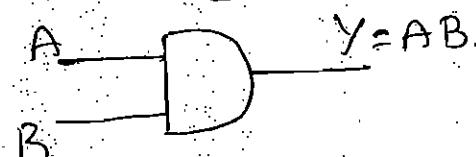

$$Y = AB$$

A	B	$\bar{A} + B$	$A(\bar{A} + B)$
0	0	1	0
0	1	1	0
1	0	0	0
1	1	1	1

A	B	$AB$
0	0	0
0	1	0
1	0	0
1	1	1

Law 2:  $A + \bar{A}B = A + B$ .

$$\begin{aligned} &= A + \bar{A}B \\ &= (A + \bar{A})(A + B) \\ &= (A + B) \end{aligned}$$

A	B	$\bar{A}B$	$A + \bar{A}B$
0	0	0	0
0	1	1	1
1	0	0	1
1	1	0	1

A	B	$A + B$
0	0	0
0	1	1
1	0	1
1	1	1

## 8. Idempotence Laws:-

Idempotence means the same value.

$$\text{Law 1: } A \cdot A = A$$

$$\text{if } A=0 \text{ then } 0 \cdot 0 = 0$$

$$\text{if } A=1 \text{ then } 1 \cdot 1 = 1$$


$$\text{Law 2: } A + A = A$$

$$\text{if } A=0 \text{ then } 0 + 0 = 0$$

$$\text{if } A=1 \text{ then } 1 + 1 = 1$$

## 9. Absorption Laws :-

$$\text{Law 1} = A + A \cdot B = A$$

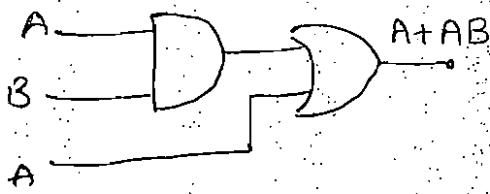

A	B	A · B	A + A · B
0	0	0	0
0	1	0	0
1	0	0	1
1	1	1	1


$$= A + A \cdot B$$

$$= A(1 + B) \quad \because 1 + B = 1$$

$$= A \cdot 1$$

$$= A.$$

$$\text{Law 2: } A(A + B) = A$$

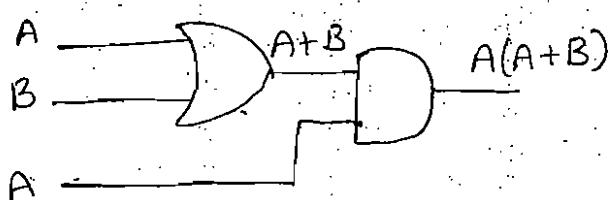

A	B	A + B	A(A + B)
0	0	0	0
0	1	1	0
1	0	1	1
1	1	1	1

$$= A \cdot A + A \cdot B$$

$$= A + A \cdot B$$

$$= A(1 + B)$$

$$= A.$$

$= A(A + \text{any term})$

$$= A$$

## 10. Consensus Theorem :-

$$\text{Theorem 1: } AB + \overline{A}C + BC = AB + \overline{A}C.$$

$$\text{L.H.S} \rightarrow AB + \overline{A}C + BC$$

$$= AB + \overline{A}C + BC (A + \overline{A})$$

$$= AB + \overline{A}C + ABC + \overline{A}BC$$

$$= AB(1 + C) + \overline{A}C(1 + B)$$

$$= AB(1) + \overline{A}C = AB + \overline{A}C.$$

$$AB + \overline{AC} + BCD = AB + \overline{AC}$$

$$\text{L.H.S} \rightarrow AB + \overline{AC} + BCD$$

$$AB + \overline{AC} + BCD(A + \overline{A})$$

$$AB + \overline{AC} + ABCD + \overline{ABC}D$$

$$AB(1 + CD) + \overline{AC}(1 + CD)$$

$$AB + \overline{AC}$$

$$\text{Theorem 2 : } (A+B)(\overline{A}+C)(B+C) = (A+B)(\overline{A}+C)$$

$$\text{L.H.S} : (A+B)(\overline{A}+C)(B+C)$$

$$(A\overline{A} + AC + \overline{A}B + BC)(B+C)$$

$$(AC + BC + \overline{A}B)(B+C)$$

$$ABC + BC + \overline{A}BC + AC + BC + \overline{A}B$$

$$= BC + AC + \overline{A}B(1 + C) + ABC$$

$$= BC + \overline{A}B + AC(1 + B)$$

$$= AC + BC + \overline{A}B$$

$$\text{R.H.S} = (A+B)(\overline{A}+C)$$

$$\therefore = A\cdot\overline{A} + AC + \overline{A}B + BC$$

$$= \overline{A}B + AC + BC$$

$$\rightarrow (A+B)(\overline{A}+C)(B+C+D) = (A+B)(\overline{A}+C)$$

If a sum of products comprises a term containing A and a term containing  $\overline{A}$ , and a third term containing the left out literals of the first two terms, then the third term is redundant.

$\rightarrow$  The function remains the same with or without the third term removed or retained.

## Transposition Theorem :-



Theorem :  $AB + \overline{A}C = (A+C)(\overline{A}+B)$

$$\begin{aligned}
 \text{R.H.S.} &= (A+C)(\overline{A}+B) \\
 &= A \cdot \overline{A} + AB + \overline{A}C + BC \\
 &= AB + \overline{A}C + BC \\
 &= AB + \overline{A}C + BC(A+\overline{A}) \\
 &= AB + \overline{A}C + ABC + \overline{A}BC \\
 &= AB(1+C) + \overline{A}C(1+B) \\
 &= AB + \overline{A}C
 \end{aligned}$$
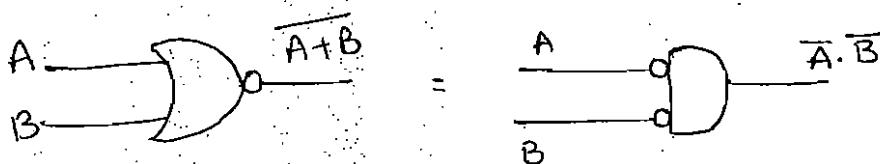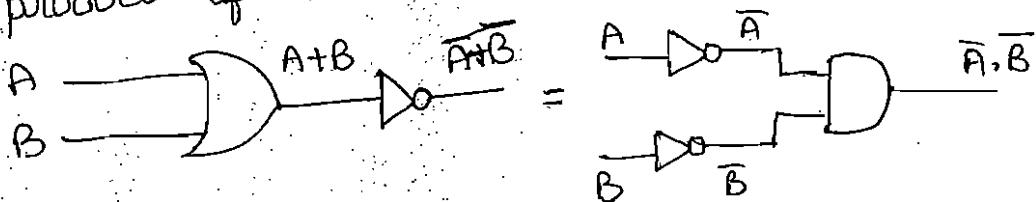
## Demorgan's Theorem :-

Law 1  $A+B = \overline{\overline{A} \cdot \overline{B}}$

The complement of a sum of variables is equal to the product of their individual complements.



A	B	$A+B$	$\overline{A+B}$
0	0	0	1
0	1	1	0
1	0	1	0
1	1	1	0

A	B	$\overline{A}$	$\overline{B}$	$\overline{A} \cdot \overline{B}$
0	0	1	1	1
0	1	1	0	0
1	0	0	1	0
1	1	0	0	0




$$\text{Similarly } \rightarrow A + B + C + D + E = \overline{\overline{A} \cdot \overline{B} \cdot \overline{C} \cdot \overline{D} \cdot \overline{E}}$$

$$\rightarrow \overline{\overline{AB} + \overline{CD} + \overline{ED}} = (\overline{AB})(\overline{CD})(\overline{ED})$$

$$= (A + \overline{B})(\overline{C} + D)(E + \overline{D})$$

$$\text{Law 2 } \overline{AB} = \overline{A} + \overline{B}$$

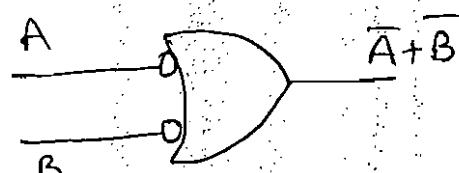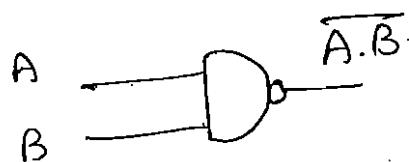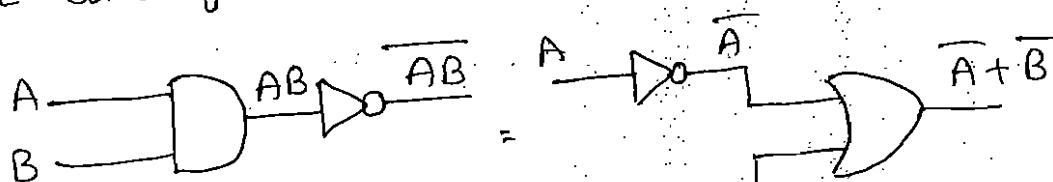The complement of the product of variables is equal to the sum of their individual complements.



A	B	A.B	A.B
0	0	0	1
0	1	0	1
1	0	0	1
1	1	1	0

A	B	A	B	A + B
0	0	1	1	1
0	1	1	0	1
1	0	0	1	1
1	1	0	0	0

### Duality:-

when changing from one logic system to another, '0' becomes '1' and '1' becomes '0'. An AND gate becomes an OR gate, and an OR gate becomes an AND gate. Given a Boolean identity, we can produce a dual identity by changing all '+' signs to '·' signs, all '·' signs to '+' signs. The variables are not complemented.

$$\rightarrow A \cdot (A \cdot B) = A \cdot B \rightarrow \overline{A + A} + B = A + B.$$

$$\rightarrow \overline{AB} + \overline{A} + AB = 0 \rightarrow \overline{A + B} \cdot \overline{A} \cdot (A + B) = 1$$

$$\rightarrow A + B = AB + \overline{A}B + A\overline{B} \rightarrow AB = (A + B)(\overline{A} + B)(A + \overline{B})$$

Reducing Boolean expressions by using Boolean theorems :-

$$* f = A[B + \bar{C}(\bar{A}B + \bar{A}\bar{C})]$$

$$f = A[B + \bar{C}((\bar{A}B)(\bar{A}\bar{C}))]$$

$$= A[B + \bar{C}(\bar{A} + \bar{B})(\bar{A} + \bar{C})]$$

$$= A[B + \bar{C}[(\bar{A} + \bar{B})(\bar{A} + \bar{C})]]$$

$$= A[B + \bar{C}[\bar{A}\bar{A} + \bar{A}\bar{C} + \bar{A}\bar{B} + \bar{B}\bar{C}]] \quad \bar{A}\cdot\bar{A} = 0$$

$$= A[B + \bar{C}[\bar{A} + \bar{A}\bar{C} + \bar{A}\bar{B} + \bar{B}\bar{C}]]$$

$$= A[B + \bar{C}[\bar{A} + \bar{A}\bar{C} + \underline{\bar{A}\bar{C}\bar{C}} + \underline{\bar{A}\bar{B}\bar{C}} + \underline{\bar{B}\bar{C}\bar{C}}]] \quad C\cdot\bar{C} = 0$$

$$= A[B + \bar{A}\bar{C} + \bar{A}\bar{B}\bar{C}]$$

$$= AB + A\bar{A}\bar{C} + A\bar{A}\bar{B}\bar{C} \quad A\cdot\bar{A} = 0.$$

$$= AB$$

$$* f = (\bar{A} + B)(\bar{B} + C) + (AB + C)$$

$$= \bar{A}\bar{B} + \bar{A}\bar{C} + B\bar{B} + BC + AB + C \quad B\cdot\bar{B} = 0$$

$$= \bar{A}\bar{B} + \bar{A}\bar{C} + BC + AB + C$$

$$= C(1 + \bar{A} + B) + AB + \bar{A}\bar{B}$$

$$= AB + \bar{A}\bar{B} + C$$

$$* f = (\bar{A} + B)(\bar{A}\bar{B}\bar{C}) + (\bar{A}\bar{C})$$

$$= (\bar{A}\cdot\bar{B})(\bar{A} + \bar{B} + \bar{C}) + A + \bar{C}$$

$$= \underline{\bar{A}\bar{A}} + \underline{\bar{A}\bar{B}} + \underline{\bar{A}\bar{C}} + \underline{\bar{A}\bar{B}} + \underline{B\bar{B}} + \underline{\bar{B}\bar{C}} + A + \bar{C}$$

$$= \bar{A} + \bar{A}\bar{B} + \bar{A}\bar{C} + \bar{B} + \bar{B}\bar{C} + A + \bar{C}$$

$$= \overline{A}(1 + \overline{B} + \overline{C}) + \overline{B}(1 + \overline{C}) + A + \overline{C}$$

$$= \overline{A} + \overline{B} + A + \overline{C} = A + \overline{A} + \overline{B} + \overline{C} = 1 + \overline{B} + \overline{C} = 1$$

\*  $f = (A + B + \overline{C})(A + \overline{B} + \overline{C})(\overline{A} + B + \overline{C})(\overline{A} + \overline{B} + \overline{C})$

$$= \underline{\overline{A}\overline{A}} + \underline{A\overline{B}} + \underline{A\overline{C}} + \underline{AB} + \underline{\overline{B}\overline{B} + \overline{B}\overline{C}} + \underline{\overline{A}\overline{C}} + \underline{\overline{B}\overline{C}} + \underline{\overline{C}\overline{C}} (\overline{A} + B + \overline{C})(\overline{A} + \overline{B} + \overline{C})$$

$$= A + A\overline{B} + A\overline{C} + AB + \overline{B}\overline{C} + \overline{B}\overline{C} (\overline{A} + B + \overline{C})(\overline{A} + \overline{B} + \overline{C})$$

$$= \underline{\overline{A}\overline{A}} + \underline{A\overline{B}\overline{A}} + \underline{A\overline{C}\overline{A}} + \underline{AB\overline{A}} + \underline{B\overline{C}\overline{A}} + \underline{\overline{B}\overline{C}\overline{A}} + \underline{AB} + \underline{\overline{A}\overline{B}\overline{B}} + \underline{A\overline{C}\overline{B}} + \underline{A\overline{B}\overline{B}}$$

$$\underline{B\cdot\overline{B}\overline{C}} + \underline{\overline{B}\overline{C}\overline{B}} + \underline{A\overline{C}} + \underline{A\overline{B}\overline{C}} + \underline{A\overline{C}\overline{C}} + \underline{A\overline{B}\overline{C}} + \underline{\overline{B}\overline{C}\overline{C}} + \underline{\overline{B}\overline{C}\overline{C}} (\overline{A} + \overline{B} + \overline{C})$$

$$= \overline{ABC} + \overline{ABC} + \overline{ABC} + AB + ABC + AB + \overline{BC} + A\overline{C} + A\overline{B}\overline{C} + A\overline{C} + A\overline{B}\overline{C}$$

$$+ B\overline{C} + \overline{BC}(\overline{A} + \overline{B} + \overline{C}).$$

$$= \overline{ABC} + \overline{ABC} + \overline{ABC} + \overline{ABA} + \overline{ABC\overline{A}} + \overline{ABA} + \overline{BC\overline{A}} + \overline{AC\overline{A}} + \overline{ABC\overline{A}} + \overline{AC\overline{A}}$$

$$+ \overline{AABC} + \overline{BC\overline{A}} + \overline{BC\overline{A}} + \overline{ABC\overline{B}} + \overline{ABC\overline{B}} + \overline{ABC\overline{B}} + \overline{ABC\overline{B}} +$$

$$\overline{ABC\overline{B}} + \overline{B\overline{C}\overline{B}} + \overline{A\overline{B}\overline{C}} + \overline{A\overline{B}\overline{C}} + \overline{A\overline{C}\overline{B}} + \overline{A\overline{C}\overline{B}} + \overline{B\overline{C}\overline{B}} + \overline{B\overline{C}\overline{B}} + \overline{ABC}$$

$$+ \overline{ABC} + \overline{ABC} + \overline{ABC} + \overline{ABC} + \overline{BC\overline{C}} + \overline{AC\overline{C}} + \overline{ABC\overline{C}} + \overline{AC\overline{C}}$$

$$+ \overline{ABC\overline{C}} + \overline{BC\overline{C}} + \overline{BC\overline{C}}.$$

$$= \overline{ABC} + \overline{ABC} + \overline{ABC} + \overline{ABC} + \overline{BC} + \overline{ABC} + \overline{BC} + A\overline{C} +$$

$$= \overline{BC}(1 + \overline{A} + A) + \overline{ABC} + \overline{ABC} + \overline{BC} + A\overline{C}$$

$$= \overline{BC} + \overline{ABC} + \overline{ABC} + \overline{BC} + A\overline{C}$$

$$= \overline{BC}(1 + A) + \overline{BC} + \overline{ABC} + A\overline{C}$$

$$= \overline{BC} + \overline{BC} + \overline{ABC} + A\overline{C}$$

$$= \overline{BC}(1 + \overline{A}) + \overline{BC} + A\overline{C}$$

$$= \overline{BC} + \overline{BC} + A\overline{C}$$

$$= \overline{C}(B + \overline{B} + A) = \overline{C}(1 + A) = \overline{C}$$

$$\begin{aligned}
 * f &= A \cdot \overline{(A \oplus B) \oplus C} \\
 \rightarrow f &= A \cdot \overline{\underbrace{[A \oplus B]}_{\substack{A \\ B}} \oplus C} \\
 &= A \left[ \overline{A \oplus B} \cdot C + (A \oplus B) \cdot \overline{C} \right] \\
 &= A \left[ (\overline{AB} + \overline{BA}) \cdot C + ((\overline{AB} + \overline{BA}) \cdot \overline{C}) \right] \\
 &= A \left[ (\overline{AB})(\overline{BA}) + \overline{C} \right] \cdot \left[ (\overline{AB} + \overline{BA}) + \overline{C} \right] \\
 &= A \left[ (\overline{A} + \overline{B})(\overline{B} + \overline{A}) + \overline{C} \right] \cdot \left[ (\overline{AB} + \overline{BA}) + \overline{C} \right] \\
 &= A \left[ (AB + \overline{A}\overline{A} + \overline{B}\overline{B} + \overline{A}\overline{B} + \overline{C}) \right] \cdot \left[ (\overline{AB} + \overline{BA} + \overline{C}) \right] \\
 &= A \left[ AB + \overline{A}\overline{B} + \overline{C} \right] \cdot \left[ (\overline{AB} + \overline{BA} + \overline{C}) \right] \\
 &= A \left[ \overline{AB}\overline{AB} + \overline{AB}\overline{BA} + \overline{ABC} + \overline{A}\overline{B}\overline{AB} + \overline{A}\overline{B}\overline{BA} + \overline{ABC} + \overline{ABC} + \overline{BAC} \right. \\
 &\quad \left. + \overline{C.C} \right] \\
 &= A \left[ ABC + \overline{ABC} + \overline{ABC} + \overline{ABC} \right] \\
 &= A \cdot ABC + A \cdot \overline{ABC} + A \cdot \overline{ABC} + A \cdot \overline{ABC} \\
 &= ABC + \overline{ABC} \\
 &= A [BC + \overline{BC}] \\
 &= A [B \odot C].
 \end{aligned}$$
  

$$\begin{aligned}
 * f &= (B+BC)(B+\overline{BC})(B+D) \\
 f &= (B \cdot B + B \cdot \overline{BC} + BC \cdot B + BC \cdot \overline{BC})(B+D) \\
 &= (B+BC)(B+D) \\
 &= B \cdot B + BD + B \cdot BC + BCD \\
 &= B + BD + \underline{BC} + BCD \\
 &= B(1+C) + BD(1+C) \\
 &= B + BD \Rightarrow B(1+D) = \underline{B}
 \end{aligned}$$

$$* f(A, B, C, D) = \overline{AB} + \overline{BC} + \overline{AD} + CD$$

Applying the consensus theorem to 2<sup>nd</sup> and 4<sup>th</sup> terms.

$$\overline{AB} + \overline{BC} + \overline{AD} + CD + \overline{BD} \quad (\overline{BC} + CD + \overline{BD} = \overline{BC} + CD)$$

3<sup>rd</sup> and 5<sup>th</sup> terms, the term  $\overline{AB}$  becomes redundant.

$$\overline{BC} + \overline{AD} + CD \quad (\overline{BD} + \overline{AD} + \overline{AB} = \overline{BD} + \overline{AD})$$

$$f_{\min} = \overline{AD} + \overline{BC} + CD$$

K-map (Karnaugh-map) :-

The K-map method, on the other hand, is a systematic method of (simplification dep) simplifying the Boolean Expressions. The K-map is a chart or a graph, composed of an arrangement of adjacent cells, each representing a particular combination of variables in sum or product form.

→ An n variable function can have  $2^n$  possible combinations of product terms in SOP form, or  $2^n$  possible combinations of sum terms in POS form.

→ A two-variable K-map will have  $2^2 = 4$  cells or squares,

→ A three-variable K-map will have  $2^3 = 8$  cells or squares

→ A four-variable K-map will have  $2^4 = 16$  cells or squares.

→ Any boolean Expression can be expressed in a standard or expanded Sum of products form or in a standard or canonical or expanded product of sums form.

→ Each of the product terms in the standard SOP form is called minterms and each of the sum terms in the standard POS form is called maxterms.

## Two-Variable K-map :- (Mapping of SOP Expressions)

A two-variable K-map has  $2^2 = 4$  cells or squares.  
4 possible combinations of the input variables A and B:

$$(\bar{A}\bar{B}, \bar{A}B, A\bar{B}, AB).$$

$$m_0 = \bar{A}\bar{B}, m_1 = \bar{A}B, m_2 = A\bar{B}, m_3 = AB.$$

\*  $f = A\bar{B} + AB$  simplify by using K-map.

A	B	0	1
		0	0
1	0	1	1
	1	1	0

A	B	$\bar{A}\bar{B}$	$\bar{A}B$
		$A\bar{B}$	$AB$
1	0	1	1
	1	1	0

The minterms of a two-variable K-map.


$$f = B.$$

\* Reduce the expression by using K-map.

$$f = A\bar{B} + AB + \bar{A}B$$

A	B	0	1
		0	1
1	0	1	0
	1	0	0

logic diagram

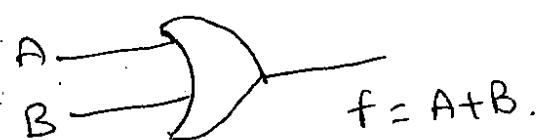

$$f = A + B$$

## mapping of POS Expressions



$$M_0 = A + B, M_1 = A + \bar{B}, M_2 = \bar{A} + B, M_3 = \bar{A} + \bar{B}$$

A	B	0	1
		0	$A + \bar{B}$
1	0	$A + B$	$\bar{A} + B$
	1	$\bar{A} + \bar{B}$	$\bar{A} + \bar{B}$

The maxterms of a two-variable K-map.

→ Reduce the expression by using K-map
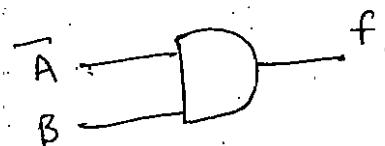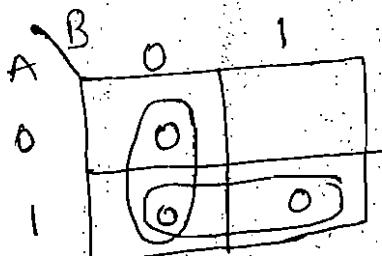
$$f = (A+B)(\bar{A}+\bar{B})(\bar{A}+B)$$



$$f = \bar{A}B$$

### Three-variable K-map

A function in three variable (A, B, C) expressed in the standard SOP form can have  $2^3 = 8$  possible combinations. They are  $\bar{A}\bar{B}\bar{C}$ ,  $\bar{A}\bar{B}C$ ,  $\bar{A}B\bar{C}$ ,  $A\bar{B}\bar{C}$ ,  $A\bar{B}C$ ,  $AB\bar{C}$ ,  $ABC$ , and  $A\bar{B}C$ . In the standard POS form can have  $2^3 = 8$  possible combinations. They are  $A+B+C$ ,  $A+B+\bar{C}$ ,  $A+\bar{B}+C$ ,  $A+\bar{B}+\bar{C}$ ,  $\bar{A}+B+C$ ,  $\bar{A}+B+\bar{C}$ ,  $\bar{A}+\bar{B}+C$  and  $\bar{A}+\bar{B}+\bar{C}$ .

		BC	00	01	11	10
		A	0	1	1	0
0	0	$\bar{A}\bar{B}\bar{C}$ (M <sub>0</sub> )	$\bar{A}\bar{B}C$ (M <sub>1</sub> )	$\bar{A}B\bar{C}$ (M <sub>2</sub> )	$A\bar{B}\bar{C}$ (M <sub>3</sub> )	
		$ABC$ (M <sub>4</sub> )	$A\bar{B}\bar{C}$ (M <sub>5</sub> )	$ABC$ (M <sub>6</sub> )	$A\bar{B}\bar{C}$ (M <sub>7</sub> )	

$A+B+C$ (M <sub>0</sub> )	$A+B+\bar{C}$ (M <sub>1</sub> )	$A+\bar{B}+\bar{C}$ (M <sub>3</sub> )	$A+\bar{B}+C$ (M <sub>2</sub> )
$\bar{A}+B+C$ (M <sub>4</sub> )	$\bar{A}+B+\bar{C}$ (M <sub>5</sub> )	$\bar{A}+\bar{B}+\bar{C}$ (M <sub>7</sub> )	$\bar{A}+\bar{B}+C$ (M <sub>6</sub> )

max terms.

minterms

\* Reduce the expression  $f = \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C + \bar{A}B\bar{C} + A\bar{B}\bar{C} + ABC$ .


$$\bar{A}\bar{B}\bar{C} = 001 = M_1$$

$$\bar{A}\bar{B}C = 101 = M_5$$

$$\bar{A}B\bar{C} = 010 = M_2$$

$$A\bar{B}\bar{C} = 110 = M_6$$

$$ABC = 111 = M_7$$

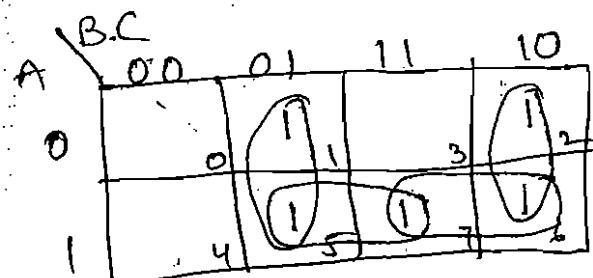

$$f_1 = m_1 + m_5 = \bar{A}\bar{B}C + A\bar{B}C = \bar{B}C(A + \bar{A}) = \bar{B}C.$$


$$f_2 = m_5 + m_7 = A\bar{B}C + ABC = AC(B + \bar{B}) = AC$$

$$f_3 = m_7 + m_6 = ABC + AB\bar{C} = AB(C + \bar{C}) = AB$$

$$f_4 = m_2 + m_6 = ABC + \bar{A}B\bar{C} = \bar{B}\bar{C}(A + \bar{A}) = \bar{B}\bar{C}$$

$$f = f_1 + f_2 + f_3 + f_4$$
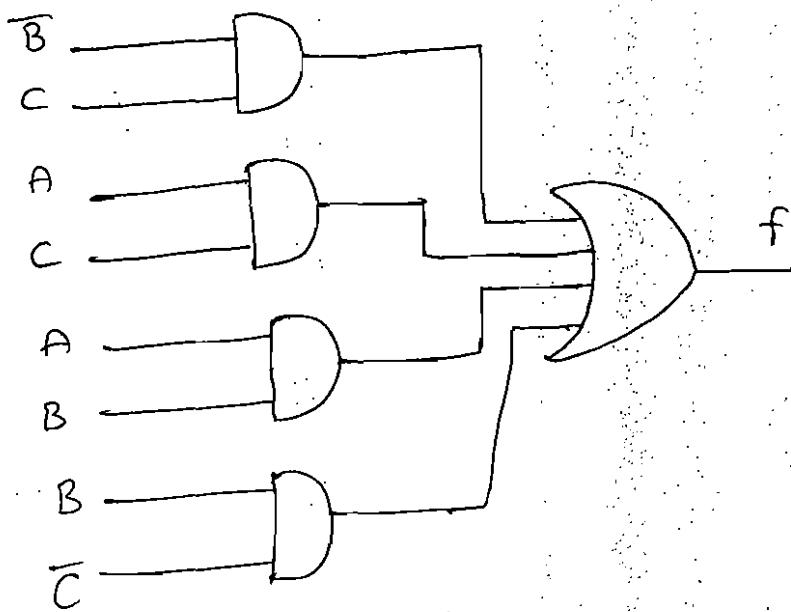
$$= \bar{B}C + AC + AB + \bar{B}\bar{C}$$



logic diagram

\* Reduce the Expression.  $f = (A+B+C)(\bar{A}+\bar{B}+\bar{C})(\bar{A}+\bar{B}+\bar{C})$

$$(A+\bar{B}+\bar{C})(\bar{A}+\bar{B}+\bar{C})$$

$$A+B+C = 000 = M_0$$

$$\bar{A}+\bar{B}+\bar{C} = 101 = M_5$$

$$\bar{A}+\bar{B}+\bar{C} = 011 = M_7$$

$$A+\bar{B}+\bar{C} = 011 = M_3$$

$$\bar{A}+\bar{B}+C = 110 = M_6$$

A	B	C	00	01	11	10	
0	0	0	0	0	1	3	2
1	1	1	0	0	0	0	0
	1	0	4	5	7	6	

$$f_1 = M_0 = A + B + C$$

$$f_2 = M_5 \cdot M_7 = (\overline{A+B+C}) (\overline{A+B+C})$$

$$\begin{aligned} &= \overline{AA} + \overline{AB} + \overline{AC} + \overline{AB} + \overline{BB} + \overline{BC} + \overline{AC} + \overline{BC} + \overline{CC} \\ &= \overline{A} + \overline{AB} + \overline{AC} + \overline{AB} + \overline{BC} + \overline{BC} \\ &= \overline{A} (1 + \overline{B} + \overline{C} + \overline{B}) + \overline{B} (\overline{B} + \overline{B}) \end{aligned}$$

$$f_2 = \overline{A} + \overline{C}$$

$$f_3 = M_3 \cdot M_7$$

$$= (A + \overline{B} + \overline{C}) (\overline{A} + \overline{B} + \overline{C})$$

$$\begin{aligned} &= \overline{AA} + \overline{AB} + \overline{AC} + \overline{AB} + \overline{BB} + \overline{BC} + \overline{AC} + \overline{BC} + \overline{CC} \\ &= \overline{A} \overline{A} + \overline{A} \overline{B} + \overline{A} \overline{C} + \overline{A} \overline{B} + \overline{B} \overline{B} + \overline{B} \overline{C} + \overline{A} \overline{C} + \overline{B} \overline{C} + \overline{C} \overline{C} \end{aligned}$$

$$= \overline{A} \overline{B} + \overline{A} \overline{C} + \overline{A} \overline{B} + \overline{B} + \overline{B} \overline{C} + \overline{A} \overline{C} + \overline{C}$$

$$= \overline{B} (1 + \overline{A} + A + \overline{C}) + \overline{C} (1 + \overline{B} + \overline{A})$$

$$\therefore = \overline{B} + \overline{C}$$

$$f_4 = M_7 \cdot M_6$$

$$= (\overline{A} + \overline{B} + \overline{C}) (\overline{A} + \overline{B} + C)$$


$$\begin{aligned} &= \overline{A} \cdot \overline{A} + \overline{A} \overline{B} + \overline{A} C + \overline{A} \overline{B} + \overline{B} \overline{B} + \overline{B} \overline{C} + \overline{A} \overline{C} + \overline{B} \overline{C} + C \cdot \overline{C} \\ &= \overline{A} \cdot \overline{A} + \overline{A} \overline{B} + \overline{A} C + \overline{B} + \overline{B} \overline{C} + \overline{A} \overline{C} + \overline{B} \overline{C} + 0 \end{aligned}$$

$$= \overline{A} (1 + \overline{B} + C + \overline{C}) + \overline{B} (1 + C + \overline{C})$$

$$\therefore = \overline{A} + \overline{B}$$

$$F = f_1 \cdot f_2 \cdot f_3 \cdot f_4$$
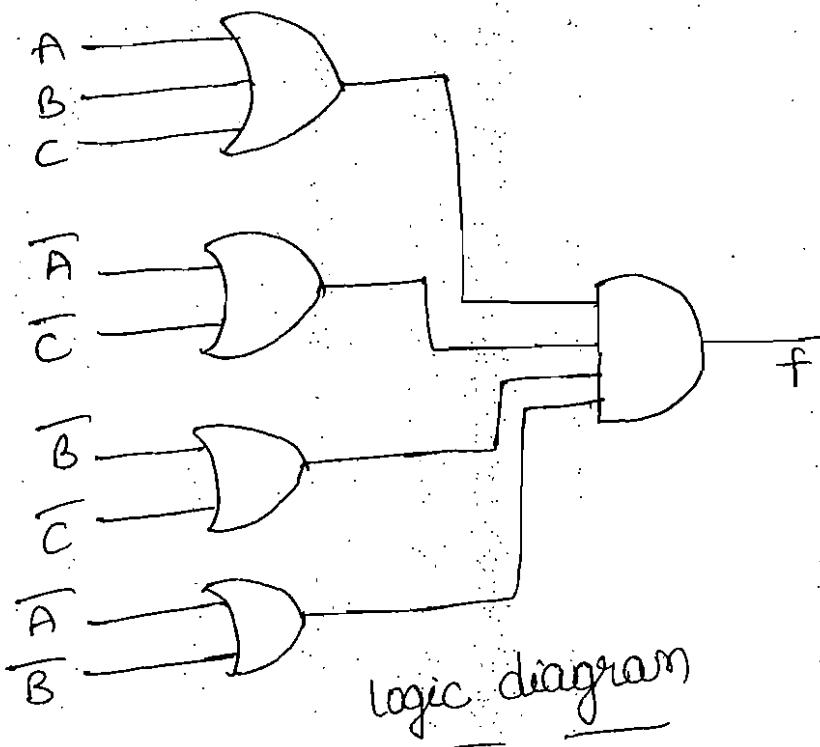
$$= (A + B + C) (\overline{A} + \overline{C}) (\overline{B} + \overline{C}) (\overline{A} + \overline{B})$$



Four-variable K-map :-

A four-variable ( $A, B, C, D$ ) expression can have  $2^4 = 16$  possible combinations.

		CD	00	01	11	10
		AB	00	01	11	10
00	$\bar{A}\bar{B}\bar{C}\bar{D}$	$\bar{A}\bar{B}C\bar{D}$	$\bar{A}\bar{B}CD$	$\bar{A}BC\bar{D}$		
01	$\bar{A}\bar{B}\bar{C}\bar{D}$	$\bar{A}\bar{B}C\bar{D}$	$\bar{A}BCD$	$\bar{A}B\bar{C}D$		
11	$A\bar{B}\bar{C}\bar{D}$	$A\bar{B}C\bar{D}$	$ABC\bar{D}$	$AB\bar{C}D$		
10	$A\bar{B}\bar{C}\bar{D}$	$A\bar{B}C\bar{D}$	$A\bar{B}CD$	$A\bar{B}C\bar{D}$		

		CD	00	01	11	10
		AB	00	01	11	10
00			$A+B+C+D$	$A+B+C+\bar{D}$	$A+B+\bar{C}+\bar{D}$	$A+B+\bar{C}+D$
01			$A+\bar{B}+C+D$	$A+\bar{B}+C+\bar{D}$	$A+\bar{B}+\bar{C}+\bar{D}$	$A+\bar{B}+\bar{C}+D$
11			$\bar{A}+\bar{B}+C+D$	$\bar{A}+\bar{B}+C+\bar{D}$	$\bar{A}+\bar{B}+\bar{C}+\bar{D}$	$\bar{A}+\bar{B}+\bar{C}+D$
10			$\bar{A}+\bar{B}+C+\bar{D}$	$\bar{A}+\bar{B}+C+D$	$\bar{A}+\bar{B}+\bar{C}+\bar{D}$	$\bar{A}+\bar{B}+\bar{C}+D$

SOP form :-

POS form :-

\* Reduce the expression  $f = \sum m(0,1,2,3,5,7,8,9,10,12,13)$  and implement the expression by using universal logic.

$$f = \sum m(0,1,2,3,5,7,8,9,10,12,13)$$

AB\CD	00	01	11	10
00	1	1	1	1
01		1	1	
11	1	1	12	13
10	1	1	14	15


$$f_1 = m_0 + m_2 + m_3 + m_5 = \overline{A}B\overline{D}$$

$$f_2 = m_1 + m_3 + m_5 + m_7 = \overline{A}D$$

$$f_3 = m_{12} + m_{13} + m_8 + m_9 = A\overline{C}$$

$$f_4 = m_8 + m_{10} + m_0 + m_2 = \overline{B}\overline{D}$$
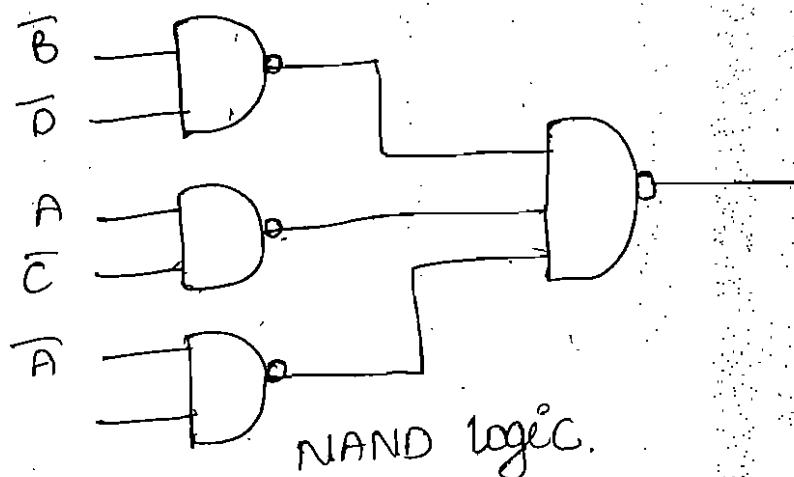
$$\begin{aligned} f_{min} &= f_1 + f_2 + f_3 \\ &= \overline{B}\overline{D} + A\overline{C} + \overline{A}D. \end{aligned}$$



\* Reduce the expression  $f = \prod M(2,8,9,10,11,12,14)$  and implement the expression by using universal logic.

$$f = \prod M(2,8,9,10,11,12,14).$$

AB	CD	00	01	11	10	01	10
00		0	1	3	0	6	
01		4	5	7			
11		12	13	15	0	14	
10		8	0	9	0	10	


$$f_1 = M_8 \cdot M_9 \cdot M_{11} \cdot M_{10} \quad f_2 = M_8 \cdot M_{12} \cdot M_{10} \cdot M_{14}$$

$$= (\bar{A} + B) \quad = (\bar{A} + D)$$

$$f_3 = M_2 \cdot M_{10}$$

$$= (B + \bar{C} + D)$$
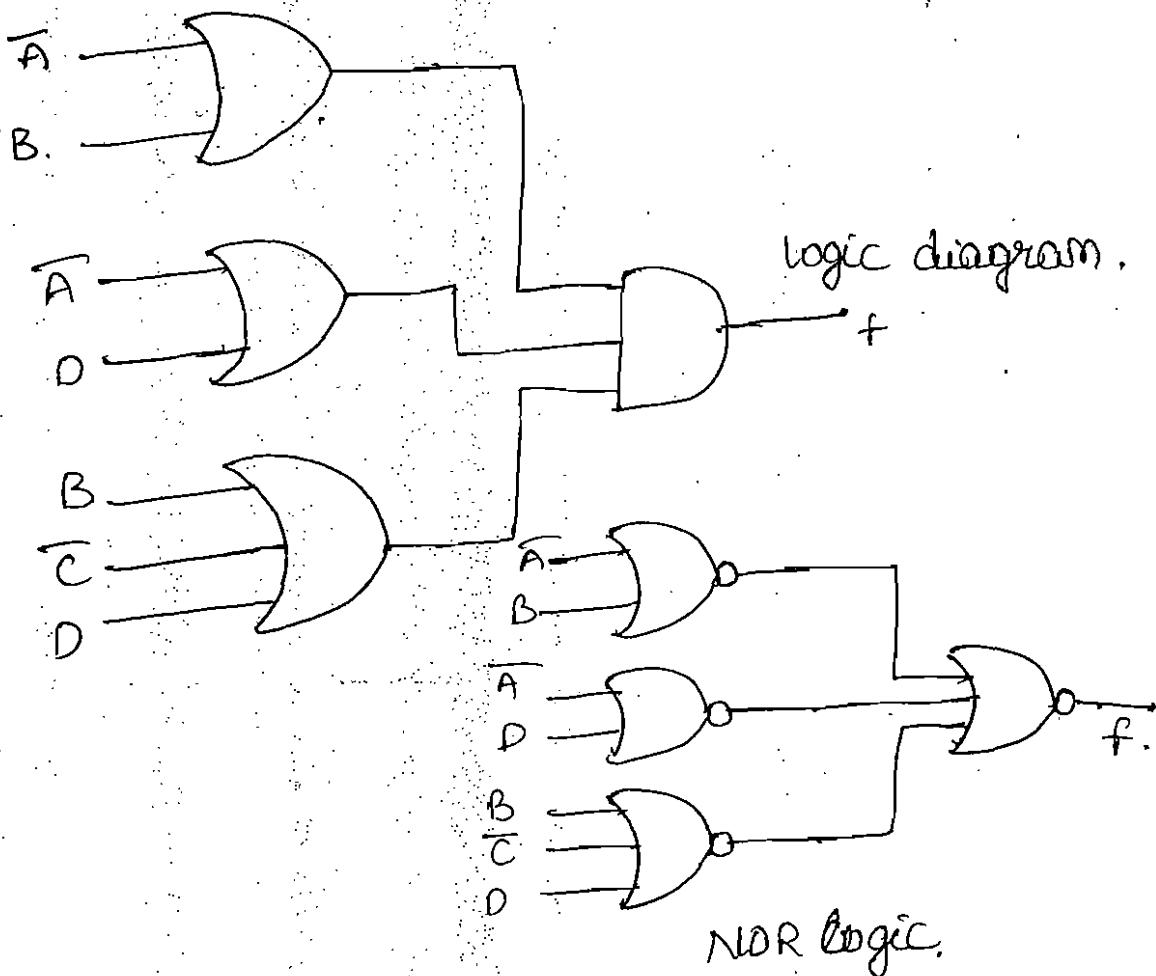
$$f_{min} = (\bar{A} + B) (\bar{A} + D) (B + \bar{C} + D)$$



### prime implicants :- [PI]

Each square or rectangle made up of the bunch of adjacent minterms is called a subcube. Each of these subcubes is called a prime implicants.

### essential prime implicants:-

The prime implicant which contains at least one 1 which cannot be covered by any other prime implicant is called an essential prime implicant [EPI].

### Redundant prime implicants:-

The prime implicant whose each 1 is covered at least by one EPI is called a redundant prime implicants. (RPI).

### Selective prime implicants:-

A prime implicant which is neither an essential prime implicant nor a redundant prime implicant is called a selective prime implicant (SPI).

AB\CD	00	01	11	10	
00	0	1	1	2	→ essential prime implicant
01	14	1	1	6	→ redundant prime implicant
11	12	13	15	14	prime implicant
10	8	9	11	10	

$$f = \sum m(5, 7, 13, 15, 9, 14, 4)$$

$$f(A,B,C,D) = \Sigma m(0,4,5,10,11,13,15).$$

	AB\CD	00	01	11	10
EPI	00	1		3	2
	01	1	1	7	5
SPI	11	1	1	7	14
	10	8	9	11	10

False prime implicants :- (FPI)

The prime implicants obtained by using the maxterms are called False prime implicants.

Essential false prime implicants:-

The FPI's which contains at least one '0' which cannot be covered by any other FPI is called Essential False prime implicants [EFPI].


	AB\CD	00	01	11	10
EFP1	00	0	1	3	2
	01	0	0	0	0
EFP1	11	0	0	0	0
	10	8	9	11	10

	AB\CD	00	01	11	10
EFP1	00	0	0	0	0
	01	0	0	0	0
EFP1	11	0	0	0	0
	10	0	0	0	0

The four corner 0's form the largest cluster of adjacent 0's, which is an FPI whose 0's are covered by essential FPI's and hence is a redundant false prime implicant (RFPI).
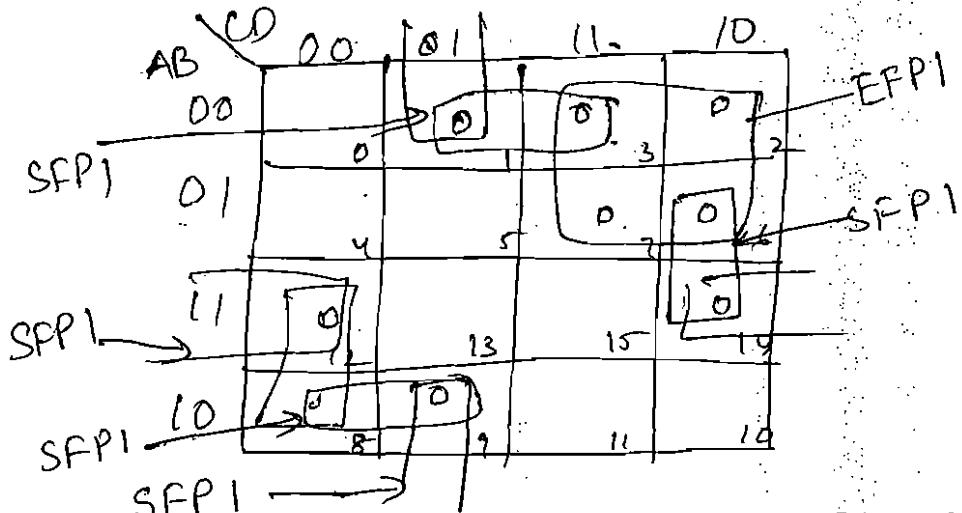
$$F(A, B, C, D) = (A + \bar{C})(A + B + \bar{D})[A \rightarrow B \rightarrow C](\bar{A} + \bar{B} + D)$$



The function has in all seven FPI's marked in figure.

The FPI is an essential FPI as it contains 0's at locations 2 and 7 which cannot be covered by any other FPI.

The remaining FPI are all SFP1's.


Five-variable K-map :-

A five-variable ( $A, B, C, D, E$ ) expression can have  $2^5 = 32$  possible combinations of input variables.

The 32 squares of the K-map are divided into 2 blocks of 16 squares each. One block taken as  $A=1$ , and another one taken as  $A=0$ .

\* Reduce the following expression in SOP and POS form.

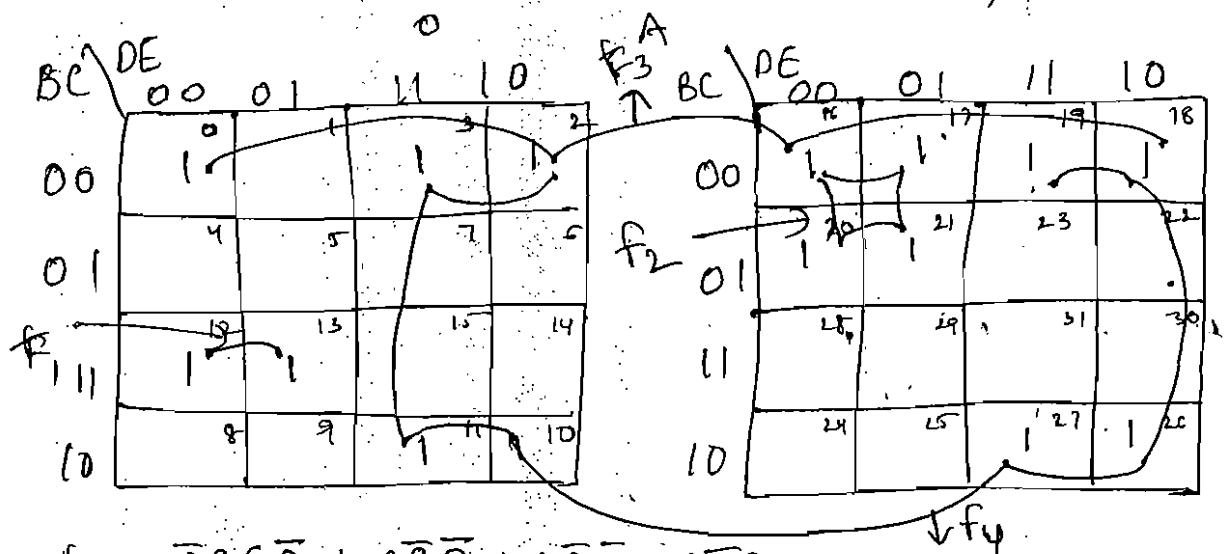
$$f = \sum m(0, 2, 3, 10, 11, 12, 13, 16, 17, 18, 19, 20, 21, 26, 27)$$



$$f_{\text{min}} = \overline{ABC}\bar{D} + \overline{AB}\bar{D} + A\bar{B}\bar{D} + \overline{A}\bar{C}\bar{D}$$

$$f_1, f_2, f_3, f_4.$$
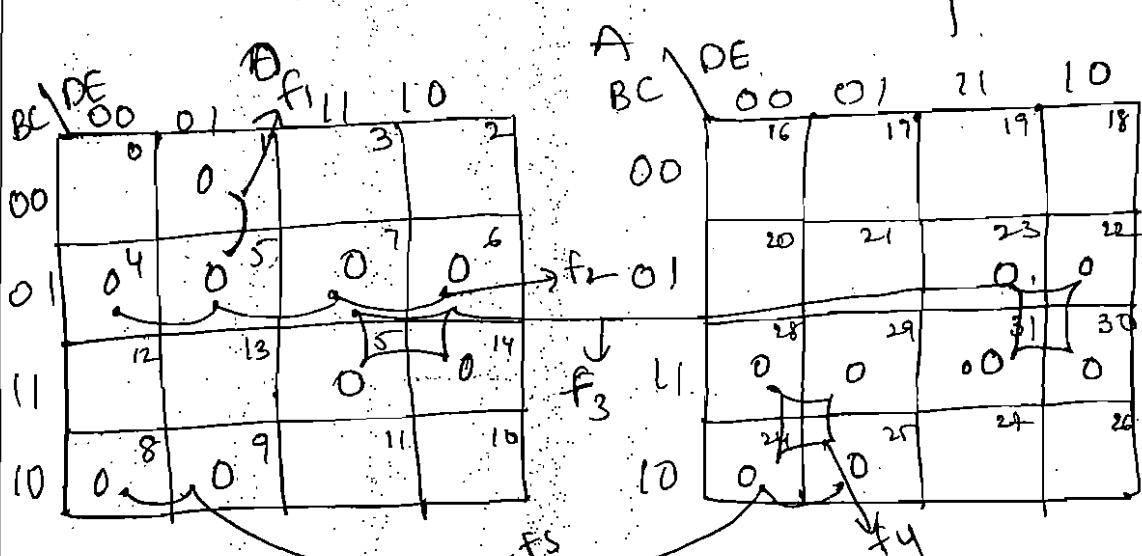
$$f = \prod M(1, 4, 5, 6, 7, 8, 9, 14, 15, 22, 23, 24, 25, 28, 29, 30, 31)$$



$$f_1 = (A+B+\bar{D}+\bar{E}) \quad f_3 = \bar{C}+\bar{D} \quad f_5 = (\bar{B}+C+\bar{D})$$

$$f_2 = (A+B+\bar{C}) \quad f_4 = \bar{A}+\bar{B}+\bar{D}$$

$$F_{\text{min}} = f_1 \cdot f_2 \cdot f_3 \cdot f_4 \cdot f_5$$

$$= (A+B+\bar{D}+\bar{E}) (A+B+\bar{C}) (\bar{C}+\bar{D})(\bar{A}+\bar{B}+\bar{D})(\bar{B}+C+\bar{D})$$


## Six-Variable K-map :-

A six-variable ( $A, B, C, D, E, F$ ) expression can have  $2^6 = 64$  possible combinations of input variables.

The 64 squares of the K-map are divided into 4 blocks of 16 squares each. One block taken as  $AB = "00"$  and remaining are " $01$ ", " $10$ ", and " $11$ ".

\* Reduce the expression
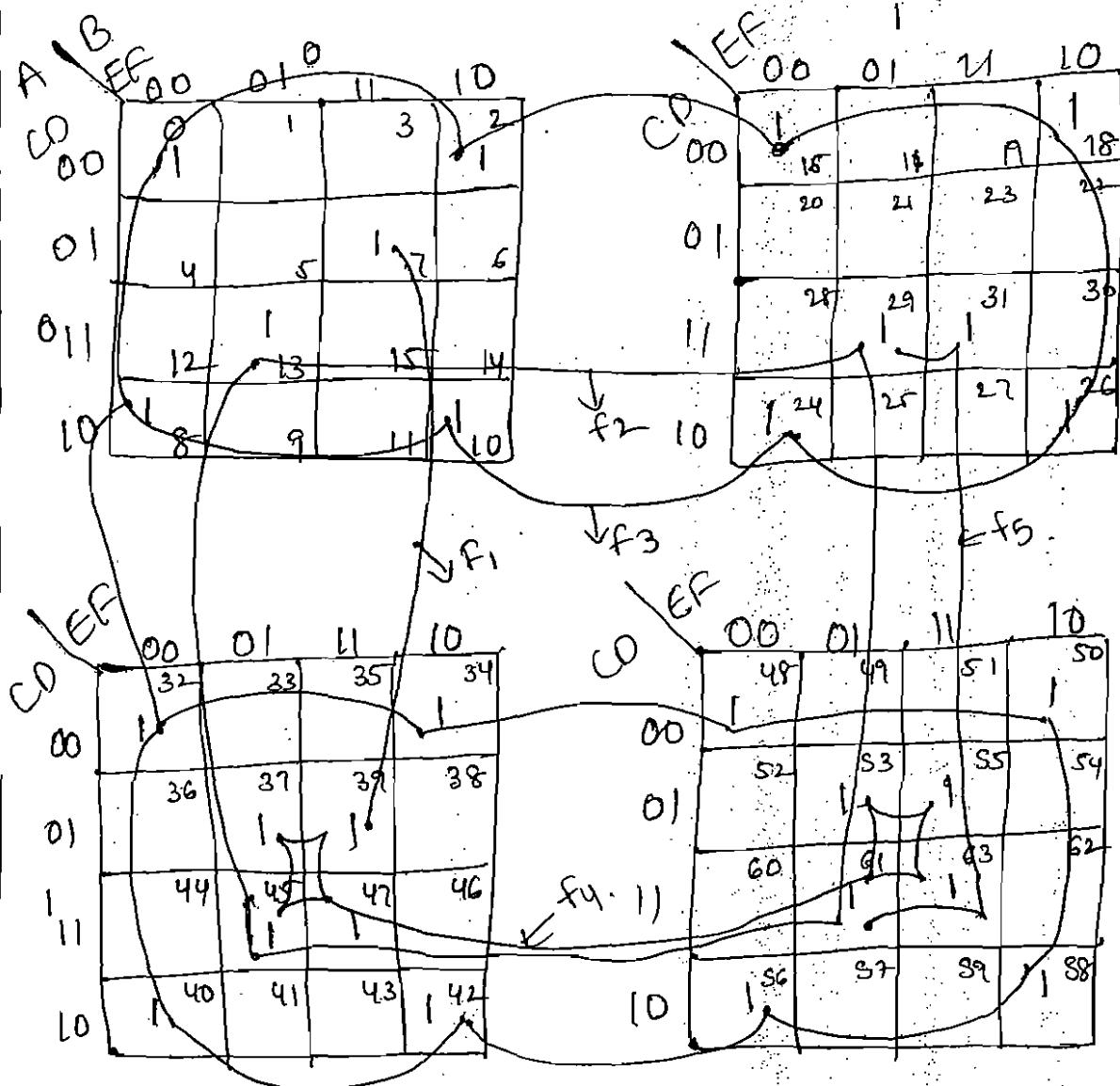
$$f = \sum m(0, 2, 7, 8, 10, 13, 16, 18, 24, 26, 29, 31, 32, 34, 37, 39, 40, 42, 45, 47, 48, 50, 53, 55, 56, 58, 61, 63)$$



$$f_1 = \overline{B}\overline{C}DEF$$

$$f_2 = C\overline{D}EF$$

$$f_3 = \overline{D}\overline{F}$$

$$f_4 = ADF$$

$$f_5 = BCDF$$

$$F_{\min} = f_1 + f_2 + f_3 + f_4 + f_5$$

$$F_{\min} = \overline{B}\overline{C}DEF + C\overline{D}\overline{E}F + \overline{D}\overline{F} + ADF + BCDF.$$


Don't care combinations :-

The combinations for which the values of the expression are not specified are called don't care combinations or optional combinations and such expressions, therefore incompletely specified. The don't care terms are denoted by d, x or q. During the process of design using an SOP map each don't care is treated as a 1 if it is helpful in map reduction. During the process of design using an POS map each don't care is treated as a 0 if it is helpful in map reduction.

→ A standard SOP expression with don't cares can be converted into a standard POS form by keeping the don't cares as they are, and writing the missing minterms of the SOP form as the maxterms of the POS form.

→ A standard POS expression with don't cares can be converted into a standard SOP form by keeping the don't cares as they are, and writing the missing maxterms of the POS form as the min terms of the SOP form.

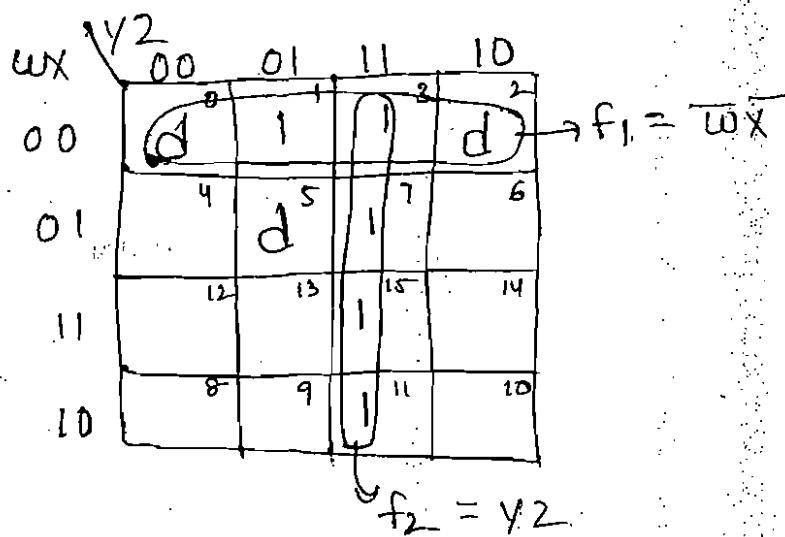
$$F(w,x,y,z) = \sum m(1,3,7,11,15) + \sum d(0,2,5).$$



$$f_{\min} = f_1 + f_2$$

$$= \overline{w}\overline{x} + yz$$
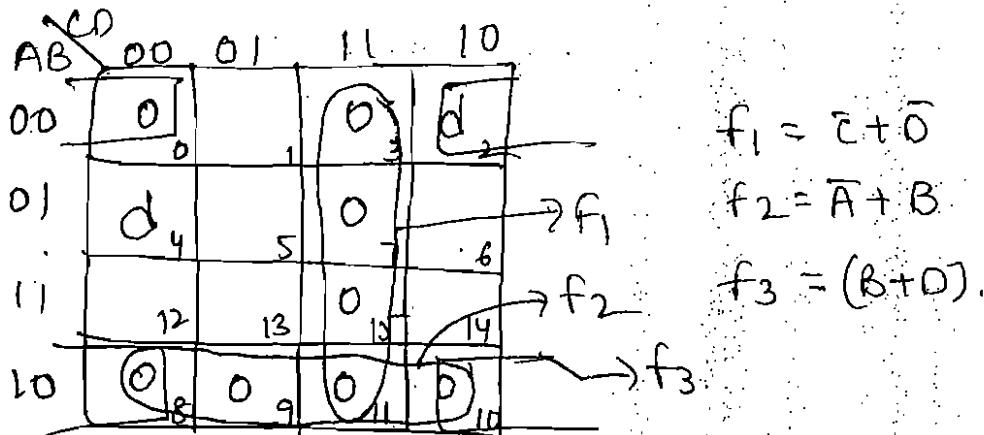
$$F(A,B,C,D) = \prod M[0,3,7,8,9,10,11,15] + \prod d[2,4]$$



$$f_{\min} = f_1 \cdot f_2 \cdot f_3 = (\overline{c} + \overline{d})(\overline{A} + B)(B + D)$$


### Limitations of K-map :-

- K-maps are not suitable when the number of variables involved exceed four. It may be used with difficulty up to five and six variable systems. But beyond 'six variable' K-maps cannot be physically visualized.
- The K-map simplification is a manual technique and simplification process is heavily dependent on the abilities of the designer. It cannot be programmed.

→ Reduce the expression  $f = \sum m(1, 5, 6, 12, 13, 14) + d(2, 4)$  by using k-map in pos form and implement by using universal logic

$$f = \sum m(1, 5, 6, 12, 13, 14) + d(2, 4) \rightarrow \text{SOP form.}$$
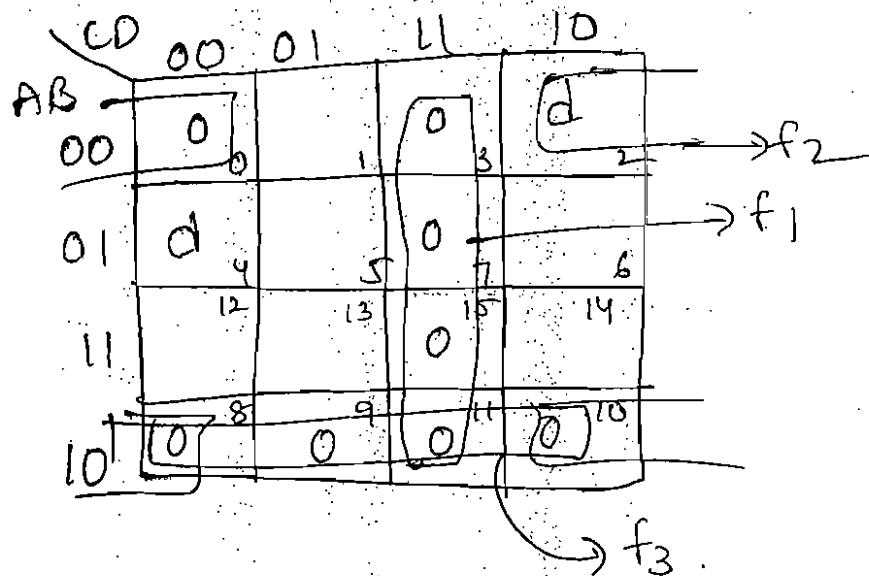
$$f = \prod M(0, 3, 7, 8, 9, 10, 11, 15), \prod d(2, 4).$$




$$f_1 = \overline{C} + \overline{D}$$

$$f_2 = (B + D)$$

$$f_3 = (\overline{A} + B)$$
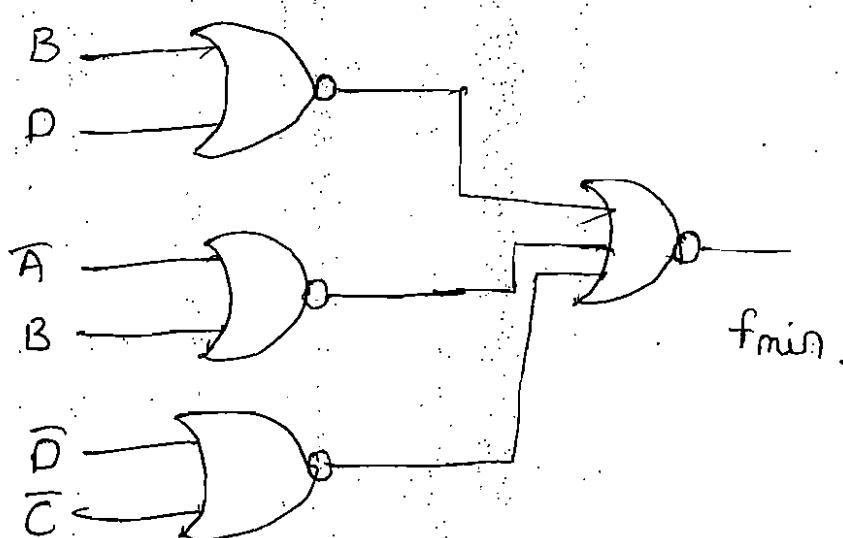
$$f_{\min} = (\overline{C} + \overline{D})(B + D)(\overline{A} + B).$$



## Aune McCluskey or tabular method :-

W.V. Aune and E.J. McCluskey developed an exact tabular method to simplify the Boolean Expression. This method is called the Aune McCluskey or tabular method.

The procedure for the minimization of a Boolean expression by the tabular method

Step 1. List all the minterms.

Step 2. Arrange all minterms in groups of the same number of 1's in their binary representation in column 1.

Step 3. Compare each term of the lowest index group with every term in the succeeding group.

Step 4 : compare the terms generated in step 2 in the same fashion combine two terms which differ by only a single 1 and whose dashes are in the same position to generate a new term.

Step 5 :- list all the prime implicants and draw the implicant chart. (The don't cares if any should not appear in the prime implicant chart).

Step 6 :- obtain essential prime implicants and write the minimal expression.

\* obtain the minimal expression for  $f = \sum m(1, 2, 3, 5, 6, 7, 8, 9, 12, 13, 15)$  using tabular method.

Step 1	Step 2	Step 3
index 1 1 000 ✓ 2 001 0 ✓ 8 1000 ✓	$\cancel{(1,3)(2)00-1}$ $\cancel{(1,5)(4)0-01}$ $\checkmark(1,9)(8)-001$	$(1,3,5,7)(2,4)0-1-T$ $(1,5,9,13)(4,8)-01-S$ $(2,3,6,7)(1,4)0-1-R$
index 2 3 001 1 ✓ 5 010 ✓ 6 011 0 ✓ 9 100 ✓ 12 110 0 ✓	$\cancel{(2,3)(1)001-}$ $\cancel{(2,6)(4)0-10}$ $\cancel{(8,9)(1)100-}$ $\checkmark(8,12)(4)1-00$ $\checkmark(3,7)(4)0-11$	$(8,9,12,13)(3,4)1-0-S$ $(5,7,13,15)(2,8)-1-1-P$
index 3 7 011 1 ✓ 13 110 1 ✓	$\checkmark(5,7)(2)01-1$ $\cancel{(5,13)(8)-101}$ $\cancel{(6,7)(1)011-}$	
index 4 15 111 1 ✓	$\checkmark(9,13)(4)1-01$ $\checkmark(12,13)(1)110-$ $(7,15)(8)-111$ $(5,15)(2)-11-1$	

Prime implicant chart

	1	2	3	5	6	7	8	9	12	13	15
P $\rightarrow 5, 7, 13, 15 \{28\}$				x		x				x	x
Q $\rightarrow 8, 9, 12, 13$							x	x	x	x	
R $\rightarrow 2, 3, 6, 7$		x	x			x					
S $\rightarrow 1, 5, 9, 13$	x			x	x			x			
T $\rightarrow 1, 3, 5, 7$	x		x	x	x	x	x	x			

$$P + Q + R + S \rightarrow BD + A\bar{C} + \bar{A}C + \bar{C}D$$

$$P + Q + R + T \rightarrow BD + A\bar{C} + \bar{A}C + \bar{A}D.$$

Simplify the following function using the branching method:

$$f(A, B, C, D, E) = \sum m(0, 4, 12, 16, 19, 24, 28, 29, 31)$$

Index 0 0 0000 ✓

(0, 4) (4) 00 - 00 W ✓

index 1 4 00100 ✓  
16 10000 ✓

(0, 16) (16) - 0000 V

index 2 12 01100 ✓  
24 11000 ✓

(4, 12) (8) 0 - 100 U  
(16, 24) (8) 1 - 000 T

index 3 19 10011 X.  
28 11100 ✓

(12, 28) (16) - 1100 S ✓  
(24, 28) (4) 11 - 00 R ✓

index 4 29 11101 ✓

(28, 29) (1) 1110 - W

index 5 31 11111 ✓

(29, 31) (2) 111 - 1 P \*

Prime implicant chart

0	4	12	16	19	24	28	29	31
---	---	----	----	----	----	----	----	----

\* P(29, 31).

X (X)

Q(28, 29)

X X

R (24, 28)

X X

S (12, 28)

X

X

T (16, 24)

X

X

U (4, 12)

X

V (0, 16)

X

W (0, 4)

X X

\* X (19)

(X)

In table x and p are essential prime implicants.

	0	4	12	16	24	28
w(0,4) (4)	x	x				
v(0,16) (16)	x			x		
u(4,12) (8)		x	x		x	x
t(16,24) (8)				x	x	x
s(12,28) (16)				x		
r(24,28) (4)					x	x
q(28,29) (1)						x

In the reduced PI chart, there were no essential

PIS, dominated rows: 8) dominating columns in column 0.  
it is covered by rows w and v. First select row w.

	12	16	24	28
v(0,16)		x		
u(4,12)	x		x	x
t(16,24)		x		
s(12,28)	x		x	x
r(24,28)				x
q(28,29)				

In this row v is dominated by row t, row u and row  
w are dominated by row s. So rows v, u, w can be reduced.


	12	16	24	28
* t(16,24)		x	x	
* s(12,28)	x		x	x
r(24,28)			x	x

In this, T and S are the secondary essential prime  
implicants. So R is redundant.

$$f_{min} = w + s + t + x + p$$

$$= \overline{AB}\overline{D}\overline{E} + BC\overline{D}\overline{E} + A\overline{C}\overline{D}\overline{E} + A\overline{B}\overline{C}DE + ABCE$$

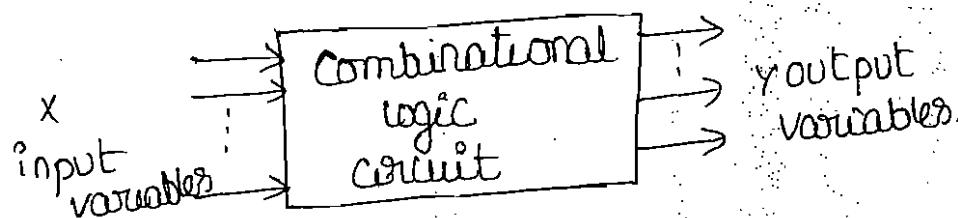logic circuits for digital systems may be combinational or sequential. In combinational circuits, the output variables at any instant of time are dependent only on the present input variables. In sequential circuits, the output variables at any instant of time are dependent on the present and past input variables.




### Adders :-

The most basic arithmetic operation is the addition of two binary digits. A combinational circuit that performs the addition of two bits is called a "half-adder". One that performs the addition of three bits (two bits and previous carry) is called a "full-adder".


### Half-adder

A half adder is a combinational circuit with two binary inputs. (augend and addend bits) and two outputs. sum and carry.

Inputs		Output	
A	B	S	C
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

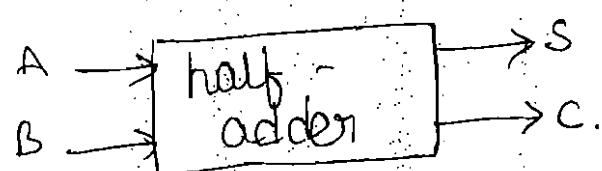


K-map for S.

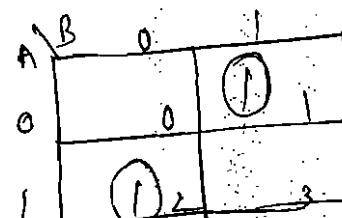

$$S = A\bar{B} + \bar{A}B$$


K-map for C

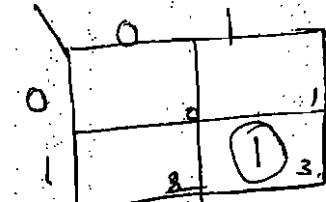

$$C = A \cdot B$$

(a) Truth table.

$$= A \oplus B$$

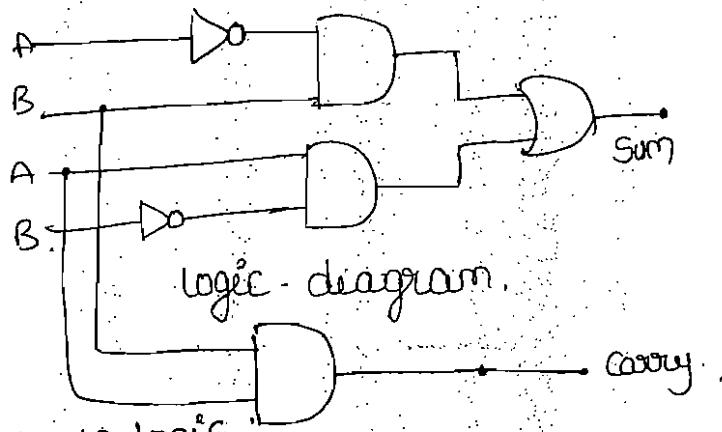

NAND logic

$$S = A \cdot B + \overline{A} \cdot \overline{B}$$

$$S = A \cdot \overline{B} + \overline{A} \cdot B + A \cdot \overline{A} + B \cdot \overline{B}$$


$$= A(\overline{A} + B) + B(\overline{A} + \overline{B})$$

$$= A \cdot \overline{AB} + B \cdot \overline{AB}$$

$$= \overline{A \cdot AB} + \overline{B \cdot AB}$$

$$= \overline{A \cdot \overline{AB}}, \overline{B \cdot \overline{AB}}$$

$$C = AB = \overline{\overline{AB}}$$

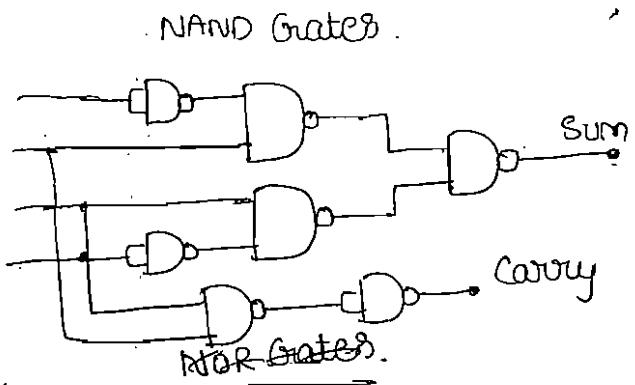

NOR logic

$$S = A \cdot \overline{B} + \overline{A} \cdot B$$

$$= A \cdot \overline{B} + \overline{A} \cdot B + A \cdot \overline{A} + B \cdot \overline{B}$$

$$= A(\overline{A} + B) + B(\overline{A} + \overline{B})$$



$$= \overline{(A+B)} \cdot \overline{(A+\overline{B})}$$

$$= \overline{(A+B)} \cdot \overline{\overline{(A+\overline{B})}}$$


$$= \overline{(A+B)} + \overline{\overline{(A+\overline{B})}}$$

$$C = AB = \overline{\overline{AB}} = \overline{AB}$$
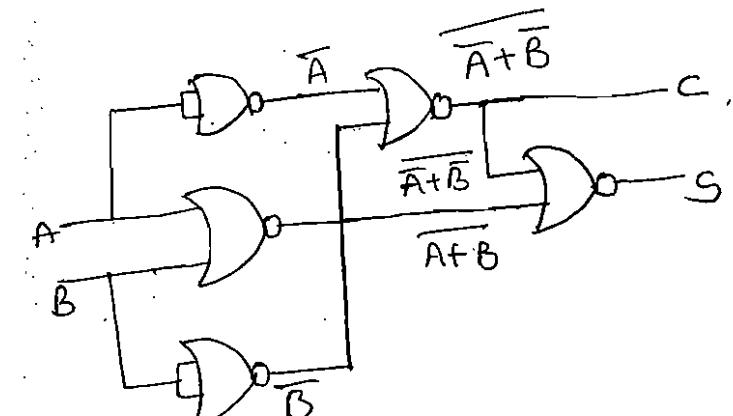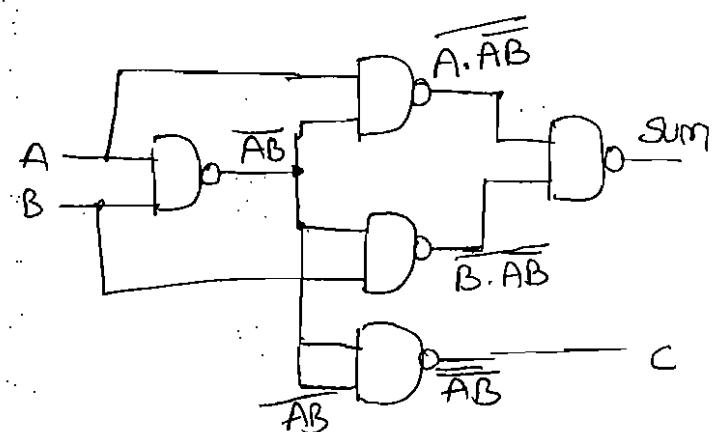
$$= \overline{\overline{A} + \overline{B}}$$




Simple logic diagram is.

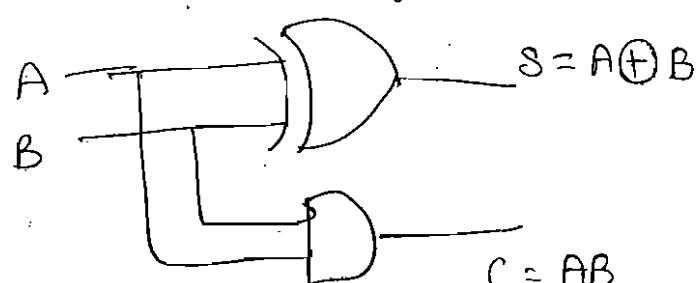
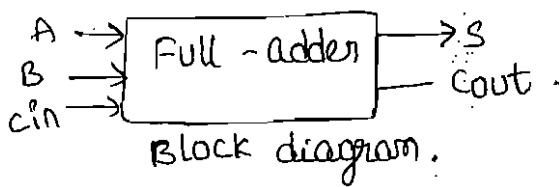
## Full adder :-

A full adder is a combinational circuit that adds two bits and a carry and outputs are sum and carry. The full-adder adds the bits A and B and the carry from the previous column called the carry-in Cin.



K-map for S.

A	B	Cin	00	01	11	10
0	0	0	0	1	1	0
1	1	0	1	0	0	1
			0	1	0	1
			1	0	0	1
			1	0	1	0
			1	1	0	1
			1	1	1	1



$$S = \overline{ABC} \cdot \text{Cin} + \overline{AB}\overline{C} \cdot \text{Cin} + A\overline{B}\overline{C} \cdot \text{Cin} + ABC \cdot \text{Cin}.$$

A	B	Cin	00	01	11	10
0	0	0	0	1	1	2
1	1	0	1	0	0	1
			0	1	0	1
			1	0	0	1
			1	1	0	1
			1	1	1	1

$$\text{Cout} = AB + BC \cdot \text{Cin} + AC \cdot \text{Cin}.$$

inputs			outputs	
A	B	Cin	S	Cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Truth table

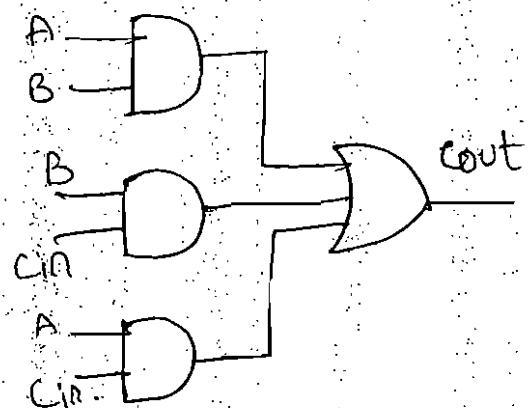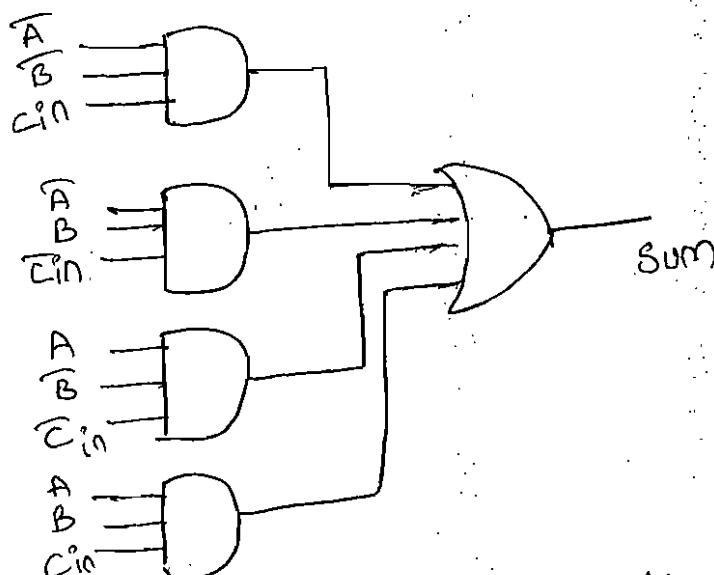

Full adder (By using two half adders and one OR gate).


$$S = \overline{ABC} \cdot \text{Cin} + \overline{AB}\overline{C} \cdot \text{Cin} + A\overline{B}\overline{C} \cdot \text{Cin} + ABC \cdot \text{Cin}$$

$$= \text{Cin} (\overline{AB} + \overline{A}\overline{B}) + \overline{\text{Cin}} (\overline{AB} + A\overline{B})$$

$$= \overline{A \oplus B} \cdot \text{Cin} + \overline{\text{Cin}} (A \oplus B)$$

$$= A \oplus B \oplus \text{Cin}.$$
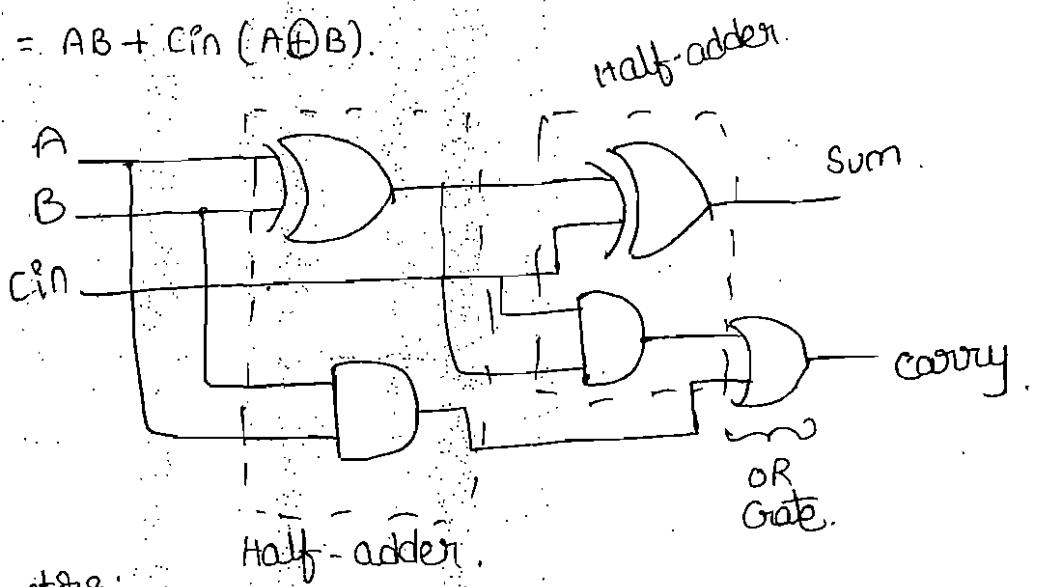
$$\begin{aligned}
 C_{out} &= \overline{ABC}_{in} + ABC_{in} + \overline{ABC}_{in} + ABC_{in} \\
 &= AB(C_{in} + \overline{C}_{in}) + \overline{ABC}_{in} + \overline{ABC}_{in} \\
 &= AB + C_{in}(\overline{AB} + A\overline{B}) \\
 &= AB + C_{in}(A \oplus B).
 \end{aligned}$$




### Subtractor:-

In subtraction, each subtrahend bit of the number is subtracted from its corresponding significant minuend bit to form a difference position.
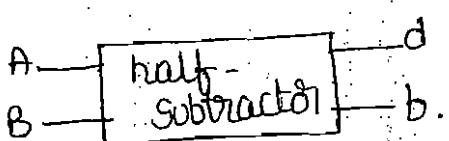
### Half-subtractor:-

A half-subtractor is a combinational circuit that subtracts one bit from the other and produces the difference. It also has an output to specify if a 1 has been borrowed.



$$= A\bar{B} + \bar{A}B$$

$$= A \oplus B$$



inputs		outputs	
A	B	d	b
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

K-map for d			
A	B	0	1
0	0	0	1
1	0	1	0

$$d = A\bar{B} + \bar{A}B$$

K-map for b			
A	B	0	1
0	0	0	1
1	0	1	0

$$b = \bar{A}B$$

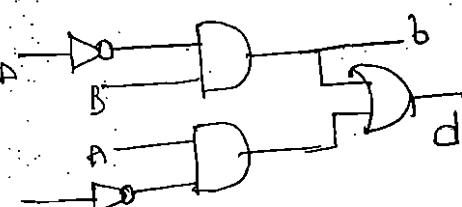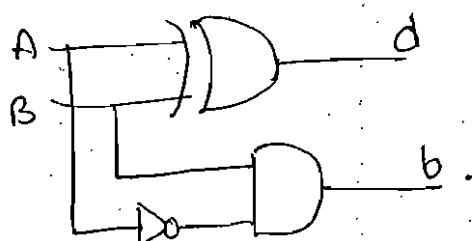

Logic diagrams of a half-subtractor.

### NAND logic :-

$$d = A\bar{B} + \bar{A}B$$

$$= AB + \bar{A}\bar{B} + A\bar{A} + B\bar{B}$$

$$= A(\bar{A} + \bar{B}) + B(\bar{A} + \bar{B})$$

$$= \underline{\underline{A \cdot \bar{A}B + B \cdot \bar{A}B}}$$


$$= \underline{\underline{A \cdot \bar{A}B \cdot B \cdot \bar{A}B}}$$

$$b = \bar{A}B$$

$$= \bar{A}B + B\bar{B}$$

$$= B(\bar{A} + \bar{B})$$

$$= B(\bar{A}B)$$

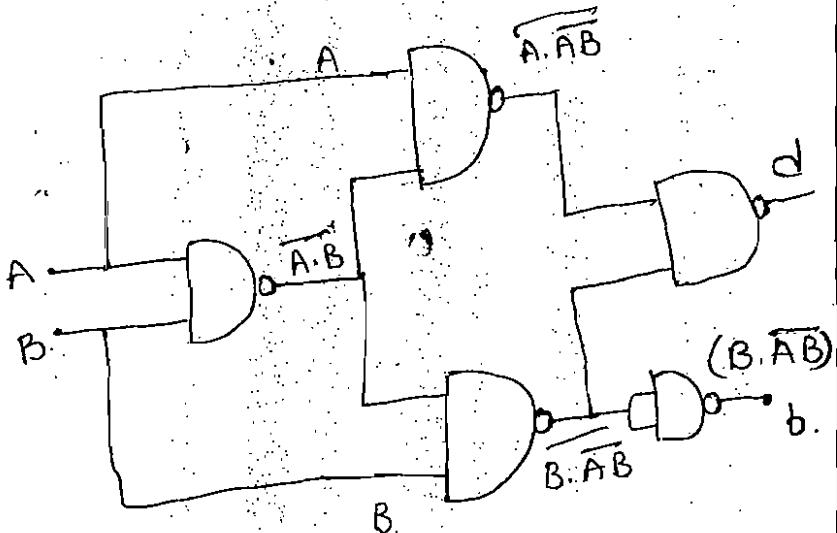

### NOR logic

$$d = A\bar{B} + \bar{A}B$$

$$= \bar{A}\bar{B} + \bar{A}\bar{B} + B\bar{B} + A\bar{A}$$

$$= \underline{\underline{B(A+B) + \bar{A}(A+B)}}$$


$$= \underline{\underline{B+A+B + A+\bar{A}+B}}$$

$$b = \bar{A}B$$

$$= \bar{A}B + A\bar{A}$$

$$= \underline{\underline{A(A+B)}}$$

$$= \underline{\underline{A + (A+B)}}$$

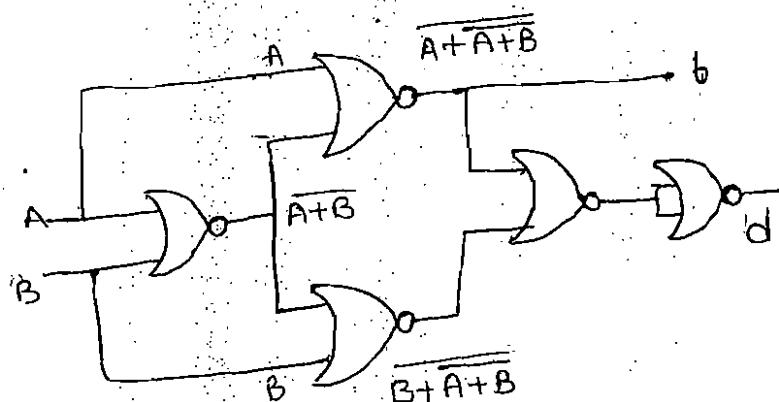

### Full - Subtractor :-

The half-subtractor can be used only for LSB subtraction. If there is a borrow during the subtraction of the LSBs, it affects the subtraction in the next higher column. the subtractend bit is subtracted from the minuend bit, considering the borrow from that column used for the subtraction in the preceding column.

In full subtractor the inputs are A, B, borrow in  $b_i$ , and outputs are difference bit (d) and borrow ( $b$ ).

inputs				
A	B	$b_i$	d	b
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

K-map for difference

$Bb_i$	00	01	11	10
A	0	0	1	1
1	1	0	1	0


$$\begin{aligned}
 d &= \bar{A}\bar{B}b_i + \bar{A}B\bar{b}_i + A\bar{B}\bar{b}_i + ABb_i \\
 &= b_i(AB + \bar{A}\bar{B}) + \bar{b}_i(\bar{A}B + A\bar{B}) \\
 &= b_i(\overline{A \oplus B}) + \bar{b}_i(A \oplus B) \\
 &= A \oplus B \oplus b_i
 \end{aligned}$$

K-map for borrow.

$Bb_i$	00	01	11	10
A	0	0	1	1
1	1	0	1	0

$$\begin{aligned}
 b &= \bar{A}\bar{B}b_i + \bar{A}B\bar{b}_i + A\bar{B}b_i + AB\bar{b}_i \\
 &= \bar{A}B(b_i + \bar{b}_i) + (AB + \bar{A}\bar{B})b_i \\
 &= \bar{A}B + (\overline{A \oplus B})b_i
 \end{aligned}$$

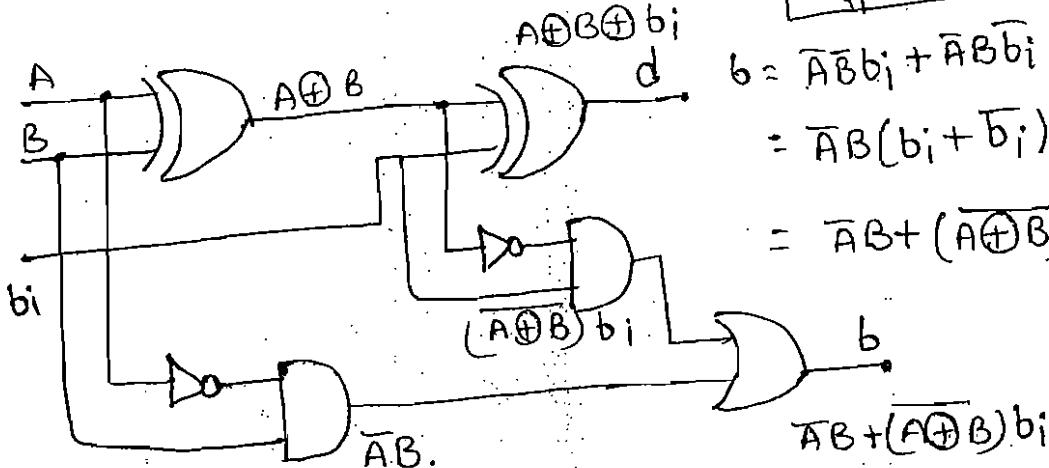
full-subtractor by using  
two half-subtractor



NAND logic:-

$$d = A \oplus B \oplus b_i = \overline{(A \oplus B) \oplus b_i} = \overline{(A \oplus B)} \cdot \overline{(A \oplus B)} \cdot b_i \cdot \overline{(A \oplus B)} \cdot b_i$$

$$\begin{aligned}
 b &= \bar{A}B + b_i \cdot \overline{(A \oplus B)} = \overline{\bar{A}B + b_i \cdot (A \oplus B)} \\
 &= \overline{\bar{A}B \cdot b_i \cdot (A \oplus B)} = \overline{\bar{A}B} \cdot \overline{b_i} \cdot \overline{(A \oplus B)} \\
 &= B \cdot \overline{A + B} \cdot b_i \cdot \overline{(b_i + (A \oplus B))} \\
 &= B \cdot \overline{A + B} \cdot b_i \cdot [b_i \cdot \overline{(A \oplus B)}]
 \end{aligned}$$

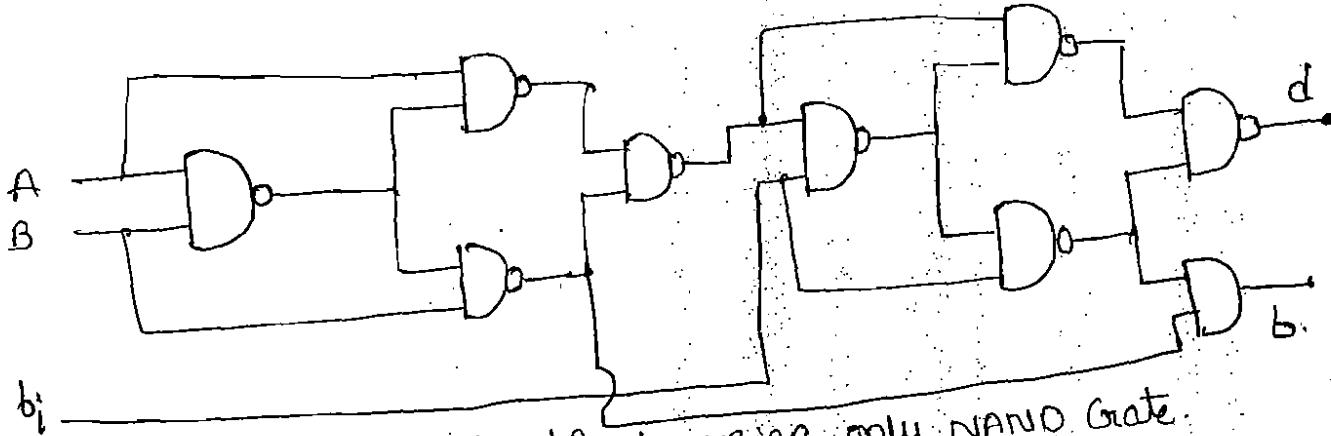

full subtractor by using only NOR Gate.

NOR logic.

$$d = \overline{A \oplus B \oplus b_i}$$

$$= \overline{(A \oplus B) b_i} + \overline{(A \oplus B)} \overline{b_i}$$

$$= [ \overline{(A \oplus B)} + \overline{(A \oplus B)} \overline{b_i} ] [ b_i + \overline{(A \oplus B)} \overline{b_i} ]$$


$$= \overline{(A \oplus B)} + \overline{\overline{(A \oplus B)} + b_i} + b_i + \overline{(A \oplus B)} + \overline{b_i}$$

$$= \overline{(A \oplus B)} + \overline{\overline{(A \oplus B)} + b_i} + \overline{b_i} + \overline{(A \oplus B)} + \overline{b_i}$$

$$b = \overline{A} \overline{B} + b_i (\overline{A \oplus B})$$

$$= \overline{A} (A + B) + (\overline{A \oplus B}) [ A \oplus B + b_i ]$$
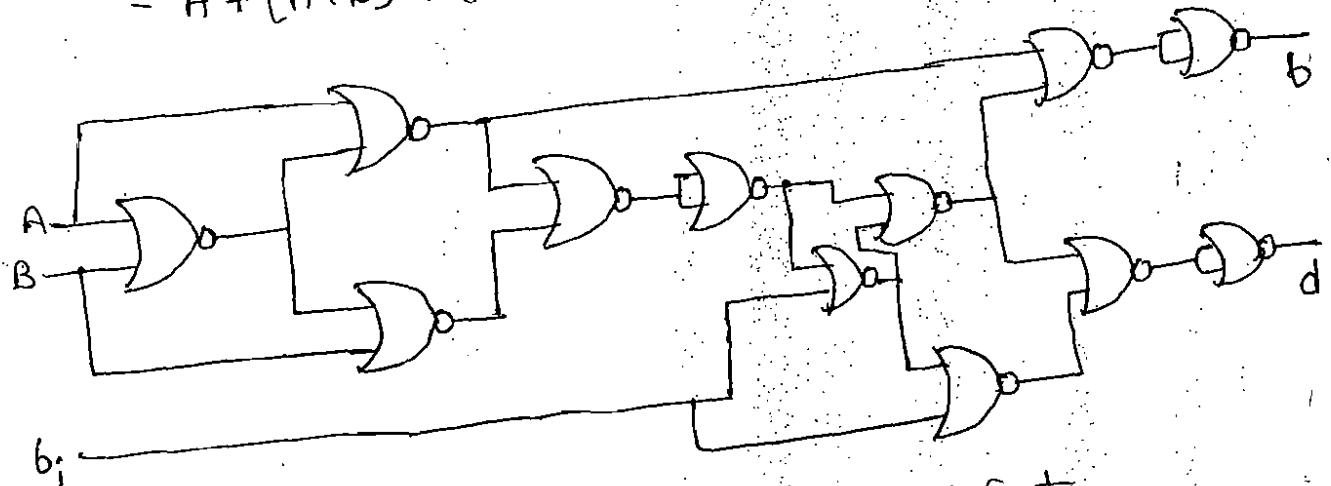
$$= A + (\overline{A} + B) + (\overline{A \oplus B}) + (A \oplus B) + b_i$$




Full subtractor by using only NOR Gate

## Applications of full adders:-
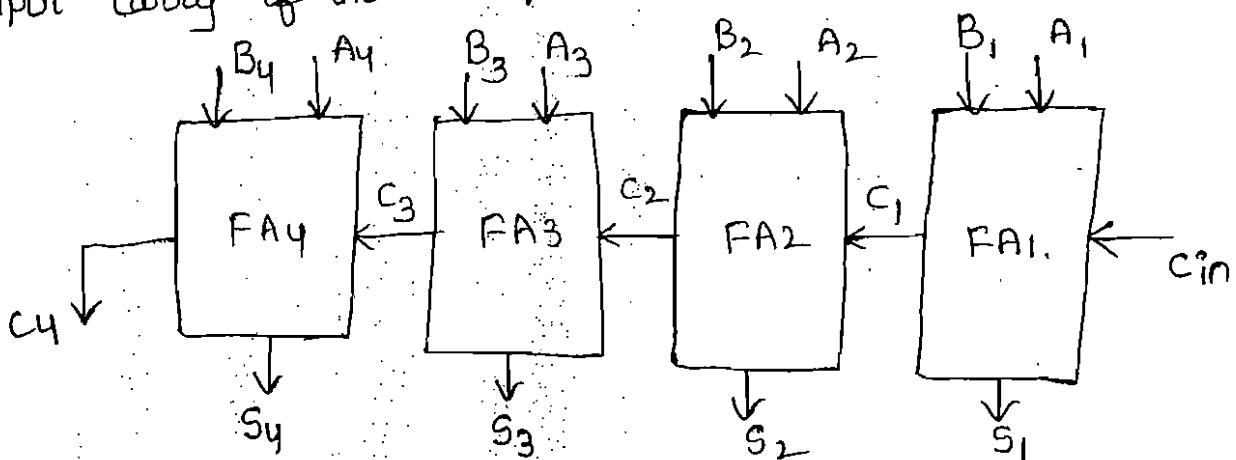
### Binary parallel adder:-

A Binary parallel adder is a digital circuit that adds two binary numbers in parallel form and produces the arithmetic sum of those numbers in parallel form. It consists of full adders connected in a chain, with the output carry from each full-adder connected to the input carry of the next full-adder in the chain.




Logic diagram of 4-bit binary parallel adder.

The inter-connection of full-adder (FA) circuits to provide a 4-bit parallel adder. The augend bits of A and addend bits of B are designated by subscript numbers from right to left, with subscript 1 denoting the lower-order bit. The input carry to the adder is  $c_{in}$  and the output carry is  $c_4$ . The S outputs generate the required sum bits. When the 4-bit full adder circuit is enclosed within an IC package, it has four terminals for the augend bits, four terminals for the addend bits, four terminals for the sum bits, and two input terminals for the input and output carries.

The parallel adder in which the carry-out of each full adder is the carry-in to the next most significant adder is called a ripple carry adder. In the parallel adder, the carry-out of each stage is connected to the carry-in of the next stage. The sum and carry out bits of any stage cannot be produced, until some time after the carry-in of that stage occurs. This is due to the propagation delays in the logic circuitry, which lead to a time delay in the addition process.
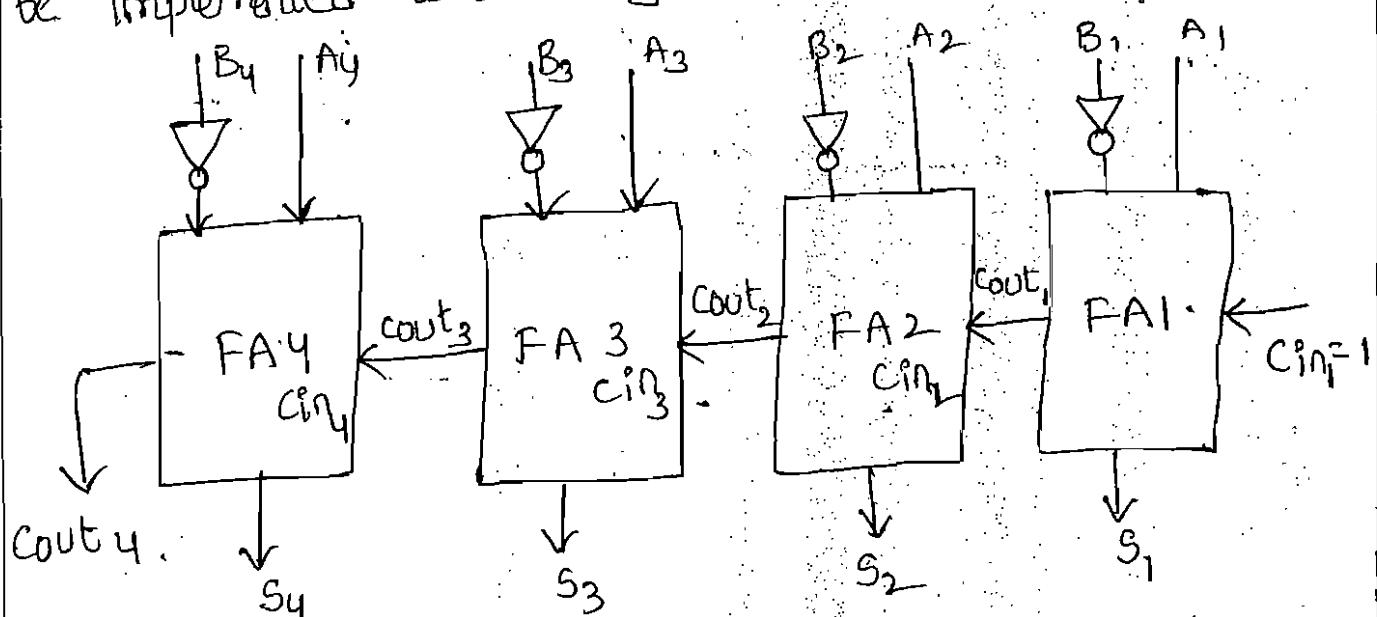
#### 4-bit parallel subtractor:-

The subtraction of binary numbers can be carried out most conveniently by means of complements. The subtraction  $A - B$  can be done by taking the 2's complement of  $B$  and adding it to  $A$ . The 2's complement can be obtained by taking the 1's complement and adding 1 to the least significant pair of bits. The 1's complement can be implemented with not gate (inverters).



Logic diagram of 4-bit parallel subtractor.

## Binary adder - Subtractor :-

The addition and subtraction operations are combined into one circuit with one common binary adder. This is done by including an X-OR gate with each full adder. The M mode input controls the operation.


→ when  $M=0$ , the circuit is an adder.

→ when  $M=1$ , the circuit is an subtractor.

Each XOR gate receives input M and one of the inputs of B.

→ when  $M=0$ ,  $B \oplus 0 = B$ . The full adder receives the value of B, the input carry is '0' and the circuit performs  $A+B$ .

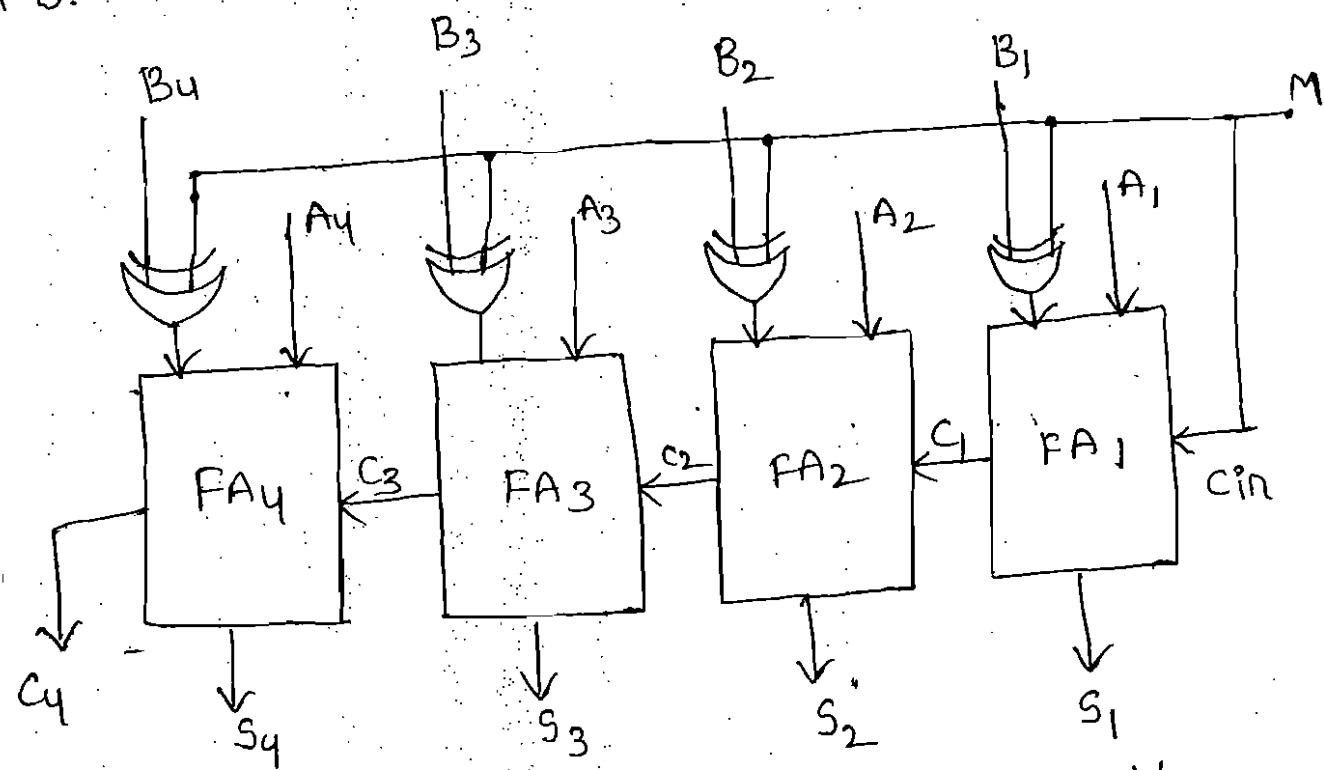→ when  $M=1$ ,  $B \oplus 1 = \bar{B}$ . The full adder receives the value of  $\bar{B}$ , the input carry is '1' and the circuit performs  $A-\bar{B}$ .




Logic diagram of a 4-bit binary - adder - subtractor.
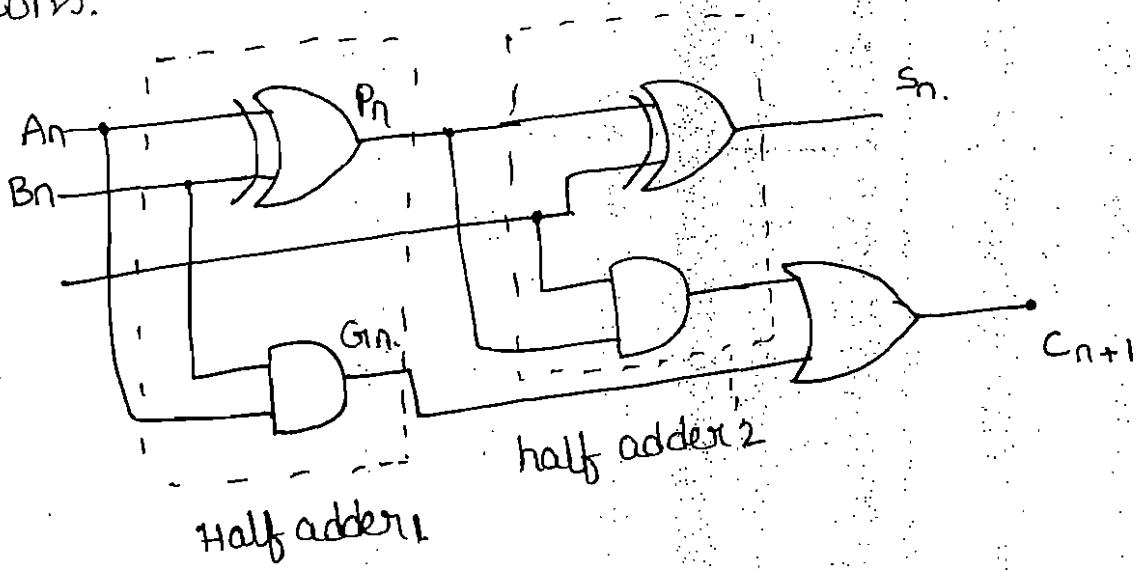
## LOOK-A-HEAD-CARRY ADDER :-

The parallel adder, the speed with which an addition can be performed is governed by the time required for the carries to propagate or ripple through all of the stages of the adder.

The look-ahead-carry adder speeds up the process by eliminating this ripple carry delay. It examines all the input bits simultaneously. The method of speeding up the process is based on the two additional functions of the full adder, called the carry generate and carry propagate functions.



### carry generate :-

consider one full adder stage,  $n^{th}$  stage of a parallel adder. carry is generated only if both the input bits are 1, that is, if both the bits A and B are 1, or whether the input carry  $c_{in}$  is a 0 or a 1. If  $G_i$  is a carry-generation function.

$$G_i = A \cdot B$$

The present bit as the  $n$ th bit, then  $G_1$  rewrite as a

$$G_n = A_n \cdot B_n.$$

carry propagation:

A carry is propagated if any one of the two input bits  $A$  &  $B$  are 1, a carry will never be propagated. On the other hand, if both  $A$  and  $B$  are 1, then it will not propagate the carry but will generate the carry.

If  $P$  is taken as a

$$P = A \oplus B.$$

The present bit as the  $n$ th bit, then  $P$  rewrite as a

$$P_n = A_n \oplus B_n.$$

For the final sum and carry outputs of the  $n$ th stage,

$$S_n = P_n \oplus C_n$$

$$( \because P_n = A_n \oplus B_n )$$

$$\begin{aligned}C_{n+1} &= C_{n+1} = G_n + P_n C_n \\&= A_n \cdot B_n + P_n C_n \\&= A_n \cdot B_n + (A_n \oplus B_n) C_n.\end{aligned}$$

Based on these, the expression for the carry-outs of various full-adders are

$$\begin{aligned}n=1, \quad C_1 &= G_0 + P_0 C_0 \\&= G_0 + (A_0 \oplus B_0) C_0 \\&= A_0 \cdot B_0 + (A_0 \oplus B_0) C_0.\end{aligned}$$

$n=2$

$$C_2 = G_{11} + P_1 \cdot C_1 = G_{11} + P_1 \cdot G_{10} + P_1 \cdot P_0 \cdot C_0$$

$n=3$

$$C_3 = G_{12} + P_2 \cdot C_2 = G_{12} + P_2 \cdot G_{11} + P_2 \cdot P_1 \cdot G_{10} + P_2 \cdot P_1 \cdot P_0 \cdot C_0$$

$n=4$


$$C_4 = G_{13} + P_3 \cdot C_3 = G_{13} + P_3 \cdot G_{12} + P_3 \cdot P_2 \cdot G_{11} + P_3 \cdot P_2 \cdot P_1 \cdot G_{10} + P_3 \cdot P_2 \cdot P_1 \cdot P_0 \cdot C_0$$

The general expression for  $n$ -stages.


$$C_n = G_{n-1} + P_{n-1} \cdot C_{n-1}$$

$$= G_{n-1} + P_{n-1} \cdot G_{n-2} + P_{n-1} \cdot P_{n-2} \cdot G_{n-3} + \dots + P_{n-1} \cdot P_0 \cdot C_0$$
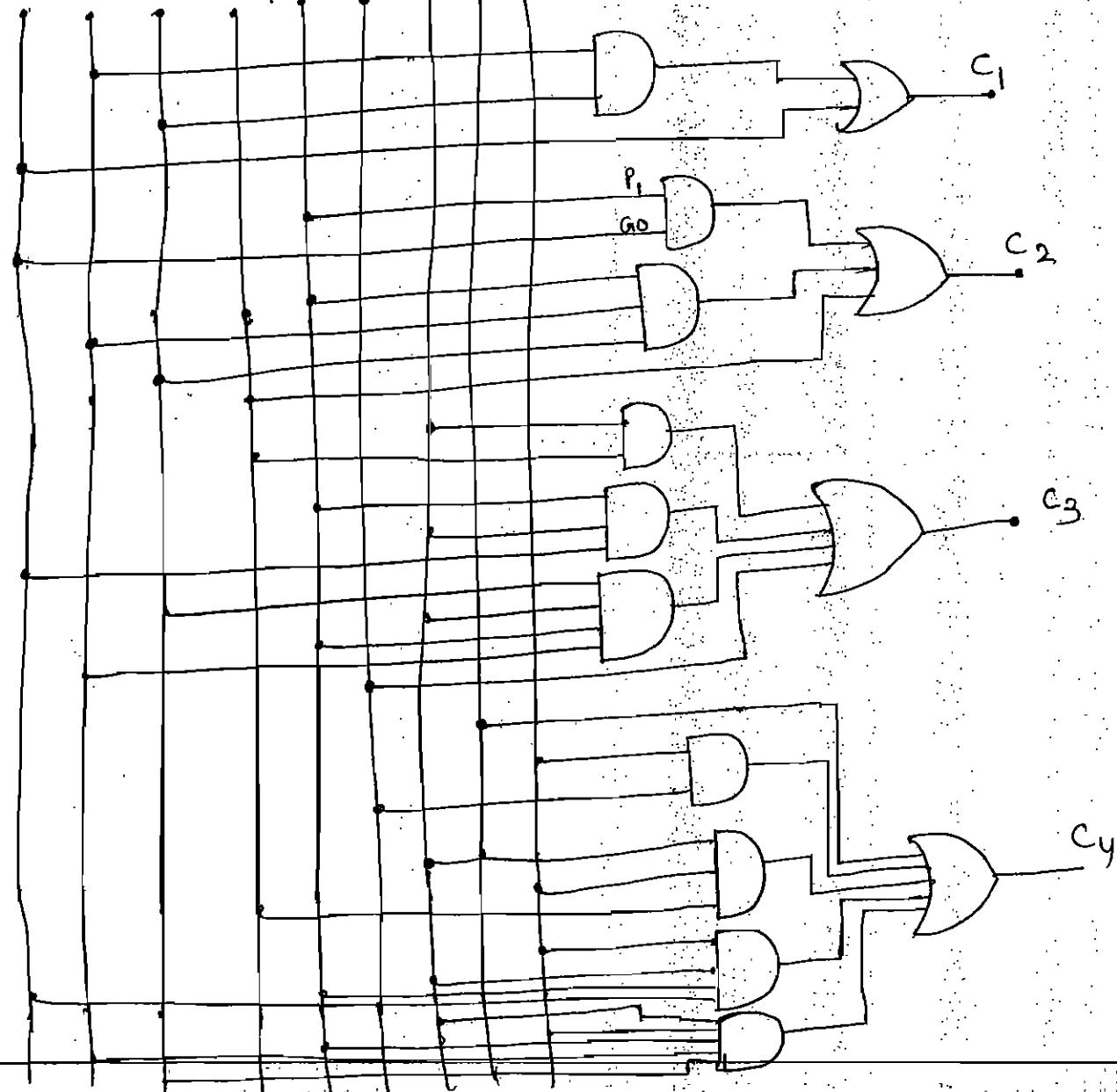
$$G_0 \quad P_0 \quad C_0 \quad G_{11} \quad P_1 \quad G_{12} \quad P_2 \quad G_{13} \quad P_3$$




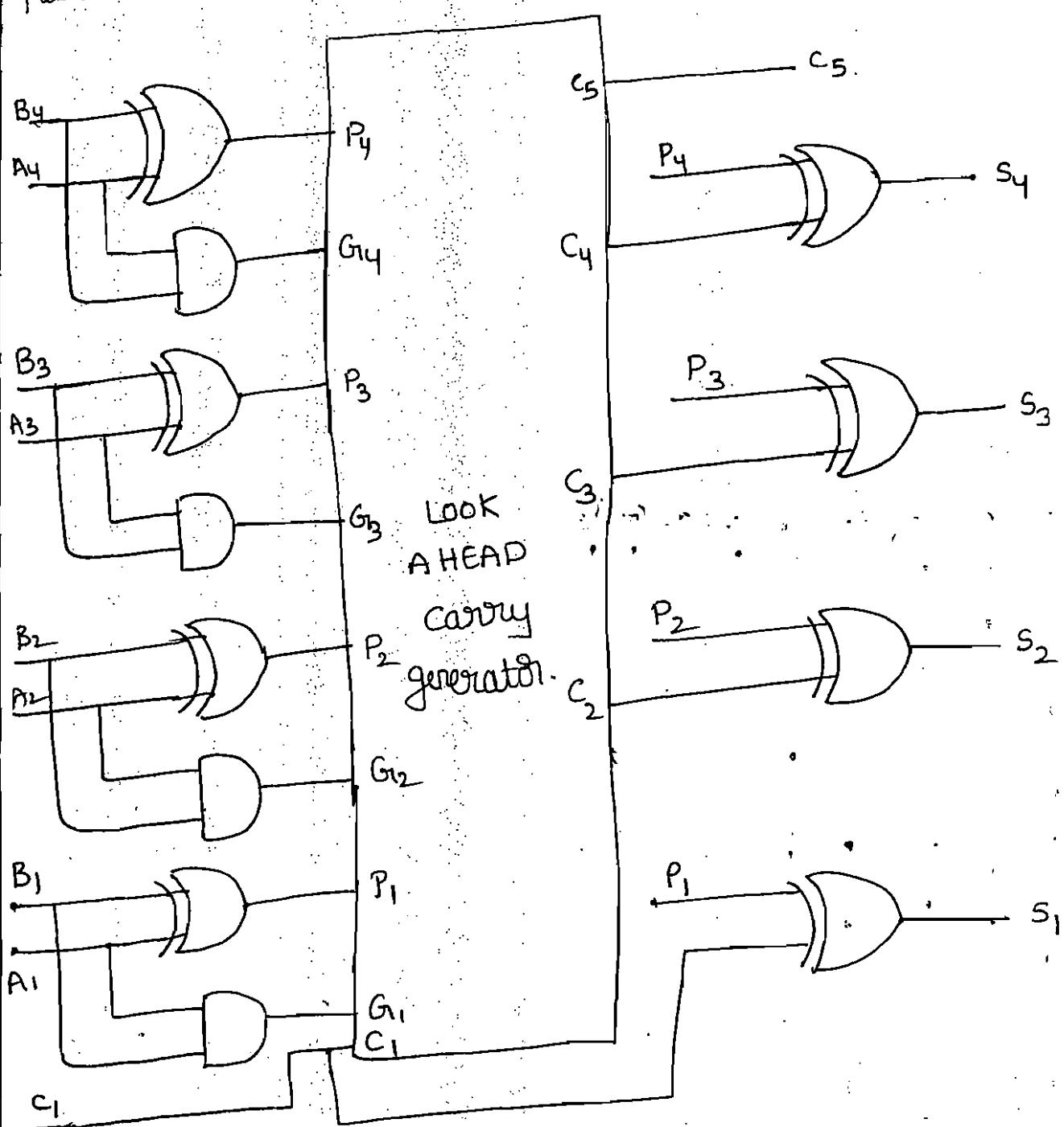The block diagram of a 4-stage look-ahead carry parallel adder is shown in the below figure.



Basic logic diagram of a 4-bit look-Ahead carry adder.

## BCD Adder :-

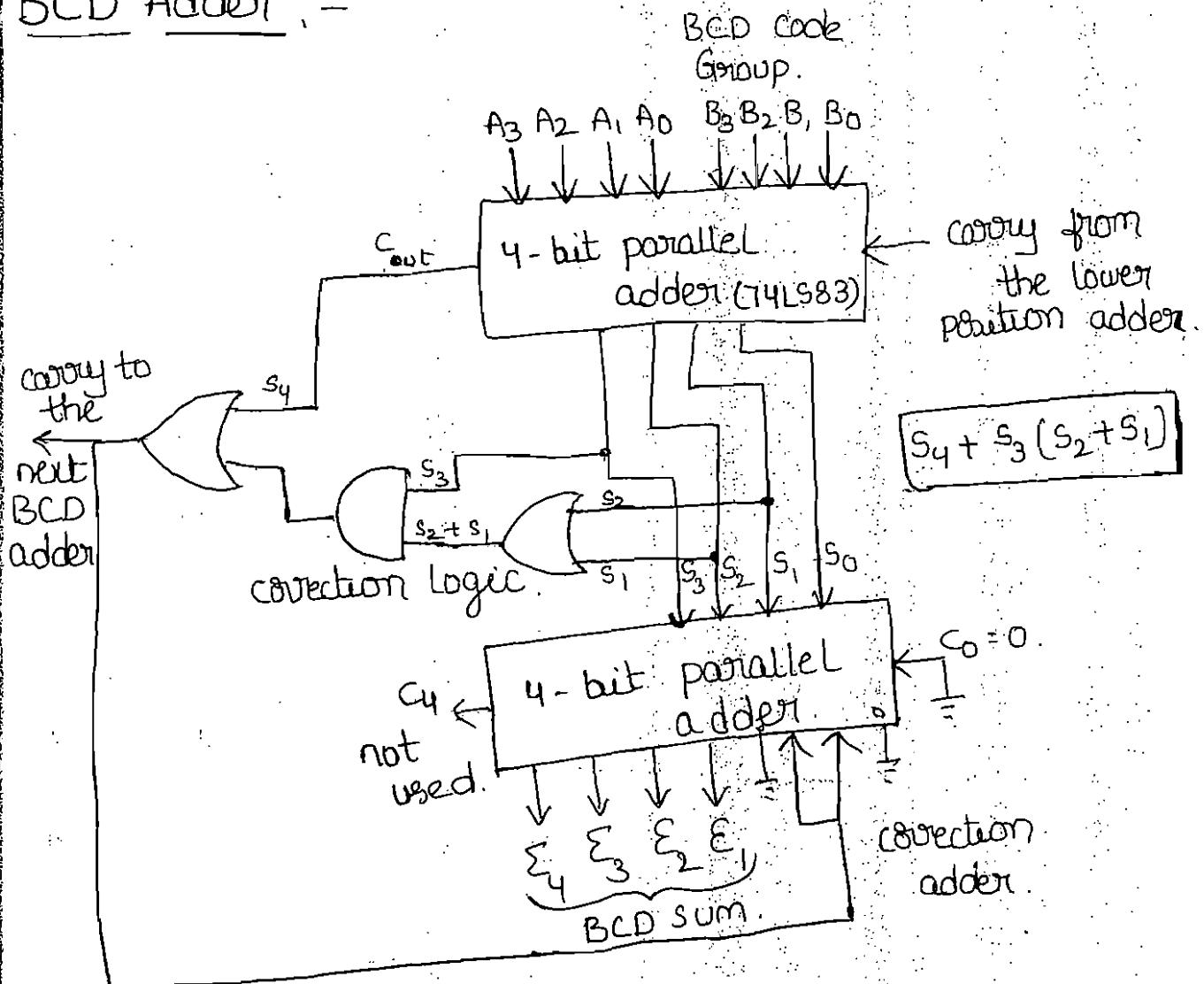

- In BCD adder, Add the 4-bit BCD code groups for each decimal digit position using binary binary addition.
- For those positions where the sum is 9 or less, the sum is in proper BCD form and no correction is needed.
- where the sum of two digits is greater than 9, a correction of 0110 should be added to that sum, to produce the proper BCD result.
- In above figure 4-bit parallel adder (using IC 74LS83). The two BCD groups  $A_3, A_2, A_1, A_0$  and  $B_3, B_2, B_1, B_0$  are applied to a 4-bit parallel adder.

The adder output will be  $C_4, S_3, S_2, S_1, S_0$ . where  $C_4$  is taken as a  $S_4$ .

→ when both the inputs are 1001. The sum output  $S_4, S_3, S_2, S_1, S_0$  can range from 00000 to 10010.

→ The circuitry for a BCD adder must include the logic needed to detect whenever the sum is greater than 01001.

$S_4$	$S_3$	$S_2$	$S_1$	$S_0$	Decimal number
0	1	0	1	0	10
0	1	0	1	1	11
0	1	1	0	0	12
0	1	1	0	1	13
0	1	1	1	0	14
0	1	1	1	1	15
1	0	0	0	0	16
1	0	0	0	1	17
1	0	0	1	0	18

→ In above Table shows the cases for greater than 1001.

The sum will be high → whenever  $S_4 = 1$ ,

→ whenever  $S_3 = 1$  and either  $S_2$  &  $S_1$  or both are 1.

$$\text{Then } X = S_4 + S_3(S_2 + S_1)$$

whenever  $X = 1$ , it is necessary to add the 0110 to the sum bits.

The circuit consists of three basic parts. The BCD code groups  $A_3, A_2, A, A_0$  and  $B_3, B_2, B, B_0$  are added together in upper 4-bit parallel adder to produce the sum  $s_4 s_3 s_2 s_1 s_0$ . The logic gates shown implement the expression for  $x$ . The lower 4-bit adder will add the carry correction 0110 to the sum bits only when  $x=1$ , producing final BCD sum output represented by  $E_3 E_2 E_1 E_0$ .

when  $x=0$ , there is no carry and no correction.

In such cases  $E_3 E_2 E_1 E_0 = s_3 s_2 s_1 s_0$ . Two or more BCD adders can be connected in cascade when two or more digit decimal numbers are to be added. The carry-out of the first BCD adder is connected as the carry-in of the second BCD adder.

### Excess-3 Adder :-


→ In excess-3 addition.

1. Add two xs-3 code groups.

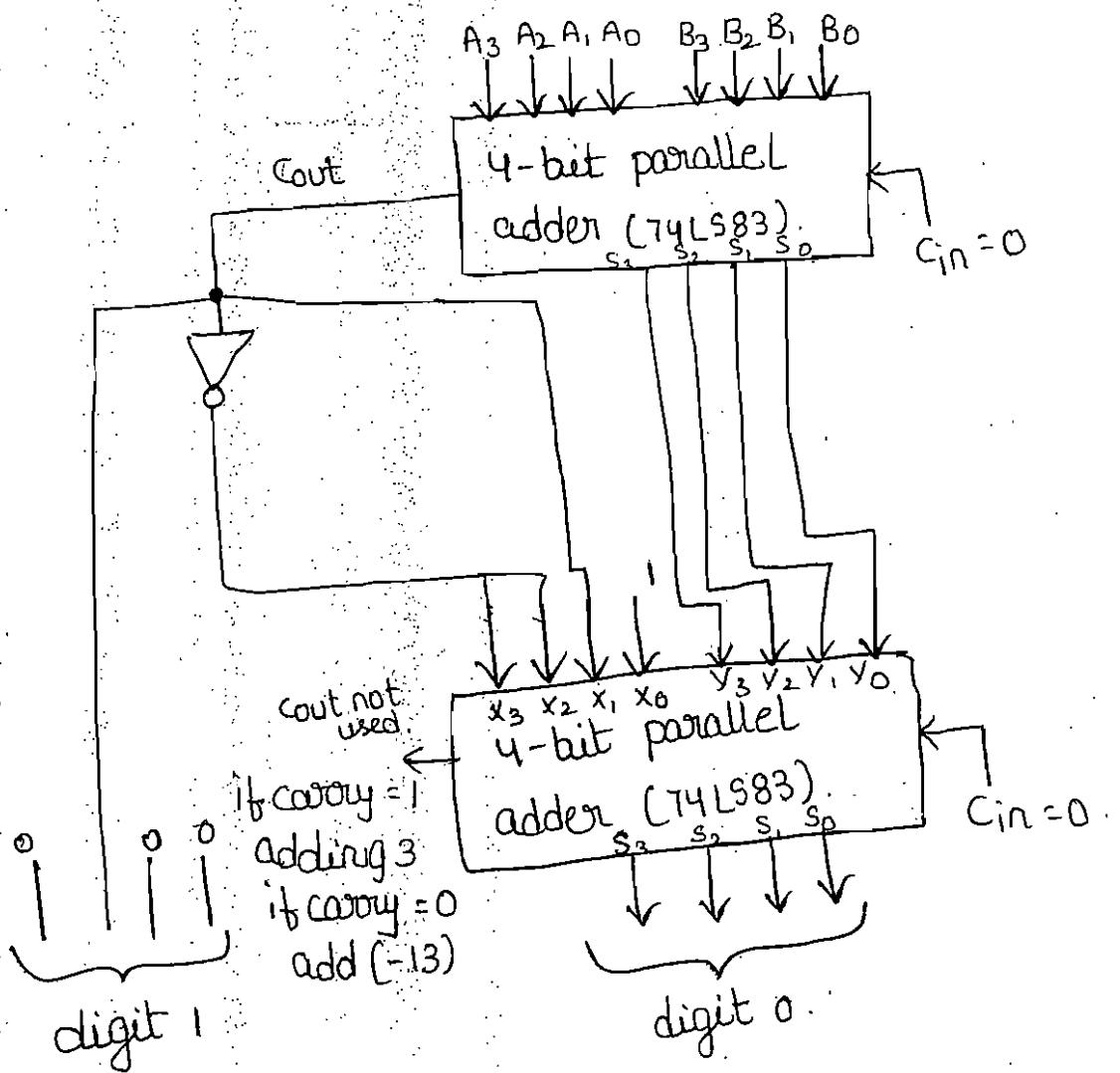2. If carry = 1 add 0011

If carry = 0 subtract 0011, & add 1101 (13 in decimal).

In figure The augend ( $A_3, A_2, A, A_0$ ) and addend ( $B_3, B_2, B, B_0$ ) in xs-3 added using the 4-bit parallel adder. If the carry is a 1, then 0011 is added to the sum bits  $s_3 s_2 s_1 s_0$  of the upper adder in the lower 4-bit parallel adder. If the carry is a '0' then 1101 is added to the sum bits.




The final Answer in XS-3 form.

### Multiplexers (data selector).

multiplexing means sharing. A multiplexer or data selector is a logic circuit that accepts several data inputs and allows only one of them at a time to get through to the output. The routing of the desired data inputs to the output is controlled by SELECT inputs. Normally there are  $2^n$  input lines and  $n$  select lines and one output.
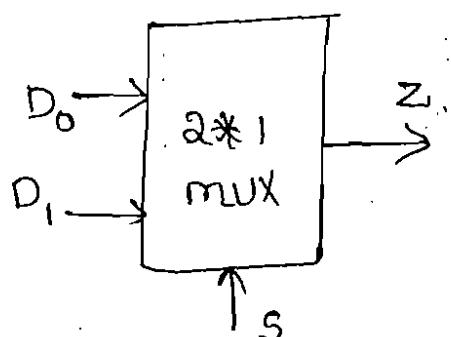
## Basic 2-input multiplexer :-


In 2-input multiplexer have 2 inputs they are  $D_0$  and  $D_1$ . and one select line  $S$ , and output is  $Z$ .



Block diagram.

S	Z
0	$D_0$
1	$D_1$

Truth table.

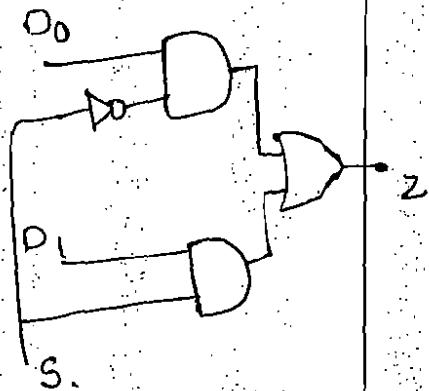

$$Z = \overline{S}D_0 + SD_1$$

logic diagram


The logic levels applied to the  $S$  inputs determines which AND gate is enabled. So that its data input passes through the OR gate to the output.

when  $S = 0$ , AND gate 1 is enabled and AND gate 2 is disabled,  $S_0, Z = D_0$

$S = 1$ , AND gate 2 is enabled and AND gate 1 is disabled,  $S_0, Z = D_1$ .


## Basic 4-input multiplexer :-

Block diagram

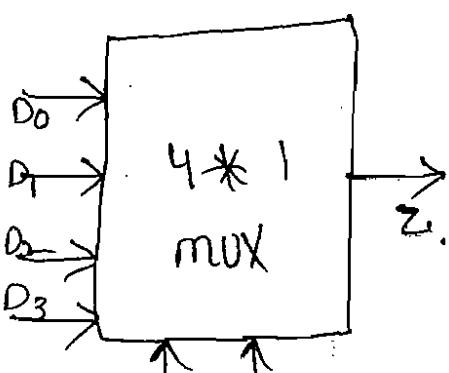

Truth table


$S_1$	$S_0$	Z
0	0	$D_0$
0	1	$D_1$
1	0	$D_2$
1	1	$D_3$

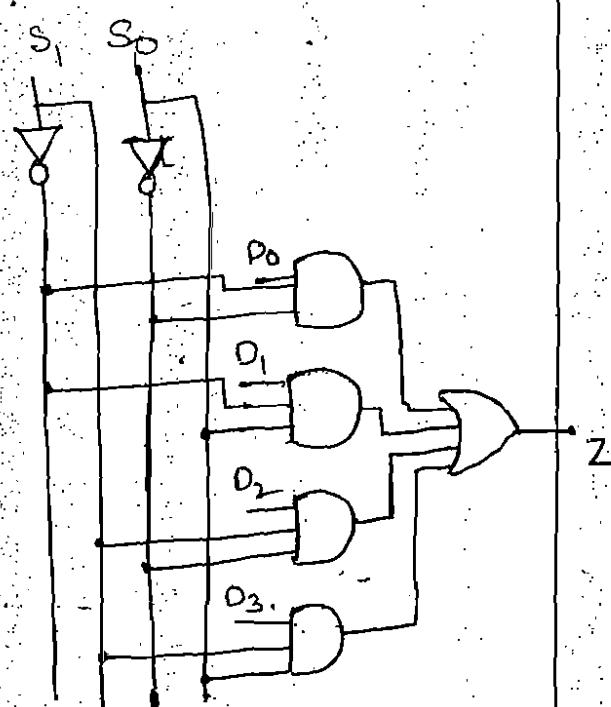

$$Z = \overline{S_1}\overline{S_0}D_0 + \overline{S_1}S_0D_1 + S_1\overline{S_0}D_2 + S_1S_0D_3$$

The 16-input multiplexor from Two 8-input multiplexors:-


To use two 8-inputs multiplexors to get a 16-inputs multiplexor, one OR gate and one inverter are also required. The four select inputs  $S_3, S_2, S_1$ , and  $S_0$  and will select one of the 16 inputs to pass through to  $X$ . The  $S_3$  input determines which multiplexer is enabled. When  $S_3 = 0$ , the left multiplexer is enabled and  $S_2, S_1$ , and  $S_0$  inputs determine which of its data inputs will appear at its output and pass through the OR gate to  $X$ . When  $S_3 = 1$ , the right multiplexer is enabled and  $S_2, S_1$ , and  $S_0$  inputs select one of its data inputs for passage to output  $X$ .

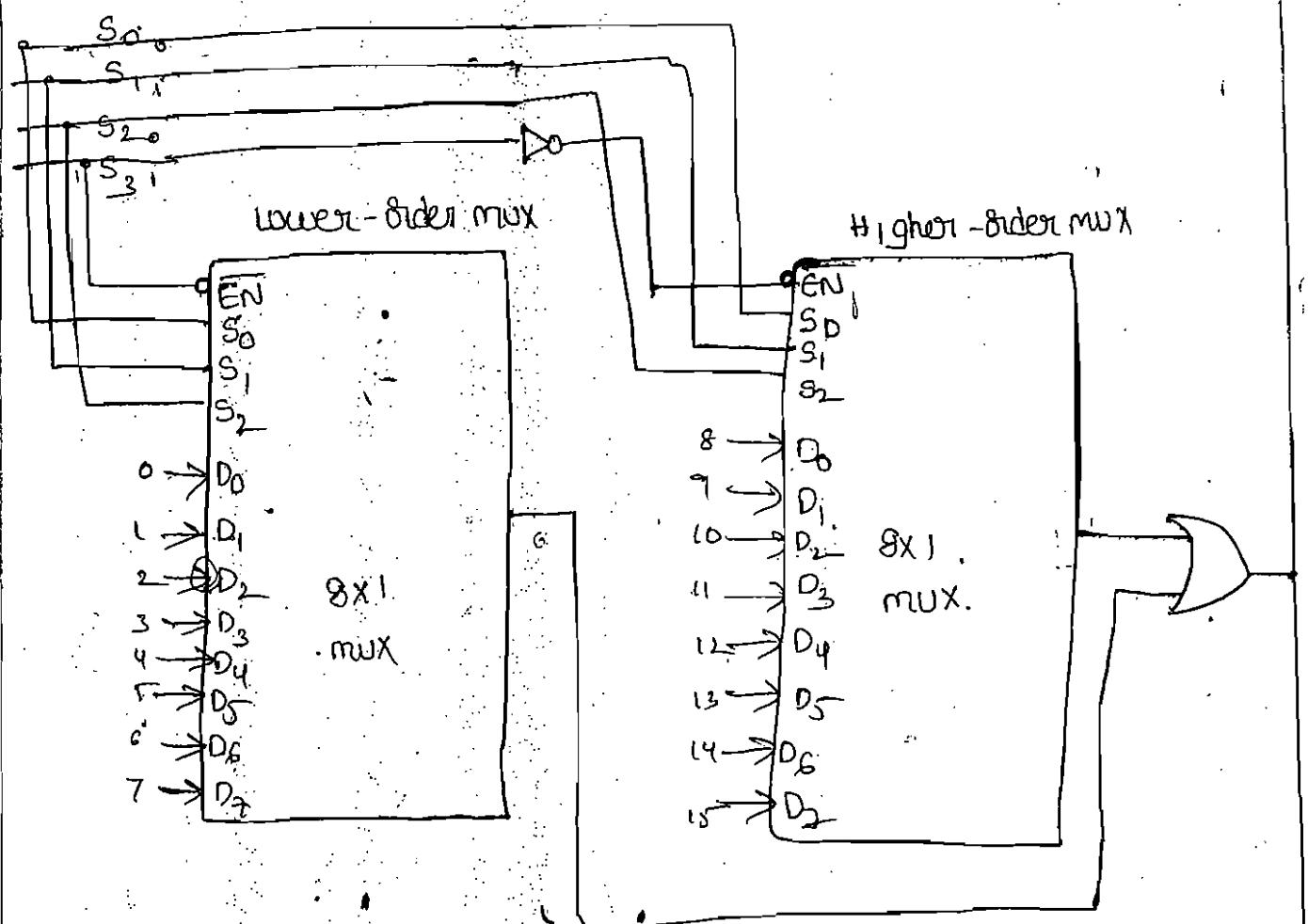

Logic diagram for cascading of two  $8 \times 1$  MUX to get  $16 \times 1$

Design of a  $32 \times 1$  mux using two  $16 \times 1$  muxes and one  $2 \times 1$  mux:

To obtain a  $32 \times 1$  mux using two  $16 \times 1$  muxes and one  $2 \times 1$  mux. A  $32 \times 1$  mux has 32 data inputs so it requires five data select lines. Since a  $16 \times 1$  mux has only four data select lines, the inputs B,C,D,E are connected to the data select lines of the both  $16 \times 1$  muxes and the most significant input A is connected to the single data select line of the  $2 \times 1$  mux. For the values of  $BCDE = 0000$  inputs 0 to 15 will appear at the input terminals 0 of the  $2:1$  mux through the output  $F_1$  of the first  $16 \times 1$  mux and inputs 16 to 31 will appear at the input terminal 1 of the  $2:1$  mux through the output  $F_2$  of the second  $16 \times 1$  mux. For  $A=0$ , output  $F=F_1$ , for  $A=1$ , output  $F=F_2$ .

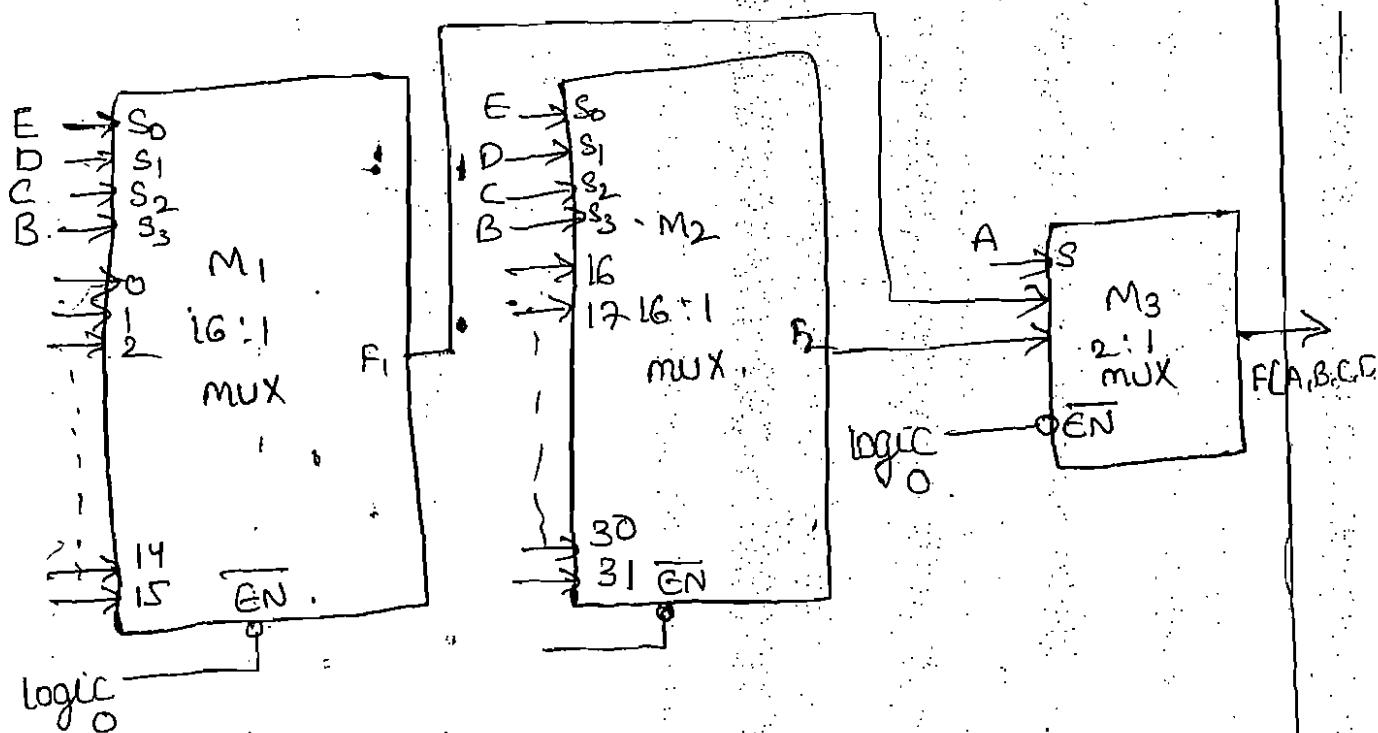


## DEMULTIPLEXERS

A demultiplexer performs the reverse operation; it takes a single input and distributes it over several outputs. so a demultiplexer is also called as a "data distributor". since it transmits the same data to different destinations. A demultiplexer is a 1-to-N device.
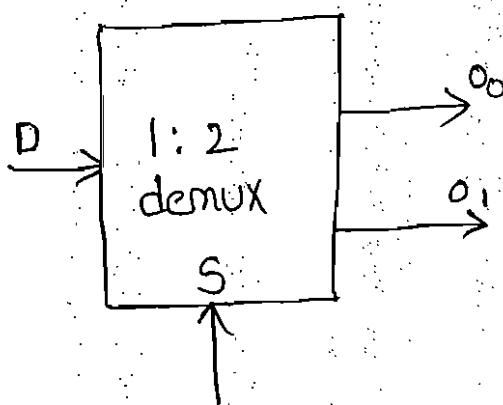
### 1-line to 2-line demultiplexer


The input data line goes to all of the AND gates. The select line enables only one gate at a time, and the data appearing on the input line will pass through the selected gate to the associated output lines.



Block diagram

S	O <sub>0</sub>	O <sub>1</sub>
0	0	D
1	D	0

Truth table

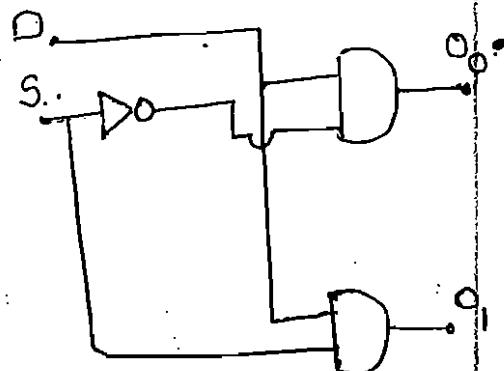

$$O_0 = DS$$


$$O_1 = DS$$

logic diagram

### 1-line to 4-line demultiplexer

S <sub>1</sub>	S <sub>0</sub>	O <sub>3</sub>	O <sub>2</sub>	O <sub>1</sub>	O <sub>0</sub>
0	0	0	0	0	D
0	1	0	0	D	0
1	0	0	D	0	0
1	1	D	0	0	0

Truth table

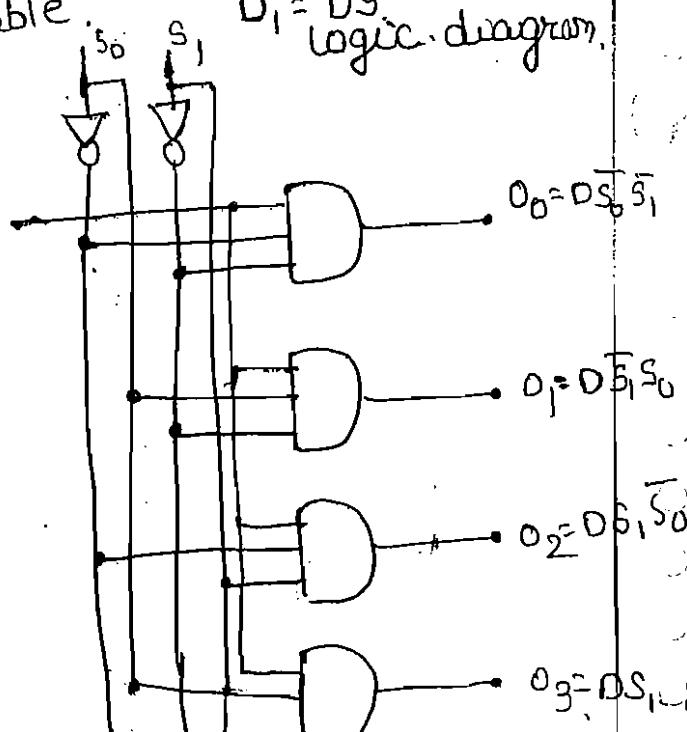


logic diagram


1-line to 8-line demultiplexer:-

$S_2$	$S_1$	$S_0$	$O_7$	$O_6$	$O_5$	$O_4$	$O_3$	$O_2$	$O_1$	$O_0$
0	0	0	0	0	0	0	0	0	0	D
0	0	1	0	0	0	0	0	0	D	0
0	1	0	0	0	0	0	0	D	0	0
0	1	1	0	0	0	0	D	0	0	0
1	0	0	0	0	D	0	0	0	0	0
1	0	1	0	0	D	0	0	0	0	0
1	1	0	0	D	0	0	0	0	0	0
1	1	1	D	0	0	0	0	0	0	0

Truth table.

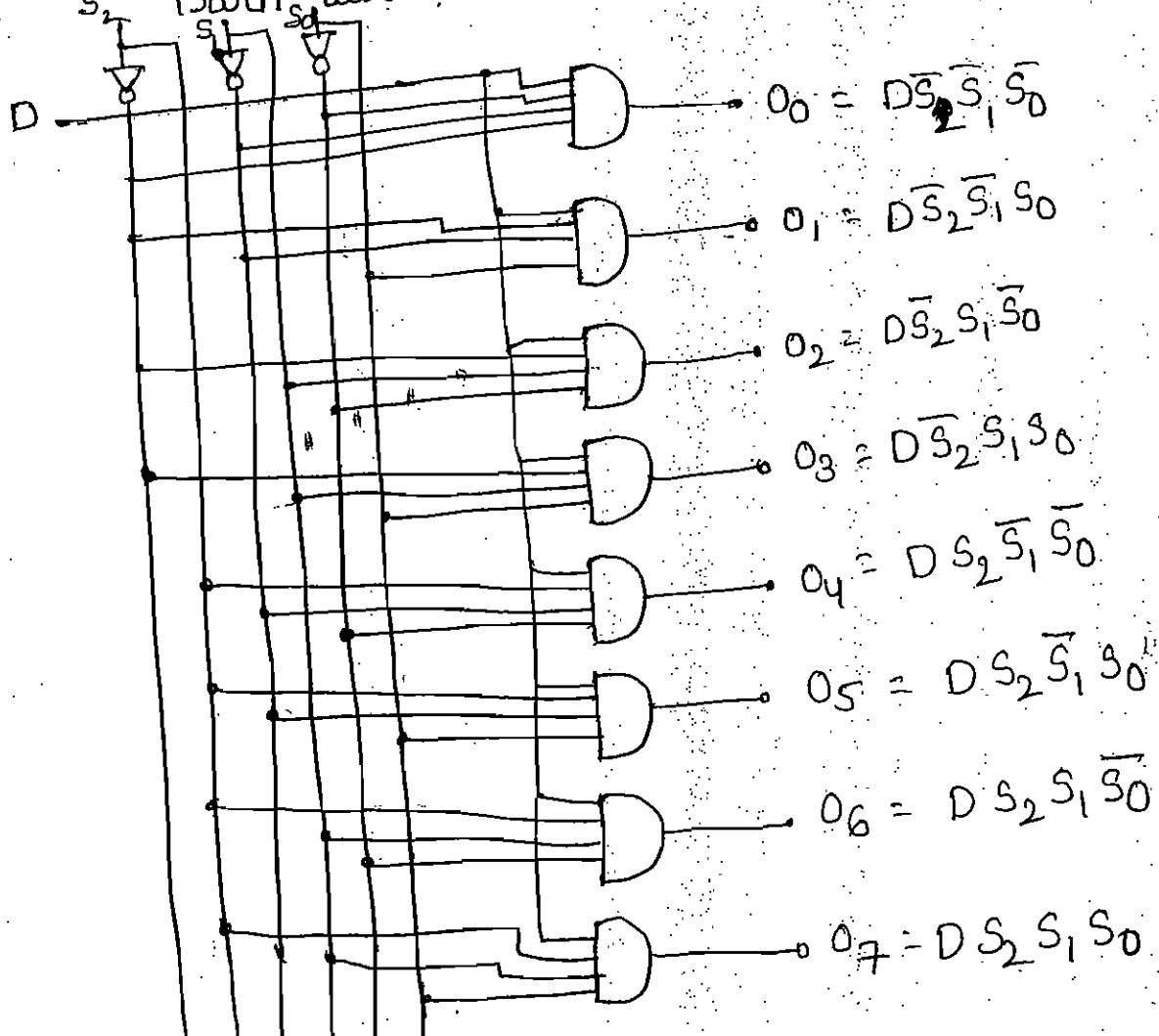


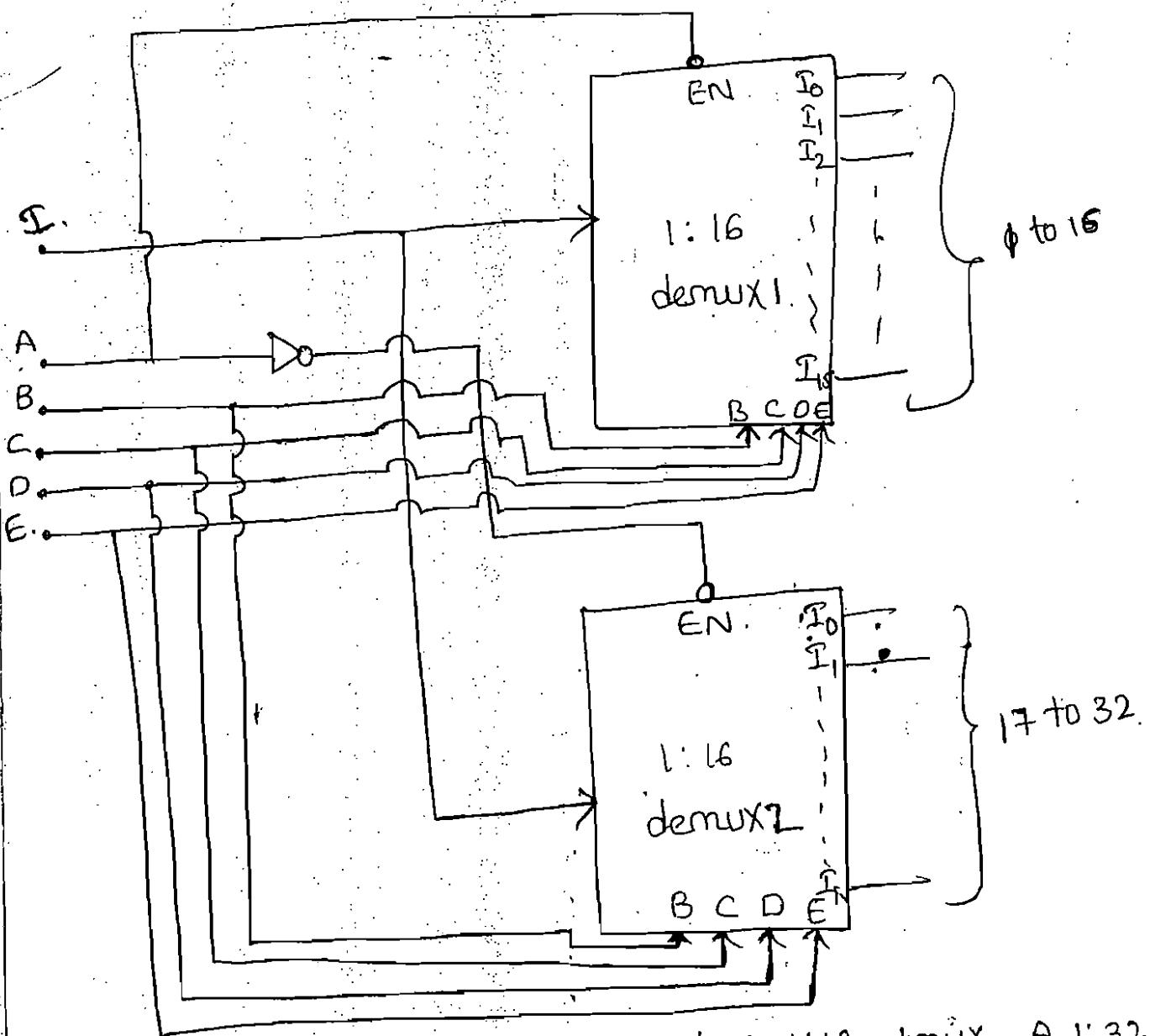
design of 1:32 demux using two 1:16 demux.



To obtain 1:32 demux using two 1:16 demux. A 1:32 demux has 32 data outputs. so it requires five data select lines. Since 1:16 demux has only four select inputs. the inputs B,C,D,E are connected to the data select lines of both the 1:16 demuxes and the most significant input A is connected to the single data select line of the both 1:16 demux's EN input. 1 to 16 will appear in the first demux when (A=0). 17 to 32 will appear in the second demux when A=1.

Encoders :-

An encoder is a device whose inputs are decimal digits and/or alphabetic characters and whose outputs are the coded representation of those inputs. An encoder is a device which converts familiar numbers or symbols into coded format. The encoder has  $2^n$  inputs and  $n$  outputs.

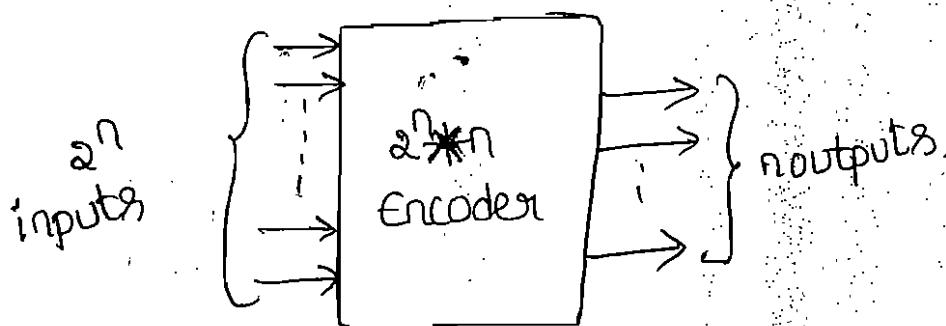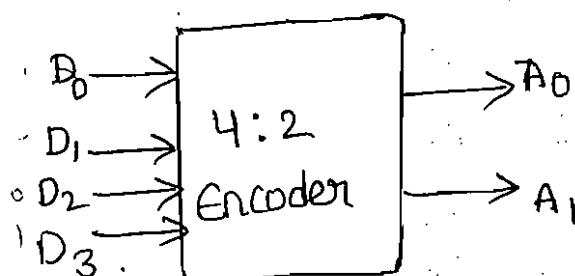4 bit - Encoder :-


Block diagram.

inputs	outputs $A_1, A_0$
$D_0$	0 0
$D_1$	0 1
$D_2$	1 0
$D_3$	1 1

Truth table.


$$A_1 = D_2 + D_3$$

$$A_0 = D_1 + D_3$$

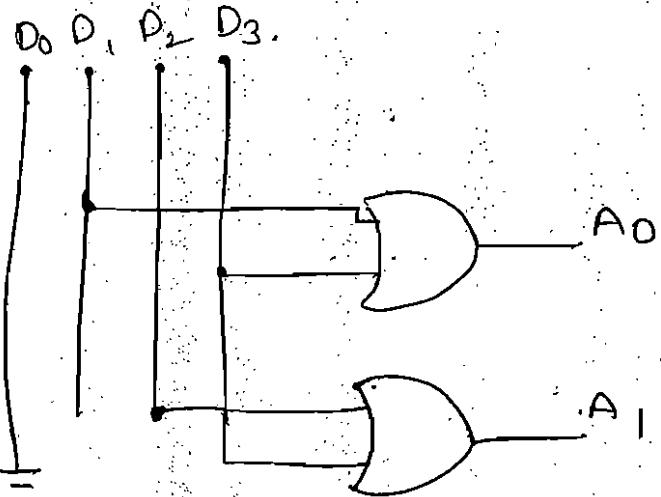
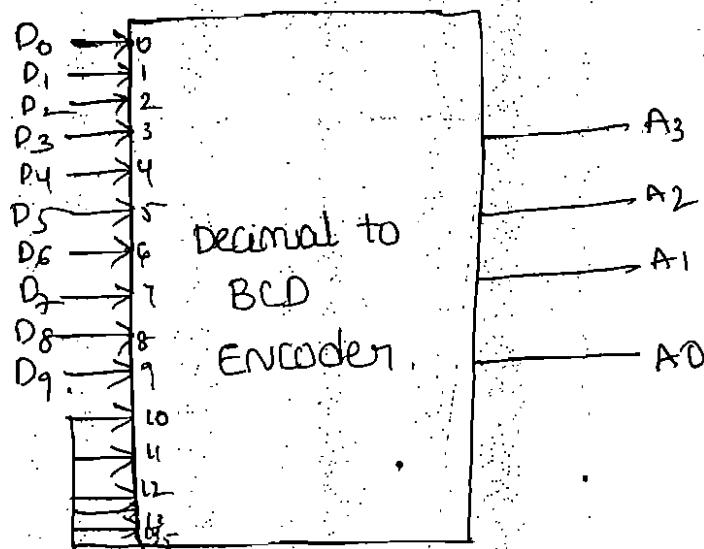
## Decimal to BCD Encoder :-


In this type of encoder has 10 inputs - one for each decimal digit, and 4 outputs corresponding to the BCD code.



Block diagram

decimal	Binary output			
	A <sub>3</sub>	A <sub>2</sub>	A <sub>1</sub>	A <sub>0</sub>
D <sub>0</sub>	0	0	0	000
D <sub>1</sub>	1	0	0	001
D <sub>2</sub>	2	0	0	100
D <sub>3</sub>	3	0	0	111
D <sub>4</sub>	4	0	1	000
D <sub>5</sub>	5	0	1	011
D <sub>6</sub>	6	0	1	110
D <sub>7</sub>	7	0	1	111
D <sub>8</sub>	8	1	0	000
D <sub>9</sub>	9	1	0	001

Truth table.

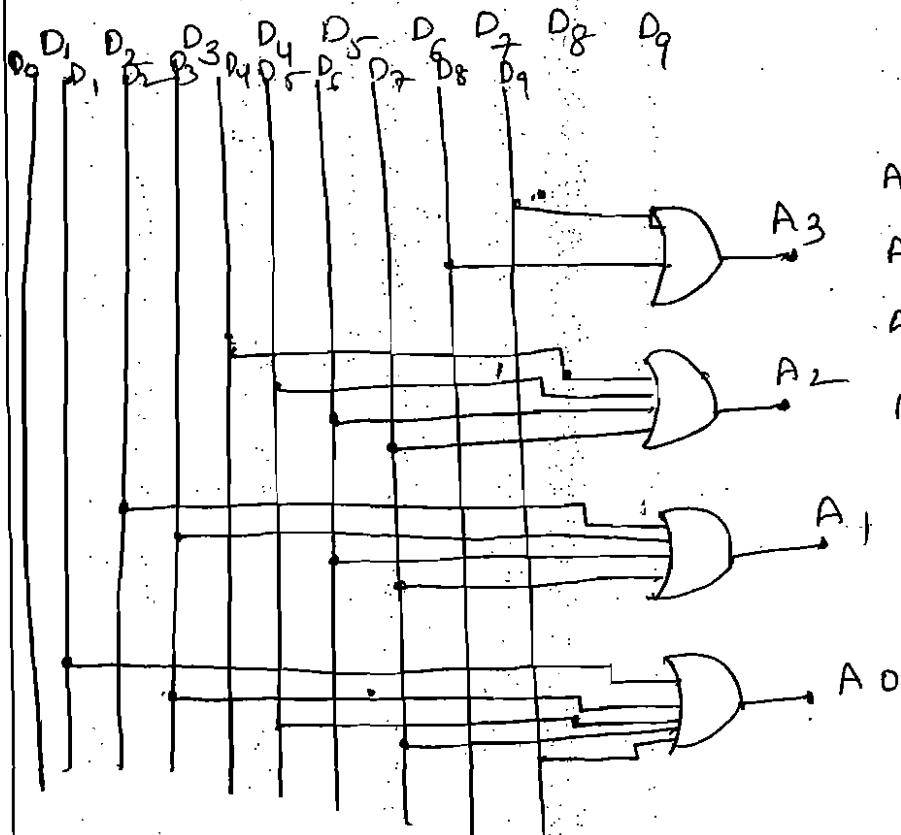

$$A_0 = D_1 + D_3 + D_5 + D_7 + D_9$$

$$A_1 = D_2 + D_3 + D_5 + D_7$$

$$A_2 = D_4 + D_5 + D_6 + D_7$$

$$A_3 = D_8 + D_9.$$

## Decoders :-

A decoder is a logic circuit that converts an  $n$ -bit binary input code into  $2^n$  output lines such that only one output line is activated for each one of the possible combinations of inputs. For each of these input combinations, only one of the output will be activated (High), all the other outputs will remain inactive (Low). Some decoders are designed to produce active low output, while all the other outputs remain high.


## 2-4 line decoder :-



A <sub>1</sub> , A <sub>0</sub>	D <sub>3</sub>	D <sub>2</sub>	D <sub>1</sub>	D <sub>0</sub>
0, 0	0	0	0	1
0, 1	0	0	1	0
1, 0	0	1	0	0
1, 1	1	0	0	0


Block diagram.

Truth table.

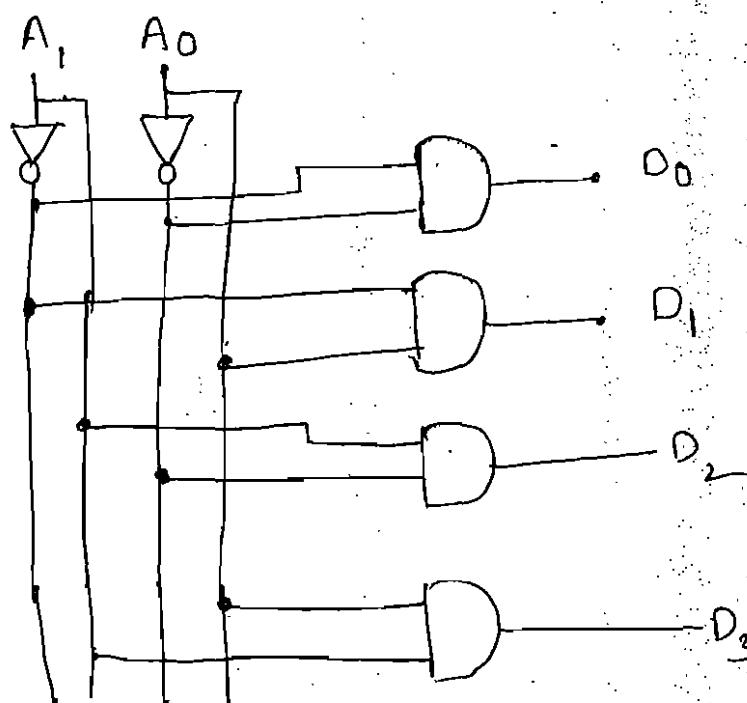

4-to-16 decoder from two 3-to-8 decoders:-


Decoders with enable inputs can be connected together to form a larger decoder. To obtain a 4-to-16 decoder it requires two 3-to-8 decoders. The most significant input bit  $A_3$  is connected through an inverter to  $\bar{E}$  on the upper decoder and directly to  $E$  on the lower decoder. Thus  $A_3$  is low, the upper decoder is enabled and the lower decoder is disabled. The bottom decoder outputs all 0's, and top 8 outputs. The bottom decoder generates minterms. When  $A_3$  is high, the lower decoder is enabled and the upper decoder is disabled. The bottom decoder generates minterms 1000 to 1111 while the outputs of the top decoder are all 0's.

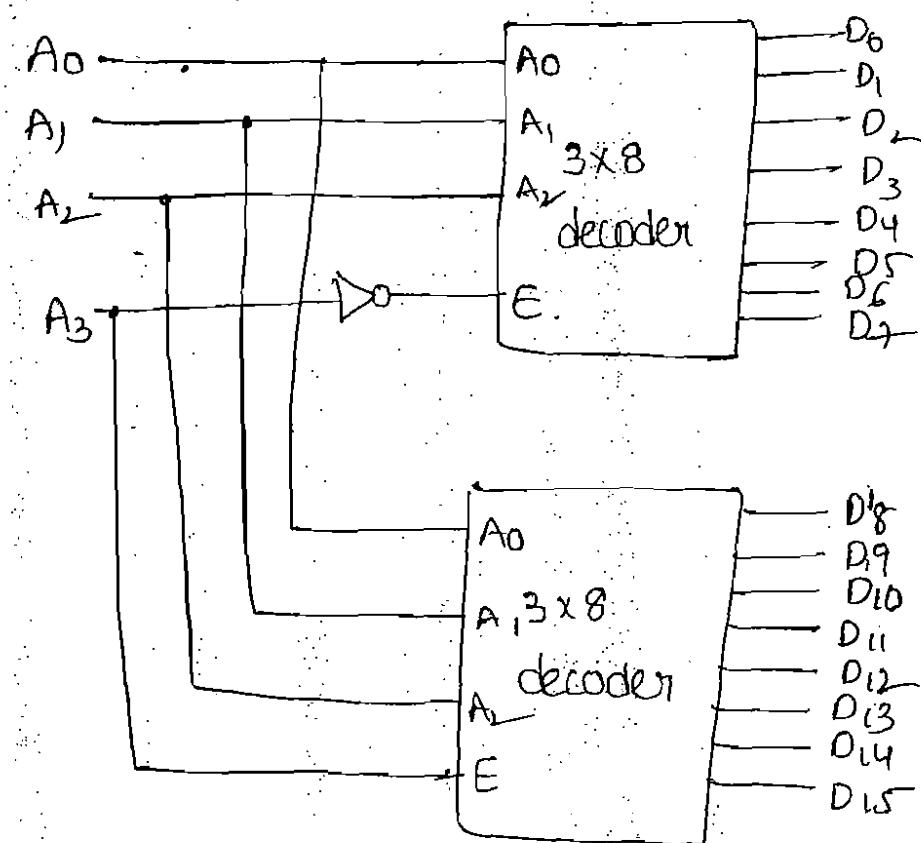

logic diagram
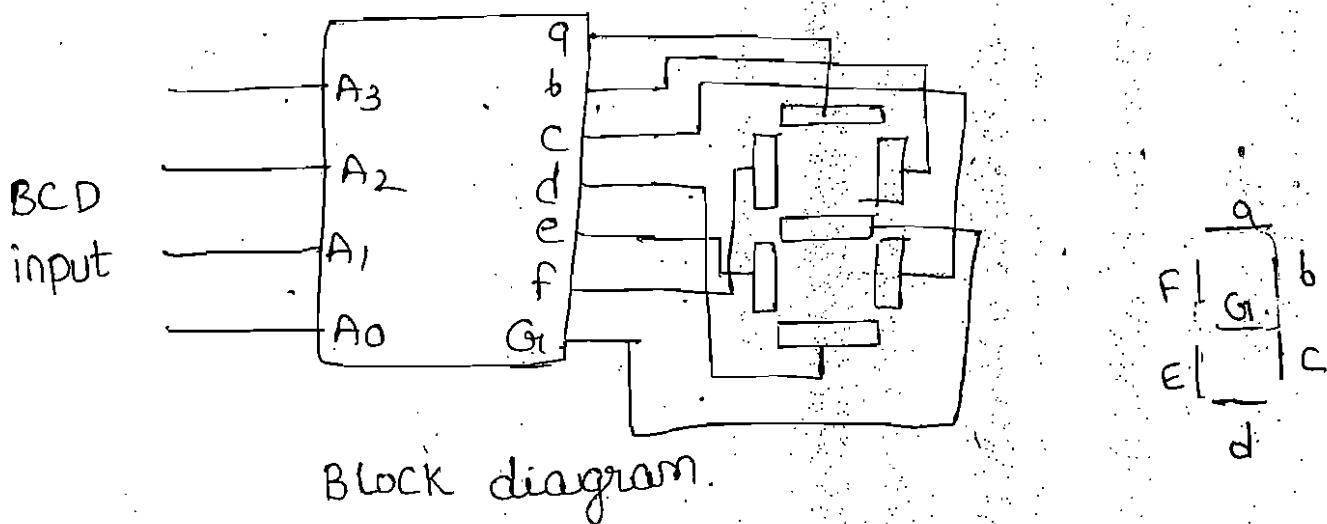
## Seven Segment Decoders :-

This type of decoders accepts the BCD code and provides outputs to energize seven segment display devices in order to produce a decimal read out. Each segment is made up of a material that emits light when current is passed through it. The most commonly used materials include LEDs, incandescent filaments and LCDs.



Decimal digit	BCD input				Seven segment code						
	A <sub>3</sub>	A <sub>2</sub>	A <sub>1</sub>	A <sub>0</sub>	a	b	c	d	e	f	G <sub>1</sub>
0	0	0	0	0	1	1	1	1	1	1	0
1	0	0	0	1	0	1	1	0	0	0	0
2	0	0	1	0	1	1	0	1	0	0	1
3	0	0	1	1	1	1	F	1	0	0	1
4	0	1	0	0	0	1	1	0	1	1	1
5	0	1	0	1	1	0	1	1	0	1	1
6	0	1	1	0	1	0	1	1	1	1	1
7	0	1	1	1	1	1	1	1	0	0	0
8	1	0	0	0	1	1	1	1	1	1	1
9	1	0	0	1	1	1	1	1	0	1	1

$$a = \text{em}(0, 2, 3, 5, 6, 7, 8, 9) + d(10, 11, 12, 13, 14, 15).$$

$$b = \text{em}(0, 1, 2, 3, 4, 7, 8, 9) + d(10, 11, 12, 13, 14, 15).$$

$$c = \text{em}(0, 1, 3, 4, 5, 6, 7, 8, 9) + d(10, 11, 12, 13, 14, 15).$$


$$d = \text{em}(0, 2, 3, 5, 6, 8, 9) + d(10, 11, 12, 13, 14, 15).$$

$$e = \text{em}(0, 2, 6, 8) + d(10, 11, 12, 13, 14, 15).$$


$$f = \text{em}(0, 4, 5, 6, 8, 9) + d(10, 11, 12, 13, 14, 15).$$

$$g = \text{em}(2, 3, 4, 5, 6, 8, 9) + d(10, 11, 12, 13, 14, 15).$$

K-map for a.



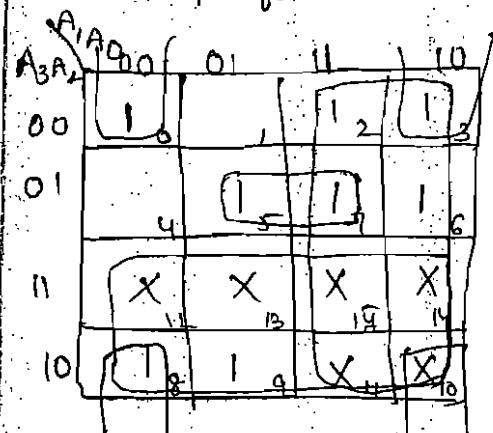


K-map for b.

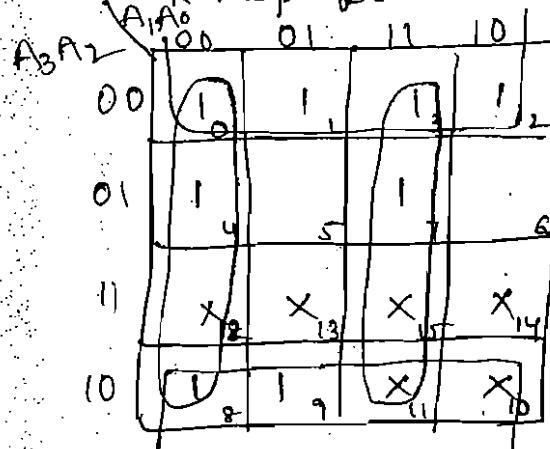

$$a = A_1 + A_3 + \bar{A}_2\bar{A}_0 + \bar{A}_3A_2A_0$$
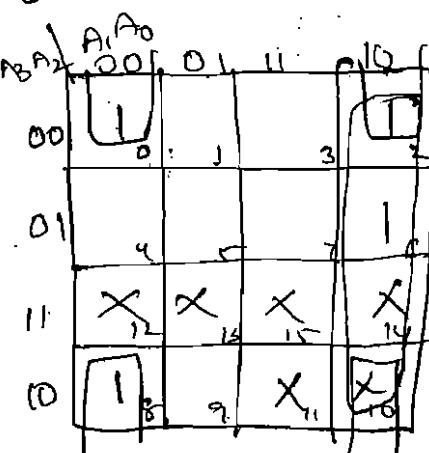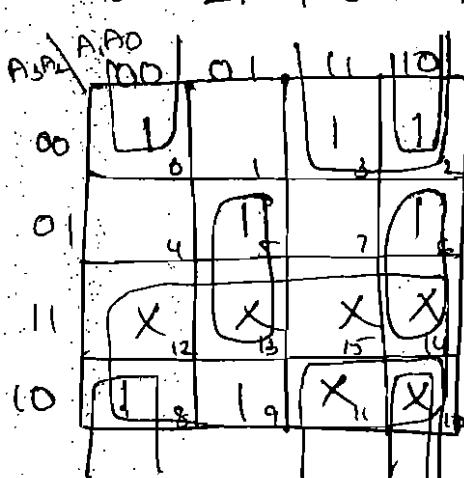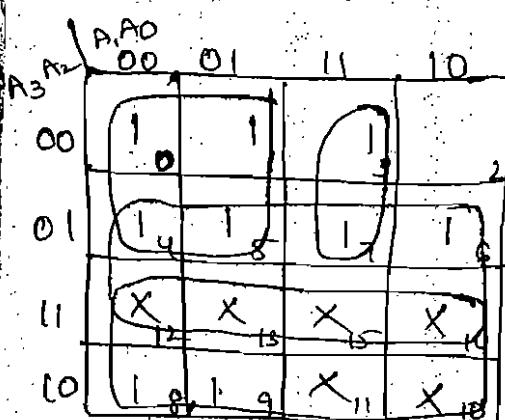
$$b = \bar{A}_2 + A_1\bar{A}_0 + A_1A_0$$



K-map for c.


K-map for d.

K-map for e.

$$c = A_2 + A_3 + \bar{A}_3\bar{A}_1 + \bar{A}_3A_1A_0$$

$$d = A_3 + \bar{A}_2A_1 + A_2\bar{A}_1A_0 + A_2A_1\bar{A}_0 + \bar{A}_2\bar{A}_0$$




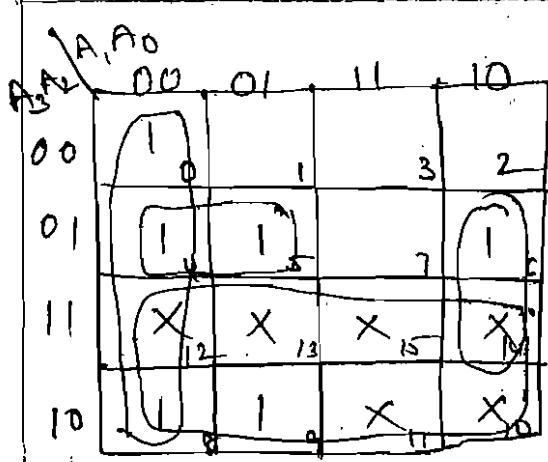
$$e = A_1\bar{A}_0 + \bar{A}_2\bar{A}_0$$







K-map for f.

$$f = \overline{A_1}\overline{A_0} + A_3 + \overline{A_3}A_2\overline{A_1} + A_2A_1\overline{A_0}$$

$$G_1 = A_3 + A_1\overline{A_0} + A_2\overline{A_1} + \overline{A_2}A_1$$

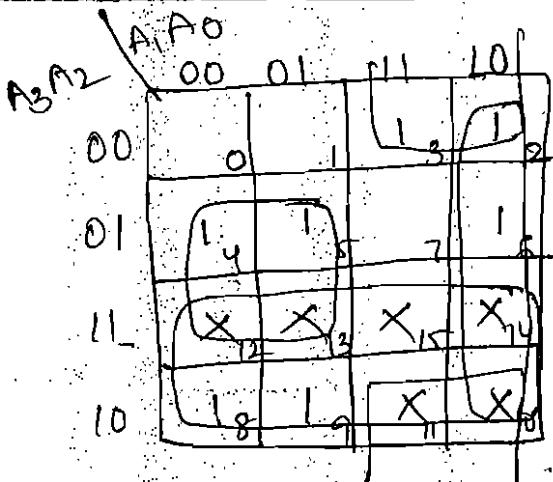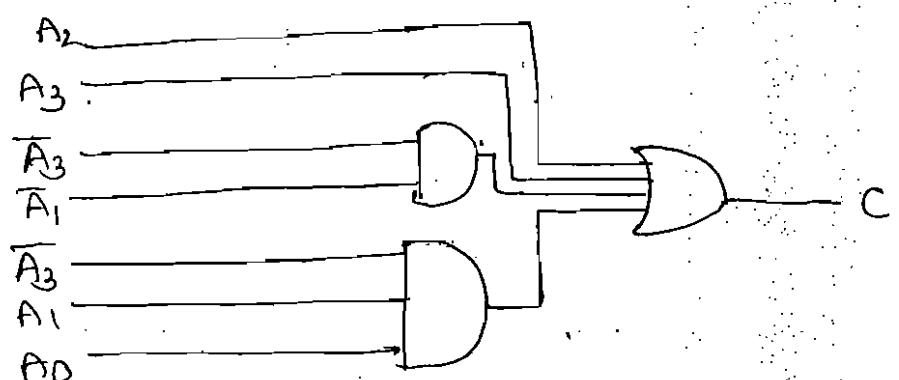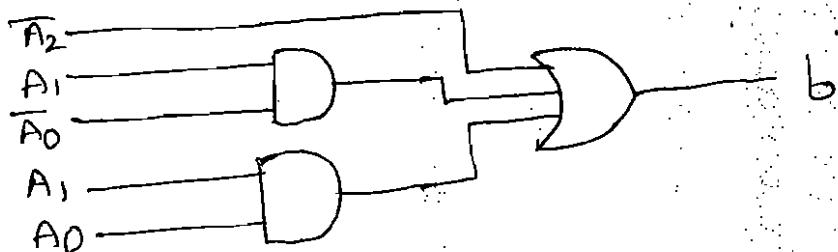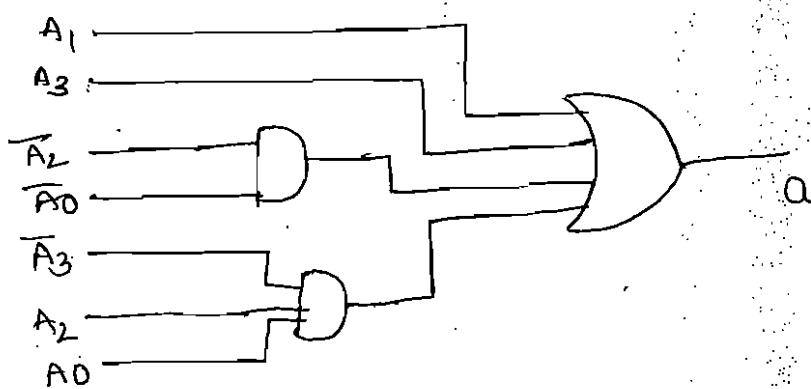
K-map for G<sub>1</sub>.

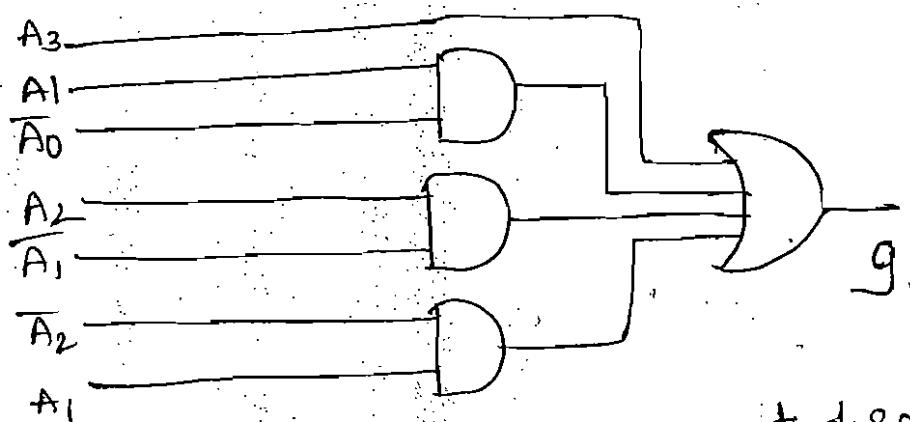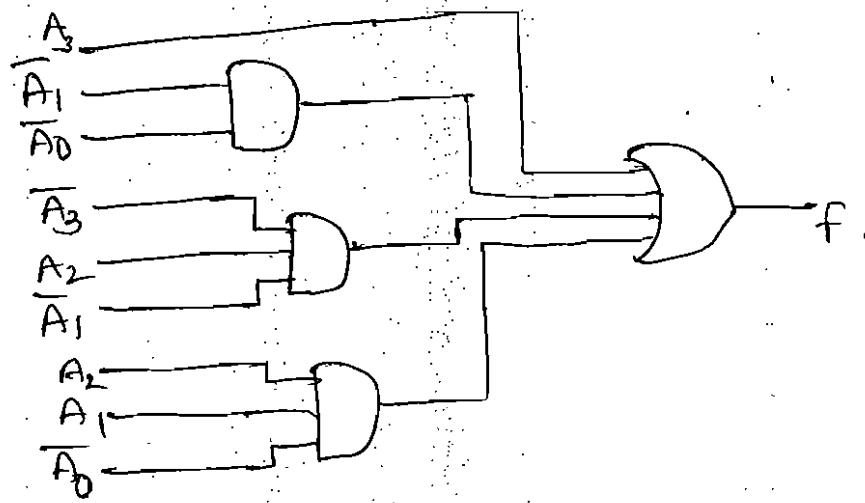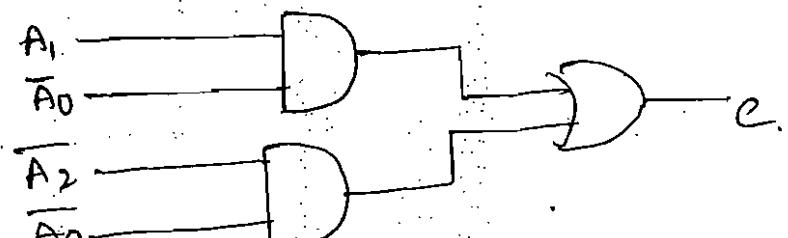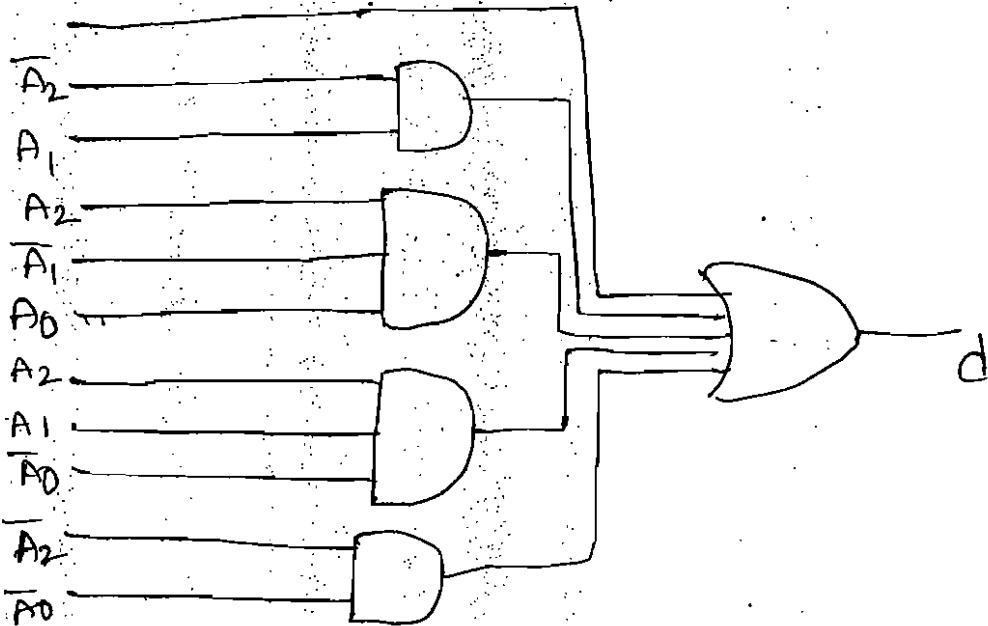

diagrams for seven segment display.

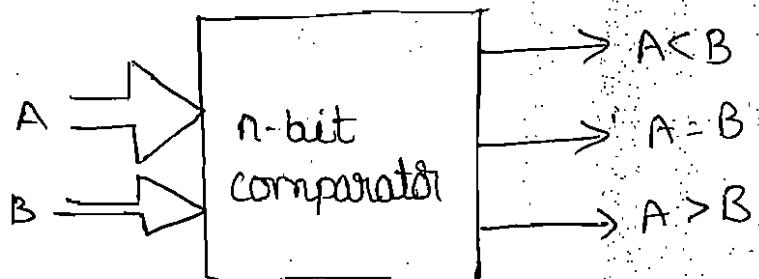
## Comparator :-

The comparator is a combinational logic circuit. It compares the magnitude of two n-bit numbers and provides the relative result as the output. The block diagram of an n-bit digital comparator has 2 inputs and three outputs. A and B are the n-bit inputs. The comparator outputs are  $A > B$ ,  $A = B$  and  $A < B$ . Depending upon the result of comparison, one of these outputs will be high.


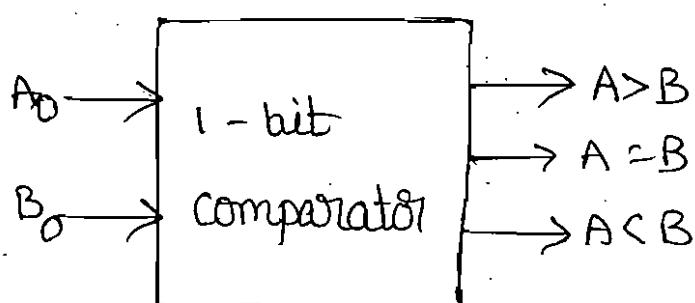
## 1-bit comparator :-

The one bit comparator is a combinational logic circuit with two inputs A and B and three outputs namely  $A < B$ ,  $A = B$ ,  $A > B$ .



Block diagram.

Inputs		outputs		
$A_0$	$B_0$	$A < B$	$A = B$	$A > B$
0	0	0	1	0
0	1	1	0	0
1	0	0	0	1
1	1	0	1	0


Truth table

In truth table

$$A = B : \overline{A_0} \overline{B_0} + A_0 B_0 = A_0 \oplus B_0$$

$$A < B : \overline{A_0} B_0$$

$$A > B : A_0 \overline{B_0}$$

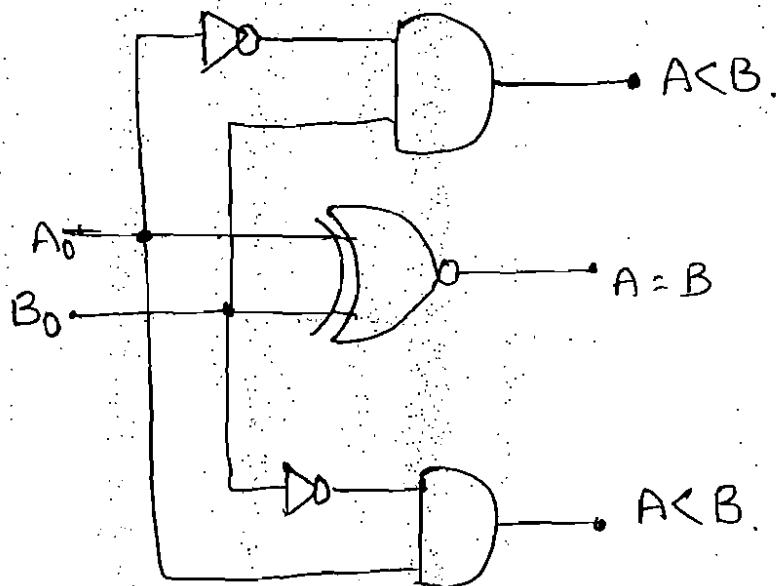

2-bit comparator :-

The logic for a 2-bit comparator. Let the two 2-bit numbers be  $A = A_1, A_0$  and  $B = B_1, B_0$ .

→ if  $A_1 = 1$  and  $B_1 = 0$ , then  $A > B$

→ if  $A_1$  and  $B_1$  are equal and  $A_0 = 1$  and  $B_0 = 0$  then  
 $A > B$ .

$$A > B : A_1 \overline{B_1} + (A_1 \oplus B_1) A_0 \overline{B_0}$$


→ if  $B_1 = 1$  and  $A_1 = 0$  then  $A < B$

→ if  $B_1$  and  $A_1$  are equal and  $B_0 = 1$  and  $A_0 = 0$  then  
 $A < B$

$$A < B : \overline{A_1} B_1 + (A_1 \oplus B_1) \overline{A_0} B_0$$

→ if  $A_1$  and  $B_1$  are equal and if  $A_0$  and  $B_0$  are equal then  
 $A = B$
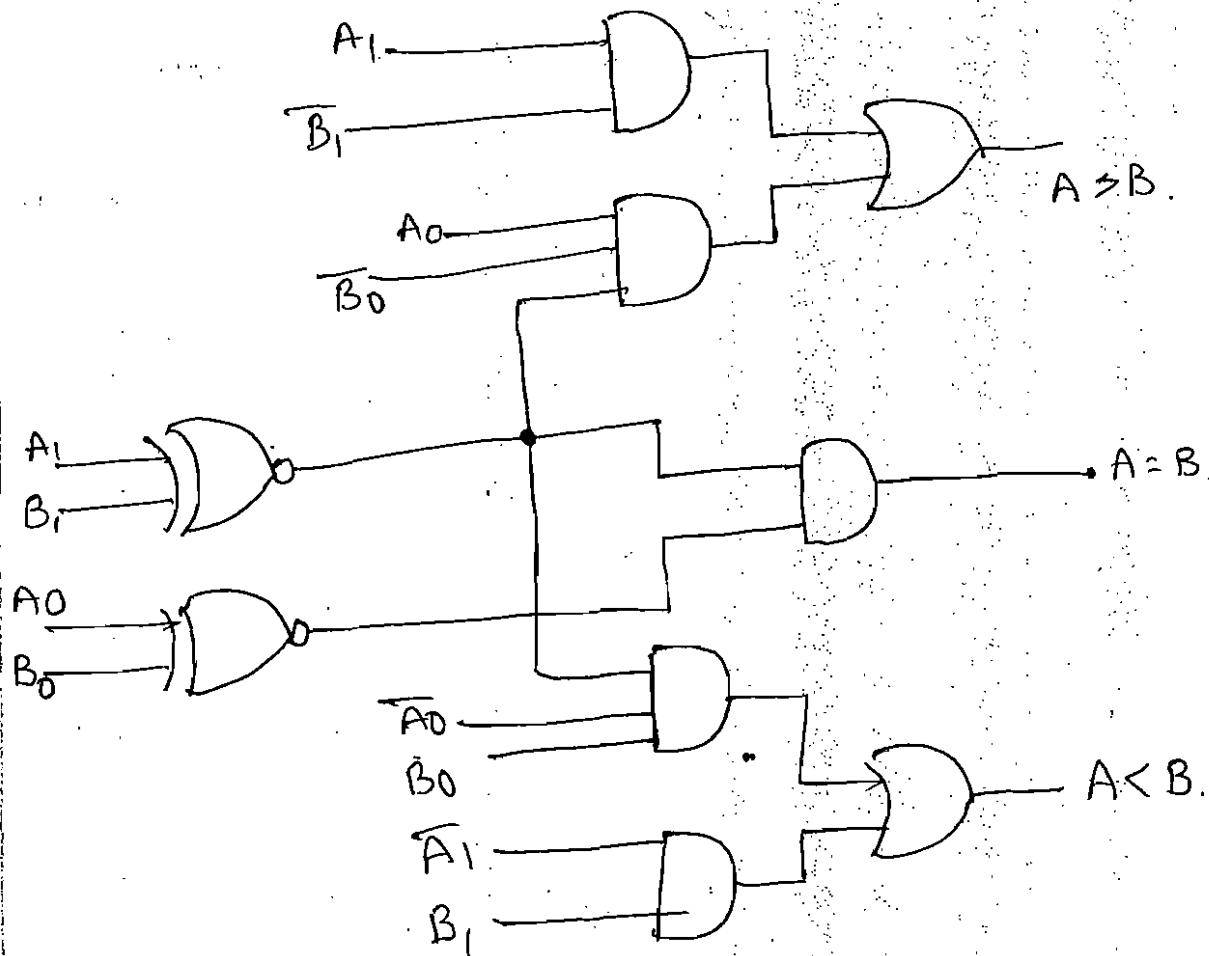
$$A = B : (A_1 \oplus B_1) (A_0 \oplus B_0)$$



#### 4-bit comparator :-


The logic for a 4-bit comparator. Let the four bit numbers will be  $A = A_3 A_2 A_1 A_0$  and  $B = B_3 B_2 B_1 B_0$ .

- if  $A_3 = 1$  and  $B_3 = 0$ , then  $A > B$  or
- if  $A_3$  and  $B_3$  are equal, and if  $A_2 = 1$  and  $B_2 = 0$ , or
- if  $A_3$  and  $B_3$  are equal,  $A_2$  and  $B_2$  are equal, and if  $A_1 \oplus B_1 = 1$  and  $B_1 = 0$ , or
- if  $A_3$  and  $B_3$  are equal, and if  $A_2$  and  $B_2$  are equal, and if  $A_1$  and  $B_1$  are equal, and if  $A_0 = 1$  and  $B_0 = 0$ .

$$(A > B) = A_3 \bar{B}_3 + (A_3 \oplus B_3) A_3 \bar{B}_2 + (A_3 \oplus B_3) (A_2 \oplus B_2) A_3 \bar{B}_1 \\ + (A_3 \oplus B_3) (A_2 \oplus B_2) (A_1 \oplus B_1) A_3 \bar{B}_0$$

$$(A < B) = \bar{A}_3 B_3 + (A_3 \oplus B_3) \bar{A}_3 B_2 + (A_3 \oplus B_3) (A_2 \oplus B_2) \bar{A}_3 B_1 \\ + (A_3 \oplus B_3) (A_2 \oplus B_2) (A_1 \oplus B_1) \bar{A}_3 B_0$$
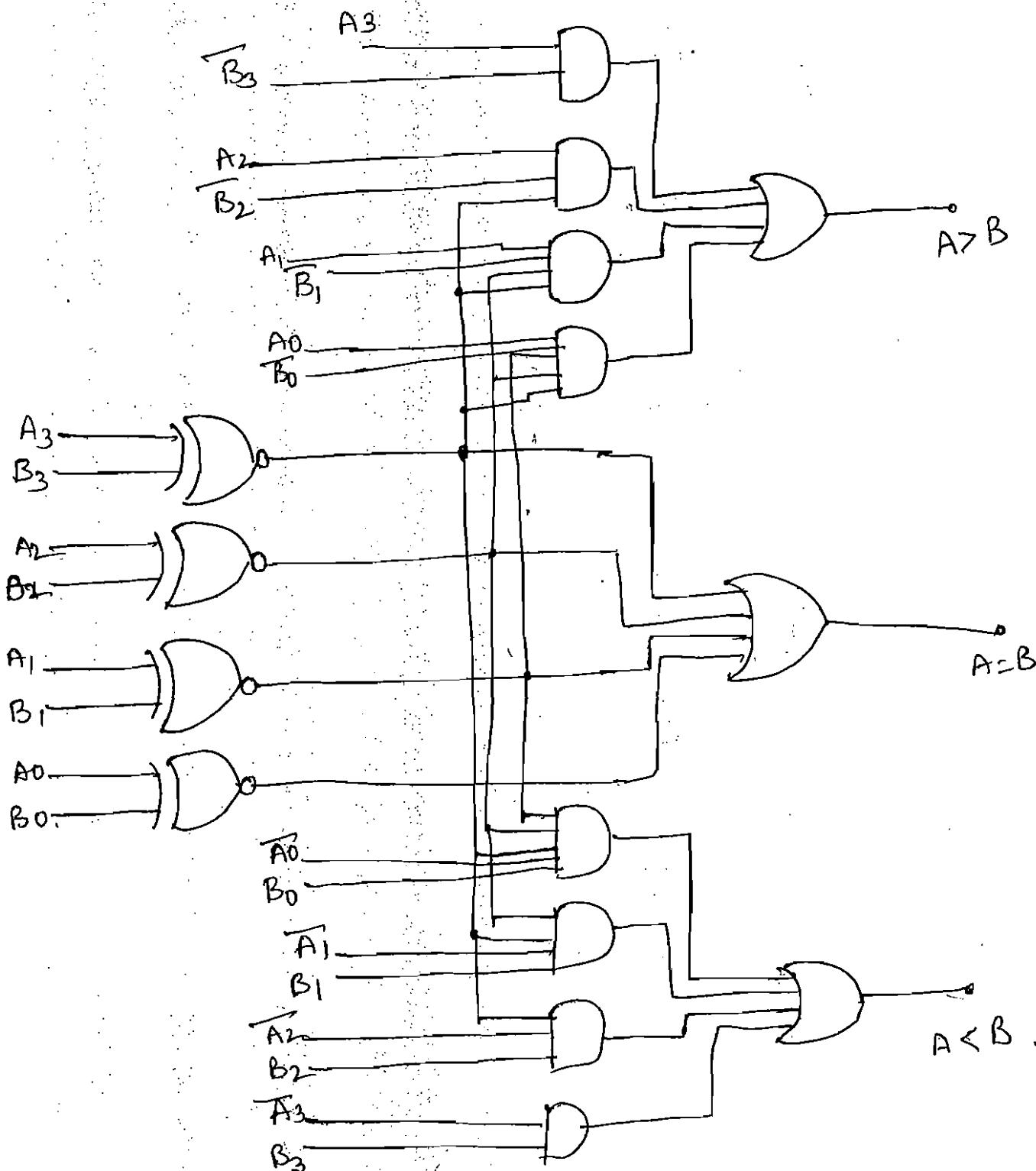
$$A = B : (A_3 \oplus B_3) (A_2 \oplus B_2) (A_1 \oplus B_1) (A_0 \oplus B_0).$$



logic diagram for 4-bit comparator.

## Priority Encoders :-

It is possible that two or more inputs are active at a time. To overcome this, priority encoders are used. A priority encoder is a logic circuit that responds to just one input in accordance with some priority system, among all those that may be simultaneously high. The most common priority system is based on the relative magnitudes of the inputs.

In some practical applications, priority encoders may have several inputs that are simultaneously high at the same time, and the principal function of the encoder in those cases is to select the input with the highest priority.

## 4-input priority Encoder :-

In 4-input priority encoder in addition to the outputs A and B, the circuit has a third output designated by V. This is a valid bit indicator that is set to 1 when one or more inputs are equal to 1. If all inputs are 0, there is no valid input and V is equal to 0. The other two outputs are not inspected when V equals 0 and are specified as don't care conditions.

Truth table

$$V = D_0 + D_1 + D_2 + D_3$$


$D_0$	$D_1$	$D_2$	$D_3$	A	B	V
0	0	0	0	X	X	0
1	0	0	0	0	0	1
X	1	0	0	0	1	1
X	X	1	0	1	0	1
X	X	X	1	1	1	1

According to the truth table. the outputs A and B are.

$$A = \text{em}(1, 2, 3, 5, 6, 7, 9, 10, 11, 13, 14, 15)$$


$$B = \text{em}(1, 3, 4, 5, 7, 9, 11, 12, 13, 15)$$

K-map for A

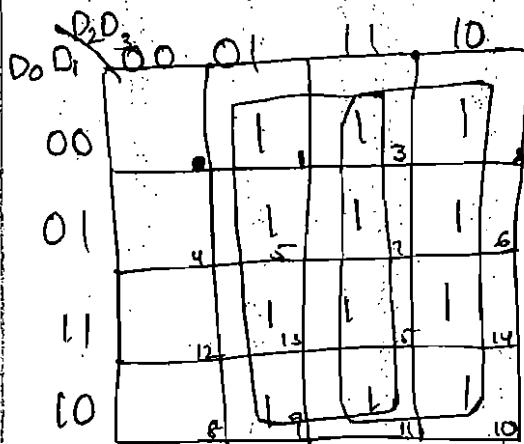


$$A = D_3 + D_2$$

K-map for B

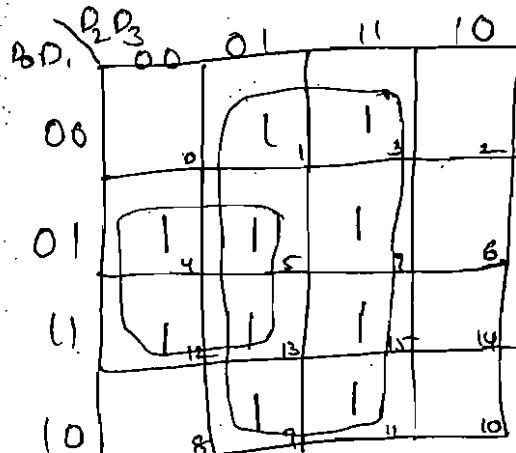

$$B = D_3 + \overline{D}_2 D_1$$

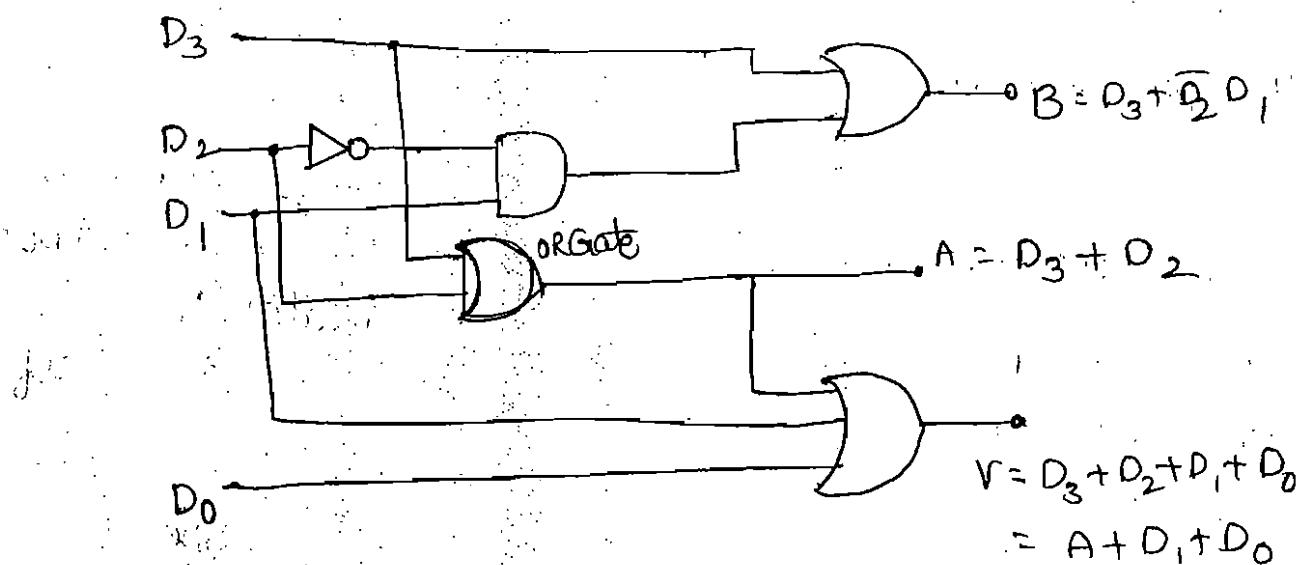

logic diagram for  
4-bit priority encoder.

## PROGRAMMABLE LOGIC DEVICES

- logic designers have a wide range of standard IC's available to them with numerous logic functions and logic circuit arrangements on a chip. In addition, these ICs are available from many manufacturers and at a reasonable low cost.
- PLD is an IC that contains large number of gates, flip-flops and registers that are interconnected on chip. This IC is said to be programmable because the specific function IC is determined by interconnecting required contacts.

Basically, there are three types of programmable device which are.

- Read only memory (ROM)
- programmable logic array (PLA)
- programmable Array logic (PAL)

### READ ONLY memory :-

- The read only memory is a type of semiconductor memory that is designed to hold data that is either permanent or will not change frequently.
- During operation, no new data can be written into a ROM, but data can be read from ROM. the process of entering data is called programming or burning-in the ROM.

→ Some ROM's cannot have their data changes once they have been programmed. others can be erased and reprogrammed as often as desired.

### Types of Rom's :-

1. Masked memory ROM
2. programmable read only memory (PROM)
3. Erasable programmable read only memory (EPROM)
4. Electrically Erasable programmable read only memory (EEPROM)

### Masked memory (Rom) :-

- cannot be reprogrammed
- Nonvolatile, retain data even when power is turn off.
- cheaper than programmable devices.
- useful for fixed programme instructions.

### PROM

- programmed by blowing built-in fuses.
- can not be reprogrammed.
- Non volatile.
- useful for small volume data storing
- user programmable

### EPROM :-


- Erasable, programmable ROM
- programmed by storing charge on insulated gates.
- Erasable with ultraviolet light
- non-volatile.

### EEPROM :-

- programmed by storing charges on insulated gates
- non volatile
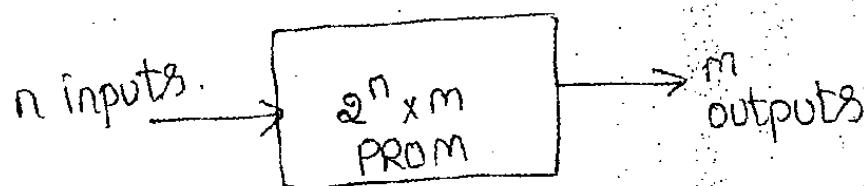
### Programmable ROM :-

- It includes both the decoder and the OR Gates with a single IC package. The following figures shows the block diagram and logic construction using 16x2 ROM.
- It consists of n input lines and m output lines.
- Each bit combination of the input variables is called an address.
- Each bit combination that comes out of the output lines is called a word.



Block diagram.

An integrated circuit with programmable gates divided into an AND array and an OR array provide an AND-OR sum of products implementation.

## EPROM :-


- Erasable, programmable ROM
- programmed by storing charge on insulated gates.
- Erasable with ultraviolet light
- non-volatile.

## EEPROM :-

- programmed by storing charges on insulated gates
- non volatile
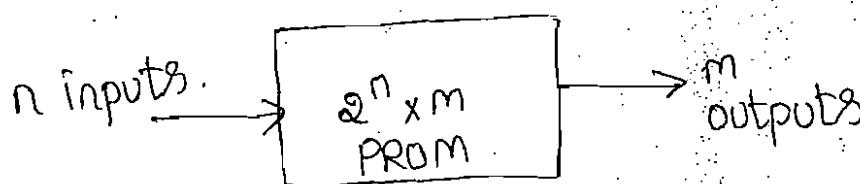
## Programmable ROM :-



- It includes both the decoder and the OR Gates with a single IC package. The following figures shows the block diagram and logic construction using 16x2 ROM.
- It consists of n input lines and m output lines.
- Each bit combination of the input variables is called an address.
- Each bit combination that comes out of the output lines is called a word.



Block diagram.

An integrated circuit with programmable gates divided into an AND array and an OR array to provide an AND-OR sum of products implementation.

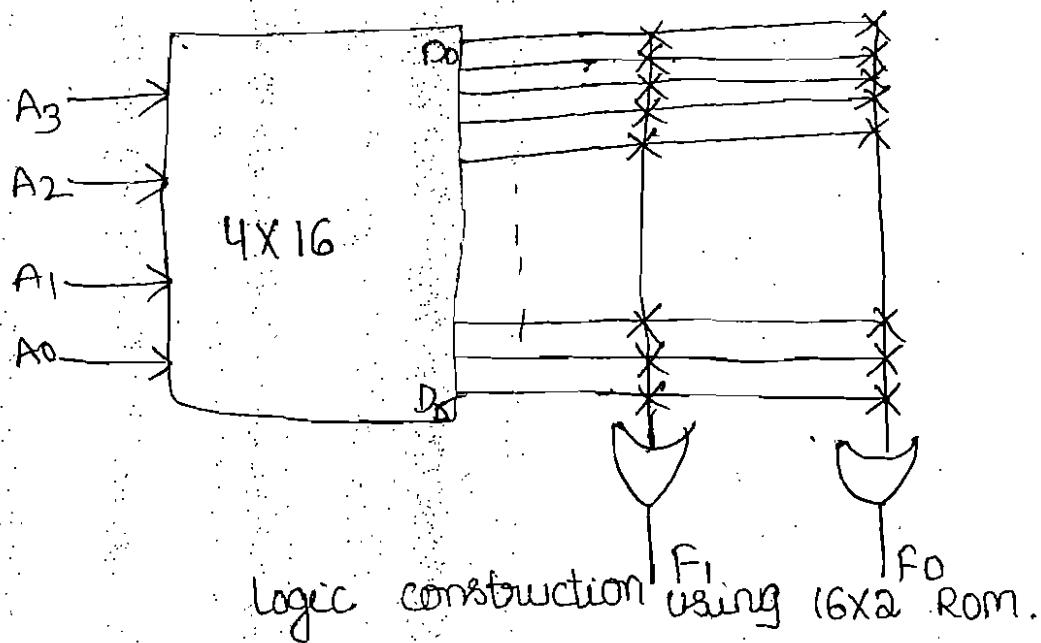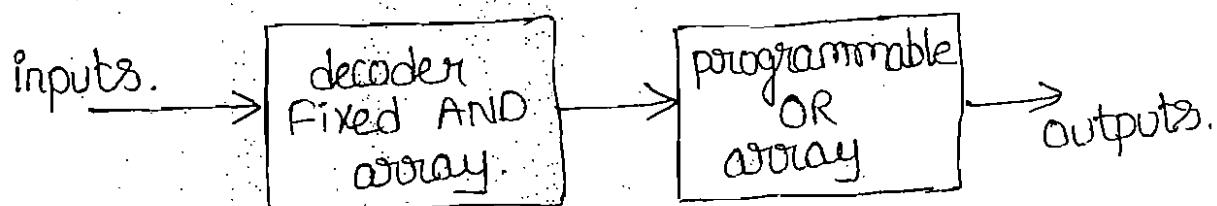The programmable read-only memory (PROM) has a fixed AND array constructed as a decoder and a programmable OR array. The AND gates are programmed to provide the product terms for the Boolean functions, which are logically summed in each OR gate.



→ Implement full-adder using PROM.

The number of inputs variables of a full adder are 3. The possible number of combinations are 8. So we need  $3 \times 8$  decoder. The number of outputs of full adder are 8. They are sum and carry.


(3)

Truth table

A	B	Cin	S	C
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

output expression for sum & carry  
 sum =  $\sum m(1,2,4,7)$   
 carry =  $\sum m(3,5,6,7)$ .

logic diagram

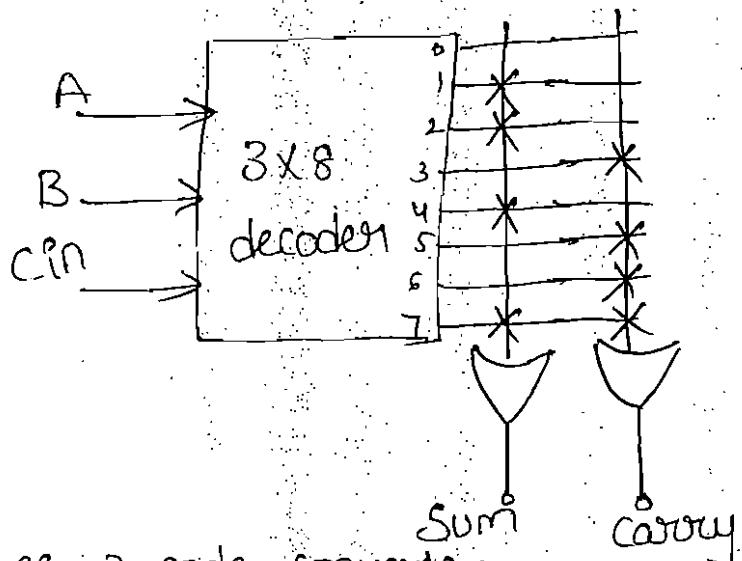

→ Design BCD to Excess-3 code converter  
 using PROM.

Step:- 1 - Truth table.

BCD				EXCESS-3			
$B_3$	$B_2$	$B_1$	$B_0$	$E_3$	$E_2$	$E_1$	$E_0$
0	0	0	0	0	0	1	1
0	0	0	1	0	1	0	0
0	0	1	0	0	1	0	1
0	0	1	1	0	1	1	0
0	1	0	0	0	1	1	1
0	1	0	1	1	0	0	0
0	1	1	0	1	0	0	1
0	1	1	1	1	0	1	0
1	0	0	0	0	0	1	1

Step 2 :-


$$E_0(B_3, B_2, B_1, B_0) = \Sigma m(0, 2, 4, 6, 8)$$

$$E_1(B_3, B_2, B_1, B_0) = \Sigma m(0, 3, 4, 7, 8)$$

$$E_2(B_3, B_2, B_1, B_0) = \Sigma m(1, 2, 3, 4, 9)$$

$$E_3(B_3, B_2, B_1, B_0) = \Sigma m(5, 6, 7, 8, 9)$$

Step 3 :- logic diagram.

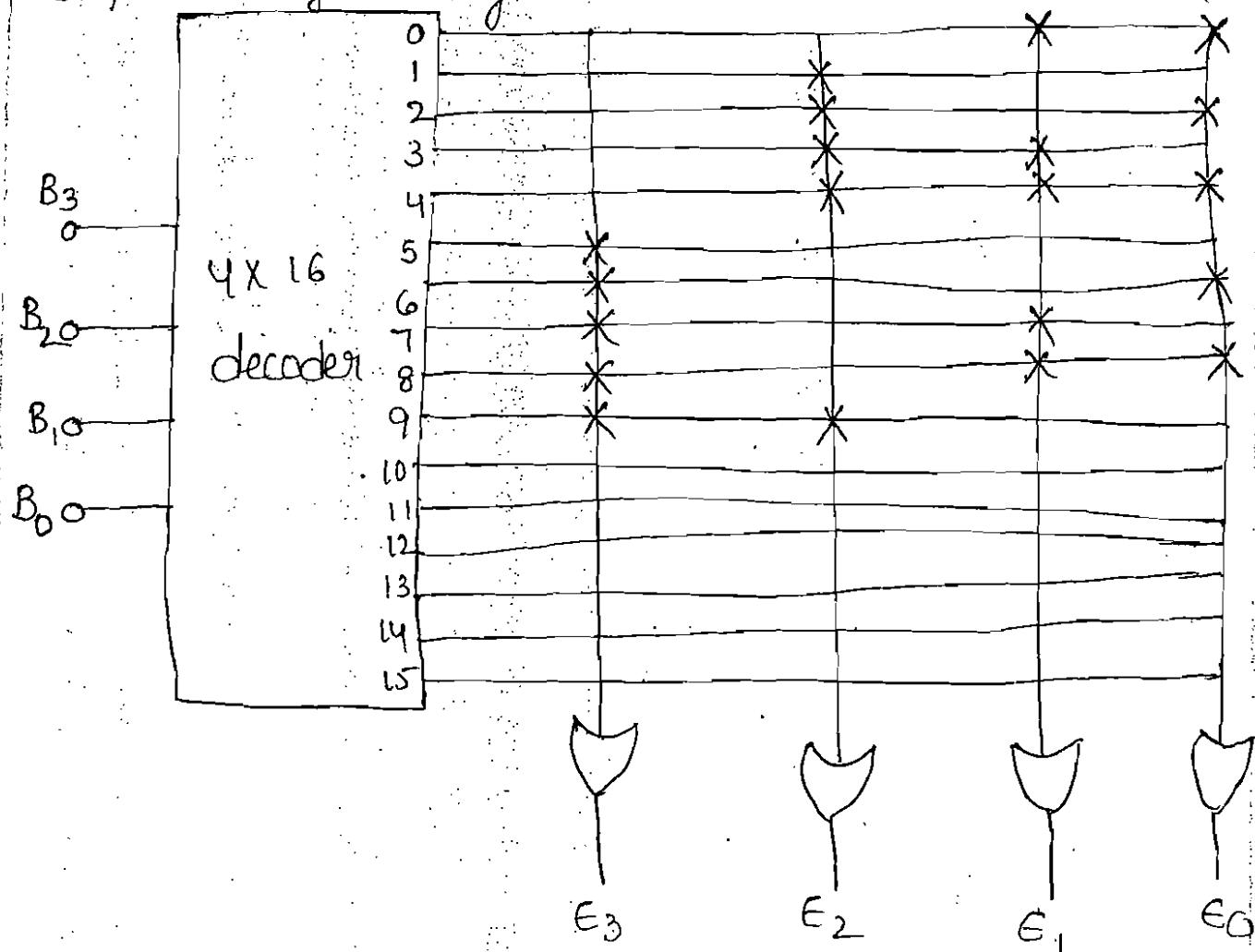

→ Implement the following Boolean expression using PROM.

$$f(A, B, C) = \overline{A}B + C + BC$$


first given expression converted into a standard SOP form

$$f(A, B, C) = \overline{A}B + C + BC$$

$$\begin{aligned}
 &= \overline{AB}(C+\overline{C}) + C(A+\overline{A})(B+\overline{B}) + BC(A+\overline{A}) \\
 &= \overline{ABC} + \overline{ABC} + \underline{\overline{ABC}} + \overline{ABC} + \overline{ABC} + \overline{ABC} + \overline{ABC} \\
 &= \overline{ABC} + \overline{ABC} + ABC + \overline{ABC} + \overline{ABC} + \overline{ABC} \\
 &\quad 0\_{11}, 0\_{10}, 111, 101, 011, 001
 \end{aligned}$$


$$f(A, B, C) = \sum m(1, 2, 3, 5, 7)$$

Logic diagram :-

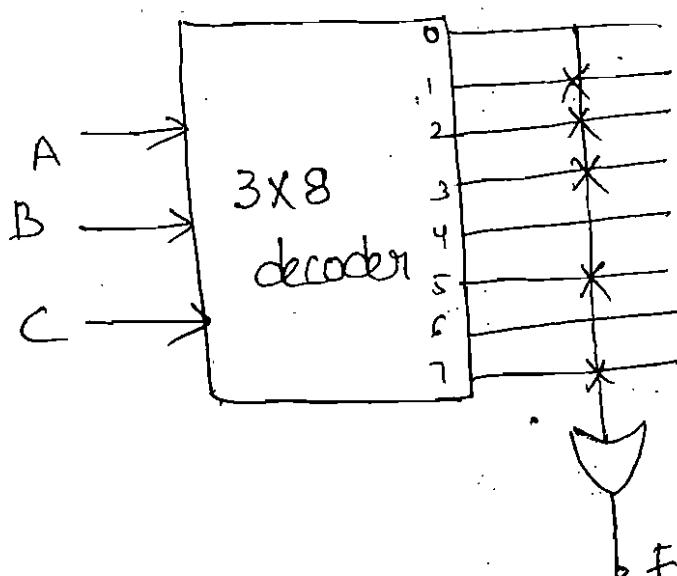

PAL:- programmable Array logic:-

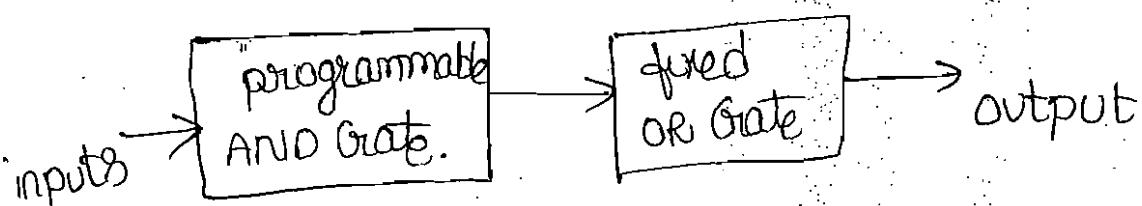The programmable Array logic is a programmable device with a fixed OR array and a programmable AND array because, only the AND gates are programmable.



→ Implement the following functions using PAL.

$$F_1(a,b,c,d) = \sum m(0,1,2,3,6,9,11)$$

$$F_2(a,b,c,d) = \sum m(0,1,6,8,9)$$

Step 1 :- K-map simplification for  $F_1$  and  $F_2$

ab	cd	00	01	11	10
00	1 1 1 0	1 1 1 1	1 1 1 1	1 1 1 1	1 1 1 1
01	1 1 1 1	1 1 1 1	1 1 1 1	1 1 1 1	1 1 1 1
11	1 1 1 1	1 1 1 1	1 1 1 1	1 1 1 1	1 1 1 1
10	1 1 1 1	1 1 1 1	1 1 1 1	1 1 1 1	1 1 1 1

$$\bar{a}\bar{b} + \bar{a}cd + \bar{b}d$$

ab	cd	00	01	11	10
00	1 1 1 1	1 1 1 1	1 1 1 1	1 1 1 1	1 1 1 1
01	1 1 1 1	1 1 1 1	1 1 1 1	1 1 1 1	1 1 1 1
11	1 1 1 1	1 1 1 1	1 1 1 1	1 1 1 1	1 1 1 1
10	1 1 1 1	1 1 1 1	1 1 1 1	1 1 1 1	1 1 1 1


$$\bar{b}\bar{c} + \bar{a}bc\bar{d}$$

Step 2 :- PAL programming table.

product terms	AND gate inputs a b c d	outputs
1	0 0 - -	
2	0 - 1 1	$F_1 = \bar{a}\bar{b} + \bar{b}cd + \bar{b}d$
3	- 0 - 1	
4	- 0 0 -	$F_2 = \bar{b}\bar{c} + \bar{a}bc\bar{d}$
5	0 1 1 0	
6	- - - -	

(5)

Step 3 :- implementation :-

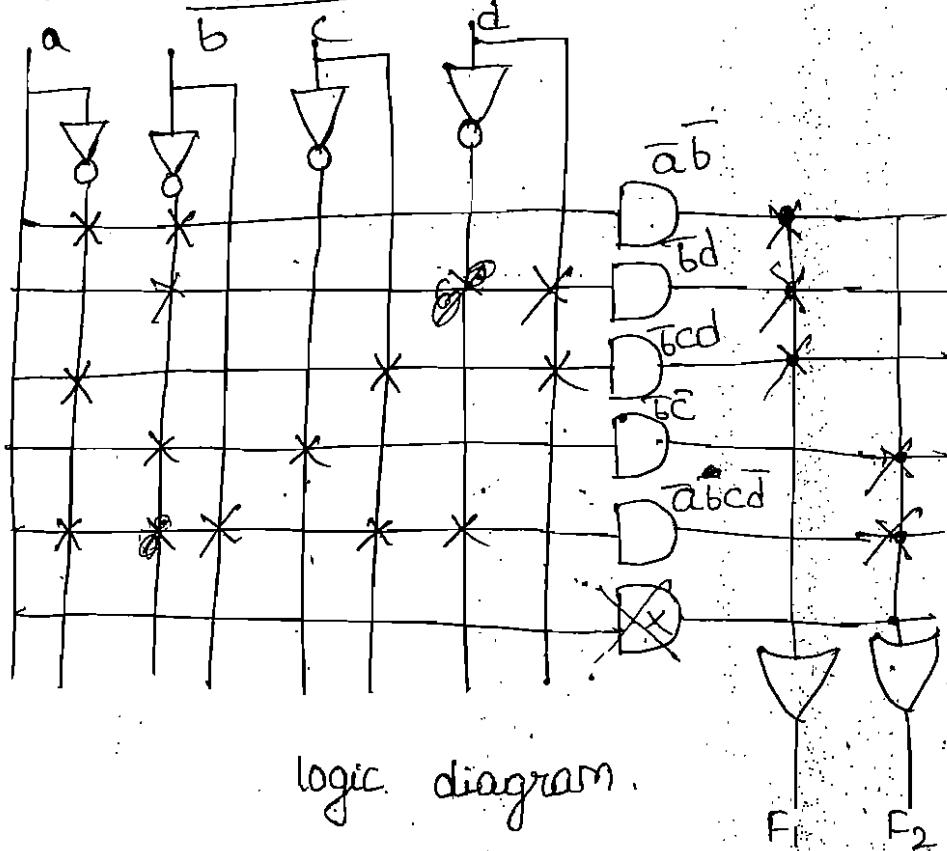

→ Implement 4-bit BCD to XS-3 code conversion  
using PAL.

Step:-1

$B_4$	$B_3$	$B_2$	$B_1$	$x_4$	$x_3$	$x_2$	$x_1$
0	0	0	0	0	0	1	1
0	0	0	1	0	1	0	0
0	0	1	0	0	1	0	1
0	0	1	1	0	1	1	0
0	1	0	0	0	1	1	1
0	1	0	1	1	0	0	0
0	1	1	0	1	0	0	1
0	1	1	1	1	0	1	0
1	0	0	0	1	0	1	1
1	0	0	1	1	1	0	0

$$X_4 = \text{Em}(5, 6, 7, 8, 9) + d(10, 11, 12, 13, 14, 15)$$

$$X_3 = \text{Em}(1, 2, 3, 4, 9) + d(10, 11, 12, 13, 14, 15)$$

$$X_2 = \text{Em}(0, 3, 4, 7, 8) + d(10, 11, 12, 13, 14, 15)$$

$$X_1 = \text{Em}(0, 2, 4, 6, 8) + d(10, 11, 12, 13, 14, 15)$$

$B_4\backslash B_3$	$B_2\backslash B_1$	00	01	11	10
00	0	1	3	2	
01	4	1	7	6	
11	$X_{12}$	$X_{13}$	$X_{15}$	$X_{14}$	
10	18	19	$X_{11}$	$X_{10}$	

$B_4\backslash B_3$	$B_2\backslash B_1$	00	01	11	10
00	0	1	3	2	
01	4	5	7	6	
11	$X_{12}$	$X_{13}$	$X_{15}$	$X_{14}$	
10	8	9	$X_{11}$	$X_{10}$	

$B_4\backslash B_3$	$B_2\backslash B_1$	00	01	11	10
00	0	1	3	2	
01	1	5	7	6	
11	$X_{12}$	$X_{14}$	$X_{15}$	$X_{14}$	
10	18	9	$X_{11}$	$X_{10}$	

$B_4\backslash B_3$	$B_2\backslash B_1$	00	01	11	10
00	0	1	3	2	
01	12	5	7	6	
11	$X_{12}$	$X_{18}$	$X_{15}$	$X_{14}$	
10	18	9	$X_{11}$	$X_{10}$	

$$X_4 = B_4 + B_3 B_2 + B_3 B_1$$

$$X_3 = B_3 \overline{B_2} \overline{B_1} + \overline{B_3} B_1 + \overline{B_3} B_2$$


$$X_2 = \overline{B_2} \overline{B_1} + B_2 B_1$$

$$X_1 = \overline{B_1}$$

(6)  
Step 2 :- programming table.

product terms.	AND Gate inputs. $B_4 \quad B_3 \quad B_2 \quad B_1$				outputs.
1	1	-	-	-	
2	-	1	1	-	$X_4 = B_4 + B_3 B_2 + B_3 B_1$
3	-	1	-	1	
4	-	1	0	0	
5	-	0	-	1	$X_3 = B_3 \bar{B}_2 \bar{B}_1 + \bar{B}_3 B_1 + \bar{B}_3 B_2$
6	-	0	1	-	
7	-	-	0	0	
8	-	-	1	1	$X_2 = \bar{B}_2 \bar{B}_1 + B_2 B_1$
9	-	-	-	-	
10	-	-	-	0	
11	-	-	-	-	$X_1 = \bar{B}_1$
12	-	-	-	-	

Step 3 :- logic diagram.

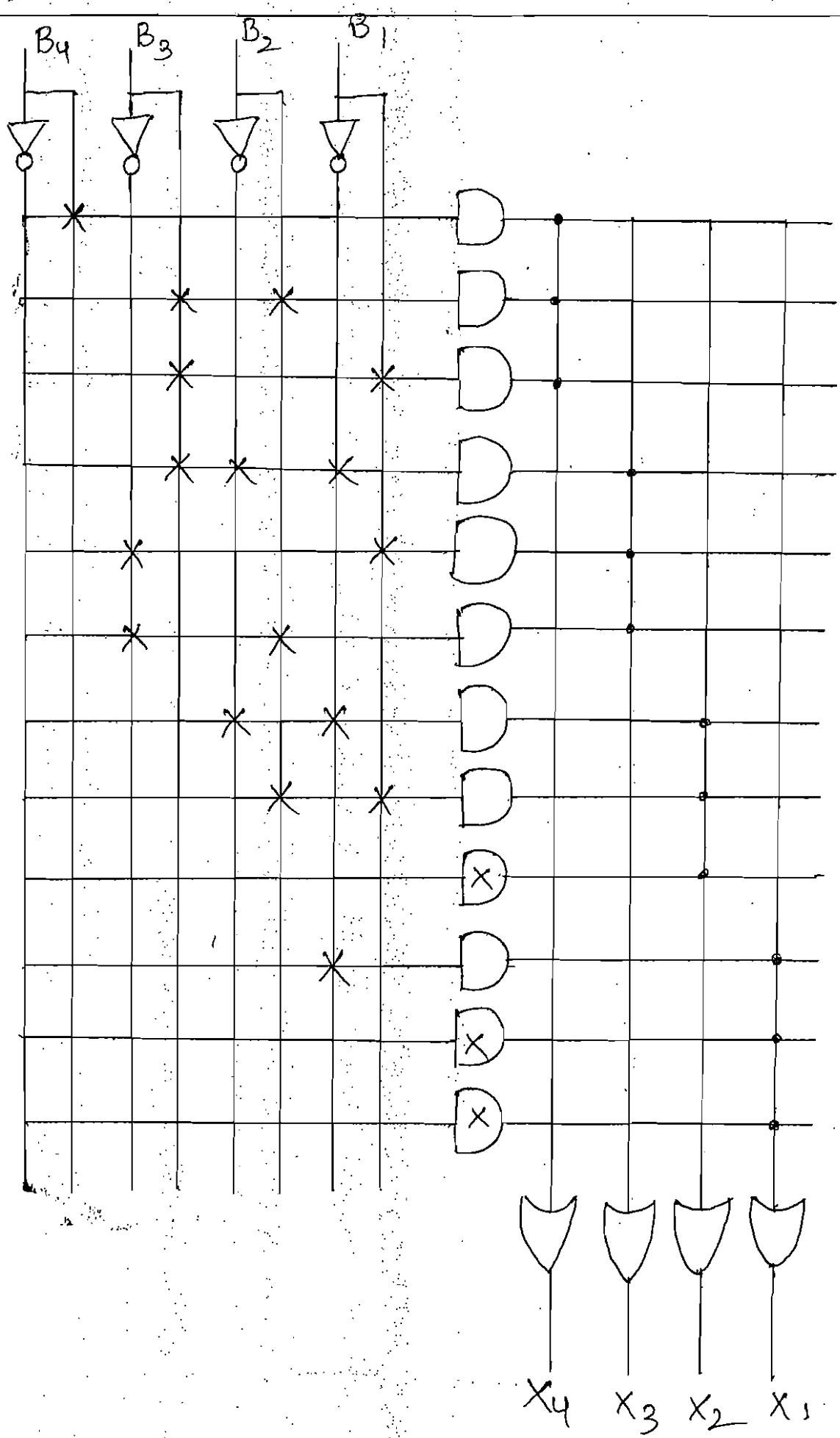

logic diagram.

Implement the following boolean functions using PAL with four inputs and 3-wide AND-OR structure. Also write the PAL programming table.

$$F_1(A, B, C, D) = \Sigma m(2, 12, 13)$$

$$F_2(A, B, C, D) = \Sigma m(7, 8, 9, 10, 11, 12, 13, 14, 15)$$

$$F_3(A, B, C, D) = \Sigma m(0, 2, 3, 4, 5, 6, 7, 8, 10, 11, 15)$$

$$F_4(A, B, C, D) = \Sigma m(1, 2, 8, 12, 13)$$

AB	CD	00	01	11	10
00		0	1	3	2
01		4	5	7	6
11		1, 2	1, 3	1, 4	1, 5
10		8	9	12	10

AB	CD	00	01	11	10
00		0	1	3	2
01		4	5	7	6
11		1, 2	1, 3	1, 4	1, 5
10		8	9	12	10

AB	CD	00	01	11	10
00		0	1	3	2
01		4	5	7	6
11		1, 2	1, 3	1, 4	1, 5
10		8	9	12	10

AB	CD	00	01	11	10
00		0	1	3	2
01		4	5	7	6
11		1, 2	1, 3	1, 4	1, 5
10		8	9	12	10

$$F_1 = AB\bar{C} + \bar{A}\bar{B}CD$$

$$F_2 = A + BCD$$


$$F_3 = \bar{A}B + CD + \bar{B}\bar{D}$$

$$\begin{aligned} F_4 &= \underbrace{ABC}_{1} + \underbrace{\bar{A}\bar{C}\bar{D}}_{2} + \underbrace{\bar{A}\bar{B}\bar{C}D}_{3} + \underbrace{\bar{A}\bar{B}\bar{C}\bar{D}}_{4} \\ &= F_1 + \bar{A}\bar{C}\bar{D} + \bar{A}\bar{B}\bar{C}D \end{aligned}$$

Step 2 :- programming table

product term	AND inputs A B C D	outputs F <sub>1</sub>
1	1 1 0 -	$F_1 = AB\bar{C} + \bar{A}\bar{B}CD$
2	0 0 1 0 -	
3	- - - - -	
4	1 - - - -	$F_2 = A + BCD$
5	1 1 1 1 -	
6	- - - - -	
7	0 1 - - -	$F_3 = \bar{A}B + CD + \bar{B}\bar{D}$
8	- - 1 1 -	
9	- 0 - 0 -	
10	- - - - 1	
11	1 - 0 0 -	$F_4 = F_1 + \bar{A}\bar{C}\bar{D} + \bar{A}\bar{B}\bar{C}D$
12	0 0 0 1 -	


Step 3 :- Implementation :-

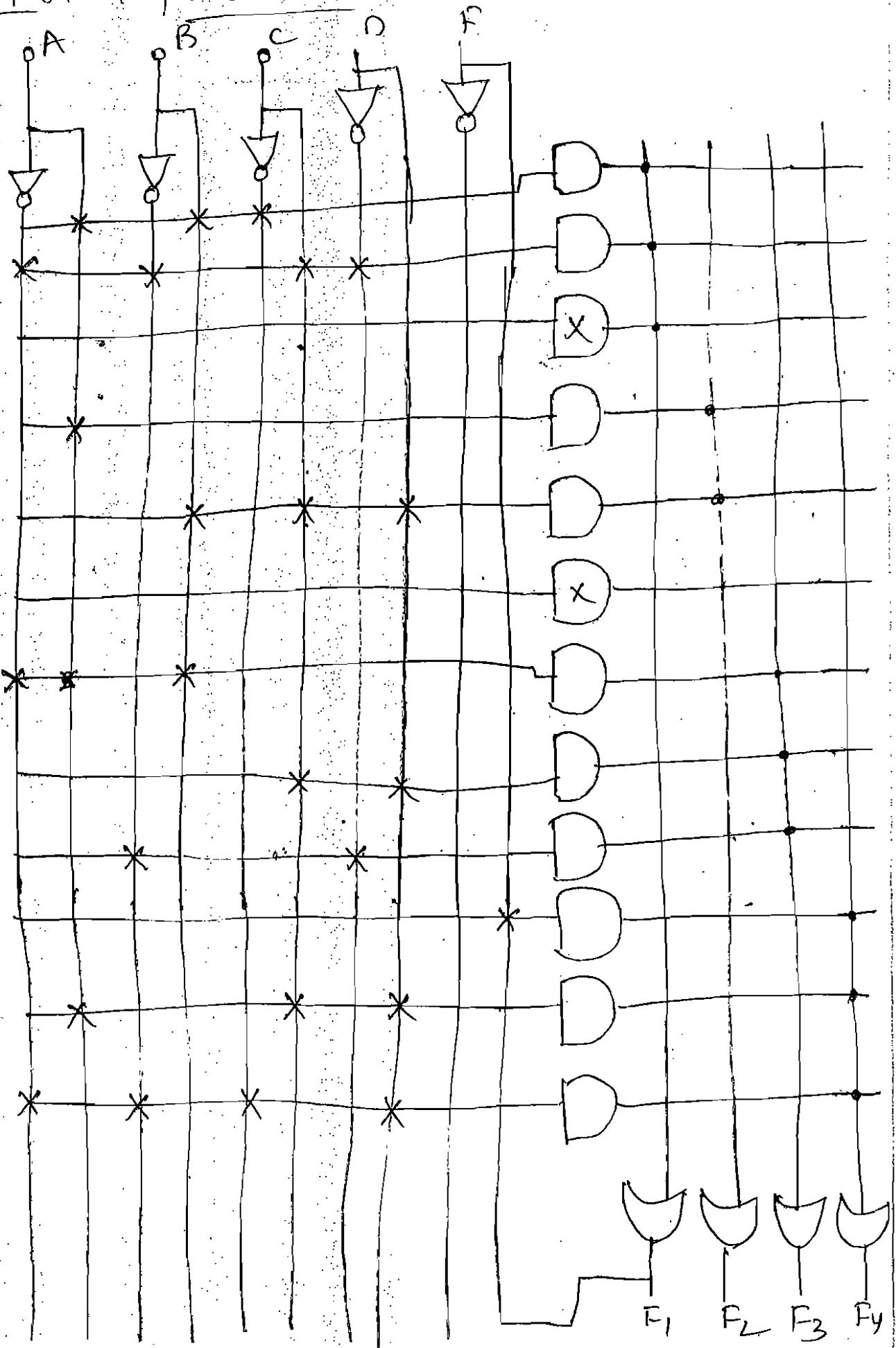

## (6)
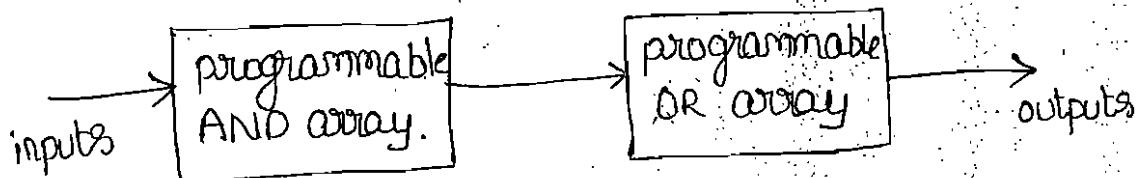
### PLA :- programmable logic Array

In programmable logic array where both the AND and OR arrays can be programmed. The product terms in the AND array may be shared by any OR gate to provide the required sum of products.




→ Implement the given boolean functions by using PLA.


$$A(x,y,z) = \Sigma m(1,2,4,6)$$

$$B(x,y,z) = \Sigma m(1,2,3,5,7)$$

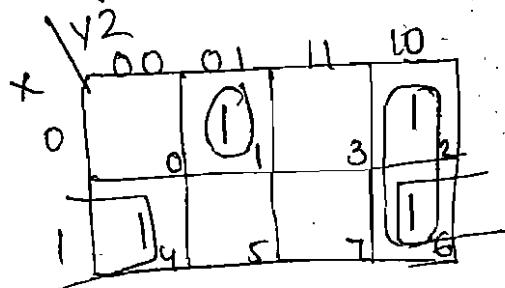Step 1 :- The K-maps for the functions A, B, their minimization, and the minimal expressions for both the true and complement of those in sum of products.


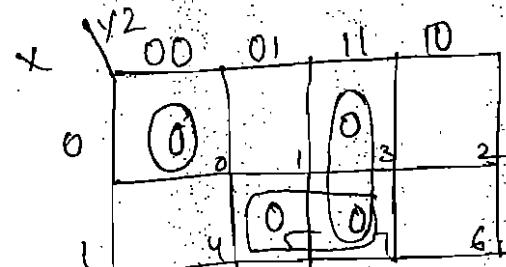
$$A(T) = x\bar{z} + y\bar{z} + \bar{x}\bar{y}z$$



$$A(C) \Rightarrow \bar{A} = xz + yz + \bar{x}\bar{y}z$$

$$A(C) = \bar{x}z + yz + \bar{x}\bar{y}z$$

K-map for A.

$$\begin{aligned}
 \text{Simplify } A(C) &= (\bar{x} + \bar{z}) \cdot (\bar{y} + \bar{z}) \cdot (x + y + z) \\
 &= (\bar{x} + \bar{z}) + (\bar{y} + \bar{z}) + (x + y + z) \\
 &= xz + yz + \bar{x}\bar{y}z
 \end{aligned}$$

$X^2$	00	01	11	10
0	0	1	1	1
1	4	5	6	7

$X^2$	00	01	11	10
0	0	0	1	3
1	1	0	5	7

$$B(T) = \overline{XY} + Z$$

$$\overline{B} = X\bar{Z} + \bar{Y}\bar{Z}$$


$$B(C) = \overline{X\bar{Z} + \bar{Y}\bar{Z}}$$

$$\begin{aligned} \text{Simplify } B(C) &= \overline{(Y+Z)(\bar{X}+Z)} \\ &= \overline{(Y+Z)} + \overline{(\bar{X}+Z)} \\ &= \bar{Y}\bar{Z} + X\bar{Z} \end{aligned}$$

$$\begin{aligned} \checkmark A(T) &= X\bar{Z} + Y\bar{Z} + \bar{X}\bar{Y}Z & B(T) &= \bar{X}Y + Z \\ A(C) &= XZ + YZ + \bar{X}\bar{Y}\bar{Z} & B(C) &= \bar{Y}\bar{Z} + X\bar{Z} \end{aligned}$$

Step 2 :- programming table.

product term	inputs $x$	$y$	$z$	outputs $A(T)$	$A(C)$	$B(T)$	$B(C)$
$X\bar{Z}$	1	-	0	1	-	-	1
$Y\bar{Z}$	-	1	0	-	-	-	-
$\bar{X}\bar{Y}Z$	0	0	1	-	-	-	-
$XZ$	1	-	1	-	1	-	-
$YZ$	-	1	1	-	1	-	-
$\bar{X}\bar{Y}\bar{Z}$	0	0	0	-	1	-	-
$\bar{X}Y$	0	1	-	-	-	1	-
$Z$	0	-	1	-	-	1	-
$\bar{Y}\bar{Z}$	-	0	0	-	-	-	1
$X\bar{Z}$	1	-	0	-	-	-	1

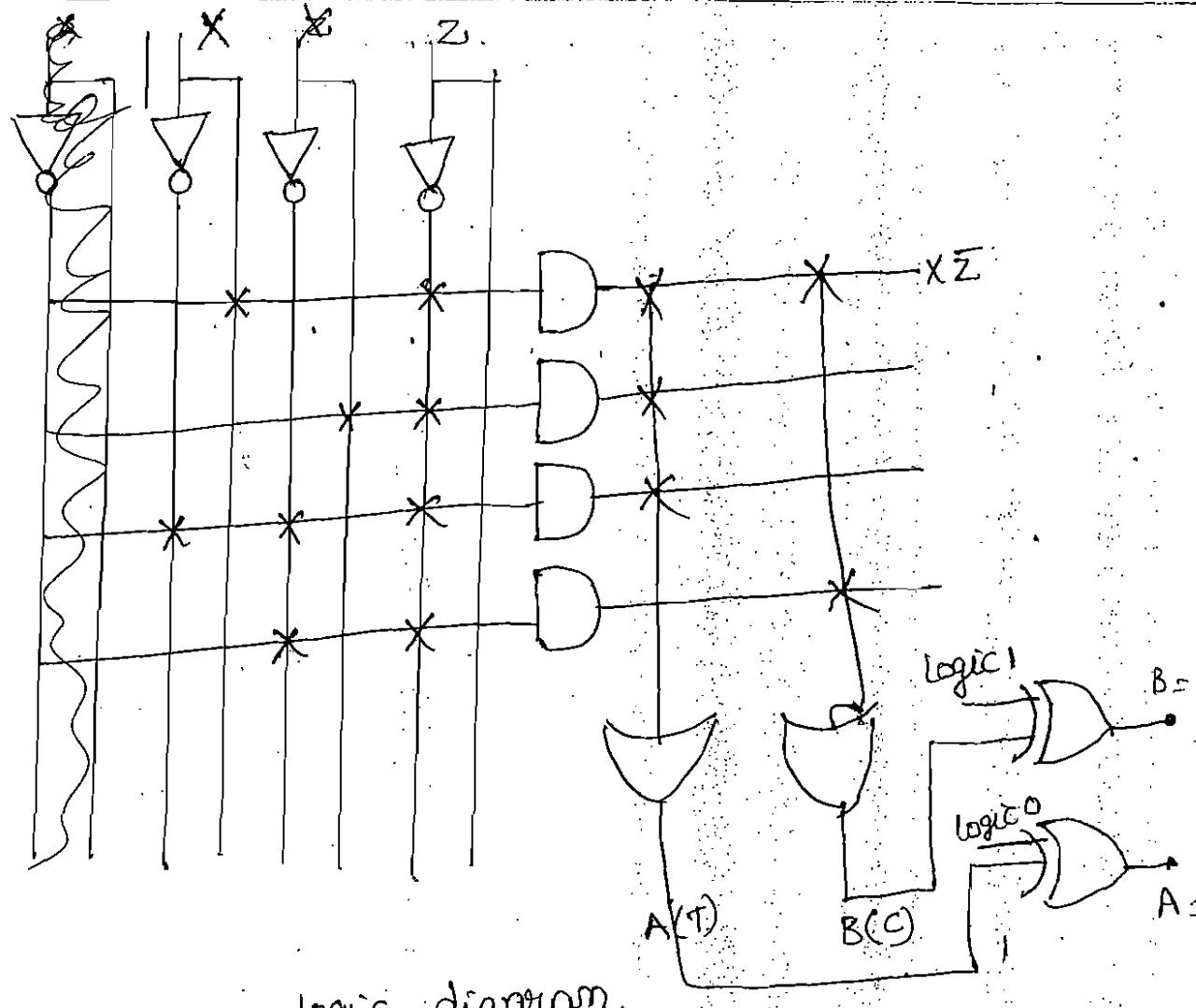


logic diagram.

→ Implement the following boolean functions  $F_1$  &  $F_2$  of a combinational logic circuit using PLA.


$$F_1(A, B, C) = \text{Em}(3, 4, 5, 7)$$

$$F_2(A, B, C) = \text{Em}(1, 4, 6).$$

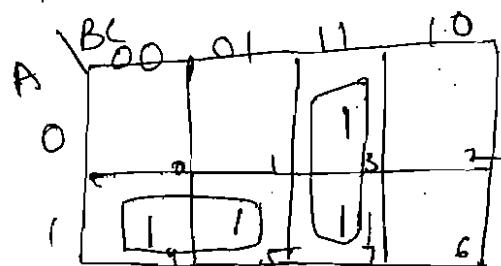Step 1:- K-map for  $F_1$  (T-S-E form) complement form



$$F_1 = A\bar{B} + BC$$

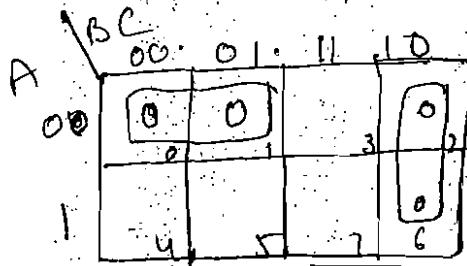

$$\begin{aligned} \overline{F_1} &= (A+B)(\bar{B}+C) \\ &= (\overline{A}+B) + (\bar{B}+C) \end{aligned}$$

$$F_1(T) = AB + BC$$

$$F_1(C)$$

$$= (\bar{A} \cdot \bar{B}) + \bar{\bar{B}} \cdot \bar{C}$$

$$= \bar{A} \cdot \bar{B} + B \cdot \bar{C}$$

K-map for  $F_2$  (true form)

		BC		AB	
		00	01	11	10
A		0	0	1	3
0					2
1		4	5	7	6

$$F_2 = \bar{A}\bar{B}C + A\bar{C}$$

K-map for  $F_2$  (complement form)

		BC		AB	
		00	01	11	10
A		0	0	1	0
0					1
1		0	1	0	0

$$\begin{aligned} F_2 &= (\bar{A} + C) \cdot (\bar{B} + \bar{C}) \cdot (\bar{A} + \bar{C}) \\ &= (\bar{A} + C) + (\bar{B} + \bar{C}) + (\bar{A} + \bar{C}) \\ &= \bar{A} \cdot \bar{C} + B \cdot C + A \cdot C. \end{aligned}$$

$$F_1(T) = A\bar{B} + BC$$

$$F_1(C) = \bar{A}\bar{B} + B\bar{C}$$


$$F_2(T) = \bar{A}\bar{B}C + A\bar{C}$$

$$F_2(C) = \bar{A}\bar{C} + BC + AC$$

when we take  $F_1(T)$  &  $F_2(T)$  get 4 product terms and also having same number of product terms while taking  $F_1(C)$ ,  $F_2(C)$ ,  $F_1(T)$  &  $F_2(T)$ . So we have to consider  $F_1(T)$  &  $F_2(T)$ .

Step 2 :- programming table

product terms	inputs			outputs	
	A	B	C	$F_1(T)$	$F_2(T)$
$A\bar{B}$	1	0	-	1	-
$B\bar{C}$	-	1	1	1	0
$\bar{A}\bar{B}C$	0	-	0	0	+
$A\bar{C}$	1	-	1	-	1

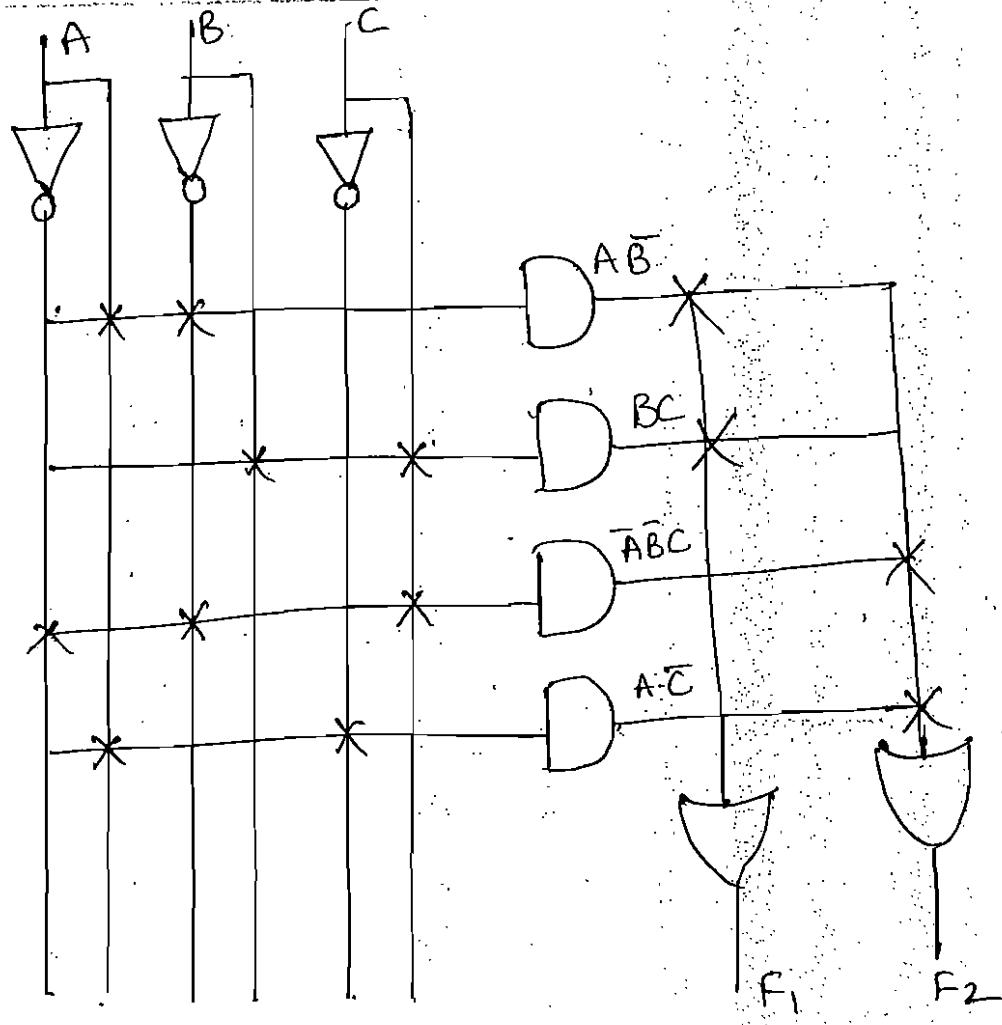

logic diagram.

→ Implement the following multi boolean function using  $3 \times 4 \times 2$  PLA.

$$F_1(a_2, a_1, a_0) = \text{Em}(0, 1, 3, 5)$$

$$F_2(a_2, a_1, a_0) = \text{Em}(3, 5, 7)$$

step 1:- K-maps.

		a <sub>0</sub>			
		00	01	11	10
a <sub>2</sub>	0	1	0	1	0
	1	4	5	7	6

$$f_1(T) = \bar{a}_1 a_0 + \bar{a}_2 \bar{a}_1 + \bar{a}_2 a_0$$

		a <sub>0</sub>			
		00	01	11	10
a <sub>2</sub>	0	0	1	1	0
	1	0	0	0	1

$$f_1 = (\bar{a}_2 + a_0)(\bar{a}_2 + \bar{a}_1)(\bar{a}_1 + a_0)$$

$$f_1(C) = \bar{a}_2 \cdot a_0 + \bar{a}_2 \cdot \bar{a}_1 + \bar{a}_1 \cdot \bar{a}_0 \\ = a_2 \cdot \bar{a}_0 + a_2 \cdot a_1 + a_1 \cdot \bar{a}_0$$

$f_2$  (True form)

$a_2 \backslash a_1 \backslash a_0$	00	01	11	10
0	0	1	1	0
1	1	0	0	1

$$f_2(T) = a_2 a_0 + a_1 a_0$$

$F_2$  (complement form..)

$a_2 \backslash a_1 \backslash a_0$	00	01	11	10
0	0	0	0	0
1	0	0	0	0

$$\bar{F}_2 = (\bar{a}_0) \cdot (a_2 + a_1)$$

$$F_2(C) = \bar{a}_0 + \bar{a}_2 \cdot \bar{a}_1$$

$$F_1(T) = \bar{a}_1 a_0 + \bar{a}_2 \bar{a}_1 + \bar{a}_2 a_0$$

$$F_1(C) = a_2 \cdot \bar{a}_0 + a_2 \cdot a_1 + a_1 \cdot \bar{a}_0$$


$$F_2(T) = a_2 a_0 + a_1 a_0$$

$$F_2(C) = \bar{a}_0 + \bar{a}_2 \cdot \bar{a}_1$$

Step 2 :- PLA programming table.

product terms	Inputs $a_2 \ a_1 \ a_0$	outputs $F_1(T)$	$F_2(C)$
$\bar{a}_1 a_0$	— 0 1	1	—
$\bar{a}_2 \bar{a}_1$	0 0 —	1	1
$\bar{a}_2 a_0$	0 — 1	1	—
$\bar{a}_0$	— — 0	—	1

Step 3 :- logic diagram :-

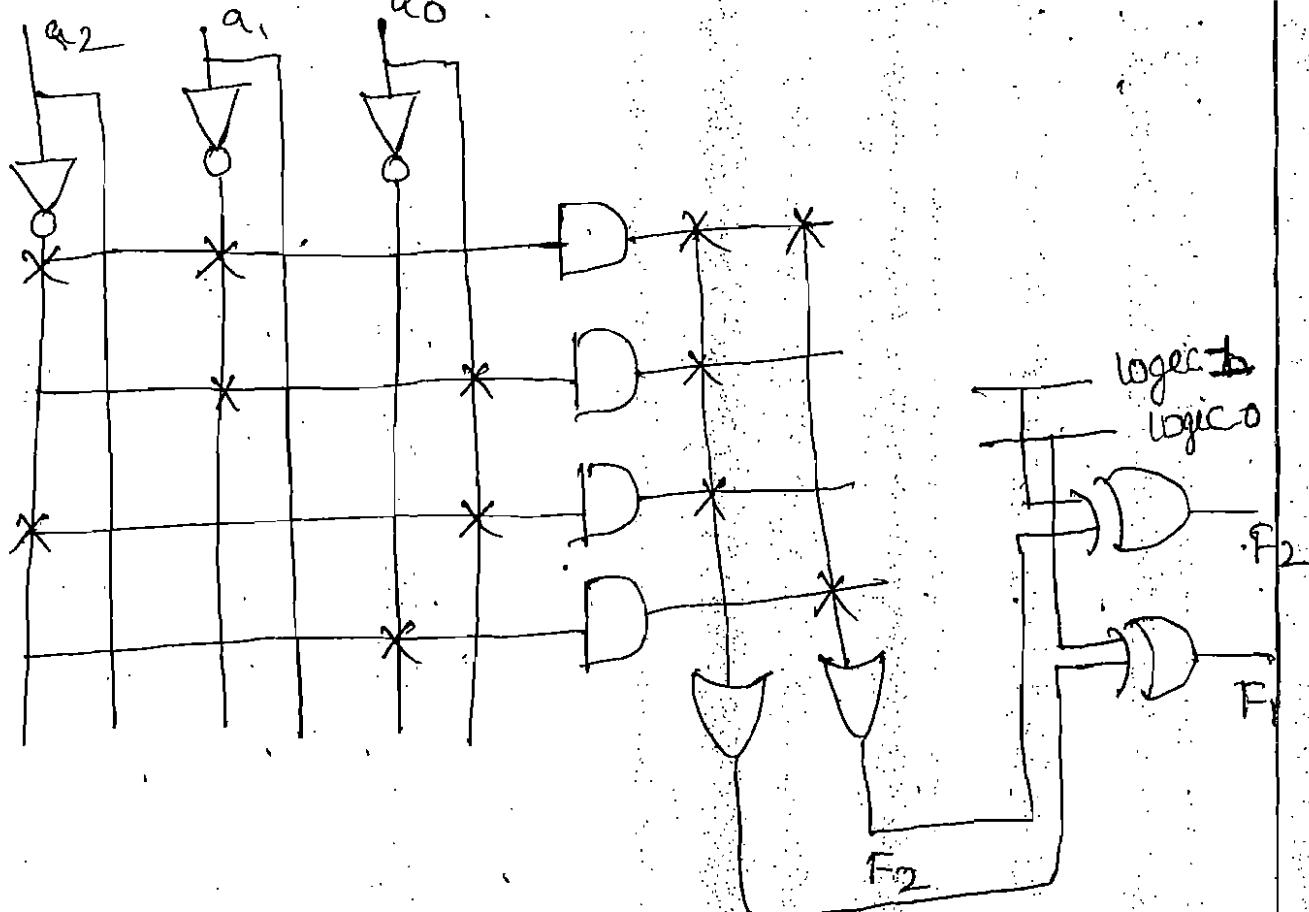


→ Implement the following using PLA.

$$A(x,y,z) = \Sigma m(1,2,4,6), \quad B(x,y,z) = \Sigma m(0,1,6,7)$$

$$C(x,y,z) = \Sigma m(2,6).$$

Step 1 :- K-map.

K-map for A (True form).

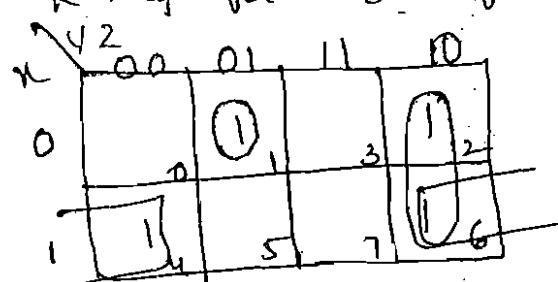

$$A(T) = x\bar{z} + y\bar{z} + \bar{z}\bar{y}z$$

K-map for A (Complement form).

$xz$	00	01	11	10
$\bar{x}$	0	0	0	1
0	0	1	1	0
1	4	5	7	6

$$A(C) = (x+y+z) \cdot (\bar{y}+\bar{z}) \cdot (\bar{x}+\bar{z})$$

$$= \bar{x}\bar{y}\bar{z} + yz + xz.$$

K-map for  $B(T)$

$x \backslash y$	00	01	10	11
0	1	1	3	2
1	4	5	7	6

$$B(T) = \overline{x}\overline{y} + xy$$

K-map for  $C(T)$

$x \backslash y$	00	01	11	10
0	0	1	3	2
1	4	5	7	6

$$C(T) = y\overline{z}$$

K-map for  $B(C)$

$x \backslash y$	00	01	11	10
0	0	1	0	0
1	0	0	1	0

$$B(C) = (\overline{x}+y)(x+\overline{y})$$

$$= \overline{x}\overline{y} + \overline{x}\overline{y}$$

$$= xy + \overline{xy}$$

K-map for  $C(C)$

$x \backslash y$	00	01	11	10
0	0	0	0	3
1	0	0	0	6

$$C(C) = \overline{y} \cdot \cancel{z} \cdot (\overline{y} \cdot \cancel{z})$$

$$= \overline{y} + \overline{z}$$


$$= \overline{y} + z$$

Step 2 :- programming table.

product term	inputs			outputs		
	$x$	$y$	$z$	$A(T)$	$B(T)$	$C(T)$
$x\overline{z}$	1	-	0	1	-	-
$y\overline{z}$	-	1	0	1	-	1
$\overline{x}\overline{y}z$	0	0	1	1	-	-
$\overline{x}\overline{y}$	0	0	-	-	1	-
$xy$	1	1	-	-	1	-


Step - 3

Logic diagram :-

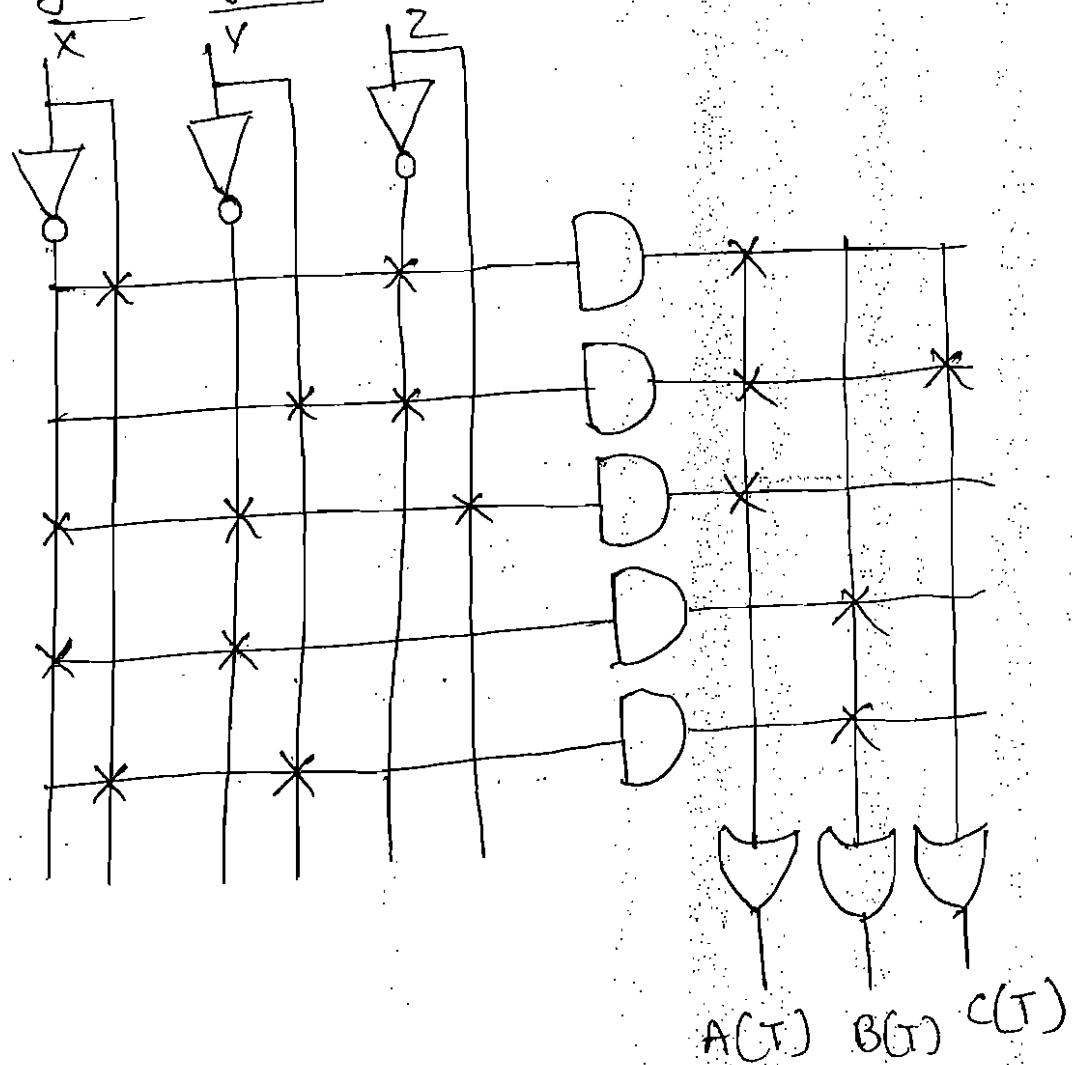


Given the logic implementation of a  $3 \times 4$  bit ROM using a decoder of a suitable size.

A  $32 \times 4$  bit ROM is to be implemented. It consists of 32 words of four bits each. There must be five input lines that form the binary numbers from 0 through 31 for the address. The five inputs are decoded into 32 distinct outputs by means of a  $5 \times 32$  decoder. Each output of the decoder represents a memory address. The 32 outputs of the decoder are connected to each of the four OR gates.

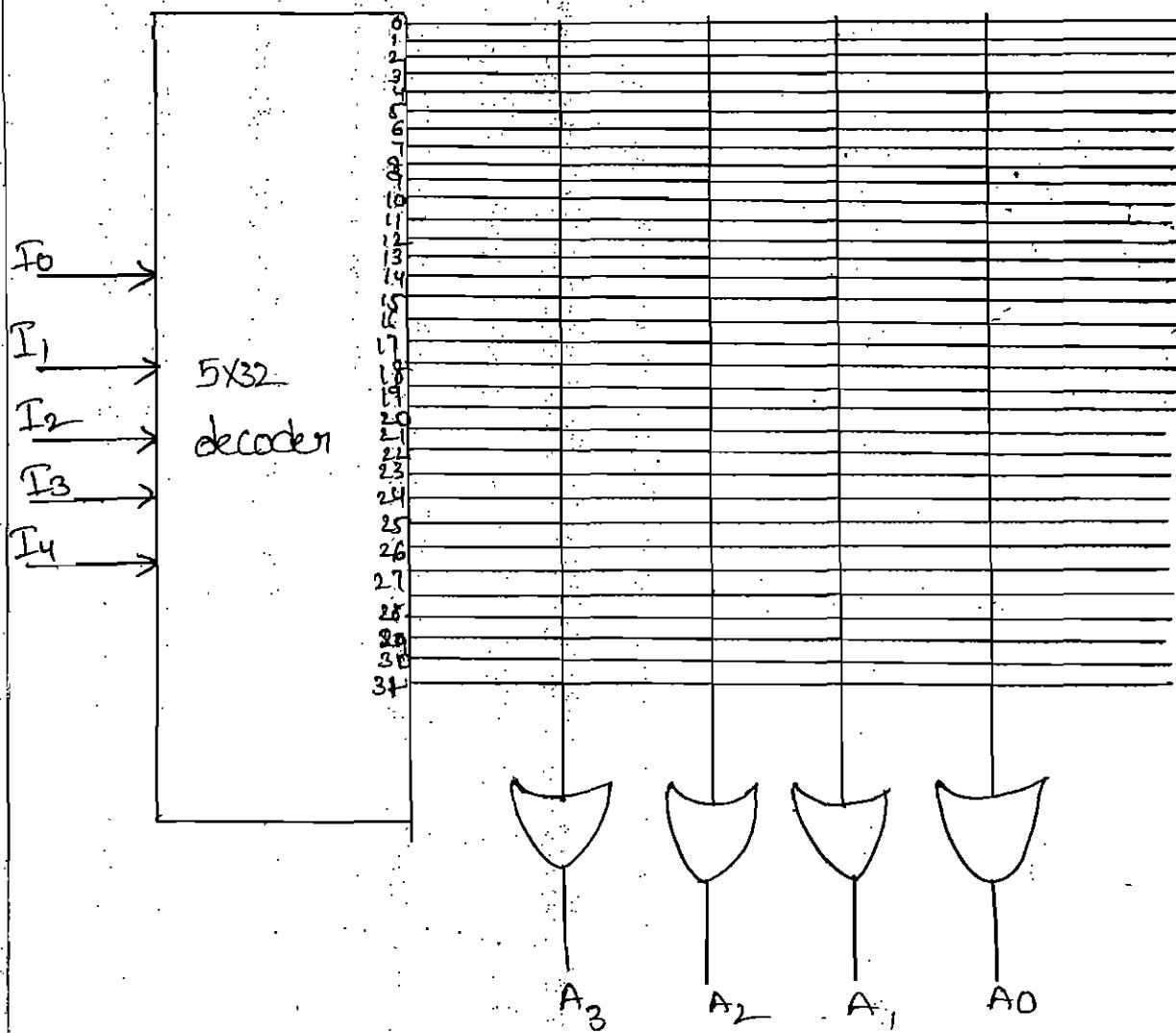

$32 \times 4$  bit ROM.

$\rightarrow 16 \times 8$  ROM.

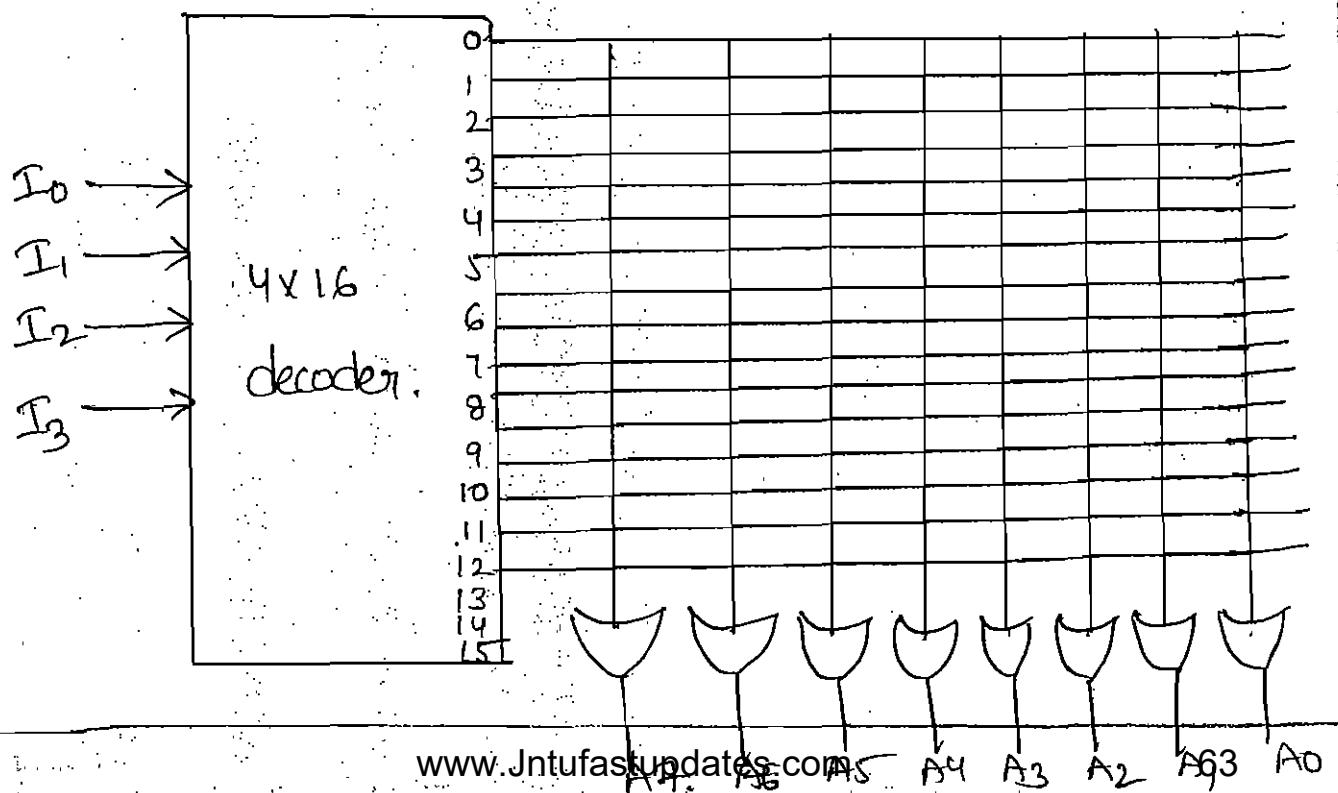

## Comparison between PROM, PLA and PAL.

PROM	PLA	PAL
1. AND array is fixed and OR array is programmable.	1. Both AND and OR arrays are programmable.	1. OR array is fixed and AND array is programmable.
2. cheaper and simple to use	2. costliest and more complex than PAL and PROM.	2. cheaper and simpler.
3. ALL minterms are decoded.	3. AND array can be programmed to get desired minterms.	3. AND array can be programmed to get desired minterms.
4. only Boolean functions in standard SOP form can be implemented using PROM.	4. Any Boolean function in SOP form can be implemented using PLA.	4. Any Boolean function in SOP form can be implemented using PAL.

→ Implement a Binary to BCD code converter by using PAL

→ I am taking 3-bit Binary P.

Binary			BCD code			
B <sub>3</sub>	B <sub>2</sub>	B <sub>1</sub>	C <sub>4</sub>	C <sub>3</sub>	C <sub>2</sub>	C <sub>1</sub>
0	0	0	0	0	0	0
0	0	1	0	0	0	1
0	1	0	0	0	1	0
0	1	1	0	0	1	1
1	0	0	0	1	0	0
1	0	1	0	1	0	1
1	1	0	0	1	1	0
1	1	1	0	1	1	1

→ Scan taking 4-binary.

$B_4\ B_3\ B_2\ B_1$	$C_8\ C_7\ C_6\ C_5\ C_4\ C_3\ C_2\ X_1$
0 0 0 0	0 0 0 0 0 0 0 0
0 0 0 1	0 0 0 0 0 0 0 1
0 0 1 0	0 0 0 0 0 0 1 0
0 0 1 1	0 0 0 0 0 0 1 1
0 1 0 0	0 0 0 0 0 1 0 0
0 1 0 1	0 0 0 0 0 1 0 1
0 1 1 0	0 0 0 0 0 1 1 0
0 1 1 1	0 0 0 0 0 1 1 1
1 0 0 0	0 0 0 0 1 0 0 0
1 0 0 1	0 0 0 0 1 0 0 1
1 0 1 0	0 0 0 1 0 0 0 0
1 0 1 1	0 0 0 1 0 0 0 1
1 1 0 0	0 0 0 1 0 0 1 0
1 1 0 1	0 0 0 1 0 0 1 1
1 1 1 0	0 0 0 1 0 1 0 0
1 1 1 1	0 0 0 1 0 1 0 1

$$C_5 = \text{Em}(10, 11, 12, 13, 14, 15)$$

$$C_4 = \text{Em}(8, 9)$$

$$C_3 = \text{Em}(4, 5, 6, 7, 14, 15)$$

$$C_2 = \text{Em}(2, 3, 6, 7, 12, 13)$$

$$C_1 = \text{Em}(1, 3, 5, 7, 9, 11, 13, 15)$$

Step 1:- K-map.

K-map for $C_5$			
$B_4\bar{B}_3$	$\bar{B}_2\bar{B}_1$	00	01
00	00	1	3
01	01	4	5
11	11	12	13
10	10	14	15

K-map for $C_4$			
$B_4\bar{B}_3$	$\bar{B}_2\bar{B}_1$	00	01
00	00	1	3
01	01	4	5
11	11	12	13
10	10	14	15

K-map for $C_3$			
$B_4\bar{B}_3$	$\bar{B}_2\bar{B}_1$	00	01
00	00	1	3
01	01	4	5
11	11	12	13
10	10	14	15

$$B_4 B_3 + B_4 B_2$$

$$B_4 \bar{B}_3 \bar{B}_2$$

$$\bar{B}_4 B_3 + B_3 B_2$$

K-map for $C_2$			
$B_4\bar{B}_3$	$\bar{B}_2\bar{B}_1$	00	01
00	00	1	3
01	01	4	5
11	11	12	13
10	10	14	15

K-map for $C_1$			
$B_4\bar{B}_3$	$\bar{B}_2\bar{B}_1$	00	01
00	00	1	3
01	01	4	5
11	11	12	13
10	10	14	15


$$B_4 B_3 \bar{B}_2 + \bar{B}_4 B_2$$

$$B_1$$

step 2:- programming table

product terms	inputs $B_4 \ B_3 \ B_2 \ B_1$	output
1	1 - 1 -	$C_5 = B_4 B_3 + B_4 B_2$
2	1 - 1 -	$C_4 = B_4 \bar{B}_3 \bar{B}_2$
3	1 0 0 -	$C_4 = B_4 \bar{B}_3 \bar{B}_2$
4	- - - -	
5	0 1 - -	$C_3 = \bar{B}_4 B_3 + B_3 B_2$
6	- 1 1 -	$C_3 = \bar{B}_4 B_3 + B_3 B_2$
7	1 1 0 -	$C_2 = B_4 \bar{B}_3 \bar{B}_2 + B_4 B_2$
8	0 - 1 -	$C_2 = B_4 \bar{B}_3 \bar{B}_2 + B_4 B_2$
9	- - - 1	$C_1 = B_1$
10	- - - -	

Step 3 :- logic diagram

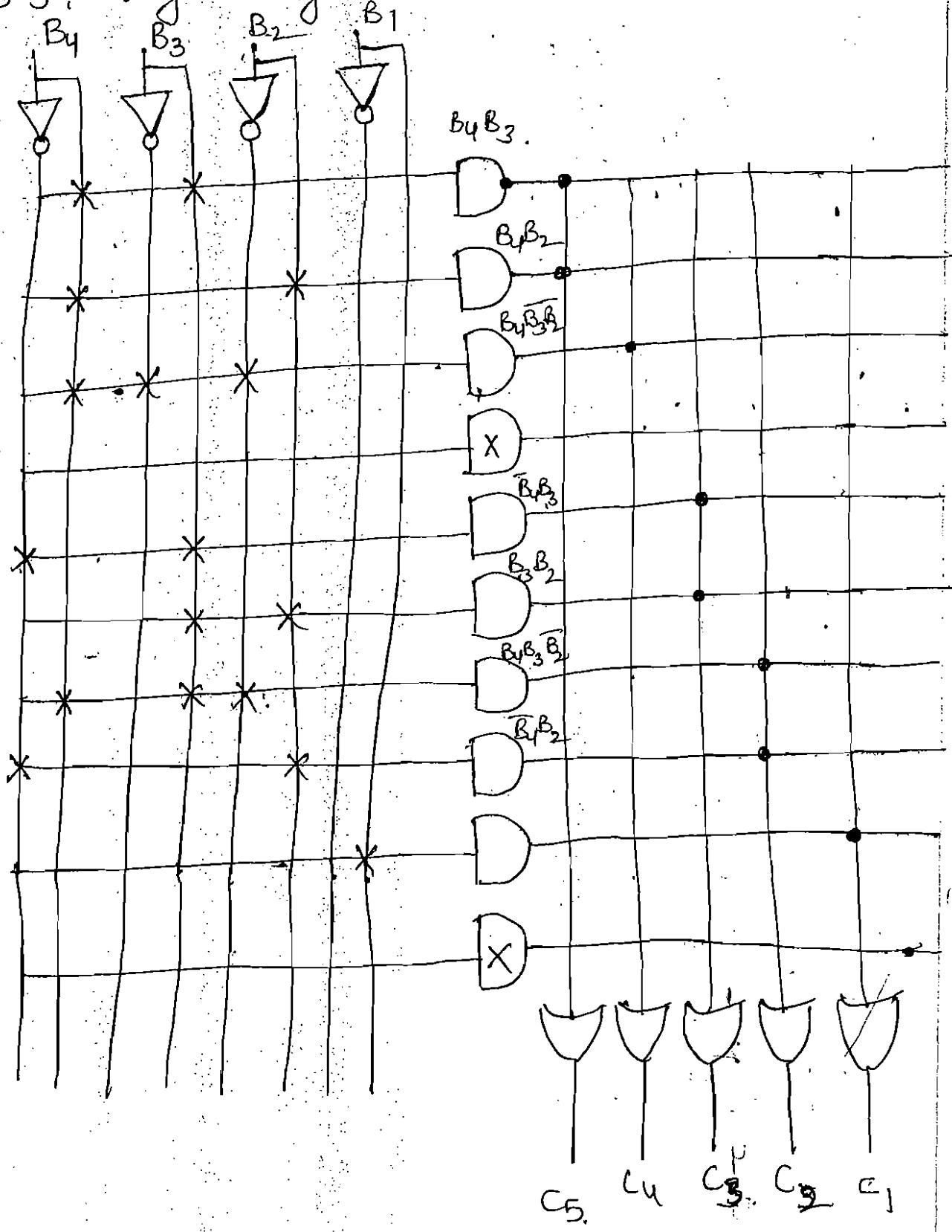

## **UNIT 5**

# **Sequential Circuits**


## **Combinational Circuit and Sequential Circuits:**

Logic Circuits can be divided into :

1. Combinational Logic Circuit
2. Sequential Logic Circuit

### ***Combinational Logic Circuit :***

Combinational Logic circuit contains logic gates where its output is determined by the combination of the current input, regardless of the output or the prior combination of input. Basically, combinational circuit can be depicted by FIG 3.1 below:

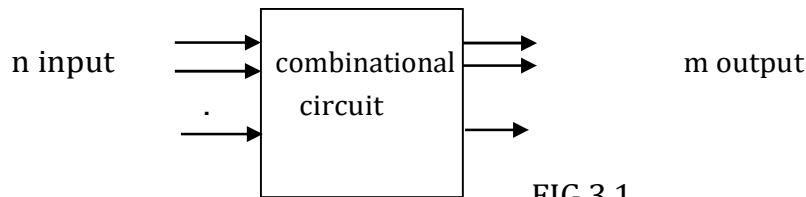


**FIG 3.1**

Examples of Combinational circuits in the computer system are decoder, parallel adder, and multiplexer.

### ***Sequential Logic Circuit :***

Sequential Logic Circuit contains logic gates arranged in parallel and its output is not only determined by the combination of the current input, but also the prior output. The circuit also contains memory elements that enable it to store the information of the prior output. Generally, sequential circuits can be depicted by FIG 3.2 below:

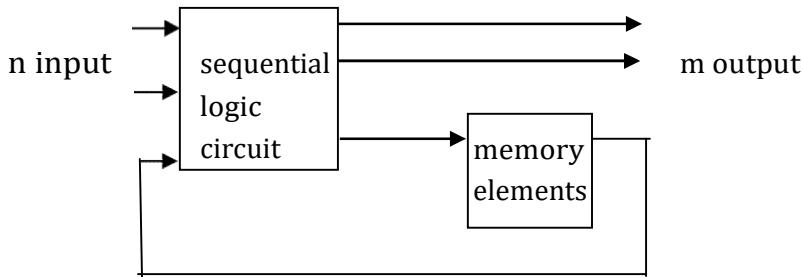

**FIG 3.2**

Examples of sequential circuits are like FLIP FLOPS, registers, counters and serial adders

- Unlike combinational logic circuits, the output of a *sequential* logic circuit depends not only on the current inputs but also on the current state of *memory elements* in the circuit.
- The binary information stored in the memory elements determines the *state* of the circuit at any given time.
- A typical sequential circuit consists of some combinational logic circuitry combined with memory elements to store the state of the circuit.
- The current state of the circuit is fed back to the combinational logic and can be considered as additional inputs to the circuit. This is called *feedback*.

Sequential circuits can be divided into

1. Synchronous
2. Asynchronous

In synchronous sequential circuit, all flip-flops are moved by the same clock pulse so that all flip-flops involved change simultaneously.

In asynchronous circuit, the change of flip-flop condition depends on the change that occurs on the input and the late time that is in the circuit. The memory elements in clocked sequential circuits are called *flip-flops*.

**difference between a latch and a flip-flop.** Now, let's make the answer easy to understand by tabulating some simple & important differences between latch and Flip-Flop.

Flip-Flop	Latch
The state of circuit changes only when the control signal goes from high to low or low to high (i.e. sensitive to signal change only).	Changes state as soon as the input signals change (of course there is some propagation delay).
Synchronous	Asynchronous
Edge triggered which means that the output of the circuit changes when there is a change in clock pulse (it may be a positive or negative edge of the clock pulse).	Level triggered which means that the output of the circuit depends on the level of the enable signal (either 1 or 0).
Built from latches (a FF is like a clocked latch). FF is used as a register.	Built from logic gates.
Works on clock pulses	Works on enable function input
Has a clock signal	Does not have a clock signal
Edge sensitive i.e. content of FF change only either at the rising or falling edge of the enable signal (usually the controlling clock signal). After the rising or falling edge of the clock signal, the content of FF remains constant even if the input changes.	Level sensitive i.e. content of latch changes immediately when there is a change in its inputs. Output is sensitive for the duration of enable signal active pulse and thus, can transmit or receive data during the active pulse only.
Sampling of the inputs is done only at a clock event for example, rising edge, falling edge.	Sampling of the inputs is done continuously only when the enable signal is on.

## Flip-Flops

### 1. Introduction

The circuits stored information about the previous history of inputs are called storage or memory elements. A primitive storage element can be constructed from a small number of gates connecting the outputs back as inputs. These circuits are binary cells capable of storing one bit of information. They have two outputs, one for the normal value and one for the complement value of bit stored in it. Primitive memory elements actually fall into two board classes : *latches* and *flip-flop*.

If a latch has only data inputs, it is called an *unlocked latch* (or only latch). Level-sensitive latches have an additional enable input, sometimes called the *clock*. Level-sensitive latches continuously sample their inputs when they are enabled.

Any change in the level of the input is propagated through to the output. When the enable signal is unasserted, the last value of the inputs is determines the state held by the latch.

Flip-flops differ from latches in that their output change only with repeat to the clock, whereas latches change output when their inputs change. Flip-flops are characterized on the basis of the clock transition that cause the output change : there are *positive edge-triggered*, *negative edge-triggered*, and *master/slave* flip-flops.


A positive edge-triggered flip-flop samples its inputs on the low-to-high clock transition. A negative edge-triggered flip-flop works in a similar fashion, with the input sampled on the high-to-low clock transition.

A master-slave flip-flop is constructed from two stage separate flip-flops. The first stage ( first flip-flop) samples the inputs on the rising edge of a clock signal. The second stage transfer them to the output on the falling edge of the clock signal.

These circuits have two additional control inputs. These are Preset and Clear, which force the output of the flip-flop or latch to the logic-1 or logic-0 state, respectively, independent of the flip-flop or latch inputs .
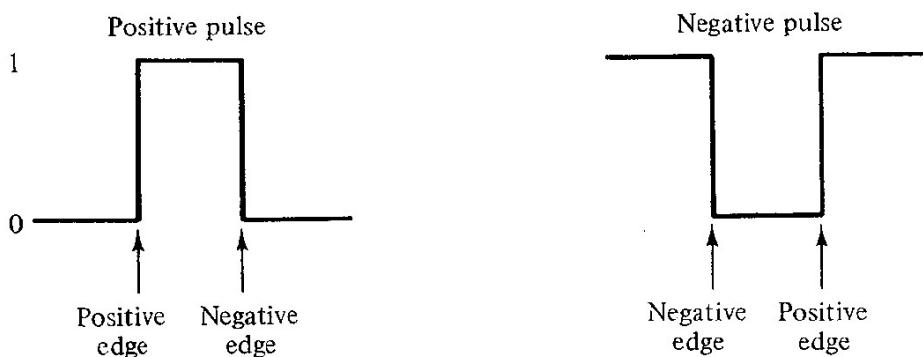
### Edge-Triggered Flip-Flop

- Edge triggered flip-flops respond only to a clock pulse edge and not to the level of the clock pulse.
- Edge-triggered flip-flops can be either positive or negative edge sensitive.




Definition of clock-pulse transition
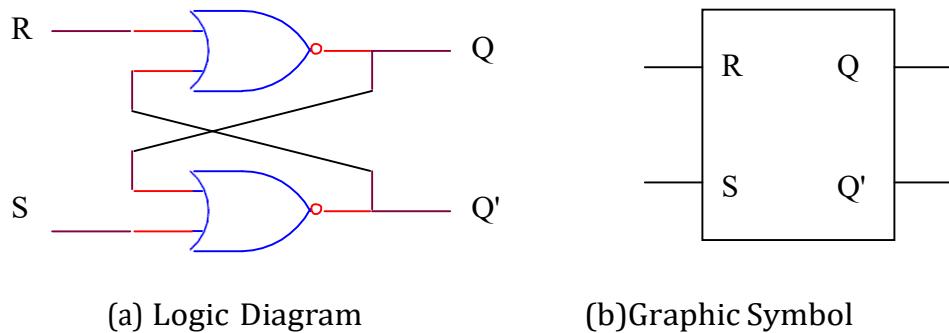
### S-R Latch:

- A S-R ( Set-Reset) latch is the simplest possible memory element.
- It is constructed by feeding the outputs of two NOR gates back to the other NOR gates input.
- The inputs R and S are referred to as the Reset and Set inputs, respectively.
- To understand the operation of the S-R latch consider the following scenarios :
  - **S=1 and R=0:** The output of the bottom NOR gate is equal to zero,  $Q' = 0$  .
  - Hence both inputs to the top NOR gate are equal to zero, thus,  $Q = 1$  .

- Hence, the input combination  $S=1$  and  $R=0$  leads to the latch being set to  $Q = 1$ .
- **$S=0$  and  $R=1$ :** Similar to the arguments above, the outputs become  $Q' = 1$  and  $Q = 0$ .
- We say that the latch is reset.
- **$S=0$  and  $R=0$ :** Assume the latch is set ( $Q' = 0$  and  $Q = 1$ ), then the output of the top NOR gate remains at  $Q = 1$  and the bottom NOR gate stays at  $Q' = 0$ .
- Similary, when the latch is in a reset state ( $Q' = 1$  and  $Q = 0$ ), it will remain there with this input combination.
- Therefore, with inputs  $S=0$  and  $R=0$ , the latch remains in its state.
- **$S=1$  and  $R=1$ :** This input combination must be avoided
- The logic diagram and graphic symbol are shown in Figure.3.3.
- The following truth table can be summarized the operation of the S-R latch.




S	R	Q	Q'	Comment
0	0	Q	Q'	Hold State
0	1	0	1	Reset
1	0	1	0	Set
1	1	-	-	Forbidden

(c) Truth table

**Figure.3.3** S-R latch with NOR gates.

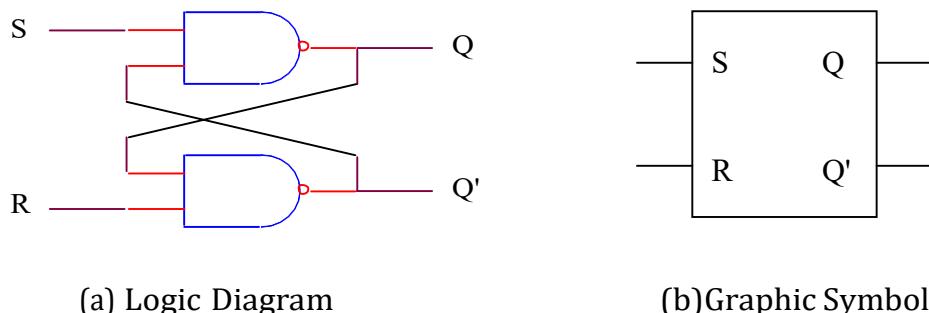- A S-R latch can also be constructed from NAND gates. The graphic symbol, logic diagram, and truth table of the latch are shown in Figure.3.4.




S	R	Q	$Q'$	Comment
1	1	Q	$Q'$	Hold State
0	1	1	0	Set
1	0	0	1	Reset
0	0	-	-	Forbidden

(c) Truth table

**Figure.3.4 S-R latch with NAND gates.**
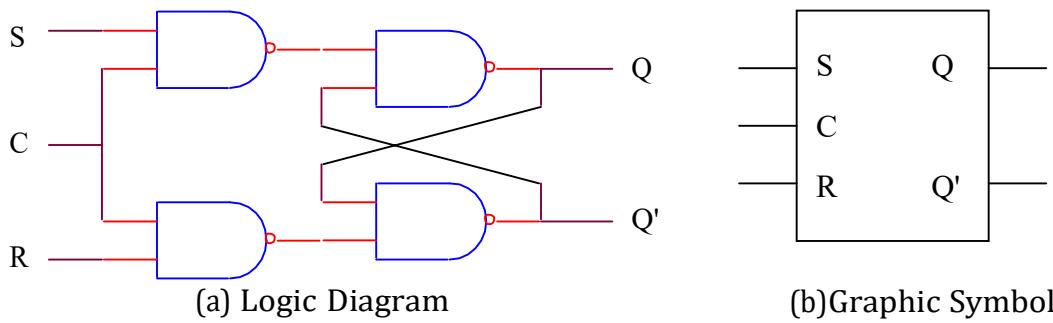
#### Level Sensitive (Clock) S-R Latch:

The operation of the S-R latch can be modified by providing an additional control input that determines when the state of the circuit is to be changed. The logic diagram, graphic symbol, and truth table of level sensitive S-R latch are shown in Figure.3.5 .




S	R	C	Q	$Q'$	Comment
0	0	1	Q	$Q'$	Hold State
0	1	1	0	1	Reset
1	0	1	1	0	Set
1	1	1	-	-	Forbidden
x	x	0	Q	$Q'$	Hold State

(c) Truth table

**Figure.3.5 Level Sensitive S-R latch with NAND gates.**
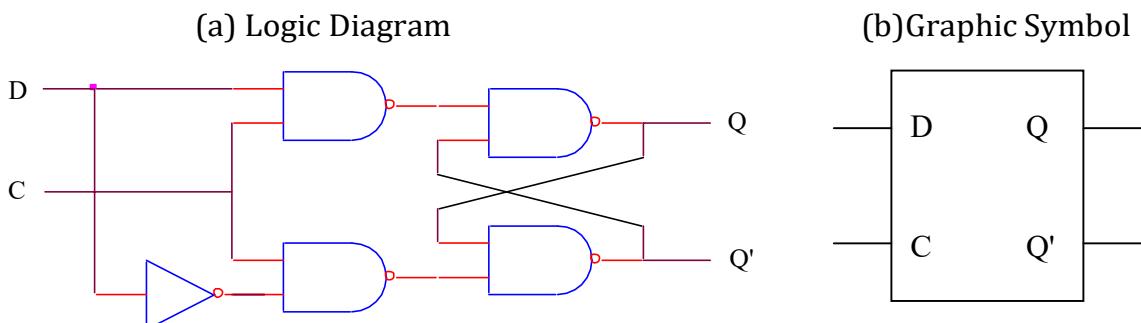
#### Level Sensitive (Clock) D (Delay) Latch :

One way to eliminate the undesirable condition of the indeterminate state in the S-R latch is to ensure that inputs S and R are never equal to 1 at the same time. This is done using a level sensitive D latch shown in Figure.3.6. The latch has only two inputs: D and C. The D input connects directly to the S input and its complement is applied to the R input. The D input is sampled when C is equal to 1. If D is equal to 1, the Q output goes to 1. If D is equal to 0, the Q output goes to 0. If C is equal to 0, the Q output remains in its previous state .




C	D	Q	Q'
1	0	0	1
1	1	1	0
0	x	Q	Q'

(c) Truth table

**Figure.3.6** Level Sensitive D latch with NAND gates.
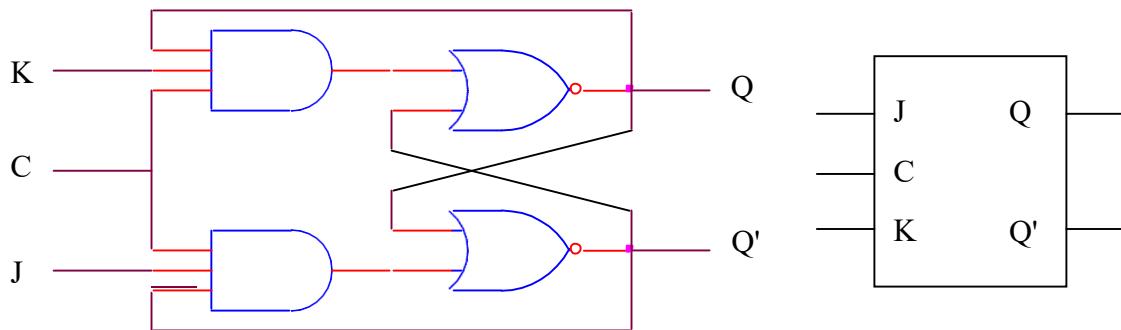
#### Level Sensitive (Clock) J-K Latch:

A level sensitive J-K latch shown in Figure.3.7 is a refinement of the S-R latch in that the indeterminate state of the S-R type is defined in the J-K type. Inputs J and K behave like inputs S and R to set and clear the latch, respectively. The input marked J is for set and the input marked K is for reset. When the both inputs J and K are equal to 1, the latch switches to its complement state, that is , if Q=1, it switches to Q=0, and vice versa. If the C is equal to 0, The output of the latch remains in its previous state .



(a) Logic Diagram

(b)Graphic Symbol

C	J	K	Q	Q'	Comment
1	0	0	Q	Q'	Hold
1	0	1	0	1	Reset
1	1	0	1	0'	Set
1	1	1	Q'	Q	Toggle
0	x	x	Q	Q'	Hold


(c) Truth table

**Figure.3.7** Level Sensitive J-K latch

#### S-R Flip-flop

The clocked SR flip-flop shown in Figure.3.8 consists of a basic NOR flip-flop and two AND gates. The outputs of the two AND gates remain at 0 as long as the clock pulse (or CP) is 0, regardless of the S and R input values. When the clock pulse goes to 1, information from the S and R inputs passes through to the basic flip-flop. With both S=1 and R=1, the occurrence of a clock pulse causes both outputs to momentarily go to 0. When the pulse is removed, the state of the flip-flop is indeterminate, ie., either state may result, depending on whether the set or reset input of the flip-flop remains a 1 longer than the transition to 0 at the end of the pulse..


1. If the value of both S and R are 0, the flip-flop will remain in its present condition (either 0 or 1).
2. If  $S = 0$  and  $R = 1$  (reset), then the flip-flop condition will change to 0 (its output,  $Q = 0$ ).
3. If  $S = 1$  (set) and  $R = 0$ , then the flip-flop condition will change to 1 (output,  $Q = 1$ ).
4. This circuit does not allow combinational input of input  $S = 1$  and  $R = 1$

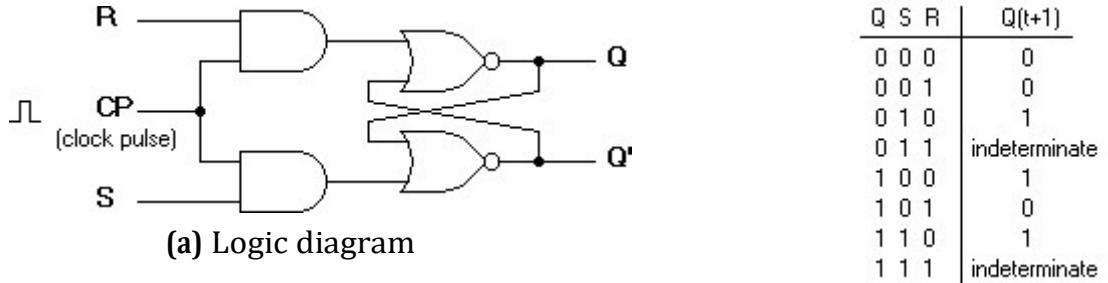

**Figure 3.8** SR flip-flop


### D Flip-Flop:

D flip flop is actually a slight modification of the above explained clocked SR flip-flop. From the figure you can see that the D input is connected to the S input and the complement of the D input is connected to the R input. The D input is passed on to the flip flop when the value of CP is '1'. When CP is HIGH, the flip flop moves to the SET state. If it is '0', the flip flop switches to the CLEAR state.

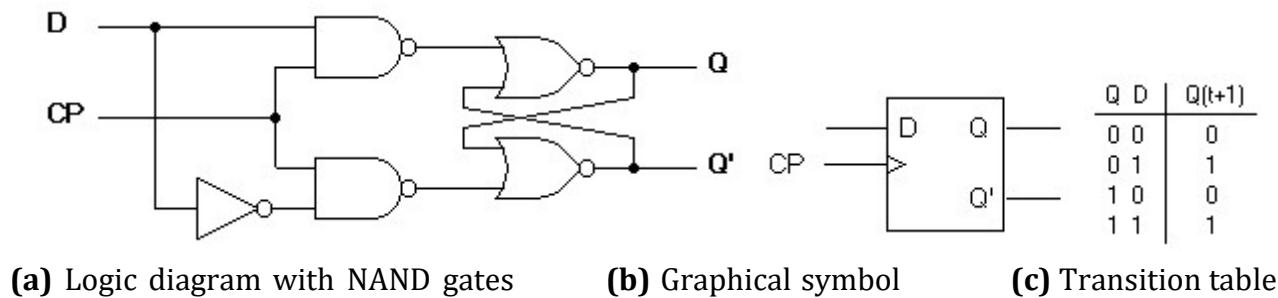

**Figure 3.9.** Clocked D flip-flop

### Positive-Edge Triggered:

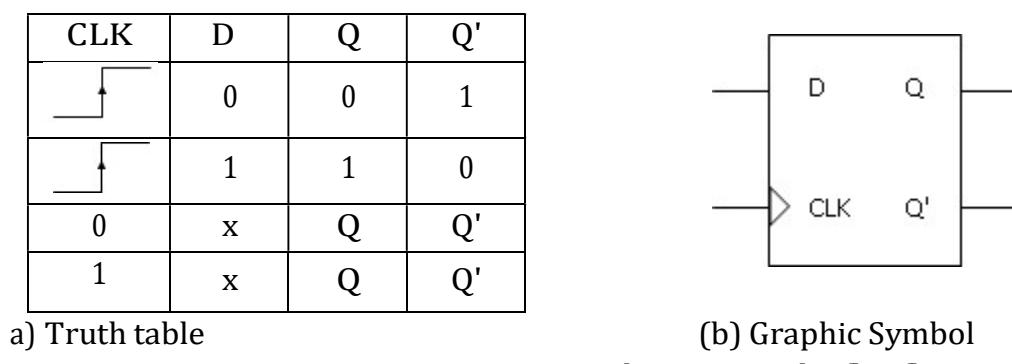


**Figure 3.10.** Positive edge-triggered D flip-flop.

### Negative-Edge Triggered:

CLK	D	Q	Q'
0	0	0	1
1	1	1	0
0	x	Q	Q'
1	x	Q	Q'

(a) Truth table

(b) Graphic Symbol

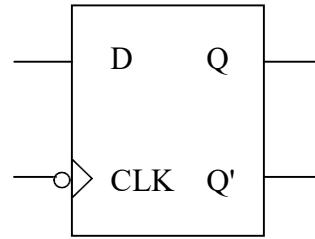

**Figure.3.11.** Positive edge-triggered D flip-flop.

### J-K Flip-Flop:


A J-K flip flop can also be defined as a modification of the S-R flip flop. The only difference is that the intermediate state is more refined and precise than that of a S-R flip flop.

The behavior of inputs J and K is same as the S and R inputs of the S-R flip flop. The letter J stands for SET and the letter K stands for CLEAR.

When both the inputs J and K have a HIGH state, the flip-flop switch to the complement state. So, for a value of  $Q = 1$ , it switches to  $Q=0$  and for a value of  $Q = 0$ , it switches to  $Q=1$ .

The circuit includes two 3-input AND gates. The output Q of the flip flop is returned back as a feedback to the input of the AND along with other inputs like K and clock pulse [CP]. So, if the value of CP is '1', the flip flop gets a CLEAR signal and with the condition that the value of Q was earlier 1. Similarly output  $Q'$  of the flip flop is given as a feedback to the input of the AND along with other inputs like J and clock pulse [CP]. So the output becomes SET when the value of CP is 1 only if the value of  $Q'$  was earlier 1.

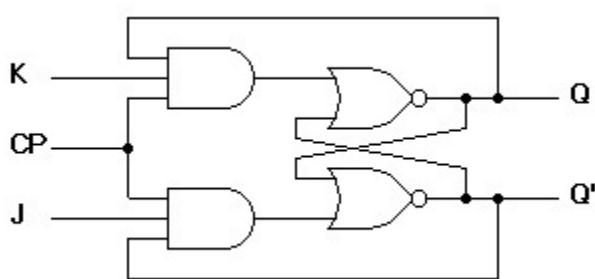The output may be repeated in transitions once they have been complimented for  $J=K=1$  because of the feedback connection in the JK flip-flop. This can be avoided by setting a time duration lesser than the propagation delay through the flip-flop. The restriction on the pulse width can be eliminated with a master-slave or edge-triggered construction.



(a) Logic diagram

Q	J	K	Q(t+1)
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

(b) Graphical symbol

(c) Transition table


**Figure.3.12.** Clocked JK flip-flop

Positive-Edge Triggered:

CLK	J	K	Q	Q'
	0	0	Q	Q'
	0	1	0	1
	1	0	1	0
	1	1	Q'	Q
0	x	x	Q	Q'
1	x	x	Q	Q'

(a)

Truth table

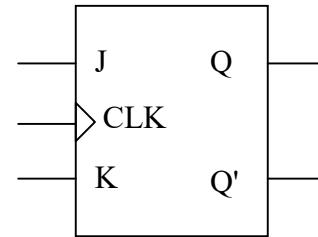

(b) Graphic Symbol

Figure.3.13. Positive edge-triggered J-K flip-flop.

Negative-Edge Triggered:

CLK	J	K	Q	Q'
	0	0	Q	Q'
	0	1	0	1
	1	0	1	0
	1	1	Q'	Q
0	x	x	Q	Q'
1	x	x	Q	Q'

(a) Truth table

(b) Graphic Symbol

Figure.3.14. Negative edge-triggered J-K flip-flop.


TFlip-Flop:

The T flip-flop is a single-input version of the J-K flip-flop. As shown in Figure.3.15, the T flip-flop is obtained from the J-k flip-flop when both inputs are tied together. The designation T comes from the ability of the flip-flop to *toggle*, or *complement*, its state. While input T is 1, The flip-flop complements its output when the clock pulse occurs. While T is 0, The output of the flip-flop remains in its previous state .


CLK	T	Q	Q'
	0	Q	Q'
	1	Q'	Q
0	x	Q	Q'
1	x	Q	Q'

(a)


Truth table

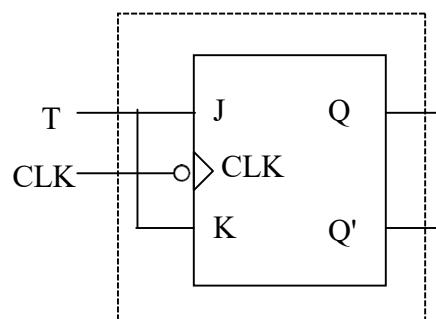

(b) Graphic Symbol

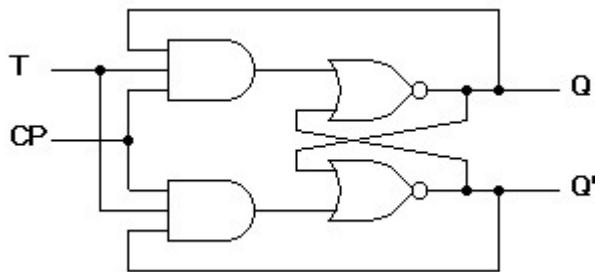**Figure.3.15.** Negative Edge-Triggered T flip-flop.

(a) Logic diagram

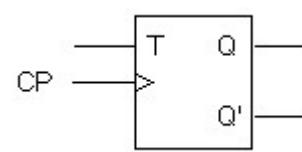

(b) Graphical symbol

Q	T	Q(t+1)
0	0	0
0	1	1
1	0	1
1	1	0

(c) Transition table


**Figure.3.16.** Clocked T flip-flop

### Introduction - Triggering of Flip-flops

The state of a flip-flop is changed by a momentary change in the input signal. This change is called a trigger and the transition it causes is said to trigger the flip-flop. The basic circuits require an input trigger defined by a change in signal level. This level must be returned to its initial level before a second trigger is applied. Clocked flip-flops are triggered by pulses.

The feedback path between the combinational circuit and memory elements can produce instability if the outputs of the memory elements (flip-flops) are changing while the outputs of the combinational circuit that go to the flip-flop inputs are being sampled by the clock pulse. A way to solve the feedback timing problem is to make the flip-flop sensitive to the pulse transition rather than the pulse duration.

The clock pulse goes through two signal transitions: from 0 to 1 and the return from 1 to 0. As shown in Figure.3.17 the positive transition is defined as the positive edge and the negative transition as the negative edge.

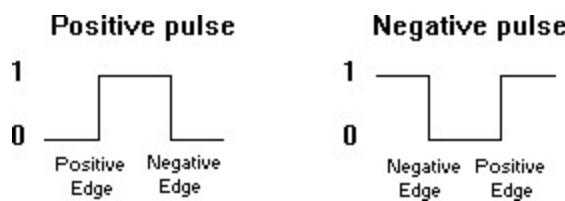
**Figure.3.17.** Definition of clock pulse transition

The clocked flip-flops already introduced are triggered during the positive edge of the pulse, and the state transition starts as soon as the pulse reaches the logic-1 level. If the

other inputs change while the clock is still 1, a new output state may occur. If the flip-flop is made to respond to the positive (or negative) edge transition only, instead of the entire pulse duration, then the multiple-transition problem can be eliminated.


### **Introduction - Master-Slave Flip-Flop:**

A master-slave flip-flop is constructed from two separate flip-flops. One circuit serves as a master and the other as a slave. The logic diagram of an SR flip-flop is shown in Figure 3.18. The master flip-flop is enabled on the positive edge of the clock pulse CP and the slave flip-flop is disabled by the inverter. The information at the external R and S inputs is transmitted to the master flip-flop. When the pulse returns to 0, the master flip-flop is disabled and the slave flip-flop is enabled. The slave flip-flop then goes to the same state as the master flip-flop.

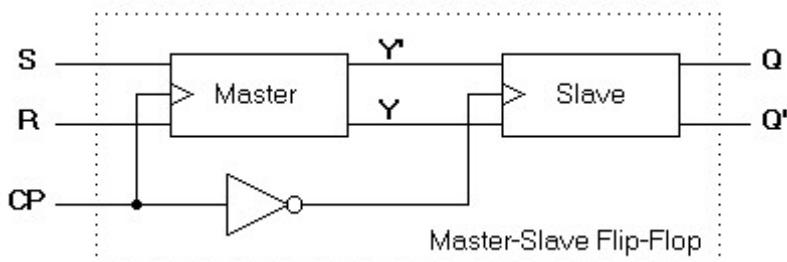

**Figure 3.18.** Logic diagram of a master-slave flip-flop


The timing relationship is shown in Figure 10 and is assumed that the flip-flop is in the clear state prior to the occurrence of the clock pulse. The output state of the master-slave flip-flop occurs on the negative transition of the clock pulse. Some master-slave flip-flops change output state on the positive transition of the clock pulse by having an additional inverter between the CP terminal and the input of the master.

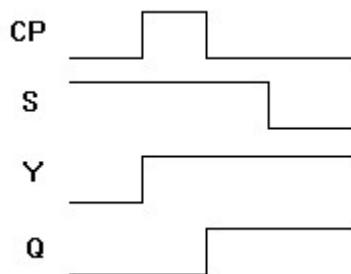

**Figure 3.19.** Timing relationship in a master slave flip-flop

### **The Master-Slave JK Flip-flop**

The **Master-Slave JK Flip-Flop** is basically two gated SR flip-flops connected together in a series configuration with the slave having an inverted clock pulse. The outputs from Q and Q' from the "Slave" flip-flop are fed back to the inputs of the "Master" with the outputs of the "Master" flip flop being connected to the two inputs of the "Slave" flip flop. This feedback configuration from the slave's output to the master's input gives the characteristic toggle of the JK flip flop as shown below.

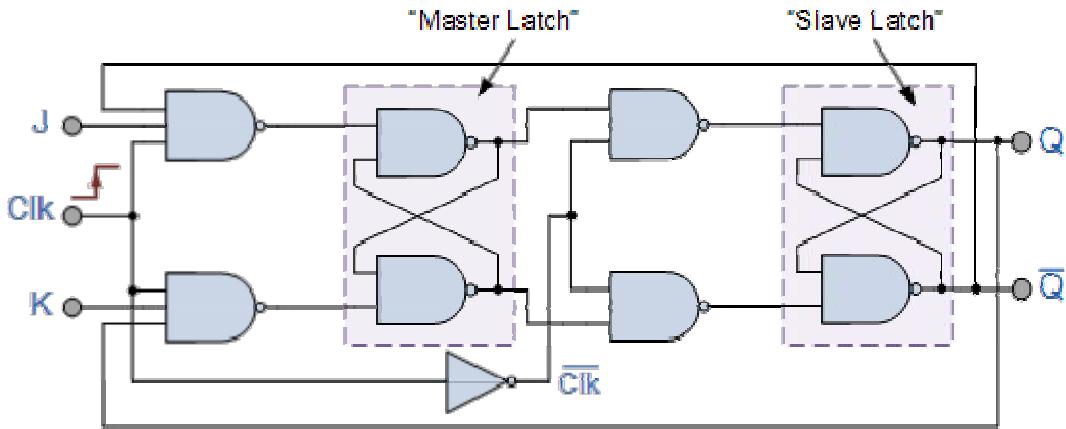

**Figure 3.20**

The input signals J and K are connected to the gated “master” SR flip flop which “locks” the input condition while the clock (Clk) input is “HIGH” at logic level “1”. As the clock input of the “slave” flip flop is the inverse (complement) of the “master” clock input, the “slave” SR flip flop does not toggle. The outputs from the “master” flip flop are only “seen” by the gated “slave” flip flop when the clock input goes “LOW” to logic level “0”. When the clock is “LOW”, the outputs from the “master” flip flop are latched and any additional changes to its inputs are ignored. The gated “slave” flip flop now responds to the state of its inputs passed over by the “master” section.

Then on the “Low-to-High” transition of the clock pulse the inputs of the “master” flip flop are fed through to the gated inputs of the “slave” flip flop and on the “High-to-Low” transition the same inputs are reflected on the output of the “slave” making this type of flip flop edge or pulse-triggered.

Then, the circuit accepts input data when the clock signal is “HIGH”, and passes the data to the output on the falling-edge of the clock signal. In other words, the **Master-Slave JK Flip flop** is a “Synchronous” device as it only passes data with the timing of the clock signal.

### Clock :

Latches are known as **level-sensitive** because their outputs are affected by their inputs as long as they are enabled. Their memory state can change during this entire time when the enable signal is asserted. In a computer circuit, however, we do not want the memory state to change at various times when the enable signal is asserted. Instead, we like to synchronize all of the state changes to happen at precisely the same moment and at regular intervals. In order to achieve this, two things are needed: (1) a synchronizing signal, and (2) a memory circuit that is not level-sensitive. The synchronizing signal, of course, is the **clock**, and the non-level-sensitive memory circuit is the flip-flop.

The clock is simply a very regular square wave signal, as shown in Figure 6.8. We call the edge of the clock signal when it changes from 0 to 1 the **rising edge**. Conversely, the **falling edge** of the clock is the edge when the signal changes from 1 to 0. We will use the symbol  $\dot{C}$  to denote the rising edge and  $\dot{\bar{C}}$  for the falling edge.

In a computer circuit, either the rising edge or the falling edge of the clock can be used as the synchronizing signal for writing data into a memory element.

This edge signal is referred to as the **active edge** of the clock. In all of our examples, we will use the rising clock edge as the active edge. Therefore, at every rising edge, data will be clocked or stored into the memory element.

Name	Graphical Symbol	Feature Table															
S-R		<table border="1"> <thead> <tr> <th>S</th><th>R</th><th><math>Q_{n+1}</math></th></tr> </thead> <tbody> <tr> <td>0</td><td>0</td><td><math>Q_n</math></td></tr> <tr> <td>0</td><td>1</td><td>0</td></tr> <tr> <td>1</td><td>0</td><td>1</td></tr> <tr> <td>1</td><td>1</td><td>-</td></tr> </tbody> </table>	S	R	$Q_{n+1}$	0	0	$Q_n$	0	1	0	1	0	1	1	1	-
S	R	$Q_{n+1}$															
0	0	$Q_n$															
0	1	0															
1	0	1															
1	1	-															
J-K		<table border="1"> <thead> <tr> <th>J</th><th>K</th><th><math>Q_{n+1}</math></th></tr> </thead> <tbody> <tr> <td>0</td><td>0</td><td><math>Q_n</math></td></tr> <tr> <td>0</td><td>1</td><td>0</td></tr> <tr> <td>1</td><td>0</td><td>1</td></tr> <tr> <td>1</td><td>1</td><td>Change condition</td></tr> </tbody> </table>	J	K	$Q_{n+1}$	0	0	$Q_n$	0	1	0	1	0	1	1	1	Change condition
J	K	$Q_{n+1}$															
0	0	$Q_n$															
0	1	0															
1	0	1															
1	1	Change condition															
D		<table border="1"> <thead> <tr> <th>D</th><th><math>Q_{n+1}</math></th></tr> </thead> <tbody> <tr> <td>0</td><td>0</td></tr> <tr> <td>1</td><td>1</td></tr> </tbody> </table>	D	$Q_{n+1}$	0	0	1	1									
D	$Q_{n+1}$																
0	0																
1	1																

Table 1: A few basic Flip-flops

A **clock cycle** is the time from one rising edge to the next rising edge or from one falling edge to the next falling edge. The speed of the clock, measured in hertz (Hz), is the number of cycles per second. Typically, the clock speed for a microprocessor in an embedded system runs around 20 MHz, while the microprocessor in a personal computer runs upwards of 2 GHz and higher. A **clock period** is the time for one clock cycle (seconds per cycle), so it is just the inverse of the clock speed.

### FF timing parameters

**Propagation delay:** propagation delay for a FF is the amount of time it takes for the output of the FF to change its state from a clock trigger or asynchronous set or rest. It is defined from the 50% point of the input pulse to the 50% point of the output pulse. Propagation delay is specified as  $t_{PHL}$  - the propagation time from a HIGH to a LOW, and as  $t_{PLH}$  - the propagation time from a LOW to a HIGH.

**Output transition time:** the output transition time is defined as the rise time or fall time of the output. The  $t_{TLH}$  is the 10% to 90% time, or LOW to HIGH transition time. The  $t_{THL}$  is the 90% to 10% time, or the HIGH to LOW transition time.

**Setup time:** the setup time is defined as the interval immediately preceding the active transition of the clock pulse during which the control or data inputs must be stable (at a valid logic level). Its parameter symbol is  $t_{su}$ .

**Hold time:** the hold time is the amount of time that the control or data inputs must be stable after the clock trigger occurs. The  $t_H$  is the parameter symbol for hold time.

**Minimum pulse width:** the minimum pulse width is required to guarantee a correct state change for the flip-flop. It is usually denoted by  $t_w$ .

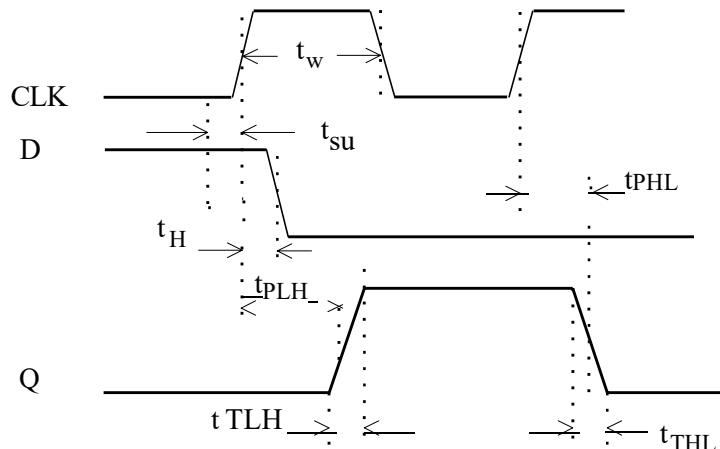








Figure.3.21

The **characteristic equation** is simply the Boolean equation that is derived directly from the characteristic table. Like the characteristic table, the characteristic equation specifies the flip-flop's next state,  $Q_{next}$ , as a function of its current state,  $Q$ , and input signals. The D flip-flop characteristic table has only one 1-minterm, which results in the simple characteristic equation for each flip-flop shown below .

### What's an Excitation Table?

The **excitation table** is like the mirror image of the characteristic table by exchanging the input signal column(s) with the output ( $Q_{next}$ ) column. The excitation table shows what the flip-flop's inputs should be in order to change from the flip-flop's current state to the next state desired. In other words, the excitation table answers the question of what the flip-flop's inputs should be when given the current state that the flip-flop is in and the next state that we want the flip-flop to go to.

Name / Symbol	Characteristic (Truth) Table	State Diagram / Characteristic Equations	Excitation Table																																																
<b>SR</b> 	$S \ R \ Q \ Q_{next}$ <table border="1"> <tr><td>0</td><td>0</td><td>0</td><td>0</td></tr> <tr><td>0</td><td>0</td><td>1</td><td>1</td></tr> <tr><td>0</td><td>1</td><td>0</td><td>0</td></tr> <tr><td>0</td><td>1</td><td>1</td><td>0</td></tr> <tr><td>1</td><td>0</td><td>0</td><td>1</td></tr> <tr><td>1</td><td>0</td><td>1</td><td>1</td></tr> <tr><td>1</td><td>1</td><td>0</td><td><math>\times</math></td></tr> <tr><td>1</td><td>1</td><td>1</td><td><math>\times</math></td></tr> </table>	0	0	0	0	0	0	1	1	0	1	0	0	0	1	1	0	1	0	0	1	1	0	1	1	1	1	0	$\times$	1	1	1	$\times$	<p>SR=00 or 01      SR=10</p> <p><math>Q=0</math>      <math>Q=1</math></p> <p><math>SR=01</math></p> <p><math>Q_{next} = S + R'Q</math></p> <p><math>SR = 0</math></p>	$Q \ Q_{next} \ S \ R$ <table border="1"> <tr><td>0</td><td>0</td><td>0</td><td><math>\times</math></td></tr> <tr><td>0</td><td>1</td><td>1</td><td>0</td></tr> <tr><td>1</td><td>0</td><td>0</td><td>1</td></tr> <tr><td>1</td><td>1</td><td><math>\times</math></td><td>0</td></tr> </table>	0	0	0	$\times$	0	1	1	0	1	0	0	1	1	1	$\times$	0
0	0	0	0																																																
0	0	1	1																																																
0	1	0	0																																																
0	1	1	0																																																
1	0	0	1																																																
1	0	1	1																																																
1	1	0	$\times$																																																
1	1	1	$\times$																																																
0	0	0	$\times$																																																
0	1	1	0																																																
1	0	0	1																																																
1	1	$\times$	0																																																
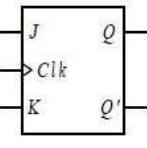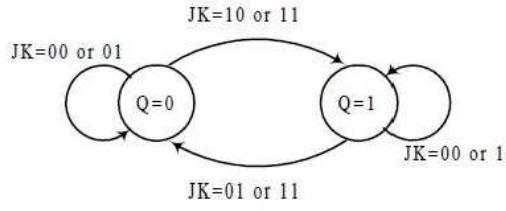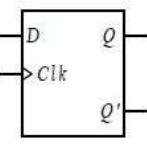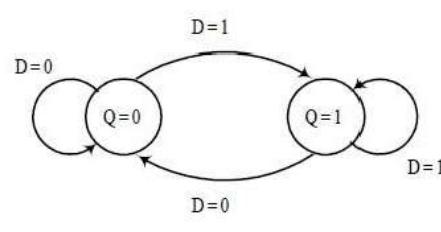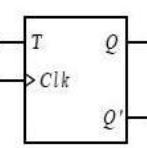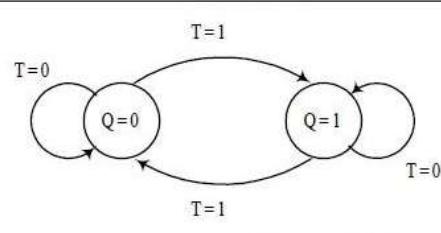
<b>JK</b> 	<table border="1"> <thead> <tr> <th><i>J</i></th> <th><i>K</i></th> <th><i>Q</i></th> <th><i>Q<sub>next</sub></i></th> </tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>0</td><td>0</td></tr> <tr><td>0</td><td>0</td><td>1</td><td>1</td></tr> <tr><td>0</td><td>1</td><td>0</td><td>0</td></tr> <tr><td>0</td><td>1</td><td>1</td><td>0</td></tr> <tr><td>1</td><td>0</td><td>0</td><td>1</td></tr> <tr><td>1</td><td>0</td><td>1</td><td>1</td></tr> <tr><td>1</td><td>1</td><td>0</td><td>1</td></tr> <tr><td>1</td><td>1</td><td>1</td><td>0</td></tr> </tbody> </table>	<i>J</i>	<i>K</i>	<i>Q</i>	<i>Q<sub>next</sub></i>	0	0	0	0	0	0	1	1	0	1	0	0	0	1	1	0	1	0	0	1	1	0	1	1	1	1	0	1	1	1	1	0	 $Q_{next} = J'K'Q + JK' + JKQ'$ $= JK'Q + JKQ + JK'Q' + JKQ'$ $= K'Q(J'+J) + JQ'(K'+K)$ $= K'Q + JQ'$	<table border="1"> <thead> <tr> <th><i>Q</i></th> <th><i>Q<sub>next</sub></i></th> <th><i>J</i></th> <th><i>K</i></th> </tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>0</td><td>×</td></tr> <tr><td>0</td><td>1</td><td>1</td><td>×</td></tr> <tr><td>1</td><td>0</td><td>×</td><td>1</td></tr> <tr><td>1</td><td>1</td><td>×</td><td>0</td></tr> </tbody> </table>	<i>Q</i>	<i>Q<sub>next</sub></i>	<i>J</i>	<i>K</i>	0	0	0	×	0	1	1	×	1	0	×	1	1	1	×	0
<i>J</i>	<i>K</i>	<i>Q</i>	<i>Q<sub>next</sub></i>																																																								
0	0	0	0																																																								
0	0	1	1																																																								
0	1	0	0																																																								
0	1	1	0																																																								
1	0	0	1																																																								
1	0	1	1																																																								
1	1	0	1																																																								
1	1	1	0																																																								
<i>Q</i>	<i>Q<sub>next</sub></i>	<i>J</i>	<i>K</i>																																																								
0	0	0	×																																																								
0	1	1	×																																																								
1	0	×	1																																																								
1	1	×	0																																																								
<b>D</b> 	<table border="1"> <thead> <tr> <th><i>D</i></th> <th><i>Q</i></th> <th><i>Q<sub>next</sub></i></th> </tr> </thead> <tbody> <tr><td>0</td><td>×</td><td>0</td></tr> <tr><td>1</td><td>×</td><td>1</td></tr> </tbody> </table>	<i>D</i>	<i>Q</i>	<i>Q<sub>next</sub></i>	0	×	0	1	×	1	 $Q_{next} = D$	<table border="1"> <thead> <tr> <th><i>Q</i></th> <th><i>Q<sub>next</sub></i></th> <th><i>D</i></th> </tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>0</td></tr> <tr><td>0</td><td>1</td><td>1</td></tr> <tr><td>1</td><td>0</td><td>0</td></tr> <tr><td>1</td><td>1</td><td>1</td></tr> </tbody> </table>	<i>Q</i>	<i>Q<sub>next</sub></i>	<i>D</i>	0	0	0	0	1	1	1	0	0	1	1	1																																
<i>D</i>	<i>Q</i>	<i>Q<sub>next</sub></i>																																																									
0	×	0																																																									
1	×	1																																																									
<i>Q</i>	<i>Q<sub>next</sub></i>	<i>D</i>																																																									
0	0	0																																																									
0	1	1																																																									
1	0	0																																																									
1	1	1																																																									
<b>T</b> 	<table border="1"> <thead> <tr> <th><i>T</i></th> <th><i>Q</i></th> <th><i>Q<sub>next</sub></i></th> </tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>0</td></tr> <tr><td>0</td><td>1</td><td>1</td></tr> <tr><td>1</td><td>0</td><td>1</td></tr> <tr><td>1</td><td>1</td><td>0</td></tr> </tbody> </table>	<i>T</i>	<i>Q</i>	<i>Q<sub>next</sub></i>	0	0	0	0	1	1	1	0	1	1	1	0	 $Q_{next} = TQ' + T'Q = T \oplus Q$	<table border="1"> <thead> <tr> <th><i>Q</i></th> <th><i>Q<sub>next</sub></i></th> <th><i>T</i></th> </tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>0</td></tr> <tr><td>0</td><td>1</td><td>1</td></tr> <tr><td>1</td><td>0</td><td>1</td></tr> <tr><td>1</td><td>1</td><td>0</td></tr> </tbody> </table>	<i>Q</i>	<i>Q<sub>next</sub></i>	<i>T</i>	0	0	0	0	1	1	1	0	1	1	1	0																										
<i>T</i>	<i>Q</i>	<i>Q<sub>next</sub></i>																																																									
0	0	0																																																									
0	1	1																																																									
1	0	1																																																									
1	1	0																																																									
<i>Q</i>	<i>Q<sub>next</sub></i>	<i>T</i>																																																									
0	0	0																																																									
0	1	1																																																									
1	0	1																																																									
1	1	0																																																									

### Conversion of Flip Flop :

For the conversion of one type of flip flop into another type of flip flop, we are required to design a combinational circuit. Steps to be followed :

**Step-1: Write the truth table of the Desired flip-flop**

**Step 2: Obtain the Excitation Table for the given Flip-Flop from its Truth Table**

**Step 3: Obtain Conversion Table**

**Step 4: Simplify the Expressions for the Inputs of the given Flip-Flop**

**Step 5: Design the Necessary Circuit and make the Connections accordingly**

### Conversion of SR flip flop:

#### 1) SR flip flop to JK flip flop:

In this case we are required to convert SR flip flop into JK flip flop. Therefore we have to first design and connect the combinational circuit to the input of SR flip flop so that it will produce same outputs as that of JK flip flop. Here the external inputs are J and K. S and R will be the outputs of designed combinational circuit which are inputs of actual flip flop. We write a truth table with J, K, Qn, Qn+1, S and R. where Qn is the present state of the flip flop and Qn+1 will be the next state obtained when the particular J and K inputs are applied.

J, K and Q<sub>n</sub> can have eight combinations. For each combination of J, K and Q<sub>n</sub> find the corresponding Q<sub>n+1</sub>, i.e. determine to which next state the JK flip flop will go from the present state Q<sub>n</sub> if the present inputs J and K are applied. Now complete the table by writing the values of S and R required to get each Q<sub>n+1</sub> from the corresponding Q<sub>n</sub>. i.e. write what values of S and R are required to change the state of the flip flop from Q<sub>n</sub> to Q<sub>n+1</sub>

**Truth Table**

Inputs		Outputs	
J	K	Q <sub>n</sub>	Q <sub>n+1</sub>
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

**Excitation Table**

Outputs		Inputs	
Q <sub>n</sub>	Q <sub>n+1</sub>	S	R
0	0	0	X
0	1	1	0
1	0	0	X
1	1	0	1
1	0	1	0
1	1	X	0

**Conversion Table**

J	K	Q <sub>n</sub>	Q <sub>n+1</sub>	S	R
0	0	0	0	0	X
0	0	1	1	X	0
0	1	0	0	0	X
0	1	1	0	0	1
1	0	0	1	1	0
1	0	1	1	X	0
1	1	0	1	1	0
1	1	1	0	0	1

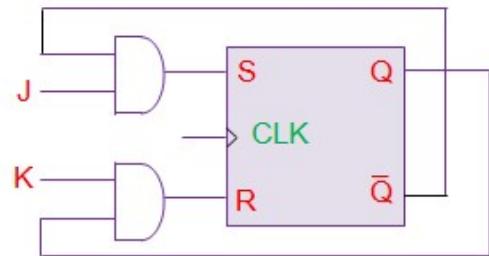
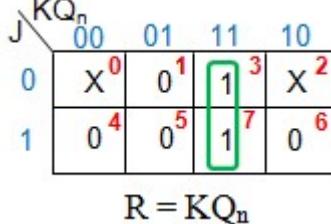
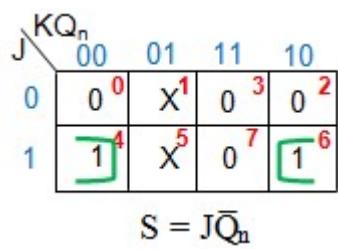


Figure.3.22

## 2) SR flip flop to D flip flop:

Similarly for the conversion of SR flip flop into the D flip flop we have connect combinational circuit to the inputs of the SR flip flop. In this case D the external input of the circuit. The output of the combinational circuit is connected to the inputs of the actual flip flop i.e. SR flip flop. Then the output of this flip flop will be the same as D flip flop.

The conversion table, K-maps, and Logic diagram for the conversion of SR flip flop to D flip flop.

### 1. Truth Table for T flip-flop

Input		Outputs	
T	Q <sub>n</sub>	Q <sub>n+1</sub>	
0	0	0	
0	1	1	
1	0	1	
1	1	0	


### 2. Excitation Table for SR flip-flop

Outputs		Inputs	
Q <sub>n</sub>	Q <sub>n+1</sub>	S	R
0	0	0	X
0	1	1	0
1	0	0	1
1	1	X	0


### 3. Conversion Table

T	$Q_n$	$Q_{n+1}$	S	R
0	0	0	0	X
0	1	1	X	0
1	0	1	1	0
1	1	0	0	1

### 4. K-map Simplification

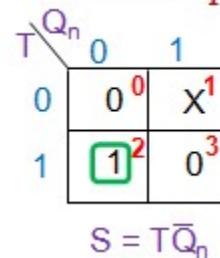

$$S = T\bar{Q}_n$$

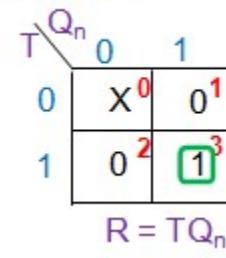

$$R = TQ_n$$

### 5. Circuit Design

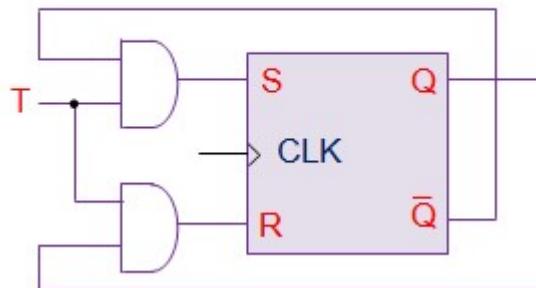


Figure.3.23

### 3. Conversion of SR Flip Flop to T Flip Flop:

#### 1. Truth Table for T flip-flop

Input		Outputs	
T	$Q_n$	$Q_{n+1}$	
0	0	0	
0	1	1	
1	0	1	
1	1	0	


#### 2. Excitation Table for SR flip-flop

Outputs		Inputs	
$Q_n$	$Q_{n+1}$	S	R
0	0	0	X
0	1	1	0
1	0	0	1
1	1	X	0


### 3. Conversion Table

T	$Q_n$	$Q_{n+1}$	S	R
0	0	0	0	X
0	1	1	X	0
1	0	1	1	0
1	1	0	0	1

### 4. K-map Simplification

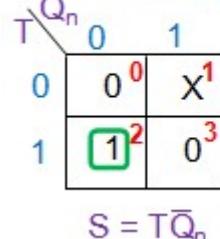

$$S = T\bar{Q}_n$$

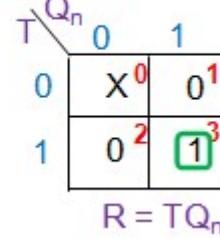

$$R = TQ_n$$

### 5. Circuit Design

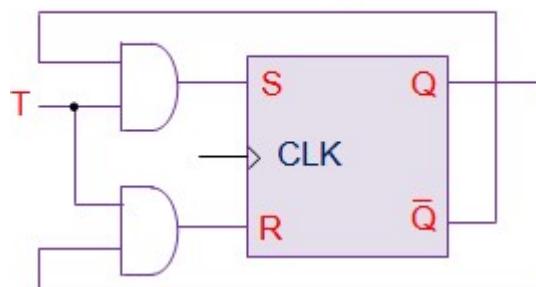


Figure.3.24

## Conversion of D flip flop :

In the last article we have discussed about "how to convert JK flip flop into SR, D and T type of flip flop". Today we are going to convert D flip flop. We can convert D flip flop into SR and JK flip flop by using suitable combinational circuit. Combinational circuits for this purpose can be designed easily by using conversion tables and K-Maps. Let us see how to convert D flip flop into different types of flip flop.

### 1. Conversion of D Flip Flop to JK Flip Flop:

In case of conversion of D flip flop to JK flip flop we have to use J and K as the external inputs and D as the input of actual flip flop. J,K and  $Q_n$  makes eight possible combinations. Express D in terms of J, K and  $Q_n$ .

The conversion table, K-Maps and logic diagram for the conversion of D flip flop into JK flip flop is shown below:

#### 1. Truth Table for JK flip-flop

Inputs		Outputs	
J	K	$Q_n$	$Q_{n+1}$
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0


#### 2. Excitation Table for D flip-flop

Outputs		Input
$Q_n$	$Q_{n+1}$	D
0	0	0
0	1	1
1	0	0
1	1	1

#### 3. Conversion Table

J	K	$Q_n$	$Q_{n+1}$	D
0	0	0	0	0
0	0	1	1	1
0	1	0	0	0
0	1	1	0	1
1	0	0	1	1
1	0	1	1	1
1	1	0	1	1
1	1	1	0	0

#### 4. K-map Simplification

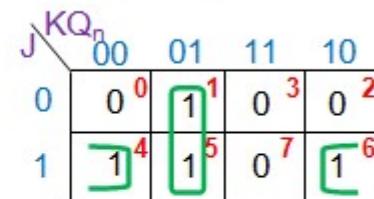

$$D = J\bar{Q}_n + \bar{K}Q_n$$

#### 5. Circuit Design

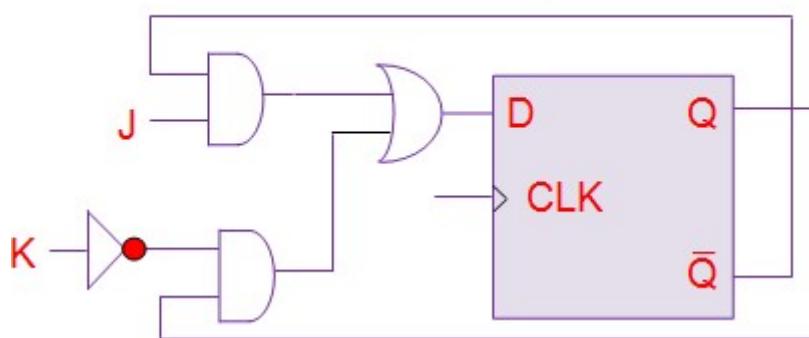


Figure.3.24

**2. Conversion of D Flip Flop to SR Flip Flop :** For converting D flip flop to SR flip flop, we use S and R as external inputs and D is the actual input to the flip flop. S, R and  $Q_n$  makes eight possible combinations, but  $S=R=1$  is an invalid combination. So, the corresponding entries for  $Q_{n+1}$  and D are don't cares. Then we have to express D in terms of S, R and  $Q_n$  for the design of required flip flop. The conversion table, K-Maps and logic diagram for the conversion of D flip flop into SR flip flop is shown below:

### 1. Truth Table for SR flip-flop

S	R	$Q_n$	$Q_{n+1}$
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	invalid	invalid
1	1	invalid	invalid


### 2. Excitation Table for D flip-flop

Outputs		Input
S	$Q_n$	D
0	0	0
0	1	1
1	0	0
1	1	1

### 3. Conversion Table

S	R	$Q_n$	$Q_{n+1}$	D
0	0	0	0	0
0	0	1	1	1
0	1	0	0	0
0	1	1	0	0
1	0	0	1	1
1	0	1	1	1
1	1	invalid	X	X
1	1	invalid	X	X

### 4. K-map Simplification

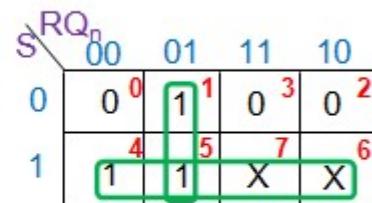

$$D = S + \bar{R}Q_n$$

### 5. Circuit Design

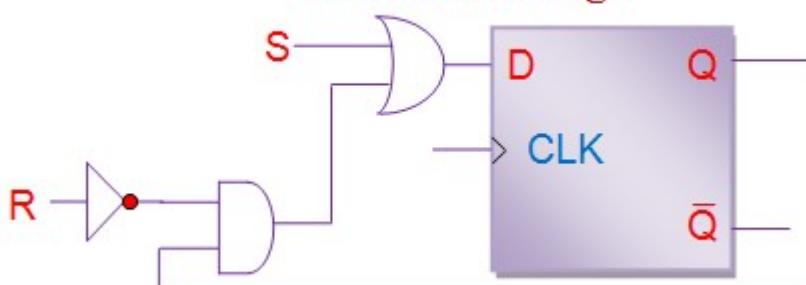


Figure.3.25

### 3. Conversion of D Flip Flop to T Flip Flop:

#### 1. Truth Table for T Flip Flop

Input		
T	$Q_n$	$Q_{n+1}$
0	0	0
0	1	1
1	0	1
1	1	0

#### 2. Excitation Table for D Flip Flop

Outputs		Input
$Q_n$	$Q_{n+1}$	D
0	0	0
0	1	1
1	0	0
1	1	1


### 3. Conversion Table

T	$Q_n$	$Q_{n+1}$	D
0	0	0	0
0	1	1	1
1	0	1	1
1	1	0	0

### 4. K-map Simplification

T	$Q_n$	0	1
0	0	0	1
1	1	1	0
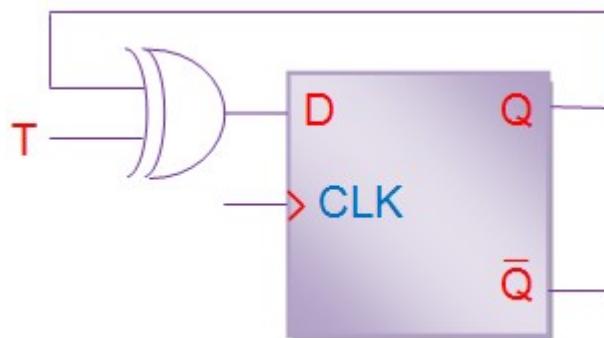
$$D = T\bar{Q}_n + \bar{T}Q_n \\ = T \oplus Q_n$$



### 5. Circuit Design

#### 4. Conversion of T Flip Flop to JK Flip Flop :

##### 1. Truth Table for JK Flip Flop

Inputs		Outputs	
J	K	$Q_n$	$Q_{n+1}$
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

##### 2. Excitation Table for T Flip Flop

Outputs		Input
$Q_n$	$Q_{n+1}$	T
0	0	0
0	1	1
1	0	1
1	1	0

### 3. Conversion Table


J	K	$Q_n$	$Q_{n+1}$	T
0	0	0	0	0
0	0	1	1	0
0	1	0	0	0
0	1	1	0	1
1	0	0	1	1
1	0	1	1	0
1	1	0	1	1
1	1	1	0	1

### 4. K-map Simplification

J	$KQ_n$	00	01	11	10
0	0	0	1	1	0
1	1	0	0	1	1

$$T = J\bar{Q}_n + KQ_n$$

## 5. Circuit Design

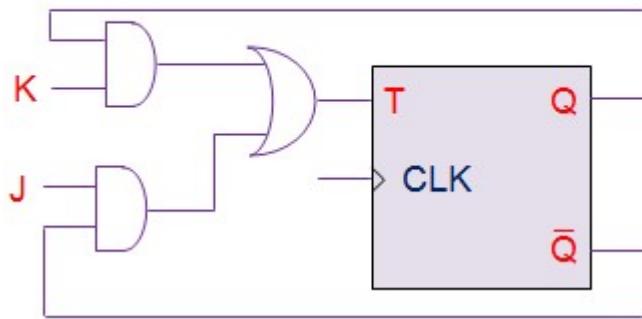

**Figure.3.27**

**Conversion of JK flip flop :** If we want to convert one type of flip flop into another type of flip flop, first we have to design a combinational circuit and after that connect it to the inputs of actual flip flop. So that the outputs of combinational circuit will be the inputs of actual flip flop and then it will produce same output as that of required flip flop.

**We can convert JK flip flop into SR flip flop, T flip flop and D type of flip flop.**

### 1) Conversion of JK flip flop to SR flip flop:

**Step 1:** Write the Truth Table of the Desired Flip-Flop, Here SR flip-flop is to be designed using JK flip-flop. Thus one needs to write the truth table for SR flip-flop.

**Truth Table for JK Flip-Flop**

Inputs		Outputs	
S	R	Present State, $Q_n$	Next State, $Q_{n+1}$
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	invalid	
1	1	invalid	

Inputs		Outputs	
J	K	$Q_n$	$Q_{n+1}$
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

**Step 2:** Obtain the Excitation Table for the given Flip-Flop from its Truth Table. Excitation tables provide the details regarding the inputs which must be provided to the flip-flop to obtain a definite next state ( $Q_{n+1}$ ) from the known current state ( $Q_n$ ).

From the truth table of JK flip-flop one can see that  $Q_{n+1}$  will become 0 from  $Q_n = 0$  for both (i)  $J = K = 0$  and (ii)  $J = 0$  and  $K = 1$  (blue entries in first and third rows of the truth table).

This means that to obtain the next state,  $Q_{n+1}$  as 0 from the current state  $Q_n = 0$ , J must be made zero while K can be either 0 or 1.

This is indicated by the first row of the excitation table (blue entries in the first row of excitation table) where the value of K is expressed as 'X' indicating don't care condition. Similarly to obtain the next state as 1 from the current state 0, one has to have J equal to 1 while K can be either 0 or 1 (indicated by green entries of the truth table). This leads to the second row of excitation table (green entries) to be filled with values  $Q_n = 0$ ,  $Q_{n+1} = 1$ ,  $J = 1$  and  $K = X$ . On the same grounds, entire excitation table needs to be filled (entries in pink and dark red colors).

**Step 3:** Append the Excitation Table of the given Flip-Flop to the Truth Table of the Desired Flip-Flop Appropriately to obtain Conversion Table, Here the conversion table is obtained by filling-up the values of the J and K inputs for the given  $Q_n$  and  $Q_{n+1}$ , by referring to the excitation table.


Excitation Table for JK Flip-Flop

Outputs		Inputs	
$Q_n$	$Q_{n+1}$	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0


Conversion Table

S	R	$Q_n$	$Q_{n+1}$	J	K
0	0	0	0	0	X
0	0	1	1	X	0
0	1	0	0	0	X
0	1	1	0	X	1
1	0	0	1	1	X
1	0	1	1	X	0
1	1	invalid		X	X
1	1	invalid		X	X

K-Maps

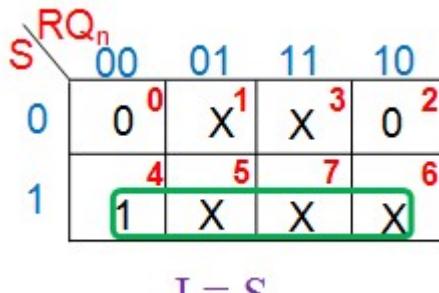

$$J = S$$

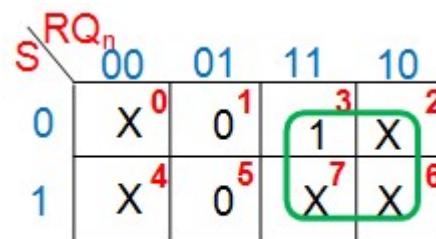

$$K = R$$

**Step 4:** Simplify the Expressions for the Inputs of the given Flip-Flop. In this case, one needs to arrive at the logical expressions for the inputs J and K in terms of S, R and  $Q_n$  using suitable simplification technique like K-map.

**Step 5:** Design the Necessary Circuit and make the Connections accordingly. Here neither additional circuit nor new connections are necessary.

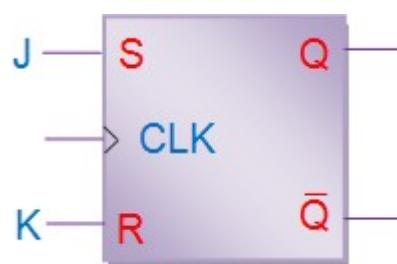


Figure.3.28

On the same grounds, one can convert the given flip-flop to any other type of flip-flop as shown below.

## 2) Conversion of JK flip flop to T flip flop:

For the conversion of JK flip flop to T type of flip flop, T will be the external input (input of combinational circuit) and the output of this combinational circuit is connected to the inputs of actual flip flop (J and K).

Then we prepare conversion table and using this table express J and K in terms of T and  $Q_n$ . The conversion table, K-Maps and logic diagram for the conversion of JK flip flop to T type of flip flop is shown below:

1. Truth Table for T Flip-Flop
2. Excitation Table for JK Flip-Flop

<table border="1" style="border-collapse: collapse; width: 100%;"> <thead> <tr> <th colspan="2">Input</th> <th colspan="2">Outputs</th> </tr> <tr> <th>T</th> <th><math>Q_n</math></th> <th><math>Q_{n+1}</math></th> <th></th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> <td>0</td> <td></td> </tr> <tr> <td>0</td> <td>1</td> <td>1</td> <td></td> </tr> <tr> <td>1</td> <td>0</td> <td>1</td> <td></td> </tr> <tr> <td>1</td> <td>1</td> <td>0</td> <td></td> </tr> </tbody> </table>	Input		Outputs		T	$Q_n$	$Q_{n+1}$		0	0	0		0	1	1		1	0	1		1	1	0		<table border="1" style="border-collapse: collapse; width: 100%;"> <thead> <tr> <th colspan="2">Outputs</th> <th colspan="2">Inputs</th> </tr> <tr> <th><math>Q_n</math></th> <th><math>Q_{n+1}</math></th> <th>J</th> <th>K</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> <td>0</td> <td>X</td> </tr> <tr> <td>0</td> <td>1</td> <td>1</td> <td>X</td> </tr> <tr> <td>1</td> <td>0</td> <td>X</td> <td>1</td> </tr> <tr> <td>1</td> <td>1</td> <td>X</td> <td>0</td> </tr> </tbody> </table>	Outputs		Inputs		$Q_n$	$Q_{n+1}$	J	K	0	0	0	X	0	1	1	X	1	0	X	1	1	1	X	0	<p>3. Conversion Table</p> <table border="1" style="border-collapse: collapse; width: 100%;"> <thead> <tr> <th>T</th> <th><math>Q_n</math></th> <th><math>Q_{n+1}</math></th> <th>J</th> <th>K</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> <td>0</td> <td>0</td> <td>X</td> </tr> <tr> <td>0</td> <td>1</td> <td>1</td> <td>X</td> <td>0</td> </tr> <tr> <td>1</td> <td>0</td> <td>1</td> <td>1</td> <td>X</td> </tr> <tr> <td>1</td> <td>1</td> <td>0</td> <td>X</td> <td>1</td> </tr> </tbody> </table>	T	$Q_n$	$Q_{n+1}$	J	K	0	0	0	0	X	0	1	1	X	0	1	0	1	1	X	1	1	0	X	1
Input		Outputs																																																																									
T	$Q_n$	$Q_{n+1}$																																																																									
0	0	0																																																																									
0	1	1																																																																									
1	0	1																																																																									
1	1	0																																																																									
Outputs		Inputs																																																																									
$Q_n$	$Q_{n+1}$	J	K																																																																								
0	0	0	X																																																																								
0	1	1	X																																																																								
1	0	X	1																																																																								
1	1	X	0																																																																								
T	$Q_n$	$Q_{n+1}$	J	K																																																																							
0	0	0	0	X																																																																							
0	1	1	X	0																																																																							
1	0	1	1	X																																																																							
1	1	0	X	1																																																																							
<b>4. K-map Simplification</b>																																																																											
 $J = T$	 $K = T$	<b>5. Circuit Design</b>																																																																									

Figure.3.29

## 3) Conversion of JK flip flop to D flip flop:

In case of converting JK flip flop into D flip flop, D is the external input of combinational circuit, whereas J and K are the inputs of actual flip flop.

D and  $Q_n$  make four combinations. So, prepare a conversion table and using this table express J and K in terms of D and  $Q_n$ .

The conversion table, K-map and logic diagram for the conversion of JK flip flop to D flip flop is shown below:

1. Truth Table for D Flip-Flop
2. Excitation Table for JK Flip-Flop

<table border="1" style="border-collapse: collapse; width: 100%;"> <thead> <tr> <th colspan="2">Input</th> <th colspan="2">Outputs</th> </tr> <tr> <th>D</th> <th><math>Q_n</math></th> <th><math>Q_{n+1}</math></th> <th></th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> <td>0</td> <td></td> </tr> <tr> <td>0</td> <td>1</td> <td>0</td> <td></td> </tr> <tr> <td>1</td> <td>0</td> <td>1</td> <td></td> </tr> <tr> <td>1</td> <td>1</td> <td>1</td> <td></td> </tr> </tbody> </table>	Input		Outputs		D	$Q_n$	$Q_{n+1}$		0	0	0		0	1	0		1	0	1		1	1	1		<table border="1" style="border-collapse: collapse; width: 100%;"> <thead> <tr> <th colspan="2">Outputs</th> <th colspan="2">Inputs</th> </tr> <tr> <th><math>Q_n</math></th> <th><math>Q_{n+1}</math></th> <th>J</th> <th>K</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> <td>0</td> <td>X</td> </tr> <tr> <td>0</td> <td>1</td> <td>1</td> <td>X</td> </tr> <tr> <td>1</td> <td>0</td> <td>X</td> <td>1</td> </tr> <tr> <td>1</td> <td>1</td> <td>X</td> <td>0</td> </tr> </tbody> </table>	Outputs		Inputs		$Q_n$	$Q_{n+1}$	J	K	0	0	0	X	0	1	1	X	1	0	X	1	1	1	X	0	<p>3. Conversion Table</p> <table border="1" style="border-collapse: collapse; width: 100%;"> <thead> <tr> <th>D</th> <th><math>Q_n</math></th> <th><math>Q_{n+1}</math></th> <th>J</th> <th>K</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> <td>0</td> <td>0</td> <td>X</td> </tr> <tr> <td>0</td> <td>1</td> <td>0</td> <td>X</td> <td>1</td> </tr> <tr> <td>1</td> <td>0</td> <td>1</td> <td>1</td> <td>X</td> </tr> <tr> <td>1</td> <td>1</td> <td>1</td> <td>X</td> <td>0</td> </tr> </tbody> </table>	D	$Q_n$	$Q_{n+1}$	J	K	0	0	0	0	X	0	1	0	X	1	1	0	1	1	X	1	1	1	X	0
Input		Outputs																																																																									
D	$Q_n$	$Q_{n+1}$																																																																									
0	0	0																																																																									
0	1	0																																																																									
1	0	1																																																																									
1	1	1																																																																									
Outputs		Inputs																																																																									
$Q_n$	$Q_{n+1}$	J	K																																																																								
0	0	0	X																																																																								
0	1	1	X																																																																								
1	0	X	1																																																																								
1	1	X	0																																																																								
D	$Q_n$	$Q_{n+1}$	J	K																																																																							
0	0	0	0	X																																																																							
0	1	0	X	1																																																																							
1	0	1	1	X																																																																							
1	1	1	X	0																																																																							
<b>4. K-map Simplification</b>																																																																											
 $J = D$	 $K = \bar{D}$	<b>5. Circuit Design</b>																																																																									

Figure.3.30

## Applications of Flip-Flops:

Some of the common uses of the Flip-Flops are as follows:

- 1) Bounce elimination switch
- 2) Latch
- 3) Registers
- 4) Counters
- 5) Memory, etc.

## The Problem of Clock Skew:

The clock doesn't arrive at all FF's at the same time. Skew is the difference between two clock edges. Correct behavior assumes next state of all storage elements determined by all storage elements *at the same time*, not possible in real systems!

- Logical clock driven from more than one physical circuit with timing behavior
- Different wire delay to different points in the circuit

### Effect of Skew on Cascaded Flip-flops :

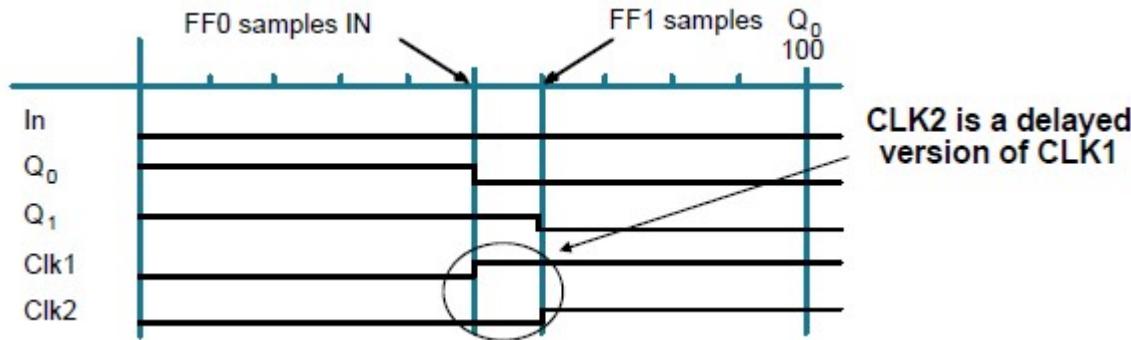


Figure.3.31

Original State:  $Q_0 = 1, Q_1 = 1, In = 0$

Because of skew, next state becomes:  $Q_0 = 0, Q_1 = 0$ , not  $Q_0 = 0, Q_1 = 1$

## Design Strategies for Minimizing Clock Skew:

- distribute clock signals in general direction of data flows
- wire carrying the clock between two communicating components should be as short as possible
- for multiphase clocked systems, distribute all clocks in similar wire paths; this minimizes the possibility of overlap
- for the non-overlap clock generate, use the phase feedback signals from the furthest point in the circuit to which the clock is distributed; this guarantees that the phase is seen as low everywhere before it allows the next phase to go high

## Shift registers:

In digital circuits, a **shift register** is a cascade of flip-flops sharing the same clock, in which the output of each flip-flop is connected to the "data" input of the next flip-flop in the chain, resulting in a circuit that shifts by one position the "bit array" stored in it, *shifting in* the data present at its input and *shifting out* the last bit in the array, at each transition of the clock input. More generally, a **shift register** may be multidimensional, such that its "data in" and stage outputs are themselves bit arrays: this is implemented simply by running several shift registers of the same bit-length in parallel.

Shift registers can have both parallel and serial inputs and outputs. These are often configured as **serial-in, parallel-out** (SIPO) or as **parallel-in, serial-out** (PISO). There are also types that have both serial and parallel input and types with serial and parallel output. There are also **bi-directional** shift registers which allow shifting in both directions: L→R or R→L. The serial input and last output of a shift register can also be connected to create a **circular shift register**

## Buffer register:

The buffer register is the simple set of registers. It is simply stores the binary word. The buffer may be controlled buffer. Most of the buffer registers used D Flip-flops.

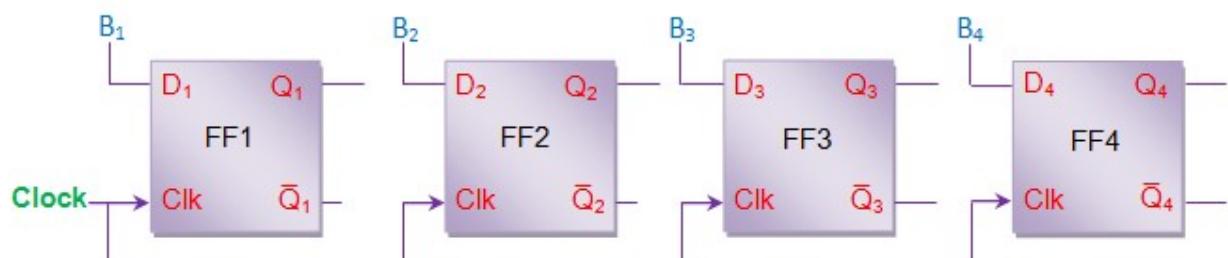


Figure 3.32: logic diagram of 4-bit buffer register

The figure shows a 4-bit buffer register. The binary word to be stored is applied to the data terminals. On the application of clock pulse, the output word becomes the same as the word applied at the terminals. i.e., the input word is loaded into the register by the application of clock pulse.

When the positive clock edge arrives, the stored word becomes:  
 $Q_4 Q_3 Q_2 Q_1 = X_4 X_3 X_2 X_1; Q=X$


## Controlled buffer register:

If goes LOW, all the FFs are RESET and the output becomes,  $Q=0000$ .

When is HIGH, the register is ready for action. LOAD is the control input. When LOAD is HIGH, the data bits X can reach the D inputs of FF's.  $Q_4 Q_3 Q_2 Q_1 = X_4 X_3 X_2 X_1; Q=X$

When load is low, the X bits cannot reach the FF's.

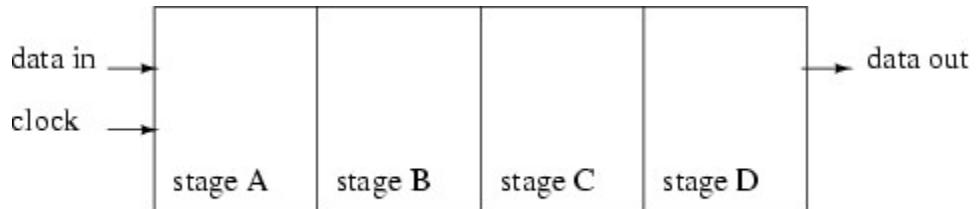
### Data transmission in shift registers:




Serial-in, serial-out shift register with 4-stages

A number of ff's connected together such that data may be shifted into and shifted out of them is called shift register. data may be shifted into or out of the register in serial form or in parallel form. There are four basic types of shift registers.

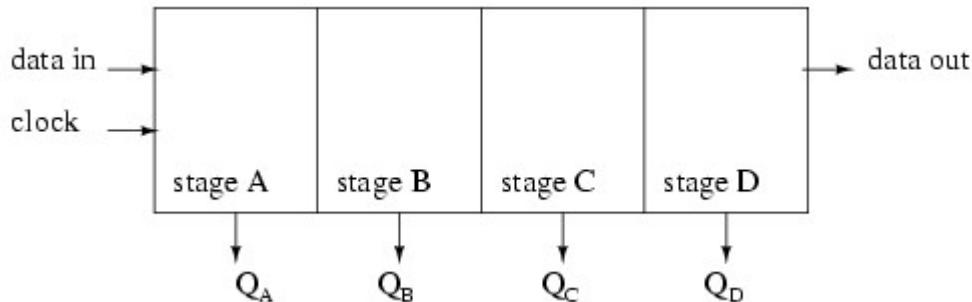1. Serial in, serial out, shift right, shift registers
2. Serial in, serial out, shift left, shift registers
3. Parallel in, serial out shift registers
4. Parallel in, parallel out shift registers



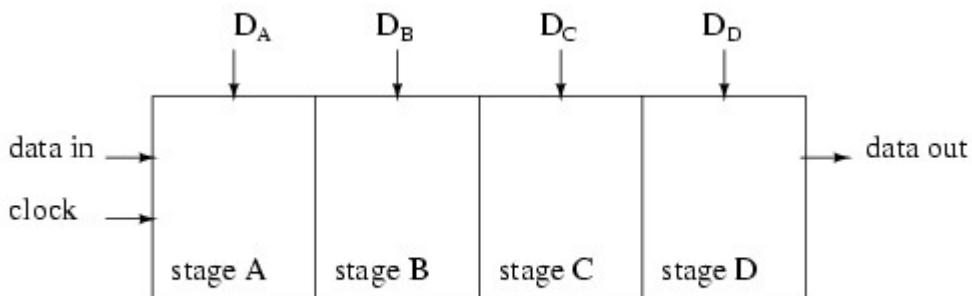Serial-in, parallel-out shift register with 4-stages



Parallel-in, serial-out shift register with 4-stages

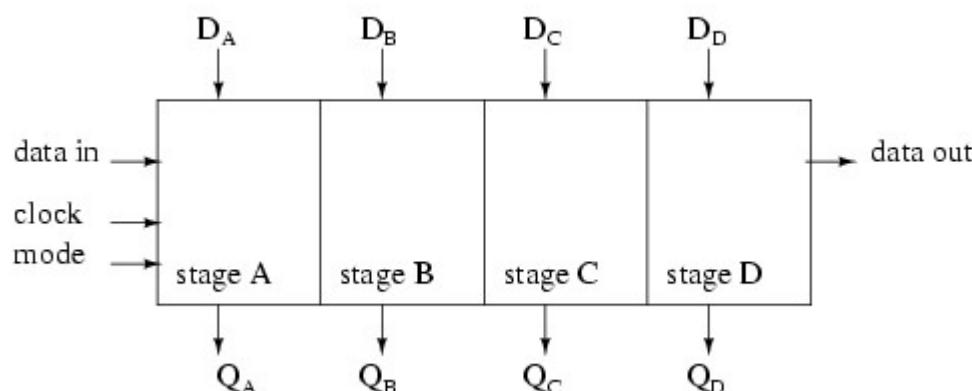


Figure.3.33 Parallel-in, parallel-out shift register with 4-stages

## Serial IN, serial OUT, shift right, shift left register:

The logic diagram of 4-bit serial in serial out, right shift register with four stages. The register can store four bits of data. Serial data is applied at the input D of the first FF. the Q output of the first FF is connected to the D input of another FF. the data is outputted from the Q terminal of the last FF.


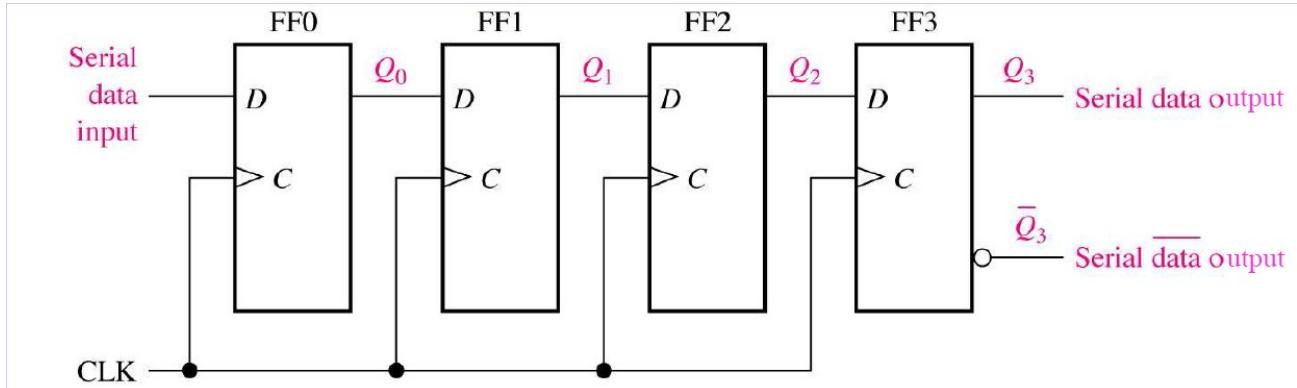


Figure.3.34

When serial data is transferred into a register, each new bit is clocked into the first FF at the positive going edge of each clock pulse. The bit that was previously stored by the first FF is transferred to the second FF. the bit that was stored by the Second FF is transferred to the third FF.

Figure.3.35

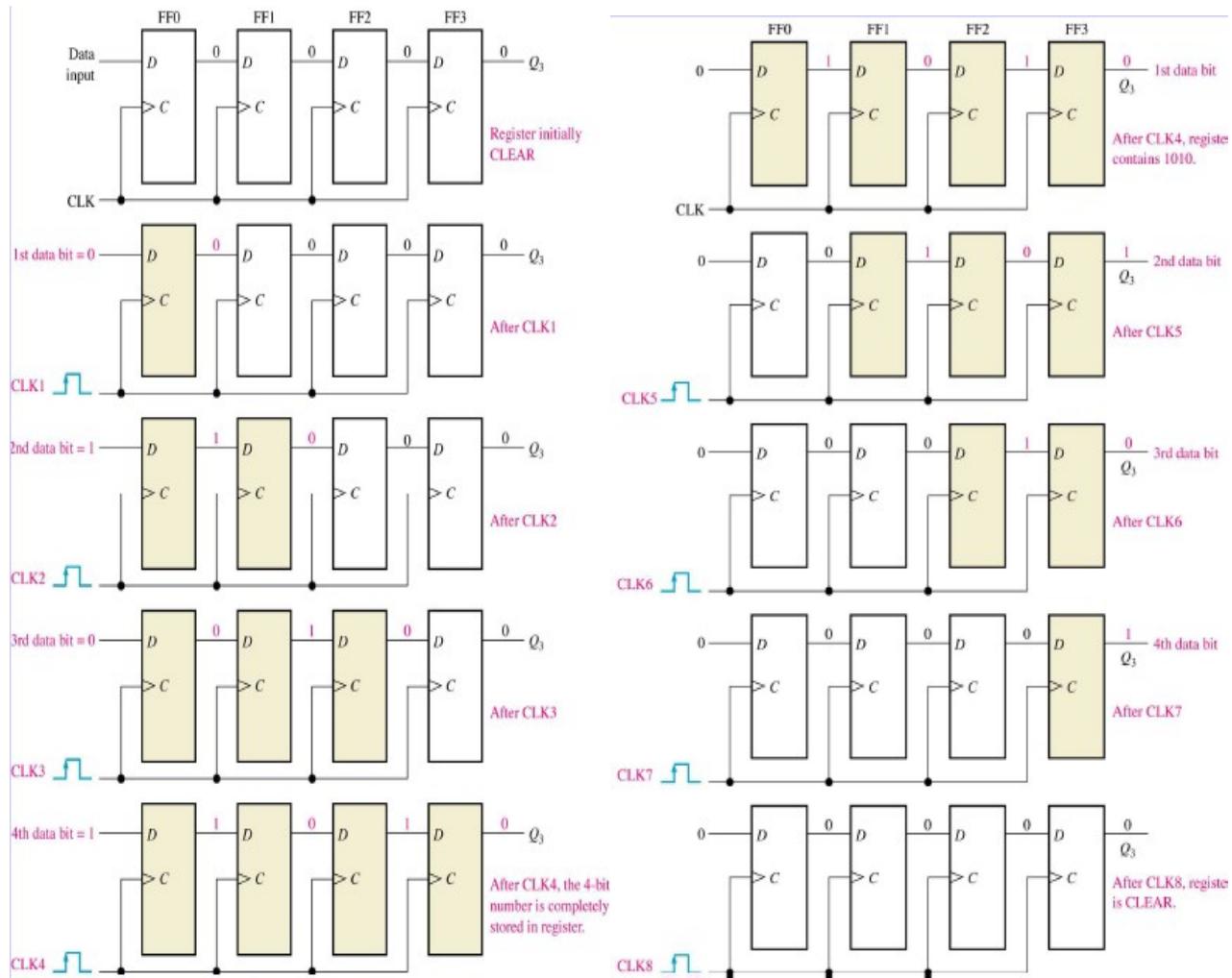


<i>CLK</i>	Serial Input <i>D</i> <sub>in</sub>	<i>Q</i> <sub>3</sub>	<i>Q</i> <sub>2</sub>	<i>Q</i> <sub>1</sub>	<i>Q</i> <sub>0</sub>
Initially		0	0	0	0
1 <sup>st</sup>	1	1	0	0	0
2 <sup>nd</sup>	1	1	1	0	0
3 <sup>rd</sup>	1	1	1	1	0
4 <sup>th</sup>	1	1	1	1	1

Direction of data travel →
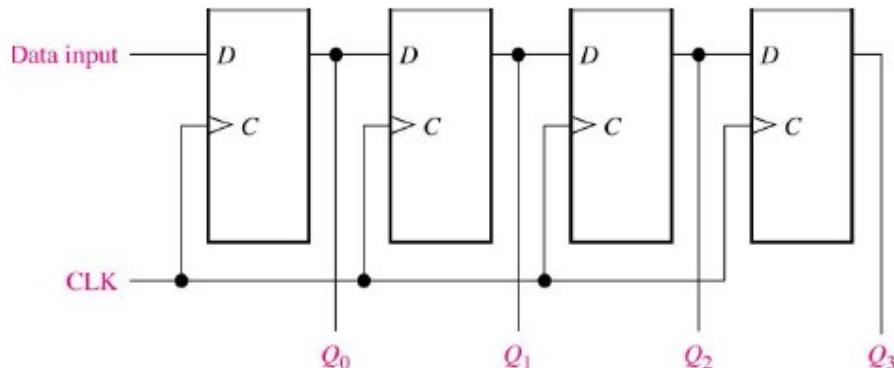
### Serial-in, parallel-out, shift register:

In this type of register, the data bits are entered into the register serially, but the data stored in the register is shifted out in parallel form.

Once the data bits are stored, each bit appears on its respective output line and all bits are available simultaneously, rather than on a bit-by-bit basis with the serial output. The serial-in, parallel out, shift register can be used as serial-in, serial out, shift register if the output is taken from the Q terminal of the last FF.



Clock Pulse No	QA	QB	QC	QD
0	0	0	0	0
1	1	0	0	0
2	0	1	0	0
3	0	0	1	0
4	0	0	0	1
5	0	0	0	0

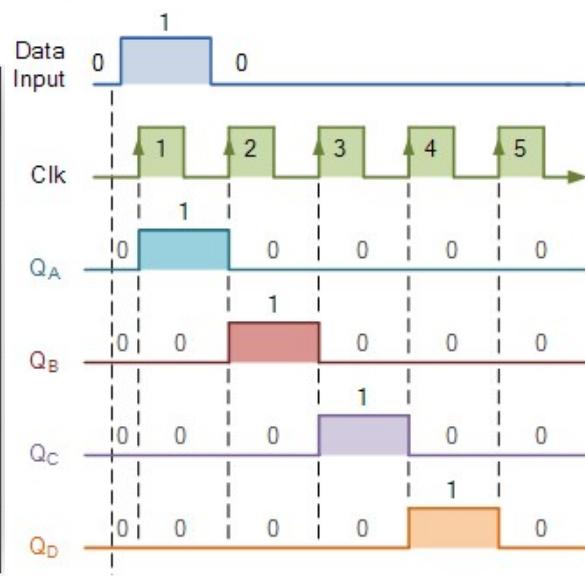


Figure.3.36

### Parallel-in, serial-out, shift register:

For a parallel-in, serial out, shift register, the data bits are entered simultaneously into their respective stages on parallel lines, rather than on a bit-by-bit basis on one line as with serial data bits are transferred out of the register serially. On a bit-by-bit basis over a single line.

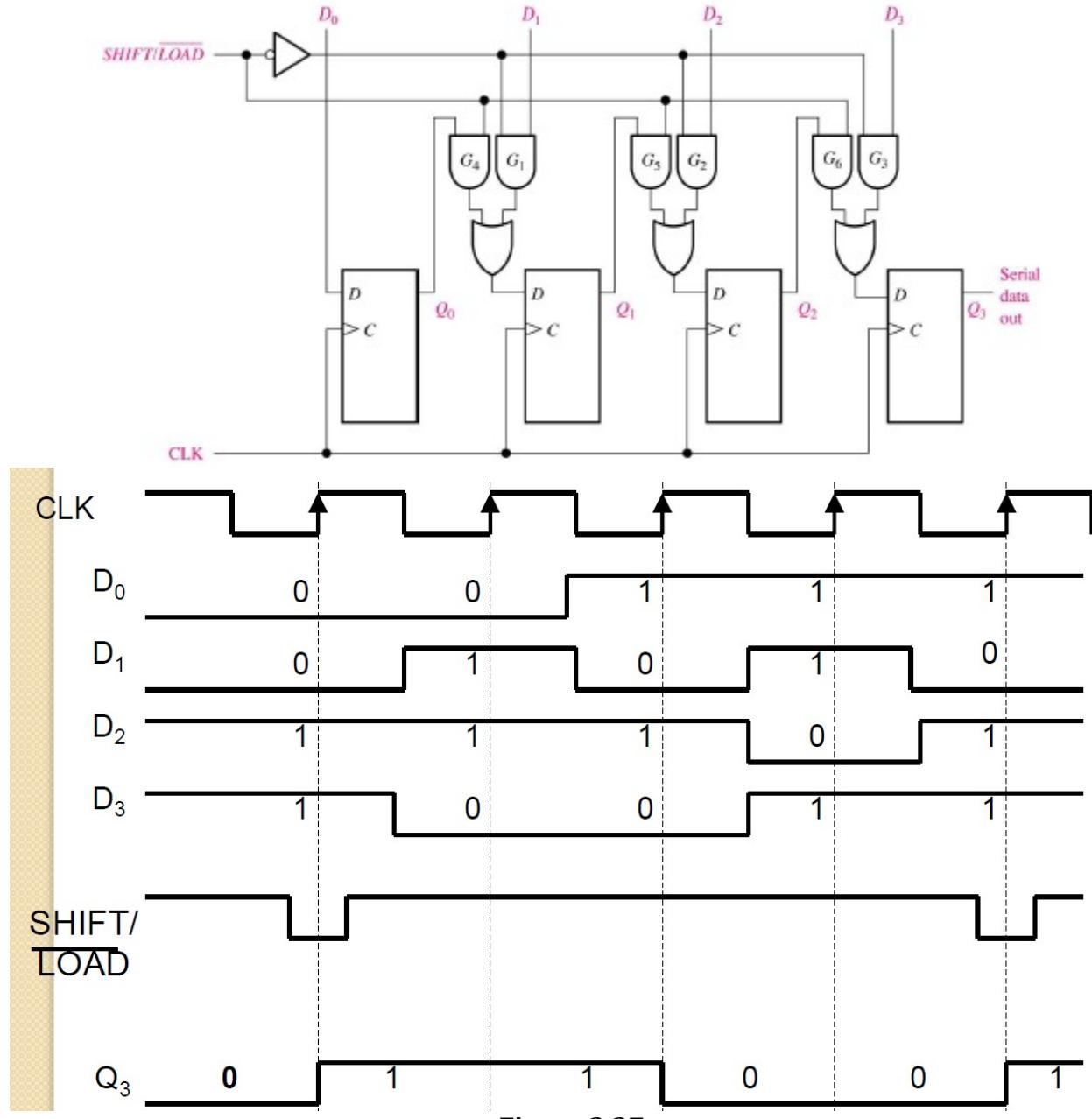


Figure.3.37

There are four data lines A, B, C, D through which the data is entered into the register in parallel form. The signal shift/ load allows the data to be entered in parallel form into the register and the data is shifted out serially from terminal Q4.

### Parallel-in, parallel-out, shift register

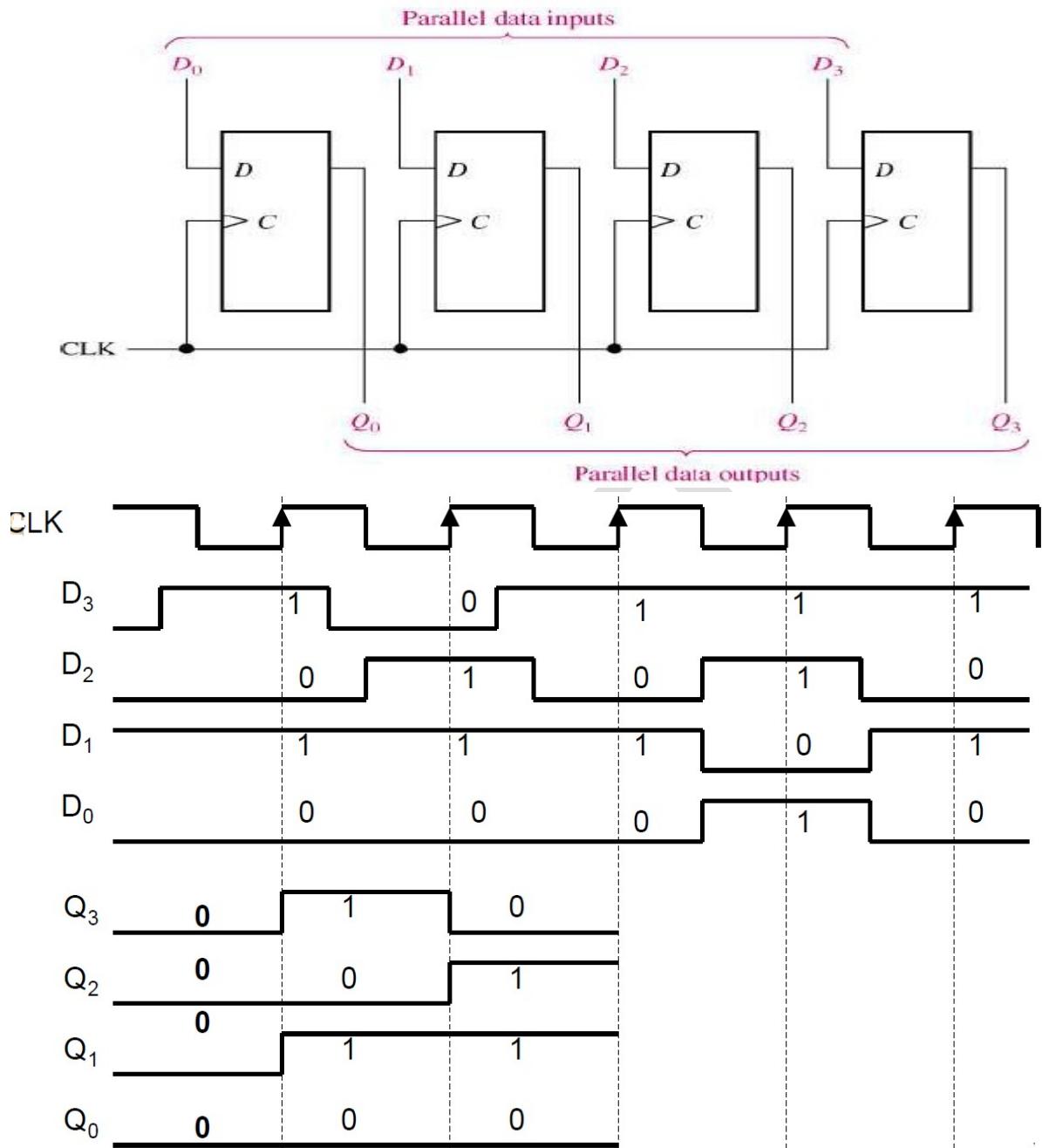


Figure.3.38

In a parallel-in, parallel-out shift register, the data is entered into the register in parallel form, and also the data is taken out of the register in parallel form. Data is applied to the D input terminals of the FF's. When a clock pulse is applied, at the positive going edge of the pulse, the D inputs are shifted into the Q outputs of the FFs. The register now stores the data. The stored data is available instantaneously for shifting out in parallel form.

### Bidirectional shift register:

A bidirectional shift register is one which the data bits can be shifted from left to right or from right to left. A fig shows the logic diagram of a 4-bit serial-in, serial out, bidirectional shift register. Right/left is the mode signal, when right /left is a 1, the logic circuit works as a shift-register.the bidirectional operation is achieved by using the mode signal and two NAND gates and one OR gate for each stage.

A HIGH on the right/left control input enables the AND gates G1, G2, G3 and G4 and disables the AND gates G5,G6,G7 and G8, and the state of Q output of each FF is passed through the gate to the D input of the following FF. when a clock pulse occurs, the data bits are then effectively shifted one place to the right. A LOW on the right/left control inputs enables the AND gates G5, G6, G7 and G8 and disables the And gates G1, G2, G3 and G4 and the Q output of each FF is passed to the D input of the preceding FF. when a clock pulse occurs, the data bits are then effectively shifted one place to the left. Hence, the circuit works as a bidirectional shift register.


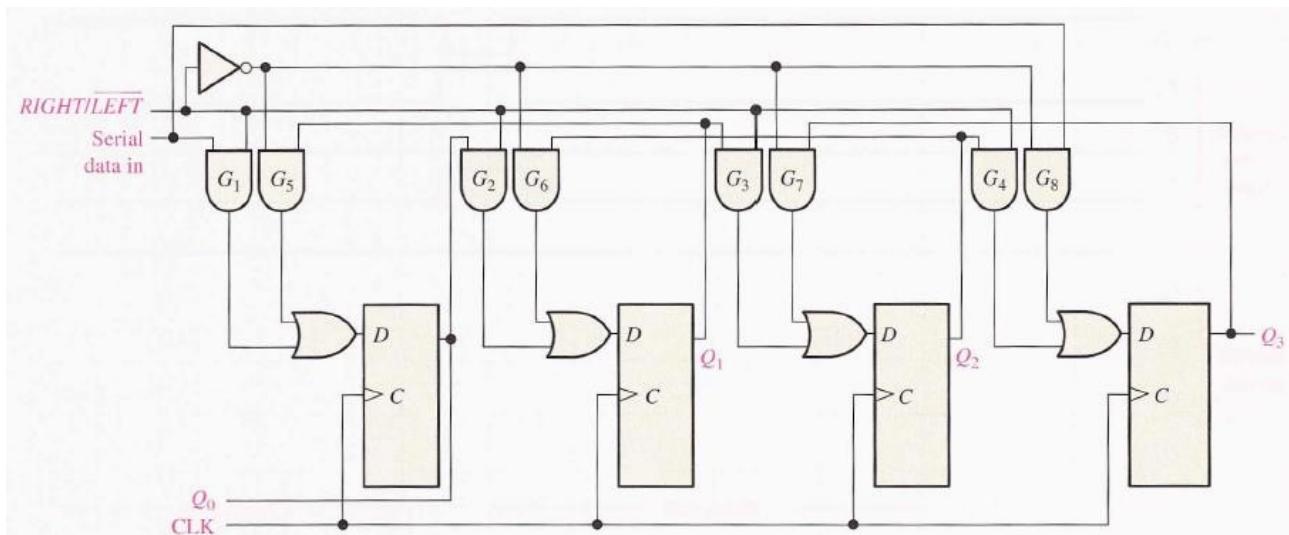


Figure 3.39: logic diagram of a 4-bit bidirectional shift register

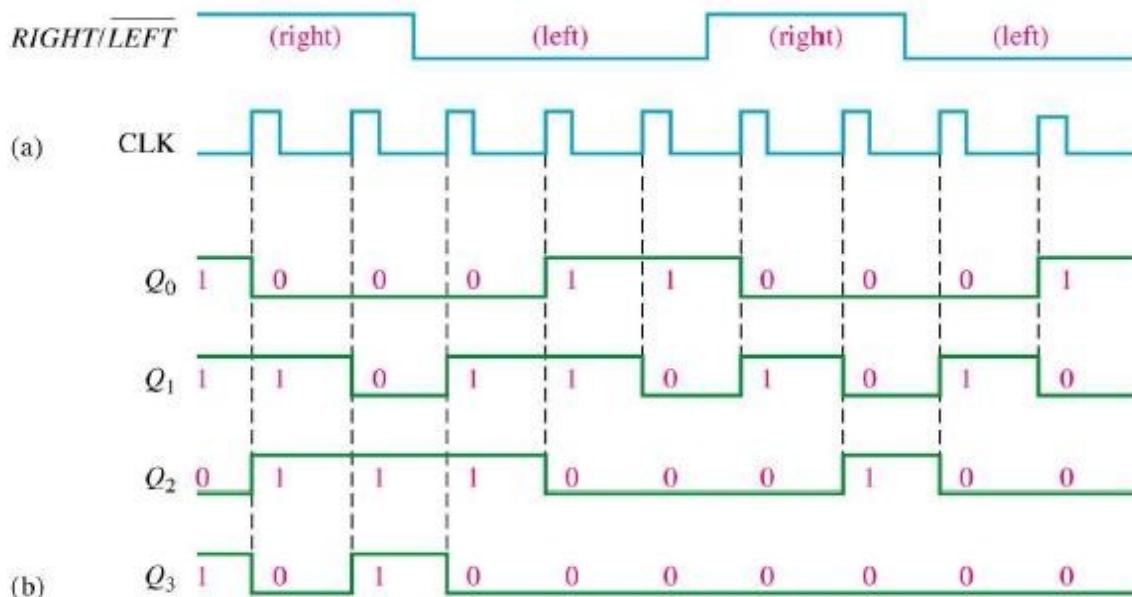

## Universal shift register:

A register is capable of shifting in one direction only is a unidirectional shift register. One that can shift both directions is a bidirectional shift register. If the register has both shifts and parallel load capabilities, it is referred to as a universal shift registers. Universal shift register is a bidirectional register, whose input can be either in serial form or in parallel form and whose output also can be in serial form or I parallel form.

The most general shift register has the following capabilities.

1. A clear control to clear the register to 0
2. A clock input to synchronize the operations
3. A shift-right control to enable the shift-right operation and serial input and output lines associated with the shift-right.
4. A shift-left control to enable the shift-left operation and serial input and output lines associated with the shift-left
5. A parallel loads control to enable a parallel transfer and the  $n$  input lines associated with the parallel transfer  $N$  parallel output lines
6. A control state that leaves the information in the register unchanged in the presence of the clock.

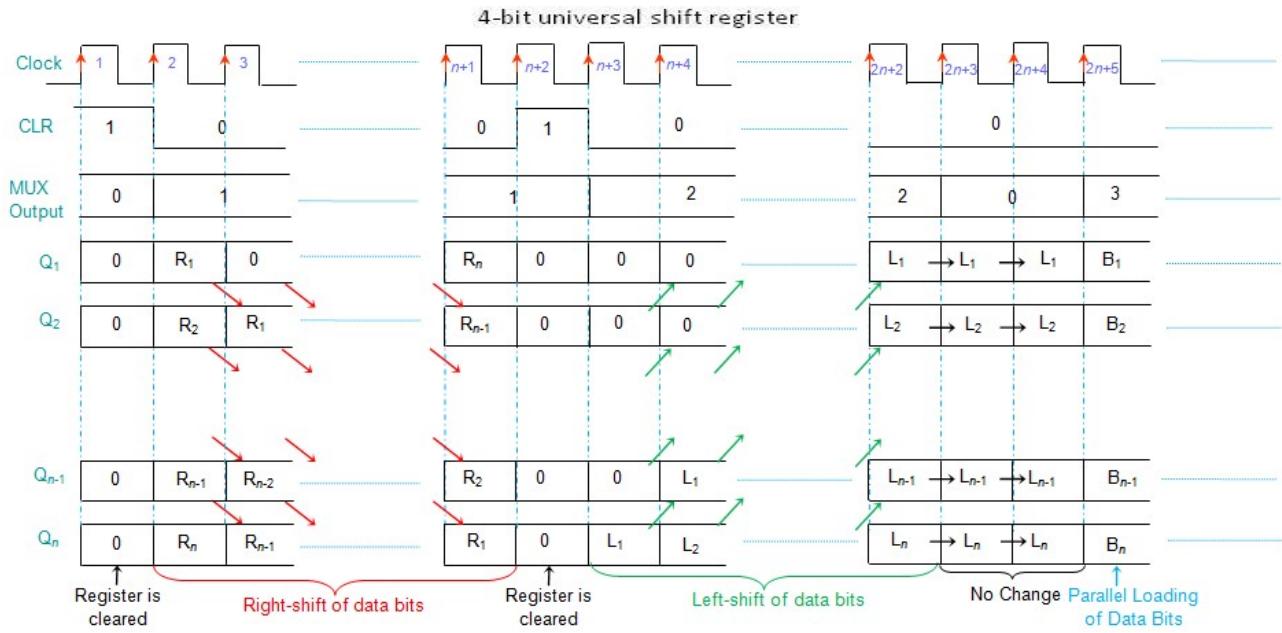
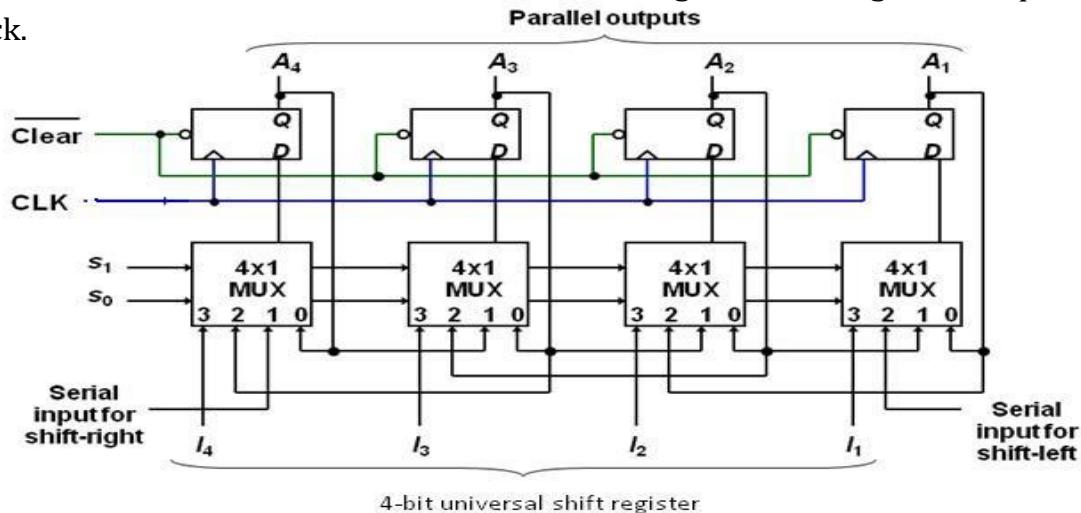


Figure.3.40

A universal shift register can be realized using multiplexers. It consists of 4 D flip-flops and four multiplexers. The four multiplexers have two common selection inputs s1 and s0. Input 0 in each multiplexer is selected when S1S0=00, input 1 is selected when S1S0=01 and input 2 is selected when S1S0=10 and input 4 is selected when S1S0=11. The selection inputs control the mode of operation of the register according to the functions entries. When S1S0=0, the present value of the register is applied to the D inputs of flip-flops. The condition forms a path from the output of each flip-flop into the input of the same flip-flop. The next clock edge transfers into each flip-flop the binary value it held previously, and no change of state occurs. When S1S0=01, terminal 1 of the multiplexer inputs have a path to the D inputs of the flip-flop. This causes a shift-right operation, with serial input transferred into flip-flop A4. When S1S0=10, a shift left operation results with the other serial input going into flip-flop A1. Finally when S1S0=11, the binary information on the parallel input lines is transferred into the register simultaneously during the next clock cycle.

## Counters:

A counter is a sequential machine that produces a specified count sequence. The count changes whenever the input clock is asserted.

There is a great variety of counter based on its construction.

1. Clock: Synchronous or Asynchronous
2. Clock Trigger: Positive edged or Negative edged
3. Counts: Binary, Decade
4. Count Direction: Up, Down, or Up/Down
5. Flip-flops: JK or T or D

**Counter** that follows the binary number sequence is called a *binary counter*. An  $n$ -bit binary counter that cycles through all  $2^n$  states in ascending (or descending) order. It consists of  $n$  flip-flops and can count in binary from 0 through  $2^n - 1$ . A counter may also follow any other sequence of states.

A modulo-  $N$  counter (also known as a divide-by-  $N$  counter) follows the sequence of  $N$  states repeatedly.

There are **two** categories of counters: **asynchronous** counters and **synchronous** counters.

In an **asynchronous** counter, all the bits in the count change synchronously with the assertion of the clock. With an asynchronous circuit, all the bits in the count do not all change at the same time.

Asynchronous counters are also called **ripple counters** because of the way the clock pulse ripples its way through the flip-flops.

In a **synchronous counter**, all flip-flops receive the common clock. Synchronous counters are faster than asynchronous counter because in synchronous counter all flip flops are clocked simultaneously.

<b>3-bit Up Counter</b>	<b>3-bit Down Counter</b>
000	000
001	111
010	110
011	101
100	100
101	011
110	010
111	001

### **Binary Ripple Counter (asynchronous UP Counter):**

A binary ripple counter is an asynchronous counter where only the first flip-flop is clocked by an external clock. Each subsequent flip-flop is triggered by the transition occurring in the preceding flip-flop.

The main characteristic of an asynchronous counter is each flip-flop derives its own clock from other flip-flops and is therefore independent of the input clock. Consequently, the output of each flip-flop may change at different time, hence the term asynchronous. From the asynchronous counter diagram above, we observed that the output of the first flip-flop becomes the clock input for the second flip-flop, and the output of the second flip-flop becomes the clock input for the third flip-flop etc.

For the first flip-flop, the output changes whenever there is a negative transition in the clock input. This means that the output of the first flipflop produces a series of square waves that is half the frequency of the clock input. Since the output of the first flip-flop becomes the clock of the second flip-flop, the output of the second flip-flop is half the frequency of its clock, i.e. the output of the first flip-flop that in turn is half the frequency of the clock input. This behavior, in essence is captured by the binary bit pattern in the counting sequence

A counter may count up or count down or count up and down depending on the input control. Going through a count sequence from 0000,0001,0010, and so on, we note that the least significant bit,  $Q_0$ , toggles once with each count pulse input.  $Q_1$  is toggled every time that  $Q_0$  changes from 1 to 0.  $Q_2$  is toggled every time that  $Q_1$  changes from 1 to 0 and so on for any other higher order bits of a ripple counter. A 4-bit binary ripple counter constructed using  $T$  flip-flops and  $D$  flip-flops is shown in Fig.

In a count-down counter, LSB is toggled with every count pulse. Any higher-order bit is toggled if the preceding bit has a transition from 0 to 1. In this counter, the complement terminals  $Q'$  of all flip-flops give the outputs. Therefore, the diagram of a binary countdown counter looks the same as the binary ripple counter in Fig. , provided that all flip-flops trigger on the positive edge of the clock. (The bubble in the C inputs must be removed.)

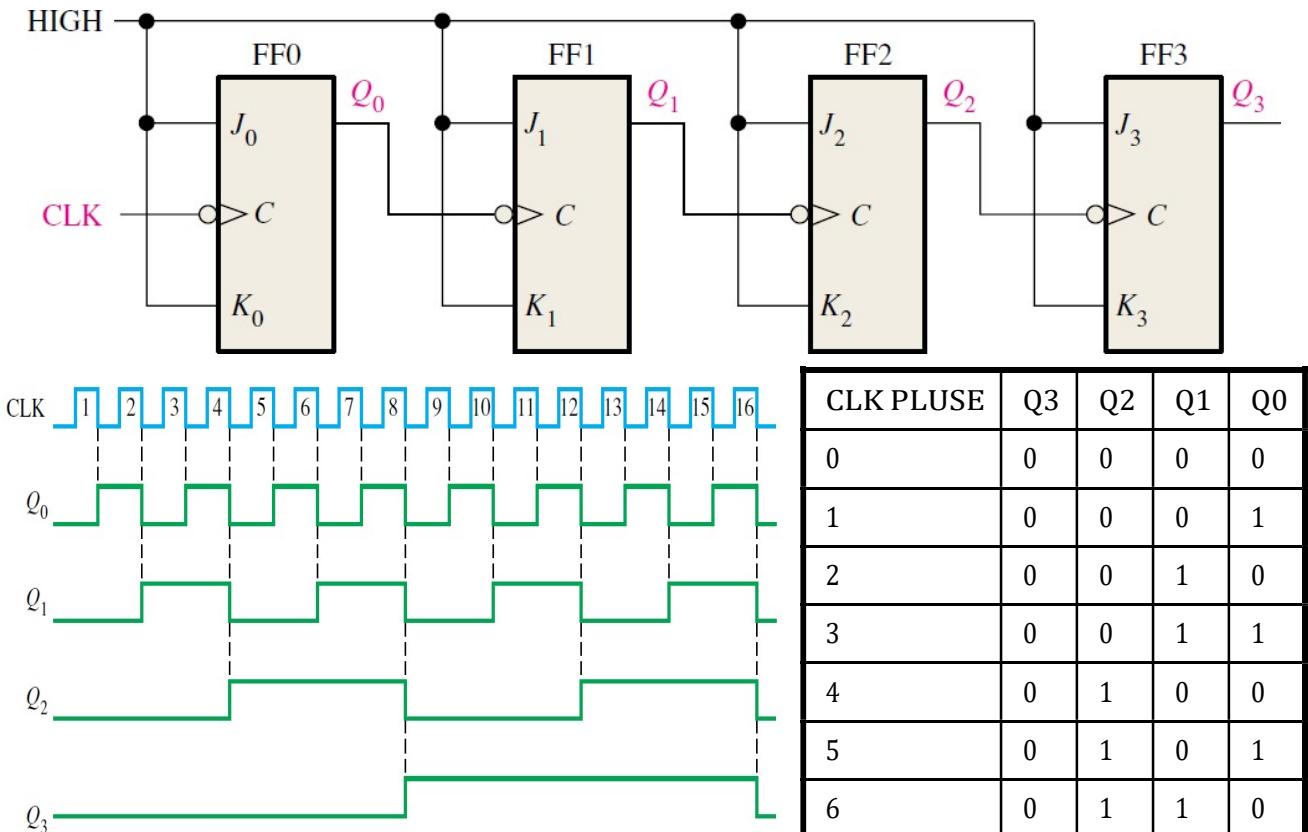


Figure.3.41



### 4-bit Ripple up counter:

A 4-bit up-counter counts from 0 to 15 or in binary, from 0000 to 1111. A 4-bit ripple up-counter, using negative edge-triggered  $J - K$  FFs is shown in Figure 8.4.9. The inputs  $J$  and  $K$  of flip-flops are connected to logic 1. Each flip-flop acts as a toggle switch.

The output of the first flip-flop feeds the clock input of the second, and the output of the second flip-flop feeds the clock input of the third, the output of which in turn feeds the clock input of the fourth flip-flop. The outputs of the four flip-flops are designated as  $Q_0$  (LSB),  $Q_1$ ,  $Q_2$  and  $Q_3$  (MSB). Figure 8.4.10 shows the waveforms appearing at  $Q_0$ ,  $Q_1$ ,  $Q_2$  and  $Q_3$  outputs as the clock signal goes through successive cycles of trigger pulses.

If you compare this counter with the up-counter in Figure 8.4.9 the only difference you will notice is that, in the down counter in Figure 8.4.11, the complement output instead of the normal output, is connected to the clock input of the next flip-flop. However, the counter output in both up and down counters, is the normal output,  $Q$ , of the flip-flops.

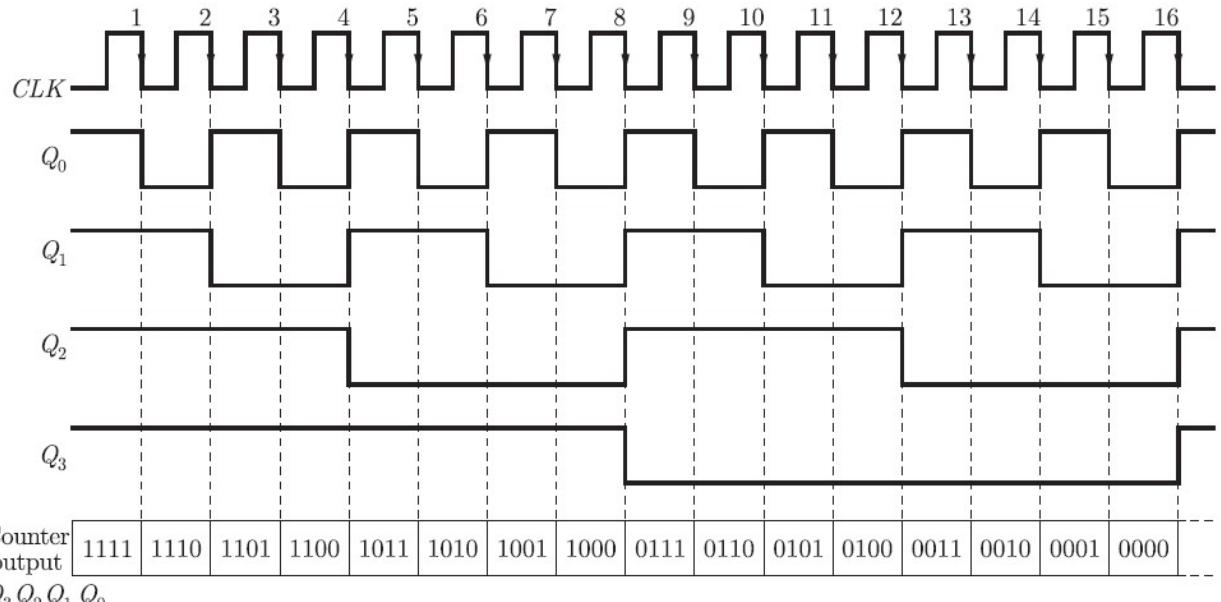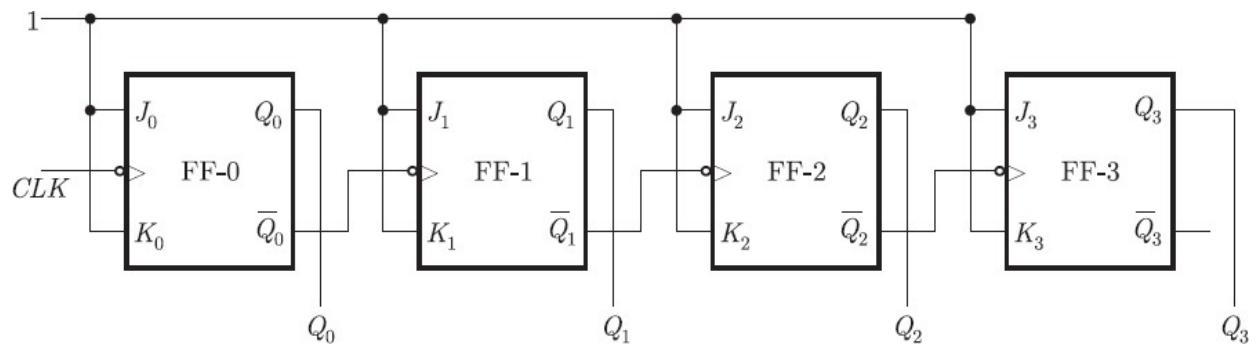The timing diagram is shown in Figure 8.4.12. It shows the waveforms appearing at  $Q_0$ ,  $Q_1$ ,  $Q_2$  and  $Q_3$  outputs as the clock signal goes through successive cycles of trigger pulses.



Clock Pulse	$Q_3$	$Q_2$	$Q_1$	$Q_0$
0	1	1	1	1
1	1	1	1	0
2	1	1	0	1
3	1	1	0	0
4	1	0	1	1
5	1	0	1	0
6	1	0	0	1
7	1	0	0	0
8	0	1	1	1
9	0	1	1	0
10	0	1	0	1
11	0	1	0	0
12	0	0	1	1
13	0	0	1	0
14	0	1	0	1
15	0	0	0	0

Figure.3.42


## Asynchronous Decade Counters:


The modulus of a counter is the number of unique states through which the counter will sequence. The maximum possible number of states (maximum modulus) of a counter is  $2^n$ , where  $n$  is the number of flip-flops in the counter. Counters can be designed to have a number of states in their sequence that is less than the maximum of  $2^n$ . This type of sequence is called a *truncated sequence*. One common modulus for counters with truncated sequences is ten (called MOD10).

Counters with ten states in their sequence are called decade counters. A decade counter with a count sequence of zero (0000) through nine (1001) is a BCD decade counter because its ten-state sequence produces the BCD code. This type of counter is useful in display applications in which BCD is required for conversion to a decimal readout. To obtain a truncated sequence, it is necessary to force the counter to recycle before going through all of its possible states. For example, the BCD decade counter must recycle back to the 0000 state after the 1001 state. A decade counter requires four flip-flops (three flip-flops are insufficient because  $2^3 = 8$ ).

Let's use a 4-bit asynchronous counter such as the one in Example 1 and modify its sequence to illustrate the principle of truncated counters. One way to make the counter recycle after the count of nine (1001) is to decode count ten (1010) with a NAND gate and connect the output of the NAND gate to the clear (*CLR*) inputs of the flip-flops, as shown in Figure 12(a).

Partial Decoding Notice in Figure 12(a) that only  $Q_1$  and  $Q_3$  are connected to the NAND gate inputs. This arrangement is an example of *partial decoding*, in which the two unique states ( $Q_1 = 1$  and  $Q_3 = 1$ ) are sufficient to decode the count of ten because none of the other states (zero through nine) have both  $Q_1$  and  $Q_3$  HIGH at the same time. When the counter goes into count ten (1010), the decoding gate output goes LOW and asynchronously resets all the flip-flops.

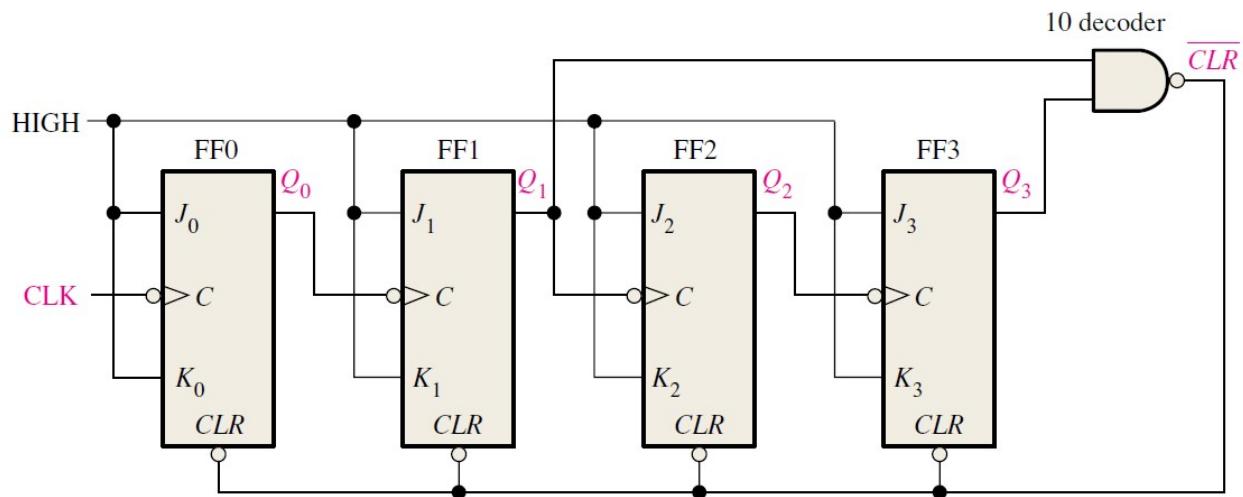

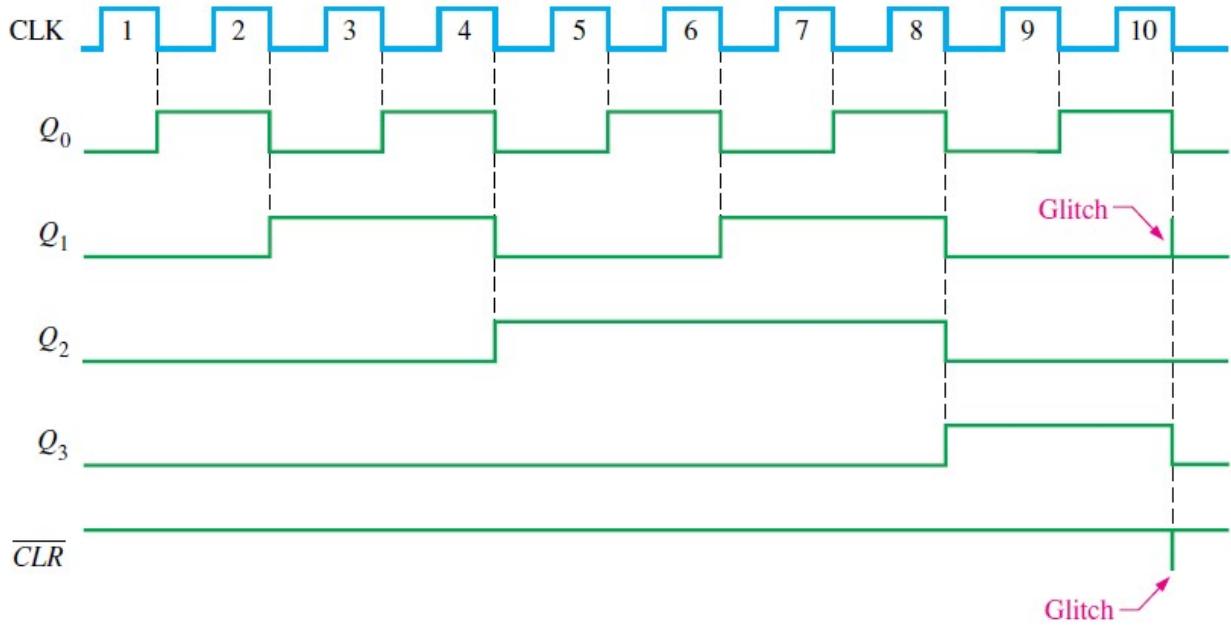

Input Pulses	D	C	B	A
0	0	0	0	0
1	0	0	0	1
2	0	0	1	0
3	0	0	1	1
4	0	1	0	0
5	0	1	0	1
6	0	1	1	0
7	0	1	1	1
8	1	0	0	0
9	1	0	0	1
10	1	0	1	0
0	0	0	0	0 (resets)

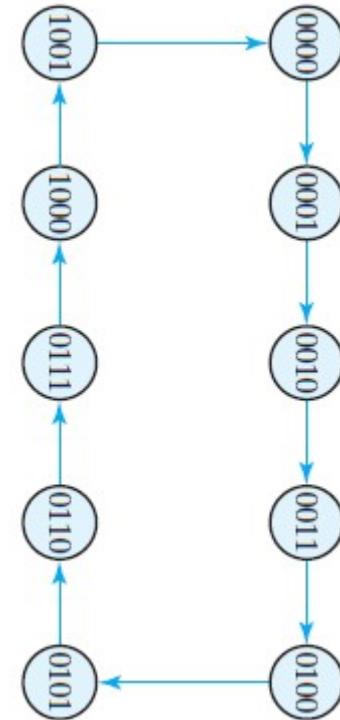


Figure 3.43

The resulting timing diagram is shown in Figure 12(b). Notice that there is a glitch on the  $Q_1$  waveform. The reason for this glitch is that  $Q_1$  must first go HIGH before the count of ten can be decoded. Not until several nanoseconds after the counter goes to the count of ten does the output of the decoding gate go LOW (both inputs are HIGH). Thus, the counter is in the 1010 state for a short time before it is reset to 0000, thus producing the glitch on  $Q_1$  and the resulting glitch on the  $\overline{CLR}$  line that resets the counter.

## **BINARY RIPPLE COUNTER WITH A MODULUS OF LESS THAN $2^N$ :**

The ripple counters discussed so far are full modulus counters. That is if  $n$  is the number of flip-flops or bits, then it will have MOD number equal to  $2^n$ . This is the maximum MOD-number that can be obtained using  $n$  flip-flops.

The basic  $n$ -flip-flop binary ripple counter can be modified to have a modulus less than  $2^n$ , with the help of simple externally connected combinational logic. This type of counter does not utilize all the possible states. Some of the states will be skipped. We will illustrate this simple concept with the help of an example.

### **METHODOLOGY :**


1. Determine the minimum number of flip-flops  $n$  so that  $N < 2^n$  and connect these flip-flops as a binary ripple counter
2. Find the binary number for  $N$ .
3. Identify the flip-flops for which output  $Q = 1$ , when the count is  $N$ . Choose a NAND gate with the number of inputs equal to the number of flip-flops for which output  $Q = 1$ . As an example, if the objective were to design an MOD-11 counter, then, in the corresponding count, that is, 1011, three flip-flops output are 1. The desired NAND gate would therefore be a three-input gate.
4. Connect the  $Q$  outputs of the identified flip-flops to the inputs of the NAND gate and the NAND gate output to asynchronous clear inputs of all flip-flops.

### **Design of MOD-6 Ripple Counter:**

The steps are as follows:

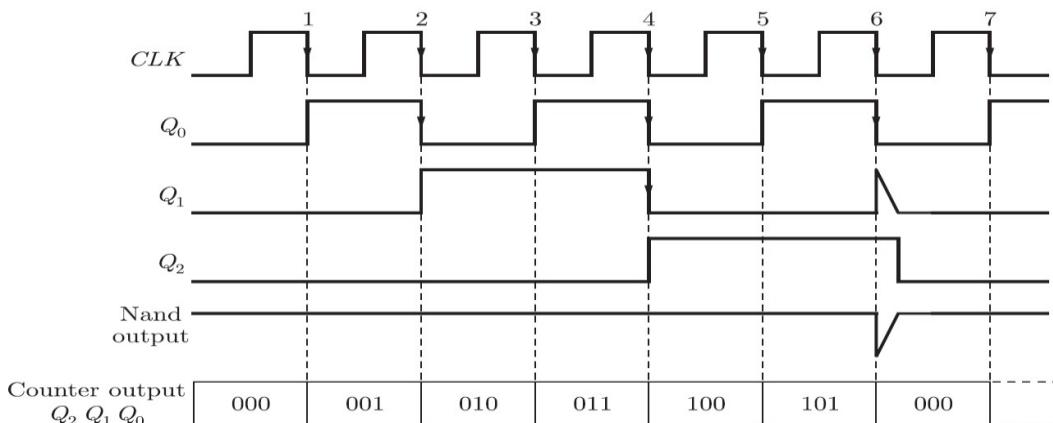
1. Here  $N = 6$ , so the minimum number of flip-flops such that  $6 < 2^3$ , will be 3. Now, connect three-flops as a binary ripple counter shown in Figure.
2. The binary number for  $N$  is 110.
3. The flip-flops for which output will be 1 at the count 110 are FF2 and FF1. So we choose a 2-input NAND gate.
4. Connect the  $Q$  outputs of the FF2 and FF1 flip-flops that is  $Q_2$  and  $Q_1$  to the inputs of the NAND gate and the NAND gate output to asynchronous clear inputs of all flip-flops.

The arrangement is shown in Figure, and the timing diagram is shown below.



**Timing Diagram of MOD-6 ripple counter**

The counter counts from 000 to 101 until NAND gate output is HIGH. But, when it goes to state 110, all NAND gate inputs becomes HIGH and its output will be LOW. Therefore, all the flip-flops will be cleared and it resets back to state 000. From timing diagram we can see that the frequency of the  $Q_2$  output is one-sixth of the input clock frequency. In other words, this MOD-6 counter has divided the input frequency by 6.

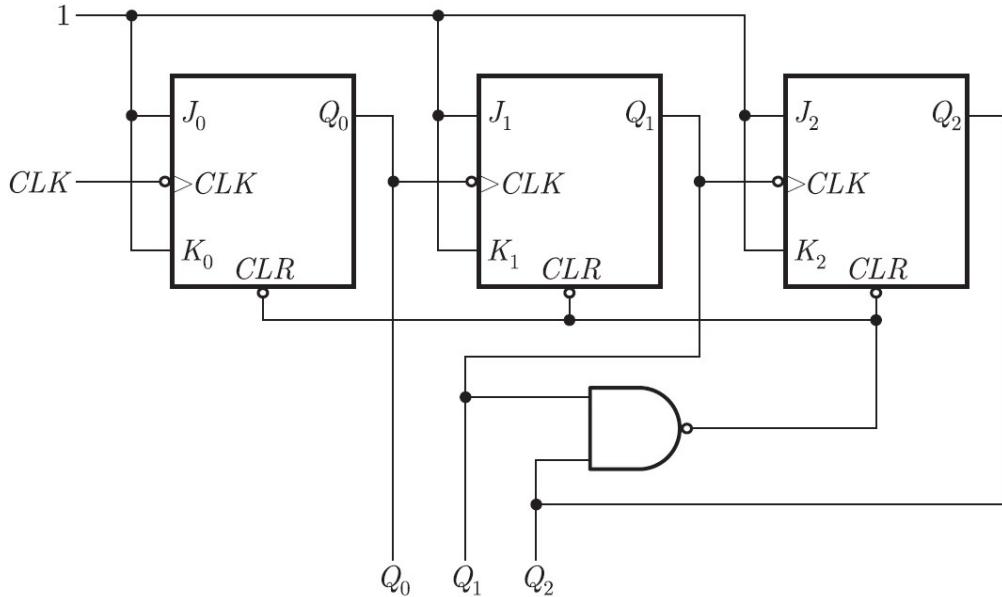

**Figure.3.44:Logic Diagram of MOD-6 Ripple Counter**

### Synchronous Counters:


In synchronous counters, all flip-flops are triggered by common clock pulse input. This is different from ripple counter where flip-flops are triggered one at a time in succession.

In this counter, the flip-flop corresponding to LSB is toggled with every clock pulse. A flip-flop in any other position is toggled on the next clock pulse provided all the preceding (lower-order) bits are equal to 1. Note that the polarity of the clock is important in the ripple counter and not here.
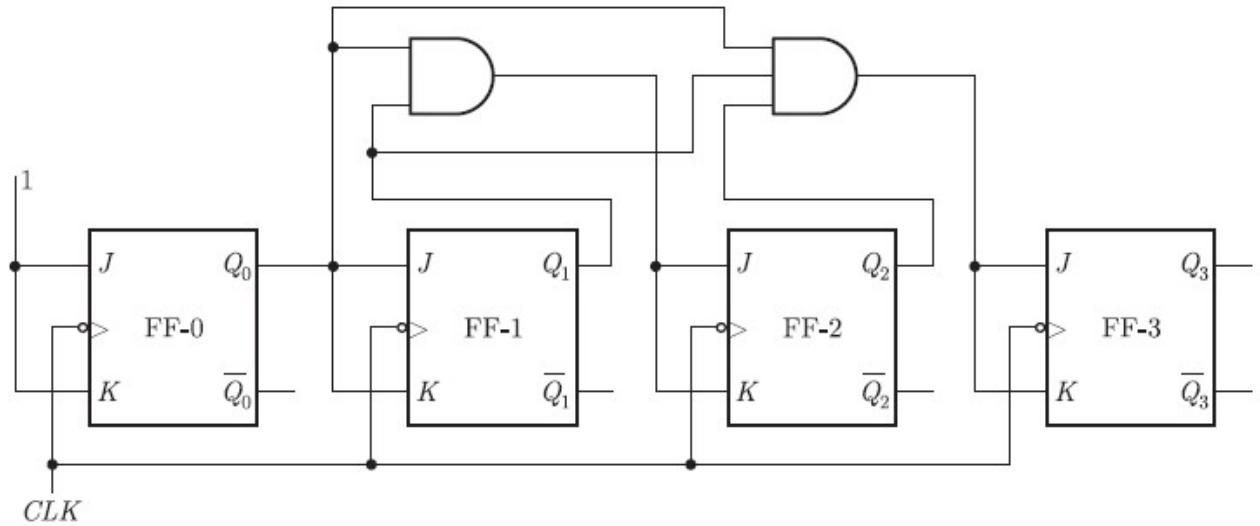
### Synchronous Binary Up Counters :


A synchronous binary counter counts from 0 to  $2^N-1$ , where N is the number of bits/flip-flops in the counter. Each flip-flop is used to represent one bit. The flip-flop in the lowest-order position is complemented/toggled with every clock pulse and a flip-flop in any other position is complemented on the next clock pulse provided all the bits in the lower-order positions are equal to 1.

For example, consider the counting sequence of a four bit binary count shown in Table. We note that flip-flop FF-0 toggles with every clock pulse, flip-flop FF-1 toggles only when the output of FF0 is in the '1' state, flip-flop FF2 toggles only with those clock pulses when the outputs of FF0 and FF1 are both in the logic '1' state and flip-flop FF3 toggles only with those clock pulses when  $Q_0$ ,  $Q_1$  and  $Q_2$  are all in the logic '1' state. Such logic can be easily implemented with AND gates as shown in Figure 8.10.1. This is a 4-bit synchronous counter using J -K flip-flop. The timing waveforms are shown in Figure 3.45 which is self-explanatory.



**Count sequence of a four bit binary counter:**

Count	$Q_3$	$Q_2$	$Q_1$	$Q_0$	Count	$Q_3$	$Q_2$	$Q_1$	$Q_0$
0	0	0	0	0	8	1	0	0	0
1	0	0	0	1	9	1	0	0	1
2	0	0	1	0	10	1	0	1	0
3	0	0	1	1	11	1	0	1	1
4	0	1	0	0	12	1	1	0	0
5	0	1	0	1	13	1	1	0	1
6	0	1	1	0	14	1	1	1	0
7	0	1	1	1	15	1	1	1	1

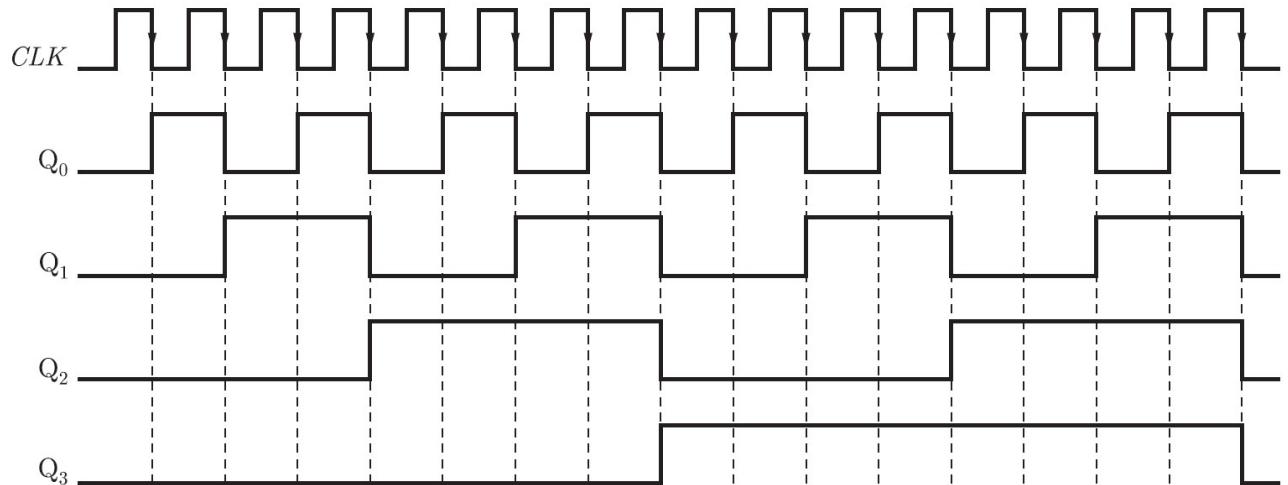

**Timing diagram of a 4-bit synchronous up-counter**  
**Figure.3.45 : 4-bit Synchronous Binary Up-Counter**


From the diagram above, we can see that although the counter is synchronous and is supposed to change simultaneously, we have a propagation delay through the AND gates which add up to give an overall propagation delay which is proportional to the number of bits of the counter. To overcome this problem, we can feed the outputs from the flip-flops directly to a many-input AND gate as follows:

There are many variations to the basic binary counter. The one described above is the binary up counter (counts upwards). Besides the up counter, there is the binary down counter, the binary up/down counter, binary-coded-decimal (BCD) counter etc. Any counter that counts in binary is called a binary counter.

### **Synchronous Binary down Counters:**

In a binary up counter, a particular bit, except for the first bit, toggles if all the lower-order bits are 1's. The opposite is true for binary down counters. That is, a particular bit toggles if all the lower-order bits are 0's and the first bit toggles on every pulse.

Taking an example,  $Q_3 Q_2 Q_1 Q_0 = 0100$ . On the next count,  $Q_3 Q_2 Q_1 Q_0 = 0011$ .  $Q_0$ , the lowest-order bit, is always complemented.  $Q_1$  is complemented because all the lower-order positions ( $Q_0$  only in this case) are 0's.  $Q_2$  is also complemented because all the lower-order positions,  $Q_1$  and  $Q_0$  are 0's. But  $Q_3$  is not complemented the lower-order positions,  $Q_2 Q_1 Q_0 = 011$ , do not give an all 0 condition.

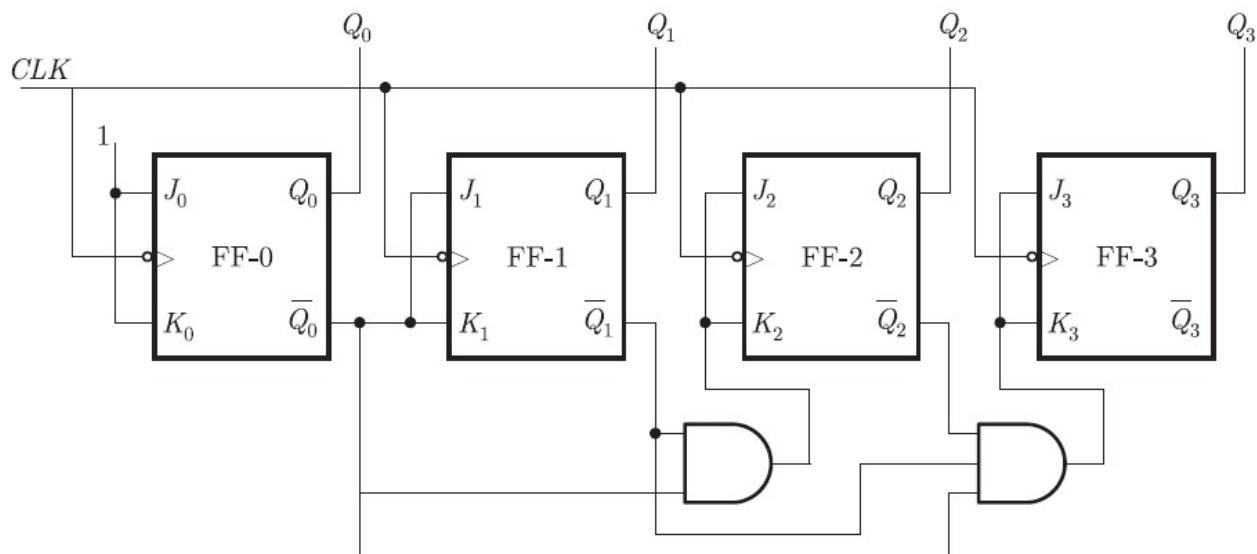


**Figure.3.46 : 4-bit Synchronous Binary Down Counter**

The implementation of a synchronous binary down counter is exactly the same as that of asynchronous binary up counter except that the inverted output from each flip-flop is used. All the methods used improve a binary up counter can be similarly applied here.

### **Synchronous Binary Up/Down Counters:**

The similarities between the implementation of a binary up counter and a binary down counter leads to the possibility of a binary up/down counter, which is a binary up counter and a binary down counter combined into one. Since the difference is only in which output of the flip-flop to use, the normal output or the inverted one, we use two AND gates for each flip-flop to "choose" which of the output to use.

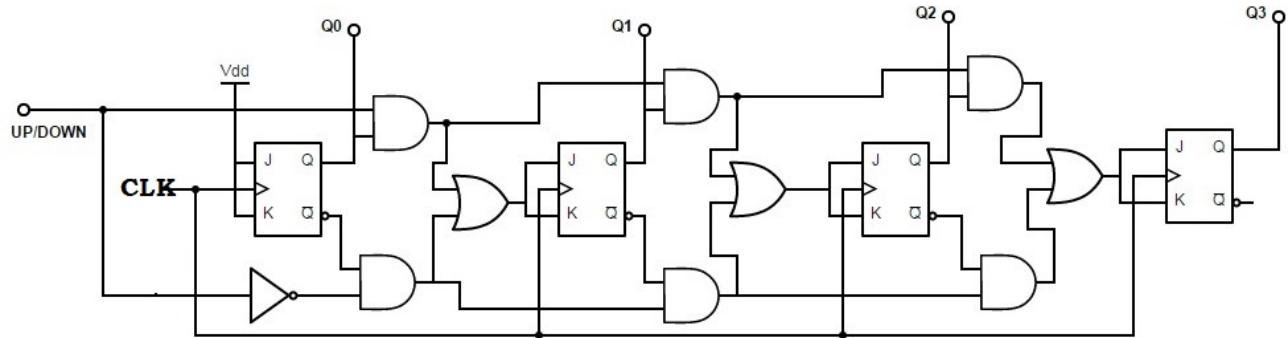

**Figure.3.47 : 4-bit Synchronous Binary Up/Down Counter**

From the diagram, we can see that COUNT-UP and COUNT-DOWN are used as control inputs to determine whether the normal flip-flop outputs or the inverted ones are fed into the J-K inputs of the following flip-flops. If neither is at logic level 1, the counter doesn't count and if both are at logic level 1, all the bits of the counter toggle at every clock pulse. The OR gate allows either of the two outputs which have been enabled to be fed into the next flip-flop. As with the binary up and binary down counter, the speed up techniques apply.

### **DESIGN OF SYNCHRONOUS COUNTERS:**

In this section, we will discuss a commonly used technique to design synchronous counter using  $J$  - $K$  flip-flop or  $D$  flip-flop or  $T$  flip-flop. The design of synchronous counters basically involves designing a suitable combinational logic circuit that takes its inputs from the normal and complemented outputs of the flip-flops used and decodes the different states of the counter to generate the correct logic states for the inputs of the flip-flops such as  $J$ ,  $K$ ,  $D$ , etc.

#### **Design Procedure**

The design procedure of synchronous counter is as follows:

##### **1. Number of Flip-flops**

Find the number of flip-flops required. For a Mod- $M$  counter, the minimum number of flip-flops required is  $n$ , such that  $M \# 2^n$ .

##### **2. State Transition Diagram**

Draw the state transition diagram showing all possible states. Note that we can also include invalid state in the state transition diagram. If the next state to invalid state is not mentioned, we take it 000.

##### **3. Choice of Flip-flops and Excitation Table**

Select the type of the flip-flops to be used and write the excitation table for the counter. An excitation table is a table that lists the present state (PS), the next state (NS) and the required excitations of the flip-flops inputs.

Note that entries for excitations corresponding to invalid states are taken as don't care.

##### **4. Minimal Expression for Flip-flop Inputs**

Prepare K-map for each input of flip-flops in terms of the present states of flip-flops. Obtain the minimal expressions for the excitations of the FFs using the K-maps

##### **5. Logic Diagram:** Connect the inputs of the flip-flops as per the simplified Boolean equations

## Design of a Synchronous MOD-10 (BCD or Decade) Counter:

A BCD or Decade (MOD-10) counter has ten states i.e., 0 to 9. We consider the design of MOD-10 counter using  $J$ - $K$  flip-flops. The steps of design are as follows:

### Step 1: Number of Flip-flops

Here, modulus  $M = 10$ , so  $10 \# 2^4$  and therefore, the number of flipflops required will be 4.

### Step 2: State Transition Diagram

The state diagram for the BCD counter is drawn as shown in Figure.

### Step 3: Choice of Flip-flops and Excitation Table


$J$ - $K$  flip-flops are selected and the excitation table of a mod-10 counter using  $J$ - $K$  flip-flops is drawn as in Table 8.11.4. Note that six states 1010, 1011, 1100, 1101, 1110 and 1111 are invalid, so the excitation inputs corresponding to these states are taken as don't care and hence these states are not included in state diagram as well as in excitation table.

Excitation table for MOD-10 counter

Present state				Next state				Required excitations							
$Q_3$	$Q_2$	$Q_1$	$Q_0$	$Q_3$	$Q_2$	$Q_1$	$Q_0$	$J_3$	$K_3$	$J_2$	$K_2$	$J_1$	$K_1$	$J_0$	$K_0$
0	0	0	0	0	0	0	1	0	X	0	X	0	X	1	X
0	0	0	1	0	0	1	0	0	X	0	X	1	X	X	1
0	0	1	0	0	0	1	1	0	X	0	X	X	0	1	X
0	0	1	1	0	1	0	0	0	X	1	X	X	1	X	1
0	1	0	0	1	0	0	1	0	X	X	0	0	X	1	X
0	1	0	1	0	1	1	0	0	X	X	0	1	X	X	1
0	1	1	0	0	1	1	1	0	X	X	0	X	0	1	X
0	1	1	1	1	0	0	0	1	X	X	1	X	1	X	1
1	0	0	0	1	0	0	1	X	0	0	X	0	X	1	X
1	0	0	1	0	0	0	0	X	1	0	X	0	X	X	1
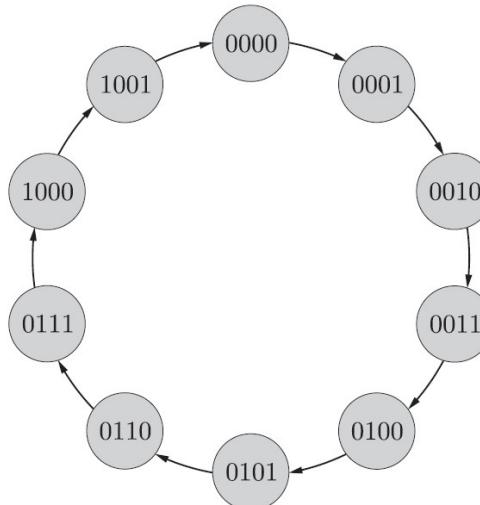
### Step 4: Minimal Expression for Flip-flop Inputs

The K-maps for excitations of flip-flops  $J_3$ ,  $K_3$ ,  $J_2$ ,  $K_2$ ,  $J_1$ ,  $K_1$ ,  $J_0$  and  $K_0$  in terms of the present state of flip-flops  $Q_3$ ,  $Q_2$ ,  $Q_1$  and  $Q_0$  can be drawn as shown below.



State diagram of synchronous MOD-10 (BCD) counter

		$Q_3 Q_2$	$Q_1 Q_0$	00	01	11	10
		$Q_3 Q_2$	$Q_1 Q_0$	00	01	11	10
00	00	0	0	X	X		
01	01	0	0	X	X		
11	11	0	1	X	X		
10	10	0	0	X	X		

$$J_3 = Q_2 Q_1 Q_0$$

		$Q_3 Q_2$	$Q_1 Q_0$	00	01	11	10
		$Q_3 Q_2$	$Q_1 Q_0$	00	01	11	10
00	00	X	X	X	X		0
01	01	X	X	X	X	1	
11	11	X	X	X	X	X	
10	10	X	X	X	X	X	

$$K_3 = Q_0$$

		$Q_3 Q_2$	$Q_1 Q_0$	00	01	11	10
		$Q_3 Q_2$	$Q_1 Q_0$	00	01	11	10
00	00	0	X	X	0		
01	01	0	X	X	0		
11	11	1	X	X	X	X	
10	10	0	X	X	X	X	

$$J_2 = Q_1 Q_0$$

		$Q_3 Q_2$	$Q_1 Q_0$	00	01	11	10
		$Q_3 Q_2$	$Q_1 Q_0$	00	01	11	10
00	X	0	X	X			
01	X	0	X	X			
11	X	1	X	X			
10	X	0	X	X			

$$K_2 = Q_1 Q_0$$

		$Q_3 Q_2$	$Q_1 Q_0$	00	01	11	10
		$Q_3 Q_2$	$Q_1 Q_0$	00	01	11	10
00	X	X	X	X			
01	X	X	X	X			
11	1	1	X	X			
10	0	0	X	X			

$$K_1 = Q_0$$

		$Q_3 Q_2$	$Q_1 Q_0$	00	01	11	10
		$Q_3 Q_2$	$Q_1 Q_0$	00	01	11	10
00	0	0	X	0			
01	1	1	X	0			
11	X	X	X	X			
10	X	X	X	X			

$$J_1 = \bar{Q}_3 Q_0$$

**Step 5: Logic Diagram:** Using the above minimized expressions, the logic diagram for the MOD-3 counter can be drawn as shown in Figure.

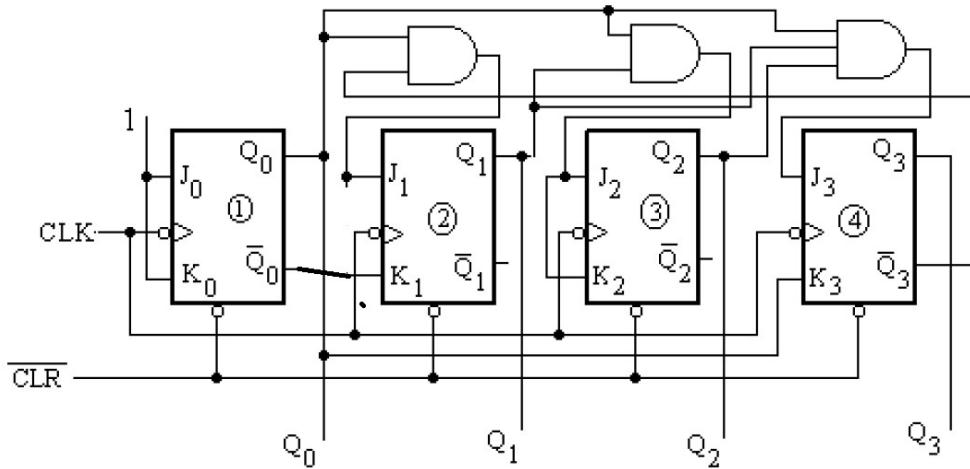


Figure.3.48

### Synchronous BCD Counter using T FF:

A BCD counter counts in binary-coded decimal from 0000 to 1001 and back to 0000. Because of the return to 0 after a count of 9, a BCD counter does not have a regular pattern, unlike a straight binary count. The state table of a BCD counter is listed in Table. The input conditions for the T flip-flops are obtained from the present- and next-state conditions. Also shown in the table is an output  $y$ , which is equal to 1 when the present state is 1001. In this way,  $y$  can enable the count of the next-higher significant decade while the same pulse switches the present decade from 1001 to 0000.

The flip-flop input equations can be simplified by means of maps. The unused states for minterms 10 to 15 are taken as don't-care terms. The simplified functions are


$$\begin{aligned} TQ1 &= 1; & TQ2 &= Q8Q1; & TQ4 &= Q2Q1 \\ TQ8 &= Q8Q1 + Q4Q2Q1; & y &= Q8Q1 \end{aligned}$$

Present State				Next State				Output	Flip-Flop Inputs			
$Q_8$	$Q_4$	$Q_2$	$Q_1$	$Q_8$	$Q_4$	$Q_2$	$Q_1$	$y$	$TQ_8$	$TQ_4$	$TQ_2$	$TQ_1$
0	0	0	0	0	0	0	1	0	0	0	0	1
0	0	0	1	0	0	1	0	0	0	0	1	1
0	0	1	0	0	0	1	1	0	0	0	0	1
0	0	1	1	0	1	0	0	0	0	1	1	1
0	1	0	0	0	1	0	1	0	0	0	0	1
0	1	0	1	0	1	1	0	0	0	0	1	1
0	1	1	0	0	1	1	1	0	0	0	0	1
0	1	1	1	0	0	0	0	0	1	1	1	1
1	0	0	0	1	0	0	1	0	0	0	0	1
1	0	0	1	0	0	0	0	1	1	0	0	1

### Binary Counter with Parallel Load:


Counters employed in digital systems quite often require a parallel-load capability for transferring an initial binary number into the counter prior to the count operation. Figure 6.14 shows the top-level block diagram symbol and the logic diagram of a four-bit register that has a parallel load capability and can operate as a counter. When equal to 1, the input load control disables the count operation and causes a transfer of data from the four data inputs into the four flip-flops. If both control inputs are 0, clock pulses do not change the state of the register.

Clear	CLK	Load	Count	Function
0	X	X	X	Clear to 0
1	↑	1	X	Load inputs
1	↑	0	1	Count next binary state
1	↑	0	0	No change

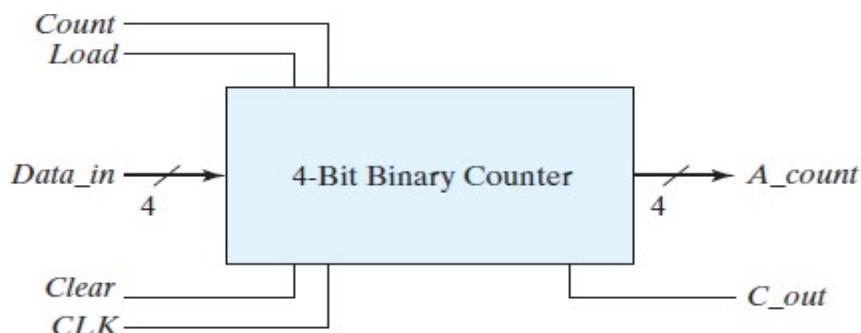



### **Ring Counters:**

Ring counters are implemented using shift registers. It is essentially a circulating shift register connected so that the last flip-flop shifts its value into the first flip-flop. There is usually only a single 1 circulating in the register, as long as clock pulses are applied.

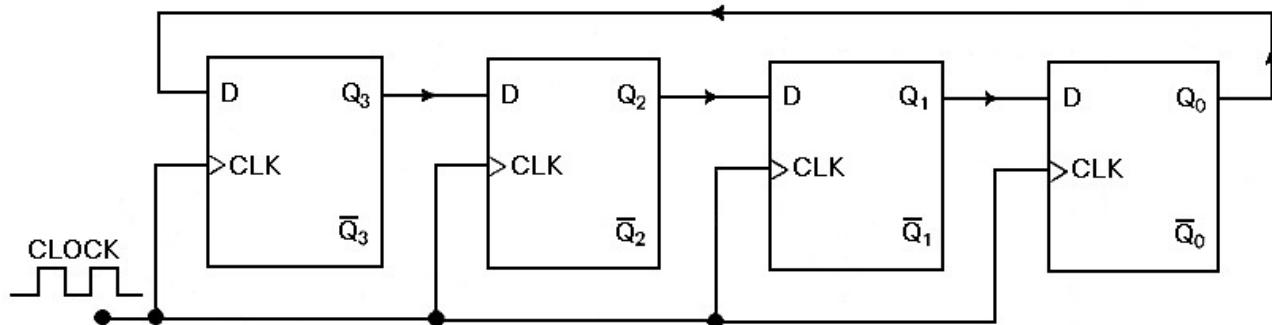

**Figure 3.49 :4-bit Synchronous Ring Counter**

Clock Pulse	$Q_0$	$Q_1$	$Q_2$	$Q_3$
0	1	0	0	0
1	0	1	0	0
2	0	0	1	0
3	0	0	0	1
4	1	0	0	0
5	0	1	0	0
6	0	0	1	0
7	0	0	0	1

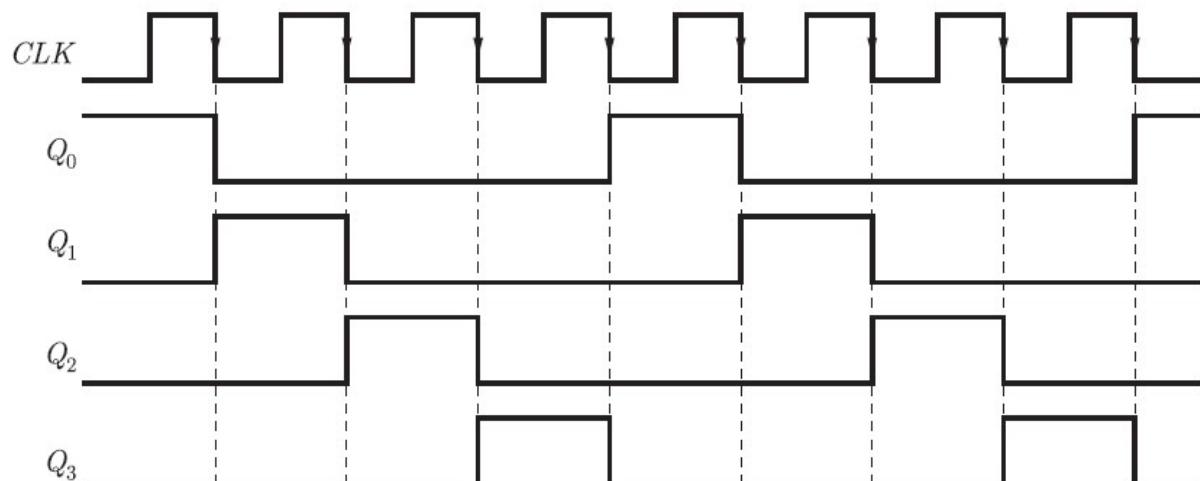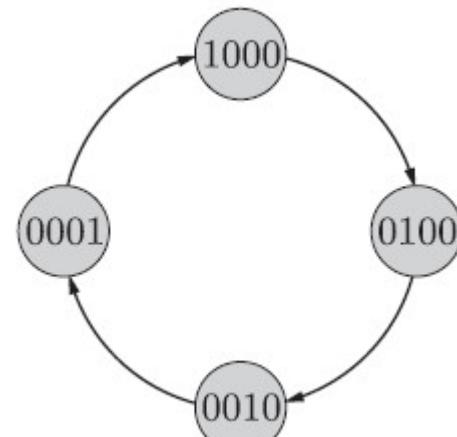

Let us assume that flip-flop FF0 is initially set to a '1' and all other flip-flops are reset to '0'. The counter output is therefore 1000. With the first clock pulse, this '1' gets shifted to the second flip-flop output and the counter output becomes 0100. Similarly, with the second and third clock pulses, the counter output will become 0010 and 0001. With the fourth clock pulse, the counter output will again become 1000. The sequence repeats after four clock pulses. From the above discussion we note the following point.


The ring counter above functions as a MOD-4 counter since it has four distinct states and each flip-flop output waveform has a frequency equal to one-fourth of the clock frequency. A ring counter can be constructed for any MOD number. A MOD-N ring counter will require N flip-flops connected in the arrangement as the diagram above.

A ring counter requires more flip-flops than a binary counter for the same MOD number. For example, a MOD-8 ring counter requires 8 flip-flops while a MOD-8 binary counter only requires 3 ( $2^3 = 8$ ).

### ***Johnson/Twisted-Ring Counters:***

The Johnson counter, also known as the twisted-ring counter, is exactly the same as the ring counter except that the inverted output of the last flip-flop is connected to the input of the first flip-flop.


The Johnson counter on the other hand is constructed by providing feedback from the inverted output of the last flip-flop to the  $D$  input of the first flip-flop. The  $Q$  output of each stage is connected to the  $D$  input of the next stage, but the  $Q$  output of the last stage is connected to the  $D$  input of first stage, therefore, the name twisted ring counter. This type of feedback produces a unique sequence of states. Figure 8.13.4 shows the logic diagram of a basic four-bit Johnson counter using  $D$  flip-flops.

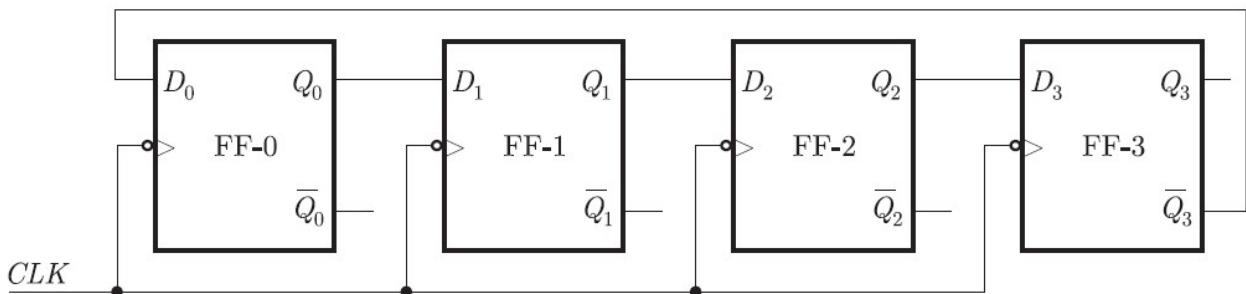

**Figure 3.50 :4-bit Synchronous Johnson Counter**

Clock Pulse	$Q_0$	$Q_1$	$Q_2$	$Q_3$
0	0	0	0	0
1	1	0	0	0
2	1	1	0	0
3	1	1	1	0
4	1	1	1	1
5	0	1	1	1
6	0	0	1	1
7	0	0	0	1
8	0	0	0	0
9	1	0	0	0

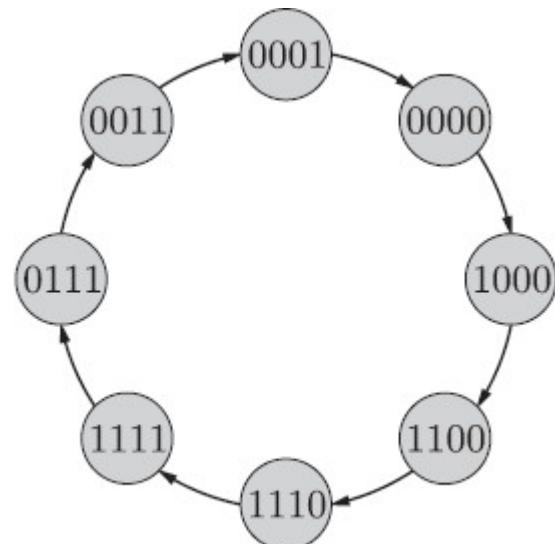**Count Sequence of a 4-bit Johnson Counter**



**State diagram of Johnson counter**

The MOD number of a Johnson counter is twice the number of flip-flops. In the example above, three flip-flops were used to create the MOD-6 Johnson counter. So for a given MOD number, a Johnson counter requires only half the number of flip-flops needed for a ring counter. However, a Johnson counter requires decoding gates whereas a ring counter doesn't. As with the binary counter, one logic gate (AND gate) is required to decode each state, but with the Johnson counter, each gate requires only two inputs, regardless of the number of flip-flops in the counter. Note that we are comparing with the binary counter using the speed up technique discussed above. The reason for this is that for each state, two of the N flip-flops used will be in a unique combination of states. In the example above, the combination  $Q_2 = Q_1 = 0$  occurs only once in the counting sequence, at the count of 0. The state 010 does not occur. Thus, an AND gate with inputs (not  $Q_2$ ) and (not  $Q_2$ ) can be used to decode for this state. The same characteristic is shared by all the other states in the sequence.

A Johnson counters represent a middle ground between ring counters and binary counters. A Johnson counter requires fewer flip-flops than a ring counter but generally more than a binary counter; it has more decoding circuitry than a ring counter but less than a binary counter. Thus, it sometimes represents a logical choice for certain applications.

**Example :** Design a synchronous Mod-10 counter to count in the sequence 0, 2, 4, 5, 6, 8, 9, 3, 1, 7, 0. Use J K flip-flops to design the counter.

**Solution:** For the design of this decade counter, four J K flip-flops are required. The state diagram showing the required states in the counter in sequence wise is given in figure.

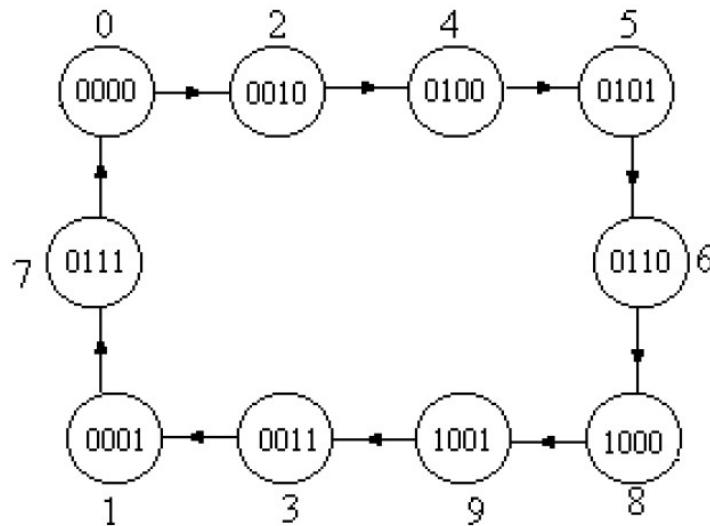


Table shows present states of the counting sequence and next states after the clock pulse and input values of the flip-flops.

The K-maps for all inputs of the flip-flops are drawn as shown in figures through (g) and the expressions for these inputs are given as:

Present States				Next States											
$Q_3$	$Q_2$	$Q_1$	$Q_0$	$Q_3$	$Q_2$	$Q_1$	$Q_0$	$J_3$	$K_3$	$J_2$	$K_2$	$J_1$	$K_1$	$J_0$	$K_0$
0	0	0	0	0	0	1	0	0	$\varphi$	0	$\varphi$	1	$\varphi$	0	$\varphi$
0	0	0	1	0	1	1	1	0	$\varphi$	1	$\varphi$	1	$\varphi$	0	0
0	0	1	0	0	1	0	0	0	$\varphi$	1	$\varphi$	$\varphi$	1	0	$\varphi$
0	0	1	1	0	0	0	1	0	$\varphi$	0	$\varphi$	$\varphi$	1	$\varphi$	0
0	1	0	0	0	1	0	1	0	$\varphi$	$\varphi$	0	0	$\varphi$	1	$\varphi$
0	1	0	1	0	1	1	0	0	$\varphi$	$\varphi$	0	1	$\varphi$	1	1
0	1	1	0	1	0	0	0	1	$\varphi$	$\varphi$	1	$\varphi$	1	0	$\varphi$
0	1	1	1	0	0	0	0	0	$\varphi$	$\varphi$	1	$\varphi$	1	$\varphi$	1
1	0	0	0	1	0	0	1	$\varphi$	0	0	$\varphi$	0	$\varphi$	1	$\varphi$
1	0	0	1	0	0	1	1	$\varphi$	1	0	$\varphi$	1	$\varphi$	$\varphi$	0

$Q_3 Q_2$	00	01	11	10
$Q_1 Q_0$	00	0	$\varphi$	$\varphi$
00	0	0	$\varphi$	$\varphi$
01	0	0	$\varphi$	$\varphi$
11	0	0	$\varphi$	$\varphi$
10	0	(1) $\varphi$	$\varphi$	$\varphi$

$$J_3 = Q_2 \cdot Q_1 \cdot \bar{Q}_0$$

$Q_3 Q_2$	00	01	11	10
$Q_1 Q_0$	00	$\varphi$	$\varphi$	0
00	$\varphi$	$\varphi$	$\varphi$	1
01	$\varphi$	$\varphi$	$\varphi$	1
11	$\varphi$	$\varphi$	$\varphi$	1
10	$\varphi$	$\varphi$	$\varphi$	$\varphi$

$$K_3 = Q_0$$

$Q_3 Q_2$	00	01	11	10
$Q_1 Q_0$	00	0	$\varphi$	$\varphi$
00	0	$\varphi$	$\varphi$	0
01	1	$\varphi$	$\varphi$	0
11	0	$\varphi$	$\varphi$	$\varphi$
10	1	$\varphi$	$\varphi$	$\varphi$

$$J_2 = Q_1 \cdot \bar{Q}_0 + \bar{Q}_3 \cdot \bar{Q}_1 \cdot Q_0$$

$Q_3 Q_2$	00	01	11	10
$Q_1 Q_0$	00	$\varphi$	0	$\varphi$
00	$\varphi$	0	$\varphi$	$\varphi$
01	1	$\varphi$	$\varphi$	0
11	0	1	$\varphi$	$\varphi$
10	$\varphi$	$\varphi$	$\varphi$	$\varphi$

$$K_2 = Q_1$$

$Q_3 Q_2$	00	01	11	10
$Q_1 Q_0$	00	1	0	$\varphi$
00	1	0	$\varphi$	0
01	1	1	$\varphi$	1
11	$\varphi$	$\varphi$	$\varphi$	$\varphi$
10	$\varphi$	$\varphi$	$\varphi$	$\varphi$

$$J_1 = \bar{Q}_3 \cdot \bar{Q}_2 + Q_0$$

$Q_3 Q_2$	00	01	11	10
$Q_1 Q_0$	00	0	1	$\varphi$
00	0	1	$\varphi$	1
01	$\varphi$	0	$\varphi$	$\varphi$
11	$\varphi$	$\varphi$	$\varphi$	$\varphi$
10	0	0	$\varphi$	$\varphi$

$$J_0 = Q_2 \cdot \bar{Q}_1 + Q_3$$


$Q_3 Q_2$	00	01	11	10
$Q_1 Q_0$	00	$\varphi$	$\varphi$	$\varphi$
00	$\varphi$	$\varphi$	$\varphi$	$\varphi$
01	0	1	$\varphi$	0
11	0	1	$\varphi$	$\varphi$
10	$\varphi$	$\varphi$	$\varphi$	$\varphi$

$$K_0 = Q_2 \cdot Q_0$$

$$J_3 = Q_2 \cdot Q_1 \cdot \bar{Q}_0$$

$$J_1 = \bar{Q}_3 \cdot \bar{Q}_2 + Q_0, K_3 = Q_0, K_1 = 1 \text{ (directly from the table)}$$
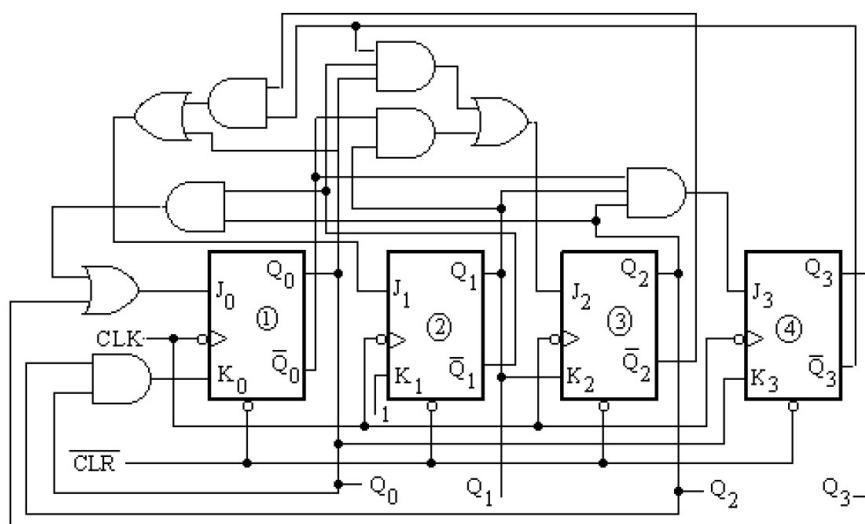
$$J_2 = Q_1 \cdot \bar{Q}_0 + \bar{Q}_3 \cdot \bar{Q}_1 \cdot Q_0, J_0 = Q_2 \cdot \bar{Q}_1 + Q_3, K_2 = Q_1, K_0 = Q_2 \cdot Q_0$$



The logic circuit diagram of this synchronous counter, whose outputs will be in the given sequence, is shown in figure.

## SUPPLEMENT READING

### What makes propagation delay?

**[Ans]** All *real* devices have some delay associated with transferring an input change to the output. Although a *ideal* gate doesn't have such a delay, any implementation in the real world takes time to do its job. This delay that is due to the signal propagation through the device is called the *propagation delay*.

### What is Setup time?


**[Ans]** Setup time is a timing parameter associated with Sequential Devices (for simplicity henceforth I will be only referring to the Flip Flop). The Setup time is used to meet the minimum pulse width requirement for the first (Master) latch makes up a flip flop is. More simply, the *setup time* is the amount of time that an input signal (to the device) must be stable (unchanging) before the clock ticks in order to guarantee minimum pulse width and thus avoid possible metastability---

### What is Hold time?

**[Ans]** Hold time is also a timing parameter associated with Flip Flops and all other sequential devices. The Hold time is used to further satisfy the minimum pulse width requirement for the first (Master) latch that makes up a flip flop. The input must not change until enough time has passed after the clock tick to guarantee the master latch is fully disabled. More simply, *hold time* is the amount of time that an input signal (to a sequential device) must be stable (unchanging) after the clock tick in order to guarantee minimum pulse width and thus avoid possible metastability.

### What do Setup and Hold time look like on a timing diagram?

**[Ans]** Observe the waveform below:

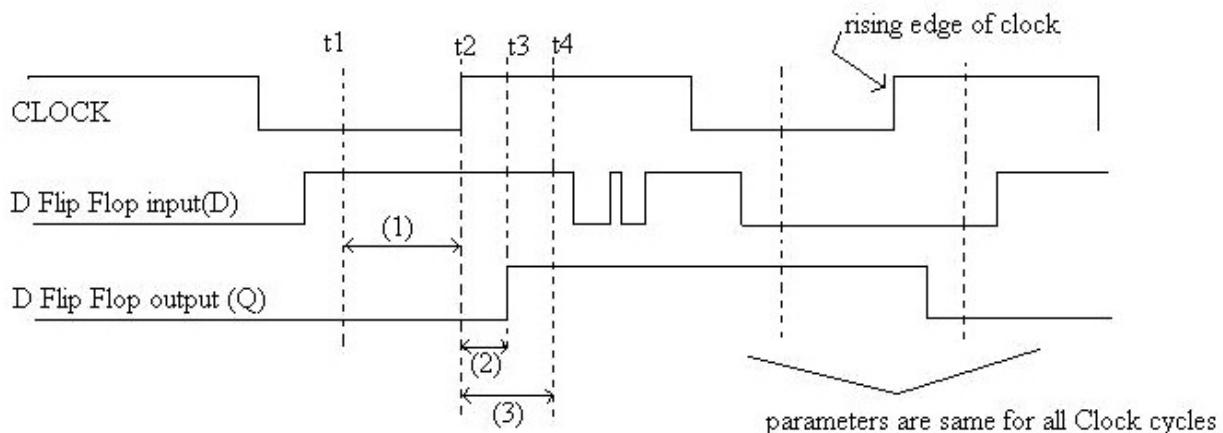

The timing diagram above illustrates three signals: the Clock, the Flip Flop Input (D) and the Flip Flop output (Q).

(1) is the Setup Time [t2 - t1]: the minimum amount of time Input must be held constant BEFORE the clock tick. Note that D is actually held constant for somewhat longer than the minimum amount. The extra "constant" time is sometimes called the setup margin.

(2) is the Propagation delay of the Flip Flop [t3 - t2]: this is the time that it takes for the new input to be to propagate and influence the output.

(3) is the Hold time [t4 - t2]: the minimum amount of time the Input is held constant AFTER the clock tick. Note that Q is actually held constant for somewhat longer than the minimum amount. The extra "constant" time is sometimes called the hold margin.

(The above timing diagram has 2 clock cycles; the timing parameters for the second cycle will also be similar to that of the first cycle).