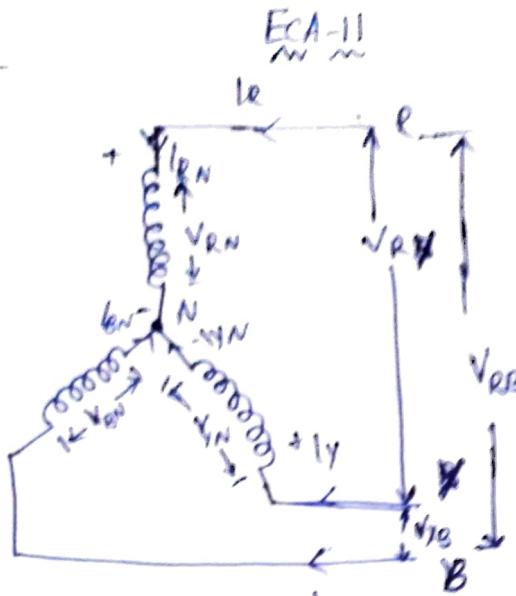


Star Connection:-



where,

V_{RN}, V_{YN}, V_{BN} are the phase voltages

I_{RN}, I_{YN}, I_{BN} are the phase currents

V_{RY}, V_{RR}, V_{RB} are the line voltages

I_R, I_Y, I_B are the line currents

$$|I_{RN}| = |I_{YN}| = |I_{BN}| = I_{ph}$$

$$|V_{RN}| = |V_{YN}| = |V_{BN}| = V_{ph}$$

$$V_{RN} = V_{ph} \sin 0^\circ = V_{ph}$$

$$V_{YN} = V_{ph} \sin(120^\circ) = V_{ph}$$

$$V_{BN} = V_{ph} \sin(240^\circ) = V_{ph} \angle -120^\circ$$

Applying KVL for $(Y-Y-N-R-R)$.

$$V_{YN} - V_{RN} + V_{RY} = 0$$

$$V_{RY} = V_{RN} - V_{YN}$$

* In Star connection the line current is equal to the phase current.

$$I_L = I_{ph}$$

Similarly:

$$V_{RB} = V_{YN} - V_{BN}$$

$$V_{RR} = V_{BN} - V_{RN}$$

Consider,

$$V_{RY} = V_{RN} - V_{YN} \\ = V_{ph} - V_{ph} \angle -120^\circ \quad [V_{ph} \angle (\cos 0 + j \sin 0)]$$

$$= (\cos 0 + j \sin 0) - \sqrt{3} [\cos(-120) + j \sin(-120)]$$

$$= \sqrt{3} \left[\frac{1}{2} - j \frac{\sqrt{3}}{2} \right]$$

$$= \sqrt{3} \left[\frac{1}{2} + j \frac{\sqrt{3}}{2} \right]$$

$$= \sqrt{3} \left[\frac{3}{2} + j \frac{\sqrt{3}}{2} \right]$$


$$= V_{ph} 1.732 \angle 30^\circ$$

$$\boxed{V_L = \sqrt{3} V_{ph} \angle 30^\circ}$$

From the above equation we can conclude that, for a star connected balanced system, the line voltage is $\sqrt{3}$ times of the phase voltage and the line voltage leads the phase voltage by 30°

$$V_{RN} = V_{AN} - V_{EN}$$

$$V_{RN} = \sqrt{3} V_{ph}$$

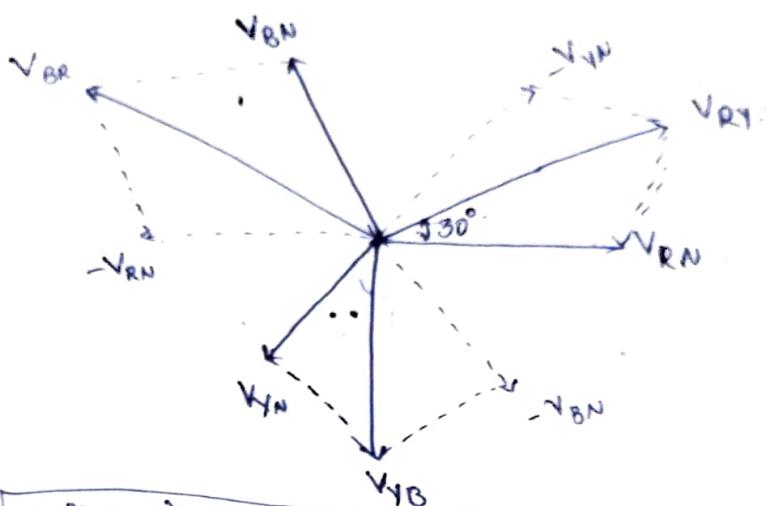


$$|V_L| = \sqrt{V_{RN}^2 + V_{AN}^2 + 2V_{RN}V_{AN} \cos 60^\circ} = \sqrt{V_{ph}^2 + V_{ph}^2 + 2V_{ph}^2 \cos 60^\circ} = \sqrt{2V_{ph}^2 + 2V_{ph}^2 \cos 60^\circ} = \sqrt{2V_{ph}^2 + V_{ph}^2} = \sqrt{3} V_{ph}$$

$$V_{RY} = \sqrt{3} V_{ph} \angle 30^\circ ; \quad V_{YB} = \sqrt{3} V_{ph} \angle -120^\circ + 30^\circ ; \quad V_{BR} = \sqrt{3} V_{ph} \angle 120^\circ + 30^\circ$$

$$= \sqrt{3} V_{ph} \angle -90^\circ$$

$$= \sqrt{3} V_{ph} \angle 120^\circ$$

3-phase delta connected system :-

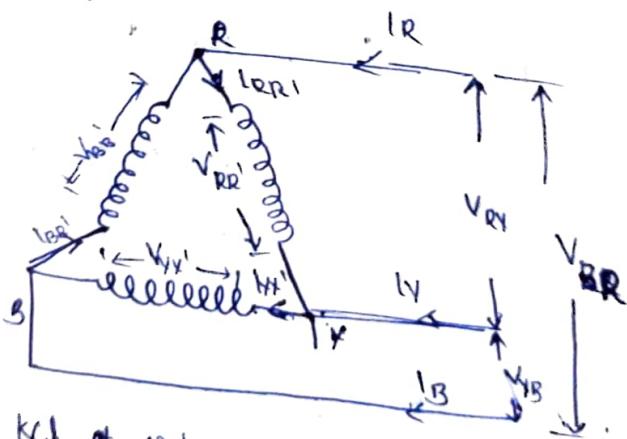

Applying KCL at Node R :-

$$I_R + I_{BB'} = I_{RR'}$$

$$I_R = I_{RR'} - I_{BB'} \quad \text{--- (2)}$$

$$I_Y = I_{YY'} - I_{RR'} \quad \text{--- (3)}$$

$$I_B = I_{BB'} - I_{YY'} \quad \text{--- (4)}$$

From the diagram we can conclude that, $V_L = V_{ph}$ because they are in parallel connection. Here,

$V_{YY'}, V_{YY}, V_{BB'}$ are the phase voltages

V_{RY}, V_{YB}, V_{BR} are the line voltages

$I_{YY'}, I_{YY}, I_{BB'}$ are the phase currents


I_R, I_Y, I_B are the line currents

$$I_{RR'} = I_{ph} \sin \omega t = I_{ph} \angle 0^\circ$$

$$I_{YY'} = I_{ph} \sin(\omega t - 120^\circ) = I_{ph} \angle -120^\circ$$

$$I_{BB'} = I_{ph} \sin(\omega t + 120^\circ) = I_{ph} \angle 120^\circ$$

Phase diagram:-

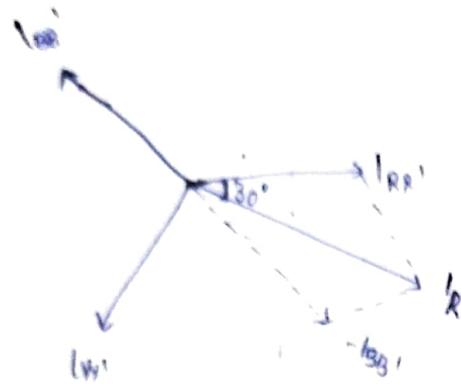

From the phase diagram we can say,

that, the line currents lag phase current by 30°.

$$I_R = I_{ph} \angle -30^\circ.$$

$$I_L = \sqrt{(I_{R\phi})^2 + (I_{B\phi})^2 + 2 I_{R\phi} I_{B\phi} \cos 60^\circ}$$

$$= \sqrt{2 I_{ph}^2 + I_{ph}^2 \frac{1}{2}}$$

$$= \sqrt{3} I_{ph}$$

$$\therefore I_L = \sqrt{3} I_{ph}$$

$$\therefore I_R = I_{ph} \angle -30^\circ$$

$$I_Y = I_{ph} \angle -120^\circ$$

$$= I_{ph} \angle -150^\circ$$

$$I_B = \sqrt{3} I_{ph} \angle 120^\circ$$

$$= \sqrt{3} I_{ph} \angle 90^\circ.$$

In a 3-p delta connected balanced system the line current is equal to $\sqrt{3}$ times of the phase current and the line current lags the phase current by 30°.

Power in 3-p star connected system:-

In a 3-p system the active power (or) the true power is equal to the sum of the power of all the individual phases.

$$\text{Active power, } P = 3 \times (\text{power in each phase}) = 3 \times V_{ph} I_{ph} \cos \phi.$$

$$\text{In star connection, } V_{ph} = \frac{V_L}{\sqrt{3}} \Rightarrow P = 3 \times \frac{V_L}{\sqrt{3}} \times I_L \cos \phi$$

$$I_L = I_{ph} = \sqrt{3} V_L I_L \cos \phi, \text{ w.}$$

Reactive power, $\text{Q} = \sqrt{3} V_L I_L \sin \phi \text{ VAR.}$

Apparent power, $S = \sqrt{3} V_L I_L \text{ VA.}$

Power in 3-p delta connected system:-

$$\text{Active power, } P = 3 \times (\text{power in each phase}) = 3 \times V_{ph} I_{ph} \cos \phi.$$

Reactive power, $\text{Q} = \sqrt{3} V_L I_L \sin \phi \text{ VAR.}$

$$\text{Apparent power, } S = \sqrt{3} V_L I_L \text{ VA.}$$

$$\Rightarrow \text{In delta, } V_{ph} = V_L, I_{ph} = \frac{I_L}{\sqrt{3}}, P = 3 \times V_L \times \frac{I_L}{\sqrt{3}} \times \cos \phi \Rightarrow P = \sqrt{3} V_L I_L \cos \phi \text{ w.}$$

Given, delta connected.

Z_{ph} for all 3 phases are equal
result of balanced load
in delta.

$$V_L = V_{ph} = 440V$$

$$I_{ph} = \frac{V_{ph} \angle 0^\circ}{Z_{ph}} = \frac{440}{(3+j15)} = 28.76 \angle -78.69^\circ$$

$$\text{Also } I_{ph(A)} = \frac{V_{ph} \angle 120^\circ}{(3+j15)} = 28.76 \angle -78.69 - 120^\circ \\ = 28.76 \angle -198.69^\circ$$

$$I_{ph(B)} = \frac{V_{ph} \angle 120^\circ}{(3+j15)} = 28.76 \angle -78.69 + 120^\circ \\ = 28.76 \angle 41.31^\circ$$

Line currents :-

$$I_L = \sqrt{3} I_{ph} \angle 30^\circ$$

$$I_R = \sqrt{3} 28.76 \angle -78.69 - 30^\circ$$

$$= 49.81 \angle -108.69 A$$

$$\text{Sum of } I_R \text{ and } I_B = 49.81 \angle -78.69 - 150^\circ$$

$$= 49.81 \angle 228.69 A$$

$$I_A = 49.81 \angle -78.69 + 90^\circ$$

$$= 49.81 \angle 11.31 A$$


$$\text{Total Active Power} = \sqrt{3} V_L I_L \cos \phi$$

$$= \sqrt{3} \times 440 \times 49.81 \cos(78.69)$$

$$P = 7444.63 W$$

$\sqrt{3} V_L I_L$

+ phase diagram: $I_{RR'}$

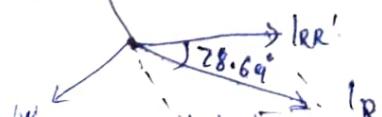

2(b) Given data: Δ -connection

$$L = 0.5H, C = 2\mu F, R = 50 \Omega$$

$$V_L = V_{ph} = 230V$$

$$2\pi f = 500$$


$$f = \frac{500}{2\pi} = 79.63 Hz$$

$$f = 63.66 Hz$$

$$Z_{eq} = Z_L + Z_{C/R}$$

$$Z_L = 2\pi f L = 2\pi f L = 400 \times 0.5 = j200 \Omega$$
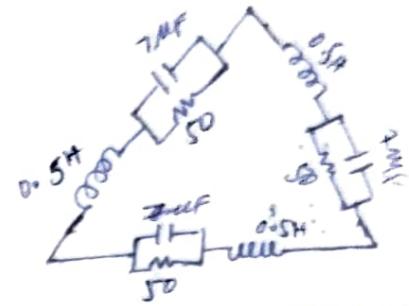
$$Z_{C/R} = \frac{R(j\omega C)}{R+j\omega C} = \frac{50(357.14)j}{50+(357.14)j} = \frac{1787.14}{360.62} \angle 92.88^\circ$$



$$Z_{C/R} = 19.51 \angle -7.96^\circ$$

$$= 19.03 - j6.85$$

$$\therefore Z_{eq} = j200 + 19.03 - j6.85 \\ = 19.03 + 193.95 j$$

$$= 199.27 \angle 75.75^\circ$$

Phase currents :-

$$I_{RR'} = \frac{V_{ph} \angle 0^\circ}{Z_{ph}} = \frac{230 \angle 0^\circ}{199.27 \angle 75.75} = 1.19 \angle -75.75^\circ$$

$$I_{YY'} = \frac{V_{ph} \angle 120^\circ}{Z_{ph}} = \frac{230 \angle 120^\circ}{199.27 \angle 75.75} = 1.19 \angle -195.75^\circ$$

$$I_{BB'} = \frac{V_{ph} \angle 120^\circ}{Z_{ph}} = \frac{230 \angle 120^\circ}{199.27 \angle 75.75} = 1.19 \angle 44.25^\circ$$

Line currents :-

$$I_R = I_{RR'} \angle -30^\circ = \sqrt{3} \times 1.19 \angle -195.75 - 30^\circ \\ = 2.06 \angle -105.75^\circ$$

$$I_Y = \sqrt{3} I_{YY'} \angle -30^\circ = \sqrt{3} \times 1.19 \angle -195.75 - 30^\circ \\ = 2.06 \angle 225.75^\circ$$

$$I_B = \sqrt{3} I_{BB'} \angle -30^\circ = \sqrt{3} \times 1.19 \angle 44.25 - 30^\circ \\ = 2.06 \angle 144.25^\circ$$

$$\text{Active power} = \sqrt{3} V_L I_L \cos \phi$$

$$= \sqrt{3} \times 230 \times 2.06 \times \cos(75.75) = 202 W$$

SW Pdelta = 0.8 Pstar

Q(b)

$$8(b) \quad (20-j15) = Z \quad \left. \begin{array}{l} \Delta\text{-connection} \\ I_b = \sqrt{3} I_{ph} \\ V_{ph} = 330 \angle 0^\circ \end{array} \right.$$

$I_{ph} = ? \quad I_b = ?$

$$\therefore V_b = V_{ph} = 330$$

Phase currents:-

$$I_{ph}(R) = \frac{V_{ph}}{Z_{ph}} = \frac{330 \angle 0^\circ}{20-j15}$$

$$I_{ph}^1 = 13.2 \angle 36.86^\circ$$

$$I_{ph}^1 = \frac{V_{ph} \angle 0^\circ}{Z_{ph}} = \frac{330 \angle 0^\circ}{(20-j15)}$$

$$= 13.2 \angle -83.13^\circ$$

$$I_{ph}^2 = \frac{V_{ph} \angle 120^\circ}{Z_{ph}} = \frac{330 \angle 120^\circ}{(20-j15)}$$

$$= 13.2 \angle 156.86^\circ$$

Phase currents:-

$$I_R = \sqrt{3} |I_{ph}| \angle -30^\circ$$

$$= \sqrt{3} \times 13.2 \angle 36.86 - 30^\circ$$

$$= 22.86 \angle 6.86^\circ$$

$$I_Y = \sqrt{3} |I_{ph}| \angle -120^\circ$$

$$= \sqrt{3} \times 13.2 \angle 36.86 - 120^\circ$$

$$= 22.86 \angle 113.14^\circ$$

$$I_B = \sqrt{3} |I_{ph}| \angle 90^\circ$$

$$= \sqrt{3} \times 13.2 \angle 36.86 + 90^\circ$$

$$= 22.86 \angle 126.86^\circ$$

(ii) Given data:-

$$L = 0.8 \text{ H}$$

$$C = 6 \mu\text{F}, R = 90 \Omega$$

$$V_b = V_{ph} = 1100 \text{ V}$$

$$f = 50 \text{ Hz}$$

$$Z_{eq} = Z_L + Z_{CHR}$$

$$= \frac{1}{R + jX_L}$$

$$= \frac{1}{90 + j50 \times 0.8}$$

$$= 562.83 \Omega$$

$$Z_{CHR} = \frac{R+jX_C}{R+X_C} = \frac{90 \times 530.51 \text{ J}}{90 + 530.51 \text{ J}}$$

$$= \frac{47746.48 \angle 90^\circ}{538.09 \angle 99.62^\circ}$$

$$= 88.73 \angle -9.62^\circ$$

$$= 87.48 \angle 14.82^\circ$$

$$Z_{eq} = j62.83 + 87.48 - j14.82$$

$$= 87.48 + j48.01$$

$$= 99.78 \angle 28.75^\circ$$

Phase currents:-

$$I_{ph}(RR) = \frac{V_{ph} \angle 0^\circ}{Z_{ph}} = \frac{1100 \angle 0^\circ}{99.78 \angle 28.75} = 4 \angle -28.75^\circ$$

$$I_{ph}^1 = \frac{V_{ph} \angle 0^\circ}{Z_{ph}} = \frac{1100 \angle 0^\circ}{99.78 \angle 28.75} = 4 \angle 14.82^\circ$$

$$I_{ph}^2 = \frac{V_{ph} \angle 120^\circ}{Z_{ph}} = \frac{1100 \angle 120^\circ}{99.78 \angle 28.75} = 4 \angle 91.25^\circ$$

Line currents:-

$$I_R = \sqrt{3} |I_{ph}| \angle -30^\circ = \sqrt{3} \times 4 \angle -28.75 - 30^\circ$$

$$= 6.92 \angle -58.75^\circ$$

$$I_Y = \sqrt{3} |I_{ph}| \angle 30^\circ = \sqrt{3} \times 4 \angle 148.75 - 30^\circ = 6.92 \angle 118.75^\circ$$

$$I_B = \sqrt{3} |I_{ph}| \angle 90^\circ = \sqrt{3} \times 4 \angle 91.25 - 30^\circ = 6.92 \angle 61.25^\circ$$

Active power, $P = \sqrt{3} V_L I_L \cos \phi$

$$= \sqrt{3} \times 400 \times 6.92 \times \cos(28.75^\circ)$$

$$P = 4203.30 \text{ W}$$

Given data:-
 $Z = R + jX_C$
 $R = 10\Omega$, $X_C = 10\mu F$, $V_L = 115V$, $f = 50Hz$, $\phi = 24^\circ$.
 $I_L = \frac{V_L}{Z} = \frac{115}{(10 + j10)} = 11.5 \angle -45^\circ A$
 $P_{L\text{ active}} = V_L I_L \cos\phi = 115 \times 11.5 \cos(-45^\circ) = 692W$
 $P_{L\text{ reactive}} = V_L I_L \sin\phi = 115 \times 11.5 \sin(-45^\circ) = 692 \angle -90^\circ VAr$

In star connection, $V_L = \sqrt{3}V_{ph}$, $I_L = \sqrt{3}I_{ph}$, $P_L = \sqrt{3}P_{ph}$, $Q_L = \sqrt{3}Q_{ph}$.

Phase currents:
 $I_{ph} = \frac{V_{ph}}{Z} = \frac{115}{(10 + j10)} = 11.5 \angle -45^\circ A$
 $I_{ph} = \frac{I_L}{\sqrt{3}} = \frac{11.5}{\sqrt{3}} = 6.58 \angle -45^\circ A$
 $I_{ph} = \frac{V_{ph}}{R} = \frac{115}{10} = 11.5 A$

Line currents = phase currents.
 i. Real power, $P = \sqrt{3} V_L I_L \cos\phi$
 $= \sqrt{3} \times 115 \times 11.5 \cos(-45^\circ)$
 $P = 17228.35 W$

ii. Reactive power, $Q = \sqrt{3} V_L I_L \sin\phi$
 $= \sqrt{3} \times 115 \times 11.5 \sin(-45^\circ)$
 $Q = 5411.12 VAr$

Ques 7(a)
 Given data:-
 $V_L = V_{ph} = 220V$ (Δ -connection).
 $Z_{ph} = (15 + j20) \Omega$.
 Phase currents:-
 $I_{ph}(1RR') = \frac{V_{ph}}{Z_{ph}} = \frac{220}{(15 + j20)} = 8.8 \angle -53.13^\circ A$
 $I_{ph}(1YY') = \frac{V_{ph}}{Z_{ph}} = \frac{220 \angle -120^\circ}{15 + j20} = 8.8 \angle -123.13^\circ A$
 $I_{ph}(1BB') = \frac{V_{ph}}{Z_{ph}} = \frac{220 \angle 120^\circ}{15 + j20} = 8.8 \angle 66.87^\circ A$

ii) Power in each phase = $V_{ph} I_{ph} \cos\phi$
 $= 220 \times 8.8 \times \cos(53.13^\circ)$
 $P_{phaseph} = 1161.60 W.$

iii) Line currents:-
 $I_R = \sqrt{3} \times 8.8 \angle -53.13^\circ = 15.24 \angle -53.13^\circ A$
 $I_Y = 15.24 \angle -123.13^\circ A$, $I_B = 15.24 \angle 66.87^\circ A$

of line currents.

$$= I_R + I_Y + I_B$$

$$= 15.24 \angle -83.13^\circ + 15.24 \angle -203.13^\circ + 15.24 \angle -36.87^\circ$$

$$= 0$$

8(a)

Given data :-

$$Z_{ph} = (8+j6) \Omega$$

$$V_L = 230$$

$$\text{In star, } V_2 = \sqrt{3} V_{ph}$$

$$V_{ph} = \frac{V_L}{\sqrt{3}} = \frac{230}{\sqrt{3}}$$

$$V_{ph} = 132.79 \text{ V}$$

$$\text{a) } \Rightarrow I_{ph} = \frac{V_{ph}}{Z_{ph}} = \frac{132.79}{8+j6} \\ = 13.27 \angle -36.86^\circ$$

b) power consumed by load,

$$P_{in/ph} = V_{ph} I_{ph} \cos \phi \\ = 132.79 \times 13.27 \times \cos(36.86^\circ)$$

$$P_{ph} = 1409.88 \text{ W}$$

Total power ~~1409.88~~ 29.64 W.

c) Power factor of load :-

$$\cos \phi = \tan^{-1} \left(\frac{6}{8} \right)$$

$$\cos \phi = 36.86$$

$$\cos \phi = \cos(36.86^\circ)$$

$$\cos \phi = 0.8$$

d) Reactive power = $\sqrt{3} V_L I_L \sin \phi$

$$= \sqrt{3} \times 230 \times \frac{13.27 \times 0.6}{13.27}$$

$$Q = 3171.83 \text{ VAR}$$

9(b) $Z_{ph} = 20+j10 \Omega$
 $V_L = V_{ph} = 440V$

line phase currents :-

$$I_{Rph} = \frac{V_{ph}}{Z_{ph}} = \frac{440}{20+j10} = 19.67 \angle -26.58^\circ$$

$$(I_Y)' = 19.67 \angle -26.58 + 120^\circ = 19.67 \angle -146.58^\circ$$

$$(I_B)' = 19.67 \angle 120^\circ - 26.58^\circ = 19.67 \angle 93.44^\circ$$

Line currents :-

$$I_R = \sqrt{3} \times I_{ph} \angle 30^\circ$$

$$= \sqrt{3} \times 19.67 \angle -26.58 - 30^\circ$$

$$= 34.069 \angle -56.58^\circ$$

$$I_Y = \sqrt{3} \times I_{ph} \angle 150^\circ$$

$$= \sqrt{3} \times 19.67 \angle 26.58 - 150^\circ$$

$$= 34.069 \angle -176.58^\circ$$

$$I_B = \sqrt{3} \times I_{ph} \angle 90^\circ$$

$$= \sqrt{3} \times 19.67 \angle -26.58 + 90^\circ$$

$$= 34.069 \angle 63.44^\circ$$

Active power, P

$$= \sqrt{3} V_L I_L \cos \phi$$

$$= \sqrt{3} \times 440 \times 34.069 \times \cos(26.58^\circ)$$

$$P = 23223.98 \text{ W}$$

In X-connection:

$$\Rightarrow V_{ph} = \frac{V_L}{\sqrt{3}} = \frac{V}{\sqrt{3}}$$

$$\Rightarrow I_L = I_{ph} = \frac{V_{ph}}{R}$$

$$P_X = 3(I_{ph})^2 R$$

$$= 3 \times \left(\frac{V_{ph}}{R} \right)^2 R \cdot 3 \times \frac{V}{\sqrt{3}} \times \frac{V}{\sqrt{3}} \times \frac{1}{R} R$$

$$= 3 \times \frac{V^2}{3R^2} \cdot R$$

$$= \frac{V^2}{R}$$

$$P_X = \frac{V^2}{R} - \textcircled{1}$$

Δ-connection:

$$V_{RY} = V_L = V$$

$$I_L = I_{ph} = \frac{V_{RY}}{R} = \frac{V}{R}$$

$$P_\Delta = 3(I_{ph})^2 R$$

$$= 3 \left(\frac{V_{RY}}{R} \right)^2 R$$
$$= 3 \cdot \frac{V^2}{R^2} R$$

$$P_\Delta = \frac{3V^2}{R} - \textcircled{2}$$

from eq \textcircled{1} & \textcircled{2},

$$P_\Delta = 3 P_X$$

(ii) Advantages of Poly phase system over single phase system:

- More power can be transmitted by the polyphase transmission system using the same amount of conducting material.
- Polyphase motor has a more uniform torque than the single phase motors opp torque is pulsating in nature.
- In the case of Induction motor polyphase induction motors are self-starting and more efficient but 1-ph induction motor is not self-starting.
- The C.P. of 3-ph machine is always greater than the 1-ph machine of the same size.
- A polyphase transmission line requires less conductor material a 1-ph line for transmitting the amount of power at the same voltage.
- Per the unit of output, the polyphase machine is very much cheaper.

1(a)

Show that,



UNIT-II

$W_1 + W_2 = \text{Total power. by}$
 Using two watt-meter method.

$$V_{BR} = V_{BN} - V_{RN} \Rightarrow V_{RB}$$

$$V_{YB} = V_N - V_{BN}$$

Phase diagram:-

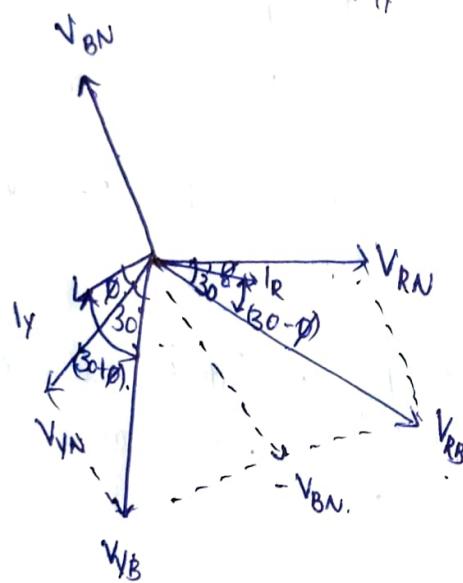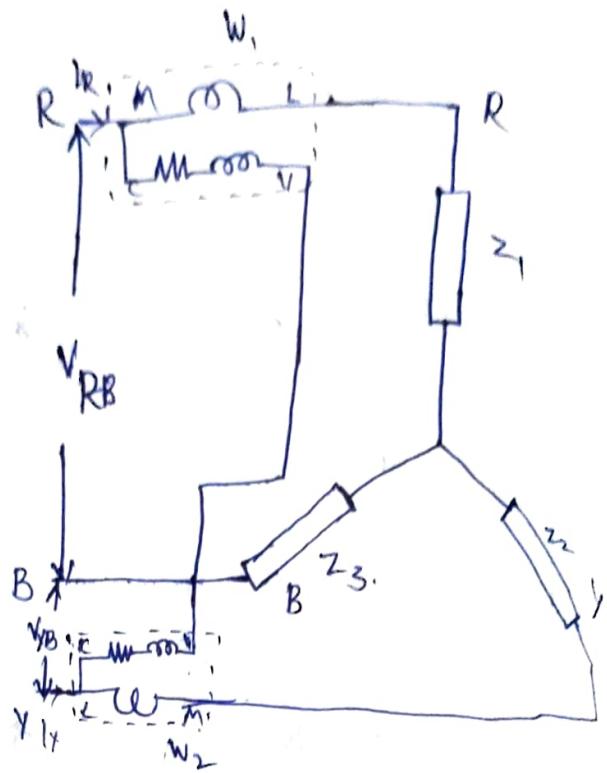

$$W_1 = V_{RB} \cdot I_R \cos(\angle V_{RB} I_R)$$

$$W_1 = V_L \cdot I_L \cos(30 - \phi)$$

$$W_2 = V_{RB} \cdot I_Y \cos(\angle V_{RB} I_Y)$$

$$W_2 = V_L \cdot I_L \cos(30 + \phi)$$

$$\therefore W_T = W_1 + W_2$$

$$= V_L I_L \cos(30 - \phi) + V_L I_L \cos(30 + \phi)$$

$$= V_L I_L [\cos(30 - \phi) + \cos(30 + \phi)]$$

$$= V_L I_L 2 \cos \phi \cdot \cos 30$$

$$= V_L I_L \phi \cos \phi \cdot \frac{\sqrt{3}}{2}$$

$$W_T = \sqrt{3} V_L I_L \cos \phi$$

∴ By using two watt-meter method, the sum of two wattmeter readings is equal to total power.

$$V_{ph} = 200 V$$

$$Z_1 = (7 + j5) \Omega = 8.6 \angle 35.5^\circ$$

$$Z_2 = (4 - j9) \Omega = 9.84 \angle -66.03^\circ$$

$$Z_3 = (8 - j6) \Omega = 10 \angle -36.86^\circ$$

$$I_{ph1} = \frac{V_{ph}}{Z_1} = \frac{200}{8.6 \angle 35.5^\circ} = 23.05 \angle 35.5^\circ$$

$$I_{ph2} = \frac{V_{ph}}{Z_2} = \frac{200 \angle -120^\circ}{9.84 \angle -66.03^\circ} = 20.32 \angle 53.97^\circ$$

$$I_{ph3} = \frac{V_{ph}}{Z_3} = \frac{200 \angle -120^\circ}{10 \angle -36.86^\circ} = 20 \angle 203.14^\circ$$

Complex Power:

$$S_1 = V_{ph} \times I_{ph1} = 200 \times 23.05$$

$$= 4680 VA$$

$$S_2 = V_{ph} \times I_{ph2} = 200 \times 20.32$$

$$= 4064 VA$$

$$S_3 = V_{ph} \times I_{ph3} = 200 \times 20$$

$$= 4000 VA$$

Total complex power,

$$S_T = S_1 + S_2 + S_3$$

$$= 4680 + 4064 + 4000$$

$$\boxed{S_T = 12744 VA}$$

a)
Given:-

$$V_L = 400$$

$$V_{ph} = \frac{V_L}{\sqrt{3}} = \frac{400}{\sqrt{3}} = 230.94 V$$

$$Z_A = 10 \angle 0^\circ$$

$$Z_B = 15 \angle 30^\circ$$

$$Z_C = 10 \angle -30^\circ$$

$$I_{ph} = \frac{230.94}{10} = 23.094 A$$

$$I_{ph2} = \frac{230.94 \angle -120^\circ}{15 \angle 30^\circ} = 15.396 \angle -150^\circ$$

$$I_{ph3} = \frac{230.94 \angle 120^\circ}{10 \angle -30^\circ} = 23.094 \angle 150^\circ$$

$$P_1 = V_{ph} I_{ph} \cos \phi$$

$$= 230.94 \times 23.094 \times \cos(120)$$

$$P_1 = 5333.32 W$$

$$P_2 = V_{ph} I_{ph} \cos \phi$$

$$= 230.94 \times 15.396 \times \cos(30)$$

$$P_2 = 3079.198 W$$

$$P_3 = V_{ph} I_{ph} \cos \phi$$

$$= 230.94 \times 23.094 \times \cos(-30)$$

$$= 4618.79 W$$

Total power, P_T

$$= P_1 + P_2 + P_3$$

$$\boxed{P_T = 13031.3 W}$$

H) b)
Given data:-

$$P_1 = 1560 W \quad | V_L = 220 V$$

$$P_2 = 2100 W$$

$$P_T = P_1 + P_2 = 1560 + 2100$$

$$= 3660 W$$

(a) The per-phase average power is then

$$P_p = \frac{1}{3} P_T = \frac{3660}{3} = 1220 W$$

(b) The total reactive power is,

$$Q_T = \sqrt{3}(P_2 - P_1) = \sqrt{3}(2100 - 1560) = 935.3 VAR$$

$$\text{Reactive power/ph} = \frac{935.3}{3}$$

$$= 311.77 VAR$$

(c) The power angle is.

$$\theta = \tan^{-1} \left(\frac{w_2}{P_1} \right)$$

$$= \tan^{-1} \left(\frac{955^3}{3660} \right)$$

$$\theta = 14.33^\circ$$

Hence the power factor is.

$$\cos \phi = 0.9689 \text{ (lagging)}$$

It is lagging pf because θ is +ve

$$P_2 > P_1$$

(d) The phase impedance is $Z_p = Z_p \angle \theta$

$$Z_p = \frac{V_p}{I_p}$$

We recall that for a delta-connected load,

$$V_p = V_L = 220\text{V}$$

$$P_p = V_p I_p \cos \phi$$

$$\Rightarrow I_p = \frac{1220}{220 \times 0.9689} = 5.723 \text{ A}$$

$$Z_p = \frac{220}{5.723} = 38.44 \Omega$$

$$Z_p = 38.44 \angle 14.33^\circ \Omega$$

Ques. Effect of load power factor on wattmeter readings in two-wattmeter method

wattmeter method :-

case-i) :- If the pf is unity then
wattmeter readings are equal i.e. $w_1 = w_2$

we know that,

$$\cos \phi = \cos \left[\tan^{-1} \sqrt{3} \left(\frac{w_1 - w_2}{w_1 + w_2} \right) \right]$$

$$1 = \cos \left(\tan^{-1} \left(\sqrt{3} \frac{(w_1 - w_2)}{w_1 + w_2} \right) \right)$$

$$\tan \left(\cos^{-1} \left(\frac{\sqrt{3}(w_1 - w_2)}{w_1 + w_2} \right) \right) = \frac{\sqrt{3}(w_1 - w_2)}{w_1 + w_2}$$

$$\frac{0}{\sqrt{3}} \text{ hence } w_1 = w_2$$

case-ii) :- If the pf is 0.5 then both
meter readings are equal and opposite.

Sign

$$\tan \left(\cos^{-1} \left(\frac{\sqrt{3}(w_1 - w_2)}{w_1 + w_2} \right) \right) = \frac{\sqrt{3}(w_1 - w_2)}{w_1 + w_2}$$

$$\frac{1}{0} \cancel{= \frac{\sqrt{3}(w_1 + w_2)}{w_1 + w_2}}$$

$$\frac{w_1 - w_2}{w_1 + w_2} = 0$$

$$w_1 = -w_2$$

case-iii) :- If pf is 0.5 then

$$\tan \left(\cos^{-1} \left(\frac{1}{2} \right) \right) = \frac{\sqrt{3} (w_1 - w_2)}{w_1 + w_2}$$


$$\frac{\sqrt{3}}{\sqrt{3}} = \frac{w_1 - w_2}{w_1 + w_2}$$

$$w_1 + w_2 = w_1 - w_2$$

$$w_2 = 0$$

If pf is 0.5 then one of the
wattmeter reading shows zero

Value :-

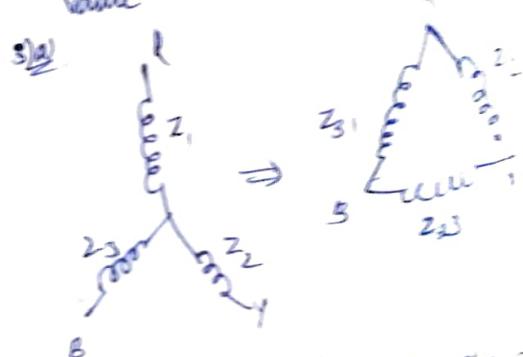

By the above figure shows the Star - Delta
transformation

$$Z_{12} = \frac{Z_1 Z_2 + Z_2 Z_3 + Z_3 Z_1}{Z_3}$$

$$Z_{23} = \frac{Z_1 Z_2 + Z_2 Z_3 + Z_3 Z_1}{Z_1}$$

$$Z_{31} = \frac{Z_1 Z_2 + Z_2 Z_3 + Z_3 Z_1}{Z_2}$$

$$I_{ph_1} = \frac{V_{AB}}{Z_{12}} ; I_{ph_2} = \frac{V_{BC}}{Z_{23}} ; I_{ph_3} = \frac{V_{CA}}{Z_{31}}$$

Line currents :-

$$I_R = I_{RY} - I_{BR}$$

$$I_Y = I_{RB} - I_{RY}$$

$$I_B = I_{BR} - I_{RB}$$

Given data :-

$$V_{AB} = 220 \angle 0^\circ \Rightarrow Z_{AB} = -j5 \Omega = 5 \angle -90^\circ$$

$$V_{BC} = 220 \angle 120^\circ \Rightarrow Z_{BC} = j10 \Omega = 10 \angle 90^\circ$$

$$V_{CA} = 220 \angle -120^\circ \Rightarrow Z_{CA} = 10 \Omega = 10 \angle 0^\circ$$

Phase currents :-

$$I_{AB} = \frac{V_{AB}}{Z_{AB}} = \frac{220}{5 \angle -90^\circ} = 44 \angle 90^\circ$$

$$I_{BC} = \frac{V_{BC}}{Z_{BC}} = \frac{220 \angle 120^\circ}{10 \angle 90^\circ} = 22 \angle 30^\circ$$

$$I_{CA} = \frac{V_{CA}}{Z_{CA}} = \frac{220 \angle -120^\circ}{10 \angle 0^\circ} = 22 \angle -120^\circ$$

Line currents :-

$$I_A = I_{AB} - I_{CA} = 44 \angle 90^\circ - 22 \angle -120^\circ$$

$$= 64 \angle 80.10^\circ$$

$$I_B = I_{BC} - I_{AB} = 22 \angle 30^\circ - 44 \angle 90^\circ$$

$$= 38.105 \angle -60^\circ$$

$$I_C = I_{CA} - I_{BC} = 22 \angle -120^\circ - 22 \angle 30^\circ$$

$$= 42.5 \angle -135^\circ$$


Power absorbed by AB phase, $P_{AB} = V_{ph} \times I_{ph} \cos \phi$

$$P_{AB} = 220 \times 44 \times \cos(-90) = 0$$

$$P_{BC} = 220 \times 22 \times \cos(90) = 0$$

$$P_{CA} = 220 \times 22 \times \cos(0) = 4840 \text{ W.}$$

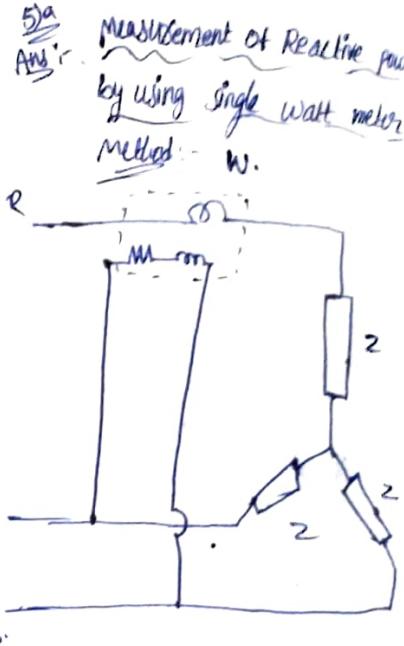Total real power absorbed (P_T) = 4840 W.



The power measured by the Wattmeter is,

$$W = V_{IB} \cdot I_B \cos(\phi_B - \theta)$$

The angle b/w V_{IB} & I_B is $(90 - \phi)$.


$$W = V_{IB} \cdot I_B \cos(90 - \phi)$$

$$W = V_{IB} \cdot I_B \sin \phi$$

$$W = V_L \cdot I_L \sin \phi. W$$

∴ The reactive power is,

$$\Theta_r = \sqrt{3} W \text{ VAR}$$

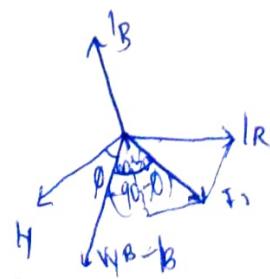

Sol:- Given data:-

because
N-wire system
 $Z_1 = (5+j7) \Omega$ it is a 1-wire system

$$Z_2 = (5+j7) \Omega$$

$$Z_3 = (8+j10) \Omega$$

$$V_L = 440V$$

$$V_{ph} = \frac{V_L}{\sqrt{3}} = \frac{440}{\sqrt{3}}$$

$$= 254.03V$$

Phase currents :-

$$I_{phR} = \frac{254.03}{5+j7} = 29.53 \angle -54.46^\circ$$

$$I_{ph(Y)} = \frac{254.03 \angle 120^\circ}{5+j7} = 29.53 \angle -174.46^\circ$$

$$I_{ph(B)} = \frac{254.03 \angle 120^\circ}{8+j10}$$

$$= 19.83 \angle 68.65^\circ$$

Line currents :-

$$I_R = I_{RY} - I_{BR}$$

$$= 29.53 \angle 54.46^\circ - 19.83 \angle 68.65^\circ$$

$$= 43.64 \angle -76.82^\circ$$

$$I_Y = I_B - I_{RY}$$

$$= 29.53 \angle -174.46^\circ - 29.53 \angle -54.46^\circ$$

$$= 51.147 \angle 155.54^\circ$$

$$I_B = I_{BR} - I_{YB}$$

$$= 19.83 \angle 68.65^\circ - 29.53 \angle -174.46^\circ$$

$$= 42.36 \angle 30.21^\circ$$

$$I_N = I_R + I_Y + I_B$$

$$= 1.84 \times 10^3 \angle 65.10^\circ$$

6(b)

Sol:-

=

$$Z_1 = 20 \angle -30^\circ$$

$$Z_2 = 40 \angle 80^\circ$$

$$Z_3 = 10 \angle 90^\circ$$

$$V_L = V_{ph} = 440V$$

$$V_{RY} = 440 \angle 0^\circ$$

$$V_{YB} = 440 \angle 120^\circ$$

$$V_{BR} = 440 \angle 120^\circ$$

Phase currents :-

$$I_{RY} = \frac{V_{RY}}{Z_1} = \frac{440 \angle 0^\circ}{20 \angle -30^\circ} = 22 \angle 30^\circ$$

$$I_{YB} = \frac{V_{YB}}{Z_2} = \frac{440 \angle 120^\circ}{40 \angle 80^\circ} = 11 \angle -20^\circ$$

$$I_{BR} = \frac{V_{BR}}{Z_3} = \frac{440 \angle 120^\circ}{10 \angle 90^\circ} = 44 \angle 30^\circ$$

Line currents :-

$$I_R = I_{RY} - I_{BR} = (22 \angle 30^\circ) - (44 \angle 30^\circ) \\ = 22 \angle -150^\circ$$

$$I_Y = I_{YB} - I_{RY} = (11 \angle -20^\circ) - (22 \angle 30^\circ) \\ = 30.26 \angle -166.16^\circ$$

$$I_B = I_{BR} - I_{YB} = 44 \angle 30^\circ - 11 \angle -20^\circ \\ = 51.76 \angle 20.63^\circ$$

Power at each phase:-

$$P_{RY} = V_{RY} \cdot I_{RY} \cos(30^\circ) \\ = 440 \times 22 \times \cos(-30^\circ) \\ = 8383.125 W$$

$$P_{YB} = 440 \times 11 \times \cos(80^\circ) = 840.45 W$$

$$P_{BR} = 440 \times 44 \times \cos(90^\circ) = 0$$

$$\therefore \text{Total Power} = P_{RY} + P_{YB} + P_{BR}$$

$$= 8383.125 + 840.45 + 0$$

$$\boxed{P = 9223.575 W}$$

$$Z_R = 8 \angle 30^\circ$$

$$Z_Y = 10 \angle 20^\circ$$

$$Z_B = 20 \angle 0^\circ$$

$$V_L = 100V$$

$$V_{ph} = \frac{V_L}{\sqrt{3}} = \frac{100}{\sqrt{3}} = 30.94 \angle 30^\circ$$

$$V_{ph} = 30.94 \angle 30^\circ$$

$$\sqrt{R}$$

$$\sqrt{B} = 30.94 \angle -90^\circ$$

$$\sqrt{Y} = 30.94 \angle 150^\circ$$

Using star delta transformation:-

$$Z_{RY} = \frac{Z_R Z_Y + Z_Y Z_B + Z_B Z_R}{Z_B}$$

$$= \frac{8 \angle 30^\circ \cdot 10 \angle 20^\circ + 10 \angle 20^\circ \cdot 20 \angle 0^\circ + 20 \angle 0^\circ \cdot 8 \angle 30^\circ}{20 \angle 0^\circ}$$

$$= \frac{432.19 \angle 29.02^\circ}{20}$$

$$= 21.6 \angle 29.023^\circ$$

$$Z_{YB} = \frac{432.19 \angle 29.02^\circ}{8 \angle 30^\circ}$$

$$= 54.02 \angle -0.98^\circ$$

$$Z_{BR} = \frac{432.19 \angle 29.02^\circ}{10 \angle 20^\circ}$$

$$= 43.219 \angle 9.02^\circ$$

Phase currents:-

$$I_{RY} = \frac{V_{RY}}{Z_{RY}} = \frac{30.94 \angle 30^\circ}{21.6 \angle 29.023^\circ}$$

$$= 10.69 \angle 0.977^\circ$$

$$I_{YB} = \frac{V_{YB}}{Z_{YB}} = \frac{30.94 \angle 90^\circ}{54.02 \angle -0.98^\circ}$$

$$= 4.27 \angle -89.02^\circ$$

$$I_{BR} = \frac{V_{BR}}{Z_{BR}} = \frac{30.94 \angle 150^\circ}{43.219 \angle 9.02^\circ}$$

$$= 5.343 \angle 140.98^\circ$$

Line currents:-

$$I_R = I_{RY} - I_{BR}$$

$$= 10.69 \angle 0.977^\circ - 5.343 \angle 140.98^\circ$$

$$= 15.17 \angle -12.10^\circ$$

$$I_Y = I_{YB} - I_{RY}$$

$$= 4.27 \angle -89.02^\circ - 10.69 \angle 0.977^\circ$$

$$= 11.51 \angle -157.24^\circ$$

$$I_B = I_{BR} - I_{YB}$$

$$= 5.343 \angle 140.98^\circ - 4.27 \angle -89.02^\circ$$

$$= 8.72 \angle 118.95^\circ$$

10(a).
SOL:

Applying KVL for loop 1:-

$$100 \angle 0^\circ + (1+j)I_1 + (1+j)2(I_1 - I_2) - 100 \angle 120^\circ = 0$$

$$(1+j)I_1 + (1+j)2I_1 - (1+j)2I_2 + 173.2 \angle 30^\circ = 0$$

$$I_1(1+j_1 + 1+j_2) - (1+j_2)I_2 + 173.2 \angle 30^\circ = 0$$

$$(2+j_3)I_1 - (1+j_2)I_2 = -173.2 \angle 30^\circ$$

LQ1

Applying KVL for loop 2:-

$$100 \angle -120^\circ + (1+j)2(I_2 - I_1) + (1+j)4I_2 - 100 \angle 40^\circ = 0$$

$$-(1+j)2I_1 + I_2(1+j_2 + 3+j_4) + 173.2 \angle -90^\circ = 0$$

$$-(1+j)2I_1 + (4+j)6I_2 = -173.2 \angle -90^\circ$$

$$\begin{bmatrix} 2+j_3 & -(1+j)2 \\ -(1+j)2 & (1+j)6 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} -173.2 \angle 30^\circ \\ -173.2 \angle -90^\circ \end{bmatrix}$$

$$\Delta = (2+j_3)(1+j)6 - (1+j)2(1+j)2$$

$$\Delta = 26 \angle 112.61^\circ - 5 \angle 126.86^\circ$$

$$\Delta = 21.189 \angle 109.28^\circ$$

$$\Delta_1 = \begin{vmatrix} -173.2 \angle 30^\circ & -(1+j2) \\ -173.2 \angle 90^\circ & (1+j2) \end{vmatrix}$$

$$\begin{aligned}\Delta_1 &= -173.2 \angle 30^\circ (1+j2) - (173.2 \angle 90^\circ) (1+j2) \\ &= -(80.38 + j1246.37) - (346.4 - j173.2) \\ &= -80.38 - 346.4 + j1246.37 + j173.2 \\ &= -426.78 + j1419.57 \\ &= 1482.33 \angle 106.73^\circ\end{aligned}$$

$$\Delta_2 = \begin{vmatrix} 2+j3 & -173.2 \angle 30^\circ \\ -(1+j2) & -173.2 \angle 90^\circ \end{vmatrix}$$

$$\begin{aligned}&= -(173.2 \angle 90^\circ)(2+j3) - (173.2 \angle 30^\circ)(1+j2) \\ &= -(519.6 - j346.4) - (-23.20 + j386.59) \\ &= -519.6 + 23.20 - j346.4 - j386.59 \\ &= -496.4 - j732.99\end{aligned}$$

$$\Delta_2 = 885.26 \angle -124.10^\circ$$

$$\therefore I_1 = \frac{\Delta_1}{\Delta} = \frac{1482.33 \angle 106.73^\circ}{21.189 \angle 109.28^\circ} \\ = 69.95 \angle -2.55^\circ.$$

$$I_2 = \frac{\Delta_2}{\Delta} = \frac{885.26 \angle -124.10^\circ}{21.189 \angle 109.28^\circ} \\ = 41.77 \angle 126.62^\circ$$

$$\therefore I_1 = I_A = 69.95 \angle -2.55^\circ$$

$$I_2 = I_C = 41.77 \angle 126.62^\circ$$

$$I_1 - I_2 = I_B = 69.95 \angle -2.55^\circ - 41.77 \angle 126.62^\circ \\ = 28.18^\circ A$$

$$\text{At } b, V_L = 1434 \text{ V}$$

$$3-\text{D} \quad \text{Im} \rightarrow Z_{ph} = (1.25 + j0.77) \Omega$$

$$V_{ph} = \frac{1434}{\sqrt{3}} = 250.517 \text{ V}$$

$$I_{Im} = \frac{V_{ph}}{Z_{ph}} = \frac{250.517}{1.25 + j0.77} \\ = 100 \angle -60^\circ A$$

$$I_{Sm} = 120A, \text{ at } 0.87 \text{ leading}$$

$$\phi_{Sm} = \cos^{-1}(0.87)$$

$$\theta_{Sm} = 29.54^\circ$$

$$I_{Sm} = 100 \angle 29.54^\circ$$

$$I = I_{Sm} + I_{Im}$$

$$= 100 \angle 60^\circ + 120 \angle 29.54^\circ$$

$$I = 156.82 \angle 10.07^\circ A$$

Total power factor, $\cos \phi = \cos \theta_{Sm}$

$$\cos \phi = 0.985 \text{ lagging.}$$

Input power, $P_{in} = \sqrt{3} V_L I_L \cos \phi$

$$P_{in} = \sqrt{3} \times 1434 \times 156.82 \times 0.985$$

$$W_1 + W_2 = 116.11 \text{ kW} \quad \text{--- (1)}$$

$$W_2 = 116.11 \times 10^3 - W_1$$

But,

$$\phi = \tan^{-1} \left\{ \frac{\sqrt{3}(W_1 - W_2)}{W_1 + W_2} \right\}$$

$$10.07 = \tan^{-1} \left(\frac{\sqrt{3}(W_1 - W_2)}{W_1 + W_2} \right)$$

$$0.178 = \frac{\sqrt{3}(W_1 - W_2)}{W_1 + W_2}$$

$$W_1 + W_2 = \frac{\sqrt{3}}{0.178} (W_1 - W_2)$$

$$W_1 + W_2 = 9.73 (W_1 - W_2)$$

$$\frac{116.11 \times 10^3}{9.73} = w_1 - w_2$$

$$11933.19 = w_1 - w_2 \quad \text{--- (1)}$$

By solving eq (1) & (2)


$$\begin{aligned} w_1 + w_2 &= 11611 \times 10^3 \\ w_1 - w_2 &= 11933.19 \\ 2w_1 &= 128043.19 \end{aligned}$$

$$w_1 = 64021.59$$

$$w_1 = 64.02 \text{ kVA}$$

$$w_2 = 116.11 \times 10^3 - 64.02 \times 10^3$$

$$w_2 = 52.09 \text{ kVA}$$

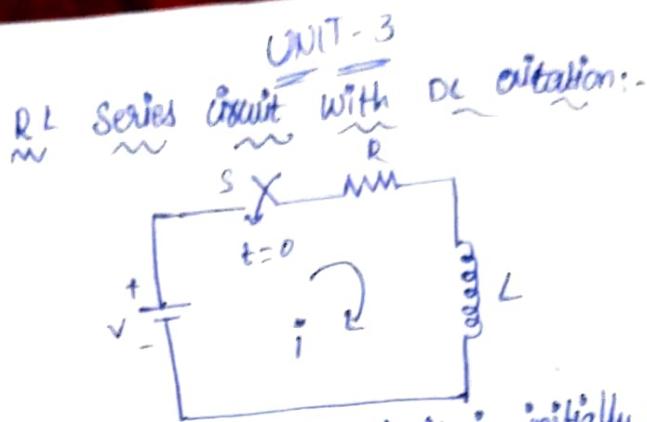

The inductor in the circuit is initially uncharged and it is in series with resistor R.

Apply KVL in the circuit,

$$-V + iR + L \frac{di}{dt} = 0$$

$$iR + L \frac{di}{dt} = V$$

$$\frac{di}{dt} + \frac{iR}{L} = \frac{V}{L} \quad \text{--- (1)}$$

The above eq is in the form of 1st order differential equation and it is in the form of following standard first order differential equation,

$$\frac{dx}{dt} + Px = Q \quad \text{--- (2)}$$

C.F. of eq (1) we have two parts $\left\langle \begin{array}{l} \text{C.F.} \\ \text{P.I.} \end{array} \right\rangle$

$$C.F. = I(C.F.) = A e^{-Pt} \quad \text{by comparing with eq (2)}$$

$$P = \frac{R}{L}$$

$$\therefore C.F. \text{ of eq (1), } i(C.F.) = A e^{-R/L t}$$

$$\gamma = \frac{L}{R}$$

$$i(C.F.) = A e^{-t/\gamma}$$

$$P.I., i(P.I.) = e^{-Pt} \int e^{Pt} dt$$

$$\text{By comparing eq (1) & (2), } A = \frac{V}{L}$$

$$P.I. \text{ of eq (1), } i(P.I.) = e^{-R/L t} \int \frac{V}{L} e^{R/L t} dt$$

$$= e^{-R/L t} \frac{V}{L} \left[\frac{e^{R/L t}}{R} \right]$$

$$= \left[e^{-R/L t} \cdot e^{R/L t} \right] \left[\frac{V}{L} \cdot \frac{1}{R} \right]$$

$$i(P.I.) = \frac{V}{R}$$

The solution for $i(t)$

$$i(t) = Ae^{-t/\gamma} + \frac{V}{R}$$

$$i(0) = Ae^{-0/\gamma} + \frac{V}{R}$$

By substituting initial conditions

$$t=0, i(0)=0$$

$$i(0) = Ae^{-0/\gamma} + \frac{V}{R}$$

$$0 = A + \frac{V}{R}$$

$$\boxed{A = -\frac{V}{R}}$$

$$i(t) = \frac{V}{R} [1 - e^{-t/\gamma}] \text{ at } t \geq 0$$

$$\text{at } t = 2\gamma \text{ then, } i(t) = 0.632 \frac{V}{R}$$

$$t = 2\gamma \text{ then, } i = 0.865 \frac{V}{R}$$

$$t = 3\gamma \text{ then, } i = 0.95 \frac{V}{R}$$

$$t = 4\gamma \text{ then, } i = 0.982 \frac{V}{R}$$

$$\text{consider, } i(t) = \frac{V}{R} [1 - e^{-t/\gamma}]$$

$$V_L(t) = \frac{L \frac{di}{dt}(t)}{dt}$$

$$= L \cdot \frac{d}{dt} \left[\frac{V}{R} [1 - e^{-t/\gamma}] \right]$$

$$\gamma = 4R \\ = L \frac{d}{dt} \left[\frac{V}{R} - \frac{V}{R} e^{-t/\gamma} \right]$$

$$= L \left[0 - \frac{V}{R} e^{-t/\gamma} \cdot \frac{1}{\gamma} \right]$$

$$= \frac{V}{R} e^{-t/\gamma} \quad (L=1H)$$


$$= V e^{-t/\gamma}$$

$$\boxed{V_L(t) = V e^{-t/\gamma}}$$


$$V_R(t) = iR$$

$$= \frac{V}{R} [1 - e^{-t/\gamma}] \cdot R$$
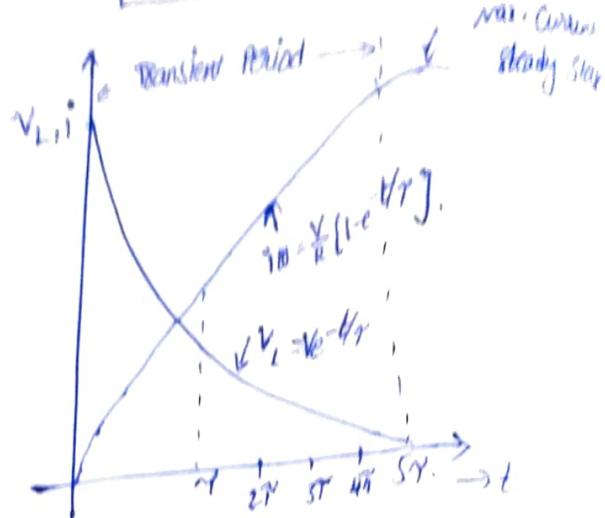
$$\boxed{V_R(t) = V [1 - e^{-t/\gamma}]} \quad \text{Ans. Current steady state}$$



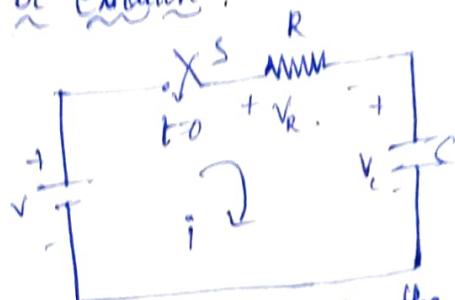Transient Response of RC Series Circuit with DC excitation :-



At $t=0$ we are closing the switch.

Apply KVL in above circuit

$$-V + V_R + V_C = 0$$

$$V_R + V_C = V$$

$$V_R = iR$$

$$i = C \frac{dV_C}{dt}$$

$$V_R = C \frac{dV_C}{dt} \cdot R$$

$$V = RC \frac{dV_C}{dt} + V_C = V$$

$$\frac{dv_c}{dt} + \frac{1}{RC} v_c = \frac{V}{RC} - 0$$

this is in the form of

$$\frac{dx}{dt} + px = Q$$

by comparing eq ① with ② we get

$$p = \frac{1}{RC}, Q = \frac{V}{RC}$$

the solution of 1st order differential eq is given below.

$$v_c(t) = CF + P.I.$$

$$\therefore v_c(t) = Ae^{-pt}$$

$$CF \quad v_c(CF) = Ae^{-\frac{t}{RC}}$$

$$= Ae^{-\frac{t}{RC}} \cdot \frac{1}{RC} e^{-\frac{t}{RC}}$$

$$\gamma = RC \quad v_c(CF) = Ae^{-t/\gamma}$$

$$\begin{aligned} P.I. \quad v_c(P.I.) &= e^{-pt} \int a e^{pt} dt \\ &= e^{-\frac{t}{RC}} \int \frac{V}{RC} e^{\frac{t}{RC}} dt \\ &= e^{-\frac{t}{RC}} \cdot \frac{V}{RC} \left[\frac{e^{\frac{t}{RC}}}{\frac{1}{RC}} \right] \\ &= e^{-\frac{t}{RC}} \cdot \frac{V}{RC} \left[\frac{RC}{1} \right] \end{aligned}$$

$$\boxed{v_c(P.I.) = V}$$

$$\therefore v_c(t) = v_c(C.F) + v_c(P.I.)$$

$$= Ae^{-t/\gamma} + V$$

We get the value of γ by substituting initial condition at $t=0$.

$$0 = Ae^0 + V$$

$$A = -V$$

$$v_c(t) = -Ve^{-t/\gamma} + V$$

$$\boxed{v_c(t) = V [1 - e^{-t/\gamma}]}$$

$$At t = \gamma \text{ then } v_c = 0.632 V$$

$$t = 2\gamma \text{ then } v_c = 0.865 V$$

$$t = 3\gamma \text{ then } v_c = 0.950 V$$

$$t = 4\gamma \text{ then } v_c = 0.981 V$$

$$t = 5\gamma \Rightarrow v_c = 0.993 V$$

$$i_c(t) = C \frac{dv_c}{dt}$$

$$= C \frac{d}{dt} [V(1 - e^{-t/\gamma})]$$

$$= C \frac{d}{dt} [V - Ve^{-t/\gamma}]$$

$$= C \{ 0 - V \left[\frac{1}{RC} \right] e^{-t/RC} \}$$

$$= C \left[\frac{V}{RC} e^{-t/\gamma} \right]$$

$$\boxed{i_c(t) = \frac{V}{RC} e^{-t/\gamma}}$$

$$At t = \gamma \text{ then } i_c = 0.367 \frac{V}{R}$$

$$t = 2\gamma \Rightarrow i_c = 0.135 \frac{V}{R}$$

$$t = 3\gamma \quad i_c = 0.049 \frac{V}{R}$$

$$t = 4\gamma \quad i_c = 0.019 \frac{V}{R}$$


$$t = 5\gamma \quad i_c = 6.2 \times 10^{-3} \frac{V}{R}$$


≈ 0 .

$$v_R(t) = i(R)$$

$$= \frac{V}{R} e^{-t/\gamma}$$

$$\boxed{v_R(t) = Ve^{-t/\gamma}}$$

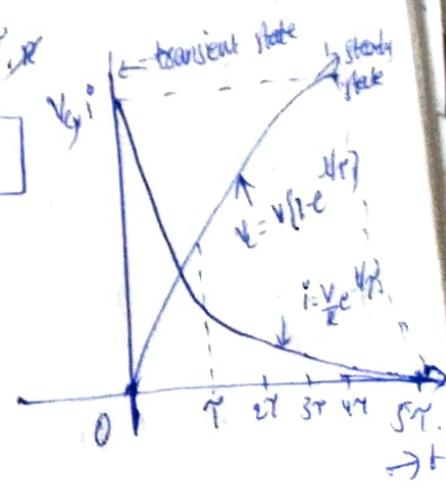

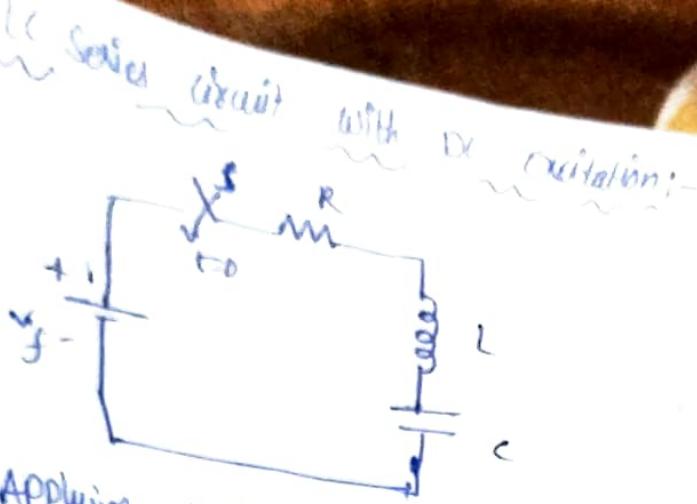

Applying KVL for the above circuit,

$$-V_f + V_R + V_L + V_C = 0$$

$$V_R + V_L + V_C = V_f$$

$$i(t)R + L \frac{di(t)}{dt} + V_C = V_f \quad \text{---(i)}$$

The current flowing through the capacitor is given by

$$i_C(t) = \frac{C \frac{dV_C(t)}{dt}}{dt} = \ddot{i}(t)$$

Substitute in eq (i),

$$RC \frac{dV_C(t)}{dt} + L \frac{d}{dt} \left[\frac{C \frac{dV_C(t)}{dt}}{dt} \right] + V_C(t) = V_f.$$

$$\frac{LC \frac{d^2V_C(t)}{dt^2}}{dt^2} + RC \frac{dV_C(t)}{dt} + V_C(t) = V_f.$$

Divide LC with above equation on both sides.

$$\frac{d^2V_C(t)}{dt^2} + \frac{R}{L} \frac{dV_C(t)}{dt} + \frac{V_C(t)}{LC} = \frac{V_f}{LC}$$

$$\text{Let } \frac{d}{dt} = D, \quad \frac{d^2}{dt^2} = D^2$$

$$D^2 V_C(t) + \frac{R}{L} D V_C(t) + \frac{V_C(t)}{LC} = \frac{V_f}{LC}$$

$$(D^2 + D \frac{R}{L} + \frac{1}{LC}) V_C(t) = \frac{V_f}{LC}$$

The characteristic of eq (i) is given by

$$D^2 + D \frac{R}{L} + \frac{1}{LC} = 0$$

Case-i: The roots are real and distinct

$$V_C(t) = V_f + A e^{p_1 t} + B e^{p_2 t}.$$


Case-ii: The roots are real and equal

$$V_C(t) = V_f + (A + Bt)e^{p_1 t}.$$

Case-iii: The roots are complex

$$V_C(t) = V_f + (A \cos \omega t + B \sin \omega t) e^{-\alpha t}.$$

Source free circuit:-

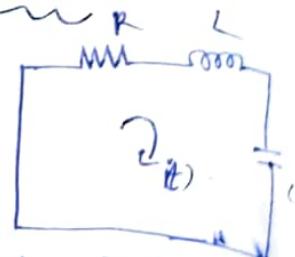

Apply KVL for the circuit

$$i(t)R + L \frac{di(t)}{dt} + \frac{1}{C} \int i dt - 0$$

Differentiate with respect to 't'

$$\frac{di(t)}{dt}R + L \frac{d^2i(t)}{dt^2} + \frac{i}{C} = 0.$$

$$L \frac{d^2i(t)}{dt^2} + R \frac{di(t)}{dt} + \frac{i}{C} = 0$$

$$\frac{d^2i(t)}{dt^2} + \frac{R}{L} \frac{di(t)}{dt} + \frac{i}{LC} = 0$$

$$\mu L \cdot \frac{d}{dt} \left(D_1 \cdot \frac{d^2}{dt^2} \right) = D^L$$

$$D^L i(t) + \frac{R}{L} D(i(t)) + \frac{V_0}{L} = 0$$

$$3T_1 + 3\left(-V_1 + \frac{1}{2}T_1\right) = V_1$$

$$3T_1 + 3V_1 - \frac{3}{2}T_1 = V_1$$

$$(D^L + \frac{R}{L} + \frac{1}{LC}) i(t) = 0 \quad \text{--- (2)}$$

The characteristic equation of eq (2) is given by $D^L + \frac{R}{L} D + \frac{1}{LC} = 0$.

Case (i): The roots are real and unequal

$$i(t) = A e^{D_1 t} + B e^{D_2 t}$$

Case (ii): The roots are real & equal


$$i(t) = (At + B)e^{D_1 t}$$

Case (iii): The roots are complex.

$$i(t) = (A \cos \omega t + B \sin \omega t)e^{-\alpha t}$$

UNIT-4

Substitute I_4 value in above equation

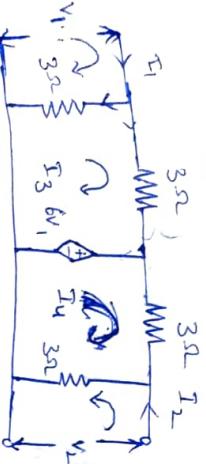

Applying KVL for loop 1.

$$3I_1 - 3I_3 = V_1 \quad \text{--- (1)}$$

Applying KVL for loop 2:

$$3I_2 + 6V_1 + 3(I_3 - I_1) = 0$$

$$-3I_1 + 6I_3 + 6V_1 = 0$$

$$I_3 = -V_1 + 3I_1 \quad \text{--- (2)}$$

$$I_3 = -V_1 + \frac{1}{2}I_1 \quad \text{--- (2)}$$

$$\frac{3}{2}I_1 = -2V_1 \quad \text{--- (6)}$$

$$\frac{3}{2}I_1 + 2V_1 = 0$$

$$3I_2 + 3(V_1 + 2V_1) = 0 \quad \text{ADD eqn 1 and eqn 6}$$

$$V_1 = \frac{1}{3}V_2 + \frac{1}{2}I_2$$

$$V_1 = \frac{1}{3}V_2 - \frac{3}{2}I_2$$

$$I_4 = \frac{1}{3}V_2 - \frac{9}{2}I_2$$

$$I_4 = \frac{3}{2}V_2 - \frac{9}{2}I_2$$

$$6\left(\frac{1}{3}V_2 - I_2\right) - 3I_2 - 6V_1 = 0$$

$$2V_2 - 6I_2 - 3I_2 - 6V_1 = 0$$

$$-9I_2 - 6V_1 = -2V_2 \Rightarrow 2V_2 + 9I_2$$

$$+ (9I_2 + 6V_1) = -2V_2$$

$$\frac{9}{2}I_2 + 3V_1 = V_2$$

$$V_1 = \frac{1}{3}V_2 - \frac{3}{2}I_2 \quad \text{--- (7)}$$

Substitute eqn (7) in eqn (1)

$$\frac{3}{2}I_1 + 2\left(\frac{1}{3}V_2 - \frac{3}{2}I_2\right) = 0$$

$$V_1 = \frac{1}{3} V_2 + \frac{2}{3} V_3 + 2 V_4$$

$$V_1 = \frac{1}{3} V_2 + \frac{2}{3} V_3 + 2 V_4$$

$$V_1 = \frac{1}{3} V_2 + \frac{2}{3} V_3 + 2 V_4$$

$$A = \frac{1}{3}, \quad B = \frac{2}{3}$$

$$C = -\frac{1}{3}, \quad D = -2$$

$$\text{Given: } 2I_1 + 2I_2 = 6 \text{ A}$$

$$I_{12} = 2I_1 = 4 \text{ A}$$

The Z-PARAMETRIC equations are:

$$V_1 = 2I_1 T_1 + 2I_{12} T_2$$

$$V_2 = 2I_2 T_1 + 2I_{12} T_2$$

$$T_1 = \frac{1}{4} V_1 + 0.1 V_2$$

$$V_1 = 6T_1 + 4T_{12} - 0$$

$$T_2 = \frac{1}{4} V_2 + 0.1 V_1 \quad (3)$$

S substitute eq(3) in eq(2).

$$V_1 = 6T_1 + 4(T_2 - 0.1 V_1)$$

$$V_1 = 6T_1 + 4\left(\frac{1}{4}V_2 + 0.1 V_1\right)$$

$$T_2 = 5V_1 + 0.5V_2 + 0.1 V_1$$

$$T_2 = -\frac{2}{3}V_1 + \frac{1}{6}V_2 \quad (4)$$

Substit. eq(3) in eq(4)

$$V_1 = 6T_1 + 4\left(\frac{1}{3}T_1 + \frac{1}{6}V_2\right)$$

$$V_1 = 6T_1 + \frac{8}{3}T_1 + \frac{2}{3}V_2$$

$$V_1 = \frac{10}{3}T_1 + \frac{2}{3}V_2$$

Similarly:

$$\begin{cases} 3.333 & 0.666 \\ -0.666 & 0.666 \end{cases}$$

(D) H-PARAMETERS in terms of T-PARAMS.


T-PARAMS

H-PARAMS

$$V_1 = 5V_1 - 8T_2 - 0$$

$$Y_1 = CY_1 - DT_2 - 0$$
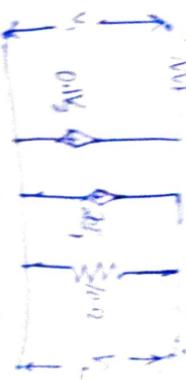
$$T_2 = \frac{C Y_1 - D T_1}{D} \Rightarrow T_2 = \frac{C}{D} Y_1 - \frac{1}{D} T_1$$



H-PARAMETER equation equivalent of the circuit

$$\text{Apply KVL for loop 1}$$

$$V_1 = HT_1 + 0.1V_2 \quad (1)$$

$$Y_2 = HT_2 + 0.1V_2 \quad (2)$$

$$T_2 = 5T_1 + 0.5V_1 + 0.1V_2 \quad (3)$$

$$T_1 = \frac{1}{4}V_1 + 0.1V_2$$

$$T_2 = \frac{1}{4}V_2 + 0.1V_1$$

Applying KVL for loop 1:-

$$100I_1 + 200(I_1 + I_2 + \frac{V_1}{500}) = V_2$$

$$240I_2 + 200I_1 + \frac{2}{5}V_1 = V_2.$$

$$I_2 = \frac{V_2 - \frac{2}{5}V_1 - 200I_1}{240}$$

$$I_2 = \frac{1}{240}V_2 - \frac{1}{600}V_1 - \frac{5}{6}I_1 \quad (2)$$

Substitute eq(2) in eq(1).

$$I_1 = \frac{1}{500}V_1 - \frac{2}{3}\left(\frac{1}{240}V_2 - \frac{1}{600}V_1 - \frac{5}{6}I_1\right)$$

$$I_1 = \frac{1}{500}V_1 - \frac{1}{360}V_2 + \frac{1}{900}V_1 + \frac{5}{9}I_1$$

$$I_1 - \frac{5}{9}I_1 = V_1\left(\frac{1}{500} + \frac{1}{900}\right) - \frac{1}{360}V_2$$

$$\frac{4}{9}I_1 = V_1\left(\frac{1}{2250}\right) - \frac{1}{360}V_2$$

$$I_1 = \frac{7}{2250} \times \frac{9}{4}V_1 - \frac{1}{360} \times \frac{9}{4}V_2$$

$$I_1 = \frac{7}{1000}V_1 - \frac{1}{160}V_2 \quad (3)$$

Substitute eq(3) in eq(2).

$$I_2 = \frac{1}{240}V_2 - \frac{1}{600}V_1 - \frac{5}{6}\left(\frac{7}{1000}V_1 - \frac{1}{160}V_2\right)$$

$$I_2 = \frac{1}{240}V_2 - \frac{1}{600}V_1 - \frac{7}{1200}V_1 + \frac{1}{192}V_2$$

$$I_2 = V_1\left(-\frac{1}{600} - \frac{7}{1200}\right) + V_2\left(\frac{1}{240} + \frac{1}{192}\right)$$

$$I_2 = \frac{-3}{400}V_1 + \frac{3}{320}V_2$$

γ -Parameters are,

$$\gamma = \begin{bmatrix} \frac{7}{1000} & -\frac{1}{160} \\ -\frac{3}{400} & \frac{3}{320} \end{bmatrix}$$


2 parameters are $\begin{bmatrix} 10 & 2 \\ 10 & 6 \end{bmatrix}$

γ -Parameters are:-

$$\gamma = \frac{1}{100} \begin{bmatrix} 6 & -2 \\ -10 & 10 \end{bmatrix}$$

$$= \frac{1}{100} \begin{bmatrix} \frac{6}{40} & \frac{2}{40} \\ -\frac{10}{40} & \frac{10}{40} \end{bmatrix}$$
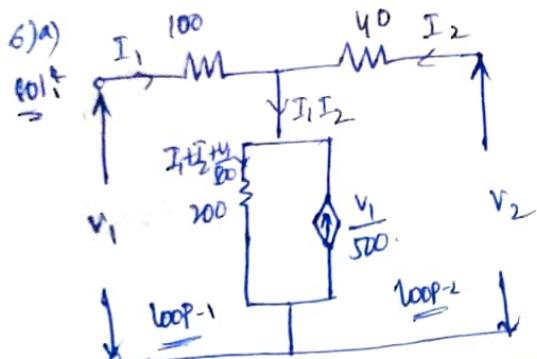
$$\gamma = \begin{bmatrix} 0.15 & -0.05 \\ -0.25 & 0.25 \end{bmatrix}$$



Applying KVL for loop 1:- γ -Parameters.

$$100I_1 + 200(I_1 + I_2 + \frac{V_1}{500}) = V_1$$

$$300I_1 + 200I_2 + \frac{2}{5}V_1 = V_1$$

$$300I_1 + 200I_2 = V_1 - \frac{2}{5}V_1$$

$$300I_1 + 200I_2 = \frac{3}{5}V_1$$

$$\boxed{V_1 = 500I_1 + \frac{5}{3}(200)I_2}$$

$$V_1 = 500I_1 + 333.33I_2$$

$$I_1 = \frac{\frac{3}{5}V_1 - 200I_2}{300}$$

$$I_1 = \frac{\frac{3}{5} \times \frac{1}{300}V_1 - \frac{200}{300}I_2}{300}$$

$$I_1 = \frac{1}{500}V_1 - \frac{2}{3}I_2 \quad // \quad (1)$$


9) (a) $Z_{AB} = 9\Omega$, 8-a-b repeated

(b)

(c)

Applying KVL for loop 1:-

$$8I_1 + 6(I_2 + I_3) = V_1$$

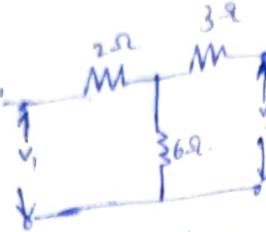

$$8I_1 + 6I_2 = V_1 \quad \text{---(1)}$$

$$8I_1 + 6\left(\frac{V_1 - V_2}{3}\right) = V_1$$

$$8I_1 + \frac{2}{3}V_2 - 6I_1 = V_1$$

$$V_1 = \frac{2}{3}V_2 + 6I_1$$

$$I_1 = \frac{1}{6}V_2 - \frac{3}{2}I_2 \quad \text{---(2)}$$

Also:

$$V_1 = AV_2 + BI_2$$

$$I_1 = CV_2 + DI_2$$

$$8\left(\frac{1}{6}V_2 - \frac{3}{2}I_2\right) + 6I_2 = V_1$$

$$\frac{4}{3}V_2 - 12I_2 + 6I_2 = V_1$$

$$V_1 = -6I_2 + \frac{4}{3}V_2 \quad \text{---(3)}$$

$$A = \frac{4}{3}, B = 6$$

$$C = \frac{1}{6}, D = \frac{3}{2}$$

10) (a) Y-parameter

10) (b) Y-parameter

Applying KVL for loop 1:-

$$2I_1 + 4(I_2 - I_3) = V_1$$

$$6I_1 - 4I_3 = V_1$$

Applying KVL for loop 2:-

$$2I_3 + 4(I_3 - I_2) + 4(I_3 - V_2) = 0$$

$$40I_3 - 4I_2 - 4I_3 = 0 \quad \text{---(1)}$$

Applying KVL for loop 3:-

$$5I_4 + 4(I_4 + I_2) + 4(I_4 - I_3) = 0$$

$$10I_4 + 4I_2 - 4I_3 = 0 \quad \text{---(2)}$$

Applying KVL for loop 4:-

$$4(I_2 + I_4) = V_2$$

$$4I_2 + 4I_4 = V_2$$

$$I_4 = \frac{V_2 - 4I_2}{4}$$

$$I_4 = \frac{1}{4}V_2 - I_2$$

Consider, eq (1),

$$-4I_3 = V_1 - 6I_1$$

$$I_3 = -\frac{1}{4}V_1 + \frac{3}{2}I_1 \quad \text{---(3)}$$

Substitute ~~I4~~ $\frac{1}{4}V_2$ Value in eq (2),

$$10\left(\frac{1}{4}V_1 + \frac{3}{2}I_1\right) - 4I_2 - 4\left(\frac{1}{4}V_2 - I_2\right) = 0$$

$$-\frac{10}{4}V_1 + 15I_1 - 4I_2 - V_2 + 4I_2 = 0$$

$$-11I_1 - \frac{5}{2}V_1 + 4I_2 = V_2$$

$$\Rightarrow 10\left(\frac{1}{4}V_2 - I_2\right) + 4I_2 - 4\left(\frac{1}{4}V_1 + \frac{3}{2}I_1\right) = 0$$

$$\frac{5}{2}V_2 - 10I_2 + 4I_2 + V_1 - 6I_1 = 0$$

$$-6I_1 - 6I_2 + \frac{5}{2}V_2 = V_1$$

Ans:- Symmetry for Y-parameter:

$$I_1 = Y_{11}V_1 + Y_{12}V_2 \Rightarrow I_2 = 0$$

$$I_2 = Y_{21}V_1 + Y_{22}V_2$$

$$-Y_{11}V_1 = Y_{12}V_2$$

$$V_1 = -\frac{Y_{12}}{Y_{11}}V_2$$

$$I_2 = Y_{21}\left(-\frac{Y_{12}}{Y_{11}}V_2\right) + Y_{22}V_2$$

$$I_2 = \frac{Y_{12}Y_{21}}{Y_{11}}V_2 + Y_{22}V_2$$

$$I_2 = \frac{-Y_{12}Y_{21}V_1 + Y_{11}Y_{22}V_2}{Y_{11}}$$

$$I_2 = \frac{\Delta V}{Y_{11}} \Rightarrow \frac{V_2}{Y_{11}}$$

out post is open circuited $I_2 = 0$.

$$Y_{11}V_1 = -Y_{22}V_2$$

$$V_2 = -\frac{Y_{21}}{Y_{22}} V_1$$

Substitute V_2 in eq (1)

$$I_1 = Y_{11}V_1 + Y_{12}\left(\frac{-Y_{21}}{Y_{22}} V_1\right)$$

$$I_1 = Y_{11}V_1 + \frac{Y_{12}V_{21}}{Y_{22}} V_1$$

$$I_1 = \left(\frac{Y_{11}Y_{22} - Y_{12}Y_{21}}{Y_{22}}\right) V_1$$

$$\frac{I_1}{V_1} = \frac{\Delta}{Y_{22}}$$

$$\frac{V_1}{I_1} = \frac{Y_{22}}{\Delta}$$

By the definition of symmetry,

$$\frac{V_1}{I_1} = \frac{V_2}{I_2}$$

$$\frac{Y_{11}}{\Delta} = \frac{Y_{22}}{\Delta}$$

$$\boxed{Y_{11} = Y_{22}}$$

Reciprocity condition for Y parameters:-

If o/p post is short circuited, then

$$V_1 = 0, I_1 = -I_2^1, V_2 = V_1 \Rightarrow \frac{V_2}{I_1} = \frac{1}{Y_{12}}$$

$$-I_1^1 = Y_{12}V_2$$

$$\frac{V_2 - I_1^1}{V_2} = Y_{12} \Rightarrow \frac{V_2}{I_1^1} = -Y_{12}$$

If o/p post is short circuited, then,

$$V_2 = 0, I_2 = -I_1^1, V_1 = V_2 \Rightarrow \frac{V_1}{I_1^1} = \frac{1}{Y_{21}}$$

$$-I_1^1 = Y_{21}V_1$$

$$\frac{-I_1^1}{V_1} = Y_{21}$$

$$\frac{V_1}{I_1^1} = -Y_{21}$$

By the definition,

$$\frac{V_1}{I_1^1} = \frac{V_2}{I_1^1} \Rightarrow \boxed{Y_{21} = Y_{12}},$$

(2) \rightarrow Parameters in terms of h -parameters

Sol: h parameters

$$V_1 = h_{11}I_1 + h_{12}V_2$$

$$I_2 = h_{21}I_1 + h_{22}V_2$$

$$\begin{aligned} \text{↑ parameter} \\ V_1 &= Z_1I_1 + Z_2I_2 \\ V_2 &= Z_2I_1 + Z_{22}I_2 \end{aligned}$$

$$V_2 = \frac{I_2 - h_{21}I_1}{h_{22}}$$

$$V_2 = \frac{1}{h_{22}}I_2 - \frac{h_{21}}{h_{22}}I_1 \quad \rightarrow (1)$$

$$V_1 = h_{11}I_1 + h_{12}\left(\frac{1}{h_{22}}I_2 - \frac{h_{21}}{h_{22}}I_1\right)$$

$$V_1 = h_{11}I_1 + \frac{h_{12}}{h_{22}}I_2 - \frac{h_{12}h_{21}}{h_{22}}I_1$$

$$V_1 = \frac{h_{12}}{h_{22}}I_2 + \left(h_{11} - \frac{h_{12}h_{21}}{h_{22}}\right)I_1$$

$$V_1 = \frac{\Delta}{h_{22}}I_1 + \frac{h_{12}}{h_{22}}I_2$$

$$\therefore Z_{11} = \frac{\Delta}{h_{22}} \quad \boxed{Z_{21} = -\frac{h_{21}}{h_{22}}}$$

$$Z_{12} = \frac{h_{12}}{h_{22}} \quad \boxed{Z_{22} = \frac{1}{h_{22}}}$$

(3)

Applying KVL for loop 1:-

$$I_1 + 3(I_1 - I_3) = V_1$$

$$7I_1^3 - I_3 = V_1$$

$$\text{Applying KVL for loop 2:-} \quad 3(I_3 - I_1) + V_2 + 5(I_3 + I_2) = 0$$

$$3I_3^2 - 3I_1 + V_2 + 5I_3 + 5I_2 = 0 \quad (1)$$


$$5I_2 + 5I_3 = V_2$$

$$5I_2 + 5I_3 = V_2 \quad (3)$$

$$5I_2 + 5I_3 = -8I_3 + 3I_1 - 5I_2$$

$$10I_2 + 13I_3 = 3I_1$$
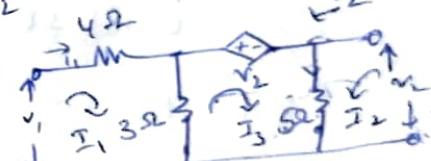
$$I_3 = \frac{3I_1 - 10I_2}{13} \quad (5)$$



$$8I_3 - 3I_1 + 5I_2 = -V_2$$

$$-8I_3 + 3I_1 - 5I_2 = V_2 \quad (4)$$

$$\frac{V_1 - 7I_1}{3} = \frac{3I_1 - 10I_2}{13}$$

$$V_1 = 10I_1 + \frac{6}{11}V_2$$

$$13V_1 - 9I_1 = -9I_1 + 30I_2$$

$$13V_1 = -9I_1 + 30I_2$$

$$13V_1 = 82I_1 + 30I_2$$

$$V_1 = \frac{82}{13}I_1 + \frac{30}{13}I_2$$

$$V_1 = 6.307I_1 + 2.307I_2$$

Substitute eq(5) in eq(3),

$$5I_2 + 5\left[\frac{3I_1 - 10I_2}{13}\right] = V_2$$

$$5I_2 + \frac{15}{13}I_1 - \frac{50}{13}I_2 = V_2$$

$$\frac{15}{13}I_1 + I_2(5 - \frac{50}{13}) = V_2$$

$$1.153I_1 + 1.153I_2 = V_2$$

$$I_1 = I_1 A$$

$$I_2 A = I_2 B \quad (00) \quad I_1 B = -I_2 A$$

$$I_2 B = I_2$$

$$V_2 = V_2$$

$$V_1 = V_1 A$$

$$V_1 B = V_1$$

∴

$$Z_{11} = 0.485 \Omega$$

$$Z_{12} = 2.307 \Omega$$

$$Z_{21} = 1.153 \Omega$$

$$Z_{22} = 1.153 \Omega$$

∴

ABD parameters are highly useful in characterizing the cascade



$$V_1 = 10I_1 + 6I_2$$

$$V_2 = 6I_1 + 11I_2$$

$$I_2 = \frac{V_2 - 6I_1}{11} + I_1 V_L$$

$$V_1 = 10I_1 + 6\left(\frac{V_2 - 6I_1}{11}\right)$$

Cascade connection:



from above network; $V_1 = V_1 A$

$$V_1 A = V_1 B$$

$$V_2 = V_2$$


$$V_2 B = V_2$$

$$V_3 = V_3 A$$

∴

ABD

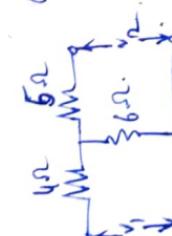parameters are highly useful in characterizing the cascade



$$V_1 = h_{11}I_1 + h_{12}V_L$$

$$V_2 = h_{21}I_1 + h_{22}V_L$$

UNIT-5 - Two Port Network.

Two port Network:

A pair of terminals through which a current may enter or leave a network is known as port.


Two terminal devices or elements (such as resistor, capacitors, and inductors) results in one-port network.

Most of the circuits we have dealt with so far are two-terminal or one-port circuits.

A two-port network is an electrical network with two separate ports for input and output.

It has two terminal pairs acting as access points. The current entering one terminal of a pair leaves the other terminal in the pair.

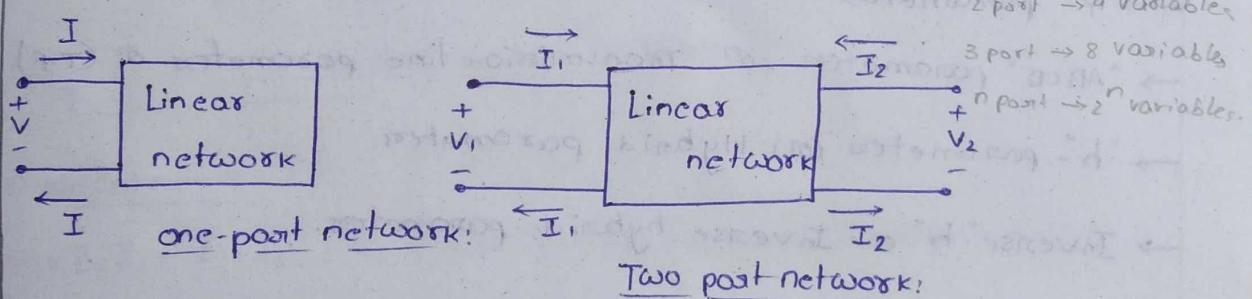Port \rightarrow A pair of terminals which are accessible for external connection.



2 Reasons why to study two port network:

1. Such networks are useful in communication, control system,

power systems and electronics.

2. Knowing the parameters of a two-port network enables us to treat it as a "black box" when embedded within a larger network.

From the network, we can observe that there are 4 variables that is I_1 , I_2 , V_1 and V_2 , which two are independent.

The various term that relate these voltages and currents are called parameters.

$$\left. \begin{array}{l} V_1 \\ I_1 \end{array} \right\} \text{dependent} \quad \left. \begin{array}{l} V_2 \\ I_2 \end{array} \right\} \text{Independent} \quad \text{variables} \longrightarrow ①$$

$\begin{cases} I_1 \\ I_2 \end{cases}$ dependent $\begin{cases} V_1 \\ V_2 \end{cases}$ Independent variables \rightarrow ②

$\begin{cases} V_1 \\ V_2 \end{cases}$ dependent $\begin{cases} I_1 \\ I_2 \end{cases}$ Independent variables \rightarrow ③.

$\begin{cases} V_2 \\ I_2 \end{cases}$ dependent $\begin{cases} V_1 \\ I_1 \end{cases}$ Independent \rightarrow ④

$\begin{cases} V_1 \\ I_2 \end{cases}$ dependent $\begin{cases} V_2 \\ I_1 \end{cases}$ Independent \rightarrow ⑤

$\begin{cases} I_1 \\ V_2 \end{cases}$ dependent $\begin{cases} V_1 \\ I_2 \end{cases}$ Independent variables \rightarrow ⑥

\therefore six set of parameters.

\rightarrow "Z" parameters

\rightarrow "Y" parameters

\rightarrow "ABCD" parameters or Transmission line parameters or (T.P)

\rightarrow "h" - parameters (or) Hybrid parameters.

\rightarrow Inverse "h" or Inverse hybrid parameters.

i) Z parameters:

$\begin{cases} V_1 \\ V_2 \end{cases}$ Dependent $\begin{cases} I_1 \\ I_2 \end{cases}$ Independent variables.

$$V_1 = Z_{11} I_1 + Z_{12} I_2 \quad \rightarrow ①$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2 \quad \rightarrow ②$$

$$Z_{11} = \frac{V_1}{I_1}, \quad Z_{12} = \frac{V_1}{I_2}, \quad Z_{21} = \frac{V_2}{I_1}, \quad Z_{22} = \frac{V_2}{I_2}$$

Z parameters are also called "open circuit characteristics"


$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$ To find $Z_{11}, Z_{21}, Z_{12}, Z_{22}$ we need to open circuit the port 1 & port 2.

$Z_{11} \rightarrow$ input driving point impedance.

$Z_{12} \rightarrow$ Transfer impedance from port 1 to port 2.

Before starting actual analysis of two port network, it is necessary to assume following:

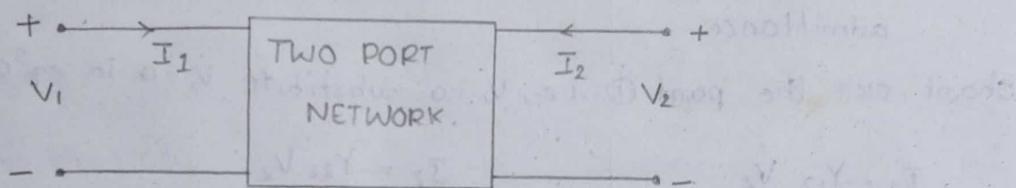1. The voltages and current in the actual network inside box are not available for the measurements. In other words, the measurements can be made on a box consisting network using only port variables.
2. The network inside the box is assumed to consist only the linear elements. Also the network may consist dependent sources but independent sources are not allowed.
3. If the network consists energy storing elements such as inductor and capacitor, then the initial condition on them is assumed to be zero.




Two port network with standard positive port voltages and currents.

Z parameters:


$$V_1 = Z_{11}I_1 + Z_{12}I_2 ; V_2 = Z_{21}I_1 + Z_{22}I_2$$

$I_2 = 0$	$I_1 = 0$
$Z_{11} = V_1/I_1$	$Z_{12} = V_1/I_2$
$Z_{21} = V_2/I_1$	$Z_{22} = V_2/I_2$

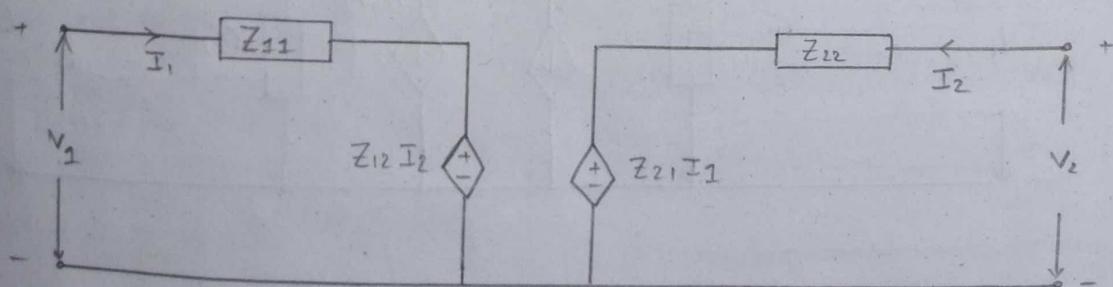Equivalent circuit of Z-parameters eqn's:



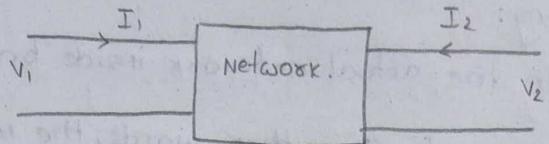2) Y -parameters (or) admittance parameters (or) short ckt parameters



I_1, I_2 acts as dependent; V_1, V_2 acts as independent variables.

$$I_1 = Y_{11} V_1 + Y_{12} V_2 \rightarrow ①$$

$$I_2 = Y_{21} V_1 + Y_{22} V_2 \rightarrow ②$$

Short ckt the point ② i.e., $V_2 = 0$. substitute $V_2 = 0$ in eq ① & ②

$$I_1 = Y_{11} V_1$$

$$Y_{11} = I_1 / V_1$$

input driving point
admittance

$$I_2 = Y_{21} V_1$$

$$Y_{21} = I_2 / V_1$$

Transfer impedance, admittance

Short ckt the point ① i.e., $V_1 = 0$. substitute $V_1 = 0$ in eq ① & ②

$$I_1 = Y_{12} V_2$$

$$Y_{12} = I_1 / V_2$$

Transfer admittance

$$I_2 = Y_{22} V_2$$


$$Y_{22} = I_2 / V_2$$

output driving point admittance.

In Matrix form;

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

Equivalent circuit of y -parameters:

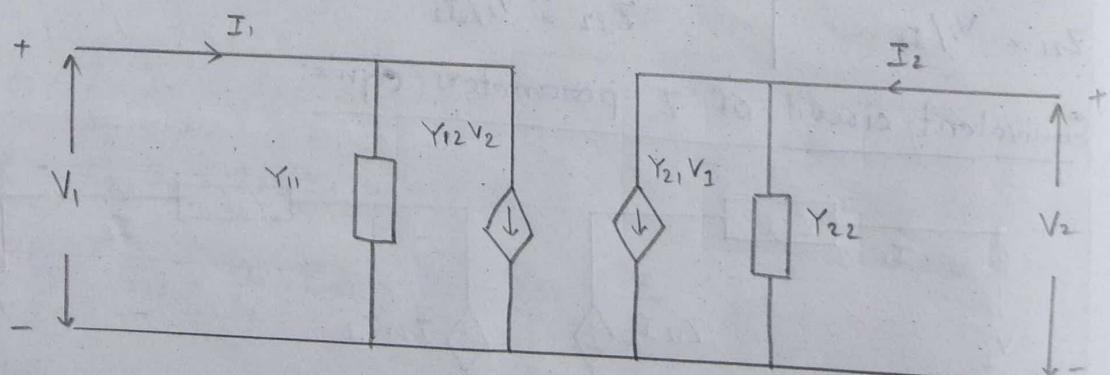

Eg ① Find the Z parameters for the network shown below.

Sol: Method ①:

Z parameters eqns are

$$V_1 = Z_{11} I_1 + Z_{12} I_2$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2$$

Point ② is open circuited i.e., put $I_2 = 0$:-

$$Z_{11} = \frac{V_1}{I_1}; \quad Z_{21} = \frac{V_2}{I_1}$$

$$V_1 = I_1 R_{eq} \Rightarrow I_1 [3 + 10] \Rightarrow 13 I_1$$

$$\therefore Z_{11} = \frac{V_1}{I_1} = 13 \Omega$$

$$V_2 = I_1 \times 10$$

$$\therefore Z_{21} = \frac{V_2}{I_1} = 10 \Omega$$

Point ① is open circuited i.e., put $I_1 = 0$:-

$$Z_{22} = \frac{V_2}{I_2}; \quad V_{12} = \frac{V_1}{I_2}$$

$$V_2 = I_2 R_{eq} \Rightarrow I_2 (10 + 5) \Rightarrow 15 I_2$$


$$\therefore Z_{22} = \frac{V_2}{I_2} = 15 \Omega$$

$$V_1 = 10 I_2$$

$$\therefore Z_{12} = \frac{V_1}{I_2} = 10 \Omega$$

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 13\Omega & 10\Omega \\ 10\Omega & 15\Omega \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

Z parameters

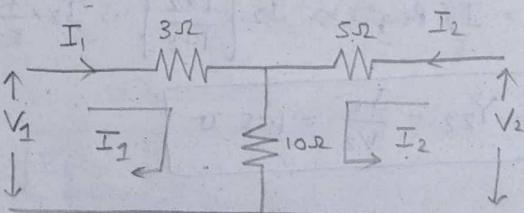

Method ②:

Apply KVL to loop ①

$$3I_1 + 10[I_1 + I_2] = V_1$$

$$V_1 = 13I_1 + 10I_2 \rightarrow ①$$

Apply KVL to loop ②

$$5I_2 + 10[I_2 + I_1] = V_2$$

$$V_2 = 10I_1 + 15I_2 \rightarrow ②$$

Compare the eqn ① & ② with Z parameters equations.


$$\therefore Z_{11} = 13 \Omega \quad Z_{12} = 10 \Omega$$

$$Z_{21} = 10 \Omega \quad Z_{22} = 15 \Omega$$

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 13\Omega & 10\Omega \\ 10\Omega & 15\Omega \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

$\underbrace{\hspace{1cm}}$
Z-parameters

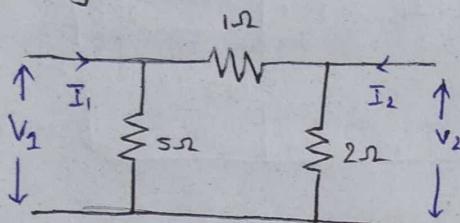Eg. ② Find "y" parameters for the network shown below.



Sol:


$$\text{Method ①: } I_1 = Y_{11}V_1 + Y_{12}V_2$$

$$I_2 = Y_{21}V_1 + Y_{22}V_2$$

Take $V_2 = 0$ i.e., short circuit the port ②


$$V_1 = I_1 \text{ (Req)} \Rightarrow I_1 \left[\frac{1 \times 5}{1+5} \right] \Rightarrow I_1 = \frac{5}{6} V_1$$
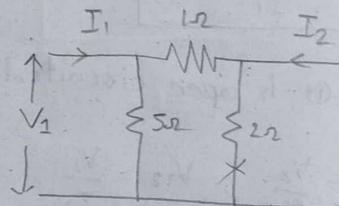
$$\therefore \frac{I_1}{V_1} = \frac{6}{5} \quad \boxed{Y_{11} = 1.2 \text{ v}}$$



$$I_2 = -I_1 \times \frac{5}{1+5}$$

$$V_1 = -1 I_2$$

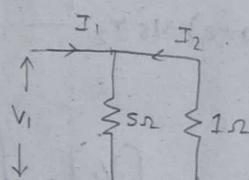


$$\boxed{Y_{21} = \frac{I_2}{V_1} = -1 \text{ v}}$$

Take $V_1 = 0$ i.e., short circuit the port ①.


$$V_2 = I_2 \text{ Req} \Rightarrow I_2 \left[\frac{1 \times 2}{1+2} \right] \Rightarrow I_2 = \frac{2}{3} V_2$$
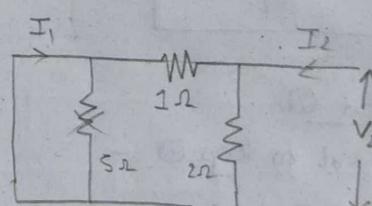
$$\therefore Y_{22} = \frac{I_2}{V_2} = 1.5 \text{ v}$$




$$V_2 = 4I_1$$
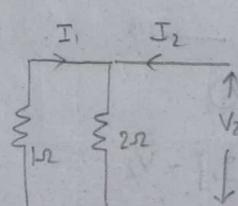
$$\therefore Y_{12} = \frac{I_1}{V_2} = -1 \text{ v}$$



$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 1.2 \text{ v} & -1 \text{ v} \\ -1 \text{ v} & 1.5 \text{ v} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

Method ②:

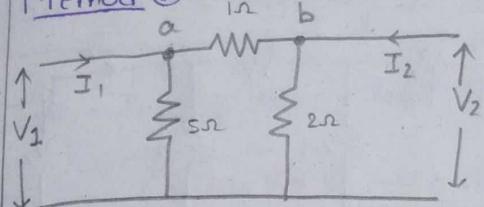

Consider a, b are 2 nodes.

$$\text{Apply KCL to node "a": } I_1 = \frac{V_1}{1} + \frac{V_1 - V_2}{1} \Rightarrow V_1 \left[\frac{1}{1} + 1 \right] + V_2 (-1)$$

$$\therefore I_1 = 1.2 V_1 + V_2 (-1) \rightarrow ①$$


$$\text{Apply KCL to node "b": } I_2 = \frac{V_2}{3} + \frac{V_2 - V_1}{1} \Rightarrow V_1 (-1) + V_2 \left[1 + \frac{1}{3} \right]$$

$$\therefore I_2 = V_1 (-1) + V_2 (1.3) \rightarrow ②$$

Compose the γ parameter equation with equations ① & ②.


$$Y_{11} = 1.2 \Omega, Y_{12} = -1 \Omega, Y_{21} = -1 \Omega, Y_{22} = 1.5 \Omega$$

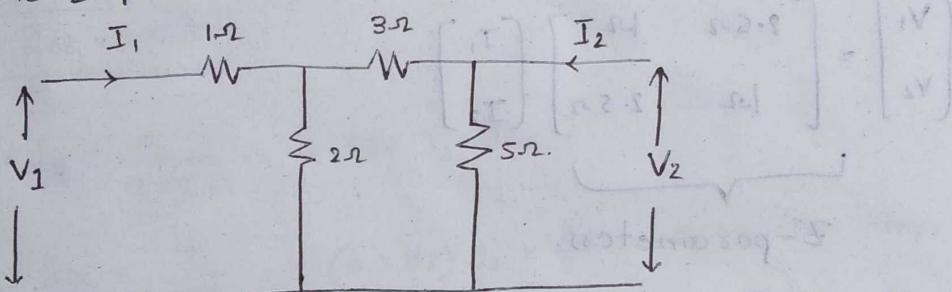Eg ③ Find the Z-parameters for the circuit shown in figure.



Sol: The equations are ① $V_1 = Z_{11} I_1 + Z_{12} I_2$; ② $V_2 = Z_{21} I_1 + Z_{22} I_2$.

① open ckt the port ② i.e., $I_2 = 0$.

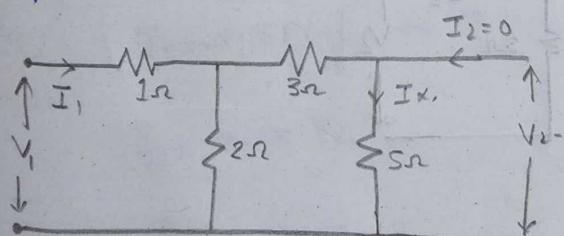

$$V_1 = I_1, \text{Req}$$

$$V_1 = I_1 \left[\left(3 + s \right) / 2 \right] + 1$$

$$V_1 = I_1 \cdot 2 \cdot 6$$

$$Z_{11} = \frac{V_1}{I_1} = 2 \cdot 6$$

$$Z_{11} = \frac{V_1}{I_1}, Z_{21} = \frac{V_2}{I_1}$$

$$\therefore Z_{11} = 2.6 \Omega$$

I_x can be find out by using current division rule.


$$I_x = I_1 \times \frac{2}{2+3+s} = 0.2 I_1$$

$$V_2 = s \times (0.2 I_1) \Rightarrow 1 I_1 \quad \therefore \frac{V_2}{I_1} = Z_{21} = 1.2 \quad \therefore Z_{21} = 1.2$$

② Open circuit port ① i.e., $I_1 = 0$.

$$Z_{22} = \frac{V_2}{I_2}; Z_{12} = \frac{V_1}{I_2}$$

$$V_2 = I_2 R_{eq}$$

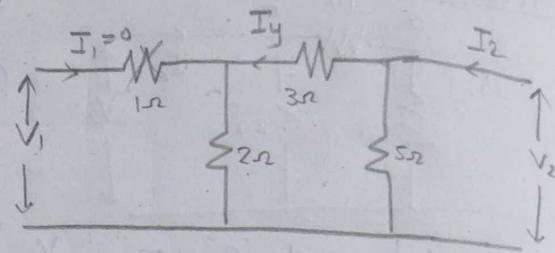

$$R_{eq} = (2+3)/2 = 2.5\Omega$$

$$\therefore \frac{V_2}{I_2} = 2.5\Omega \quad [Z_{22} = 2.5\Omega]$$

$$V_1 = I_y 2$$

I_y can be found out by taking current division rule.

$$I_y = I_2 \times \frac{5}{5+2+3} = 0.5 I_2$$


$$\therefore V_1 = 2(0.5 I_2) = I_2$$

$$\therefore \frac{V_1}{I_2} = 1\Omega \quad [Z_{12} = 1\Omega]$$

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 2.5\Omega & 1\Omega \\ 1\Omega & 2.5\Omega \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

Z-parameters.

Eg: ④ Find y parameters.

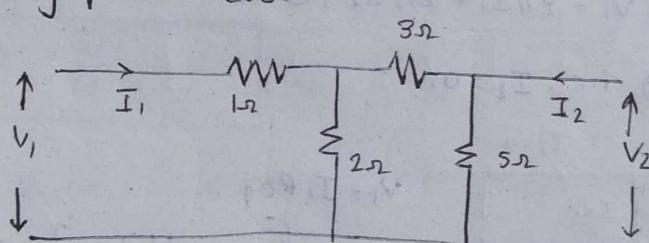

Sol:

$$I_1 = Y_{11} V_1 + Y_{12} V_2$$

$$I_2 = Y_{21} V_1 + Y_{22} V_2$$

Step ①: Short ckt the port, $V_2 = 0$.


$$Y_{11} = \frac{I_1}{V_1}; Y_{21} = \frac{I_2}{V_1}$$

$$V_1 = I_1 R_{eq}$$

$$V_1 = I_1 [2/13 + 1]$$

$$Y_{11} = 2.2\Omega$$
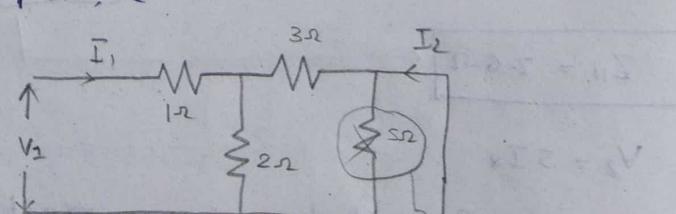
$$\therefore \frac{I_1}{V_1} = \frac{1}{2.2} = 0.45\Omega$$



neglected

$$Y_{11} = \frac{I_1}{V_1} = 0.45 \text{ mho.} \Rightarrow I_1 = 0.45 V_1$$

$$I_2 = -I_1 \cdot \frac{2}{2+3} \Rightarrow -I_1(0.4) \xrightarrow{\text{substitute above } I_1 \text{ value in this eqn}} I_2 = -(0.45V_1)(0.4) \Rightarrow 0.18V_1$$

$$\therefore \frac{I_2}{V_1} = -0.18.$$

$$Y_{21} = -0.18$$

Step ②: short circuit the port ①; $V_1 = 0$.

$$Y_{12} = \frac{I_1}{V_2}; Y_{22} = \frac{I_2}{V_2}.$$

$$I_2 = V_2 / Z_{\text{eq}} \Rightarrow V_2 \left[((1/2) + 3) // s \right]$$

$$I_2 = V_2 / (3.66 // s) \Rightarrow V_2 / 2.11$$

$$\therefore \frac{I_2}{V_2} = \frac{1}{2.11} \Rightarrow 0.47 \text{ V}$$

$$\therefore Z_{22} = 0.47$$

$$I_x = +I_y \times \frac{s}{5+3.66} \Rightarrow 0.577 I_2 \text{ Amps}$$

$$\therefore I_y = I_x \times \frac{2}{1+2} \Rightarrow (0.577) I_2 \times \frac{2}{3} \Rightarrow 0.381 I_2 \text{ Amps.}$$

$$\therefore I_1 = -I_y = -0.381 I_2$$

$$I_1 = -0.381 [0.47 V_2]$$


$$I_1 = -0.18 V_2$$

$$\therefore \frac{I_1}{V_2} = -0.18$$


$$Y_{12} = -0.18$$

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \underbrace{\begin{bmatrix} 0.45V_1 & -0.18V_1 \\ -0.18V_1 & 0.47V_2 \end{bmatrix}}_{Y\text{-parameters.}} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

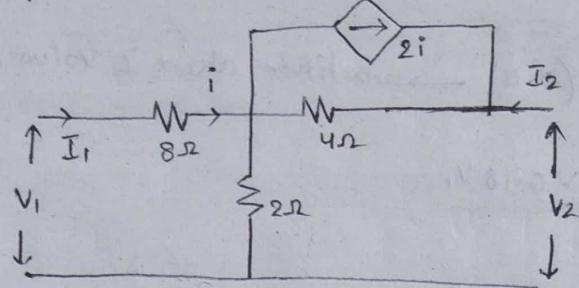Eg: ⑤ find Z-parameters for the network shown below.



Sol:

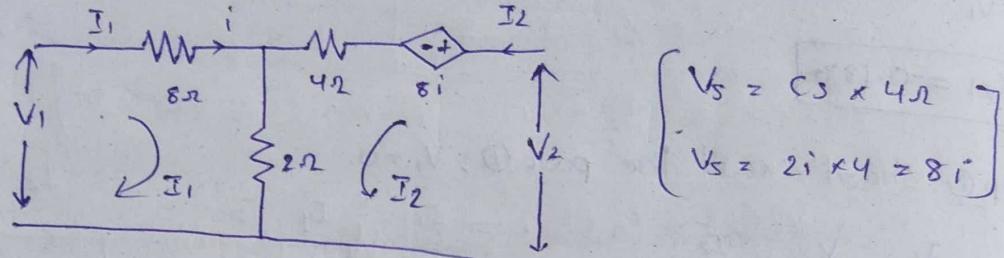

Step ①: apply KVL to the port ②, port ①:

$$V_1 = 8I_1 + 2(I_1 + I_2) \Rightarrow 10I_1 + 2I_2 \rightarrow ①$$


$$V_2 = 8i + 4I_2 + 2(I_2 + I_1) \Rightarrow 8I_1 + 4I_2 + 2I_2 + 2I_1$$

$$V_2 = 10I_1 + 6I_2 \rightarrow ②$$

Compare the eqn's ① & ② with Z-parameter equations.

$$Z = \begin{bmatrix} 10\Omega & 2\Omega \\ 10\Omega & 6\Omega \end{bmatrix}$$

Eg: ⑥ find Z parameters.

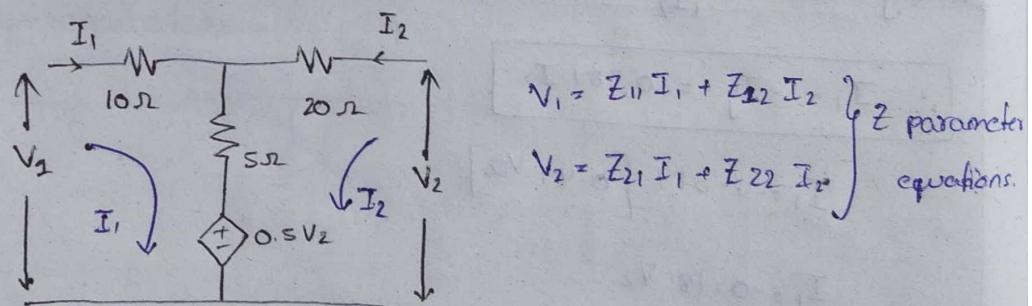

Apply KVL to both loops;

$$V_1 = 10I_1 + 5(I_1 + I_2) + 0.5V_2 \Rightarrow 15I_1 + 5I_2 + 0.5V_2 \rightarrow ①$$

$$V_2 = 20I_2 + 5(I_2 + I_1) + 0.5V_2 \Rightarrow 5I_1 + 25I_2 + 0.5V_2$$

$$V_2 - 0.5V_2 = 5I_1 + 25I_2$$

$$0.5V_2 = 5I_1 + 25I_2 \rightarrow ②$$

$$V_2 = 10I_1 + 50I_2 \rightarrow ③$$

Substitute eqn ② in eqn ①.

$$V_1 = 1S I_1 + S I_2 + 0.5 V_2 \Rightarrow 1S I_1 + S I_2 + [S I_1 + 2S I_2]$$


$$V_1 = 20 I_1 + 30 I_2 \rightarrow ④$$

Combine eqn ③ & ④ with Z parameter equation.

$$\therefore Z_{11} = 20 \Omega, Z_{12} = 30 \Omega, Z_{21} = 10 \Omega, Z_{22} = 50 \Omega.$$

$$Z = \begin{bmatrix} 20 \Omega & 30 \Omega \\ 10 \Omega & 50 \Omega \end{bmatrix}$$

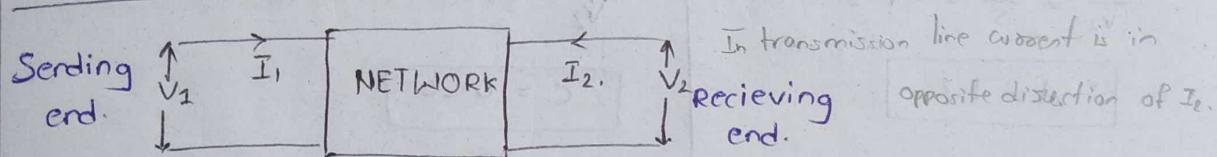③ ABCD parameters (or) Transmission line (or) General parameters:



$$\left. \begin{array}{l} V_1 = AV_2 - BI_2 \rightarrow ① \\ I_1 = CV_2 - DI_2 \rightarrow ② \end{array} \right\} \text{General or chain parameters.}$$

① Take $I_2 = 0$ i.e., open circuit the point ②.

$$\left. \begin{array}{l} V_1 = AV_2 \\ A = \frac{V_1}{V_2} \end{array} \right| \quad \left. \begin{array}{l} I_1 = CV_2 \\ C = \frac{I_1}{V_2} \end{array} \right|$$

↓ ↓

reverse gain (ratio) transfer admittance (Y)

voltage

② Take $V_2 = 0$ i.e., short circuit the point ②.

$$\left. \begin{array}{l} V_1 = -BI_2 \\ B = -\frac{V_1}{I_2} \end{array} \right| \quad \left. \begin{array}{l} I_1 = -DI_2 \\ D = -\frac{I_1}{I_2} \end{array} \right|$$


↓ ↓

transfer impedance reverse current gain (ratio)

$\therefore \frac{1}{D} = \text{forward current gain.}$

$\therefore \frac{1}{A} = \text{forward voltage gain.}$

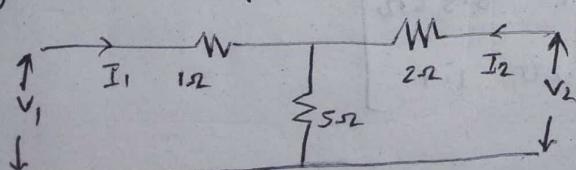Ex. ⑦ Find the general CKT parameters for network shown below.



$$V_1 = AV_2 - BI_2$$

$$I_1 = CV_2 - DI_2.$$

① Open ckt the port ② i.e., $I_2 = 0$.


$$V_1 = I_1 R_{eq}$$

$$\frac{V_1}{I_1} = R_{eq} = (1 + 5) = 6\Omega$$

$$\frac{V_1}{V_2} = 6\Omega$$

$$\frac{V_1}{V_2} = \frac{6}{5} = 1.2 = A$$

$$\therefore A = 1.2$$

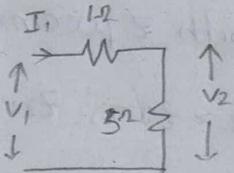

$$\therefore V_2 = 5I_1$$

$$\therefore I_1 = \frac{V_2}{5}$$

$$\frac{I_1}{V_2} = \frac{1}{5} = 0.2\Omega = C$$

$$\therefore C = 0.2\Omega$$

② short ckt the port ② i.e., $V_2 = 0$.


$$D = -\frac{I_1}{I_2}$$

$$B = -\frac{V_1}{I_2}$$

$$I_2 = -I_1 \left(\frac{5}{5+1} \right) = -I_1 / 1.4$$

$$\therefore \frac{I_2}{I_1} = -\frac{1}{1.4}$$
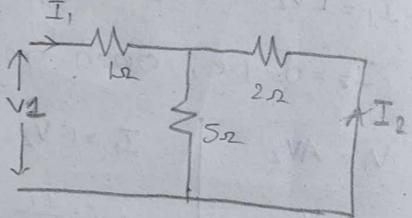
$$\frac{I_1}{I_2} = -1.4 = D \quad \boxed{\therefore D = -1.4}$$



$$V_1 = I_1 (R_{eq}) \Rightarrow I_1 \left([2/1.5] + 1 \right) \Rightarrow I_1 (2.4)$$

$$V_1 = I_1 (2.4)$$

$$V_1 = (I_2 \times -1.4) (2.4)$$

$$\frac{V_1}{I_2} = -3.36\Omega$$

$$-\frac{V_1}{I_2} = -(-3.36\Omega) = 3.36\Omega$$

$$\boxed{\therefore B = 3.36\Omega}$$

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} 1.2 & 3.36\Omega \\ 0.2\Omega & 1.4 \end{bmatrix}$$

For inverse transmission line parameters:-

$$V_2 = A' V_1 - B' I_1$$

$$I_2 = C' V_1 - D' I_1$$

(4) Hybrid parameters or H-parameters:

These are widely used in modelling of electronic component

i.e., particularly transistors.

$$V_1 = h_{11} I_1 + h_{12} V_2$$

$$I_2 = h_{21} I_1 + h_{22} V_2$$

① short circuit the point ② i.e., $V_2 = 0$.


$$h_{11} = \frac{V_1}{I_1} \quad (\text{Input impedance}) ; \quad h_{21} = \frac{I_2}{V_2} \quad [\text{Current gain}]$$

② open circuit the point ① i.e., $I_1 = 0$.

$$h_{22} = \frac{I_2}{V_2} \quad h_{12} = \frac{V_1}{V_2} \quad [\text{voltage gain}]$$

(output admittance)

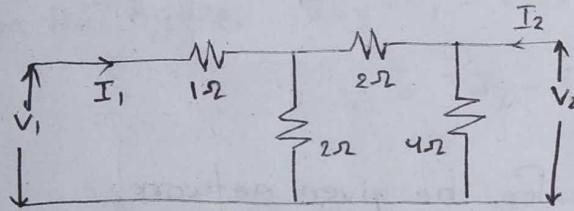Eg: Find the "h" parameters for the given circuit.




$$V_1 = h_{11} I_1 + h_{12} [V_2]$$

$$I_2 = h_{21} I_1 + h_{22} V_2$$

① short circuit the point ② $V_2 = 0$.

$$h_{11} = \frac{V_1}{I_1} \quad | \quad h_{21} = \frac{I_2}{I_1}$$
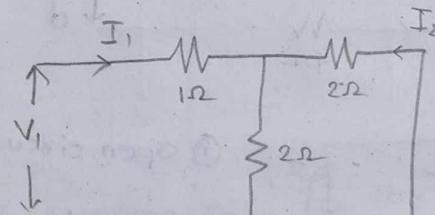
$$V_1 = I_1 (R_{eq}) \Rightarrow I_1 \left[1 + 2/\frac{1}{2} \right]$$




$$\therefore \frac{V_1}{I_1} = 2\Omega \quad \boxed{h_{11} = 2\Omega}$$

$$-I_2 = I_1 \left(\frac{2}{2+2} \right) = I_1 \frac{2}{4}$$

$$\frac{I_2}{I_1} = -\frac{1}{2} = -0.5$$

$$\boxed{h_{21} = -0.5}$$

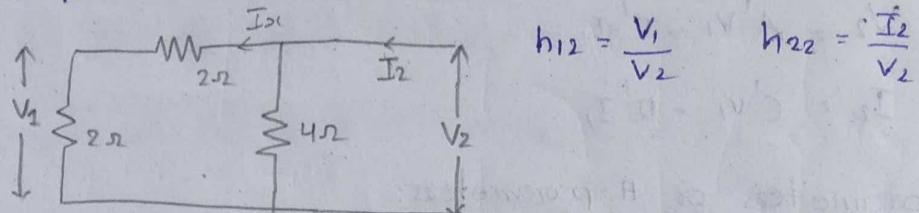② Open circuit the part ①, i.e., $I_2 = 0$. ($I_1 = 0$)



$$h_{12} = \frac{V_1}{V_2} \quad h_{22} = \frac{I_2}{V_2}$$

$$V_2 = I_2 (Req) \Rightarrow I_2 \left((2+2)/4 \right) \Rightarrow 2I_2.$$

$$\frac{V_2}{I_2} = 2 \Rightarrow \frac{I_2}{V_2} = \frac{1}{2} = 0.5 \text{ v} \quad (\therefore I_2 = 0.5V_2)$$

$$\therefore h_{22} = 0.5 \text{ v}$$

$$V_1 = 2I_{2c} \Rightarrow 2 \left[I_2 \times \frac{4}{4+4} \right] \Rightarrow 2 \left[I_2 \times \frac{1}{2} \right]$$

$$V_1 = I_2$$


$$V_1 = 0.5V_2$$

$$\frac{V_1}{V_2} = 0.5$$

$$h_{12} = 0.5$$

$$h = \begin{bmatrix} 2 & +0.5 \\ -0.5 & 0.5 \end{bmatrix}$$

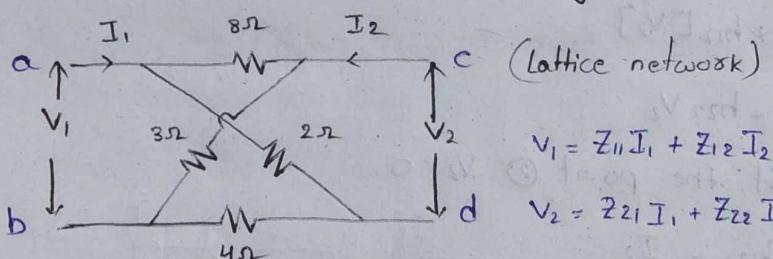
Eg. ⑨ Find out the Z-parameters for the given network.



$$V_1 = Z_{11}I_1 + Z_{12}I_2$$

$$V_2 = Z_{21}I_1 + Z_{22}I_2$$

Sol:

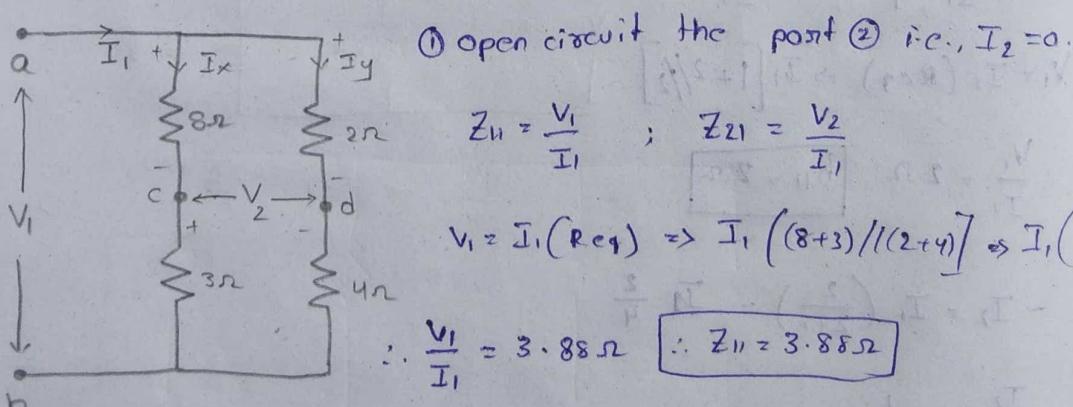

① Open circuit the point ② i.e., $I_2 = 0$.

$$Z_{11} = \frac{V_1}{I_1} ; \quad Z_{21} = \frac{V_2}{I_1}$$

$$V_1 = I_1 (Req) \Rightarrow I_1 \left((8+3)/(2+4) \right) \Rightarrow I_1 (1/6)$$

$$\therefore \frac{V_1}{I_1} = 3.88 \Omega \quad \therefore Z_{11} = 3.88 \Omega$$

$$(V_2 = 2(I_y) - 8(I_x))$$

$$\text{from the fig: } 2I_y - V_2 - 8I_x = 0.$$

$$V_2 = 2Iy - 8Ix \Rightarrow 2 \left[I_1 \left(\frac{6}{6+11} \right) \right] - 8 \left[I_1 \left(\frac{6}{6+11} \right) \right]$$

$$\therefore V_2 \Rightarrow 2I_1 \left[\frac{11}{17} \right] - 8I_1 \left[\frac{6}{17} \right]$$

$$V_2 = I_1 \left[\frac{22}{17} \right] - I_1 \left[\frac{48}{17} \right] \Rightarrow I_1 \left[\frac{22-48}{17} \right] \Rightarrow I_1 \left[\frac{-26}{17} \right]$$

$$\therefore \frac{V_2}{I_1} = -1.52 \Omega$$


$$\therefore Z_{21} = -1.52 \Omega$$

② open circuit the port ①, i.e., $I_1 = 0$.

$$Z_{12} = \frac{V_1}{I_2} \quad | \quad Z_{22} = \frac{V_2}{I_2}$$

$$\therefore V_2 = I_2 (R_{eq}) \Rightarrow I_2 (10/17)$$
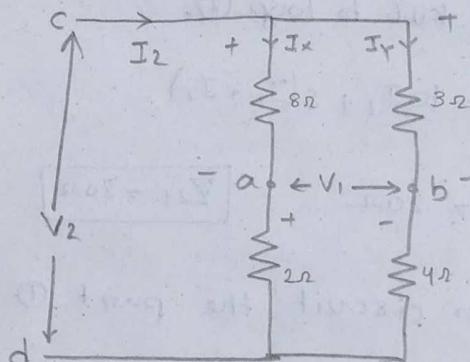
$$\frac{V_2}{I_2} = \frac{10 \times 7}{10+7} \Rightarrow \frac{70}{17} \Rightarrow 4.11 \Omega$$



$$\therefore Z_{22} = 4.11 \Omega$$

From the figure, $3Iy - V_1 - 8Ix = 0$


$$V_1 = 3Iy - 8Ix \Rightarrow 3 \left[I_2 \frac{10}{10+7} \right] - 8 \left[I_2 \frac{7}{10+7} \right]$$

$$\therefore \frac{V_1}{I_2} = \frac{30}{17} - \frac{56}{17} \Rightarrow -\frac{26}{17} = -1.52 \Omega$$

$$\therefore Z_{12} = -1.52 \Omega$$

$$Z \Rightarrow \begin{bmatrix} 3.88 \Omega & -1.52 \Omega \\ -1.52 \Omega & 4.11 \Omega \end{bmatrix}$$

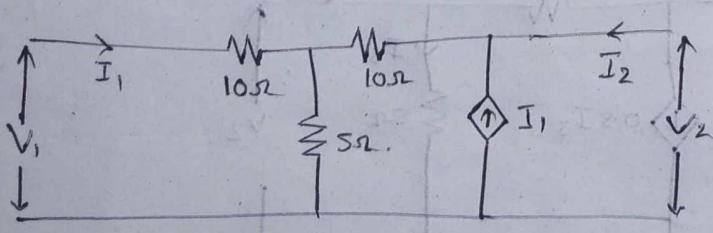Q: Determine the open circuit parameters for the given network.




$$V_1 = Z_{11} I_1 + Z_{12} I_2$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2$$

① Open circuit the port ② i.e., $I_2 = 0$.
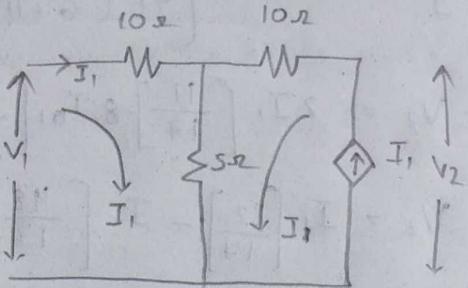
$$Z_{11} = \frac{V_1}{I_1} \quad Z_{21} = \frac{V_2}{I_1}$$



Apply KVL to loop ①

$$V_1 = 10I_1 + 5(I_1 + I_2)$$

$$V_1 = 10I_1 + 10I_1$$

$$\frac{V_1}{I_1} = 20\Omega \quad \therefore Z_{11} = 20\Omega$$

Apply KVL to loop ②.

$$V_2 = 10I_1 + 5(I_1 + I_2)$$


$$\frac{V_2}{I_1} = 20\Omega \quad \therefore Z_{21} = 20\Omega$$

② Open circuit the port ① i.e., $I_1 = 0$.

$$V_2 = I_2 (5\Omega)$$

$$\frac{V_2}{I_2} = 10 + 5 = 15\Omega$$

$$\therefore Z_{22} = 15\Omega$$

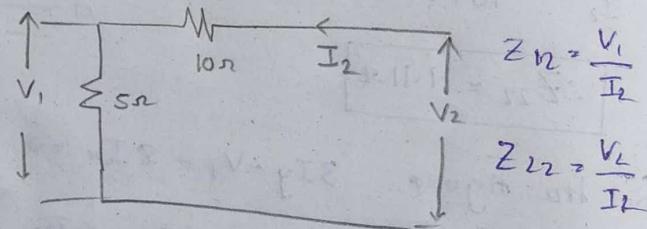


$$V_1 = 5I_2$$

$$\frac{V_1}{I_2} = 5\Omega \quad \therefore Z_{12} = 5\Omega$$

$$Z = \begin{bmatrix} 20\Omega & 5\Omega \\ 5\Omega & 15\Omega \end{bmatrix}$$

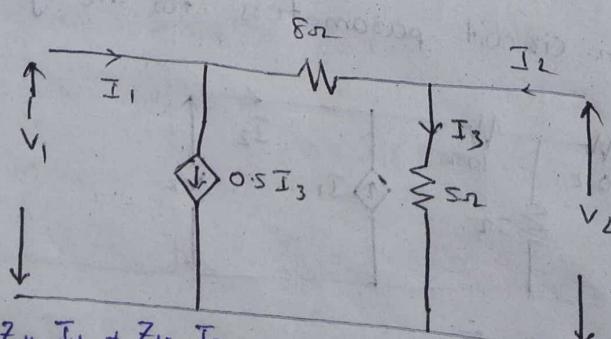Eg 11. A network shown below obtain open circuit parameters.



$$(V_1) = Z_{11} I_1 + Z_{12} I_2$$

$$(V_2) = Z_{21} I_1 + Z_{22} I_2$$

① Open ckt the port ② i.e., $I_2 = 0$.


$$Z_{11} = \frac{V_1}{I_1}, \quad Z_{21} = \frac{V_2}{I_1}$$

$$V_1 = 8I_3 + 5I_3$$

$$V_1 = 13I_3 \Rightarrow 13\left(\frac{I_1}{1.5}\right)$$

$$\frac{V_1}{I_1} = 8.66\Omega$$

$$Z_{11} = 8.66\Omega$$

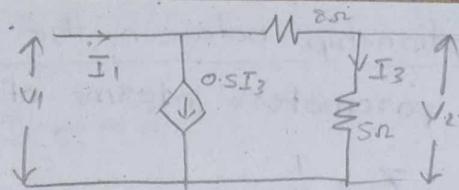

$$\begin{cases} I_1 = 0.5I_3 + I_3 \\ I_1 = 1.5I_3 \\ I_3 = \frac{I_1}{1.5} \end{cases}$$

$$V_2 = 5I_3 \Rightarrow 5\left(\frac{I_1}{1.5}\right)$$

$$\frac{V_2}{I_1} = 3.33\Omega$$

$$Z_{21} = 3.33\Omega$$

② Open ckt the port ① i.e., $I_1 = 0$.

$$Z_{12} = \frac{V_1}{I_2}, \quad Z_{22} = \frac{V_2}{I_2}$$

$$I_2 = I_3 + 0.5I_3$$

$$I_2 = I_3 (1.5)$$

$$I_3 = \frac{I_2}{1.5}$$

$$V_2 = 5I_3 = 5\left(\frac{I_2}{1.5}\right) \Rightarrow \frac{V_2}{I_2} = \frac{5}{1.5} = 3.33$$

$$V_2 = 8(0.5I_3) + V_1$$

$$\therefore Z_{22} = 3.33\Omega$$

$$V_2 = 8\left(0.5 \times \frac{I_2}{1.5}\right) + V_1$$

$$3.33I_2 - 2.66I_2 = V_1$$

$$V_1 = 0.66I_2$$

$$\frac{V_1}{I_2} = 0.66\Omega \quad \therefore Z_{12} = 0.66\Omega$$

$$Z = \begin{bmatrix} 8.66\Omega & 0.66\Omega \\ 3.33\Omega & 3.33\Omega \end{bmatrix}$$

Relationship between the parameters:

i) a) Z parameters in terms of Y parameters.

$$Z = \frac{1}{Y}$$

$$[Z] = [Y]^{-1}$$

$$\begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} = \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix}^{-1} \Rightarrow \frac{1}{\Delta Y} \begin{bmatrix} Y_{22} & -Y_{12} \\ -Y_{21} & Y_{11} \end{bmatrix}$$

$$\text{Where } \Delta Y = Y_{11}Y_{22} - Y_{12}Y_{21}$$

$$Z_{11} = \frac{Y_{22}}{\Delta Y}; \quad Z_{12} = -\frac{Y_{12}}{\Delta Y}; \quad Z_{21} = -\frac{Y_{21}}{\Delta Y}; \quad Z_{22} = \frac{Y_{11}}{\Delta Y}.$$

b) Z parameters in terms of ABCD parameters:-

Eq's of ABCD parameters.

$$V_1 = AV_2 - BI_2 \rightarrow ①$$

$$I_1 = CV_2 - DI_2 \rightarrow ②$$

Z parameter equations.

$$V_1 = Z_{11}I_1 + Z_{12}I_2$$

$$V_2 = Z_{21}I_1 + Z_{22}I_2.$$

from eq ②

$$CV_2 = I_1 + D I_2.$$

$$V_2 = \frac{1}{C}I_1 + \frac{D}{C}I_2 \rightarrow ③$$

Substitute eq ③ in eq ①.

$$V_1 = A \left[\frac{1}{C}I_1 + \frac{D}{C}I_2 \right] - BI_2 \Rightarrow I_1 \frac{A}{C} + I_2 \left[\frac{AD-BC}{C} \right] I_2$$

$$V_1 = I_1 \left[\frac{A}{C} \right] + I_2 \left[\frac{AD-BC}{C} \right] \rightarrow ④$$

Compare the eq ③ & ④ with Z parameter equations.

$$\boxed{\begin{aligned} Z_{11} &= \frac{A}{C} & Z_{12} &= \frac{AD-BC}{C} \\ Z_{21} &= \frac{1}{C} & Z_{22} &= \frac{D}{C} \end{aligned}}$$

c) Parameters (Z) in terms of h-parameters.

$$V_1 = h_{11}I_1 + h_{12}V_2 \rightarrow ①$$

$$I_2 = h_{21}I_1 + h_{22}V_2 \rightarrow ②$$

$$\begin{aligned} V_1 &= Z_{11}I_1 + Z_{12}I_2 \\ V_2 &= Z_{21}I_1 + Z_{22}I_2 \end{aligned} \quad \left. \begin{array}{l} \text{Z parameter} \\ \text{equations} \end{array} \right\}$$

from eq ②

$$h_{22}V_2 = -h_{21}I_1 + I_2$$

$$\therefore V_2 = -\frac{h_{21}}{h_{22}}I_1 + \frac{1}{h_{22}}I_2 \rightarrow ③$$

Substitute eq ③ in ①.

$$V_1 = h_{11}I_1 + h_{12} \left[-\frac{h_{21}}{h_{22}}I_1 + \frac{1}{h_{22}}I_2 \right]$$

$$V_1 = h_{11} I_1 + \frac{h_{12} \times -h_{21}}{h_{22}} I_1 + \frac{h_{22}}{h_{22}} I_2$$

$$V_1 = \left[\frac{h_{11}h_{22} - h_{12}h_{21}}{h_{22}} \right] I_1 + \left[\frac{h_{22}}{h_{22}} \right] I_2 \rightarrow ④$$

Compare eq' ③ & ④ with Z-parameter equations.

$$Z_{11} = \frac{\Delta h}{h_{22}}, \quad Z_{12} = \frac{1}{h_{22}}, \quad Z_{21} = \frac{-h_{21}}{h_{22}}, \quad Z_{22} = \frac{h_{12}}{h_{22}}$$

a) Y-parameters in terms of z-parameters:

$$[Y] = [Z]^{-1}$$

$$\begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix}^{-1} \Rightarrow \frac{1}{\Delta Z} \begin{bmatrix} Z_{22} & -Z_{12} \\ -Z_{21} & Z_{11} \end{bmatrix}$$

$$Y_{11} = \frac{Z_{22}}{\Delta Z}, \quad Y_{12} = -\frac{Z_{12}}{\Delta Z}, \quad Y_{21} = -\frac{Z_{21}}{\Delta Z}, \quad Y_{22} = \frac{Z_{11}}{\Delta Z}$$

Where; $\Delta Z = Z_{11}Z_{22} - Z_{12}Z_{21}$

b) Y-parameters in terms of ABCD parameters.

Equations of ABCD parameters

Y-parameters eq' 5.

$$V_2 = AV_2 - BI_2 \rightarrow ①$$

$$I_1 = Y_{11}V_1 + Y_{12}V_2$$

$$I_1 = CV_2 - DI_2 \rightarrow ②$$

$$I_2 = Y_{21}V_1 + Y_{22}V_2$$

from eq' ①

$$BI_2 = -V_1 + AV_2$$

$$I_2 = -\frac{1}{B}V_1 + \frac{A}{B}V_2 \rightarrow ③$$

Substitute eq' ③ in eq' ②.

$$I_1 \Rightarrow CV_2 - D \left[-\frac{1}{B}V_1 + \frac{A}{B}V_2 \right] \Rightarrow CV_2 + \frac{D}{B}V_1 - \frac{AD}{B}V_2$$

$$\therefore I_1 = \frac{D}{B}V_1 + \frac{BC-AD}{B}V_2 \rightarrow ④$$

Compare eq' ③ & ④ with Y-parameter equations.

$$Y_{11} = \frac{D}{B}, \quad Y_{12} = \frac{BC-AD}{B}$$

$$Y_{21} = -\frac{1}{B}, \quad Y_{22} = \frac{A}{B}$$

c) Y-parameters in terms of h-parameters:

h-parameters eqn's

Y-parameter eqn's

$$V_1 = h_{11} I_1 + h_{12} V_2 \rightarrow ①$$

$$I_1 = Y_{11} V_1 + Y_{12} V_2$$

$$I_2 = h_{21} I_1 + h_{22} V_2 \rightarrow ②$$

$$I_2 = Y_{21} V_1 + Y_{22} V_2$$

from eqn ①.

$$h_{11} I_1 = V_1 - h_{12} V_2$$

$$I_1 = \frac{1}{h_{11}} V_1 - \frac{h_{12}}{h_{11}} V_2 \rightarrow ③$$

Substitute eqn ③ in eqn ②.

$$I_2 = h_{21} \left[\frac{1}{h_{11}} V_1 - \frac{h_{12}}{h_{11}} V_2 \right] + h_{22} V_2$$

$$I_2 = \frac{h_{21}}{h_{11}} V_1 - \frac{h_{21} h_{12}}{h_{11}} V_2 + h_{22} V_2$$

$$I_2 = \frac{h_{21}}{h_{11}} V_1 + \frac{h_{11} h_{22} - h_{12} h_{21}}{h_{11}} V_2 \rightarrow ④$$

Compare eqn ③ & ④ with Y-parameter equations.

$$\boxed{Y_{11} = \frac{1}{h_{11}} ; Y_{12} = -\frac{h_{12}}{h_{11}} ; Y_{21} = \frac{h_{21}}{h_{11}} ; Y_{22} = \frac{\Delta h}{h_{11}}}$$

3) ABCD parameters in terms of Z-parameters:

Z parameter eqn ⑤

ABCD parameter eqn ⑤

$$V_1 = Z_{11} I_1 + Z_{12} I_2 \rightarrow ①$$

$$V_1 = A V_2 - B I_2$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2 \rightarrow ②$$

$$I_1 = C V_2 - D I_2$$

From eqn ②.

$$Z_{21} I_1 = V_2 - Z_{22} I_2$$

$$I_1 = \left(\frac{1}{Z_{21}} \right) V_2 - \left(\frac{Z_{22}}{Z_{21}} \right) I_2 \rightarrow ③$$

Substitute eqn ③ in eqn ①.

$$V_1 = Z_{11} \left[\frac{V_2}{Z_{21}} - \frac{Z_{22}}{Z_{21}} I_2 \right] + Z_{12} I_2$$

$$V_1 = \frac{Z_{11}}{Z_{21}} V_2 - \frac{Z_{11} Z_{22}}{Z_{21}} I_2 + Z_{12} I_2 \Rightarrow \frac{Z_{11}}{Z_{21}} V_2 = \left[\frac{Z_{11} Z_{22} - Z_{12} Z_{21}}{Z_{21}} \right] I_2 \rightarrow ④$$

Compare the eqn ③ & ④ with ABCD parameters.

$$\boxed{A = \frac{Z_{11}}{Z_{21}} ; B = \frac{\Delta Z}{Z_{21}} ; C = \frac{1}{Z_{21}} ; D = \frac{Z_{22}}{Z_{21}}}$$

b) ABCD parameters in terms of Y-parameters:

Y-parameter eq's

$$I_1 = Y_{11}V_1 + Y_{12}V_2 \rightarrow ①$$

$$I_2 = Y_{21}V_1 + Y_{22}V_2 \rightarrow ②$$

ABCD-parameters.

$$V_1 = AV_2 - BI_2.$$

$$I_1 = CV_2 - DI_2.$$

from eqⁿ ②:-

$$Y_{21}V_1 = -Y_{22}V_2 + I_2$$

$$V_1 = \left[-\frac{Y_{22}}{Y_{21}} \right] V_2 - \left[-\frac{1}{Y_{21}} \right] I_2 \rightarrow ③$$

Substitute eqⁿ ③ in eqⁿ ①.

$$I_1 = Y_{11} \left[-\frac{Y_{22}}{Y_{21}} V_2 + \frac{I_2}{Y_{21}} \right] + Y_{12} V_2 \Rightarrow -\frac{Y_{11}Y_{22}}{Y_{21}} V_2 + I_2 \frac{Y_{11}}{Y_{21}} + Y_{12} V_2$$

$$\therefore I_1 = \frac{Y_{12}Y_{21} - Y_{11}Y_{22}}{Y_{21}} V_2 - \left[-\frac{Y_{11}}{Y_{21}} \right] I_2 \rightarrow ④$$

Compare eqⁿ ③ & ④ with ABCD eqⁿ's

$$A = \frac{-Y_{22}}{Y_{21}} ; B = -\frac{1}{Y_{21}} ; C = -\frac{\Delta Y}{Y_{21}} ; D = -\frac{Y_{11}}{Y_{21}}$$

c) ABCD parameters in terms of H-parameters.

H-parameter equations

$$V_1 = h_{11}I_1 + h_{12}V_2 \rightarrow ①$$

ABCD eqⁿ's

$$V_1 = AV_2 - BI_2.$$

$$I_2 = h_{21}I_1 + h_{22}V_2 \rightarrow ②$$

$$I_1 = CV_2 - DI_2.$$

from eqⁿ ②

$$h_{21}I_1 = I_2 - h_{22}V_2 \Rightarrow I_1 = \left[-\frac{h_{22}}{h_{21}} \right] V_2 - \left[\frac{-1}{h_{21}} \right] I_2 \rightarrow ③$$

Substitute eqⁿ ③ in eqⁿ ①.

$$V_1 = h_{11} \left[-\frac{h_{22}}{h_{21}} V_2 + \frac{I_2}{h_{21}} \right] + h_{12}V_2 \Rightarrow \left[\frac{h_{12}h_{21} - h_{11}h_{22}}{h_{21}} \right] V_2 + \left[\frac{h_{11}}{h_{21}} \right] I_2$$

$$\therefore V_1 = \left[\frac{h_{12}h_{21} - h_{11}h_{22}}{h_{21}} \right] V_2 - \left[-\frac{h_{11}}{h_{21}} \right] I_2 \rightarrow ④$$

Compare eqⁿ ③ & ④ with ABCD parameter equations.

$$A = \frac{h_{12}h_{21} - h_{11}h_{22}}{h_{21}}$$

$$B = -\frac{h_{11}}{h_{21}}$$

$$C = -\frac{h_{22}}{h_{21}}$$

$$D = \frac{-1}{h_{21}}$$

4) a) h-parameters in terms of z-parameters.

WKT, h-parameter eqn's

$$V_1 = h_{11} I_1 + h_{12} V_2$$

$$I_2 = h_{21} I_1 + h_{22} V_2$$

z-parameter equation

$$V_1 = Z_{11} I_1 + Z_{12} I_2 \rightarrow ①$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2 \rightarrow ②$$

From eq' ②.

$$V_2 = Z_{21} I_1 + Z_{22} I_2$$

$$Z_{22} I_2 = V_2 - Z_{21} I_1$$

$$I_2 = \frac{V_2}{Z_{22}} - \frac{Z_{21}}{Z_{22}} I_1 \Rightarrow \left[-\frac{Z_{21}}{Z_{22}} \right] I_1 + \left[\frac{1}{Z_{22}} \right] V_2 \rightarrow ③$$

Substitute eq' ③ in eq' ①.

$$V_1 = Z_{11} I_1 + Z_{12} \left[-\frac{Z_{21}}{Z_{22}} I_1 + \frac{V_2}{Z_{22}} \right]$$

$$= Z_{11} I_1 - \frac{Z_{12} Z_{21}}{Z_{22}} I_1 + \frac{Z_{12}}{Z_{22}} V_2$$

$$V_1 = \left[\frac{Z_{11} Z_{22} - Z_{12} Z_{21}}{Z_{22}} \right] I_1 + \frac{Z_{12}}{Z_{22}} V_2 \rightarrow ④$$

From eq' ④ & ①. Compare with the eq' ③ of h-parameters.

$$h_{11} = \frac{\Delta Z}{Z_{22}} \quad h_{12} = \frac{Z_{12}}{Z_{22}}$$

$$h_{21} = -\frac{Z_{21}}{Z_{22}} \quad h_{22} = \frac{1}{Z_{22}}$$

b) h-parameters in terms of Y-parameters:

WKT, Y-parameter eqn's

$$I_1 = Y_{11} V_1 + Y_{12} V_2 \rightarrow ①$$

$$I_2 = Y_{21} V_1 + Y_{22} V_2 \rightarrow ②$$

H-parameter eqn's

$$V_1 = h_{11} I_1 + h_{12} V_2$$

$$I_2 = h_{21} I_1 + h_{22} V_2$$

From eq' ①

$$Y_{11} V_1 = I_1 - Y_{12} V_2$$

$$V_1 = \frac{1}{Y_{11}} I_1 - \frac{Y_{12}}{Y_{11}} V_2 \rightarrow ③$$

Substitute eq' ③ in eq' ②.

$$I_2 = Y_{21} \left[\frac{1}{Y_{11}} I_1 - \frac{Y_{12}}{Y_{11}} V_2 \right] + Y_{22} V_2.$$

$$I_2 = \frac{Y_{21}}{Y_{11}} I_1 + V_2 \left[\frac{Y_{11}Y_{22} - Y_{12}Y_{21}}{Y_{11}} \right] \rightarrow \textcircled{4}.$$

from \textcircled{3} & \textcircled{4}.

$$h_{11} = \frac{1}{Y_{11}}$$

$$h_{12} = -\frac{Y_{12}}{Y_{11}}$$

$$h_{21} = \frac{Y_{21}}{Y_{11}}$$

$$h_{22} = \frac{Y_{22}}{Y_{11}}$$

c) H-terms of ABCD parameters:

ABCD parameters

H-parameters

$$V_1 = AV_2 - BI_2 \rightarrow \textcircled{1}$$

$$V_1 = h_{11} I_1 + h_{12} V_2$$

$$I_1 = CV_2 - DI_2 \rightarrow \textcircled{2}$$

$$I_2 = h_{21} I_1 + h_{22} V_2.$$

From eq' \textcircled{4}.

$$I_1 = CV_2 - DI_2$$

$$-DI_2 = I_1 - CV_2.$$

$$I_2 = \frac{1}{D} I_1 + \frac{C}{D} V_2 \rightarrow \textcircled{3}.$$

Substitute eq' \textcircled{3} in \textcircled{1}.

$$V_1 = AV_2 - B \left[-\frac{1}{D} I_1 + \frac{C}{D} V_2 \right]$$

$$V_1 = AV_2 + \frac{B}{D} I_1 - \frac{BC}{D} V_2,$$

$$V_1 = \frac{B}{D} I_1 - \frac{AD - BC}{D} V_2. \rightarrow \textcircled{4}$$

Compare eq' \textcircled{3} & \textcircled{4} with H-parameter equations.


$$h_{11} = \frac{B}{D}$$

$$h_{12} = \frac{AD - BC}{D}$$

$$h_{21} = -\frac{1}{D}$$

$$h_{22} = \frac{C}{D}$$

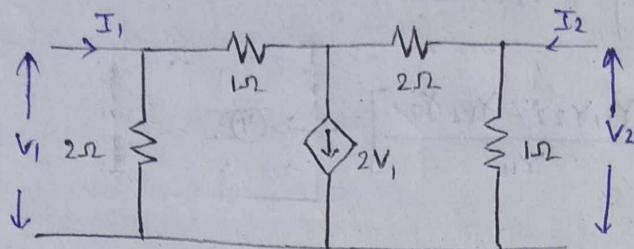Eg. (12) obtain ABCD parameters for the network shown below.



Let us solve Y₁ parameters for given network.

$$I_1 = Y_{11}V_1 + Y_{12}V_2$$

$$I_2 = Y_{21}V_1 + Y_{22}V_2.$$

① S.C. port ①, i.e., $V_2 = 0$.

$$Y_{11} = \frac{I_1}{V_1} \quad | \quad Y_{21} = \frac{I_2}{V_1}$$

Apply KCL at node @

$$I_1 = \frac{V_1}{2} + \frac{V_1 - V_x}{1}$$

$$I_1 = V_1 \left(\frac{1}{2} + 1 \right) - V_{xc} = V_1 (1.5) - V_x. \rightarrow ①$$

Apply KCL at node ⑥

$$2V_1 + \frac{V_{xc} - V_1}{1} - I_2 = 0.$$

$$2V_1 + \frac{V_{xc} - V_1}{1} - \frac{(-V_x)}{2} = 0.$$

$$2V_1 - V_1 + V_x \left[1 + \frac{1}{2} \right] = 0.$$

$$V_1 + 0.5V_x = 0.$$

$$V_x = -\frac{V_1}{0.5}$$

Substitute in eq ①

$$I_1 = V_1 (1.5) - V_x \Rightarrow V_1 \times 1.5 - \left(-\frac{V_1}{0.5} \right)$$

$$I_1 \Rightarrow V_1 \left[1.5 + \frac{1}{0.5} \right]$$

$$I_1 \Rightarrow V_1 (+2.5)$$

$$Y_{11} = \frac{I_1}{V_1} = +2.5 \text{ S} \Rightarrow \therefore Y_{11} = 2.5 \text{ S}$$

$$\therefore ZT_2 = -2V_x$$

$$\therefore \frac{I_2}{V_1} = -\frac{2}{2} = -1 \text{ S}$$

$$Y_{21} = -1 \text{ S}$$


$$(1) \quad I_2 = \frac{V_x}{2} = \frac{V_1}{0.5 \times 2}$$

$$\therefore \frac{I_2}{V_1} = \frac{+1}{3} = 0.33 \text{ S}$$

$$Y_{21} = 0.33 \text{ S}$$

Q. S. c the port ① i.e., $V_1 = 0$.

$$Y_{22} = \frac{I_2}{V_2} \quad | \quad Y_{12} = \frac{I_1}{V_2}$$

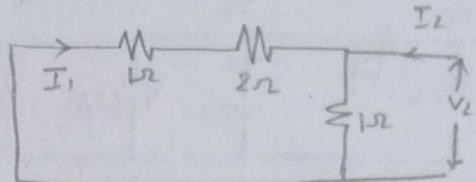


$$V_2 = I_2 (R_{eq}) \Rightarrow I_2 (3/1)$$

$$V_2 \Rightarrow I_2 \frac{3}{4}$$

$$\frac{I_2}{V_2} = \frac{4}{3} = 1.33 \text{ u} \quad \boxed{Y_{22} = 1.33 \text{ u}}$$

$$-3I_1 = V_2$$

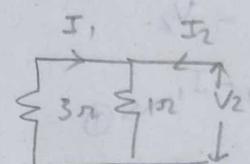

$$\frac{I_1}{V_2} = -\frac{1}{3} \Rightarrow -0.33 \text{ u}$$

$$\boxed{Y_{12} = -0.33 \text{ u}}$$

Now ABCD parameters are

$$A = -\frac{Y_{22}}{Y_{21}} \Rightarrow \frac{-1.33}{+0.33} = -4.033$$

$$B = -\frac{1}{Y_{21}} = \frac{-1}{+0.33} = -3.033 \Omega \Rightarrow -3.033 \Omega$$


$$C = -\frac{\Delta Y}{Y_{21}} \Rightarrow \frac{Y_{12} Y_{21} - Y_{11} Y_{22}}{Y_{21}} \Rightarrow \frac{(-0.33 \times 0.33) - (2.15 \times 1.33)}{+0.33}$$

$$= 7.0334 \text{ soho} \Rightarrow -9.0334 \text{ u.}$$

$$D = -\frac{Y_{11}}{Y_{21}} \Rightarrow -\frac{2.15}{+0.33} = 6.54$$

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} -4.033 & -3.033 \Omega \\ -9.033 \text{ soho} & 6.54 \end{bmatrix}$$

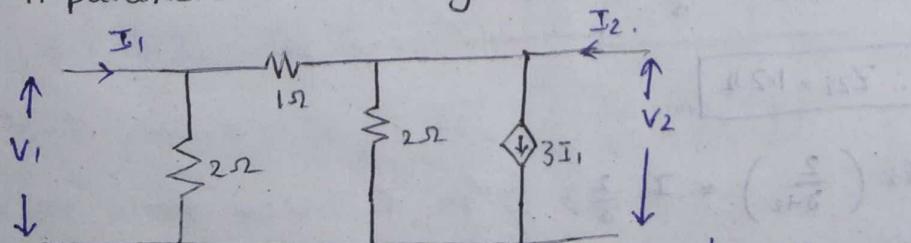Eg. 13 obtain H parameters for the given network.




Sol: let us find out Z-parameters for given network.

$$V_1 = Z_{11} I_1 + Z_{12} I_2$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2$$

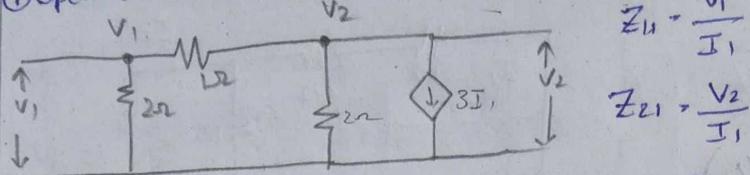① Open circuit the port ② i.e., $I_2 = 0$.



$$Z_{11} = \frac{V_1}{I_1}$$

$$Z_{21} = \frac{V_2}{I_1}$$

Apply KCL at node ①

$$I_1 = \frac{V_1}{2} + \frac{V_1 - V_2}{1}$$

$$I_1 = V_1 \left(\frac{1}{2} + 1 \right) - V_2$$

$$I_1 = 1.5V_1 - V_2.$$

$$V_2 = 1.5V_1 - I_1 \Rightarrow ①$$

Apply KCL at ②

$$\frac{V_2 - V_1}{1} + \frac{V_2}{2} + 3I_1 = 0.$$

$$1.5V_2 - V_1 + 3I_1 = 0.$$

Substitute eqn ① in above eqn

$$1.5(1.5V_1 - I_1) - V_1 + 3I_1 = 0.$$

$$2.25V_1 - 1.5I_1 - V_1 + 3I_1 = 0.$$

$$1.25V_1 = -1.5I_1$$

$$\frac{I_1}{V_1} = -0.83325.$$

$$\boxed{\frac{V_1}{I_1} = -1.2\Omega}$$

$$\boxed{Z_{11} = -1.2\Omega}$$


$$\therefore V_1 = -1.2I_1$$

$$V_2 = 1.5V_1 - I_1 \Rightarrow V_2 = 1.5(-1.2I_1) - I_1$$

$$\frac{V_2}{I_1} = -1.8 - 1 \Rightarrow -2.8\Omega$$

$$\boxed{Z_{21} = -2.8\Omega}$$

② Open the port ① i.e., $I_2 = 0$.

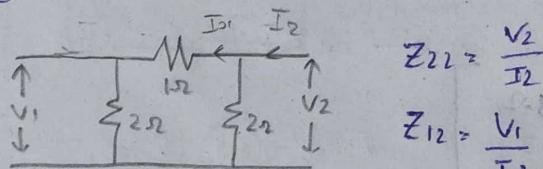

$$Z_{22} = \frac{V_2}{I_2}$$

$$Z_{12} = \frac{V_1}{I_2}$$

$$V_2 = I_2 \text{ deg}$$

$$\frac{V_2}{I_2} = 3/I_2 \Rightarrow \frac{6}{5} = 1.2\Omega$$

$$\therefore Z_{22} = 1.2\Omega$$

$$I_1 = I_2 \left(\frac{2}{3+2} \right) = I_2 \cdot \frac{2}{5}.$$

$$\therefore V_1 = 2I_2 \Rightarrow 2 \times \frac{2}{5} \times I_2$$

$$\frac{V_1}{I_2} = \frac{4}{5} = 0.8\Omega$$

$$\boxed{Z_{12} = 0.8\Omega}$$

$$H_{11} = \frac{Z_{11}}{Z_{22}} = \frac{(-1.2)(1-2) - (-2.8)(0.8)}{1.2} \Rightarrow 0.66752$$

$$h_{12} = \frac{Z_{12}}{Z_{22}} = \frac{0.8}{1.2} = 0.667$$

$$h_{21} = -\frac{Z_{21}}{Z_{22}} \Rightarrow \frac{(-2.8)}{1.2} = -2.33$$


$$h_{22} = \frac{1}{Z_{22}} = 0.833333333$$

$$\begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} = \begin{bmatrix} 0.66752 & 0.667 \\ -2.33 & 0.833333333 \end{bmatrix}$$

Reciprocity and symmetry condition in Two-port network parameters:-

A network is termed to be reciprocal, if the ratio of the response variable to the excitation variable remains same even if the positions of response and excitation are interchanged.

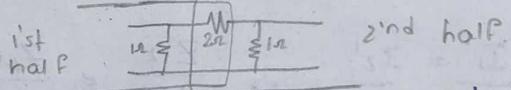A symmetrical network is defined as a network which can be divided into two halves with each half as a mirror image of other. (Q1)



If the impedance measured at one port is equal to the impedance measured at the other port with remaining port is open circuited then network is said to be symmetrical.

(Q2) When the input port impedance is equal to output port impedance then it is called symmetrical. ($Z_{11} = Z_{22}$)

① a. condition of reciprocity for Z-parameters:

The equations of Z-parameters are.

$$V_1 = Z_{11}I_1 + Z_{12}I_2 \rightarrow ①$$

$$V_2 = Z_{21}I_1 + Z_{22}I_2 \rightarrow ②$$

$$V_1 = V_1 ; V_2 = 0 ; I_2 = -I_2' \quad [:\text{from the fig}]$$

Substitute above values in eqn ① & ②

$$V_1 = Z_{11}I_1 - Z_{12}I_2'$$

$$0 = Z_{21}I_1 - Z_{22}I_2'$$

Substitute I_1 value.


$$V_1 = Z_{11} \left[\frac{Z_{22}I_2'}{Z_{21}} - Z_{12}I_2' \right]$$

$$I_1 = \frac{Z_{22}I_2'}{Z_{21}} \rightarrow ③$$

$$V_1 = I_2' \left[\frac{Z_{11}Z_{22} - Z_{12}Z_{21}}{Z_{21}} \right]$$

$$\therefore \frac{I_2'}{V_1} = \frac{Z_{21}}{\Delta Z} \quad \rightarrow ④$$

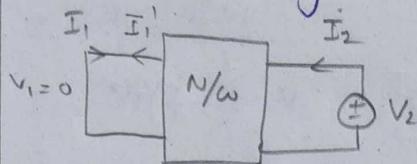Now interchange response and excitation positions.



From the fig: $V_2 = V_1$, $I_1 = 0$, $I_1' = -I_2$.

Substitute the values in eq's ① & ②.

$$0 = -Z_{11}I_1' + Z_{12}I_2 \quad | \quad V_2 = -Z_{21}I_1' + Z_{22}I_2$$

$$I_2 = \frac{Z_{11}I_1'}{Z_{12}} \quad | \quad V_2 = -Z_{21}I_1' + Z_{22} \left[\frac{Z_{11}I_1'}{Z_{12}} \right]$$

$$V_2 = \left[-\frac{Z_{12}Z_{21} + Z_{11}Z_{22}}{Z_{12}} \right] I_1'$$

$$\therefore \frac{I_1'}{V_2} = \frac{Z_{12}}{\Delta Z} \quad \rightarrow ⑤$$

For condition of reciprocity.

$$\frac{I_1'}{V_2} = \frac{I_2'}{V_1} \Rightarrow \frac{Z_{12}}{\Delta Z} = \frac{Z_{21}}{\Delta Z} \Rightarrow Z_{12} = Z_{21}$$

① b. \therefore Symmetry condition for Z-parameters:

$$V_1 = Z_{11}I_1 + Z_{12}I_2 \rightarrow ①$$

$$V_2 = Z_{21}I_1 + Z_{22}I_2. \rightarrow ②$$

① i/p port impedance.

$$\frac{V_1}{I_1} \Big|_{I_2=0}$$

From eq ①

$$\frac{V_1}{I_1} = Z_{11} \rightarrow ③$$

② o/p port impedance.

$$\frac{V_2}{I_2} \Big|_{I_1=0}$$

From eq ②

$$V_2 = Z_{22}I_2$$

$$\frac{V_2}{I_2} = Z_{22} \rightarrow ④$$

From eq ③ & ④.

$$\frac{V_1}{I_1} = \frac{V_2}{I_2} \Rightarrow Z_{11} = Z_{22}$$

② a) Reciprocity for Y-parameters:

The equations of Y parameters;

$$I_1 = Y_{11}V_1 + Y_{12}V_2 \rightarrow ①$$

$$I_2 = Y_{21}V_1 + Y_{22}V_2 \rightarrow ②$$

From the fig; $V_2 = 0$, $I_2 = -I_2'$, $V_1 = V_1$

Substitute above values in eqn's ① & ② only.


$$-I_2' = Y_{21}V_1 + 0$$

$$\boxed{\frac{I_2'}{V_1} = -Y_{21}} \Rightarrow ③$$

Now interchange the source and excitation positions.

From the fig; $V_1 = 0$, $I_1 = -I_1'$,

$$V_2 = V_2$$

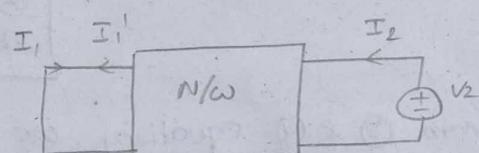

Substitute above values in eqn ①.

$$[-I_1'] = 0 + Y_{12}V_2$$

$$\boxed{\frac{I_1'}{V_2} = -Y_{12}} \rightarrow ④$$

From ③ & ④ reciprocity condition,

$$\frac{I_2'}{V_1} = \frac{I_1'}{V_2} \Rightarrow Y_{21} = Y_{12}$$

Condition for reciprocity: $\boxed{Y_{21} = Y_{12}}$

② b) symmetry condition for Y parameters:

Y eqn's; $I_1 = Y_{11}V_1 + Y_{12}V_2 \rightarrow ①$

$$I_2 = Y_{21}V_1 + Y_{22}V_2 \rightarrow ②$$

① i/p posit admittance.

$$\frac{V_1}{I_1} \Big|_{I_2=0}$$

Substitute $I_2 = 0$ in eq ②.

$$\alpha = Y_{21}V_1 + Y_{22}V_2$$

$$\therefore V_2 = -\frac{Y_{21}}{Y_{22}}V_1$$

Substitute V_2 in eq ① $I_1 = Y_{11}V_1 + Y_{12} \left[-\frac{Y_{21}}{Y_{22}}V_1 \right]$

$$I_1 = V_1 \left[\frac{Y_{11}Y_{22} - Y_{12}Y_{21}}{Y_{22}} \right]$$

$$\frac{V_1}{I_1} = \frac{Y_{22}}{\Delta Y} \rightarrow \textcircled{3}.$$

Now, op post Impedance $\left| \frac{V_2}{I_2} \right|_{I_1=0}$.

Substitute $I_1=0$ in eqn \textcircled{1}.

$$\begin{aligned} 0 &= Y_{11}V_1 + Y_{12}V_2 & I_2 &= Y_{21} \left[-\frac{Y_{12}}{Y_{11}} V_2 \right] + Y_{22}V_2 \\ \therefore V_1 &= -\frac{Y_{12}}{Y_{11}} V_2 & I_2 &= \left[\frac{Y_{11}Y_{22} - Y_{12}Y_{21}}{Y_{11}} \right] V_2 \\ && \boxed{\frac{V_2}{I_2} = \frac{Y_{11}}{\Delta Y}} & \rightarrow \textcircled{4} \end{aligned}$$

From \textcircled{3} & \textcircled{4} equations we get Symmetry condition.

$$\frac{V_1}{I_1} = \frac{V_2}{I_2} \Rightarrow \frac{Y_{22}}{\Delta Y} = \frac{Y_{11}}{\Delta Y}$$

$$\boxed{Y_{22} = Y_{11}} \rightarrow \text{symmetry condition.}$$

③ Reciprocity Conditions for ABCD parameters

The equations of ABCD parameters;

$$V_1 = AV_2 - BI_2 \rightarrow \textcircled{1}$$

$$I_1 = CV_2 - DI_2 \rightarrow \textcircled{2}$$


From the fig; $V_1 = V_1$, $I_2 = -I_2'$, $V_2 = 0$.

Substitute the above values in the eqn \textcircled{1}


$$V_1 = A(0) - B(-I_2')$$

$$V_1 = B I_2'$$
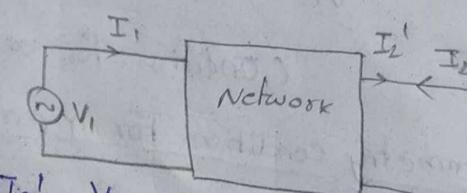
$$\boxed{\frac{I_2'}{V_1} = \frac{1}{B}} \rightarrow \textcircled{3}$$



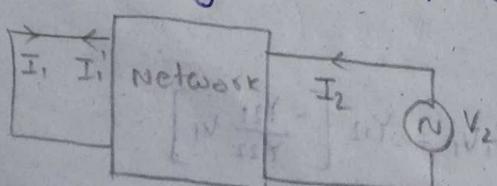Now interchange the des posse and excitation positions.



From the fig; $V_2 = V_2$, $V_1 = 0$, $I_1' = -I_1$

Substitute the above values in eqⁿ ②

$$-I_1' = CV_2 - DI_2 \rightarrow ④$$

Substitute the above values in eqⁿ ①.

$$0 = AV_2 - BI_2$$

$$\therefore I_2 = \frac{AV_2}{B}$$

Substitute the value of I_2 in eqⁿ ④.

$$-I_1' = CV_2 - \left[\frac{AV_2}{B} \times D \right]$$

$$-I_1' = CV_2 - \frac{ADV_2}{B}$$

$$-I_1' = \left[\frac{BC - AD}{B} \right] V_2$$

$$\boxed{\frac{I_1'}{V_2} = \frac{AD - BC}{B}} \rightarrow ⑤$$

Equate the equations ③ & ⑤ to get reciprocity condition.

$$\frac{I_2'}{V_1} = \frac{I_1'}{V_2}$$

$$\frac{1}{B} = \frac{AD - BC}{B}$$

$$\therefore AD - BC = 1 \quad \text{Condition for reciprocity.}$$

③ b. Symmetry condition for ABCD parameters:

$$\text{ABCD parameter equations are; } V_1 = AV_2 - BI_2 \rightarrow ①$$

$$I_1 = CV_2 - DI_2 \rightarrow ②$$

① i/p port impedance.

$$\boxed{\frac{V_1}{I_1} \mid I_2 = 0}$$

From eqⁿ ①

$$V_1 = AV_2 - 0$$

From eqⁿ ②

$$I_1 = C\left(\frac{V_1}{A}\right) - 0.$$

$$\therefore V_2 = \frac{V_1}{A}$$

$$\therefore \boxed{\frac{V_1}{I_1} = \frac{A}{C}} \rightarrow ③$$

② o/p port impedance.

$$\boxed{\frac{V_2}{I_2} \mid I_1 = 0}$$

From eqⁿ ②.

$$0 = CV_2 - DI_2.$$

$$CV_2 = DI_2$$

$$\boxed{\frac{V_2}{I_2} = \frac{D}{C}} \rightarrow ④.$$

∴ From ③ & ④ equations.

$$\frac{V_1}{I_1} = \frac{V_2}{I_2}$$

$$\frac{A}{C} = \frac{D}{C}$$


∴ $A = D$ is the condition for symmetry network.

④ a. Reciprocity condition for h-parameters:

The equations of h parameters;

$$V_1 = h_{11}I_1 + h_{12}V_2 \rightarrow ①$$
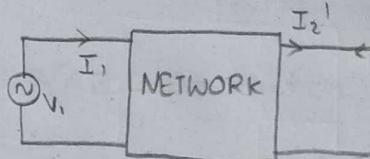
$$I_2 = h_{21}I_1 + h_{22}V_2 \rightarrow ②.$$



From fig; $V_2 = 0, V_1 = V_1, I_2 = -I_2'$

Substitute the above values in eqⁿ ① & ②.

$$V_1 = h_{11}I_1 + 0.$$


$$V_1 = h_{11} \left[-\frac{I_2'}{h_{21}} \right]$$

$$-I_2' = h_{21}I_1$$

$$I_1 = \left[-\frac{I_2'}{h_{21}} \right]$$

$$\boxed{\frac{I_2'}{V_1} = -\frac{h_{21}}{h_{11}}} \rightarrow ③.$$

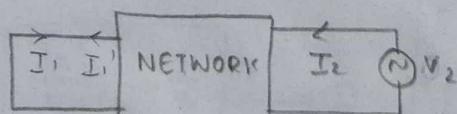Now replace the response and excitation positions.



From fig; $V_1 = 0, I_1 = -I_1', V_2 = V_2$

Substitute the above values in eqⁿ ①.

$$0 = h_{11}(-I_1') + h_{12}V_2$$

$$h_{11}I_1' = h_{12}V_2$$

$$\boxed{\frac{I_1'}{V_2} = \frac{h_{12}}{h_{11}}} \rightarrow ④$$

for reciprocity condition equate ③ & ④ equations.

$$\frac{I_2}{V_1} = \frac{I_1}{V_2}$$

$$-\frac{h_{21}}{h_{11}} = \frac{h_{12}}{h_{22}}$$

$\therefore h_{12} = -h_{21}$ is the condition of reciprocity.

Q) b. symmetry condition for h-parameters:

The equations of h-parameters; $V_1 = h_{11} I_1 + h_{12} V_2 \rightarrow ①$
 $I_2 = h_{21} I_1 + h_{22} V_2 \rightarrow ②$.

① i/p port impedance.

$$\frac{V_1}{I_1} \Big|_{I_2=0}$$

From eqⁿ ①.

$$V_1 = h_{11} I_1 + h_{12} V_2$$

$$V_1 = h_{11} I_1 + h_{12} \left[-\frac{h_{21} I_1}{h_{22}} \right]$$

$$\therefore V_1 = \left[\frac{h_{11} h_{22} - h_{12} h_{21}}{h_{22}} \right] I_1$$

From eqⁿ ②

$$0 = h_{21} I_1 + h_{22} V_2$$

$$V_2 = -\frac{h_{21} I_1}{h_{22}}$$

$$\boxed{\frac{V_1}{I_1} = \frac{\Delta h}{h_{22}}} \rightarrow ③$$

② o/p port impedance.

$$\frac{V_2}{I_2} \Big|_{I_1=0}$$

From eqⁿ ②.

$$I_2 = h_{21}(0) + h_{22} V_2$$

$$I_2 = h_{22} V_2$$

$$\boxed{\frac{V_2}{I_2} = \frac{1}{h_{22}}} \rightarrow ④$$

From eqⁿ's ③ & ④.

$$\frac{V_1}{I_1} = \frac{V_2}{I_2}$$

$$\frac{1}{h_{22}} = \frac{\Delta h}{h_{22}}$$



$\therefore \Delta h = 1$ is the condition for symmetry.

	Reciprocity condition	Symmetry condition
Z	$Z_{12} = Z_{21}$	$Z_{11} = Z_{22}$
Y	$Y_{12} = Y_{21}$	$Y_{11} = Y_{22}$
ABCD	$AD - BC = 1$	$A = D$
h	$h_{12} = -h_{21}$	$h_{11} = 1$

Inconnection of Two-port Networks:

1. Series connection
2. Parallel connection.
3. Cascade connection.

Series connection:-

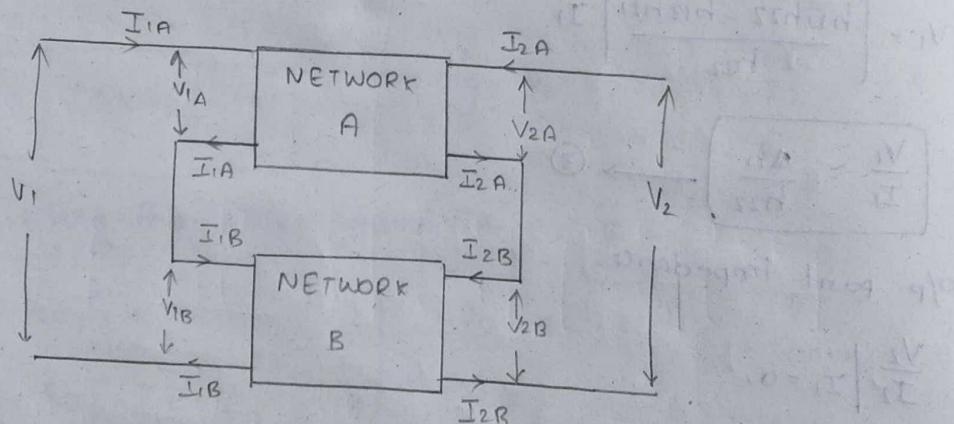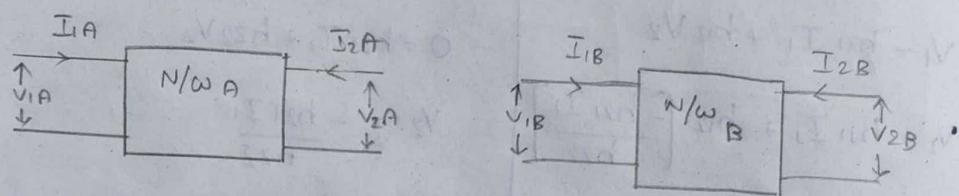

From the above network:

$$\therefore I_1 = I_{1A} = I_{1B}$$

$$I_2 = I_{2A} = I_{2B}$$

$$\therefore V_1 = V_{1A} + V_{1B}$$

$$V_2 = V_{2A} + V_{2B}$$

The open circuit or z-parameters are highly preferable in characterizing the series connected two port network.

for n/w A Z parameter equations are:

$$V_{1A} = Z_{11A} I_{1A} + Z_{12A} I_{2A}$$

$$V_{2A} = Z_{21A} I_{1A} + Z_{22A} I_{2A}.$$

for n/w B Z parameter equations are:

$$V_{1B} = Z_{11B} I_{1B} + Z_{12B} I_{2B}$$

$$V_{2B} = Z_{21B} I_{1B} + Z_{22B} I_{2B}.$$

$$\therefore V_1 = V_{1A} + V_{1B} \Rightarrow Z_{11A} I_1 + Z_{12A} I_2 + Z_{11B} I_1 + Z_{12B} I_2$$

$$\therefore V_1 = I_1 (Z_{11A} + Z_{11B}) + I_2 [Z_{12A} + Z_{12B}]$$

$$\therefore V_2 = V_{2A} + V_{2B} \Rightarrow Z_{21A} I_1 + Z_{22A} I_2 + Z_{21B} I_1 + Z_{22B} I_2$$


$$\therefore V_2 = I_1 (Z_{21A} + Z_{21B}) + I_2 (Z_{22A} + Z_{22B})$$

Overall Z-parameters;

$$\begin{bmatrix} Z_{11A} & Z_{12A} \\ Z_{21A} & Z_{22A} \end{bmatrix} + \begin{bmatrix} Z_{11B} & Z_{12B} \\ Z_{21B} & Z_{22B} \end{bmatrix} = \begin{bmatrix} Z_{11A} + Z_{11B} & Z_{12A} + Z_{12B} \\ Z_{21A} + Z_{21B} & Z_{22A} + Z_{22B} \end{bmatrix}$$

For n/w A For n/w B For overall network.

Parallel connection:

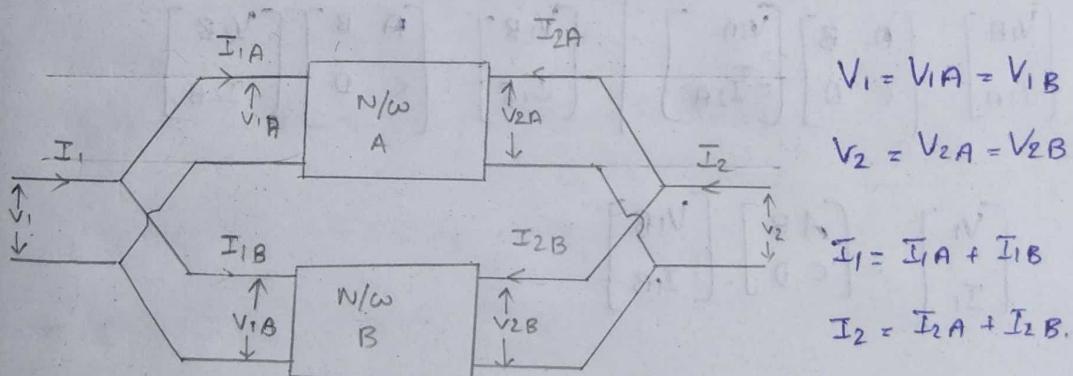

The Y parameters are highly useful to characterize parallel connected two port network.

For network A Y-parameter eq's,

$$I_{1A} = Y_{11A} V_{1A} + Y_{12A} V_{2A}$$

$$I_{2A} = Y_{21A} V_{1A} + Y_{22A} V_{2A}$$

For network B Y-parameter eq's

$$I_{1B} = Y_{11B} V_{1B} + Y_{12B} V_{2B}$$

$$I_{2B} = Y_{21B} V_{1B} + Y_{22B} V_{2B}$$

$$I_1 = I_{1A} + I_{1B} \Rightarrow Y_{11A} V_1 + Y_{12A} V_2 + Y_{11B} V_1 + Y_{12B} V_2$$

$$\therefore I_1 \Rightarrow V_1 [Y_{11A} + Y_{11B}] + V_2 [Y_{12A} + Y_{12B}]$$


$$\text{similarly, } I_2 = V_1 [Y_{21}A + Y_{21}B] + V_2 [Y_{22}A + Y_{22}B]$$

overall γ -parameters

$$\begin{bmatrix} Y_{1A} + Y_{1B} & Y_{12A} + Y_{12B} \\ Y_{21A} + Y_{21B} & Y_{22A} + Y_{22B} \end{bmatrix}$$

Eg
Q

• Cascade connection:

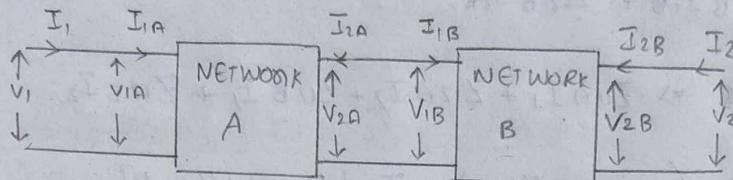

$V_1 = V_{1A}$ $V_{2A} = V_{1B}$ $V_{2B} = V_2$	$I_1 = I_{1A}$ $I_{2A} = -I_{1B}$ (or) $I_{1B} = -I_{2A}$ $I_{2B} = I_2$
---	--

ABCD parameters are highly useful in characterizing the cascade connected two port network.

For Network A, ABCD eqn's

$$V_{1A} = A V_{2A} - B I_{2A}$$

$$I_{1A} = C V_{2A} - D I_{2A}$$

$$\begin{bmatrix} V_{1A} \\ I_{1A} \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_{2A} \\ -I_{2A} \end{bmatrix}$$

For n/w-B, ABCD eqn's.

$$V_{1B} = A V_{2B} - B I_{2B}$$

$$I_{1B} = C V_{2B} - D I_{2B}$$

$$\begin{bmatrix} V_{1B} \\ I_{1B} \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_{2B} \\ -I_{2B} \end{bmatrix}$$

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_{1B} \\ I_{1B} \end{bmatrix}$$

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \underbrace{\begin{bmatrix} A & B \\ C & D \end{bmatrix} \times \begin{bmatrix} A & B \\ C & D \end{bmatrix}}_{\text{for finding } (A) \text{ reaction}} \begin{bmatrix} V_{2B} \\ -I_{2B} \end{bmatrix}$$

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$$

$$[A_11 + B_12] V_1 + [A_12 + B_11] V_2 = I_1$$

Eg. ① Obtain H-parameters for the given network.

Sol: Apply KVL to loop ①.

$$V_1 = (I_1 - I_3)1 + 2(I_1 + I_2)$$

$$V_1 \Rightarrow 3I_1 + 2I_2 - I_3 \rightarrow ①.$$

Apply KVL to loop ②:-

$$V_2 = 4[I_2 + I_3] + 2[I_2 + I_1]$$

$$V_2 = 2I_1 + 6I_2 + 4I_3 \rightarrow ②.$$

Apply KVL to loop ③:-

$$6I_3 + 4[I_3 + I_2] + 1[I_3 - I_1] = 0.$$

$$-I_1 + 4I_2 + 10I_3 + 1I_3 = 0.$$

$$11I_3 = I_1 - 4I_2$$

$$I_3 = 0.09I_1 - 0.36I_2$$

Substitute I_3 in eqn ① & ②.

$$V_1 = 3I_1 + 2I_2 - [0.09I_1 - 0.36I_2]$$

$$V_1 = 2.91I_1 + 2.36I_2 \rightarrow ③$$

$$V_2 = 2I_1 + 6I_2 + 4[0.09I_1 - 0.36I_2]$$

$$V_2 = 2.36I_1 + 4.56I_2 \rightarrow ④$$


From ③ & ④


$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \underbrace{\begin{bmatrix} 2.91\Omega & 2.36\Omega \\ 2.36\Omega & 4.56\Omega \end{bmatrix}}_{Z\text{-parameter equations.}} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

H-parameters equations:

$$h_{11} = \frac{Z_{11}Z_{22} - Z_{12}Z_{21}}{Z_{22}} = \frac{2.91 \times 4.56 - 2.36^2}{4.56} \Rightarrow 1.68\Omega.$$
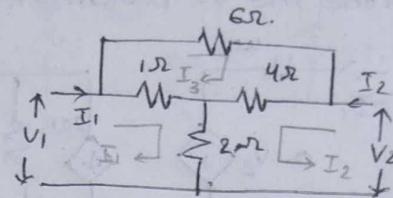
$$h_{12} = \frac{Z_{12}}{Z_{22}} = \frac{2.36}{4.56} \Rightarrow 0.517; h_{21} = \frac{-Z_{21}}{Z_{22}} = \frac{-2.36}{4.56} \Rightarrow -0.517; h_{22} = \frac{1}{Z_{22}} = \frac{1}{4.56} \Rightarrow 0.21\Omega$$



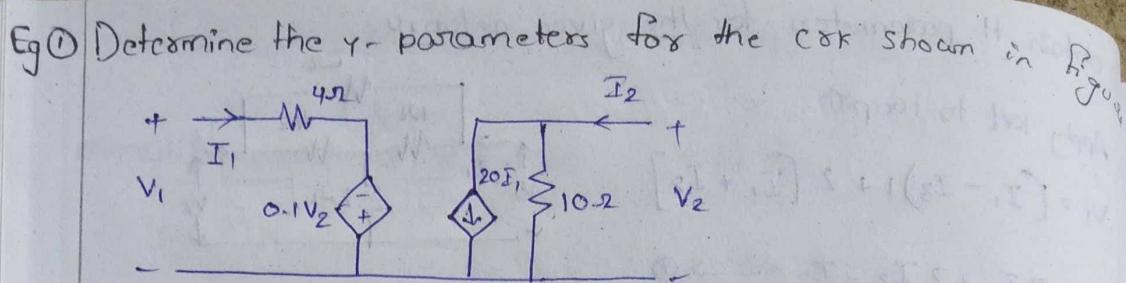

Sol: WKT, h parameter equations are,

$$V_1 = h_{11}I_1 + h_{12}V_2 \rightarrow ① \quad I_2 = h_{21}I_1 + h_{22}V_2 \rightarrow ②$$

Given circuit is an equivalent circuit of hybrid parameters.

Apply KVL to 1st loop.

$$V_1 = 4I_1 - 0.1V_2 \rightarrow ③$$

Apply KCL to 2nd half

$$I_2 = \frac{V_2}{10} + 20I_1$$

$$I_2 = 20I_1 + 0.1V_2 \rightarrow ④$$

Compare ③ & ④ with ① & ②.

$$h \text{ parameters} = \begin{bmatrix} 4 & -0.1 \\ 20 & 0.1 \end{bmatrix}$$

Now γ -parameters in terms of H parameters.

$$\gamma_{11} = \frac{1}{h_{11}} = \frac{1}{4} = 0.25 \Omega$$

$$\gamma_{12} = \frac{-h_{12}}{h_{11}} = \frac{0.1}{4} = 0.025 \Omega$$


$$\gamma_{21} = \frac{h_{21}}{h_{11}} = \frac{20}{4} = 5 \Omega$$


$$\gamma_{22} = \frac{1/h}{h_{11}} \Rightarrow \frac{h_{11}h_{22} - h_{12}h_{21}}{h_{11}} \Rightarrow \frac{4 \times 0.1 + 0.1 \times 20}{4} = 0.6 \Omega$$

$$\gamma \text{-parameters are } \begin{bmatrix} 0.25 & 0.025 \\ 5 & 0.6 \end{bmatrix}$$

Eg:

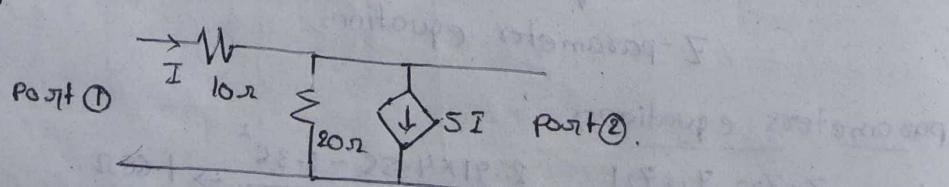② Determine the impedance parameters for the network shown in Fig.



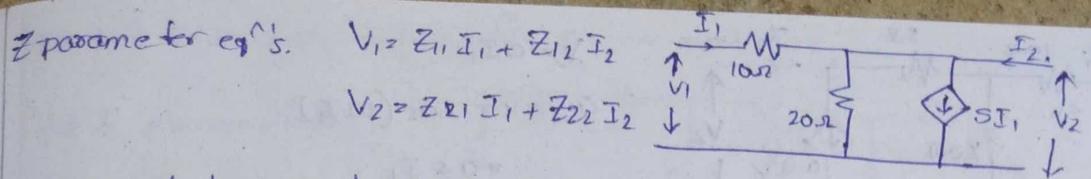

open circuit the port ② i.e., $I_2 = 0$.

$$Z_{11} = \frac{V_1}{I_1}, \quad Z_{21} = \frac{V_2}{I_1}$$

Apply KVL to loop.



$$V_1 = 10I_1 + 20I_1 - 100I_1,$$

$$V_1 = -70I_1$$

$$\therefore \frac{V_1}{I_1} = \boxed{Z_{11} = -70\Omega}$$

$$V_2 = 20I_1 - 100I_1,$$

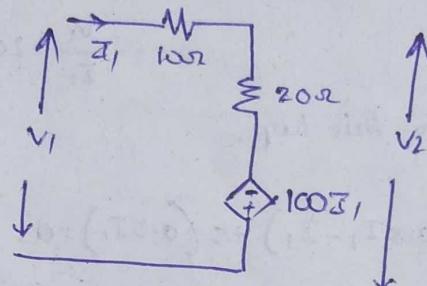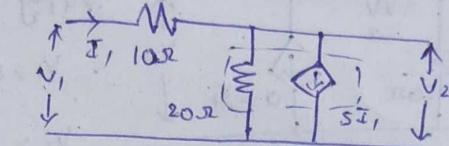
$$\therefore \frac{V_2}{I_1} = \boxed{Z_{21} = -80\Omega}$$



open circuit the port ① i.e., $I_1 = 0$.

$$Z_{12} = \frac{V_1}{I_2}, \quad Z_{22} = \frac{V_2}{I_2}$$

$$\therefore V_2 = 20I_2$$

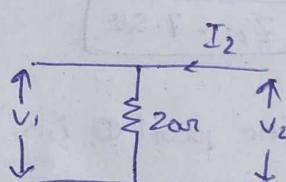

$$\frac{V_2}{I_2} = 20\Omega \Rightarrow \boxed{Z_{22} = 20\Omega}$$


$$\therefore V_1 = 20I_2$$

$$\frac{V_1}{I_2} = 20\Omega \Rightarrow \boxed{Z_{12} = 20\Omega}$$

Z parameter equations are

$$\begin{bmatrix} -70\Omega & 20\Omega \\ -80\Omega & 20\Omega \end{bmatrix}$$

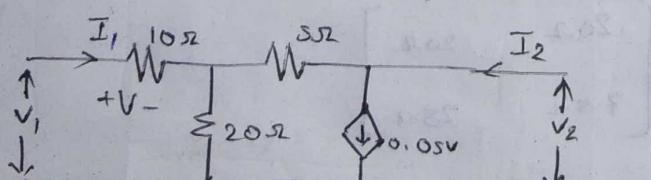③ Determine M-parameters for the network shown in figure.




Let us find out "Z" for the above network

$$V_1 = Z_{11}I_1 + Z_{12}I_2$$

$$V_2 = Z_{21}I_1 + Z_{22}I_2$$

① Open circ port ② $I_2 = 0$.

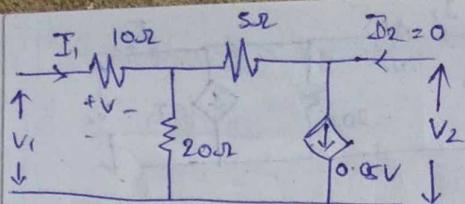
$$Z_{11} = \frac{V_1}{I_1}, \quad Z_{21} = \frac{V_2}{I_1}$$



$$V = 10I_1$$

$$0.05V = 0.05(10I_1)$$

$$= 0.5I_1$$

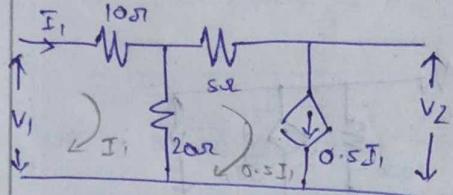

Apply KVL to loop ①.

$$V_1 = 10I_1 + 20(I_1 - 0.5I_1)$$

$$V_1 = 10I_1 + 20I_1 - [10I_1]$$

$$\frac{V_1}{I_1} = 20\Omega \quad \therefore Z_{11} = 20\Omega$$


Apply KVL to this loop.

$$V_2 + 20(0.5I_1 - I_1) + 5(0.5I_1) = 0$$

$$V_2 = -10I_1 + 20I_1 - 2.5I_1$$

$$V_2 = 7.5I_1$$
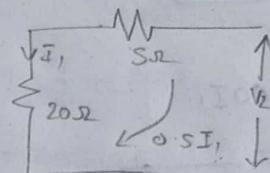
$$\frac{V_2}{I_1} = 7.5\Omega \quad Z_{21} = 7.5\Omega$$




② Open circuit the part ① i.e., $I_1 > 0$.

$$Z_{22} = \frac{V_2}{I_2}, \quad Z_{12} = \frac{V_1}{I_2}$$

$$\therefore V_2 = 5I_2 + 20I_2$$
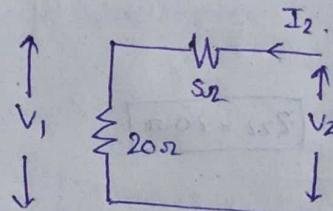
$$\therefore \frac{V_2}{I_2} = Z_{22} = 25\Omega$$



$$\therefore V_1 = 20I_2$$

$$\therefore \frac{V_1}{I_2} = 20\Omega \quad \therefore Z_{12} = 20\Omega$$

$$Z \text{ parameters} = \begin{bmatrix} 20\Omega & 20\Omega \\ 7.5\Omega & 25\Omega \end{bmatrix}$$

In terms of Z parameters:

$$h_{11} = \frac{Z_{11}}{Z_{22}} = 14\Omega$$


$$h_{21} = -\frac{Z_{21}}{Z_{22}} = -0.3$$

$$h_{12} = \frac{Z_{12}}{Z_{22}} = 0.8$$

$$h_{22} = \frac{1}{Z_{22}} = 0.09\Omega$$

(4) Find γ & Z parameters for given network.

γ & Z parameters.

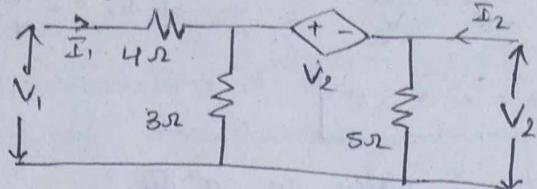

Sol: Let us


$$I_1 = Y_{11}V_1 + Y_{12}V_2$$

$$I_2 = Y_{21}V_1 + Y_{22}V_2$$

① Short circuit the point ② i.e., $V_2 = 0$.

$$V_1 = 4I_1$$

$$V_1 = 4(-I_2)$$

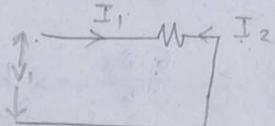

$$\frac{I_1}{V_1} = \frac{1}{4} = Y_{11}$$

$$\frac{I_2}{V_2} = -\frac{1}{4} = Y_{21}$$


$$\therefore Y_{11} = 0.25 \Omega$$

$$\therefore Y_{21} = -0.25 \Omega$$

② S.C the point ① i.e., $V_1 = 0$.

$$Y_{12} = \frac{I_1}{V_2}$$

$$Y_{22} = \frac{I_2}{V_2}$$

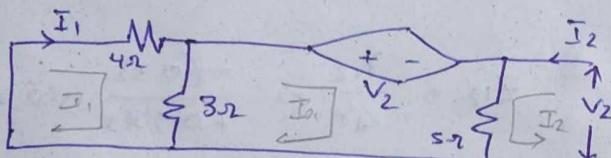

Apply KVL to loop ①

$$4I_1 + 3(I_1 - I_x) = 0$$

$$7I_1 - 3I_x = 0$$

$$I_x = \frac{7}{3}I_1 \rightarrow ①$$

Apply KVL to loop ②

$$V_2 = s(I_2 + I_x)$$

$$V_2 = sI_2 + sI_x$$

→ ②

Apply KVL to loop ③

$$3(I_x - I_1) + V_2 + s(I_x + I_2) = 0$$

$$8I_x - 3I_1 + sI_2 + V_2 = 0$$

$$8I_x = 3I_1 - V_2 - sI_2 \rightarrow ③$$

$$I_x = \frac{3}{8}I_1 - \frac{s}{8}I_2 - \frac{V_2}{8}$$

Substitute eqn ① in eqn ③.

$$8\left(\frac{7}{3}\right)I_1 = 3I_1 - V_2 - sI_2$$

$$\frac{56}{3}I_1 - 3I_1 + sI_2 = -V_2$$

$$18.66I_1 - 3I_1 + sI_2 = -V_2$$

$$I_1(15.66) + sI_2 = -V_2 \rightarrow ④$$

Substitute eqn ① in eqn ④.

$$V_2 = sI_2 + s\left(\frac{7}{3}I_1\right)$$

$$V_2 = 11.66I_1 + sI_2 \rightarrow ⑤$$

Subtract ⑤ - ④

$$[V_2 = 11.66I_1 + sI_2] - [-V_2 = 18.66I_1 + sI_2]$$

$$2V_2 = -4I_1$$

$$\frac{2}{-4} = \frac{\bar{I}_1}{V_2} \rightarrow \bar{I}_1 = \frac{2V_2}{-4}$$

$$\therefore Y_{12} = -0.5V$$

Substitute \bar{I}_1 value in eqn ④

$$15.66 \left(\frac{2V_2}{-4} \right) + 5\bar{I}_2 = -V_2$$

$$-7.83V_2 + 5\bar{I}_2 = -V_2$$

$$5\bar{I}_2 = -V_2 + 7.83V_2$$

$$\frac{\bar{I}_2}{V_2} = \frac{6.83}{5} \Rightarrow 1.366V$$

$$\therefore Y_{22} = 1.366V$$

$$Y \text{ parameters are } = \begin{bmatrix} 0.25V & -0.5V \\ -0.25V & 1.366V \end{bmatrix}$$

$\therefore Z$ parameters in terms of Y parameters are

$$Z_{11} = \frac{Y_{22}}{\Delta Y} \Rightarrow \frac{1.366}{+0.25685} \Rightarrow +6.32\Omega$$

$$Z_{12} = -\frac{Y_{12}}{\Delta Y} \Rightarrow \frac{-(0.5)}{+0.25685} \Rightarrow 2.314\Omega$$

$$Z_{21} = \frac{-Y_{21}}{\Delta Y} \Rightarrow \frac{-(0.25)}{+0.25685} \Rightarrow 1.157\Omega$$


$$Z_{22} = \frac{Y_{11}}{\Delta Y} \Rightarrow \frac{0.25}{+0.25685} \Rightarrow 1.157\Omega$$

$$\therefore \text{where } \Delta Y \Rightarrow [Y_{11}Y_{22} - Y_{12}Y_{21}]$$

$$\Delta Y \Rightarrow 0.25 \times 1.366 - 0.5 \times 0.25 \Rightarrow +0.25685$$

$$Z \text{ parameters are } = \begin{bmatrix} 6.32 & 2.314\Omega \\ 1.157\Omega & 1.157\Omega \end{bmatrix}$$

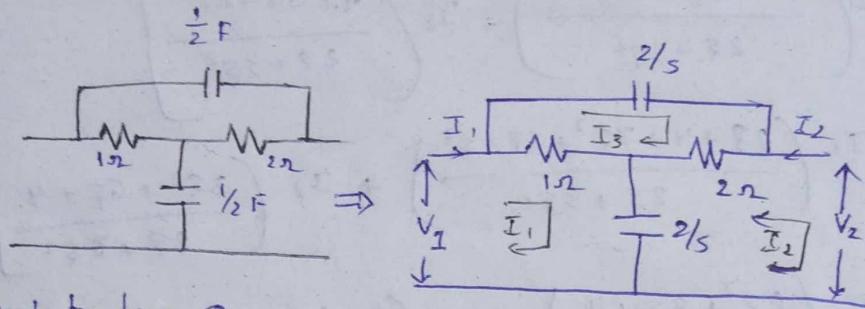Eg: Find the open circuit $\left[\because \left(\frac{1}{2}F\right) \Rightarrow \frac{1}{Cs} \Rightarrow \frac{1}{\frac{1}{2}s} = \frac{2}{s} \right]$



Sol: Apply KVL to loop ①.

$$1(I_1 - I_3) + \frac{2}{s}(I_1 + I_2) = V_1$$

$$I_1 \left(1 + \frac{2}{s} \right) + \frac{2}{s} I_2 - I_3 = V_1$$

$$V_1 = I_1 \left(\frac{s+2}{s} \right) + I_2 \left(\frac{2}{s} \right) - I_3 \rightarrow ①$$

Apply KVL to loop ②:

$$2(I_2 + I_3) + \frac{2}{s}(I_2 + I_1) = V_2$$

$$V_2 = \frac{2}{s} I_1 + I_2 \left(2 + \frac{2}{s} \right) + 2 I_3$$

$$\frac{V_2}{2} = \frac{2}{s} I_1 + I_2 \left(\frac{2s+2}{s} \right) + 2 I_3 \rightarrow ②$$

Apply KVL to loop ③:

$$\frac{2}{s} I_3 + (1[I_3 - I_1]) + 2(I_3 + I_2) = 0$$

$$-I_1 + 2I_2 + I_3 \left(\frac{2}{s} + 1 + 2 \right) = 0$$

$$-I_1 + 2I_2 + I_3 \left(\frac{2+3s}{s} \right) = 0$$

$$I_3 \left(\frac{2+3s}{s} \right) = I_1 - 2I_2$$

$$I_3 = I_1 \left(\frac{s}{2+3s} \right) - I_2 \left(\frac{2s}{2+3s} \right) \rightarrow ③$$

Sub eqn ③ in ① & ②:-

$$V_1 = I_1 \left(\frac{s+2}{s} \right) + I_2 \left(\frac{2}{s} \right) - I_1 \left(\frac{s}{2+3s} \right) + I_2 \left(\frac{2s}{2+3s} \right)$$

$$= I_1 \left(\frac{s+2}{s} - \frac{s}{2+3s} \right) + I_2 \left(\frac{2}{s} + \frac{2s}{2+3s} \right)$$

$$= I_1 \left(\frac{(s+2)(2+3s) - s^2}{2s+3s^2} \right) + I_2 \left(\frac{4+6s+2s^2}{2s+3s^2} \right)$$

$$= I_1 \left(\frac{2s+4+3s^2+6s-s^2}{2s+3s^2} \right) + I_2 \left(\frac{2s^2+6s+4}{2s+3s^2} \right)$$

$$V_1 = I_1 \left(\frac{2s^2+8s+4}{2s+3s^2} \right) + I_2 \left(\frac{2s^2+6s+4}{2s+3s^2} \right) \rightarrow ④$$

from eq "②"

$$V_2 = \frac{2}{s} I_1 + I_2 \left(\frac{2s+2}{s} \right) + 2 \left[I_1 \left(\frac{2s}{2+3s} \right) - I_2 \left(\frac{2s}{2+3s} \right) \right]$$

$$V_2 \Rightarrow \frac{2}{s} I_1 + I_2 \left(\frac{2s+2}{s} \right) + I_1 \left(\frac{2s}{2+3s} \right) - I_2 \left(\frac{4s}{2+3s} \right)$$

$$V_2 = I_1 \left[\frac{\frac{2}{s} + \frac{2s}{2+3s}}{2+3s} \right] + I_2 \left[\frac{2s+2}{s} - \frac{4s}{2+3s} \right]$$

$$V_2 = I_1 \left[\frac{4+6s+2s^2}{3s^2+2s} \right] + I_2 \left[\frac{4s+6s^2+4+6s-4s^2}{3s^2+2s} \right]$$

$$V_2 = I_1 \left[\frac{2s^2+6s+4}{3s^2+2s} \right] + I_2 \left[\frac{2s^2+10s+4}{3s^2+2s} \right] \rightarrow ⑤$$

Compare eq "④ & ⑤"

with Z-parameter equations

$$V_1 = Z_{11} I_1 + Z_{12} I_2; V_2 = Z_{21} I_1 + Z_{22} I_2.$$

$$Z_{11} = \frac{2s^2+8s+4}{3s^2+2s}, Z_{12} = \frac{2s^2+6s+4}{3s^2+2s}$$

$$Z_{21} = \frac{2s^2+6s+4}{3s^2+2s}, Z_{22} = \frac{2s^2+10s+4}{3s^2+2s}$$