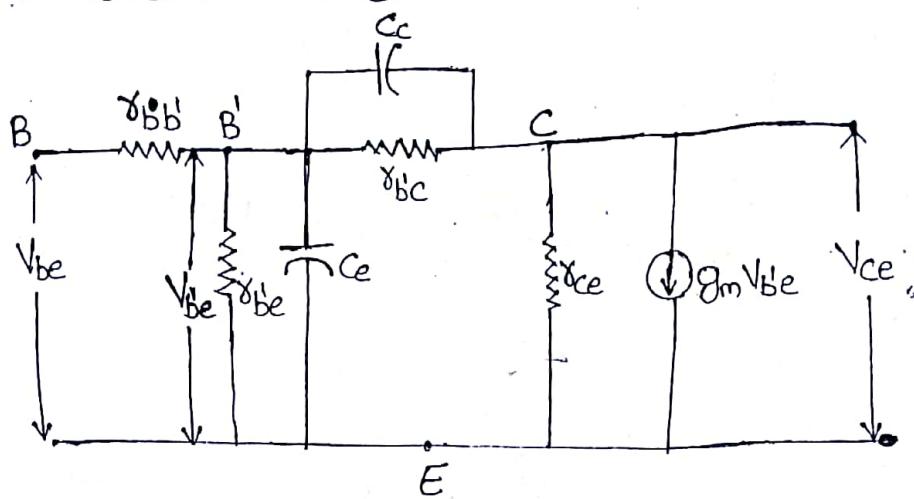


23/11/18  
Friday.

## Transistor High Frequency Model (8) Hybrid $\pi$ model. (8) Giocoletto Model.

The h-parameter model is valid at low and mid frequencies at high frequencies the junction capacitors of the transistors begin to dominate with frequency response.

Giocoletto proposed a model for high frequencies. This model is called High frequency model (8) Hybrid  $\pi$  model or Giocoletto model.



$r_{bb}'$  = base spreading resistance.

$g_m V_{be}$  = This represents collector current which is a result of excess carriers injected by emitter to the base. This current is directly proportional to  $V_{be}$ .

$r_{be}$  = This represents resistance across the base-emitter junction

$r_{bc}$  = This represents a resistance across the collector-base junction. It is result of base width modulation.  $r_{bc}$  is very large.

$r_{ce}$  = This represents a effective resistance between collector and emitter.

$C_e(C_\pi)$  = This represents emitter-base junction capacitance (Forward bias capacitance & diffusion capacitance)


$C_c (C_{ab})$  = This represents collector base junction capacitance.

(Reverse bias capacitance & Transition capacitance)

$\theta_m$  = Transconductance.

Determination of hybrid - $\pi$ - conductances:

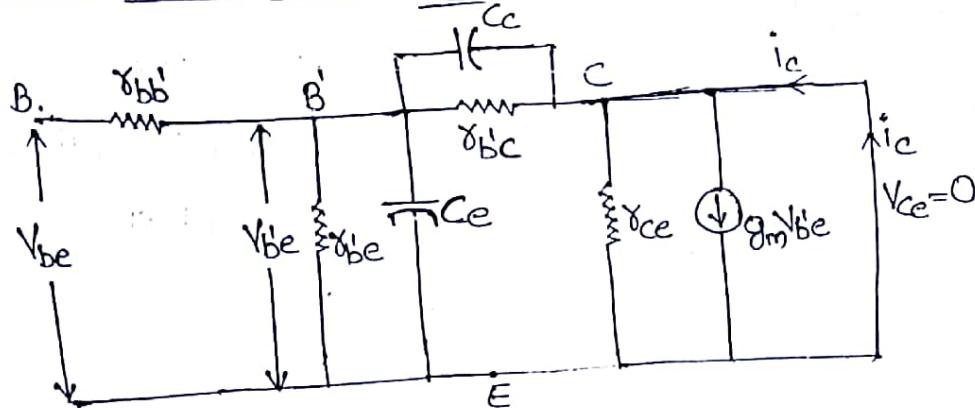Trans conductance ( $\theta_m$ ): (short circuit Trans conductance)



In the above circuit  $V_{CE} = 0$ .

∴ The short circuit collector current is given by

$$i_c = \theta_m V_{BE} \Big|_{V_{CE}=0}$$

$$\theta_m = \frac{i_c}{V_{BE}} \Big|_{V_{CE}=0} = \frac{\Delta I_c}{\Delta V_{BE}} \Big|_{V_{CE}=0}$$

$V_{B'E} \approx V_{BE}$  ( $\theta_{bb}'$  is very small).

$$\theta_m = \frac{\partial I_c}{\partial V_{BE}} \Big|_{V_{CE}} = \frac{\partial I_c}{\partial V_{BE}} \Big|_{V_{CE}}$$

$$I_c = -\alpha I_E + I_{Co}$$

$$\frac{\partial I_c}{\partial V_{BE}} = -\alpha \frac{\partial I_E}{\partial V_{BE}}$$

$$\frac{\partial I_c}{\partial V_{BE}} = -\frac{\alpha}{\left(\frac{\partial V_{BE}}{\partial I_E}\right)}$$

$\frac{\partial V_{BE}}{\partial I_E}$  is the dynamic resistance of the base emitter

$$\frac{\partial V_{BE}}{\partial I_E} = \frac{V_T}{2}$$

$$g_m = \left| \frac{\partial I_C}{\partial V_{BE}} \right|_{V_{CE}} = \frac{-\alpha}{mV_T} = \frac{-\alpha I_E}{mV_T}$$

$\therefore m = 1$  for silicon.


$$g_m = \frac{-\alpha I_E}{V_T}$$

$$I_C \approx -\alpha I_E$$

$$g_m = \left| \frac{I_C}{V_T} \right|$$


24/11/18  
Saturday.

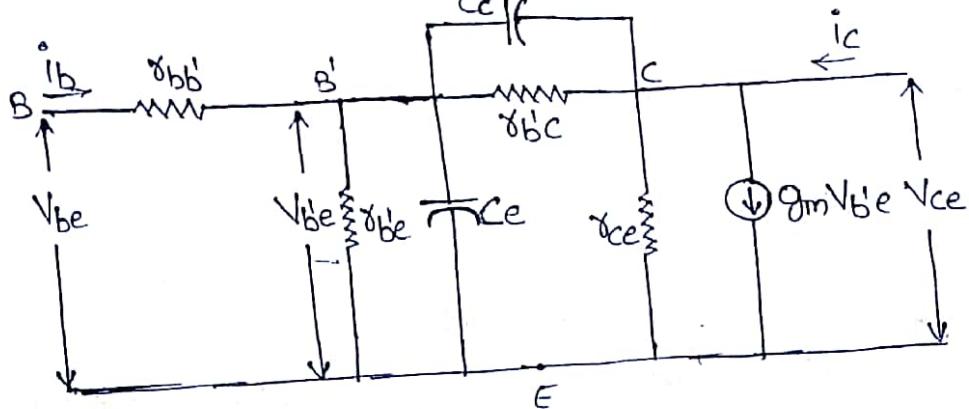Input conductance  $g_{bb}'$  ( $\gamma_{bb}'$ ): (short circuit input conductance)



Consider the hybrid  $\pi$  model at low frequencies. The capacitors  $C_e, C_c$  can be replaced with open circuit because their impedance will be very high at low frequencies.  $\gamma_{bc}'$  is a very large resistor so that it can be replaced with open circuit.

Set  $V_{ce} = 0$  to find  $i_c$

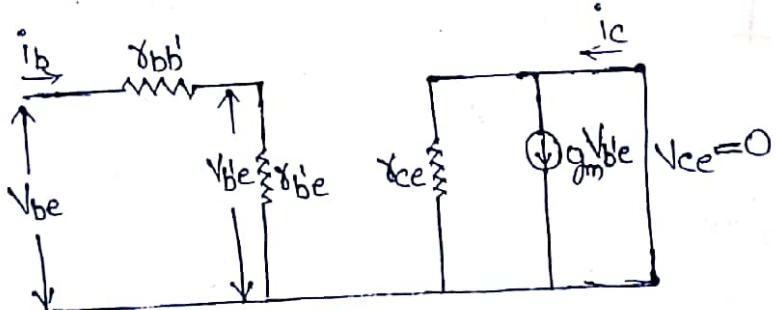


$$i_c = g_m V_{be}$$

$$V_{be}' = i_b \gamma_{bb}'$$

$$i_c = (g_m \gamma_{bb}') (i_b)$$

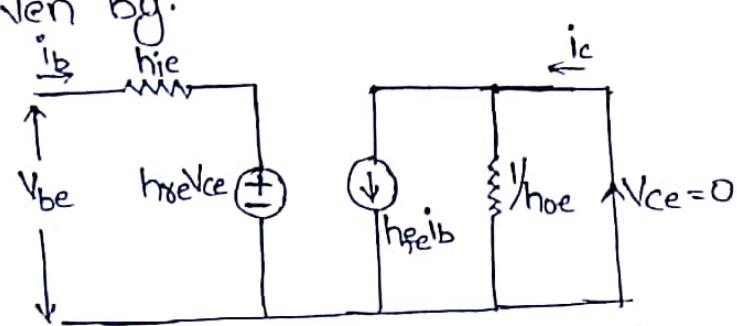At low frequencies the h-parameter model with  $V_{ce}=0$  is given by:



From the above circuit:

$$i_c = h_{fe} i_b.$$


$$\therefore g_m \gamma_{be} i_b = h_{fe} i_b$$

$$\gamma'_{be} = \frac{h_{fe}}{g_m}$$

$$\gamma'_{be} = \frac{1}{\gamma'_{be}} = \frac{g_m}{h_{fe}}$$

Base spreading Resistance ( $\gamma_{bb}'$ ):

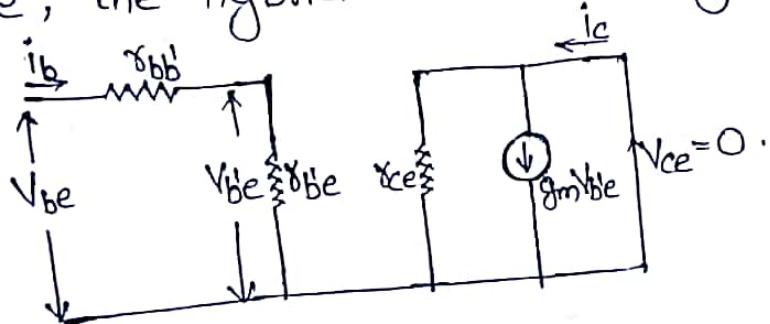At low frequencies with  $V_{ce}=0$  and  $\gamma'_{bc}$  being very large, the hybrid  $\pi$  model is given by:




In the above circuit

$$V_{be} = i_b \gamma_{bb}' + i_b \gamma'_{be}$$

~~$$V_{be} = i_b (\gamma_{bb}' + \gamma'_{be})$$~~

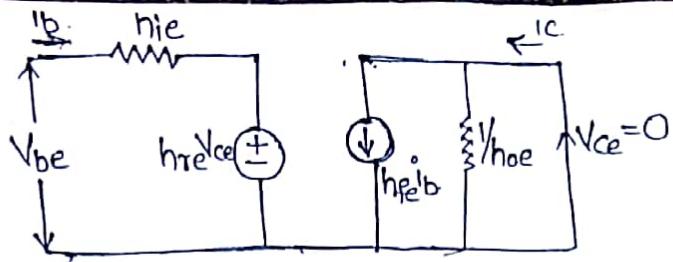The h-parameter model with  $V_{ce}=0$  is given by



In the above circuit.

$$V_{be} = i_b h_{ie} + h_{re} V_{ce}. \quad (\because V_{ce} = 0)$$

$$V_{be} = i_b h_{ie}$$

$$\therefore i_b (\gamma_{bb}' + \gamma_{be}') = i_b h_{ie}.$$

$$\gamma_{bb}' + \gamma_{be}' = h_{ie}.$$

$$\boxed{\gamma_{bb}' = h_{ie} - \gamma_{be}'}$$


RGLII/18  
Monday.

➤

( $\gamma_{bc}$ )

Feed back conductance ( $\gamma_{bc}$ ): (Open circuit feedback conductance)

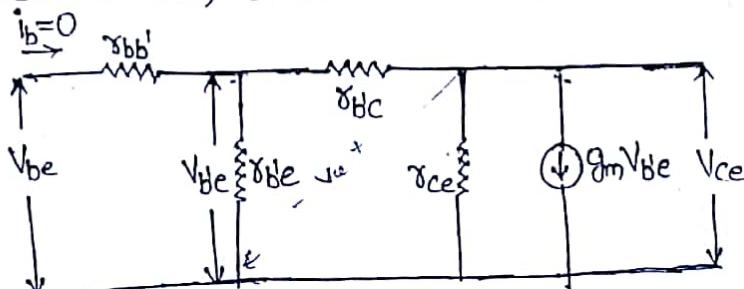If the hybrid  $\pi$  model is used at low frequencies, the capacitors  $C_e, C_c$  can be replaced with open circuits.




If  $i_b = 0$ ,  $\gamma_{be}$ ,  $\gamma_{bc}$  will be in series.

voltage across  $\gamma_{be}$  is

$$V_{be} = \frac{V_{ce} \gamma_{be}}{\gamma_{be} + \gamma_{bc}}$$

$$V_{be} = V_{be}' = \frac{V_{ce} \gamma_{be}}{\gamma_{be} + \gamma_{bc}}$$

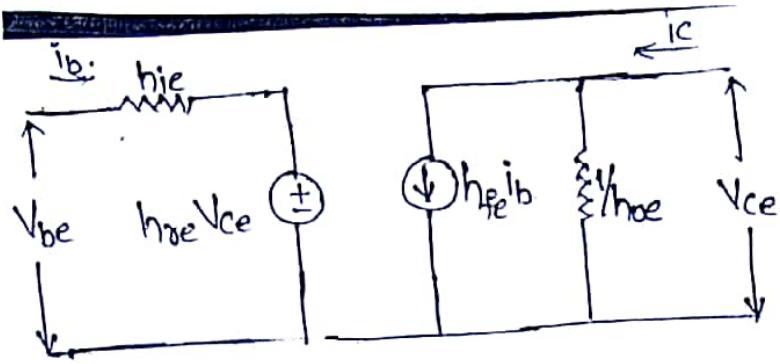The h-parameter model at low frequencies is



$$V_{be} = h_{fe} i_b + h_{re} V_{ce}$$

if  $i_b = 0$ ,

$$V_{be} = h_{re} V_{ce}$$

∴ From the above two circuits we have

$$\frac{V_{ce} - V_{be}}{\gamma_{be} + \gamma_{bc}} = h_{re} V_{ce}.$$

$$\frac{\gamma_{be}}{\gamma_{be} + \gamma_{bc}} = h_{re}.$$

$$\gamma_{be} = h_{re} \gamma_{be} + h_{re} \gamma_{bc}$$

$$\gamma_{be} \gamma_{bc} = \gamma_{be} (1 - h_{re})$$

$$h_{re} \ll 1$$

$$h_{re} \gamma_{bc} = \gamma_{be}.$$

$$\gamma_{bc} = \frac{\gamma_{be}}{h_{re}}$$


$$\boxed{\gamma_{bc} = \frac{1}{\gamma_{bc}} = \frac{h_{re}}{\gamma_{be}} = \gamma_{be} h_{re}.}$$



28/11/18  
Wednesday

Output conductance ( $g_{ce}$ ): (Open circuit output conductance) ( $\frac{1}{g_{ce}}$ )

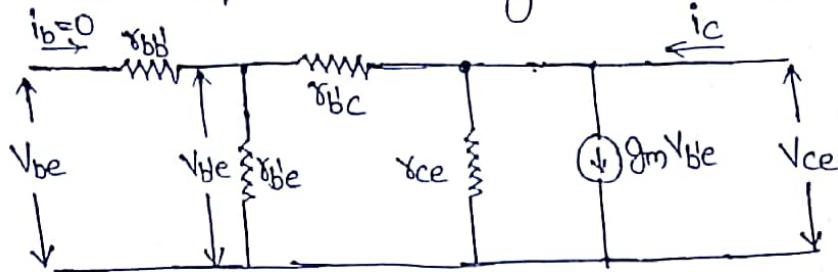At low frequencies the hybrid  $\pi$  model is given by.



set  $i_b = 0$ ,  $r_{be}$ ,  $r_{bc}$  will be in series.

By applying KCL

$$i_c = g_m V_{be} + \frac{V_{ce}}{r_{ce}} + \frac{V_{ce}}{r_{bc} + r_{be}}$$

$$\frac{1}{r_{ce}} = g_{ce}$$

$$g_{bc} = \frac{1}{r_{bc}}$$


$$V_{be} = \frac{V_{ce} \cdot r_{be}}{r_{bc} + r_{be}}$$

$$i_c = \frac{g_m r_{be}}{r_{bc} + r_{be}} V_{be} + V_{ce} g_{ce} + \frac{V_{ce}}{r_{bc}} \quad [\because r_{bc} \gg r_{be}]$$

$$i_c = g_m h_{re} V_{ce} + V_{ce} g_{ce} + V_{ce} g_{bc} \quad [\because h_{re} = \frac{r_{be}}{r_{be} + r_{bc}}]$$

$$\frac{i_c}{V_{ce}} = g_m h_{re} + g_{ce} + g_{bc} \quad \rightarrow ①$$

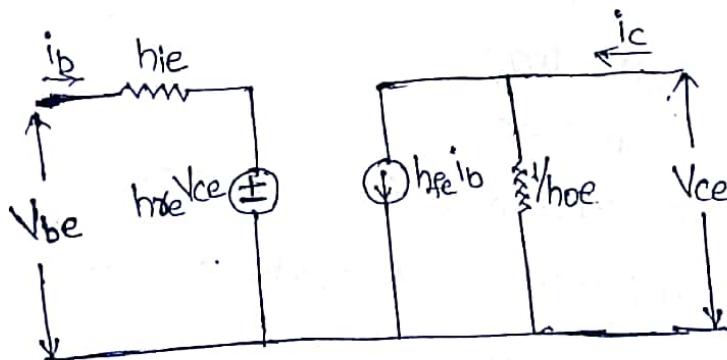The h-parameter model at low frequencies is given by



By applying KCL at o/p node.

$$i_c = h_{fe} i_b + \frac{V_{ce}}{h_{oe}}$$

$$\text{if } i_b = 0, i_c = h_{oe} V_{ce}$$

$$\frac{i_c}{V_{ce}} = h_{oe} \rightarrow ②$$

quating the above equations ① & ② we get

$$i_{ce} = g_m h_{oe} + g_{ce} + g_{bc}$$

$$g_{ce} = h_{oe} - g_m h_{oe} - g_{bc}$$

But  $g_{bc}$  is very large.


$\therefore g_{bc}$  is very small.

$$g_{ce} = h_{oe} - g_m h_{oe}$$

Derivation of hybrid π capacitances:

Diffusion Capacitance ( $C_e$ ) & ( $C_{\pi}$ ) & ( $C_{be}$ ):

(d) Base Emitter Junction Capacitance:

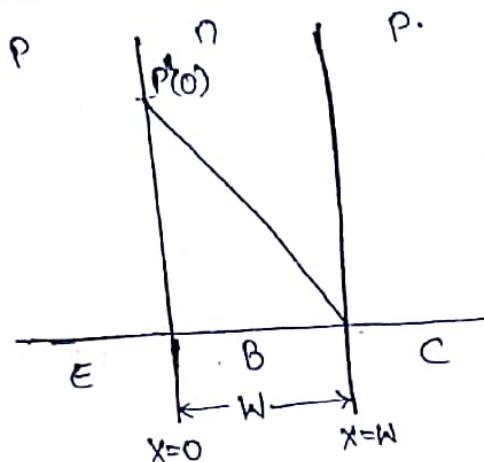

The above figure BE junction is forward biased and BC junction is reverse biased.

$p'(0)$  is the excess hole concentration at  $x=0$

The excess hole concentration at  $x=W$  will be zero because all the holes will be swept by the collector.

$\therefore$  The average excess hole concentration in the base is given by  $\frac{1}{2} p'(0)$

Total charge  $Q$

The excess charge in the base region is given by.

$$Q = \frac{1}{2} P(0) \times q \times A W$$

The diffusion hole current density is given by

$$J_p = -q D_p \frac{dP}{dx}$$

$$P' = P - P_0$$

$$\frac{dP'}{dx} = \frac{dP}{dx} - 0$$

$$J_p = -q D_p \frac{dP'}{dx}$$

$$\text{current } I = A J_p = -A q D_p \frac{dP'}{dx}$$

$$I = -A q D_p \left( \frac{0 - P(0)}{W - 0} \right)$$

$$I = \frac{A q D_p P(0)}{W}$$

$$P'(0) = \frac{IW}{AqD_p}$$

$$\therefore Q = \frac{1}{2} \frac{IW}{AqD_p} \times \cancel{A} \times \cancel{W}$$

$$Q = \frac{IW^2}{2D_p}$$

The diffusion capacitance  $C_e = \frac{dQ}{dV} = \frac{d}{dV} \left( \frac{IW^2}{2D_p} \right)$

$$= \frac{W^2}{2D_p} \cdot \frac{dI}{dV}$$

$$= \frac{W^2}{2D_p} \frac{1}{\left( \frac{dV}{dI} \right)}$$

$\frac{dV}{dI} = \gamma_e$  = dynamic resistance of BE Junction.

$$\therefore C_e = \frac{1}{2} \frac{W^2}{D_p} \frac{1}{\gamma_e}$$

$$W.K.T. \quad \gamma_e = \frac{\eta V_T}{I_E} \quad , \quad \eta = 1 \text{ for Si}$$

$$\gamma_e = \frac{V_T}{I_E}$$

$$\therefore C_e = \frac{1}{2} \frac{W'}{D_p} \cdot \frac{I_E}{V_T}$$

$$I_C \approx I_E, \alpha \approx 1$$

$$I_C \approx I_E$$

$$C_e = \frac{1}{2} \frac{W'}{D_p} \left( \frac{I_C}{V_T} \right)$$

$$C_e = \frac{g_m W'}{2 D_p}$$

Transition capacitance ( $C_c$ ) & ( $C_{b'c}$ ):-

Collector-Base Junction capacitance ( $C_{b'c}$ ):-

Collector-Base junction ~~capacitance~~ is a Reverse biased junction.  
The capacitance at this junction is given by

$$C_c = \frac{EA}{W}$$

where  $W \rightarrow$  width of the depletion Region.



$$W \propto \sqrt{V_j}$$

$$\text{where } V_j = V_0 + V_d$$

The General expression for the Reverse biased capacitance is given by

$$C_c = \frac{C_0}{\left(1 + \frac{V_d}{V_0}\right)^n}$$

$$\text{where } n = 2 \text{ or } 3$$



$$C_c = \frac{C_0}{\left(1 + \frac{V_d}{V_0}\right)^n}$$

29/11/18  
Thursday


CE short circuit current gain (g)  $\beta$  cut off frequency ( $f_B$ )

(Q) CE short circuit unity gain frequency ( $f_T$ ) (8)


CE short circuit unity gain Bandwidth product ( $f_T$ )

(Q) Derive  $\beta$ ,  $\alpha$  cut off frequencies for a short circuit

CE Amplifier:

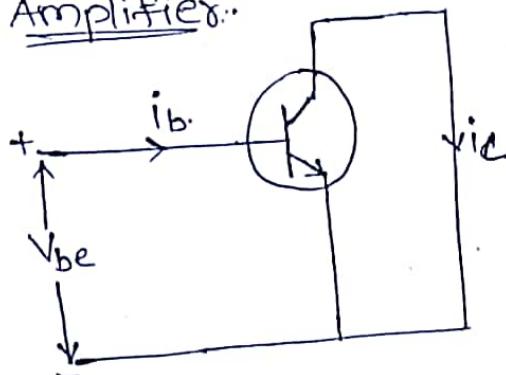


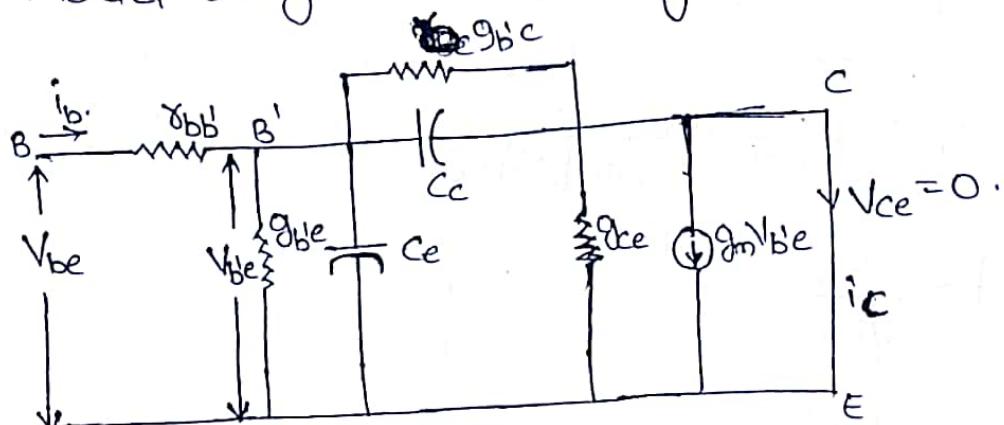The above circuit shows a CE Amplifier with short circuited output. Replacing the transistor with hybrid  $\pi$  model to get the following circuit.



$r_{bc}$  is very large &  $r_{bb}$  is very small.

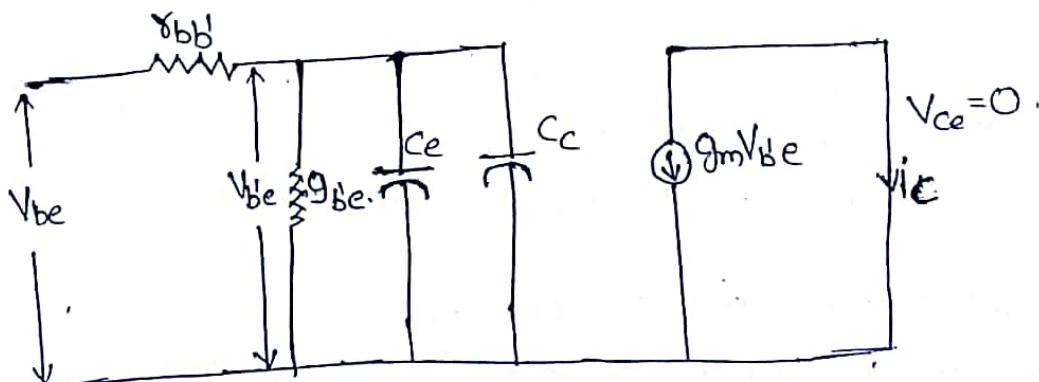$g_{ce}$  is short circuited. The modified circuit is given below.



$$\text{Let } C_e + C_c = C_i$$

zcl at input node

$$i_b = V_{BE} g_{BE} + \frac{V_{BE}}{jR\pi fC_B}$$

$$i_b = V_{BE} [g_{BE} + jR\pi fC_B]$$

$$\text{current gain } A_I = \frac{i_E}{i_b} = \frac{-g_m V_{BE}}{g_{BE} [g_{BE} + jR\pi fC_B]}$$

$$A_I = \frac{-g_m}{g_{BE} + jR\pi fC_B}$$

$$A_I = \frac{-g_m / g_{BE}}{1 + j \frac{R\pi f C_B}{g_{BE}}}$$


$$A_I = \frac{-h_{FE}}{1 + j(\frac{f}{f_p})}$$

$$\text{where } \frac{f_p}{f_p} = \frac{g_{BE}}{R\pi C_i} = \frac{g_{BE}}{R\pi [C_c + C_e]}$$

$$|A_I| = \frac{h_{FE}}{\sqrt{1 + (\frac{f}{f_p})^2}}$$

$$\text{at } f=0, |A_I| = h_{FE}$$

$$\text{at } f=f_p, |A_I| = \frac{h_{FE}}{\sqrt{2}}$$

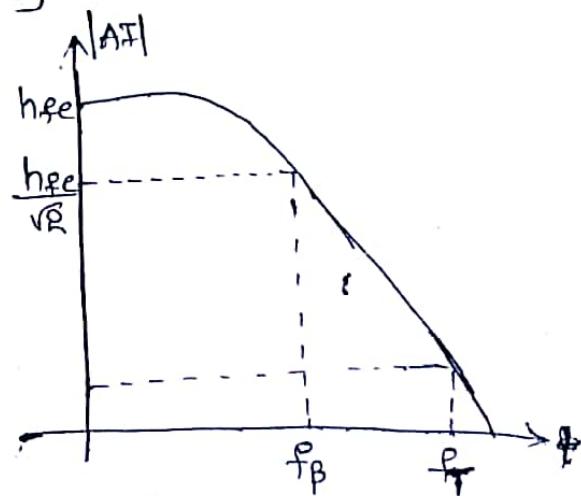

$f_p$  is upper cut off frequency and bandwidth.

$f_p$  is also called as  $\beta$ -cut off frequency.

\*  $h_{FE}$  is the maximum current gain.

Let  $f_T$  be the unity gain frequency. At this frequency

$$|A_I| = 1$$

∴ At  $f = f_T$ ,  $|AI| = 1$

$$\Rightarrow 1 = \frac{h_{fe}}{\sqrt{1 + (\frac{f_T}{f_B})^2}}$$

As  $f_T \gg f_B$ ,  $\Rightarrow \frac{f_T}{f_B} \gg 1$

$$1 = \frac{h_{fe}}{\sqrt{(\frac{f_T}{f_B})^2}}$$

$$\frac{f_T}{f_B} = h_{fe}$$

$f_T = h_{fe} f_B \rightleftharpoons (\text{max gain})(\text{bandwidth})$

\* For a given amplifier, gain bandwidth product is constant.

a-cut off frequency ( $f_\alpha$ ):

$f_\alpha$  is cut off frequency for a short circuit CB amplifier. The short circuit current gain is given by.

$$|AI| = \frac{h_{fb}}{\sqrt{1 + (\frac{f}{f_\alpha})^2}} \quad ; \quad AI = \frac{-h_{fb}}{1 + j(\frac{f}{f_\alpha})}$$

$$\text{At } f = f_\alpha ; |AI| = \frac{h_{fb}}{\sqrt{2}}$$

∴  $f_\alpha$  is upper cut off frequency and bandwidth.  
Let  $f_T$  be the unity gain frequency.

at  $f = f_T$ ,  $|AI| = 1$ ,  $f_T \gg f_\alpha$ .

$$1 = \frac{h_{fb}}{\sqrt{1 + (\frac{f_T}{f_\alpha})^2}} \approx \frac{h_{fb}}{\sqrt{(\frac{f_T}{f_\alpha})^2}}$$

$$\therefore f_T = h_{fb} \cdot f_\alpha$$

$f_T = (\text{gain})(\text{band width})$

For a given amplifier;  $f_T$  is constant


$$\therefore h_{fe} f_B = h_{fB} f_\alpha.$$

$$f_\alpha = \left( \frac{h_{fe}}{h_{fB}} \right) f_B.$$


$$h_{fB} = \frac{h_{fe}}{1+h_{fe}} \Rightarrow \frac{h_{fe}}{h_{fB}} = 1+h_{fe}.$$

$$\therefore f_\alpha = (1+h_{fe}) f_B.$$

E current gain with resistive load :-

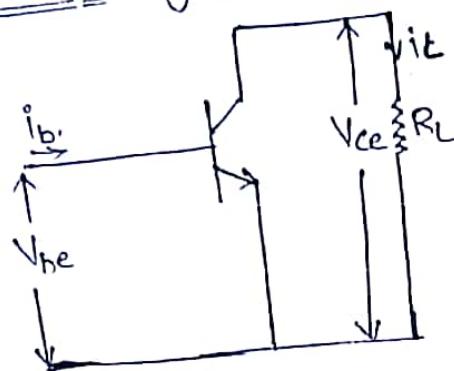


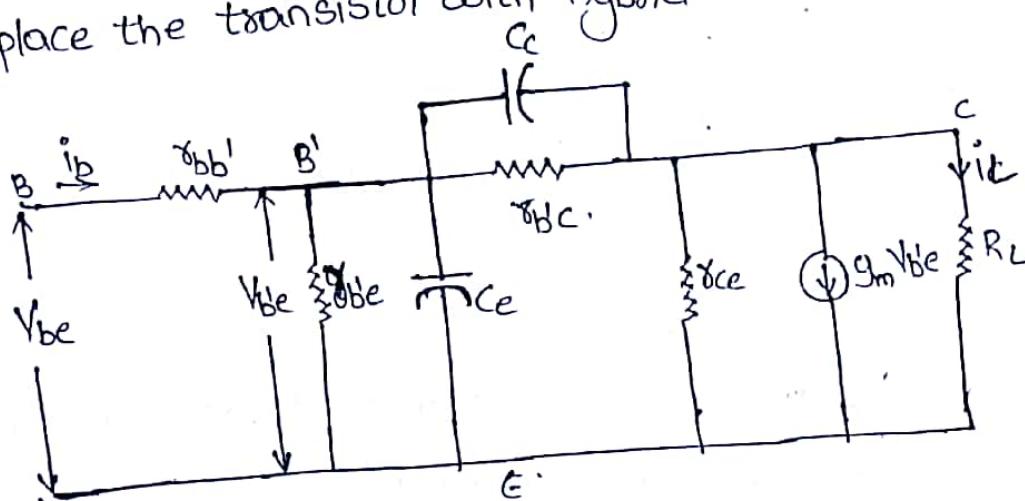Replace the transistor with hybrid  $\pi$  model




$R_{be}$  is very large  $\Rightarrow$  open circuit.
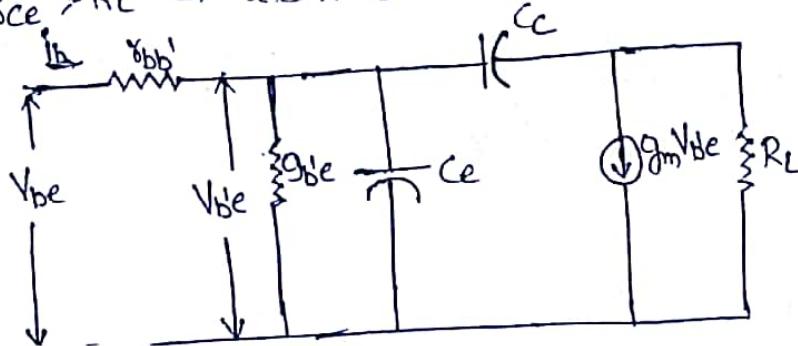
$$R_{ce} > R_L \Rightarrow R_{ce} \parallel R_L \approx R_L$$



The above circuit is modified using miller's theorem.

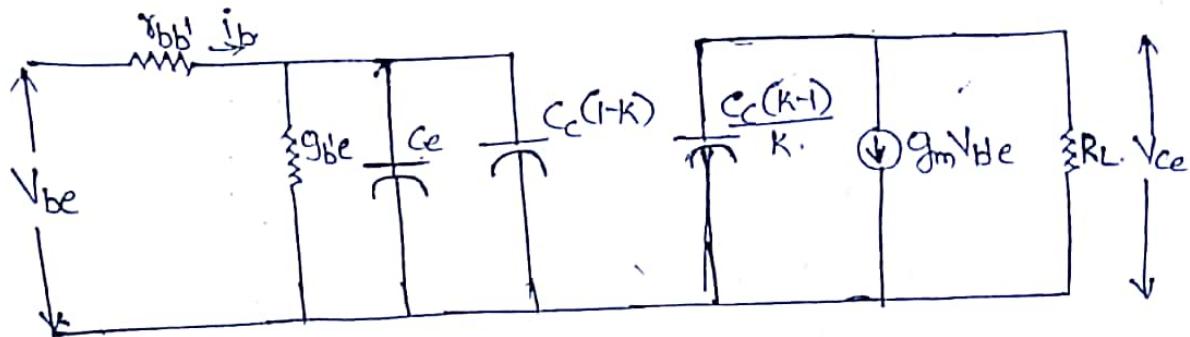Let  $\frac{V_{ce}}{V_{be}} = K$  then the above circuit is given as.




$$C_c \left(\frac{K-1}{K}\right) = C_c \left(1 - \frac{1}{K}\right)$$

$K$  is voltage gain of CE amplifier and  $K$  is a large negative number.

$$\therefore C_c \left(1 - \frac{1}{K}\right) \approx C_c$$
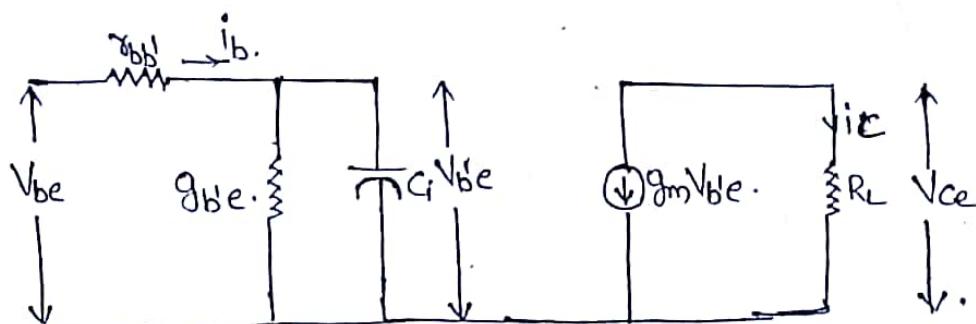
$$\cancel{(jX_C) // R_L} \approx R_L \quad (C_c // R_L \approx R_L)$$



where  $C_f = C_e + C_c$ :

$$K = \frac{V_{ce}}{V_{be}} = \frac{i_c R_L}{V_{be}} = -\frac{g_m V_{be} \cdot R_L}{V_{be}} = -g_m R_L$$

$$i_c = -g_m V_{be}$$

$$i_b = V_{be} (g_{be}) + \frac{V_{be}}{\frac{1}{j2\pi f C_f}}$$

$$i_b = V_{be} (g_{be} + j2\pi f C_f)$$

$$\text{Gain} = \frac{i_c}{i_b} = \frac{-g_m V_{BE}}{(g_{BE} + j2\pi f_C) V_{BE}}$$

$$AI = \frac{-g_m}{(g_{BE} + j2\pi f_C)}$$

$$= \frac{-g_m / g_{BE}}{1 + j \frac{2\pi f_C}{g_{BE}}}$$

$$AI = \frac{-h_{FE}}{1 + j(\frac{\varphi}{\varphi_p})}$$

$$\text{where } \varphi_p = \frac{g_{BE}}{2\pi C_i} = \frac{g_{BE}}{2\pi [C_e + C_c(1 + g_m R_L)]}$$

$$|AI| = \frac{h_{FE}}{\sqrt{1 + (\frac{\varphi}{\varphi_p})^2}}$$

$$\text{at } \varphi = \varphi_p, |AI| = \frac{h_{FE}}{\varphi_p}$$

$$\text{at } \varphi = \varphi_T, |AI| = 1$$


$$1 = \frac{h_{FE}}{\sqrt{1 + (\frac{\varphi_T}{\varphi_p})^2}}$$

$$\therefore \frac{\varphi_T}{\varphi_p} \gg 1$$

$$1 = \frac{h_{FE}}{\frac{\varphi_T}{\varphi_p}}$$

$$\frac{\varphi_T}{\varphi_p} = h_{FE}$$
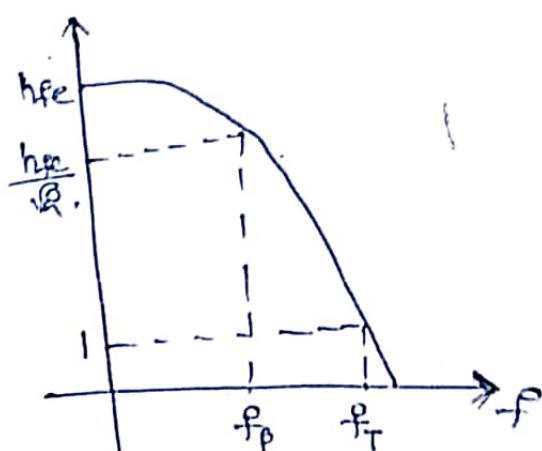
$$\boxed{\varphi_T = h_{FE} \cdot \varphi_p}$$



## Typical values of hybrid π model parameters:

$$g_m = 50 \text{ mA/V} = 5 \text{ mhos.}$$

$$\gamma_{bb} = 100 \Omega$$

$$\gamma_{be} = 1 \text{ k}\Omega$$

$$\gamma_{ce} = 80 \text{ k}\Omega$$

$$\gamma_{b'c} = 4 \text{ M}\Omega$$

$$C_e = 100 \text{ pF}$$

$$C_c = 3 \text{ pF}$$

### Formulas:

$$* \text{ Transconductance } g_m = \frac{I_c}{V_T}$$

$$* \text{ Input conductance } g_{be} = \frac{g_m}{h_{fe}}$$

$$* \text{ Base spreading Resistance } \gamma_{bb} = h_{ie} - \gamma_{be}$$

$$* \text{ Feed back conductance } g_{b'c} = g_{be} h_{re}$$

$$* \text{ Output conductance } g_{ce} = h_{oe} - g_m h_{re}$$

$$* f_B = \frac{g_{be}}{2\pi(C_e + C_c)}$$

$$* f_T = h_{fe} f_B = \frac{h_{fe} g_{be}}{2\pi(C_e + C_c)}$$

we know that

$$g_m = g_{be} h_{fe}$$

$$\therefore f_T = \frac{g_m}{2\pi(C_e + C_c)}$$



Determine the transconductances of a BJT-transistor of hybrid π model with  $\beta=1$ ,  $h_{ie}=4K$ ,  $h_{re}=2.5 \times 10^{-4}$ ,  $h_{fe}=224$ ,  $h_{oe}=25 \mu A/V$  and the biasing current  $i_c=2mA$  at the room temperature.

Given:

$$\beta = 1$$

$$h_{ie} = 4K$$

$$h_{re} = 2.5 \times 10^{-4}$$

$$h_{fe} = 224$$

$$h_{oe} = 25 \mu A/V$$

$$i_c = 2mA$$

$$V_T = 26mV$$

$$g_m = \frac{i_c}{V_T} = \frac{2mA}{26mV} = 0.0769 mhos = 76.9 \mu mhos$$

$$g_{be} = \frac{g_m}{h_{fe}} = \frac{76.9 \times 10^{-3}}{224} = 0.343 mhos$$

$$\gamma_{be} = \frac{1}{g_{be}} = 2.9 K$$

$$\gamma_{bb} = h_{ie} - \gamma_{be} = 4K - 2.9K = 1.08K$$

$$g_{bc} = g_{be} \cdot h_{re} = 0.343 \times 10^{-3} \times 2.5 \times 10^{-4} = 85.8 \mu mhos$$

$$= 0.0858 \mu mhos$$

$$\gamma_{bc} = \frac{1}{g_{bc}} = 11.66 M$$

$$g_{ce} = h_{oe} - g_m h_{re} = 25 \mu - 76.9 \mu \times 2.5 \times 10^{-4}$$

$$= 5.77 \mu mhos$$

01/12/18  
Saturday

2. Following are a low frequency parameters for a transistor at room temperature.  $|I_{C1}| = 5 \text{ mA}$ ,  $h_{ie} = 1 \text{ k}\Omega$ ,  $h_{fe} = 100$ ,  $h_{oe} = 4 \times 10^{-5}$ ,  $h_{re} = 10^4$ ,  $C_{cb} = 2 \text{ pF}$ ,  $f_T = 10 \text{ MHz}$ . Compute various high parameters.

A. Given :

$$|I_{C1}| = 5 \text{ mA}$$

$$h_{ie} = 1 \text{ k}\Omega$$

$$h_{fe} = 100$$

$$h_{oe} = 4 \times 10^{-5}$$

$$h_{re} = 10^4$$

$$f_T = 10 \text{ MHz}$$

$$C_{cb} = 2 \text{ pF}$$

$$V_T = 26 \text{ mV}$$

$$g_m = \frac{i_c}{V_T} = \frac{5 \text{ mA}}{26 \text{ mA}} = 192.30 \text{ m.mhos.}$$

$$g_{be} = \frac{g_m}{h_{fe}} = \frac{192.30 \times 10^{-3}}{100} = 1.92 \text{ m.mhos.}$$

$$\gamma_{be} = \frac{1}{g_{be}} = \frac{1}{1.92 \times 10^{-3}} = 520 \text{ }\Omega.$$

$$\gamma_{bb} = h_{ie} - \gamma_{be} = 1 \text{ k} - 520 \text{ }\Omega = 480 \text{ }\Omega.$$

$$g_{bc} = g_{be} h_{re} = 1.92 \times 10^{-3} \times 10^4 = 192 \text{ n.mhos.}$$

$$\gamma_{bc} = \frac{1}{g_{bc}} = 5.20 \text{ M}\Omega.$$

$$g_{ce} = h_{oe} - g_m h_{re} = 4 \times 10^{-5} - 192.30 \times 10^{-3} \times 10^4 = 80.77 \mu\text{mhos.}$$

We know that

$$f_T = \frac{g_m}{2\pi(C_e + C_C)}$$

$$10 \times 10^6 = \frac{192.30 \times 10^{-3}}{2\pi(C_e + 2 \times 10^{-12})}$$

$$2 \times 10^{-12} + Ce = \frac{192.30 \times 10^{-3}}{2\pi \times 10 \times 10^6}$$

$$Ce = 3.06 \times 10^{-9} - 2 \times 10^{-12}$$

$$Ce = 3.05 \text{ nF}$$

→

5. Following are the measurements of a transistor at room temperature,  $i_c = 5 \text{ mA}$ ,  $V_{ce} = 10 \text{ V}$ ,  $h_{fe} = 100$ ,  $h_{ie} = 600 \Omega$ ,  $|A_I| = 10$  at  $10 \text{ MHz}$ ,  $C_c = 3 \text{ pF}$ . Find  $\gamma_{be}$ ,  $\gamma_{bb}$ ,  $f_p$ ,  $f_T$ ,  $C_e$ ,  $R_\alpha$ .

A. Given

$$i_c = 5 \text{ mA}$$

$$V_{ce} = 10 \text{ V}$$

$$h_{fe} = 100$$

$$h_{ie} = 600 \Omega$$

$$|A_I| = 10 \text{ at } 10 \text{ MHz}$$

$$C_c = 3 \text{ pF}$$

$$g_m = \frac{i_c}{V_T} = \frac{5 \text{ mA}}{26 \text{ mA}} = 192.30 \text{ m mhos.}$$

$$\gamma_{be} = \frac{g_m}{h_{fe}} = \frac{192.30 \text{ m mhos}}{100} = 1.92 \text{ m mhos.}$$

$$\gamma_{be} = \frac{1}{g_{be}} = 520 \Omega$$

$$\gamma_{bb} = h_{ie} - \gamma_{be} = 600 - 520 = 80 \Omega$$

We know that

$$|A_I| = \frac{h_{fe}}{\sqrt{1 + (\frac{R_o}{f_p})}}$$

$$\text{at } f = 10 \text{ MHz}, |A_I| = 10$$

$$10 = \frac{100}{\sqrt{1 + \left(\frac{10 \times 10^6}{f_p}\right)}}$$

$$\sqrt{1 + \left(\frac{10 \times 10^6}{f_p}\right)^2} = \frac{100}{10}.$$

$$1 + \left(\frac{10 \times 10^6}{f_p}\right)^2 = 100.$$

$$\left(\frac{10 \times 10^6}{f_p}\right)^2 = 99$$

$$\left(\frac{10 \times 10^6}{f_p}\right)^2 = f_p^2.$$

$$\frac{10 \times 10^6}{99} = f_p^2$$

$$f_p = \sqrt{\frac{(10 \times 10^6)^2}{99}}$$

$$f_p = 1 \text{ MHz.}$$

$$f_T = h_{fe} f_p.$$

$$= 100 \times 1 \text{ M}$$

$$= 100 \text{ MHz.}$$

$$f_T = \frac{9m}{2\pi [C_e + C_C]} \Rightarrow 100 \times 10^6 = \frac{192 \cdot 30 \times 10^{-3}}{2\pi [C_e + 3 \times 10^{-12}]}$$

$$C_e + 3 \times 10^{-12} = \frac{192 \cdot 30 \times 10^{-3}}{2\pi \times 100 \times 10^6}$$

$$C_e = 306.05 \times 10^{-12} - 3 \times 10^{-12}$$

$$C_e = 303.05 \text{ pF.}$$

$$f_\alpha = (1 + \beta) f_p \quad (\beta \approx h_{fe})$$


$$f_\alpha = (1 + h_{fe}) f_p$$

$$f_\alpha = (1 + 100) 1 \times 10^6.$$


$$= 101 \text{ MHz.}$$

## ET high frequency Model:


DC frequency model of FET is given by

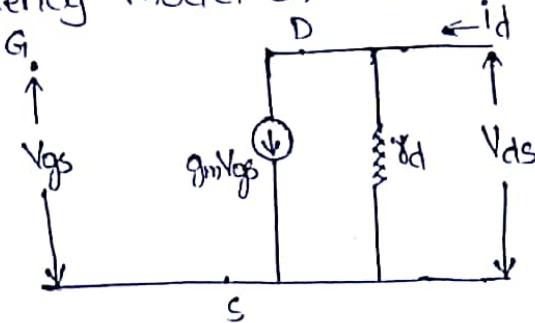

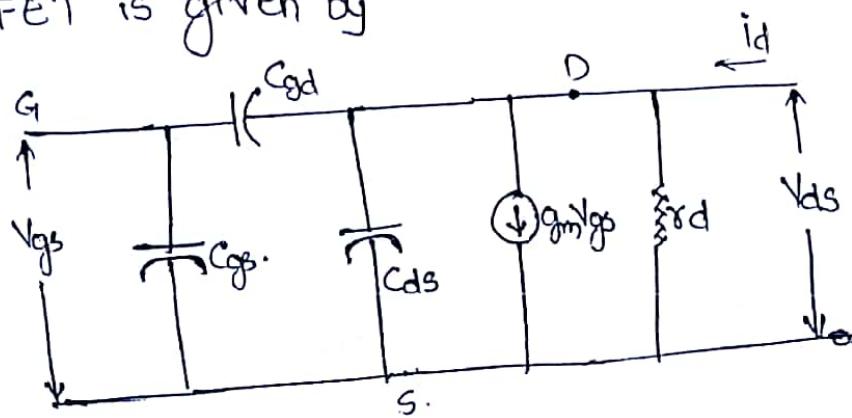
At high frequencies junction capacitors will begin to dominate the frequency response. So the high frequency model of the FET is given by


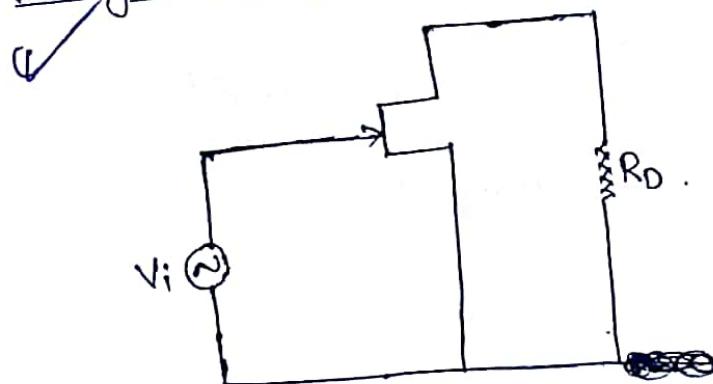
## Analysis of common source amplifier at High frequencies:



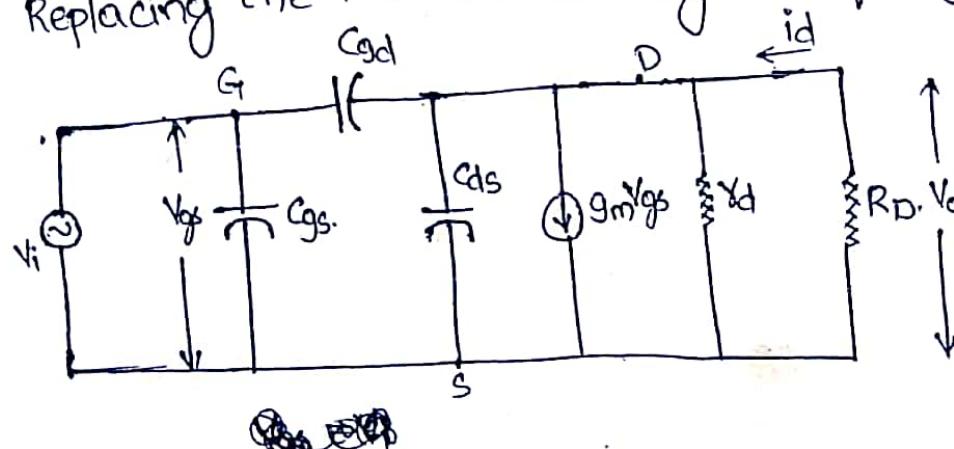Voltage Gain:  
Replacing the FET with its high frequency model.



$$V_{GS} = V_i$$

Let  $Y_{DS}$ ,  $Y_{GD}$ ,  $Y_{GS}$  are the admittances of the capacitors.

By writing KCL at the output node

$$i_d = \frac{V_o}{R_d} + g_m V_{GS} + Y_{DS} V_o + (V_o - V_{GS}) Y_{GD}$$

$$\text{Replace } V_{GS} = V_i, i_d = \frac{-V_o}{R_D}$$

$$-\frac{V_o}{R_D} = \frac{V_o}{R_d} + g_m V_i + Y_{DS} V_o + (V_o - V_i) Y_{GD}$$


$$V_i (Y_{GD} - g_m) = V_o \left( \frac{1}{R_D} + \frac{1}{R_d} + Y_{DS} + Y_{GD} \right)$$

$$\frac{V_o}{V_i} = \frac{(Y_{GD} - g_m)}{\left( \frac{1}{R_D} + \frac{1}{R_d} + Y_{DS} + Y_{GD} \right)}$$

$$\frac{V_o}{V_i} = R_D Y_{GD} (Y_{GD} - g_m)$$

$$AV = \boxed{\frac{V_o}{V_i} = \frac{-g_m + Y_{GD}}{\frac{1}{R_D} + \frac{1}{R_d} + Y_{DS} + Y_{GD}}}$$

Output Impedance :-

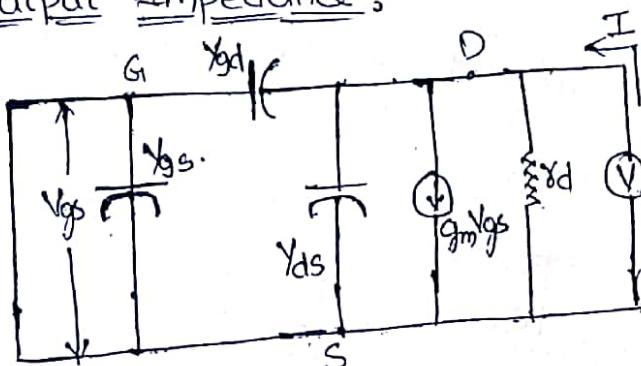


To find the output impedance set  $V_i = 0$ , disconnect  $R_D$  and connect source  $V$ .

$$Y_O = \frac{V}{I}$$

$$\Rightarrow Y_O = \frac{I}{V}$$

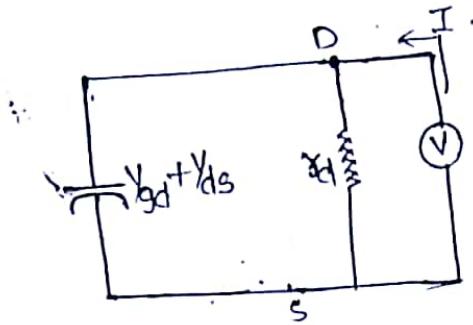Rearranging the above circuit and observing that  $V_{GS} = C$ . we get the following circuit.



By applying KCL at output node O.

$$I = \frac{V}{R_d} + V(Y_{ds} + Y_{gd})$$

$$\frac{I}{V} = Y_o = \frac{1}{R_d} + (Y_{ds} + Y_{gd})$$

Output Admittance including  $R_d$ .


$$Y'_o = Y_o \parallel \frac{1}{R_d}$$

$$= Y_o + \frac{1}{R_d}$$

$$Y'_o = \frac{1}{R_d} + \frac{1}{R_d} + Y_{ds} + Y_{gd}$$

Input impedance/admittance :-

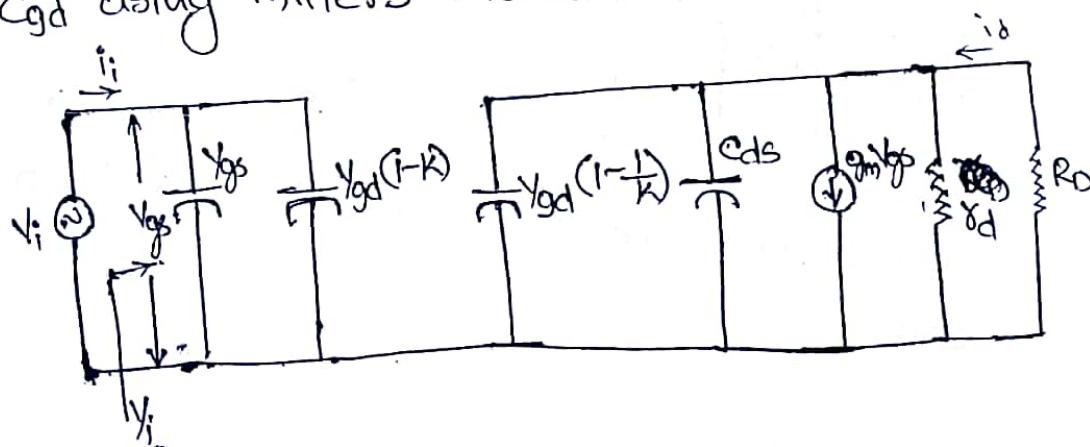To find the input impedance split the feed back capacitor  $C_{gd}$  using miller's theorem.



Input admittance  $Y_i = Y_{gs} + Y_{gd}(1-K)$  where  $K = Av$ .


Net input capacitance

$$C_i = C_{gs} + C_{gd}(1-K)$$


$$A\dot{I} = \frac{-id}{i_i} = \frac{\frac{V_o}{R_D}}{\frac{V_i}{R_i}} = \frac{V_o}{V_i} \cdot \frac{R_i}{R_D} = A\dot{V} \cdot \frac{1}{Y_i} \cdot \frac{1}{R_D}$$

05/12/18  
Wednesday
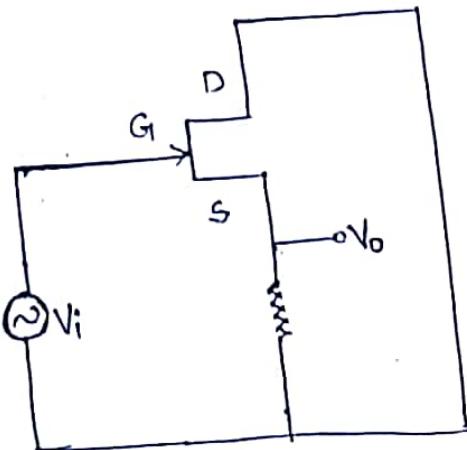
## Common drain Amplifier analysis at High frequencies:



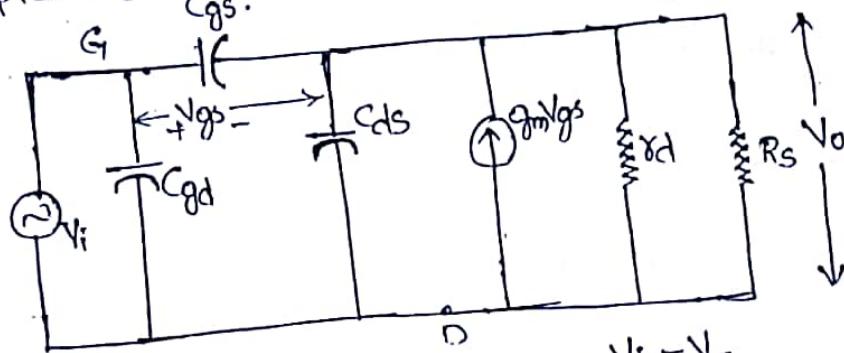Replacing the FET with high  $C_{gs}$ . Frequency model.



In the above circuit  $V_{gs} = V_i - V_o$   
Voltage Gain:

Applying KCL at output node.

$g_m V_{gs} = \frac{V_o}{Y_d} + \frac{V_o}{R_S} + V_o Y_{ds} + (V_o - V_i) Y_{gs}$ .

$$g_m V_{gs} = V_o \left[ \frac{1}{Y_d} + \frac{1}{R_S} + Y_{ds} + Y_{gs} \right] - V_i Y_{gs}.$$

$$g_m (V_i - V_o) = V_o \left[ \frac{1}{Y_d} + \frac{1}{R_S} + Y_{ds} + Y_{gs} + g_m \right] = V_i [g_m + Y_{gs}]$$


$$A\dot{V} = \frac{V_o}{V_i} = \frac{g_m + Y_{gs}}{\frac{1}{Y_d} + \frac{1}{R_S} + Y_{ds} + Y_{gs} + g_m}$$

∴

Input admittance:

- find output admittance set  $V_i = 0$  and disconnect  $s$  and connect voltage source  $V$

$$Y_o = \frac{I}{V}$$

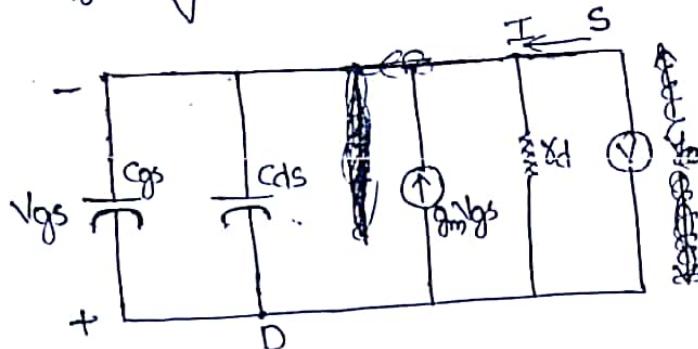

KCL gives

$$I + g_m V_{gs} = \frac{V}{r_d} + V Y_{ds} + V Y_{gs}$$

In the above circuit  $V_{gs} = -V$

$$I - g_m V_{gs} = \frac{V}{r_d} + V Y_{ds} + V Y_{gs}$$

$$I = V \left[ g_m + \frac{1}{r_d} + Y_{ds} + Y_{gs} \right]$$


$$Y_o = \frac{I}{V} = g_m + \frac{1}{r_d} + Y_{ds} + Y_{gs}$$

$$Y'_o = Y_o \parallel \frac{1}{R_s} = Y_o + \frac{1}{R_s}$$


$$Y'_o = g_m + \frac{1}{r_d} + Y_{ds} + Y_{gs} + \frac{1}{R_s}$$

Input admittance:

Input admittance:

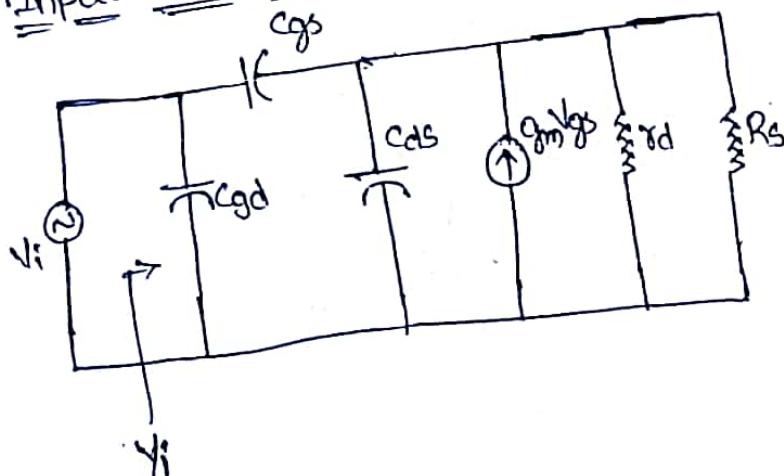

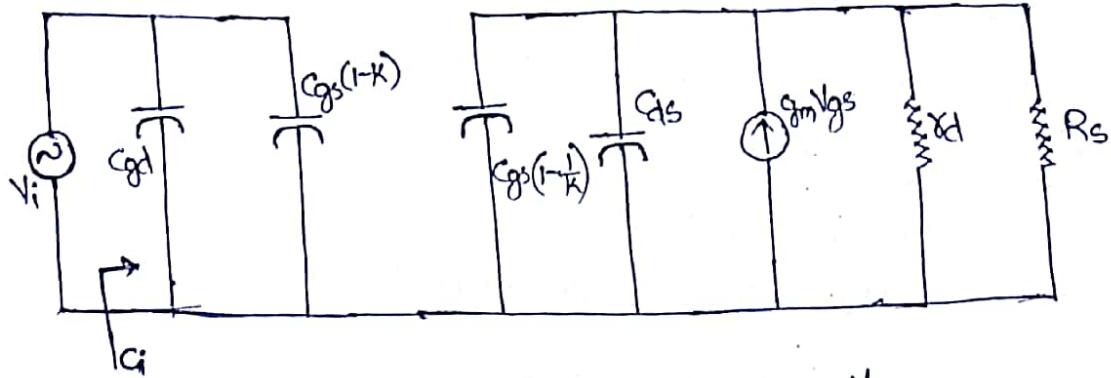To find the input admittance the capacitance  $C_{gs}$  is split in two parts using miller's theorem as shown in the follow figure.



$$C_i = C_{gd} + C_{gs}(1-k) \quad , \text{ where } k = A_v = \frac{V_o}{V_i}$$

$$C_i = C_{gd} + C_{gs}(1-A_v)$$

$$Y_i = Y_{gd} + Y_{gs}(1-A_v)$$

## unit-2

### Multi-stage Amplifiers

#### Amplifier:-

It is an electronic device which is used to amplify a weak signal into a sufficiently strong signal.

#### Multi-stage Amplifiers:-

If the system contains several amplifiers cascaded together that system is called multi-stage amplifier.


The process of connecting output of one amplifier to the input of another amplifier is called cascading.

#### Need for Multi-stage Amplifiers:-

##### Reason:-
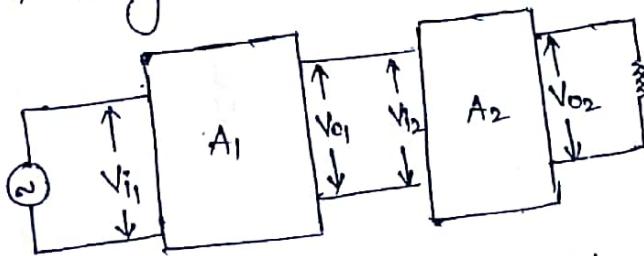
##### To achieve larger gain :-

If the gain of a single stage is not sufficient when the output of this stage can be connected to another stage and the overall gain will be the product of both stages.



$$\text{The overall gain } AI = \frac{V_{o2}}{V_{i1}} = \frac{V_{o2}}{V_{i2}} \times \frac{\frac{V_{i2}}{V_{i1}}}{\frac{V_{i2}}{V_{i1}}} \times \frac{V_{o1}}{V_{i1}} \quad [\text{But } V_{o1} = V_{i2}]$$

$$AI = \frac{V_{o2}}{V_{i2}} \times \frac{V_{o1}}{V_{i1}}$$


$$AI = A_2 A_1$$

as/12/18  
Thursday

### Reason - 2 :-
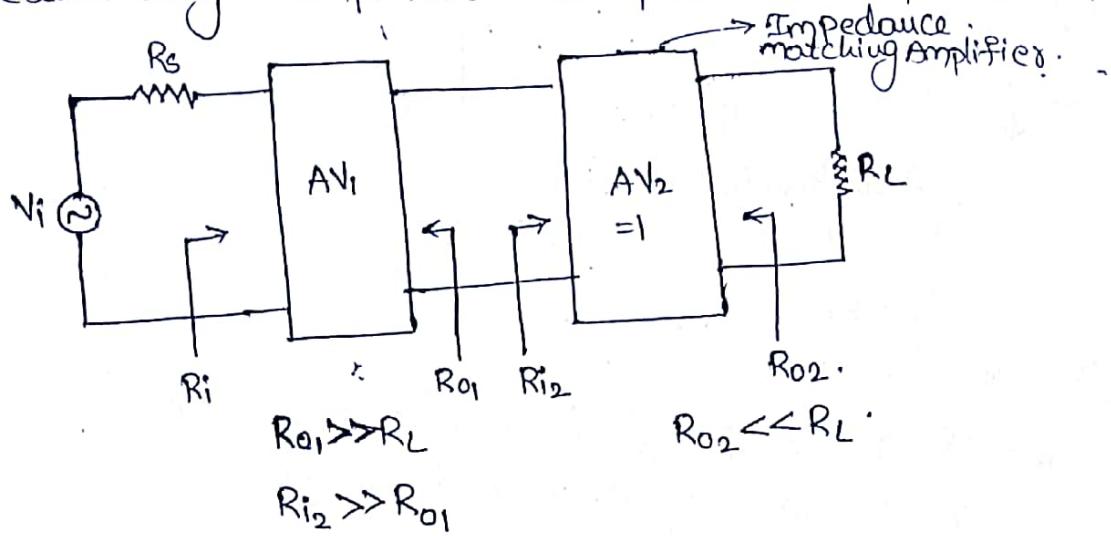
#### To provide Impedance Matching:

If the output impedance of an amplifier is not properly matched with load impedance  $R_L$ , then we need an extra stage amplifier that provides impedance matching.



### Distortion :-

If the output of the amplifier is not an exact replica of the input then we say that the amplifier has distortion.

#### Types of Distortion

1) Non-linear Distortion (2) Harmonic Distortion (3) Amplitude Distortion

2) Frequency Distortion



3) Phase Distortion

1) Non-Linear Distortion (2) Harmonic Distortion (3) Amplitude Distortion

If the dynamic transfer curve of the amplifier is not a straight line non-linear distortion occurs.


In this type of distortion output contains signals with fundamental frequency and signals which are harmonics.

? the fundamental frequency.

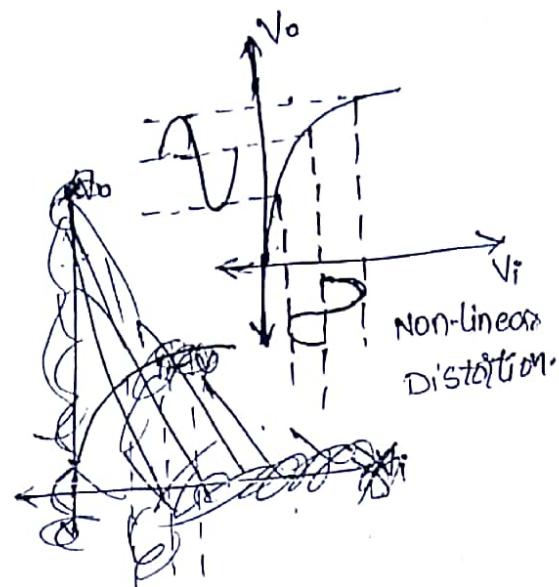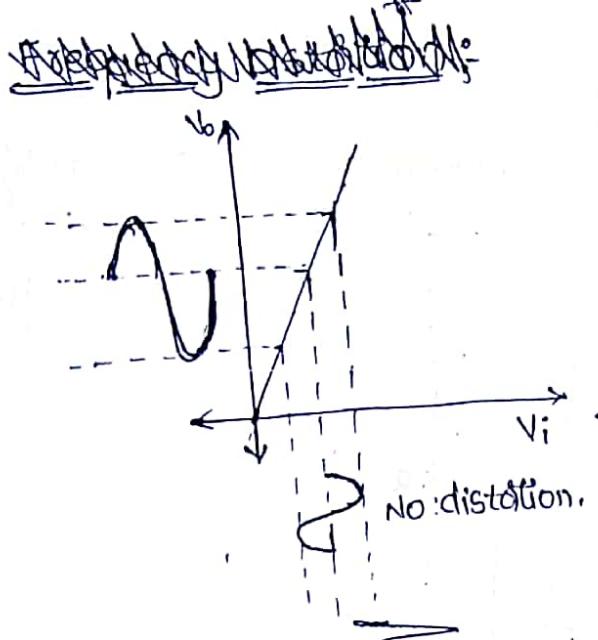

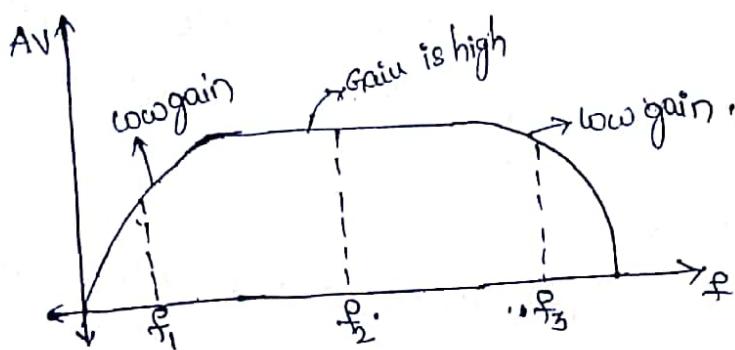
### Frequency Distortion:

If the amplifier provides different gains at different frequencies then we say that the amplifier has frequency distortion.


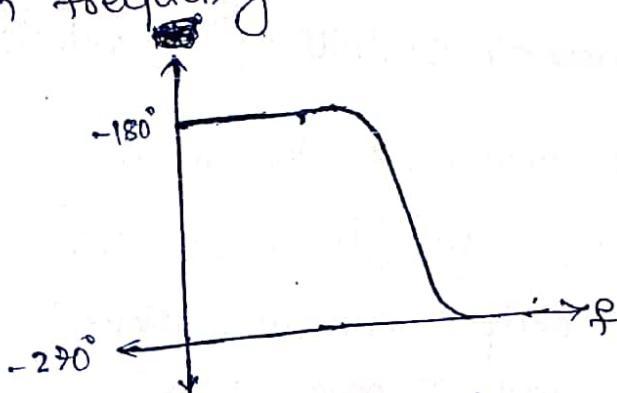
### Phase Distortion:

If the phase shift provided by the amplifier changes with frequency then there exist phase distortion.



## Methods of coupling in Multi stage Amplifiers:

There are 3 types of coupling mechanisms used in multi-stage amplifier; depending upon the type of coupling.

1) RC coupled Amplifiers


2) Transformer coupled Amplifier.

3) Direct coupled Amplifier.

### 1) RC coupled Amplifier:-

In this type of Amplifiers the output of previous stage is coupled to the next stage through coupling capacitor and resistive load. This type of coupling

is shown in following figure.

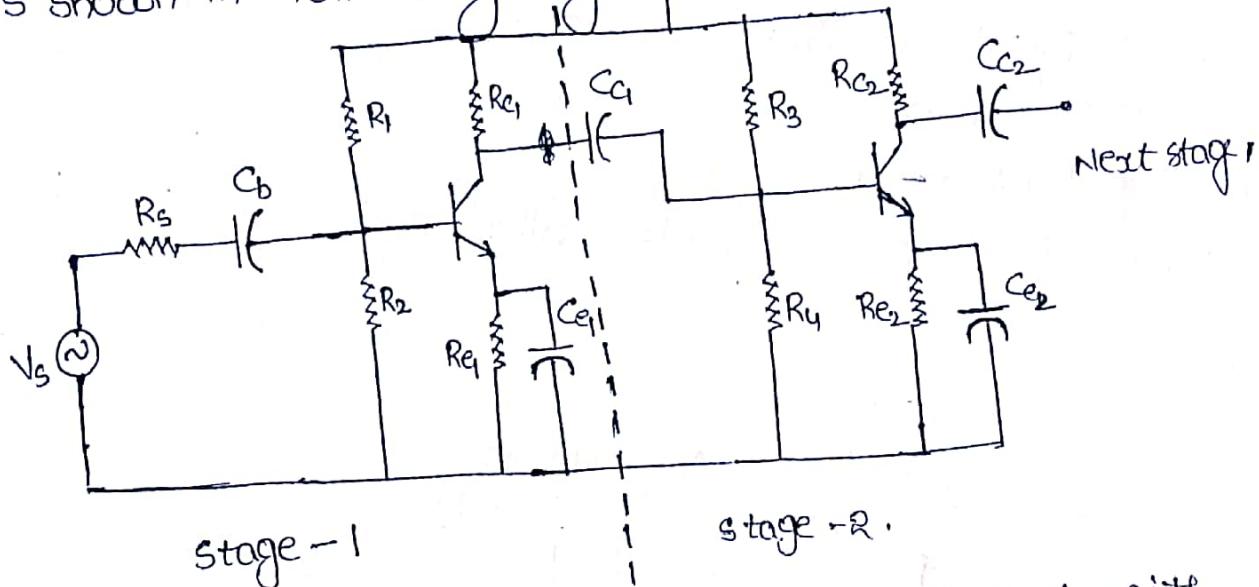

In the above figure capacitor  $C_c$  connects stage-1 with stage-2. This capacitor is called coupling capacitor.

At low frequencies impedance of  $C_c$  is high

∴ Amount of signal reaching the next stage will be low


As frequency increases impedance of  $C_c$  decreases

and more signal reaches the next stage, so gain increases.

At mid frequencies,  $C_c$  is almost a short circuit.

∴ Gain will be maximum and constant.

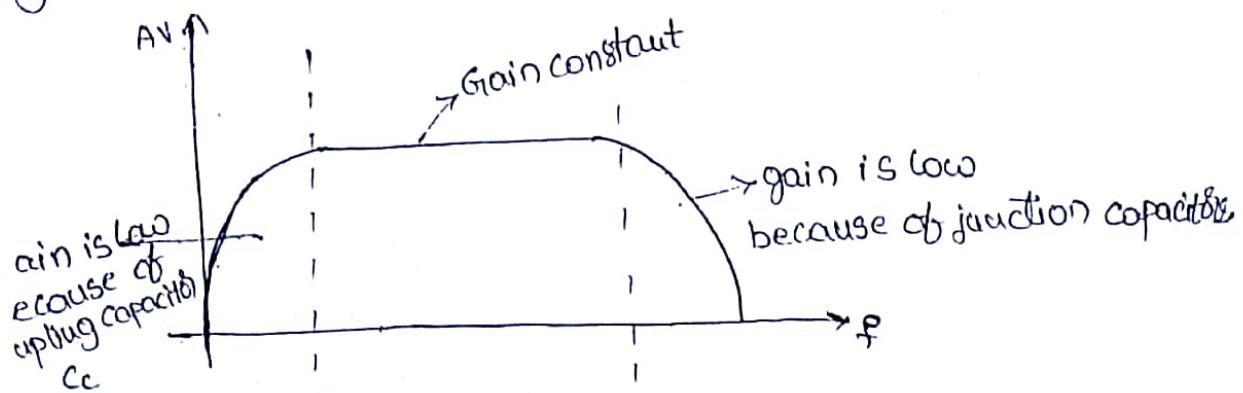high frequencies junction capacitors will appear parallel to the signal path. These capacitors will pass the AC signal and hence gain decreases at high frequencies.




### Frequency response of RC coupled amplifier.

= In DC signals coupling capacitor  $C_c$  is an open circuit. The DC signal of one stage will not interact with the DC signal of next stage.

Hence this capacitor is also called as blocking capacitor.


7/12/18  
Friday.

### Transformer Coupled Amplifiers:

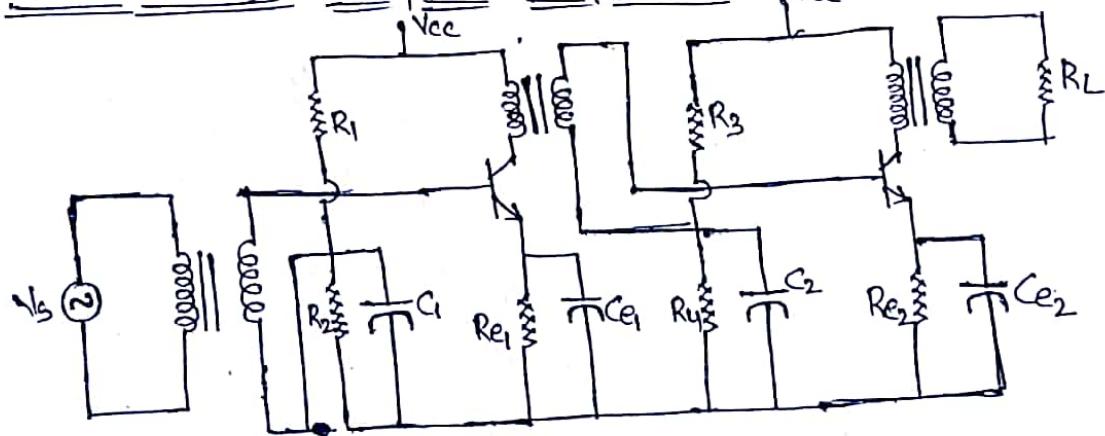


In the above figure output of one stage connected to the input of another stage through a transformer since transformer couples only AC signals and blocks DC signals.

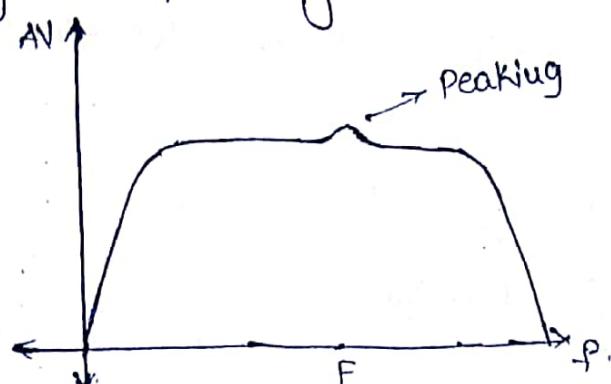$\therefore$  DC signals of individual sources are isolated.  
 The frequency response of transformer coupled amp  
 may have peaking



### Direct coupled Amplifiers:

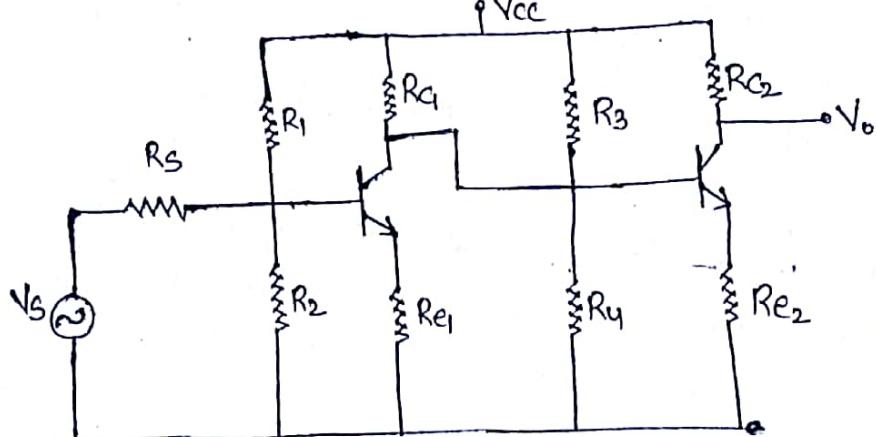

The above figure shows a direct coupled amplifier. Because of direct coupling the low frequency response will be very good.

At high frequencies the gain will be falls due to junction capacitors.

The DC signals of one stage interact with DC signals of next stages.

$\therefore$  care must be taken in the design.


The Frequency response of a direct coupled Amplifier is.



Effect of coupling, Bypass, Junction capacitors on the frequency response of RC coupled Amplifiers:

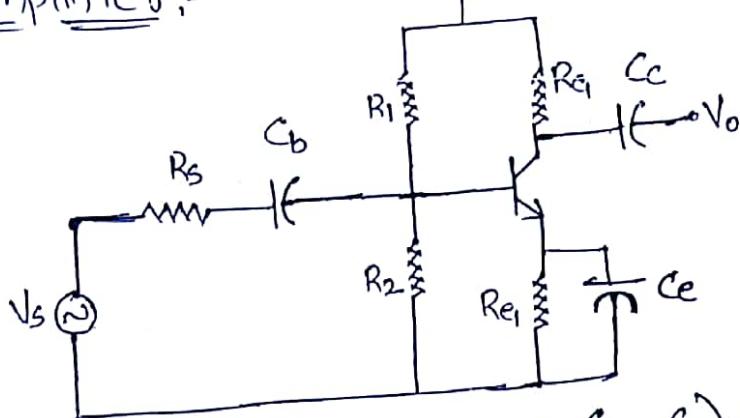(Q1)

Explain the frequency response curve of RC coupled Amplifiers:



Coupling & Blocking capacitors ( $C_c, C_b$ ):

\* These capacitors will block the DC signals and allow only AC signal.

\* At low frequencies the impedance of the capacitor is high. It allows less amount of AC signal to pass through and hence gain will be low.

\* At mid frequencies the impedance of  $C_c, C_b$  will be very low and hence they act as short circuit and gain will be high.

Bypass capacitor ( $C_e$ ):

If bypass capacitor  $C_e$  is not present, both AC & DC signals will pass through  $R_e$ . This will provide negative feed back for AC signal and gain decreases.

To avoid this by pass capacitor  $C_e$  must be connected across  $R_e$ .


Now AC signals with  $C_e$  and DC signals will pass through  $R_e$ . and hence AC signal feed back is avoided.

## Junction capacitors:-

These capacitors are also called as parasitic capacitors. At low & mid frequencies they act as open circuits because they are very very small capacitors. Hence there is no impact on frequency response at low & mid frequencies.

At high frequency the impedance of these capacitors begins to fall.


∴ The gain also begins to fall.

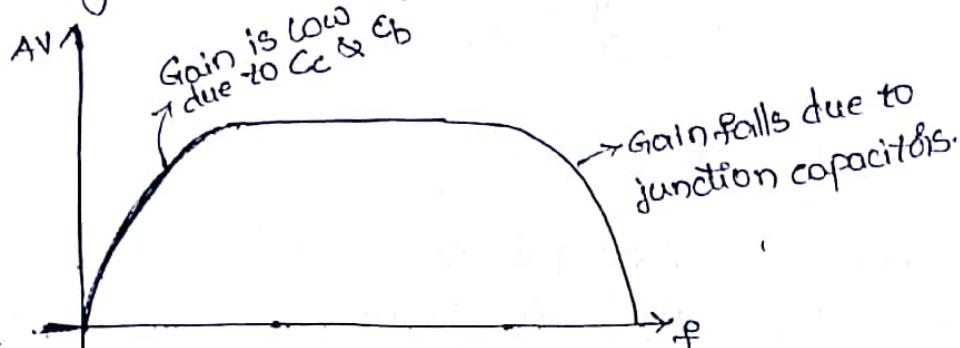

08/12/18  
Saturday.
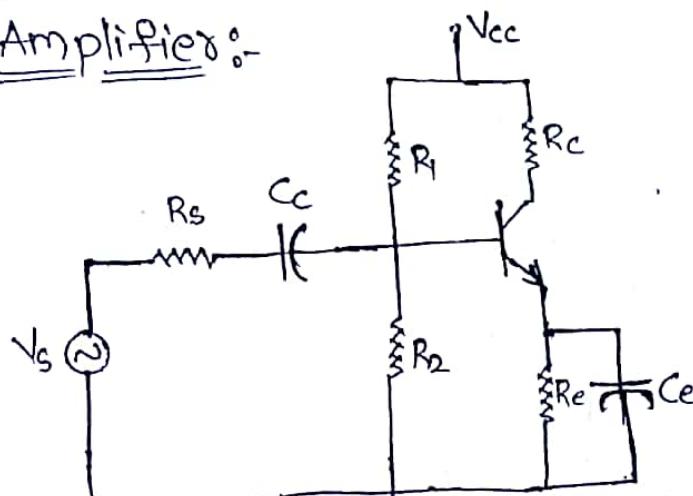
## Effect of coupling capacitor on the Low Frequency Response:

Lower cut off frequency due to  $C_c$  in a RC coupled Amplifier:-




The above figure shows RC coupled amplifier.


Let  $C_e \gg C_c$

∴ The impact of  $C_e$  can be neglected and it can be replaced with a short circuit.



The AC equivalent circuit is given by

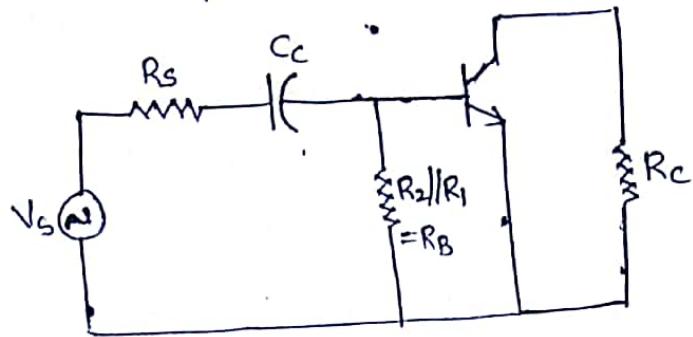

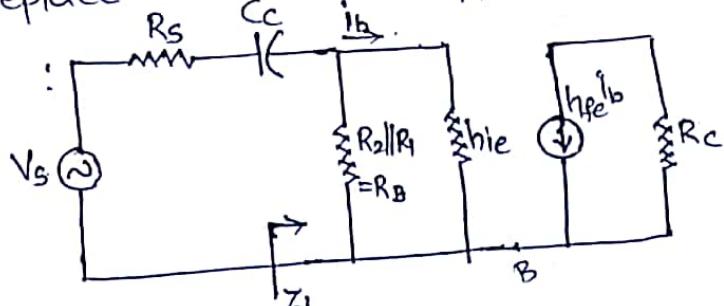Replace BJT with approximate h-parameter model.



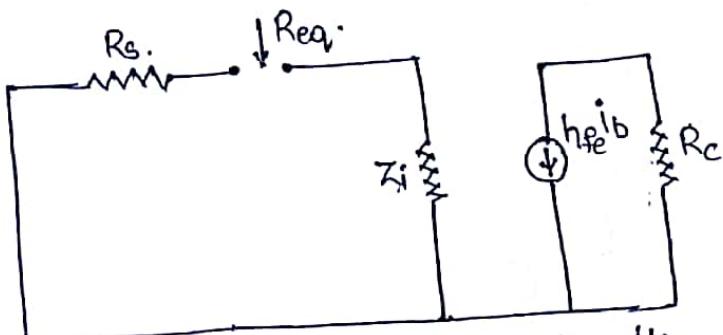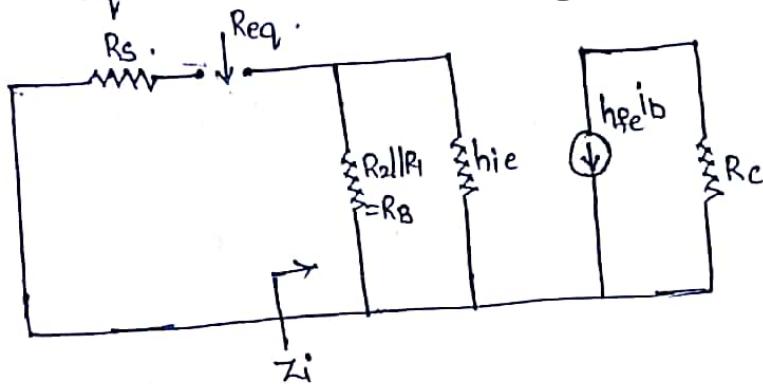To find equivalent resistance seen by  $C_c$ . Set  $V_s = 0$  and find  $R_{eq}$  from the following circuit.



$$\text{where } Z_i = R_B \parallel h_{ie} \approx R_1 \parallel R_2 \parallel h_{ie}$$

$$R_{eq} = Z_i + R_s$$

The cut off frequency due to  $C_c$  is given by


$$\therefore f_L = \frac{1}{2\pi R_{eq} C_c}$$

$$\therefore f_L = \frac{1}{2\pi(R_s + Z_i)C_C}$$



Impact of bypass capacitor ( $C_C$ ) on the low frequency response (i) lower cut off frequency of the RC coupled Amplifier due to bypass capacitor ( $C_C$ ):

Assume  $C_C \gg C_e$

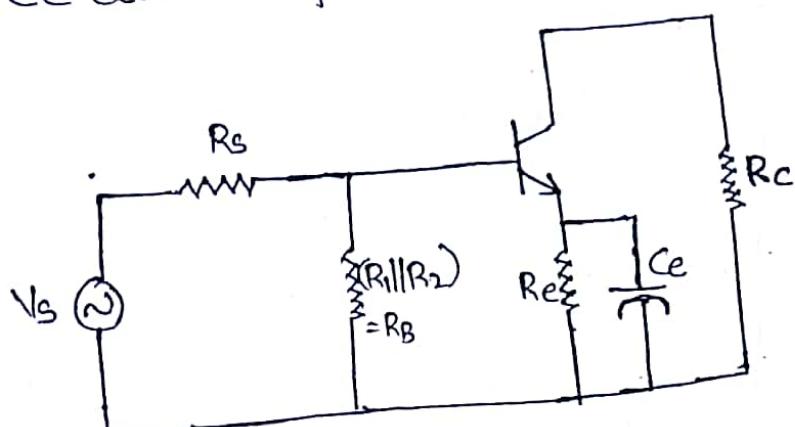∴ The lower cut off frequency is decided by  $C_e$  and  $C_C$  can be replaced with a short circuit.



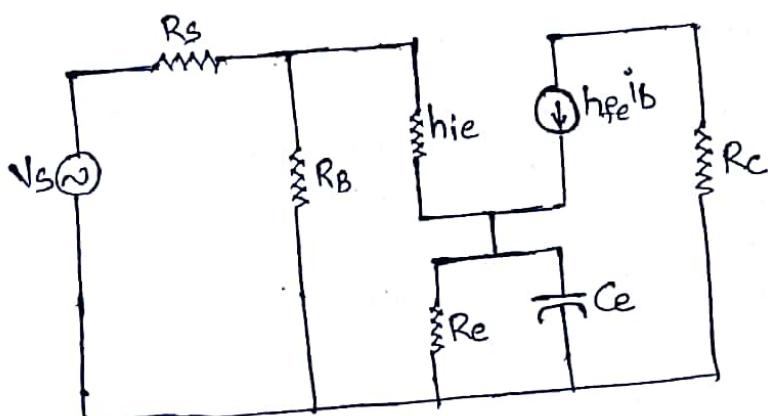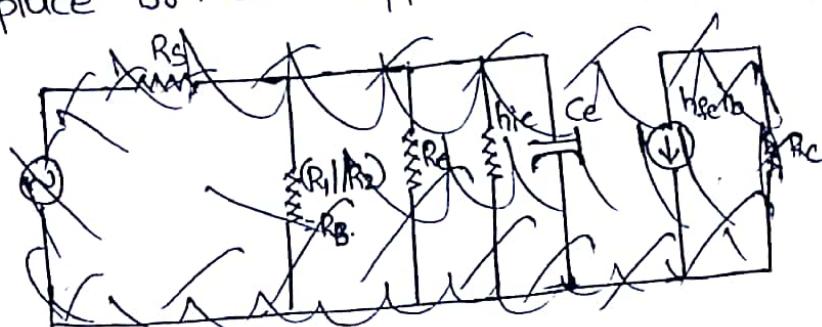Replace BJT with approximate h-parameter model.




To find the cut off frequency due to  $C_e$ . we must find the equivalent resistance seen by  $C_e$ .


set  $V_s = 0$ , Remove  $R_e$ ,  $C_e$ .

assume independent voltage source  $V$ . let  $I$  be the current.

$$\text{let } R_o = \frac{V}{I}$$

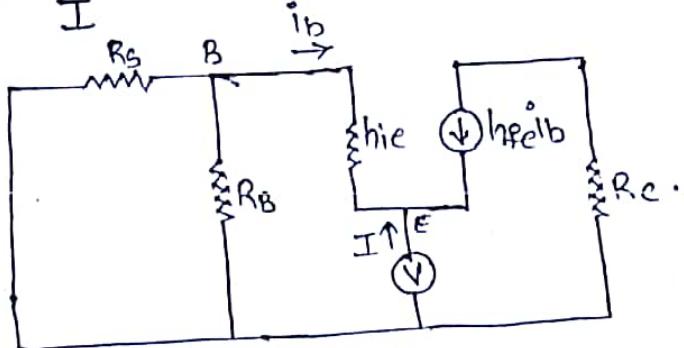

$$\text{let } R_s \parallel R_B = R'_s$$

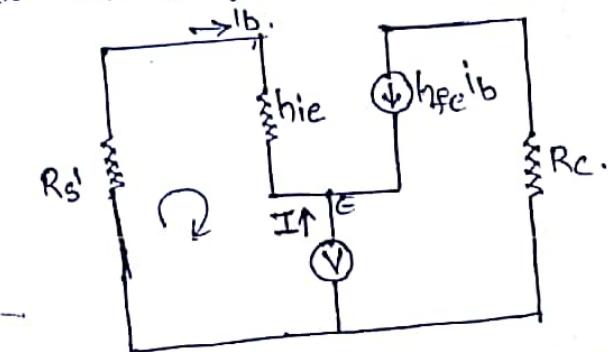

By Applying KVL & KCL at emitter node.

$$i_b + I + h_{fe}i_b = 0$$

$$i_b(1 + h_{fe}) = -I$$

$$I = -(1 + h_{fe})i_b$$

By applying KVL to the <sup>input</sup> loop


$$R'_s i_b + h_{ie} i_b + V = 0$$

$$V = -(R'_s + h_{ie}) i_b$$

$$R_o = \frac{V}{I} = \frac{-(R'_s + h_{ie}) i_b}{-(1 + h_{fe}) i_b}$$

$$\therefore R_o = \frac{V}{I} = \frac{(R'_s + h_{ie})}{1 + h_{fe}}$$

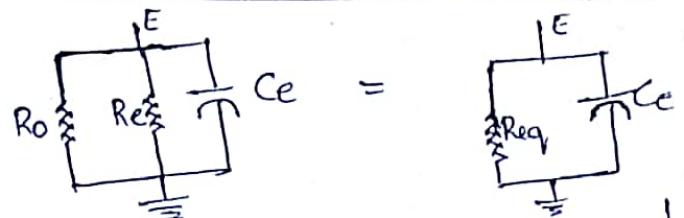∴ The effective circuit between the emitter and ground is.




$$\therefore \text{cut off frequency } f_L = \frac{1}{2\pi R_{\text{req}} C_e}$$

$$\therefore f_L = \frac{1}{2\pi [(R_s + h_{ie})/(R_e)] C_e}$$


12/12/2018  
Wednesday.

Analysis of RC coupled Amplifier at low, mid, high frequency Range :-

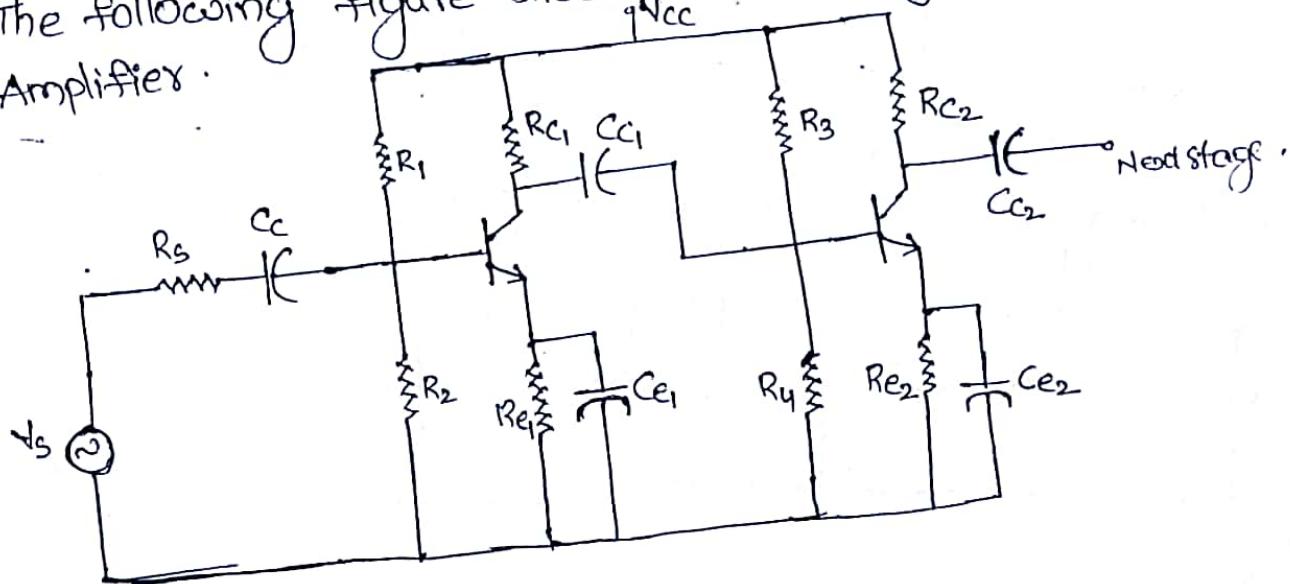The following figure shows a two stage RC coupled Amplifier.




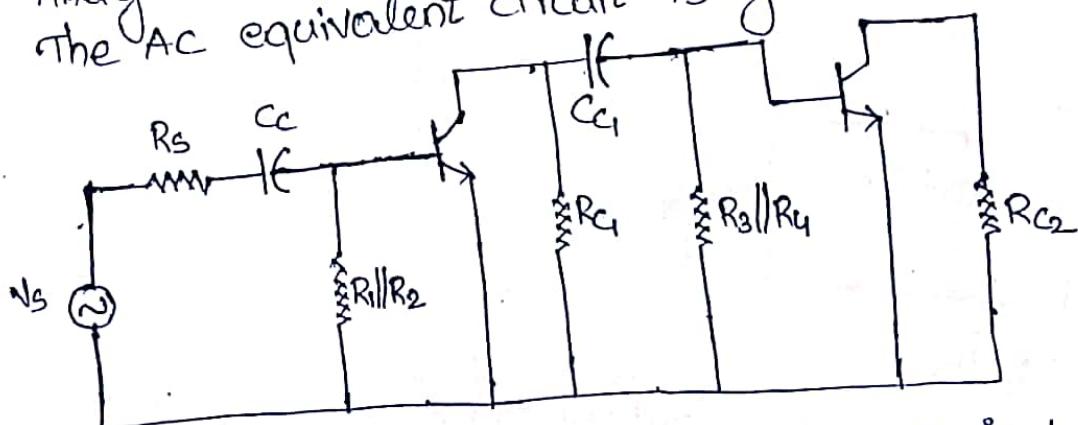\*Analysis  
The AC equivalent circuit is given by




In the above figure, we assumed that  $C_e$  is large.

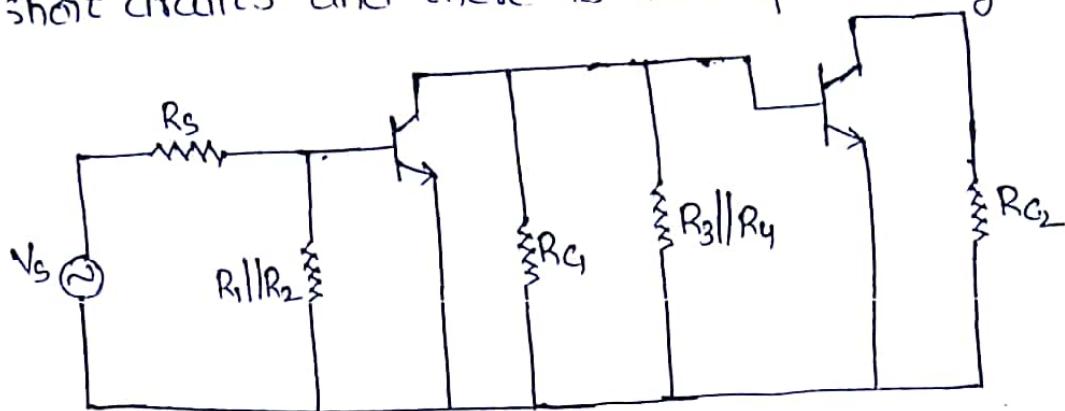
Analysis in the mid frequency Range (Mid Frequency Gain):  
 At mid frequencies coupling capacitors can be replaced with short circuits and there is no impact of junction capacitors.



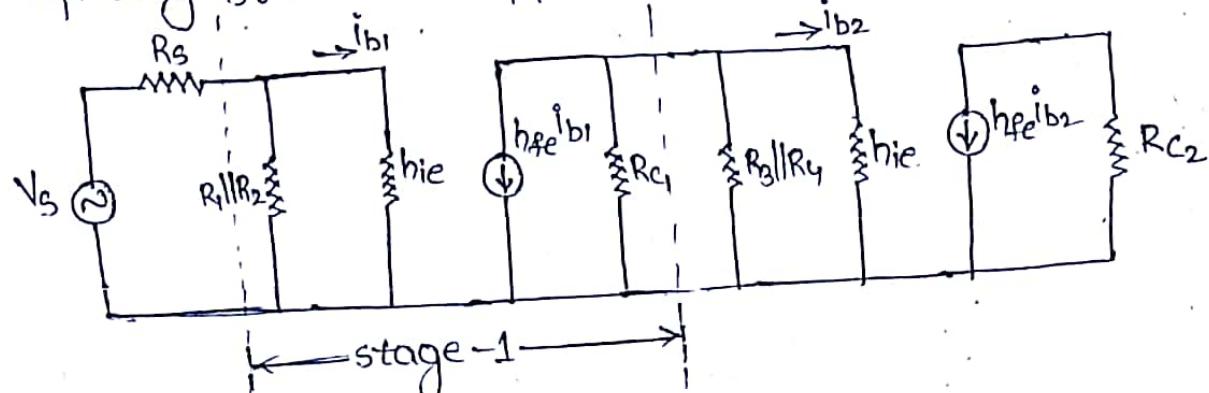Replacing BJT with approximate H-parameter model.



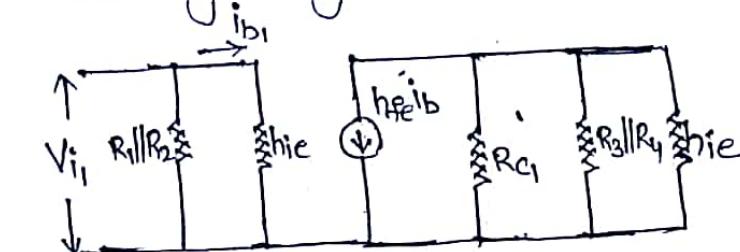Isolating stage-1, to calculate the gain.




Normally  
 $R_1, R_2 \gg h_{ie}$ .

$R_3, R_4 \gg h_{ie}$

$\therefore R_1 \parallel R_2 \parallel h_{ie} \approx h_{ie}$
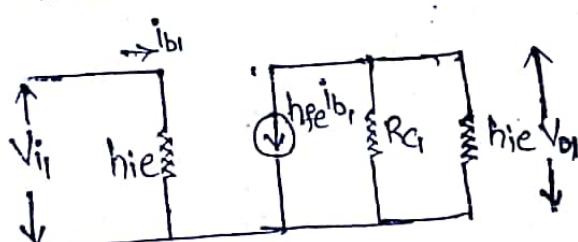
$$R_3 \parallel R_4 \parallel h_{ie} \approx h_{ie}$$



$$V_{i1} = h_{ie} i_{b1}$$

By writing the KCL at output node.

$$h_{fe} i_{b1} + \frac{V_{o1}}{R_C} + \frac{V_{o1}}{h_{ie}} = 0$$

$$V_{o1} \left[ \frac{1}{R_C1} + \frac{1}{h_{ie}} \right] = -h_{fe} i_{b1}$$

$$V_{o1} = \frac{-h_{fe} i_{b1}}{\frac{1}{R_C1} + \frac{1}{h_{ie}}} = \frac{-h_{fe} i_{b1} \cdot R_C1 \cdot h_{ie}}{R_C1 + h_{ie}}$$


∴ Mid Frequency Gain

$$A_m = \frac{V_{o1}}{V_{i1}} = \frac{-h_{fe} i_{b1} R_C1 h_{ie}}{R_C1 + h_{ie}}$$


$$A_m = \boxed{\frac{-h_{fe} R_C1}{R_C1 + h_{ie}}}$$

Analysis in the low frequency Range (low frequency gain):  
Assume  $C_e \gg C_c$ , so that the low frequency response is dominated by  $C_c$


AC circuits at low frequencies is

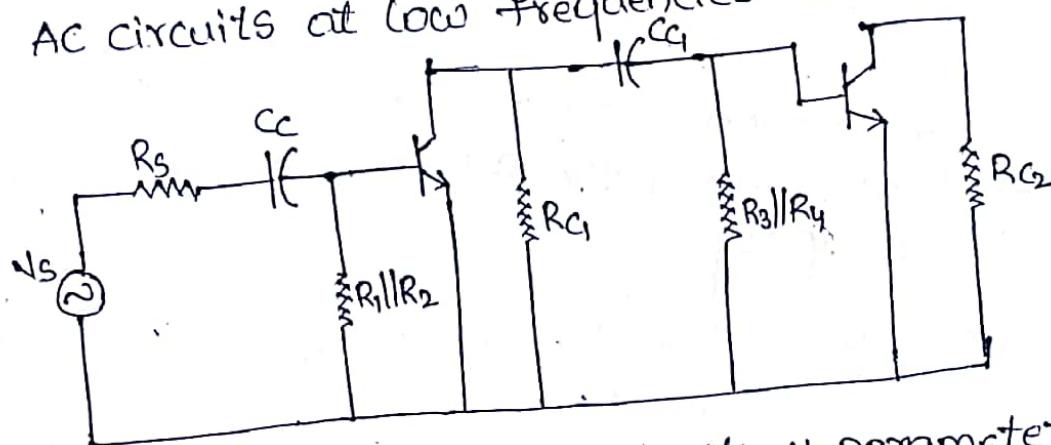

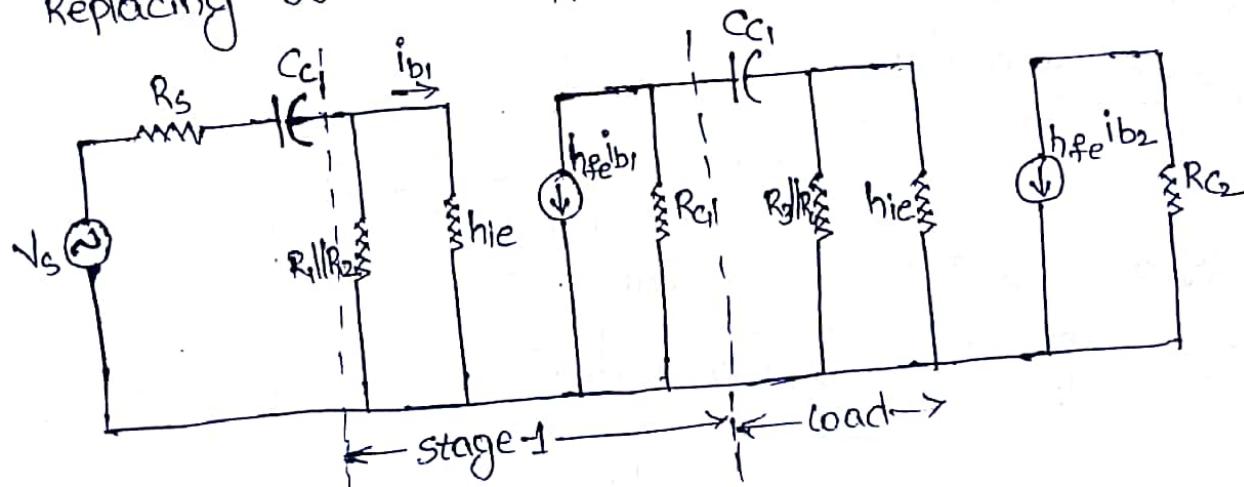Replacing BJT with approximate H-parameter model.



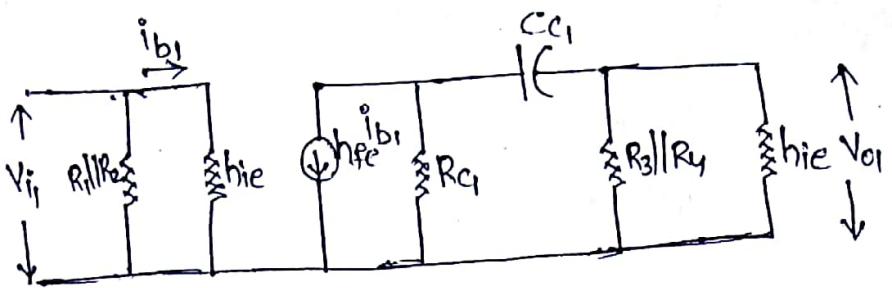Isolating stage-1 ~~and~~ including load.




Assume  $h_{ie}$  is very small.

$$R_1, R_2, R_3, R_4 \gg h_{ie}$$


$$R_1 \parallel R_2 \parallel h_{ie} \approx h_{ie}$$
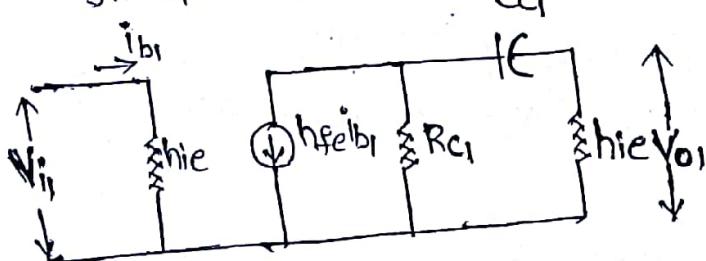
$$R_3 \parallel R_4 \parallel h_{ie} \approx h_{ie}$$



$$V_{i1} = h_{ie} i_{b1}$$

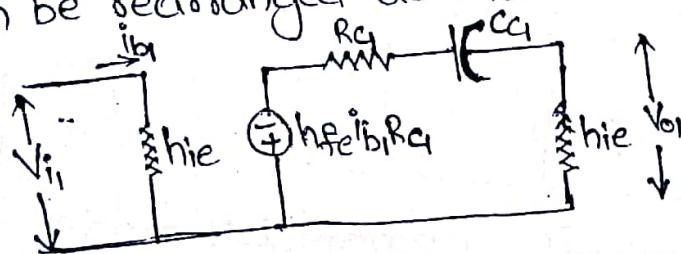using source transformation technique the above circuit can be rearranged as shown in the following figure.



From the above circuit

$$V_{o1} = \frac{-h_{fe} i_{b1} R_4 \times h_{ie}}{h_{ie} + R_4 + \frac{1}{j2\pi f C_1}}$$

Low frequency Gain :

$$A_L = \frac{V_{o1}}{V_{i1}} = \frac{\frac{-h_{fe} i_{b1} R_4 \cdot h_{ie}}{h_{ie} + R_4 + \frac{1}{j2\pi f C_1}}}{h_{ie} i_{b1}}$$

$$A_L = \frac{-h_{fe} R_4}{R_4 + h_{ie} + \frac{1}{j2\pi f C_1}}$$


$$A_L = \frac{\frac{-h_{fe} R_C}{R_A + h_{ie}}}{1 - j \frac{1}{2\pi f C_L (R_A + h_{ie})}}$$

$$A_L = \frac{A_m}{1 - j \frac{f_L}{f}} \Rightarrow |A_L| = \frac{A_m}{\sqrt{1 + \left(\frac{f_L}{f}\right)^2}}$$

$$\text{at } f = f_L; |A_L| = \frac{A_m}{\sqrt{R}}$$

$\therefore f_L$  is lower cut-off frequency.

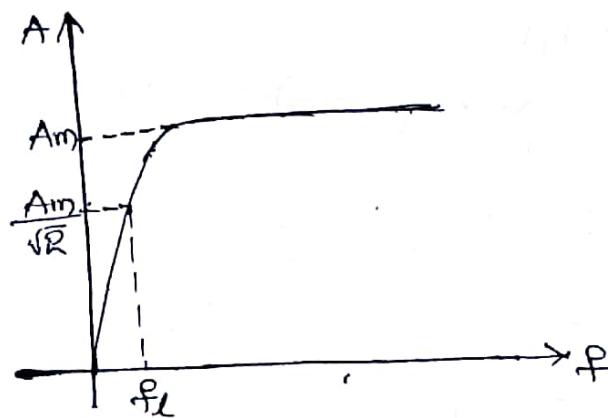
$$f_L = \frac{1}{2\pi C_L (R_A + h_{ie})}$$





13/12/18  
Thursday
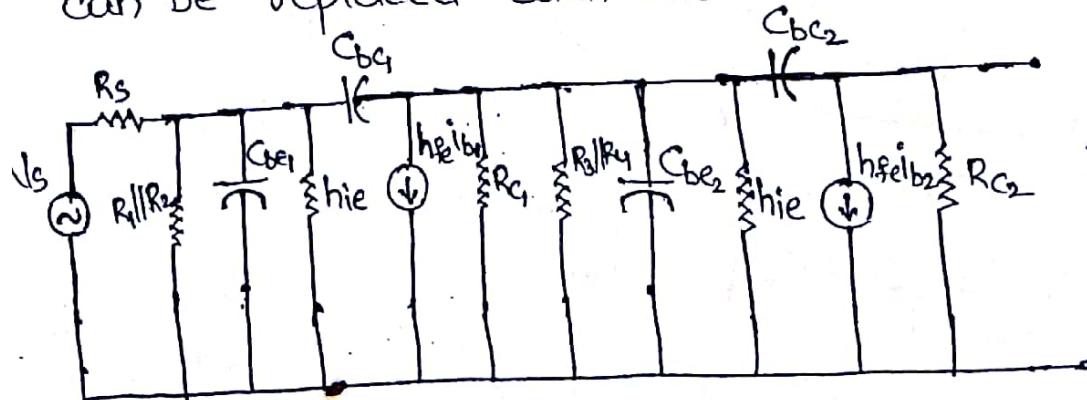
### Analysis in the high Frequency Range:

At high frequencies junction capacitors dominate the frequency response. coupling capacitor and bypass capacitor can be replaced with short circuit.



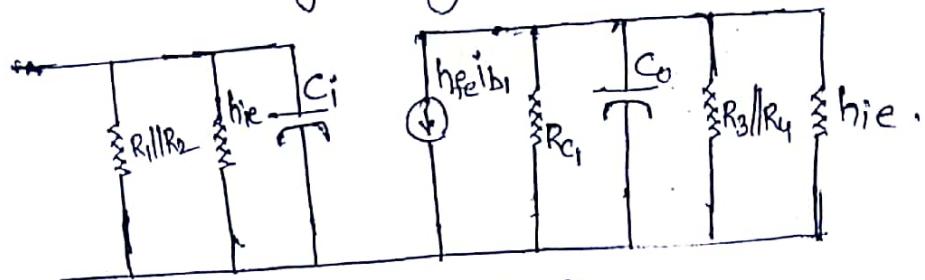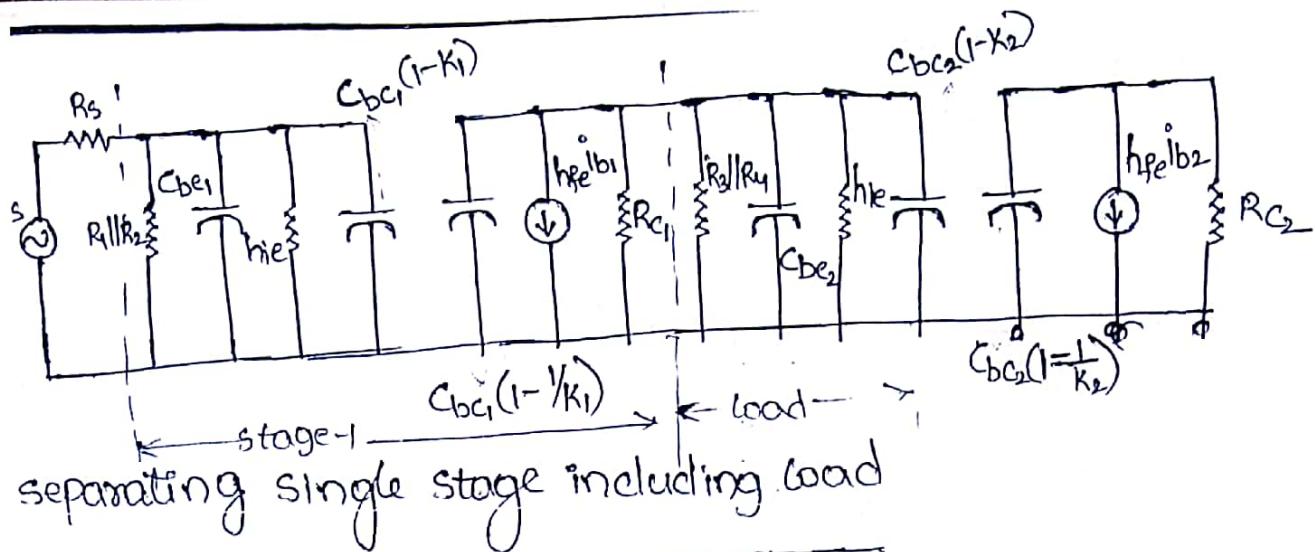


$$\text{where } C_1 = C_{be1} + C_{bc1}(1-k_1)$$

$$C_0 = C_{be2} + C_{bc2}(1-k_2) + C_{bc2}(1-k_2)$$

Assume  $R_1 \parallel R_2 \parallel h_{ie} \parallel X_C \approx h_{ie}$

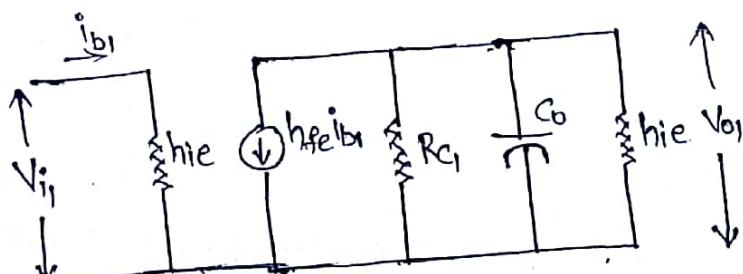$R_3 \parallel R_4 \parallel h_{ie} \approx h_{ie}$



$$V_{i1} = h_{ie} i_{b1}$$

By writing KCL at the output loop

$$h_{fe} i_{b1} + \frac{V_{o1}}{R_{C1}} + \frac{V_{o1}}{\frac{1}{j2\pi f C_0}} + \frac{V_{o1}}{h_{ie}} = 0$$

$$V_{o1} \left[ \frac{1}{R_{C1}} + \frac{1}{h_{ie}} + j2\pi f C_0 \right] = -h_{fe} i_{b1}$$

$$V_{o1} = \frac{-h_{fe} i_{b1}}{\frac{1}{R_{C1}} + \frac{1}{h_{ie}} + j2\pi f C_0}$$

$$V_{o1} = \frac{-h_{fe} i_b R_{c1} h_{ie}}{R_{c1} h_{ie} + j 2\pi f_C R_{c1} h_{ie}}$$

$$\begin{aligned} A_h &= \frac{V_{o1}}{V_{i1}} = \frac{\frac{-h_{fe} i_b \cdot R_{c1} \cdot h_{ie}}{R_{c1} + h_{ie} + j 2\pi f_C R_{c1} h_{ie}}}{h_{ie} i_b} \\ &= \frac{-h_{fe} R_{c1}}{R_{c1} h_{ie} + j 2\pi f_C R_{c1} h_{ie}} \\ &\stackrel{*}{=} \frac{-h_{fe} \cdot R_{c1}}{R_{c1} h_{ie}} \\ &= \frac{1}{1 + j \frac{2\pi f_C R_{c1} h_{ie}}{R_{c1} h_{ie}}} \end{aligned}$$

$$A_h = \frac{A_m}{1 + j \left( \frac{f}{f_h} \right)}$$



$$\therefore f_h = \frac{R_{c1} h_{ie}}{2\pi C_o R_{c1} h_{ie}} = \frac{1}{2\pi C_o \left( \frac{R_{c1} h_{ie}}{R_{c1} + h_{ie}} \right)}$$

$$f_h = \frac{1}{2\pi C_o (R_{c1} || h_{ie})}$$

$$\therefore |A_h| = \frac{|A_m|}{\sqrt{1 + \left( \frac{f}{f_h} \right)^2}}$$

$$\text{At } f = f_h, |A_h| = \frac{A_m}{\sqrt{2}}$$

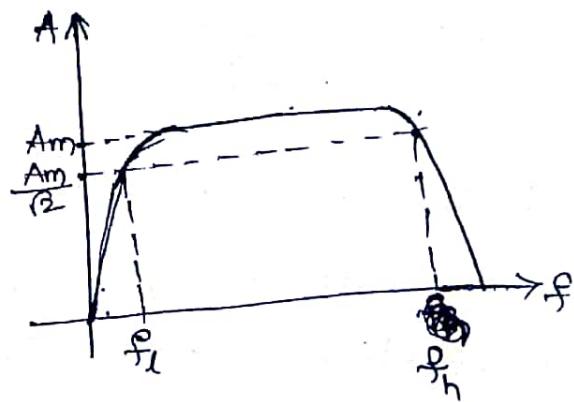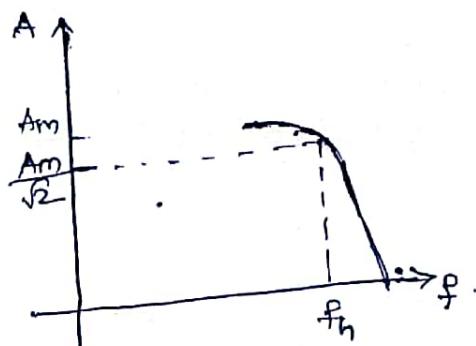$\therefore f_h$  is upper cut off frequency.



1. Derive the relationship between mid frequency gain and low frequency gain for an RC-coupled Amplifier.

1. Derive  $A_m$  and  $A_L$ .

2. Derive the relationship between mid frequency gain and high frequency gain for an RC-coupled Amplifier.

1. Derive  $A_m$  &  $A_h$ .

3. Impact of coupling capacitor on gain

1. Derive  $A_L$ .

Effect of cascading on gain and band width :-

Effect on gain :-

Cascading increases gain, the overall gain of a cascaded amplifier is the product of individual gains.

Effect on Bandwidth :-

Cascading decreases the band width.

Effect of cascading on lower cut off frequency (or) lower cut off frequency of an n-stage cascaded Amplifier.

Let  $A_L, A_m, A_h$  be the low, mid, high frequency gains of an individual stage.

$$A_L = \frac{A_m}{\sqrt{1 + (\frac{f_L}{f_h})^2}}$$

$$A_h = \frac{A_m}{\sqrt{1 + (\frac{f_h}{f_L})^2}}$$

$f_L, f_h$  are lower and upper cut off frequencies of individual stage amplifier.

n-similar stages are cascaded

Let  $A_L, A_M, A_H$  are the low, mid, high frequency gains of n-stage amplifier.

Let  $f_L, f_H$  are the lower & upper cut off frequencies of n-stage amplifier.

$$A_L = \frac{A_M}{\sqrt{1 + \left(\frac{f_L}{f}\right)^2}}$$

$$A_H = \frac{A_M}{\sqrt{1 + \left(\frac{f}{f_H}\right)^2}}$$

$$A_L = (A_M)^n, \quad A_M = (A_m)^n, \quad A_H = (A_h)^n$$

$$A_L = (A_L)^n$$

$$\frac{A_M}{\sqrt{1 + \left(\frac{f_L}{f}\right)^2}} = \left[ \frac{A_m}{\sqrt{1 + \left(\frac{f_L}{f}\right)^2}} \right]^n$$

$$\frac{A_M}{\sqrt{1 + \left(\frac{f_L}{f}\right)^2}} = \frac{A_m^n}{\sqrt{1 + \left(\frac{f_L}{f}\right)^2}}$$

$$\frac{A_M}{\sqrt{1 + \left(\frac{f_L}{f}\right)^2}} = \frac{A_m^n}{\left(\sqrt{1 + \left(\frac{f_L}{f}\right)^2}\right)^n}$$

$$\sqrt{1 + \left(\frac{f_L}{f}\right)^2} = \left[ \sqrt{1 + \left(\frac{f_L}{f}\right)^2} \right]^n$$

$$1 + \left(\frac{f_L}{f}\right)^2 = \left[ 1 + \left(\frac{f_L}{f}\right)^2 \right]^n$$

Put  $f = f_L$  in above equation

$$2 = \left[ 1 + \left(\frac{f_L}{f}\right)^2 \right]^n$$

$$2^{1/n} = 1 + \left(\frac{f_L}{f}\right)^2$$

$$\left(\frac{f_L}{f_H}\right)^2 = 2^n - 1$$

$$f_L = \frac{f_H}{\sqrt{2^n - 1}}$$

$f_L$  is always more than  $f_H$

Effect of cascading on upper cut off frequency ( $f_U$ ) upper cut off frequency of n-stage cascaded Amplifier :-

$$A_H = (A_h)^n$$

$$\frac{A_M}{\sqrt{1 + \left(\frac{f}{f_H}\right)^2}} = \left[ \frac{A_m}{\sqrt{1 + \left(\frac{f}{f_H}\right)^2}} \right]^n$$

$$\frac{A_M}{\sqrt{1 + \left(\frac{f}{f_H}\right)^2}} = \frac{A_m^n}{\left( \sqrt{1 + \left(\frac{f}{f_H}\right)^2} \right)^n}$$

$$\frac{A_M}{\sqrt{1 + \left(\frac{f}{f_H}\right)^2}} = \frac{A_m}{\left( \sqrt{1 + \left(\frac{f}{f_H}\right)^2} \right)^n}$$

$$\sqrt{1 + \left(\frac{f}{f_H}\right)^2} = \left[ \sqrt{1 + \left(\frac{f}{f_H}\right)^2} \right]^n$$

$$1 + \left(\frac{f}{f_H}\right)^2 = \left[ 1 + \left(\frac{f}{f_H}\right)^2 \right]^n$$

Put  $f = f_H$  in the above equation

$$2 = \left[ 1 + \left(\frac{f_H}{f_H}\right)^2 \right]^n$$

$$2^n = 1 + \left(\frac{f_H}{f_H}\right)^n$$

$$\left(\frac{f_H}{f_H}\right)^n = 2^n - 1$$



$$f_H = \omega_h$$



$$\frac{f_H}{f_L} = \sqrt{2^n - 1}$$

$$f_H = f_L (\sqrt{2^n - 1})$$

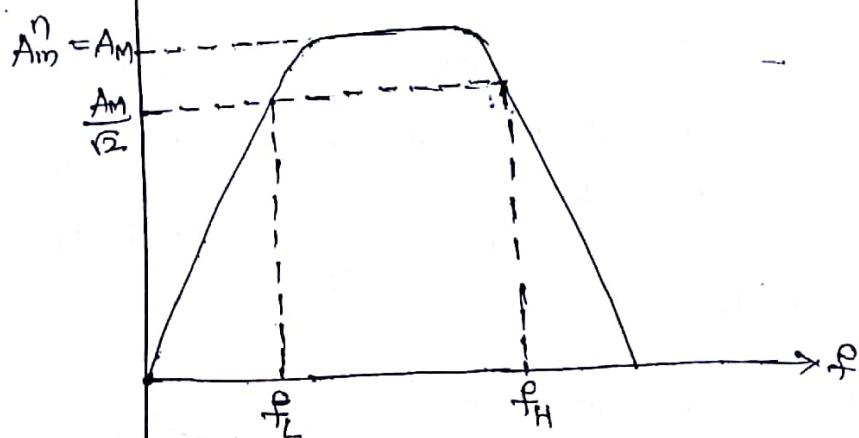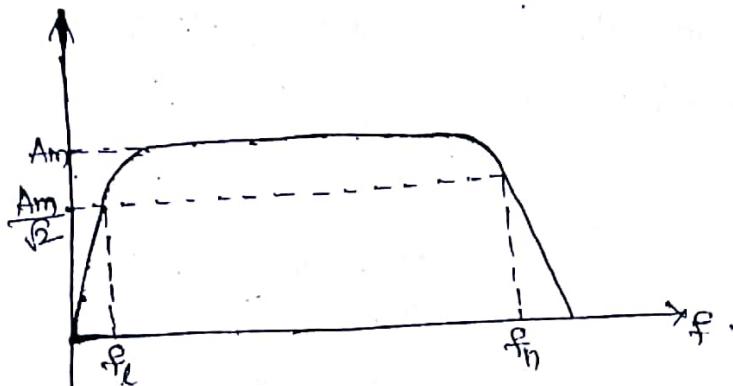$\therefore f_H < f_L$ . ( $f_H$  is always less than  $f_L$ )



From the diagram we can observe that cascading decrease the band width.

~~Bandwidth of individual stage is~~

$$BW = f_H - f_L, \text{ normally } f_L \ll f_H$$

$$BW = f_H :$$

Bandwidth of n-stage amplifier

$$(BW)_n = f_H - f_L, \text{ normally } f_L \ll f_H$$

$$(BW)_n \approx f_H$$

$$(BW)_n = f_H \approx f_h (\sqrt{2^n} - 1)$$

$$(BW)_n = (BW) (\sqrt{2^n} - 1).$$

12/18  
Today:



identically  
the bandwidth of a 3-stage cascaded amplifier extends  
from 20 Hz to 20 kHz determine bandwidth of individual  
stages and also determine the lower and upper cut off  
frequencies of individual stages.

- Given

$$n = 3$$

$$f_L = 20 \text{ Hz}$$

$$f_H = 20 \text{ kHz}$$

$$f_L = \frac{f_L}{\sqrt{2^n} - 1}$$

$$\Rightarrow f_L = f_L (\sqrt{2^n} - 1)$$

$$= 20 (\sqrt{2^3} - 1)$$

$$= 10.196 \text{ Hz} \approx 10.2 \text{ Hz}$$

$$f_H = f_h (\sqrt{2^n} - 1)$$

$$f_h = \frac{f_H}{\sqrt{2^n} - 1} = \frac{20 \times 10^3}{\sqrt{2^3} - 1} = 39.2 \text{ kHz}$$

$$\text{Band width of individual stage} = f_h - f_L$$

$$= 39.2 \text{ kHz} - 10.2 \text{ Hz}$$

$$= 39.18 \text{ kHz}$$



Q. Band width of single stage Amplifier is 50 kHz, if such stages are cascaded, determine the band width of cascaded Amplifier.

A: Given

$$BW = 50 \text{ kHz}$$

$$n = 4$$

$$(BW)_n = ?$$

We know that

$$(BW)_n \cong (BW) \sqrt{2^{n-1}}$$

$$= 50 \times 10^3 \sqrt{2^{14-1}}$$

$$= 21.74 \text{ kHz}$$

∴

3. An amplifier has a gain of 20db. and lower and upper cut off frequencies of 500Hz, 50K. How many amplifiers are needed in cascade to achieve a gain of 60db. What are the lower and upper cut off frequencies of cascaded amplifier.

A: Let  $A_1 \text{ db}$  be the gain of single stage.

Let  $A \text{ db}$  be the gain of cascaded stages.

The number of stages is given by.

$$n = \frac{A \text{ db}}{A_1 \text{ db}}$$

In the given problem, no of required stage is

$$n = \frac{60 \text{ db}}{20 \text{ db}} = 3$$

$$f_L = 500 \text{ Hz}$$


$$f_L = \frac{f_L}{\sqrt{2^{n-1}}} = \frac{500}{\sqrt{2^{13-1}}} \Rightarrow f_L = 980.72 \text{ Hz}$$

$$f_H = 50 \text{ kHz}$$

$$f_H = f_H (\sqrt{2^{n-1}})$$
$$= 50 \times 10^3 (\sqrt{2^{13-1}})$$


$$\int \rho = 95.19 \text{ kHz}$$

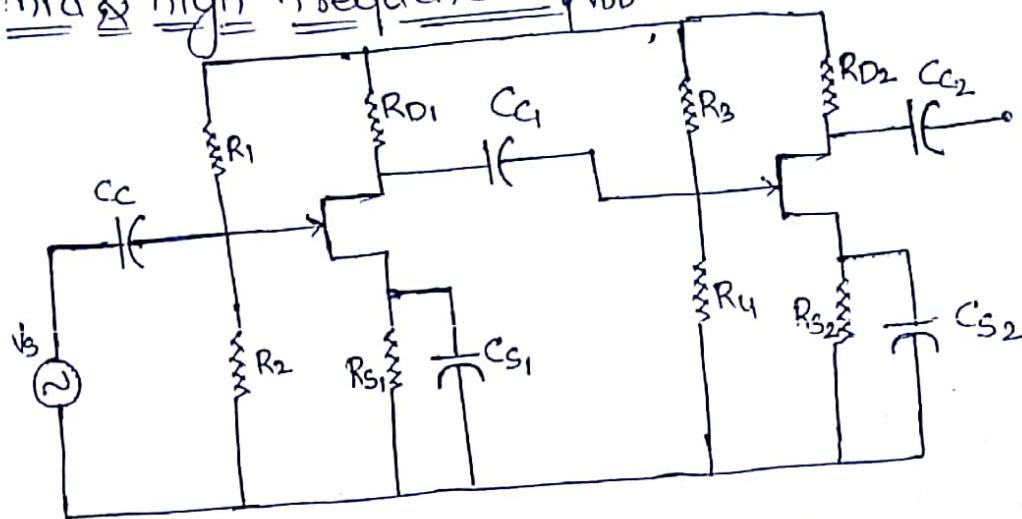Analysis of an RC-coupled FET Amplifier at  $\omega_0$ , mid & high frequencies!




Analysis in the mid-frequency range :-

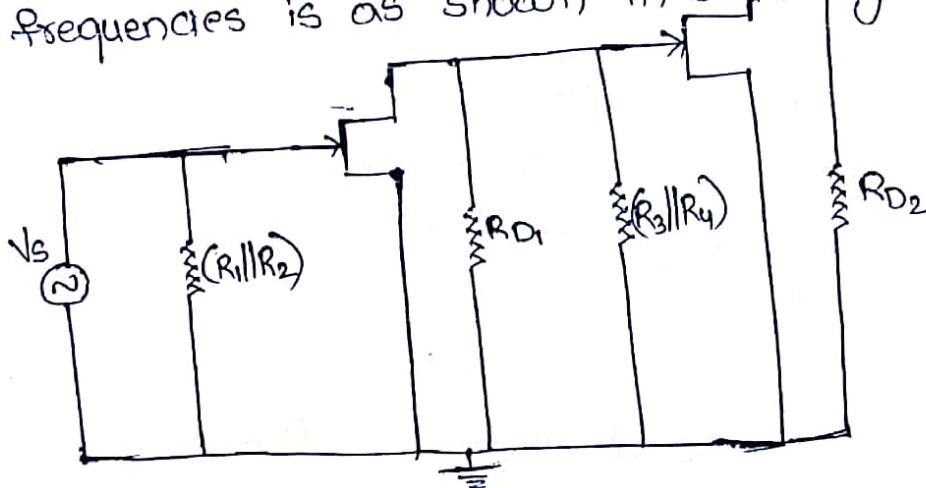
At mid frequencies coupling and bypass capacitors will be replaced with short circuit. The AC circuit at mid frequencies is as shown in below figure




FET small signal equivalent circuit is.

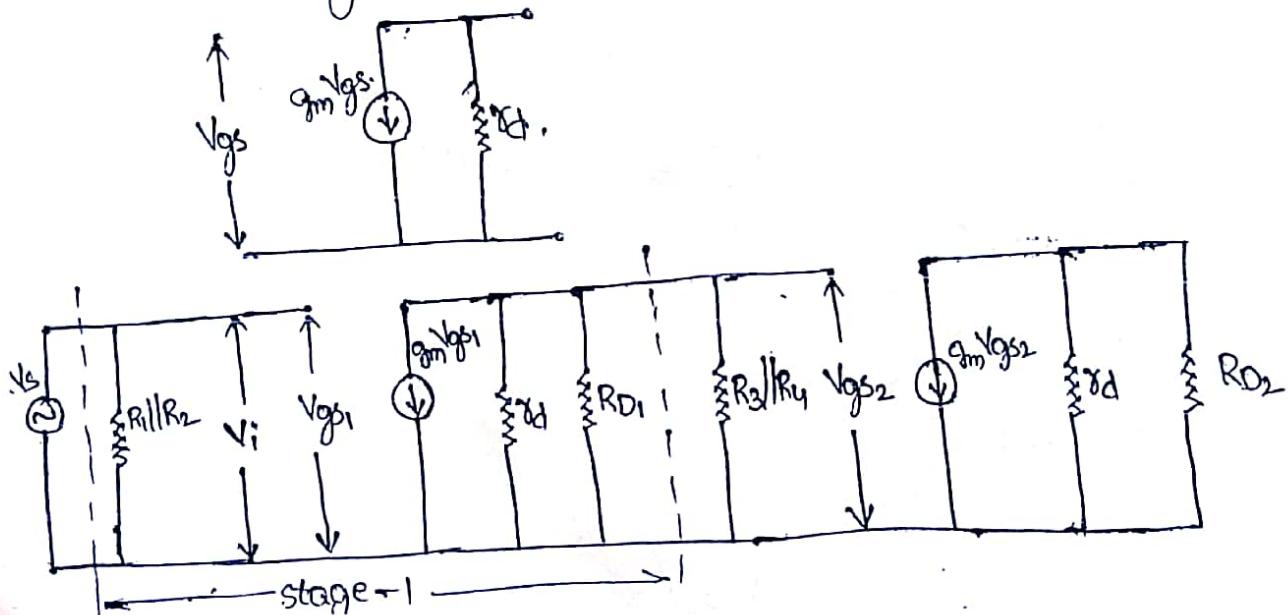

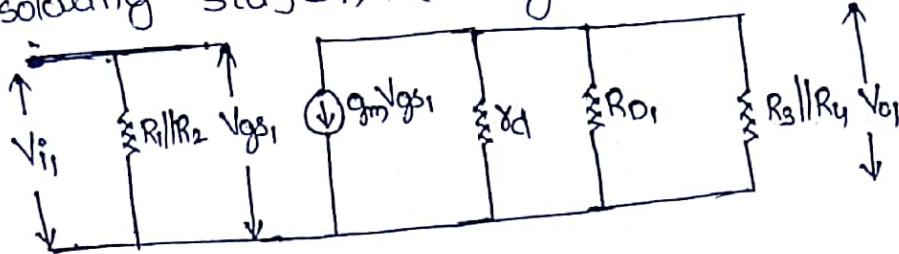Isolating stage, including load to calculate the gain.



15/2/18  
Saturday.

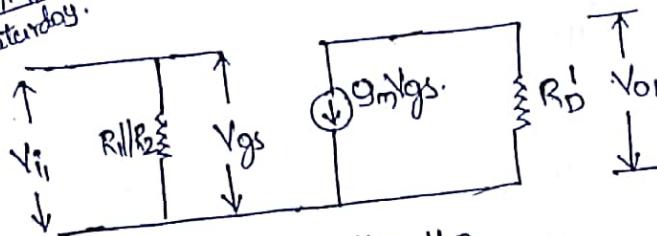

$$R_D' = \gamma_d \parallel R_D \parallel R_3 \parallel R_4$$

$$V_{ii} = V_{gs}$$

$$V_{o1} = -g_m V_{gs} R_D'$$


$$A_m = \frac{V_{o1}}{V_{ii}} = -\frac{g_m V_{gs} R_D'}{V_{gs}}$$

$$\boxed{A_m = -g_m R_D'}$$


Analysis in low frequency Range :-

At low frequencies coupling capacitor will dominate the frequency response.

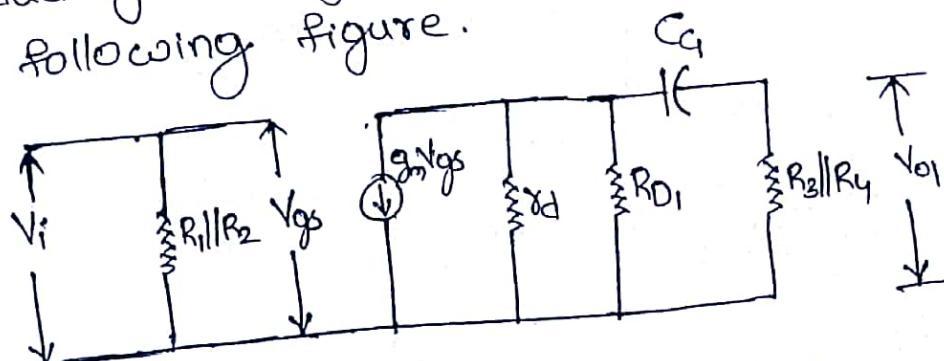The equivalent circuit of a single stage FET Amplifier including loading from the next stage is shown in following figure.



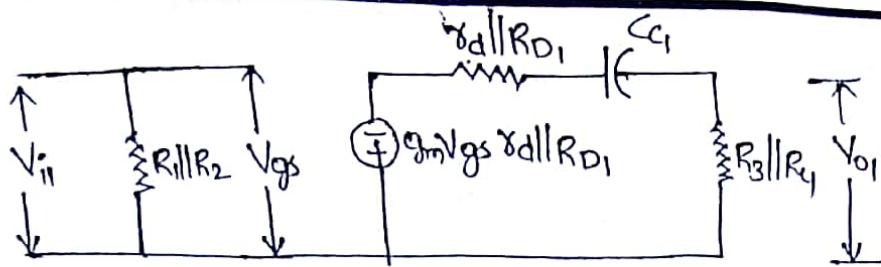By using source transformation technique the circuit is:



$$V_{o1} = \frac{-g_m V_{gs} (\gamma_d || R_{D1}) \times R_3 || R_4}{\gamma_d || R_{D1} + \frac{1}{j 2\pi f C_{C1}} + R_3 || R_4}$$

$$V_{o1} = \frac{-g_m V_{gs} (\gamma_d || R_{D1}) \times (R_3 || R_4)}{1 (\gamma_d || R_{D1}) + (R_3 || R_4)}$$

$$\times \frac{1}{1 + \frac{1}{j 2\pi f C_{C1} (\gamma_d || R_{D1} + R_3 || R_4)}}$$

$$V_{o1} = \frac{-g_m V_{gs} R_D'}{1 - j \left( \frac{f_L}{f} \right)}$$

where  $R_D' = \frac{(\gamma_d || R_{D1}) \times (R_3 || R_4)}{(\gamma_d || R_{D1}) + (R_3 || R_4)}$

$$\therefore f_L = \frac{1}{2\pi C_{C1} (R_3 || R_4 + \gamma_d || R_{D1})}$$

$$V_{i1} = V_{gs}$$

$$A_L = \frac{V_{o1}}{V_{i1}} = \frac{-g_m V_{gs} R_D'}{1 - j \left( \frac{f_L}{f} \right)} = \frac{-g_m R_D'}{1 - j \left( \frac{f_L}{f} \right)}$$


$$A_L = \frac{A_m}{1 - j \left( \frac{f_L}{f} \right)}$$

at  $f = f_L$


$$A_L = \frac{A_m}{j \frac{f_L}{f}}$$

$f_L \rightarrow$  lower cut off frequency.

\* Analysis in the high frequency Range:

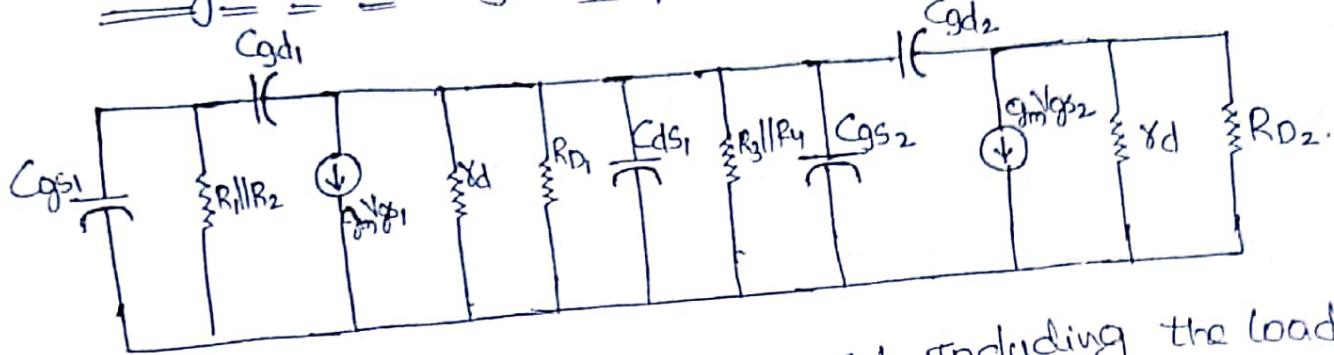

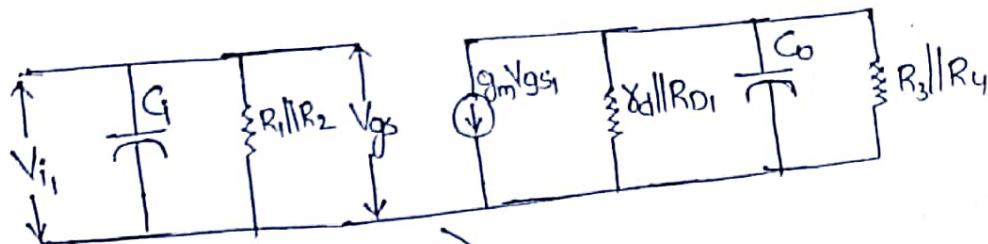Using Miller's theorem, the stage-1 including the load can be isolated as follows.



$$C_i = C_{gs} + C_{gd}(1 - k_1)$$

$$C_o = C_{gd}(1 - \frac{1}{k_1}) + C_{ds_1} + C_{gs_2} + C_{gd_2}(1 - k_2)$$

Apply KCL at output node.

$$g_m V_{gs_1} + \frac{V_{o1}}{\gamma_d || R_{D1}} + \frac{V_{o1}}{\frac{1}{j 2\pi f C_o}} + \frac{V_{o1}}{(R_3 || R_4)} = 0$$

$$V_{o1} \left[ \frac{1}{\gamma_d || R_{D1}} + \frac{1}{R_3 || R_4} + j 2\pi f C_o \right] = -g_m V_{gs_1}$$

$$V_{o1} \left[ \frac{1}{R_{D1}} + j 2\pi f C_o \right] = -g_m V_{gs_1}$$

$$V_{o1} \left[ \frac{1}{R_{D1}} + j 2\pi f C_o \right] = -g_m V_{i_1}$$

$$\frac{1}{\gamma_d || R_{D1}} + \frac{1}{R_3 || R_4} = \frac{1}{R_{D1}}$$

$$V_{gs_1} = V_{i_1}$$

$$\frac{V_{o1}}{V_{i_1}} = \frac{-g_m R_{D1}}{1 + j 2\pi f C_o R_{D1}}$$

$$\therefore A_h = \frac{A_m}{1 + j \left( \frac{f_h}{f} \right)}$$


$$f_h = \frac{1}{2\pi C_o R_{D1}}$$

Today.


## High Input Impedance Circuits:

High input impedance circuits are needed to provide impedance matching.


e.g. CE Amplifier, CD Amplifier.

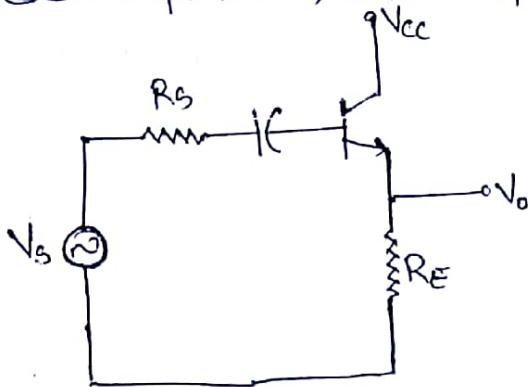

CC amplifier.

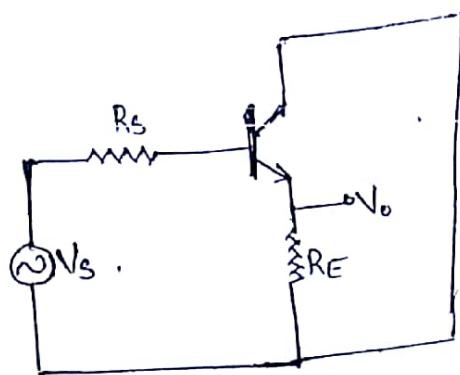


ac circuit.

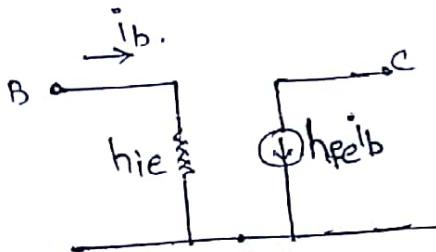

Approximate h-parameter model.

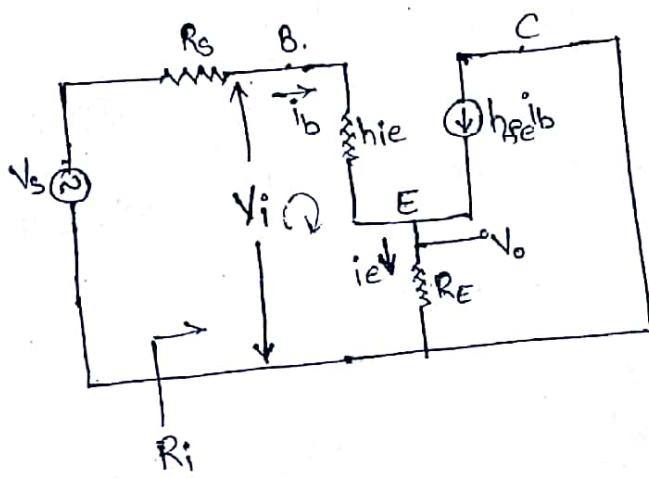Replace BJT with approximate h-parameter model.



$$\text{Current Gain: } A_I = \frac{i_e}{i_b}$$

Applying KCL at emitter node.

$$i_b + h_{fe}i_b = i_e$$

$$(1+h_{fe})i_b = i_e$$

$$\therefore A_I = \frac{i_e}{i_b} = (1+h_{fe})$$

Input Impedance:

$$R_i = \frac{V_i}{i_b}$$

Applying KVL to input loop:

$$-V_i + i_b h_{ie} + i_e R_E = 0$$

$$V_i = i_b h_{ie} + (1+h_{fe}) i_b R_E$$

$$V_i = (h_{ie} + (1+h_{fe}) R_E) i_b$$

$$\therefore R_i = \frac{V_i}{i_b} = h_{ie} + (1+h_{fe}) R_E$$

Voltage gain:-

$$A_V = \frac{V_o}{V_i}$$

$$= \frac{i_e R_E}{i_b R_i} = \frac{A_I R_E}{R_i}$$


$$(A_I = \frac{i_e}{i_b} = (1+h_{fe}))$$

$$(R_i = h_{ie} + (1+h_{fe}) R_E)$$

$$A_V = \frac{(1+h_{fe}) R_E}{h_{ie} + (1+h_{fe}) R_E}$$

Output Impedance:-

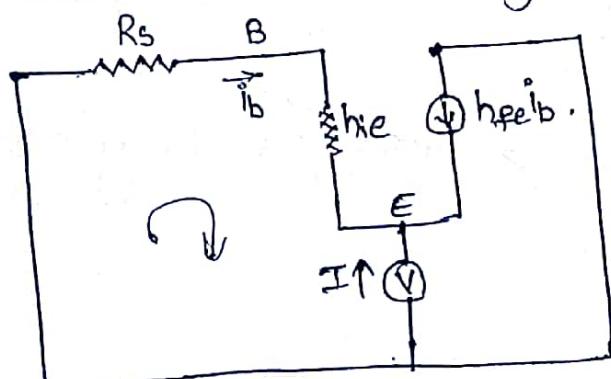To find output impedance Replace  $V_s$  with short circuit & disconnect  $R_E$  and connect voltage source  $V$ . Find  $\frac{V}{I}$  as shown in the following figure.



By applying KCL at output emitter node.

$$i_b + h_{fe}i_b + I = 0$$

$$I = -(1+h_{fe})i_b$$

Applying KCL at input

$$R_s i_b + h_{ie} i_b + V = 0$$

$$V = -(R_s + h_{ie}) i_b$$

$$R_o = \frac{V}{I} = \frac{-(R_s + h_{ie}) i_b}{-(1+h_{fe}) i_b} \Rightarrow R_o = \frac{R_s + h_{ie}}{1+h_{fe}}$$

Summary:

$$A_I = (1+h_{fe}) \rightarrow \text{large}$$

$$R_i = h_{ie} + (1+h_{fe}) R_E \rightarrow \text{large}$$

$$A_V = \frac{(1+h_{fe}) R_E}{h_{ie} + (1+h_{fe}) R_E}$$

$$h_{ie} < (1+h_{fe}) R_E$$

$$A_V \approx \frac{(1+h_{fe}) R_E}{(1+h_{fe}) R_E} \approx 1 \rightarrow \text{voltage gain low. approx}$$

$$R_o = \frac{R_s + h_{ie}}{1+h_{fe}} \rightarrow \text{low}$$


∴ CC Amplifier has high input impedance and low output impedance with unity voltage gain and large current gain.

∴ It can be used as impedance matching circuit.



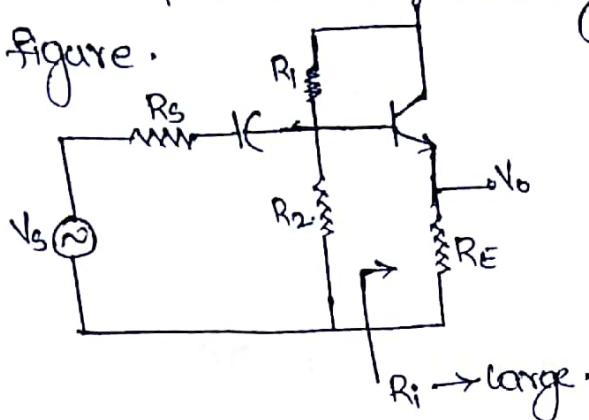
## Limitation of input impedance of CC Amplifier:

CC Amplifier with biasing resistors is shown in the following figure.



The ac circuit is shown in below figure.

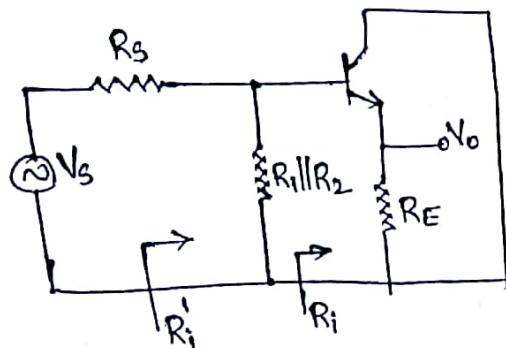

The input impedance  $R_i$  is.

$$R_i = h_{ie} + (1+h_{fe})R_E$$

The net input impedance  $R'_i$  is

$$R'_i = R_1 || R_2 || R_i$$

But  $R_1 || R_2 \gg R_i$

$\therefore R'_i \approx R_1 || R_2$  which is small.


$\therefore$  Even though CC Amplifier has large input impedance.

The net input impedance  $R'_i$  is very small because of the effect of biasing resistors.


The above problem is overcome by using a boot strapped CC Amplifier.

31/12/18 Monday

## Boot strapped CC Amplifier:-

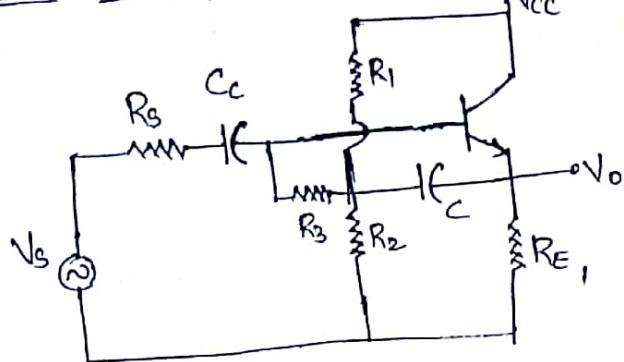

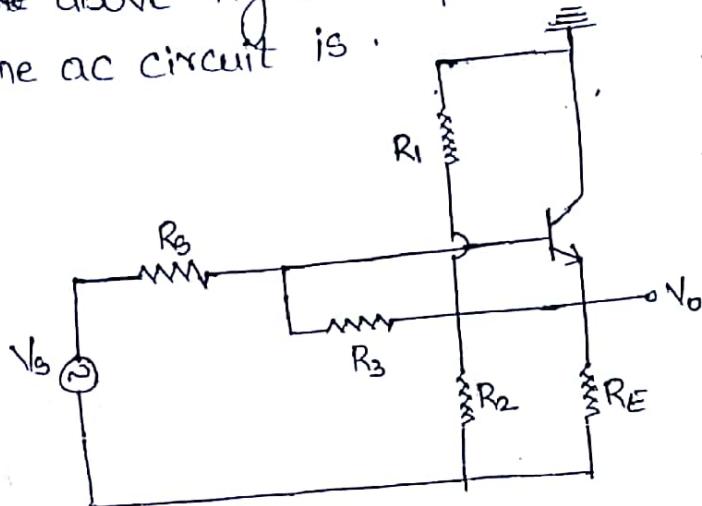
In the above figure capacitor  $C_c$  short circuits for AC signals.  
The AC circuit is:



The resistance  $R_3$  can be split using Miller's theorem.  
Then the equivalent value of  $R_3$  between base and ground

$$\text{is } \frac{R_3}{1-AV}$$

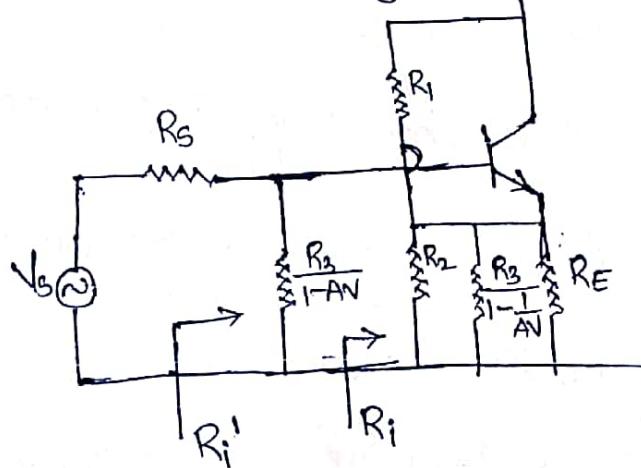where  $AV$  is voltage gain between base and emitter.



$$\therefore R_i' = \frac{R_3}{1-AV} \parallel R_i$$

$A_V$  for a CC amplifier is approximately equal to 1.

$$\therefore R'_i \approx \infty // R_i \approx R_i$$

$$\boxed{\therefore R'_i \approx R_i}$$

Parameters.	CC amplifier. approximate h-model	CC Amplifier exact approximate h-model.
$A_I$	$(1+h_{fe})$	$\frac{-h_{fc}}{1+h_{oc}R_L} = \frac{(1+h_{fe})}{1+h_{oe}R_L}$
$R_i$	$h_{ie} + A_I R_L$	$h_{ic} + h_{ic} A_I R_L = h_{ie} + A_I R_L$
$A_V$	$\frac{A_I R_L}{R_i}$	$\frac{A_I R_L}{R_i}$
$y_o$	$\frac{1+h_{fe}}{R_s + h_{ie}}$	$h_{oc} - \frac{h_{fc} h_{oc}}{R_s + h_{ic}} = h_{oe} + \frac{(1+h_{fe})}{R_s + h_{ie}}$


### Conversion Formulas :

~~$$h_{fc} \approx h_{ic} = h_{ie}$$~~

$$h_{fe} = -(1+h_{fc})$$

$$h_{oe} = 1$$

$$h_{oc} = h_{oe}$$

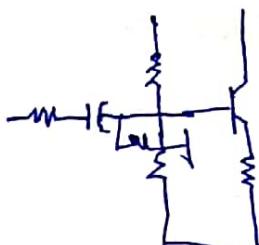


## Darlington pair :-

Darlington pair is a two stage cascaded CC Amplifier.

In applications where input impedance of single stage CC Amplifier is not sufficient, Darlington pair is used.

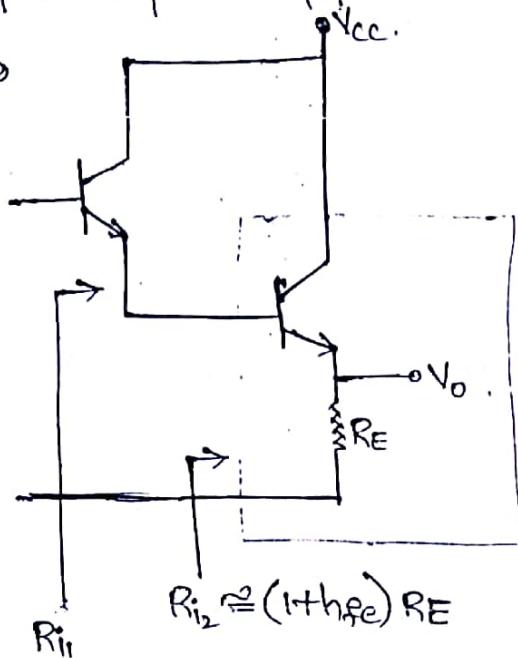Darlington pair input impedance is in the order of mega ohms



$$R_{i_2} \approx (1+h_{fe}) R_E$$

$$R_{i_1} \approx (1+h_{fe}) R_{i_2}$$

$$\approx (h_{fe})^2 R_E$$

## Analysis of second stage.

For second stage we can use approximate h-parameter model

Current gain  $AI_2 = (1+h_{fe}) \rightarrow \text{large}$ .

Input impedance  $R_{i_2} = h_{ie} + AI_2 R_E$ .

$$= h_{ie} + (1+h_{fe}) R_E$$

$$\approx (1+h_{fe}) R_E \quad \cancel{\rightarrow \text{large}}$$

Voltage gain  $AV_2 = \frac{AI_2 R_{L2}}{R_{i_2}} = \frac{AI_2 R_E}{R_{i_2}} = \frac{R_{i_2} - h_{ie}}{R_{i_2}}$

$$= \left(1 - \frac{h_{ie}}{R_{i_2}}\right) \approx 1$$

$$\text{Output Impedance} \cdot R_{O2} = \frac{R_s + h_{ie}}{1+h_{fe}} = \frac{R_{O1} + h_{ie}}{1+h_{fe}}$$

Analysis of first stage :-

For first stage analysis we must use exact model because  $B \cdot h_{oe} R_L < 0.1$  condition is not satisfied.

$$\text{Current gain, } A_{I_1} = \frac{(1+h_{fe})}{1+h_{oe} R_L} = \frac{1+h_{fe}}{1+h_{oe} R_{i2}}$$

$$A_{I_1} = \frac{(1+h_{fe})}{1+h_{oe}(1+h_{fe})R_E} \Rightarrow \text{large}$$

$$\text{Input impedance, } R_{i1} = h_{ie} + A_{I_1} R_L = h_{ie} + A_{I_1} R_{i2}$$

$$= h_{ie} + \frac{(1+h_{fe})}{1+h_{oe}(1+h_{fe})R_E} (1+h_{fe})R_E$$

$$\approx \frac{(1+h_{fe})^2 R_E}{1+h_{oe}(1+h_{fe})R_E} \Rightarrow \text{very large. Typical value in mega ohms}$$

$$\text{Voltage gain } A_{V_1} = \frac{A_{I_1} R_L}{R_{i1}}$$

$$= \frac{R_{i1} - h_{ie}}{R_{i1}} = \left(1 - \frac{h_{ie}}{R_{i1}}\right)$$

$$\approx 1$$

$$\text{Output Impedance, } Y_{O1} \approx h_{oe} + \frac{(1+h_{fe})}{(R_s + h_{ie})}$$

$$\text{Overall current gain, } AI = A_{I_1} \times A_{I_2} = \text{very large.}$$

$$\text{Overall voltage gain, } AV = A_{V_1} \times A_{V_2}$$

$$= (L_1) \times (L_1)$$

$$= L_1$$

Overall Input impedance  $R_i = R_{i1}$  = very large (megohms)

Overall output impedance  $R_o = R_{o2}$  = small


20/1/2019  
Wednesday



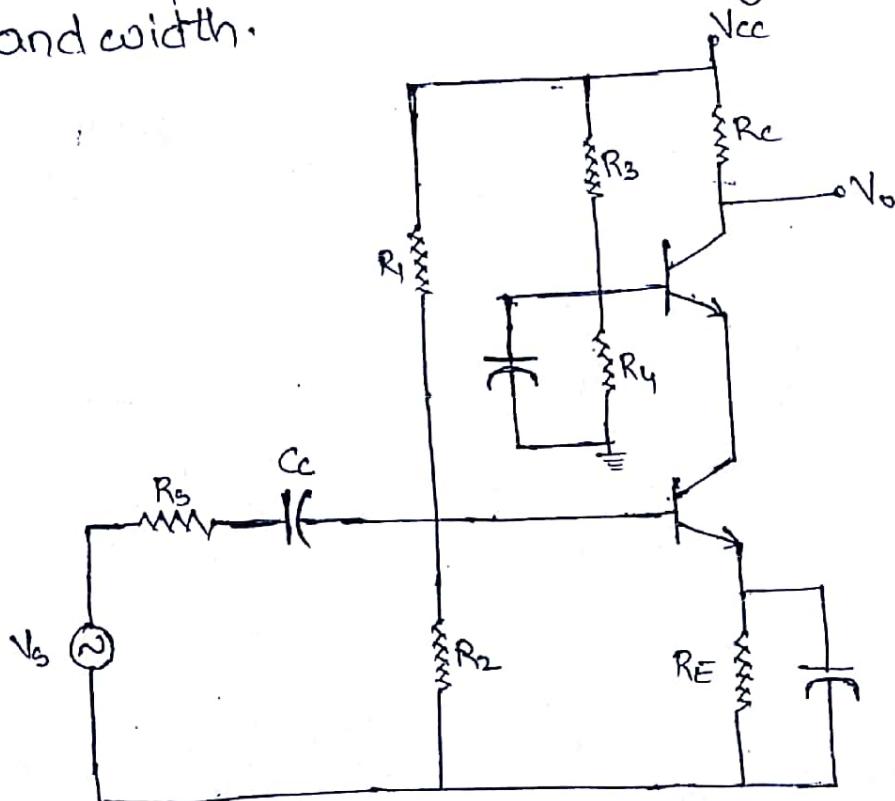
### Cascode Amplifier:-

The combination of CE, CB amplifier is called cascode Amplifier. It is a high gain Amplifier.

The bandwidth of cascode Amplifier is approximately same as the bandwidth of first stage CE Amplifier. Cascode Amplifier increases the gain without reducing the band width.



The AC circuit can be given as.

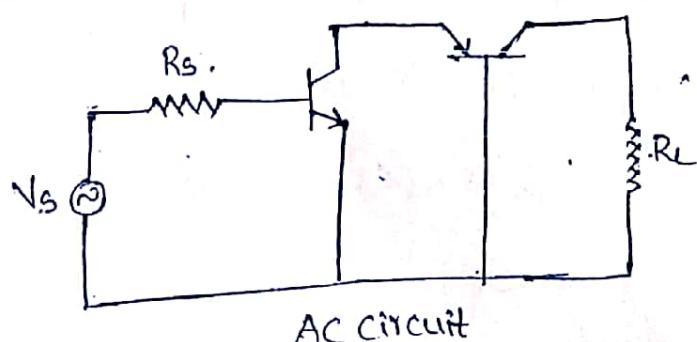

over all voltage gain of the system  $A_V = A_{V1} \times A_{V2}$

$A_{V1} \rightarrow CE$  voltage gain (large)

$A_{V2} \rightarrow CB$  voltage gain (large)

$\therefore A_V = A_{V1} \times A_{V2} = \text{very large.}$

over all current gain  $A_I = A_{I1} \times A_{I2}$

$A_{I1} \rightarrow CE$  current gain (large)

$A_{I2} \rightarrow CB$  current gain ( $\approx 1$ )

$\therefore A_I = A_{I1} \times A_{I2} \approx A_{I1}$

Input impedance of the cascode Amplifier is the input impedance of  $CE$  Amplifier which is moderate.  
The output impedance of cascode Amplifier is the output impedance of  $CB$  stage which is very large.

The disadvantage of cascode amplifier is which has very large output impedance.

Bootstrapped Darlington pair:


Even though the input impedance of darlington pair is very high, the net input impedance will fall drastically due to the following facts.

i) Due to Biasing resistors  $R_1, R_2$  that appear in parallel

with  $R_i$

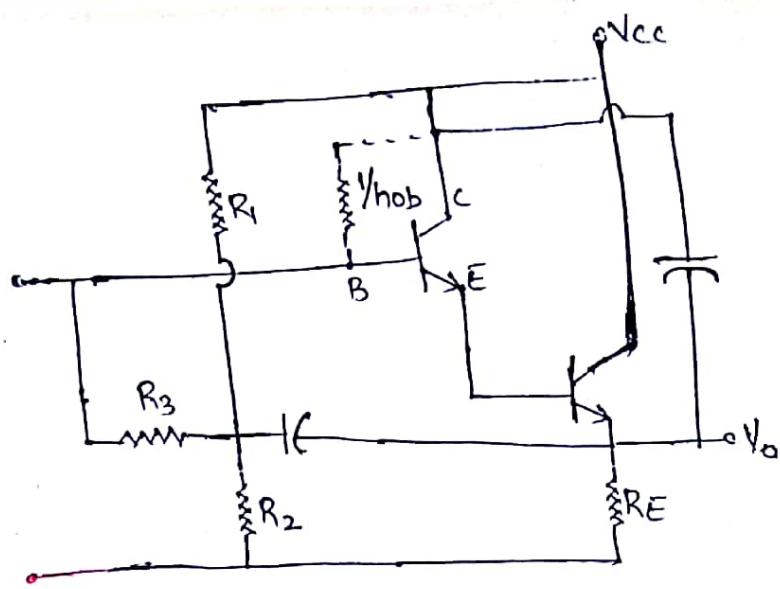
ii) The Miller equivalent of impedance  $Y_{hob}$  which is  $\frac{Y_{hob}}{1-k}$ . This impedance will appear in parallel with  $R_i$ .

Both these effects can be avoided by using bootstrapping technique as shown in the below figure.


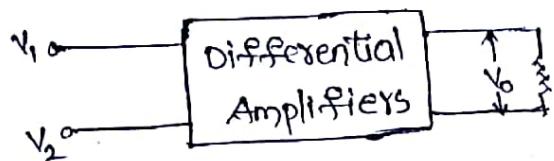
### Differential Amplifier:

Differential Amplifier is a dual input amplifier. The output of differential Amplifier is proportional to the difference of the two input signals.



$$V_o \propto (V_1 - V_2)$$

$$V_o = A_d (V_1 - V_2)$$

$$V_o = A_d V_d$$

$A_d$  = Differential gain.

Practical differential Amplifiers will amplify the not only the differential signal but also the common mode signal. The output voltage for a practical differential amplifier is:

$$V_o = A_d V_d + A_c V_c$$

$$V_d = V_1 - V_2 \text{ (difference signal)}$$

$$V_c = \frac{V_1 + V_2}{2} \text{ = common mode signal}$$

$A_d$  = Differential gain

$A_c$  = common mode gain

For ideal differential Amplifier  $A_d = 0$ .

For practical differential Amplifier  $A_d \gg A_c$ .




Common mode Rejection Ratio (CMRR) :-

It is the ratio of differential gain to common mode gain. It is represented by P.

$$CMRR = P = \left| \frac{A_d}{A_c} \right|$$

$$CMRR \text{ in dB} = P_{dB} = 20 \log \left| \frac{A_d}{A_c} \right|$$

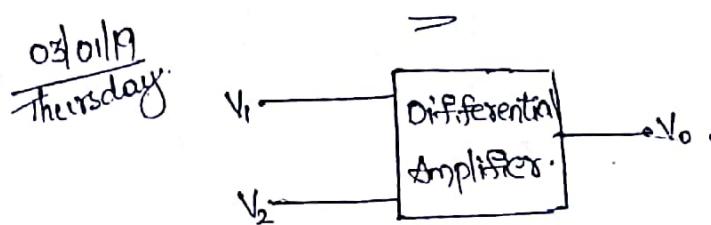

since differential Amplifier is linear, it obeys superposition.

$$V_0 = A_d V_1 + A_d V_2$$

$$\text{But } V_0 = A_d V_d + A_c V_c$$

$$V_0 = A_d (V_1 - V_2) + A_c \left( \frac{V_1 + V_2}{2} \right)$$

$$V_0 = V_1 \left( A_d + \frac{A_c}{2} \right) + V_2 \left( \frac{A_c}{2} - A_d \right)$$

$$V_0 = A_1 V_1 + A_2 V_2$$


$$\frac{A_c + A_d}{2} = A_1 \quad \rightarrow ①$$

$$\frac{A_c - A_d}{2} = A_2 \quad \rightarrow ②$$


$$\begin{aligned} ① + ② &\Rightarrow A_c = A_1 + A_2 \\ ① - ② &\Rightarrow 2A_d = A_1 - A_2 \\ &\quad A_d = \underline{\underline{A_1 - A_2}} \end{aligned}$$

Types of Differential Amplifier :-  
 Depending upon the number of inputs & outputs differential amplifiers can be divided in to four types.


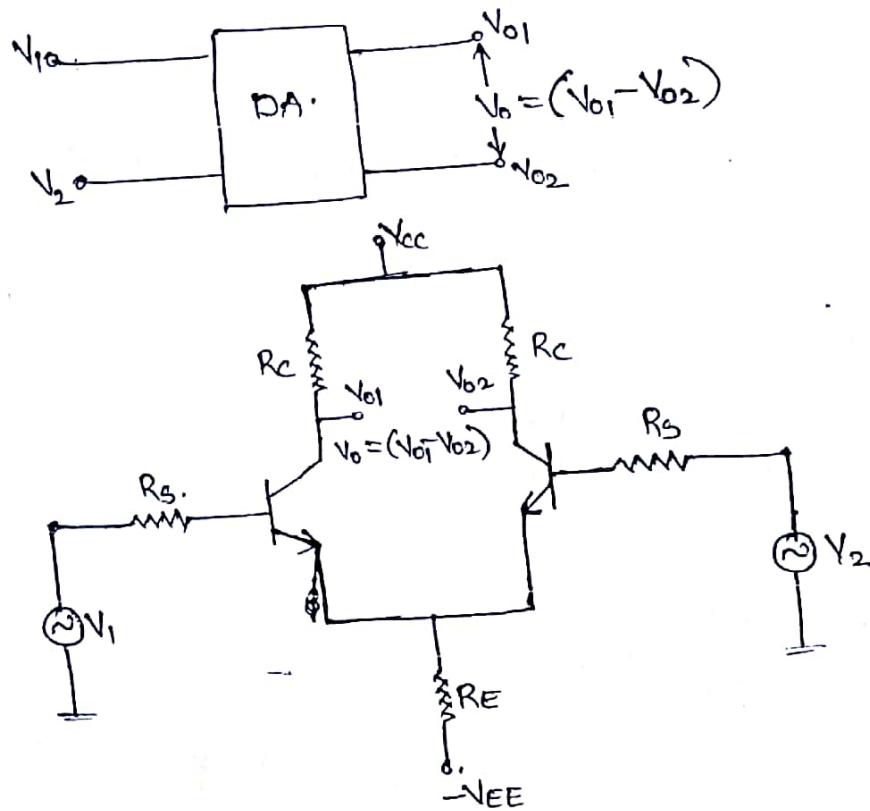
1. Dual Input balanced output differential Amplifier.




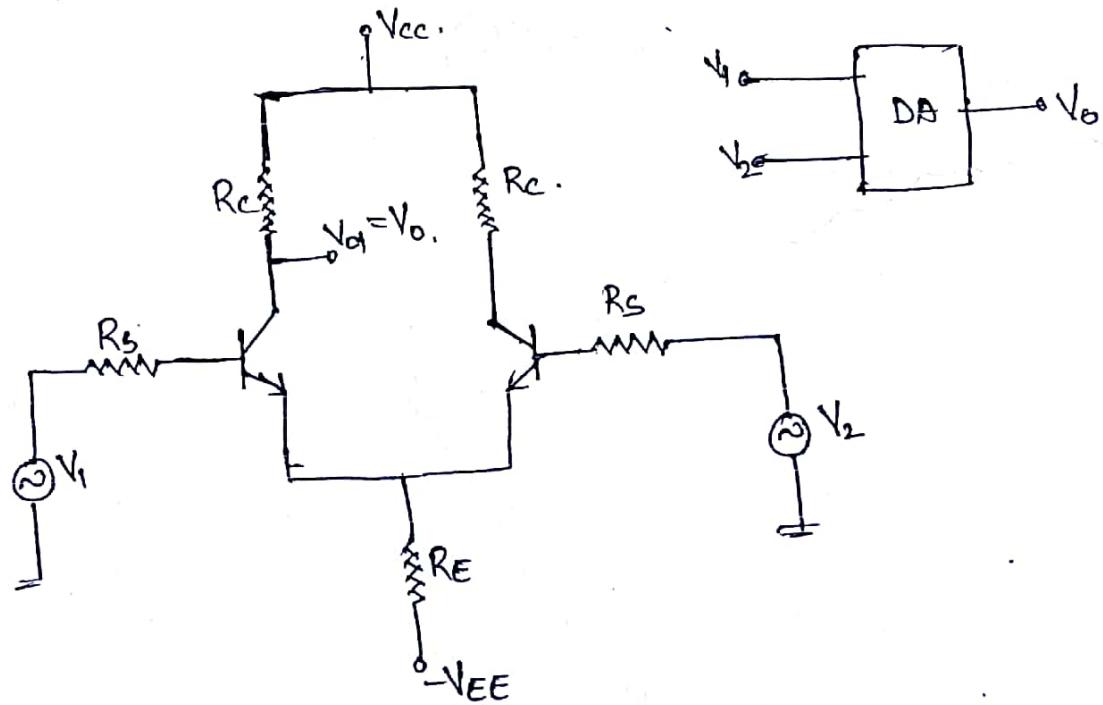
2. Dual input unbalanced output differential Amplifier.


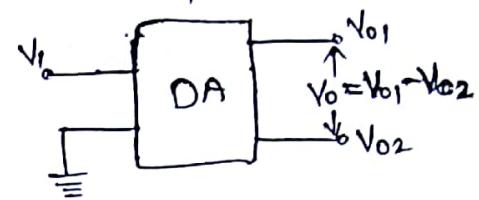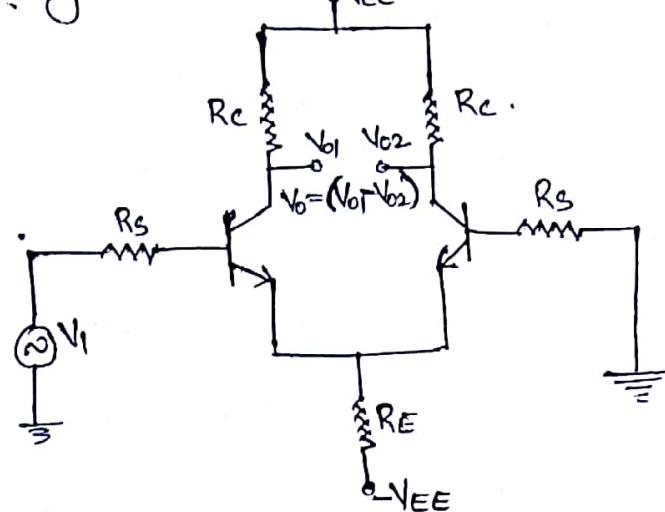
### 3) Single Input balanced output differential Amplifiers:-


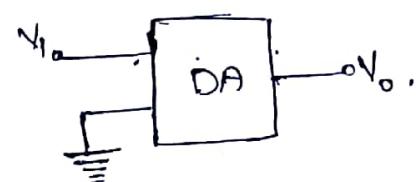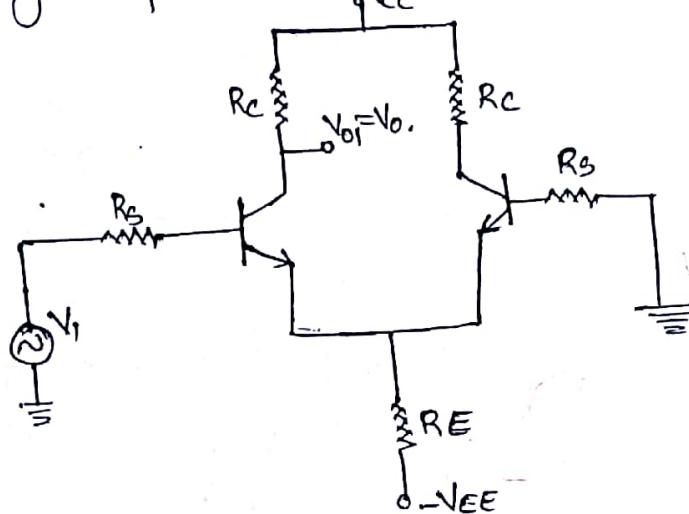
### 4) Single input unbalanced output differential Amplifier.



### Advantages of Differential Amplifier :-

1. Differential Amplifiers will have large differential gain and small common mode gain.
2. Differential Amplifiers suppresses the common mode signal.
3. Differential Amplifiers eliminates common noise present on the two input signal.
4. Power supply fluctuations ~~are suppressed~~. cause disturbance in the output and this can be eliminated using d.a.
5. Differential Amplifiers will have high input impedance.

Differential Amplifiers are direct coupled Amplifiers.  
∴ Low frequency response is very good.

04/01/19  
Friday:

### 3. Feed back Amplifiers.



#### Types of Amplifiers:-

Depending upon the type of input and output signals amplifiers can be divided in to 4 types. They are.

- 1) Voltage Amplifier
- 2) Current Amplifier.
- 3) Transconductance Amplifier.
- 4) Trans Resistance Amplifier.
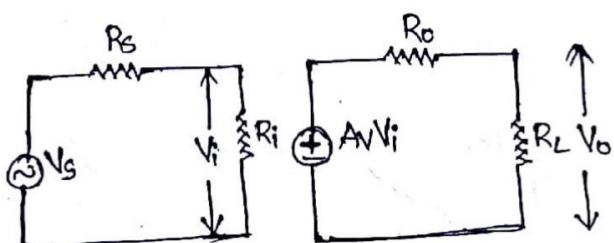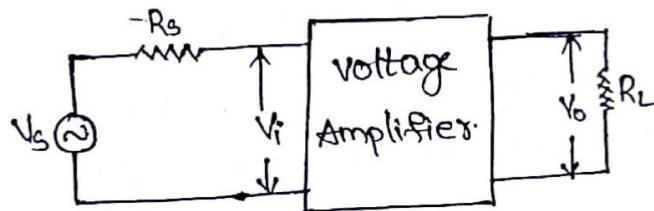
#### Voltage Amplifier :-

This type of amplifier takes voltage as an input signal and generate voltage as an output signal.



$R_i, R_o \rightarrow$  Input, output impedances.

$A_v \rightarrow$  open circuit voltage gain.

$$V_i = \frac{V_s R_i}{R_i + R_s} = \frac{V_s}{1 + \frac{R_s}{R_i}}$$

If  $R_i = \infty$

$$V_i = V_s.$$

∴ For ideal voltage amplifiers,  $R_i = \infty$

For practical voltage amplifiers  $R_i$  must be large.

i.e.,  $R_i \gg R_s$

$$V_o = \frac{A_v V_i R_L}{R_o + R_L} = \frac{A_v V_i}{1 + \frac{R_o}{R_L}}$$

If  $R_o = 0$ ;  $V_o = A_v V_i$

∴ For ideal voltage amplifiers  $R_o = 0$ .

For practical voltage amplifiers,  $R_o$  must be small.

$$V_o = \frac{A_v V_i R_L}{R_o + R_L}$$

$$\frac{V_o}{V_i} = A_v = \frac{A_v R_L}{R_o + R_L}$$

$$A_v = \frac{A_v}{1 + \frac{R_o}{R_L}}$$

If  $R_L = \infty$ ,

$$A_v = A_n$$


$A_v \rightarrow$  voltage gain.


$A_n \rightarrow$  open circuit voltage gain.


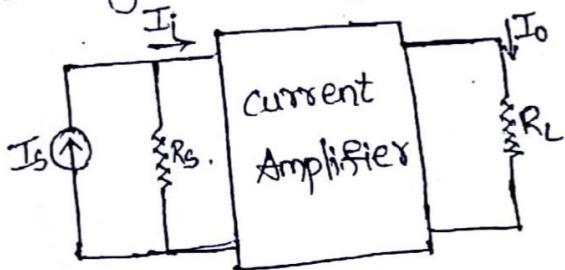
### Current Amplifier:

This type of amplifier takes current sources as an input signal and generates current as an output signal.



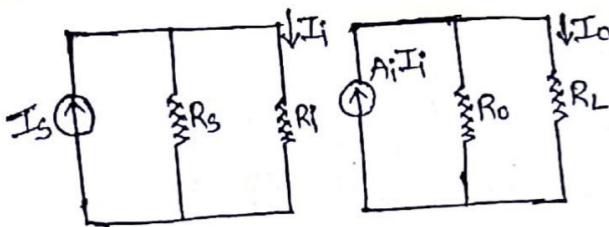

$R_i, R_o \rightarrow$  input, output impedance.  
 $A_i \rightarrow$  short circuit current gain

$$I_i = \frac{I_s R_s}{R_s + R_i} = \frac{I_s}{1 + \frac{R_i}{R_s}}$$

If  $R_i = 0$

$$\therefore I_i = I_s$$

For ideal current amplifiers  $R_i = 0$

For practical current amplifiers  $R_i$  must be very small.

$$I_o = \frac{A_i I_i R_o}{R_o + R_L} = \frac{A_i I_i}{1 + \frac{R_L}{R_o}}$$

If  $R_o = \infty$ ,

$$I_o = A_i I_i$$

For ideal current Amplifiers  $R_o = \infty$

For practical current Amplifiers,  $R_o$  must be <sup>very</sup> large.

$$I_o = \frac{A_i I_i R_o}{R_o + R_L}$$

$$AI = \frac{I_o}{I_i} = \frac{A_i R_o}{R_o + R_L}$$

$$AI = \frac{A_i}{1 + \frac{R_L}{R_o}}$$

If  $R_L = 0$ .


$$AI = A_i$$

$A_i \rightarrow$  current gain


$A_i \rightarrow$  short circuit current gain.
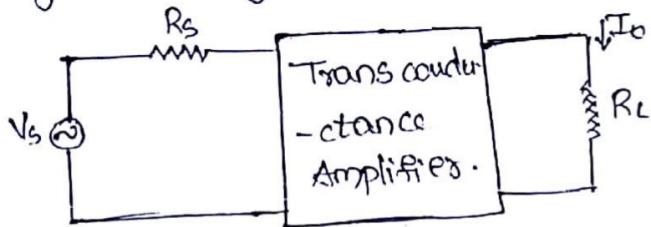
### 3) Transconductance Amplifiers:

This type of amplifier takes voltage as an input signal and generate current as an output signal.



equivalent circuit is.

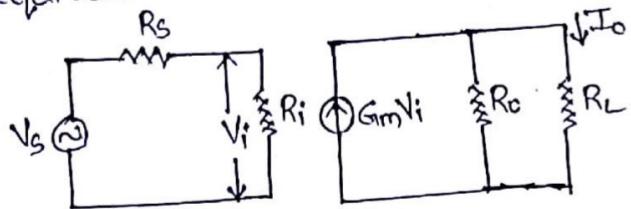

$$V_i = \frac{V_s R_i}{R_s + R_i} = \frac{V_s}{1 + \frac{R_s}{R_i}}$$

If  $R_i = \infty$ ,

$$V_i = V_s.$$

For ideal transconductance Amplifier  $R_i = \infty$

For practical transconductance Amplifier,  $R_i$  must be large

$$I_o = \frac{G_m V_i R_o}{R_o + R_L}$$

$$I_o = \frac{G_m V_i}{1 + \frac{R_L}{R_o}}$$

If  $R_o = \infty$ ,

$$I_o = G_m V_i$$

For ideal transconductance Amplifier  $R_o = \infty$

For practical transconductance Amplifier,  $R_o$  must be as large as possible.

$$I_o = \frac{G_m V_i R_o}{R_o + R_L}$$

$$\frac{I_o}{V_i} = G_M = \frac{G_m R_o}{R_o + R_L}$$

$$G_M = \frac{G_m}{1 + \frac{R_L}{R_o}}$$

If  $R_L = 0$ ,


$$G_M = G_m$$

$G_M \rightarrow$  Transconductance Gain.


$G_m \rightarrow$  Short circuit Transconductance Gain.
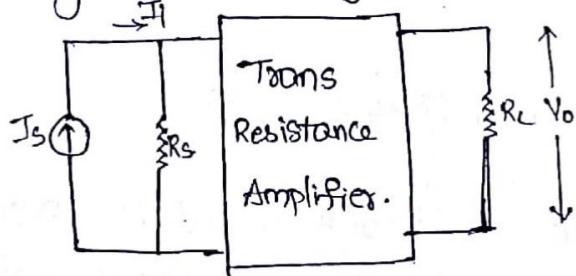
### A) Trans Resistance Amplifier :-

This type of amplifiers takes current as an input signal and generate voltage as an output signal.



Equivalent circuit, IS.

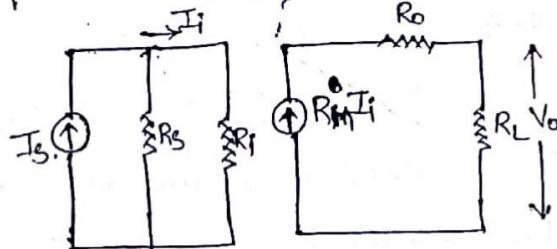

$$I_i = \frac{I_s R_s}{R_s + R_i} = \frac{I_s}{1 + \frac{R_i}{R_s}}$$

If  $R_i = 0$ ;  $I_i = I_s$ .

For ideal Amplifier  $R_i = 0$

For practical trans resistance Amplifier  $R_i$  must be small.

$$V_o = \frac{R_m I_i R_L}{R_m + R_L} = \frac{R_m I_i}{1 + \frac{R_L}{R_m}} \quad R_i \ll R_s$$

If  $R_o = 0$ ,  $V_o = R_m I_i$

For ideal transresistance Amplifier  $R_o = 0$ .

For practical transresistance Amplifier  $R_o$  should be low.

$$V_o = \frac{R_m I_i R_L}{R_o + R_L} \quad \cancel{\text{if } R_o \rightarrow 0}$$

$$R_m = \frac{V_o}{I_i} = \frac{R_m R_L}{R_o + R_L} = \frac{R_m}{\frac{R_o}{R_L} + 1}$$

If  $R_o = \infty$ ,  $\cancel{R_o + R_L}$

$$\boxed{R_o \rightarrow \infty} \\ R_M = R_m$$

$R_m$  → Trans resistance gain.  
 $R_m$  → open circuit Trans resistance gain

05/01/19  
saturday.

Definition of feed back:-


Feed back is a method (or) a process in which the output signal of an amplifier is sampled and feed back to the input.

Types of feed back:-

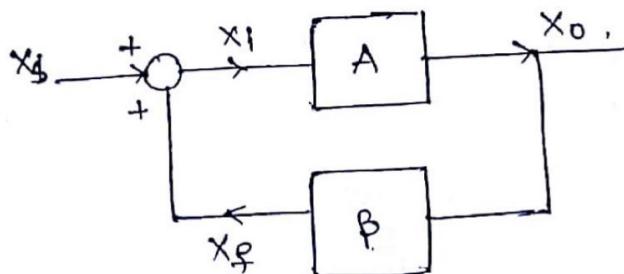1. Positive feed back
2. Negative feedback.

Positive Feed back:-

In this type of feed back, feedback signal is in phase with the input signal. This increases the net input and hence the output also increases.




$$\text{Here } x_i = x_s + x_f.$$



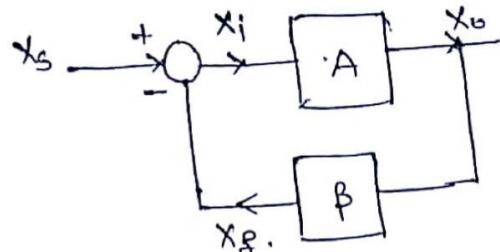
### Negative Feed back

In this type of feed back the feed back signal is out of phase with the input signal. This decreases the net input and hence the output also decreases.



$$\text{Here } x_i = x_s - x_f.$$
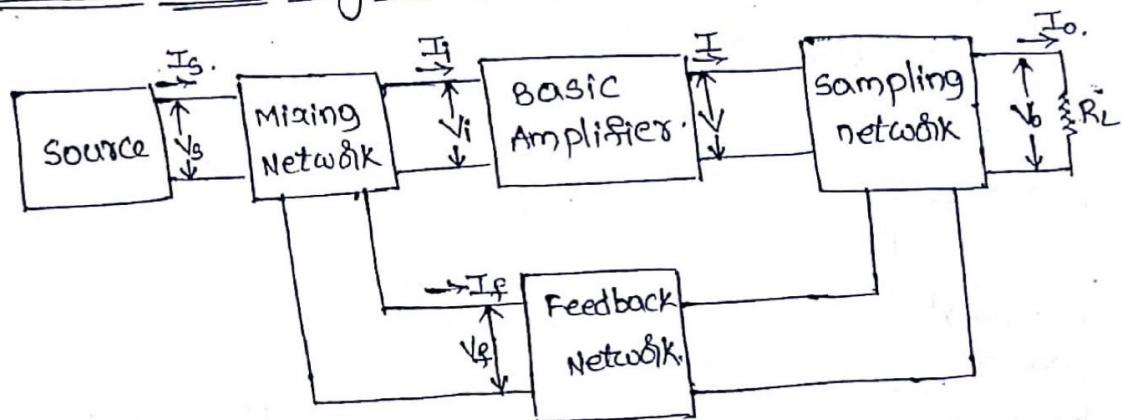
### General Block diagram of feedback circuit:




source: The signal source can be voltage source  $V_s$  & a current source  $I_s$ .

Basic Amplifier: This amplifier can be a voltage Amplifier with gain  $A_V$  & a current Amplifier with gain  $A_I$  or a transresistance amplifier with gain  $R_M$  or a transconductance amplifier with gain  $G_M$ .


Feedback Network: In general feed back network consists of passive elements like resistors and capacitors. In very rare applications the feed back network may also contain Active elements.
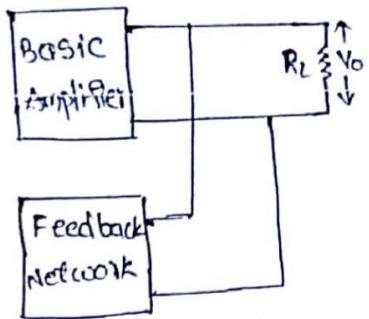
### Sampling Network:-

There are two types of sampling is possible with the output signal is voltage then it is sampled in parallel as shown in the following figure.



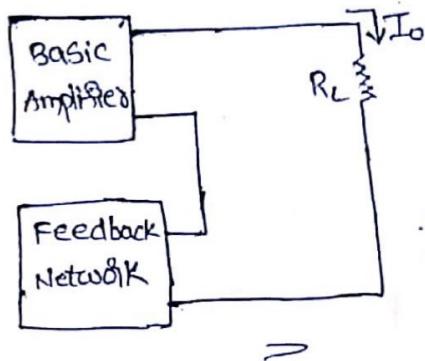If the output signal is current then the sampling is done in series as shown in figure.




↳   
 Redundant

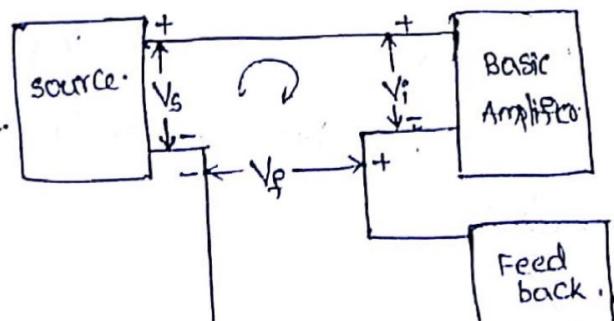
### Mixing Network or Summing Network:-

Depending upon the input and feedback signal two types of mixing is possible.


If the feedback signal is voltage signal it is added in series with the input ~~voltage~~ signal. This type of mixing is called series mixing.



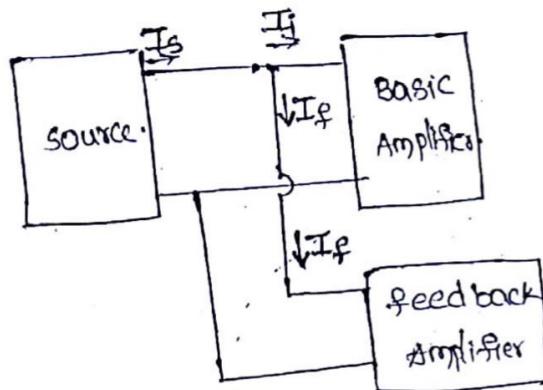If the feedback signal is current signal, then it is added in parallel with the input signal. This type of mixing is called ~~parallel~~ shunt mixing.



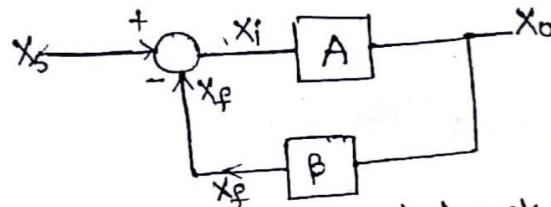Analysis of Negative Feedback Amplifier (8) Prove that negative feedback reduces the gain:



when there is no feed back

$$x_s = x_i$$

The gain without feed back.

$$A = \frac{x_o}{x_s} = \frac{x_o}{x_i}$$

$$x_o = Ax_i \rightarrow ①$$

when there is feed back

$$x_i = x_s - x_f$$

$$x_f = \beta x_o$$

$$\therefore x_i = x_s - \beta x_o \rightarrow ②$$

From ① & ②

$$x_i = x_s - \beta Ax_i$$

$$\therefore x_i = \frac{x_s}{1 + \beta A}$$

Now the gain with feedback is.

$$A_f = \frac{X_o}{X_s} = \frac{X_o}{X_i(1+AB)} = \frac{A}{1+AB}$$

$$A_f = \frac{A}{1+AB}$$

$$A_f = \frac{A}{1+AB}$$

where  $A \rightarrow$  Gain without feedback (i) open loop gain.

$A_f \rightarrow$  Gain with feedback (ii) closed loop gain

$AB \rightarrow$  loop gain.

$(1+AB) \rightarrow$  Decensitivity factor.

Normally loop gain  $AB \gg 1$

$$\therefore A_f < A$$

$\therefore$  Negative feedback reduces the Gain.

on 19<sup>th</sup> Thursday



Advantages of negative feedback:-

1) Negative feedback stabilizes the gain.

\* Negative feedback decentsifies the gain and makes the overall gain independent of  $A$ . ( $A$ -open loop gain)

2) Negative feedback increases the band width.

3) Negative feedback reduces noise.

4) Negative feedback reduces distortion.

5) Negative feedback changes input & output impedances in favour of the amplifier.

Negative feedback stabilizes the gain :-

$$A_f = \frac{A}{1+AB}$$

Diff w.r.t to A on B.S.

$$\frac{dA_f}{dA} = \frac{d}{dA} \left( \frac{A}{1+AB} \right)$$

$$\frac{dA_f}{dA} = \frac{(1+AB)(1) - A(B)}{(1+AB)^2}$$

$$\frac{dA_f}{dA} = \frac{1}{(1+AB)^2}$$

$$dA_f = \frac{dA}{(1+AB)^2}$$

Divide with  $A_f$  on B.S.

$$\frac{dA_f}{A_f} = \frac{dA}{A_f(1+AB)^2} = \frac{dA}{\left(\frac{A}{1+AB}\right)(1+AB)^2}$$

$$\frac{dA_f}{A_f} = \frac{dA}{A(1+AB)} = \frac{dA}{A(1+AB)}$$

$$\boxed{\frac{dA_f}{A_f} \times 100 = \frac{\frac{dA}{A} \times 100}{(1+AB)}}$$

Negative feedback decays the gain (it) makes gain independent of A :-

$$A_f = \frac{A}{1+AB}$$

Normally loop gain is selected such that  $AB \gg 1$

$$\therefore A_f \approx \frac{A}{AB} \approx \frac{1}{B} \Rightarrow \boxed{A_f \approx \frac{1}{B}}$$

$\therefore A_f$  is independent of A.

$A_f$  is more stable because now it depends only on feed back factor  $\beta$ .

$\beta$  network consists of passive elements like resistors and capacitors which are stable.



2) Negative feedback increases the band width:-

Let  $A$ ,  $BW$  be the gain ; Bandwidth without feed back.

Let  $A_f$ ,  $BW_f$  be the gain, Bandwidth with feedback.

Gain bandwidth product is constant for an amplifier.


$$\therefore A(BW) = A_f(BW_f)$$

$$A(BW) = \frac{A}{1+AB} (BW_f)$$

$$BW_f = (1+AB) (BW)$$



3) Negative feedback Reduces noise:-

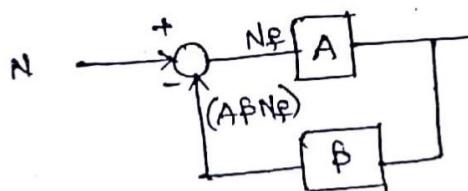

In the above figure  $N$  represents noise at the input of amplifier when there is no feedback.

$N_f$  represents noise at the input of the amplifier after introducing feedback.

From the figure we can


$$N - A\beta N_f = N_f$$

$$N = N_f + A\beta N_f$$

$$N = (1 + A\beta) N_f$$

$$N_f = \frac{N}{(1 + A\beta)}$$

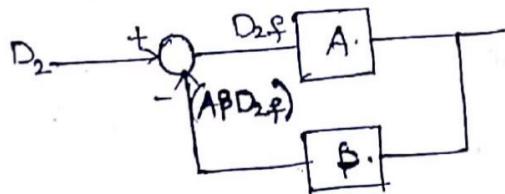i) Negative feedback Reduces distortion (Non-linear Distortion & Harmonic distortion):



Let  $D_2$  represents second harmonic distortion components without feed back.

$D_{2f}$  represents the second harmonic component with feed back.

∴ From the figure

$$D_2 \approx D_{2f} \approx 0$$

$$D_2 - A\beta D_{2f} = D_{2f}$$

$$D_2 = D_{2f} + A\beta D_{2f}$$

$$D_2 = (1 + A\beta) D_{2f}$$

$$D_{2f} = \frac{D_2}{(1 + A\beta)}$$

ii) Negative feedback changes input & output impedances in favour of the amplifier :-

If the feedback signal is returned in series, then the input impedance will increase by  $(1 + A\beta)$  times due to feed back.

For voltage series, current series feed back.

If the feed back signal is returned in shunt then input impedance decreases by  $(1+A\beta)$  times due to feedback.

Ex:- voltage shunt, current shunt  
If the output signal is voltage negative feedback reduces the output impedance by  $(1+A\beta)$  times.

Ex:- voltage shunt, current shunt voltage series.


If the output signal is current feedback increases the output impedance by  $(1+A\beta)$  times.

Ex:- current series, current shunt.

Now

Moliday  
Effect of negative feedback on input impedance :-

Voltage series feedback:-

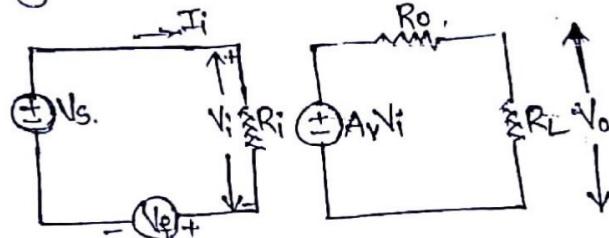

The above figure a voltage amplifier with voltage series feedback.

when there is no feedback  $V_s = V_i + V_f$  But  $V_f = 0$ .

$$\therefore V_s = V_i$$

Input impedance without feedback.

$$R_i = \frac{V_s}{I_i} = \frac{V_i}{I_i}$$

After feedback is introduced  $V_s = V_i + V_f$ .

$$\text{But } V_f = \beta V_o$$

$(V_f \text{ depends on output voltage } V_o,$   
 $\therefore V_f \propto V_o,$   
 $V_f = \beta V_o.)$

$$= \beta \frac{A_v V_i R_L}{R_o + R_L}$$

$$V_f = \beta \frac{A_v R_L}{R_o + R_L} \cdot V_i$$

$$\therefore V_f = \beta A V \cdot V_i$$

$$V_s = V_i + \beta A V \cdot V_i$$

$$V_s = V_i (1 + A \beta)$$

Input impedance with feedback is .


$$R_{if} = \frac{V_s}{I_i} = \frac{V_i (1 + A \beta)}{I_i} = R_i (1 + A \beta)$$

$$\therefore R_{if} = R_i (1 + A \beta)$$

Hence input impedance increases by  $(1 + A \beta)$  times of  $R_i$

22/11/19  
Tuesday.

Current series feedback:-

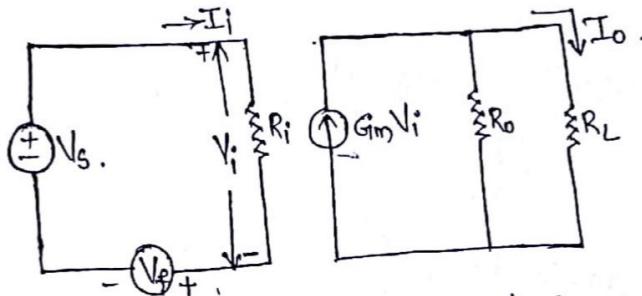

Input voltage without feed back is  $V_s = V_i$

Input impedance without feed back .

$$R_i = \frac{V_s}{I_i} = \frac{V_i}{I_i}$$

After the feedback is introduced

$$V_s = V_i + V_f$$

$$\text{Here } V_f = \beta I_o.$$

$$\therefore V_s = V_i + \beta I_o.$$

$$V_s = V_i + \beta \frac{G_m V_i R_o}{R_o + R_L}$$

$$V_s = V_i \left[ 1 + \beta \frac{G_m R_o}{R_o + R_L} \right]$$

$$V_s = V_i [1 + G_m \beta]$$


Input impedance with feed back is.

$$R_{if} = \frac{V_i}{I_i} = \frac{V_i}{I_i [1 + G_m \beta]}$$

$$R_{if} = R_i [1 + G_m \beta]$$

Hence input impedance increase by  $(1 + G_m \beta)$  times of  $R_i$

Voltage shunt feedback :-

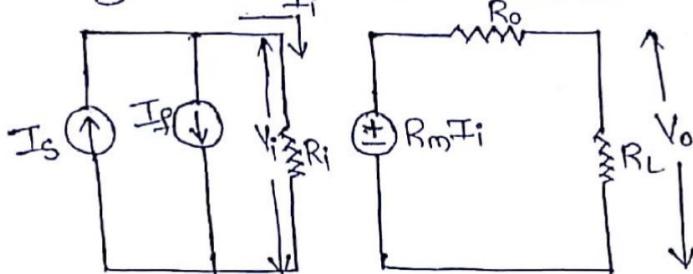

when there is no feed back  $I_s = I_i$

Input impedance without feed back is

$$R_i = \frac{V_i}{I_s} = \frac{V_i}{I_i}$$

After feedback is introduced.

$$I_s = I_f + I_i$$

$$\text{But } I_f = \beta V_o$$

$$I_s = \beta V_o + I_i$$

$$I_s = \beta \frac{R_m I_i R_L}{R_o + R_L} + I_i$$

$$I_s = I_i \left[ \beta \frac{R_m R_L}{R_o + R_L} + 1 \right]$$

$$I_s = I_i (1 + \beta R_m)$$


Input impedance with feedback is.

$$R_{if} = \frac{V_i}{I_s} = \frac{V_i}{I_i (1 + \beta R_m)} = \frac{R_i}{(1 + \beta R_m)}$$

$$R_{if} = \frac{R_i}{(1+\beta R_m)}$$

Hence input impedance decrease by  $(1+\beta R_m)$  times of  $R_i$

### Current shunt feedback:

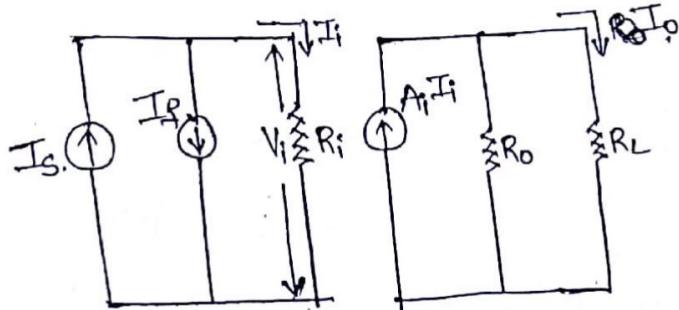

when there is no feed back  $I_s = I_i$   
Input impedance without feed back is

$$R_i = \frac{V_i}{I_s} = \frac{V_i}{I_i}$$

After feed back is introduced.

$$I_s = I_f + I_i$$

$$\text{But } I_f = \beta I_o$$

$$I_s = \beta I_o + I_i$$

$$I_s = \beta \frac{A_i I_f R_o}{R_o + R_L} + I_i$$

$$I_s = I_i \left[ \beta \frac{A_i R_o}{R_o + R_L} + 1 \right]$$

$$I_s = I_i [1 + \beta A_f]$$

Input impedance with feedback is.


$$R_{if} = \frac{V_i}{I_s} = \frac{V_i}{I_i (1 + \beta A_f)} = \frac{R_i}{(1 + \beta A_f)}$$

$$\therefore R_{if} = \frac{R_i}{(1 + \beta A_f)}$$

Hence input impedance decreases by  $(1 + \beta A_f)$  times of  $R_i$

~~RAMILY~~  
Thursday  
Effect of negative feedback on output impedance :-


Voltage series feedback:-

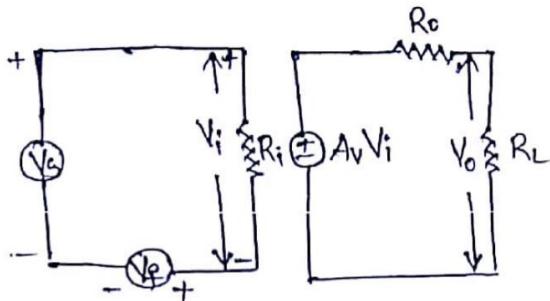

To determine output impedance set  $V_s = 0$  and disconnect  $R_L$ , connect voltage source  $V$  then the output impedance with feedback is given by

$$R_{of} = \frac{V}{I}$$

KVL at the input loop.

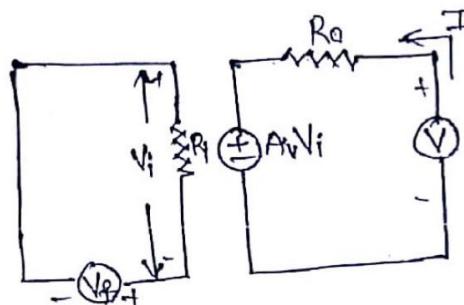

$$V_i + V_f = 0$$

$$V_i = -V_f = -\beta V_o, \text{ but } V_o = V$$

$$\therefore V_i = -V_f = -\beta V$$

KVL at output loop.

$$-V + IR_o + A_v V_i = 0.$$

$$-V + IR_o + A_v(-\beta V) = 0$$

$$V[1 + A_v \beta] = IR_o$$

Output Impedance with feedback is :

$$R_{of} = \frac{V}{I} = \frac{R_o}{(1 + A_v \beta)}$$

$$\therefore R_{of} < R_o$$

Output impedance with feedback including  $R_L$

$$R_{of}' = R_{of} \parallel R_L$$

$$= \frac{R_{of} R_L}{R_{of} + R_L}$$

$$= \frac{\frac{R_o}{1+A\beta} \cdot R_L}{\frac{R_o}{1+A\beta} + R_L}$$

$$= \frac{R_o R_L}{R_o + R_L + A\beta R_L}$$


divide both numerator & denominator  
with  $(R_o + R_L)$

$$= \frac{R_o R_L}{R_o + R_L} \cdot \frac{1 + \beta \left( \frac{A R_L}{R_o + R_L} \right)}{1 + \beta \left( \frac{A R_L}{R_o + R_L} \right)}$$

$$\therefore R_{of}' = \frac{R_o'}{1 + \beta A V}$$


$$R_o' = \frac{R_o R_L}{R_o + R_L}$$

Voltage shunt feedback :-

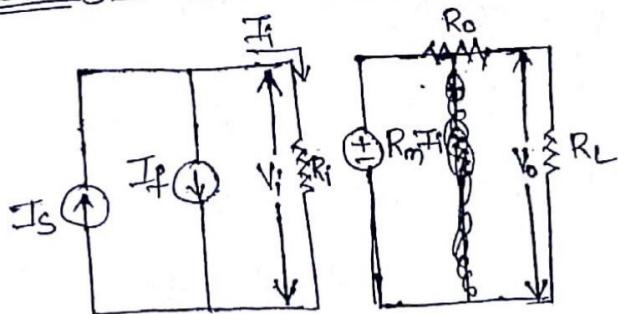

To find output impedance with feedback set  $I_S = 0$   
and disconnect  $R_L$ ; connect voltage source  $V$ .  
The output impedance with feedback is given by

$$R_{of} = \frac{V}{I}$$

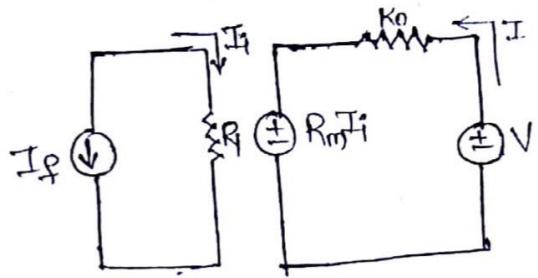

Applying KCL at input loop.

$$I_i + I_f = 0$$

$$I_i = -I_f = -\beta V_o ; V_o = V$$

Applying KVL at output loop.

$$-V + IR_o + R_m I_i = 0$$

$$-V + IR_o + R_m(-\beta V) = 0$$

$$IR_o = V(1 + \beta R_m)$$

∴ output impedance with feedback is

$$R_{of} = \frac{V}{I} = \frac{R_o}{1 + \beta R_m}$$

$$R_{of} < R_o$$

Output impedance with feedback including  $R_L$

$$R'_{of} = R_{of} || R_L$$

$$= \frac{R_{of} R_L}{R_{of} + R_L}$$

$$= \frac{\frac{R_o}{1 + \beta R_m} \cdot R_L}{\frac{R_o}{1 + \beta R_m} + R_L}$$

)

$$= \frac{R_o R_L}{R_o + R_L + \beta R_m R_L}$$


$$R'_{\text{of}} = \frac{R_o R_L}{R_o + R_L}$$

$$1 + \beta \left( \frac{R_m R_L}{R_o + R_L} \right)$$

$$R'_{\text{of}} = \frac{R'_o}{1 + \beta R_m}$$

$$\therefore R'_{\text{of}} < R'_o$$


Current series feedback:

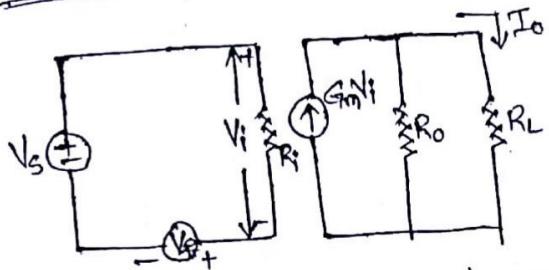

To find output impedance set  $V_s = 0$  and disconnect  $R_L$  and connect voltage source  $V_f$ .

The output impedance with feed back is given by

$$R'_{\text{of}} = \frac{V_f}{I}$$

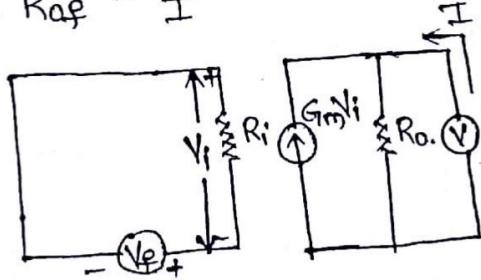

Apply KVL to the input loop:

$$V_i + V_f = 0$$

$$V_i = -V_f = -\beta I_o. \quad (\text{But } I_o = -I)$$

$$V_i = -V_f = \beta I$$

Apply KCL at output loop:

$$G_m V_i + I = \frac{V}{R_o}$$

$$G_m(\beta I) + I = \frac{V}{R_o}$$

$$I(1 + \beta G_m) = \frac{V}{R_o}$$

∴ output impedance with feedback is

$$R_{of} = \frac{V}{I} = R_o(1 + \beta G_m)$$

$$R_{of} > R_o$$

Output impedance with feedback including  $R_L$

$$R'_{of} = R_{of} \parallel R_L$$

$$= \frac{R_{of} \cdot R_L}{R_{of} + R_L}$$

$$= \frac{R_o(1 + \beta G_m) R_L}{R_o(1 + \beta G_m) + R_L}$$

$$= \frac{R_o R_L (1 + G_m \beta)}{R_o + R_L + R_o G_m \beta}$$


$$= \frac{\frac{R_o R_L}{R_o + R_L} (1 + G_m \beta)}{1 + \beta \left( \frac{G_m R_o}{R_o + R_L} \right)}$$

$$R'_{of} = \frac{R_o (1 + G_m \beta)}{1 + G_m \beta}$$

$$G_M < G_m$$


$$\therefore R'_{of} > R'_o$$

S

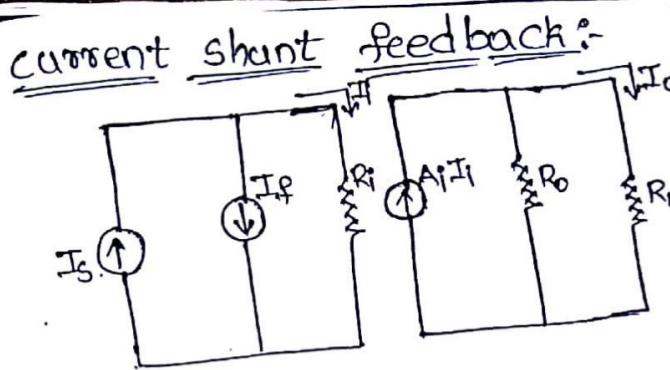

To find output impedance set  $I_S = 0$  and disconnect  $R_L$  and connect voltage source  $V$ .  
The output impedance with feedback is given by

$$R_{of} = \frac{V}{I}$$

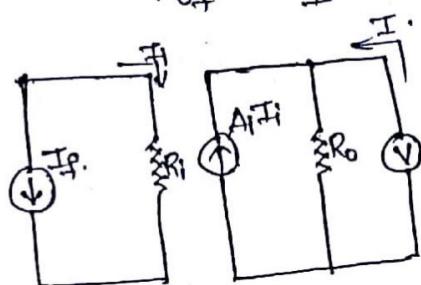

Apply KCL at input loop.

$$I_i + I_f = 0$$

$$I_i = -I_f = -\beta I_O ; \text{ But } (I_O = -I)$$

$$I_i = -I_f = \beta I$$

Apply KCL at output loop:

$$A_i I_i + I = \frac{V}{R_o}$$

$$A_i(\beta I) + I = \frac{V}{R_o}$$

$$I(1 + \beta A_i) = \frac{V}{R_o}$$

output impedance with feedback is

$$R_{of} = \frac{V}{I} = R_o(1 + \beta A_i)$$

$$R_{of} > R_o$$

Output impedance with feedback including  $R_L$

$$R_{of}' = R_{of} // R_L$$

$$= \frac{R_{of} \cdot R_L}{R_{of} + R_L}$$

$$= \frac{R_o(1+\beta A_i)R_L}{R_o(1+\beta A_i) + R_L}$$

$$= \frac{R_o R_L (1+\beta A_i)}{R_o + R_L + \beta A_i R_o}$$

$$= \frac{R_o R_L (1+\beta A_i)}{1 + \beta A_I}$$

$$A_I = \frac{A_i R_o}{R_o + R_L}$$

$$\boxed{R_{of}' = \frac{R_o (1+\beta A_i)}{1 + \beta A_I}}$$

$$A_I < A_i$$

$$\therefore R_{of}' > R_o$$

Parameter      voltage series current series voltage shunt current shunt

Transfer gain(A)       $A_{Vf} = \frac{A_V}{1+A_V\beta}$        $G_{Mf} = \frac{G_M}{1+G_M\beta}$        $R_{Mf} = \frac{R_M}{1+R_M\beta}$        $A_{Iif} = \frac{A_I}{1+A_I\beta}$

Bandwidth       $BW_f = BW(1+A_V\beta)$        $BW_f = BW(1+G_M\beta)$        $BW_f = BW(1+R_M\beta)$        $BW_f = BW(1+A_I\beta)$   
                  Increases      Increases      Increases      Increases

Distortion.       $D_2 = \frac{D_2}{1+A_V\beta}$        $D_2 = \frac{D_2}{1+G_M\beta}$        $D_2 = \frac{D_2}{1+R_M\beta}$        $D_2 = \frac{D_2}{1+A_I\beta}$   
                  Decrease ..      Decrease      Decrease      Decrease ..

Noise       $N_f = \frac{N}{1+A_V\beta}$        $N_f = \frac{N}{1+G_M\beta}$        $N_f = \frac{N}{1+R_M\beta}$        $N_f = \frac{N}{1+A_I\beta}$   
                  Decrease      Decrease      Decrease      Decrease

Input impedance       $R_{if} = R_i(1+A_V\beta)$        $R_{if} = R_i(1+G_M\beta)$        $R_{if} = \frac{R_i}{1+R_M\beta}$        $R_{if} = \frac{R_i}{1+A_I\beta}$   
                  Increase      Increase      Decrease      Decrease

<u>Parameter</u>	<u>Voltage series</u>	<u>Current series</u>	<u>Voltage shunt</u>	<u>Current shunt</u>
Output Impedance.	$R_{oF} = \frac{R_o}{1+A\beta}$	$R_{oF} = \frac{R_o}{1+A\beta}$ $R_{oF} = R_o(1+\beta G_m)$ $R_{oF} = \frac{R_o(HG_m\beta)}{(1+G_m\beta)}$	$R_{oF} = \frac{R_o}{1+\beta R_m}$ $R_{oF} = \frac{R_o}{1+\beta A_1}$	$R_{oF} = R_o(1+A\beta)$ Decrease Increase.
	$R_{oF} = \frac{R_o}{1+A\beta}$		$R_{oF} = \frac{R_o}{1+\beta R_m}$	Decrease Increase

→ Define sensitivity. & Derive an expression for the desensitivity factor in an amplifier.

A. The ratio of the percentage change in gain with feedback to the percentage change in gain without feedback.

$$\frac{dA_F}{A_F} \times 100 = \frac{\frac{dA}{A} \times 100}{1+A\beta}$$

$$\frac{\frac{dA_F}{A_F} \times 100}{\frac{dA}{A} \times 100} = \frac{1}{1+A\beta}$$

$$\boxed{\frac{\left(\frac{dA_F}{A_F}\right)}{\left(\frac{dA}{A}\right)}} = \frac{1}{1+A\beta} = \text{sensitivity}$$

$$\text{Desensitivity factor } D = \frac{1}{\text{sensitivity}} = \frac{1}{\left(\frac{1}{1+A\beta}\right)} = D = 1 + A\beta$$

28/01/19  
Monday.

→

### Fundamental Assumptions of feedback amplifier.

In a negative feedback amplifier  $A_F = \frac{A}{1+A\beta}$ . This equation is true only if 3 conditions are satisfied.

1. The input signal is transmitted to the output through Amplifier A but not through the  $\beta$  network  
 $\therefore \beta$  network must be unilateral. so that it does not trans-

mit a signal from input to output  
2. The feedback signal must be transmitted from output to input through the  $\beta$  network, but not through the amplifiers.

In other words the basic amplifier must be unilateral from input to output and does not transmit any signal from output to input.

3. The  $\beta$ -factor of the ~~feed~~ network should be independent of the source & load resistance i.e.  $R_L, R_S$ .

### Method of Analysis of a Feedback Amplifier :-

steps:-

1. Identify the topology:- Is the feedback signal  $x_f$  a voltage or current, in other words, the  $x_f$  is applied in series or shunt. Is the sampled signal  $x_o$  a voltage or current  
In other words is the sampled signal taken from output node of output loop.

2. Draw the basic amplifier circuit without feedback but taking the loading of the feedback into account.  
3. Use thevenin's source if  $x_f$  is voltage. Use norton's source if  $x_f$  is current.

4. Replace each active device by the proper model.  
(E.g. h-parameter model or hybrid  $\pi$  model).

5. Evaluate feedback factor  $\beta = \frac{x_f}{x_o}$ .

6. Evaluate  $A$  by applying KVL, KCL to the circuit obtained in step 4

7. From the values of  $A$  &  $B$ . Determine  $A_f$ ,  $R_{o_f}$ ,  $R'_o$ ,  $C$   
In step-2 the basic amplifier circuit without feedback but  
taking the effect of feedback in to account is obtained  
by following the following steps.

To find the input circuit

i) set  $V_o = 0$  for voltage sampling, In other words short  
circuit the output.

ii) Set  $I_o = 0$  for <sup>current</sup> sampling, In other words open  
circuit the output.

To find the output circuit

i) Set  $V_i = 0$  for <sup>shunt</sup> comparison, In other words short  
circuit the input node.

ii) Set  $I_i = 0$  for series comparison, In other words  
open circuit the ~~output~~ input node.

07/08/19  
Thursday

## 4. OSCILLATORS

### Oscillators:-

It is an electronic circuit which generates a periodic signal at the output without an external AC input signal.

To generate the periodic signal circuit is supplied with energy from a DC source.


(AC Signal)

### Classification of oscillators:-

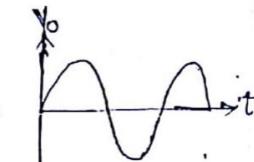
1) According to the shape of the output waveform generated, oscillators can be classified as

- sinusoidal oscillators.
- non-sinusoidal or Relaxation oscillators.
- Astable Multivibrator.


sinusoidal oscillators produce sinusoidal signals.



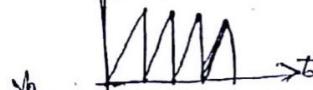Relaxation oscillators produce non-sinusoidal wave forms with abrupt discontinuities.



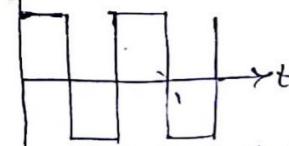Astable Multivibrator produces square or rectangular wave forms.



2) According to the frequency of the output signal, oscillators can be classified as

- Audio frequency oscillators (upto 20KHz)
- Radio frequency oscillators (20KHz to 30MHz)
- Very high frequency oscillators (30MHz to 300MHz)
- Ultra high frequency oscillators (300MHz to 3GHz)
- Microwave frequency oscillators (above 3GHz)

3) According to the fundamental mechanism oscillators are classified into

- Feed back oscillators.


## b) Negative resistance oscillator.

Feedback oscillators use positive feedback to produce oscillation and they satisfy the Barkhausen criteria. Negative resistance oscillators use negative resistance device such as Tunn diode, UJT, SCR.

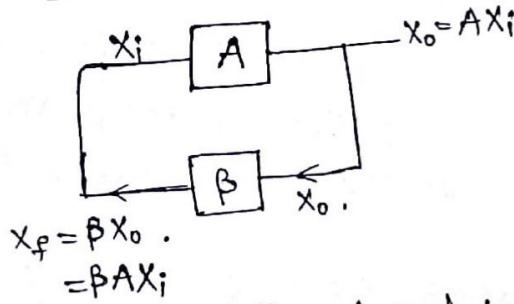- i) According to the type of components used, oscillators are classified in to RC, RL.
- a) RC phase-shift oscillator.
  - b) Wien-bridge oscillator.
  - c) LC-oscillator.
  - d) Crystal oscillator.

14/02/19  
Thursday.

Principle of working principle of oscillator, Bark-hausen criteria :-



In the above figure the closed loop system is shown. If the loop gain  $A\beta = 1$  then  $x_f = x_i$  and the circuit continues to produce  $x_o$  without any external input.

Bark hausen criteria:-

The necessary and sufficient condition for a closed loop system to produce oscillations continuously is  $A\beta = 1$ .


$$\Rightarrow |A\beta| = 1 ; \angle A\beta = 0 \text{ & integral multiple of } 2\pi.$$

This condition is called Bark hausen Criteria.

$|A\beta| = 1$  is called magnitude criteria.

$\angle A\beta = 0 \text{ & } 2\pi$  is called Angle criteria.

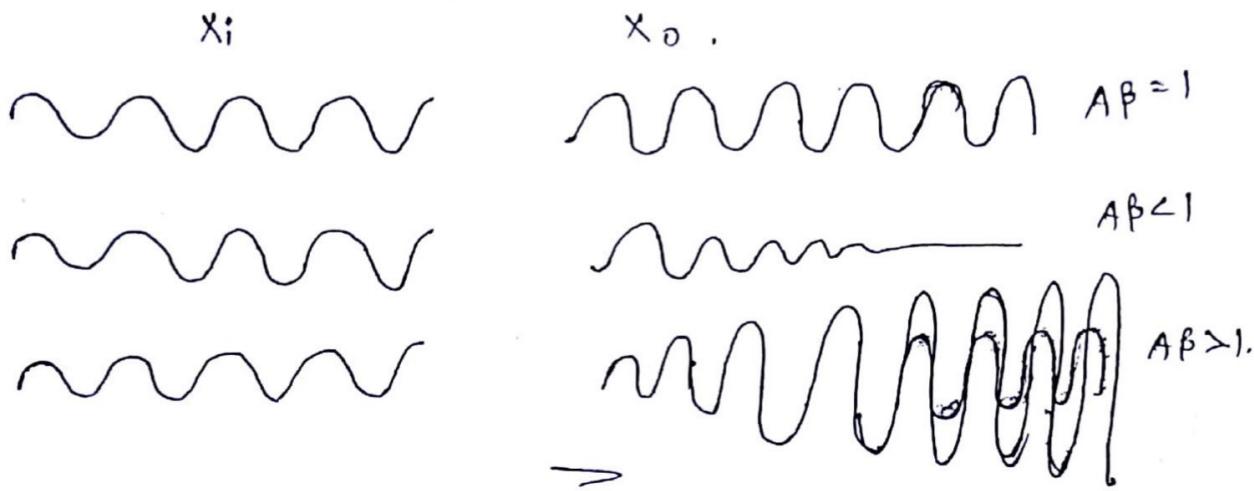If  $A\beta$  is less than 1, the amplitude of the <sup>InPut</sup> signal continues to decrease and oscillations will stop eventually. If ( $A\beta > 1$ )  $A\beta$  is greater than 1, the input signal increases continuously and hence the amplitude of the <sup>Output</sup> output signal diverges and tends to infinity ( $\infty$ )



#### Practical considerations of Barkhausen criteria:-

The required condition for oscillation is  $A\beta=1$ , according to Barkhausen criteria. But due to aging & other reasons the gain of the amplifier  $A$  may fall and this may lead to  $A\beta<1$  and oscillations will eventually stop.

∴ For all practical purposes  $A\beta$  is always set greater than 1.

Theoretically if  $A\beta > 1$  output  $x_o$  should increase continuously and become infinity. But practically as input signal increases, the amplifier moves into non-linear region reducing the gain of the amplifier.

∴ Output signal cannot increase beyond a certain level.


Note:- oscillator will have positive feed back.

## RC oscillators:-

Various types of RC oscillators are.

- 1) <sup>BJT</sup> RC phase shift oscillator.
- 2) FET RC phase shift oscillator.
- 3) Wein bridge oscillator.

## \* BJT RC phase shift oscillator:-

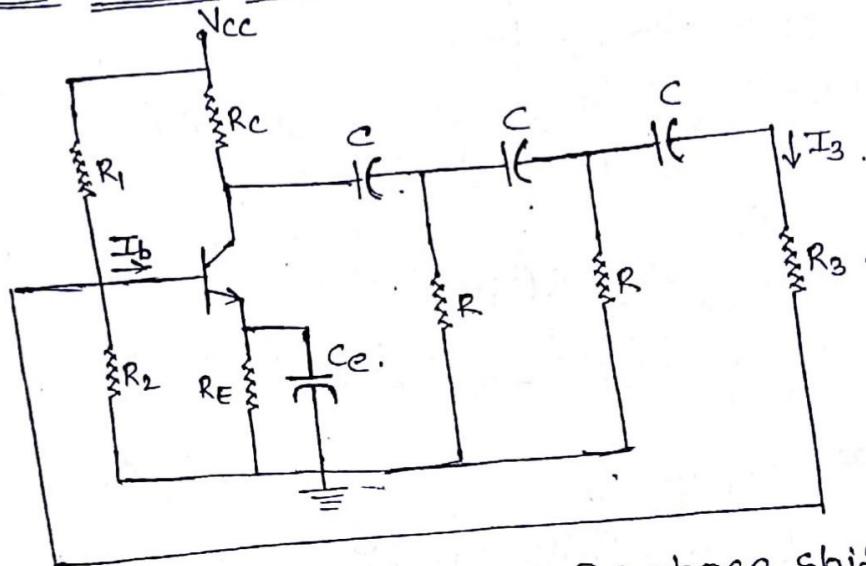

The above figure shows a BJT RC phase shift oscillator. BJT is connected in CE configuration and it produces  $180^\circ$  of phase shift.

The phase shift provided by each RC network is given by  $\tan^{-1} \left[ \frac{-1}{\omega RC} \right]$ .

By properly selecting values of  $R$  &  $C$ , the phase shift provided by each RC network is set to  $60^\circ$ .  $\therefore$  3-RC networks together produces  $180^\circ$  phase shift.


The total phase shift around the loop is  $360^\circ$ .

$\therefore$  The angle criteria of the oscillator is satisfied.


The value of  $R_3$  selected such that  $R_3 + R_i = R$

where  $R_i$  is the input impedance of BJT.

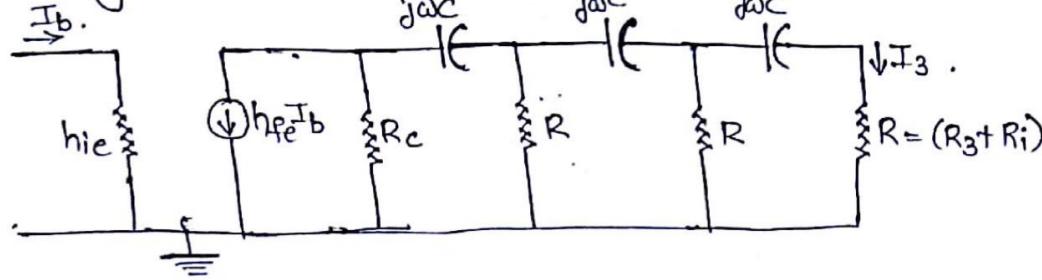Replacing the BJT with approximate h-parameter model.



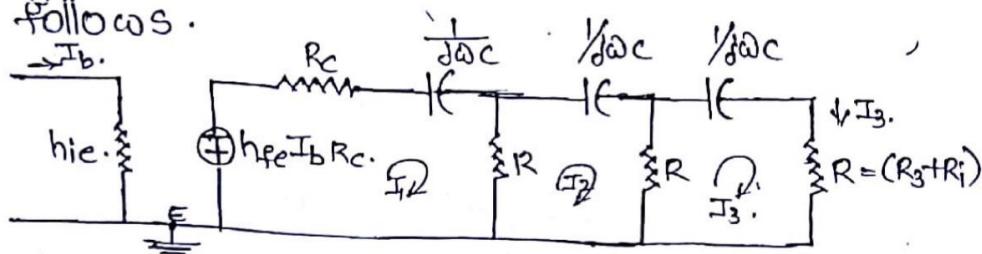Using source transformation, the above circuit can be modified as follows.



Apply KVL for loop ①

$$h_{fe}I_b R_c + R_c I_1 + \frac{1}{j\omega C} I_1 + R(I_1 - I_2) = 0.$$

$$I_1(R_c + R + \frac{1}{j\omega C}) - I_2 R = -h_{fe}I_b R_c \quad \text{---} \textcircled{1}$$

Apply KVL for loop ②

$$R(I_2 - I_1) + \frac{1}{j\omega C} I_2 + R(I_2 - I_3) = 0.$$

$$I_2(R + R + \frac{1}{j\omega C}) - I_1 R - I_3 R = 0.$$

$$I_2(2R + \frac{1}{j\omega C}) - R(I_1 - I_3) = 0 \quad \text{---} \textcircled{2}$$

Apply KVL for loop ③

$$R(I_3 - I_2) + \frac{1}{j\omega C} I_3 + I_3 R = 0.$$

$$I_3(2R + \frac{1}{j\omega C}) - I_2 R = 0 \quad \text{---} \textcircled{3}$$

$$I_1(R_c + R + \frac{1}{j\omega C}) - I_2 R = -h_{fe}I_b R_c \quad \text{---} \textcircled{1}$$

$$I_1(R_c + R + \frac{1}{j\omega C}) - I_1 R - I_3 R = 0 \quad \text{---} \textcircled{2}$$

$$-I_2 R + I_3(2R + \frac{1}{j\omega C}) = 0 \quad \text{---} \textcircled{3}$$

The above three equations can be solved by using cramer rule.

$$I_3 = \frac{\Delta_3}{\Delta}$$

$$\Delta = \begin{vmatrix} R_c + R + \frac{1}{j\omega C} & -R & 0 \\ -R & 2R + \frac{1}{j\omega C} & -R \\ 0 & -R & 2R + \frac{1}{j\omega C} \end{vmatrix}$$

$$= (R_c + R + \frac{1}{j\omega C}) \left[ (2R + \frac{1}{j\omega C})(2R + \frac{1}{j\omega C}) - R^2 \right] + R \left( 2R^2 - \frac{R}{j\omega C} \right) - 0$$

$$+ 0 (R^2 - 0)$$

$$= (R_c + R + \frac{1}{j\omega C}) \left[ 2R^2 + \frac{2R}{j\omega C} + \frac{2R}{j\omega C} + \frac{1}{(j\omega C)^2} \right] - 2R^3 - \frac{R^2}{j\omega C}$$

$$= (R_c + R + \frac{1}{j\omega C}) \left[ 2R^2 + \frac{4R}{j\omega C} - \frac{1}{(\omega C)^2} \right] - 2R^3 - \frac{R^2}{j\omega C}$$

$$= R_c R R A \text{ (cancel)}.$$

$$= R_c \left( 3R^2 + \frac{4R}{j\omega C} - \frac{1}{(\omega C)^2} \right) + R \left( 3R^2 + \frac{4R}{j\omega C} - \frac{1}{(\omega C)^2} \right) + \frac{3R^2}{j\omega C} + \frac{4R}{(j\omega C)^2}$$

$$- \frac{1}{j(\omega C)^3} - 2R^3 - \frac{R^2}{j\omega C}$$

$$= 3R_c R^2 + \frac{4R_c R}{j\omega C} - \frac{R_c}{(\omega C)^2} + 3R^3 + \frac{4R^2}{j\omega C} - \frac{R}{(\omega C)^2} + \frac{3R^2}{j\omega C} - \frac{4R}{(\omega C)^2}$$

$$- \frac{1}{j(\omega C)^3} - 2R^3 - \frac{R^2}{j\omega C}$$

$$= R^3 + 3R_c R^2 - \frac{5R}{\omega C^2} - \frac{R_c}{\omega C^2} + \frac{1}{j} \left[ \frac{4RR_c}{\omega C} + \frac{6R^2}{\omega C} - \frac{1}{\omega^3 C^3} \right]$$

$$= R^3 \left[ 1 + \frac{3R_c R^2}{R^3} - \frac{5R}{R^3 \omega C^2} - \frac{R_c}{\omega C^2 R^3} - j \left( \frac{4RR_c}{R^3 \omega C} + \frac{6R^2}{R^3 \omega C} - \frac{1}{R^3 \omega^3 C^3} \right) \right]$$

$$\Delta = R^3 \left[ 1 + 3 \left( \frac{R_c}{R} \right) - \frac{5}{(\omega RC)^2} - \frac{R_c}{R(\omega RC)} \right] - j \left( \frac{4R_c}{R} \cdot \frac{1}{\omega RC} + \frac{6}{\omega RC} - \frac{1}{(\omega RC)^3} \right)$$

$$\text{Let } \frac{R_c}{R} = K, \frac{1}{\omega R C} = \alpha.$$

$$\Delta = R^3 \left[ (1+3K - 5\alpha^2 - K\alpha^3) - j(4K\alpha + 6\alpha - \alpha^3) \right]$$

$$\Delta = R^3 \left[ (1+3K - (5+K)\alpha^2) - j((6+4K)\alpha - \alpha^3) \right]$$

$$\Delta_3 = \begin{vmatrix} R_c + R + \frac{1}{j\omega C} & -R & -h_{fe} I_b R_c \\ -R & 2R + \frac{1}{j\omega C} & 0 \\ 0 & -R & 0 \end{vmatrix}$$

$$= (R_c + R + \frac{1}{j\omega C})(0-0) + R(0-0) - h_{fe} I_b R_c (R^2 - 0)$$

$$= 0 + 0 - h_{fe} I_b R_c R^2$$

$$\Delta_3 = -h_{fe} I_b R_c R^2$$

$$I_3 = \frac{\Delta_3}{\Delta} = \frac{-h_{fe} I_b R_c R^2}{R^3 \left[ (1+3K - (5+K)\alpha^2) - j((6+4K)\alpha - \alpha^3) \right]}$$

$$\text{loop gain } A_B = \frac{I_3}{I_b} = \frac{-h_{fe} R_c}{R \left[ (1+3K - (5+K)\alpha^2) - j((6+4K)\alpha - \alpha^3) \right]}$$

$$= \frac{-h_{fe} \cdot \left( \frac{R_c}{R} \right)}{(1+3K - (5+K)\alpha^2) - j((6+4K)\alpha - \alpha^3)}$$

$$A_B = \frac{I_3}{I_b} = \frac{-h_{fe} K}{(1+3K - (5+K)\alpha^2) - j((6+4K)\alpha - \alpha^3)}$$

To satisfy Barkhausen criterion  $|A_B| = 1$ ,  $\underline{A_B} = 0$

$\therefore$  Imaginary part in the above equation must be equal to zero.

$$(6+4K)\alpha - \alpha^3 = 0.$$

$$(6+4K) - \alpha^2 = 0.$$

$$\alpha^2 = 6+4K$$

$$\alpha = \sqrt{6+4K}$$

$$\frac{1}{\omega RC} = \sqrt{6+4K}.$$

$$\frac{1}{2\pi f RC} = \sqrt{6+4K}.$$

$$f = \frac{1}{2\pi RC\sqrt{6+4K}}.$$

Condition for sustained oscillations:

The condition for sustained oscillation is  $A\beta > 1$

$$A\beta = \frac{-h_{fe} K}{(1+3K-(5+K)\alpha^2)} > 1$$

But  $\alpha^2 = 6+4K$

$$= \frac{-h_{fe} K}{(1+3K-(5+K)(6+4K))} > 1$$

$$= \frac{-h_{fe} K}{1+3K-30-20K+6K-4K^2} > 1$$

$$= \frac{-h_{fe} K}{-29-23K-4K^2} > 1$$

$$= \frac{h_{fe} K}{4K^2+23K+29} > 1$$


$$h_{fe} K > 4K^2+23K+29$$

$$h_{fe} > 4K + 23 + \frac{29}{K}$$

$$h_{fe} > 4K + \frac{29}{K} + 23.$$

∴

## FET RC phase shift oscillator :-

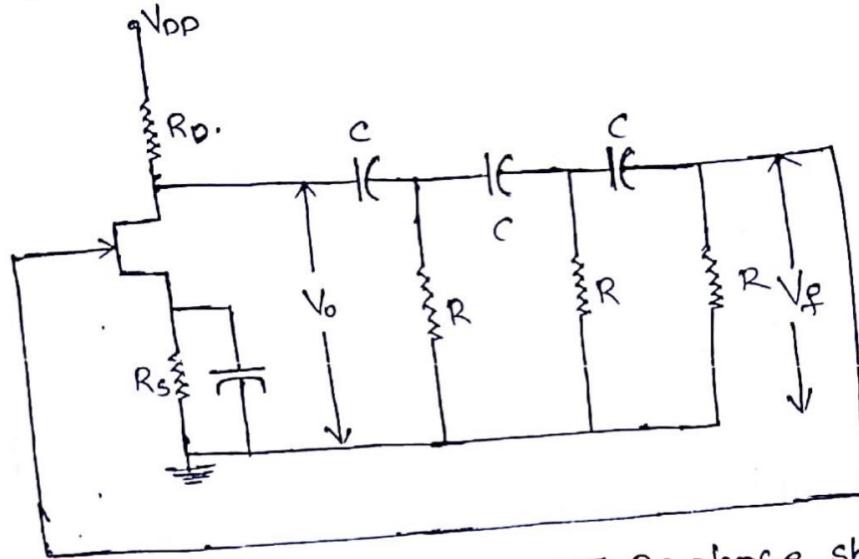

The above figure represents FET RC phase shift oscillator.  
FET is in common source configuration.


∴ It produces  $180^\circ$  phase shift.

Each RC network produces a phase shift of  $\tan^{-1}\left(\frac{1}{\omega RC}\right)$

The values of R, C are adjusted such that the phase shift produced by each RC network is  $60^\circ$ .  
∴ 3 RC networks together will produce  $180^\circ$  phase shift.

∴ the total phase shift around the loop is  $360^\circ$ .

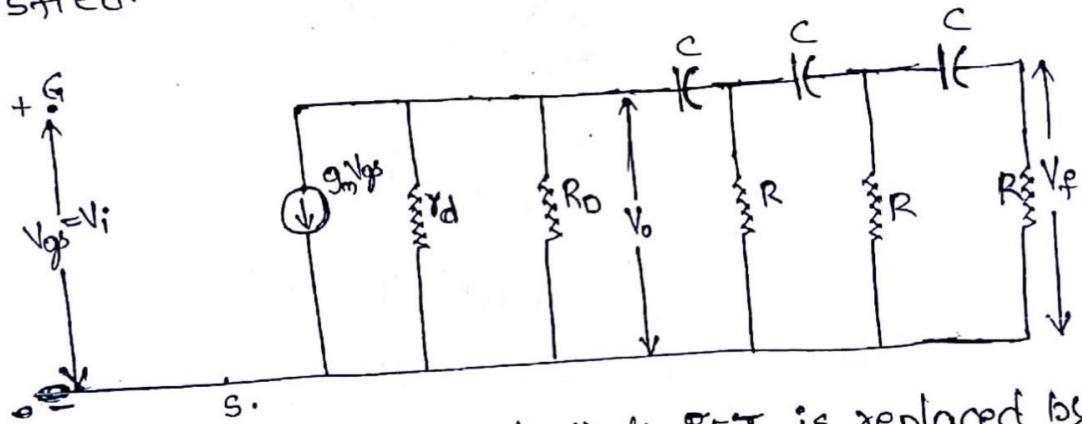The angle condition of the Barkhausen criteria is satisfied.




The above figure represents that FET is replaced by a approximate h-parameter model.

Loop gain =  $A\beta'$ ,

$$A = \frac{V_o}{V_i} ; \beta' = \frac{V_o}{V_o}$$

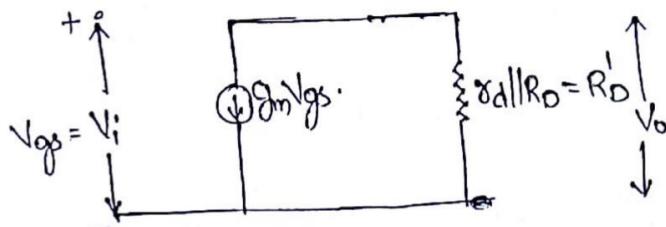The gain A can be derived from the following circuit.




$$V_o = -g_m V_{GS} \cdot R_D$$

$$V_o = -g_m R_D' V_i$$

$$\frac{V_o}{V_i} = A = -g_m R_D'$$

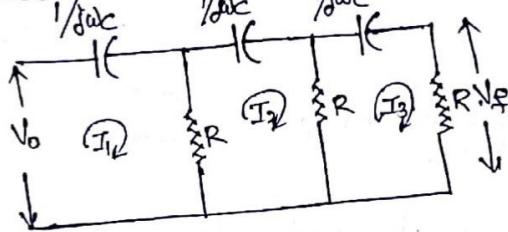To calculate  $\beta'$ ; consider the following circuit



Applying KVL to 1st loop.

$$\frac{I_1}{j\omega C} + R(I_1 - I_2) - V_o = 0.$$

$$\text{Applying } I_1(R + \frac{1}{j\omega C}) - I_2R = V_o. \rightarrow ①$$

Apply KVL to 2nd loop.

$$\frac{I_2}{j\omega C} + (I_2 - I_3)R + R(I_2 - I_1) = 0.$$

$$-I_1R + I_2(R + \frac{1}{j\omega C}) - I_3R = 0. \rightarrow ②$$

Apply KVL to 3rd loop.

$$\frac{I_3}{j\omega C} + I_3R + (I_3 - I_2)R = 0.$$

$$-I_2R + I_3(R + \frac{1}{j\omega C}) = 0 \rightarrow ③$$

8/08/19  
Monday

The above 3 equations can be solved by using crammer's rule.

$$I_3 = \frac{\Delta_3}{\Delta}$$

$$\Delta = \begin{vmatrix} R + \frac{1}{j\omega C} & -R & 0 \\ -R & 2R + \frac{1}{j\omega C} & -R \\ 0 & -R & 3R + \frac{1}{j\omega C} \end{vmatrix}$$

$$\Delta = (R + \frac{1}{j\omega C}) \left[ 4R^3 + \frac{4R}{j\omega C} + \frac{2R}{j\omega C} \cdot \frac{1}{(\omega C)} - R^2 \right] + (-R) \left( -2R^2 - \frac{R}{j\omega C} \right)$$

+ 0 (00)

$$= (R + \frac{1}{j\omega C}) \left[ 3R^3 + \frac{4R}{j\omega C} - \frac{1}{(\omega C)^2} \right] + R \left( -2R^2 - \frac{R}{j\omega C} \right)$$

$$= (R + \frac{1}{j\omega C}) \left[ 3R^3 + \frac{4R}{j\omega C} - \frac{1}{(\omega C)^2} \right] - 2R^3 - \frac{R^2}{j\omega C}$$

$$= 3R^3 + \frac{4R^2}{j\omega C} - \frac{R}{\omega C^2} + \frac{3R^2}{j\omega C} - \frac{4R}{\omega C^2} - \frac{1}{j\omega^3 C^3} - 2R^3 - \frac{R^2}{j\omega C}$$

$$= R^3 + \frac{6R^2}{j\omega C} - \frac{5R}{\omega C^2} - \frac{1}{j\omega^3 C^3}$$

$$\Delta = R^3 - \frac{5R}{\omega C^2} + \frac{1}{j} \left( \frac{6R^2}{\omega C} - \frac{1}{\omega^3 C^3} \right)$$

$$\Delta = R^3 \left[ 1 - \frac{5}{R^2 \omega^2 C^2} + \frac{1}{j} \left( \frac{6}{\omega RC} - \frac{1}{R^3 \omega^3 C^3} \right) \right]$$

$$\text{Let } \alpha = \frac{1}{\omega RC}$$

$$\Delta = R^3 \left[ 1 - 5\alpha^2 + \frac{1}{j} (6\alpha - \alpha^3) \right]$$

$$\Delta_3 = \begin{vmatrix} R + \frac{1}{j\omega C} & -R & V_0 \\ -R & RR + \frac{1}{j\omega C} & 0 \\ 0 & -R & 0 \end{vmatrix}$$

$$= \left( R + \frac{1}{j\omega C} \right) (0 - 0) - (-R)(0 - 0) + V_0 \left( R - \cancel{\left( RR + \frac{1}{j\omega C} \right)} \right)$$

$$\Delta_3 = 0 - 0 + V_0 \cancel{\left( R - \frac{1}{j\omega C} \right)}.$$

$$\Delta_3 = V_0 R'$$

$$I_3 = \frac{\Delta_3}{\Delta} = \frac{V_0 R'}{R [1 - 5\alpha^2 + \frac{1}{j} (6\alpha - \alpha^3)]}.$$

$$= \frac{V_0}{R [1 - 5\alpha^2 - j(6\alpha - \alpha^3)]}.$$

$$V_f = I_3 \cdot R = \frac{V_0 \cdot R}{R [1 - 5\alpha^2 - j(6\alpha - \alpha^3)]}$$

$$V_f = \frac{V_0}{[1 - 5\alpha^2 - j(6\alpha - \alpha^3)]}$$

$$\beta = \frac{V_f}{V_0} = \frac{1}{1 - 5\alpha^2 - j(6\alpha - \alpha^3)}$$

$$\therefore A\beta = \frac{-g_m R_D}{1 - 5\alpha^2 - j(6\alpha - \alpha^3)}$$

To satisfy Barkhausen criterion  $|A\beta| = 1, \angle A\beta = 0$

$\therefore$  Imaginary part of  $A\beta$  should be zero.

$$\therefore -(6\alpha - \alpha^3) = 0$$

$$6 - \alpha^2 = 0.$$

$$\alpha^2 = 6.$$

$$\alpha = \sqrt{6}$$

$$\frac{1}{2\pi n c} = \sqrt{6}$$

$$\frac{1}{2\pi f RC} = \sqrt{6},$$

$$\Rightarrow f = \frac{1}{2\pi RC\sqrt{6}}.$$

Condition for sustained oscillations:-

For sustained oscillations, the condition is  $A\beta > 1$

$$A\beta = \frac{-g_m R_D'}{1 - 5\alpha'} > 1$$

$$= \frac{-g_m R_D'}{1 - 5(6)} > 1$$

$$= \frac{-g_m R_D'}{1 - 29} > 1$$

$$= \frac{g_m R_D'}{29} > 1$$

$$\therefore g_m R_D' > 29$$

$$|A| > 29$$

$$|AB| > 1$$


$$|\beta| > \frac{1}{A}$$

$$|\beta| > \frac{1}{29}$$

$\Rightarrow$

Wein bridge oscillator:

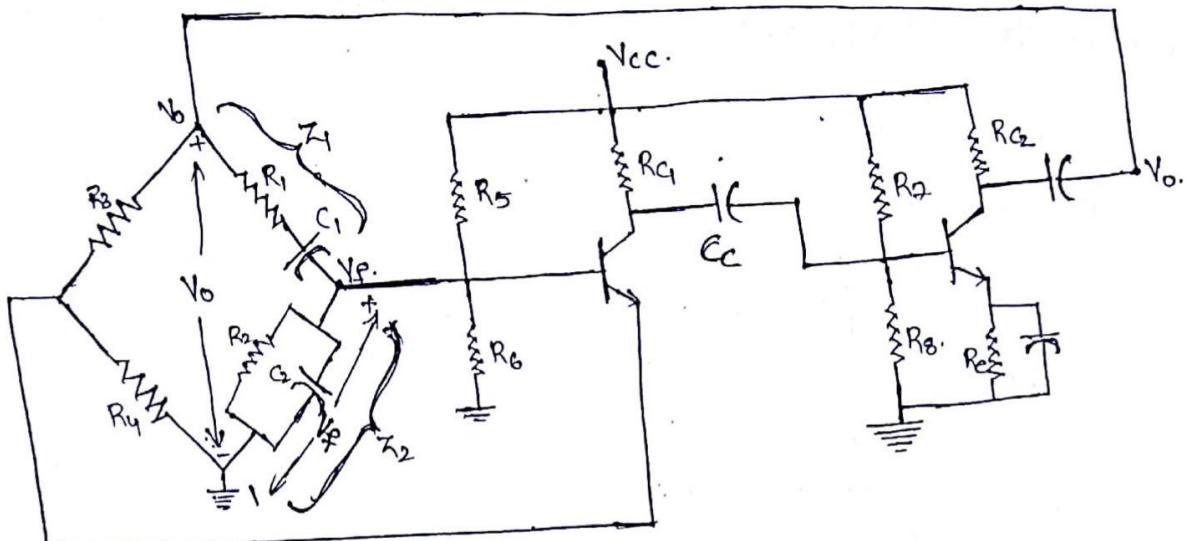The below circuit shows Wien-bridge oscillator. Each CE Amplifier produces  $180^\circ$  phase shift.  
 $\therefore$  phase shift provided by both CE Amplifiers together is  $360^\circ$ .



Under balanced condition the bridge will produce  $0^\circ$  phase shift.

$\therefore$  Total phase shift around the loop is  $360^\circ$ , satisfying the Barkhausen angle criteria.

Under Balance condition.

$$\frac{R_3}{R_4} = \frac{Z_1}{Z_2}$$

$$Z_1 = R_1 + \frac{1}{j\omega C_1} = \frac{1 + j\omega R_1 C_1}{j\omega C_1}$$

$$Z_2 = R_2 \parallel \frac{1}{j\omega C_2} = \frac{\frac{R_2}{j\omega C_2}}{\frac{1 + j\omega R_2 C_2}{j\omega C_2}} = \frac{R_2}{1 + j\omega R_2 C_2}$$

$$\frac{R_3}{R_4} = \frac{\frac{1 + j\omega R_1 C_1}{j\omega C_1}}{\frac{R_2}{1 + j\omega R_2 C_2}} = \frac{(1 + j\omega R_1 C_1)(1 + j\omega R_2 C_2)}{j\omega R_2 C_1}$$

$$\frac{R_3}{R_4} = \frac{1 + j\omega R_2 C_2 + j\omega R_1 C_1 - \tilde{\omega} R_1 R_2 C_1 C_2}{j\omega R_2 C_1}$$

$$\frac{R_3}{R_4} = \frac{1 - \tilde{\omega} R_1 R_2 C_1 C_2}{j\omega R_2 C_1} + \frac{j\omega (R_2 C_2 + R_1 C_1)}{j\omega R_2 C_1}$$

$$\frac{R_3}{R_4} = -\frac{j(1 - \tilde{\omega} R_1 R_2 C_1 C_2)}{\tilde{\omega} R_2 C_1} + \frac{R_2 C_2 + R_1 C_1}{R_2 C_1}$$

Equating the imaginary parts on both sides of the equation.

$$0 = -j(1 - \bar{\omega} R_1 R_2 C_1 C_2)$$

$$\Rightarrow \bar{\omega} R_1 R_2 C_1 C_2 = 1$$

$$\Rightarrow \bar{\omega} = \frac{1}{R_1 R_2 C_1 C_2}$$

$$\bar{\omega} = \frac{1}{\sqrt{R_1 R_2 C_1 C_2}}$$

$$2\pi f = \frac{1}{\sqrt{R_1 R_2 C_1 C_2}}$$

$$f = \frac{1}{2\pi\sqrt{R_1 R_2 C_1 C_2}}$$

$$\text{If } R_1 = R_2 = R$$

$$C_1 = C_2 = C$$

$$\boxed{f = \frac{1}{2\pi R C}}$$

Condition of sustained oscillations :-

conditions for sustained oscillations is  $AB > 1$


$$\text{In above figure } \beta = \frac{V_f}{V_o}$$

$$\therefore V_f = \frac{V_o Z_2}{Z_1 + Z_2}$$

$$\beta \doteq \frac{V_f}{V_o} = \frac{Z_2}{Z_1 + Z_2}$$

$$\begin{aligned} &= \frac{R_2}{1 + j\bar{\omega} R_2 C_2} \\ &= \frac{1 + j\bar{\omega} R_1 C_1}{j\bar{\omega} C_1} + \frac{R_2}{1 + j\bar{\omega} R_2 C_2} \end{aligned}$$
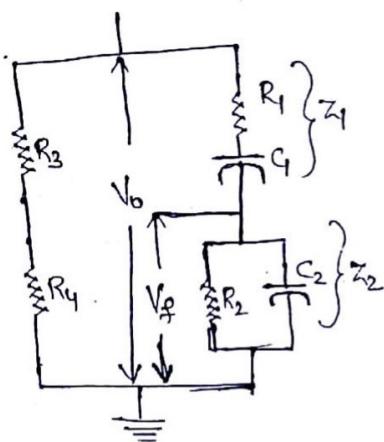
$$\begin{aligned} \beta &= \frac{R_2}{(1 + j\bar{\omega} R_2 C_2)} \\ &= \frac{(1 + j\bar{\omega} R_1 C_1)(1 + j\bar{\omega} R_2 C_2) + j\bar{\omega} R_2 C_1}{(j\bar{\omega} C_1)(1 + j\bar{\omega} R_2 C_2)} \end{aligned}$$



$$\beta = \frac{j\omega R_2 C_1}{(1+j\omega R_1 C_1)(1+j\omega R_2 C_2) + j\omega R_2 C_1}$$

$$\beta = \frac{j\omega R_2 C_1}{1+j\omega R_2 C_2 + j\omega R_1 C_1 - \tilde{\omega} R_1 R_2 C_1 C_2 + j\omega R_2 R_1}$$

Let  $R_1 = R_2 = R$

$$C_1 = C_2 = C$$

$$\beta = \frac{j\omega RC}{(1-\tilde{\omega} R C) + j3\omega RC}$$

But  $\omega RC = 1$

$$\beta = \frac{j\omega RC}{j3\omega RC} = \frac{1}{3} \Rightarrow \boxed{\beta = \frac{1}{3}}$$


$$A\beta > 1$$

$$A > \frac{1}{\beta}$$

$$\boxed{A > \frac{1}{3}}$$


$\therefore$  Minimum gain of the amplifier in Wien bridge oscillator is 3.

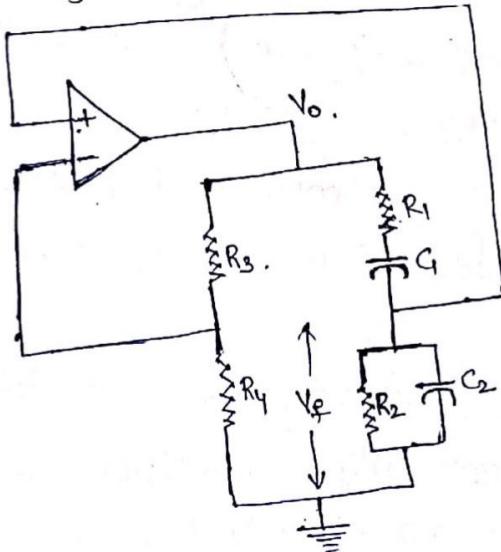Wien bridge oscillator using op-amp (optional Amplifier).



30/19  
Thursday.

## LC oscillators:

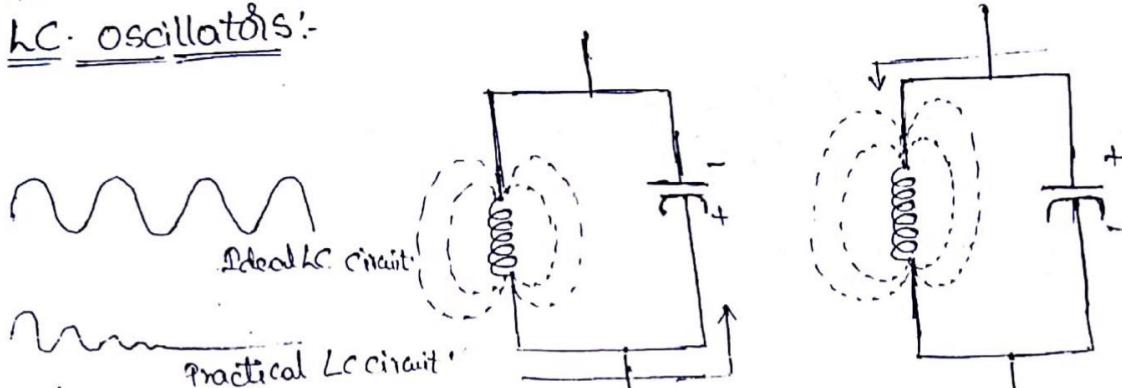

The above figure shows a parallel combination of an inductor and capacitor.

Let us assume the capacitor is initially charged and both L, C are ideal. Capacitor stores energy in the form of static electric field. Since it is connected to inductor, it begins to discharge through inductor.

All the energy stored in the capacitor is transferred to inductor. Inductor stores energy in the form of static magnetic field.

Once the inductor is fully charged, it begins to discharge through the capacitor.

∴ the stored magnetic energy gets converted into static electric energy.

This continues till the inductor is fully discharged.


This process repeats indefinitely and produces sinusoidal oscillations across the LC circuit.

But practically there exist a small resistance in the LC circuit because ideal capacitor & ideal inductor will not exist.


Because of this resistance energy is lost during each conversions and eventually oscillations will die.

LC circuit is also called as tank circuit.
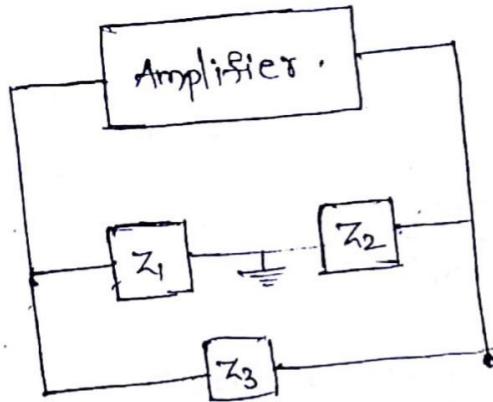
## General form of LC oscillator circuit :-



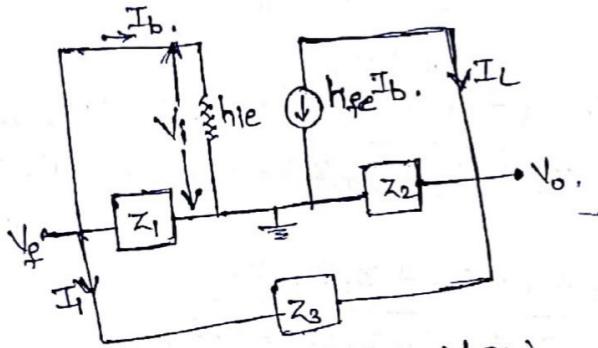The above figure shows a general LC oscillator circuit. Impedances,  $Z_1$ ,  $Z_2$  &  $Z_3$  will form the tank circuit. Assume the amplifier is a BJT amplifier. Replacing the amplifier with approximate h-parameter model.



To satisfy Barkhausen criteria  $A_f$  must be 1.

$$A = \text{Voltage gain} = \frac{V_o}{V_i} = \frac{I_L Z_L}{I_I Z_I} = \left( \frac{I_L}{I_I} \right) \frac{Z_L}{Z_I}$$

$$A = \frac{A_I \cdot Z_L}{Z_I}$$

$$A_I = \frac{I_L}{I_I} ; I_L = -h_{fe} I_b ; I_I = I_b$$

$$A_I = \frac{-h_{fe} I_b}{I_b} = -h_{fe}$$

$$Z_I = \frac{V_i}{I_I} = \frac{I_b h_{ie}}{I_b} = h_{ie}$$

The load impedance

$$Z_L = Z_2 \parallel Z'_3$$

$$\text{where } Z'_3 = Z_3 + Z'$$

$$z_1' = z_1 \parallel hie$$

$$z_1' = \frac{hie z_1}{z_1 + hie}$$

$$z_3' = z_3 + z_1' = z_3 + \frac{hie z_1}{z_1 + hie}$$

$$= \frac{z_1 z_3 + hie z_3 + hie z_1}{z_1 + hie}$$

$$z_L = z_2 \parallel z_3' = \frac{z_2 \left( \frac{z_1 z_3 + hie z_3 + hie z_1}{z_1 + hie} \right)}{z_2 + \left( \frac{z_1 z_3 + hie z_3 + hie z_1}{z_1 + hie} \right)}$$

$$= \frac{z_1 z_2 z_3 + hie z_2 z_3 + hie z_1 z_2}{z_1 z_2 + hie z_2 + z_1 z_3 + hie z_3 + hie z_1}$$


$$z_L = \frac{(hie z_1 + hie z_3 + z_1 z_3) z_2}{hie (z_1 + z_2 + z_3) + z_1 z_2 + z_1 z_3}$$

$$A = \frac{A_{II} \cdot z_L}{z_i} = \frac{-h_{fe} (hie z_1 + hie z_3 + z_1 z_3) z_2}{hie (z_1 + z_2 + z_3) + z_1 z_2 + z_1 z_3}$$


$$A = \frac{-h_{fe} (hie z_1 + hie z_3 + z_1 z_3) z_2}{hie [hie (z_1 + z_2 + z_3) + z_1 z_2 + z_1 z_3]}$$

Feedback Factor  $\beta = \frac{V_F}{V_o}$
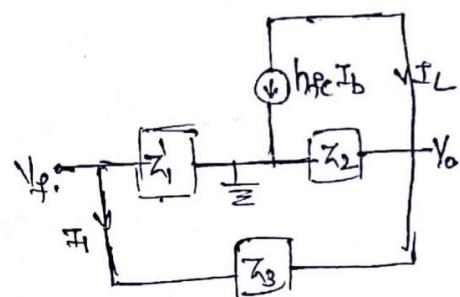
$$V_F = -I_1 z_1' = -I_1 \frac{hie z_1}{z_1 + hie}$$


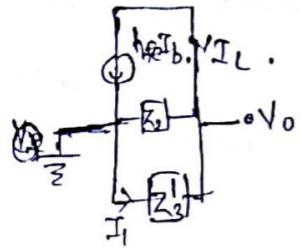
$$V_o = -I_1 Z_3' = -I_1 \times \left( \frac{Z_1 Z_3 + h_{ie} Z_3 + h_{ie} Z_1}{Z_1 + h_{ie}} \right)$$



$$\beta = \frac{V_o}{V_B} = \frac{-I_1 \cdot h_{ie} Z_1}{Z_1 + h_{ie}} = -\frac{I_1 \left( Z_1 Z_3 + h_{ie} Z_3 + h_{ie} Z_1 \right)}{Z_1 + h_{ie}}$$

$$\beta = \frac{h_{ie} Z_1}{h_{ie} Z_1 + h_{ie} Z_3 + Z_1 Z_3}$$

$$\therefore AB = \left( \frac{-h_{fe} (h_{ie} Z_1 + h_{ie} Z_3 + Z_1 Z_3) Z_2}{h_{fe} (h_{ie} (Z_1 + Z_2 + Z_3) + Z_1 Z_2 + Z_1 Z_3)} \right) \times \left( \frac{h_{ie} Z_1}{h_{ie} Z_1 + h_{ie} Z_3 + Z_1 Z_3} \right) = 1$$

$$\Rightarrow \frac{-h_{fe} Z_1 Z_2}{h_{ie} (Z_1 + Z_2 + Z_3) + Z_1 Z_2 + Z_1 Z_3} = 1$$


$$\Rightarrow h_{ie} (Z_1 + Z_2 + Z_3) + Z_1 Z_2 + Z_1 Z_3 = -h_{fe} Z_1 Z_2$$

$$\Rightarrow h_{ie} (Z_1 + Z_2 + Z_3) + Z_1 Z_2 (1 + h_{fe}) + Z_1 Z_3 = 0$$

The above equation is called the general equation for the LC oscillator.

01/08/19  
Friday.

Hartley oscillator :-

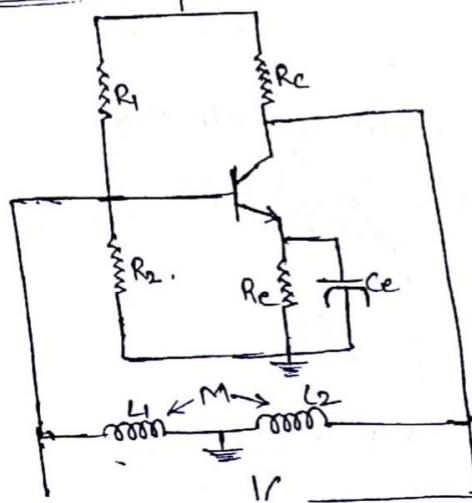

The above figure shows a hartley oscillator. The CE amplifier produces  $180^\circ$  phase shift & LC tank circuit produces  $180^\circ$  phase shift.

$\therefore$  Total phase shift is  $360^\circ$ , satisfying the Barkhausen criteria.

The general equation for the LC oscillator is

$$h_{ie} [z_1 + z_2 + z_3] + z_1 z_2 (1 + h_{fe}) + z_1 z_3 = 0.$$

$$z_1 = j\omega L_1 + j\omega M$$

$$z_2 = j\omega L_2 + j\omega M$$

$$z_3 = \frac{1}{j\omega C}$$

$$h_{ie} \left[ j\omega L_1 + j\omega M + j\omega L_2 + j\omega M + \frac{1}{j\omega C} \right] + (j\omega L_1 + j\omega M)(j\omega L_2 + j\omega M) (1 + h_{fe}) + (j\omega L_1 + j\omega M) \left( \frac{1}{j\omega C} \right) = 0.$$

$$h_{ie} \left[ j\omega L_1 + j\omega L_2 + 2j\omega M + \frac{1}{j\omega C} \right] + (j\omega)(L_1 + M)(j\omega)(L_2 + M) + (j\omega)(L_1 + M) \frac{1}{j\omega C} (1 + h_{fe}) = 0$$

$$h_{ie} j\omega \left[ L_1 + L_2 + 2M + \frac{1}{j\omega C} \right] - \omega [L_1 + M][L_2 + M] (1 + h_{fe}) + \frac{[L_1 + M]}{C} = 0$$

$$h_{ie} j\omega \left[ L_1 + L_2 + 2M - \frac{1}{\omega C} \right] - \omega [L_1 + M][L_2 + M] (1 + h_{fe}) + \frac{[L_1 + M]}{C} = 0$$

$$\underbrace{\text{Imaginary part}}_{C} \quad \underbrace{\text{Real part}}_{\omega}$$

Equating imaginary part on both sides

$$j h_{ie} \omega \left[ L_1 + L_2 + 2M - \frac{1}{\omega C} \right] = 0$$

$$L_1 + L_2 + 2M = \frac{1}{\omega^2 C}$$

$$\text{Let } L_1 + L_2 + 2M = L_{eq}$$

$$1 = \frac{1}{\omega^2 C}$$

$$\omega = \frac{1}{\sqrt{L_{eq} C}}$$

$$2\pi f = \frac{1}{\sqrt{L_{eq} C}}$$

$$f = \frac{1}{2\pi\sqrt{L_{eq} C}}$$

Condition for sustained oscillations :-

equating the real part on both sides.

$$-\tilde{\omega} [L_1 + M] [L_2 + M] (1 + h_{fe}) + \frac{[L_1 + M]}{C} = 0,$$

$$\tilde{\omega} (L_1 + M) (L_2 + M) (1 + h_{fe}) = \frac{(L_1 + M)}{C}$$

$$(L_2 + M) (1 + h_{fe}) = \frac{1}{\tilde{\omega} C} \quad \text{But } \frac{1}{\tilde{\omega} C} = L_{eq} = L_1 + L_2 + 2M$$

$$(L_2 + M) (1 + h_{fe}) = L_1 + L_2 + 2M$$

$$(L_2 + M) (1 + h_{fe}) = L_1 + L_2 + 2M$$


$$(L_2 + M) + (L_2 + M) h_{fe} = L_1 + L_2 + 2M$$

$$(L_2 + M) h_{fe} = L_1 + M$$

$$h_{fe} = \frac{L_1 + M}{L_2 + M}$$

05/03/19  
Tuesday

Colpitt's oscillator :-

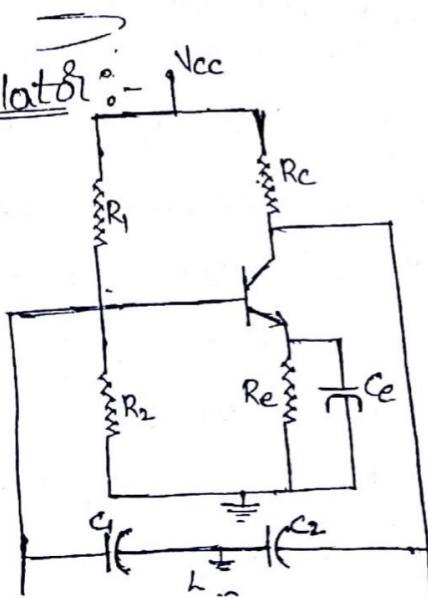

The above figure shows the Colpitt's oscillator. The C.E. amplifier produces 180° phase shift and the LC tank circuit produces another 180° phase shift.

∴ The total phase shift around the loop is 360°, satisfying the Barkhausen criteria.

The general equation for LC oscillator is.

$$h_{ie} [z_1 + z_2 + z_3] + z_1 z_2 (1 + h_{fe}) + z_1 z_3 = 0.$$

$$z_1 = \frac{1}{j\omega C_1}$$

$$z_2 = \frac{1}{j\omega C_2}$$

$$z_3 = j\omega L$$

$$h_{ie} \left[ \frac{1}{j\omega C_1} + \frac{1}{j\omega C_2} + j\omega L \right] + \left( \frac{1}{j\omega C_1} \right) \left( \frac{1}{j\omega C_2} \right) (1 + h_{fe}) + \left( \frac{1}{j\omega C_1} \right) (j\omega L) = 0$$

$$\frac{h_{ie}}{j\omega} \left[ \frac{1}{C_1} + \frac{1}{C_2} + (j\omega)^2 L \right] + \frac{1}{(j\omega)^2 C_1 C_2} (1 + h_{fe}) + \frac{L}{C_1} = 0.$$

$$\text{Let } \frac{1}{C_1} + \frac{1}{C_2} = \frac{1}{C_{eq}}$$

$$\frac{h_{ie}}{j\omega} \left[ \frac{1}{C_{eq}} - \tilde{\omega}^2 L \right] - \frac{1}{\tilde{\omega}^2} \frac{1}{C_1 C_2} (1 + h_{fe}) + \frac{L}{C_1} = 0$$

equating the imaginary part on both sides of equation,

$$\frac{h_{ie}}{\tilde{\omega}} \left[ \frac{1}{C_{eq}} - \tilde{\omega}^2 L \right] = 0$$

$$\frac{1}{C_{eq}} - \tilde{\omega}^2 L = 0$$

$$\frac{1}{C_{eq}} = \tilde{\omega}^2 L$$

$$\tilde{\omega} = \sqrt{\frac{1}{L C_{eq}}}$$

$$\therefore \omega_f = \frac{1}{\sqrt{L C_{eq}}}$$

$$f = \frac{1}{2\pi\sqrt{L C_{eq}}}$$

Condition for sustained oscillations:-

equating the real part on both sides of formula, equation

$$\frac{1}{\omega} \frac{1}{C_1 C_2} (1+h_{fe}) + \frac{1}{C_1} = 0$$

$$\frac{1}{\omega C_1 C_2} (1+h_{fe}) = \frac{1}{C_1}$$

$$\omega_L = \frac{1+h_{fe}}{C_2}$$

$$\frac{1}{C_{eq}} = \frac{1+h_{fe}}{C_2}$$

$$\frac{1}{C_1} + \frac{1}{C_2} = \frac{1}{C_{eq}} + \frac{h_{fe}}{C_2}$$

$$\frac{1}{C_1} = \frac{h_{fe}}{C_2}$$

$$h_{fe} = \frac{C_2}{C_1}$$

Drawback in colpitt's oscillator:-

colpitt's oscillator is a high frequency oscillator. the value of  $C_1, C_2$  will be very small. From the circuit we can observe that  $C_1$  is between base & ground &


$C_2$  is between collector & ground.

But there exist parasitic capacitances junction capacitances between base & ground & collector and ground. these parasitic capacitances will be in parallel with  $C_1$  &  $C_2$  and hence the actual value

of  $C_{eq}$  will change. Hence it is difficult to accuratly predict the frequency. This problem can be

avoided by adding a small capacitor  $C_3$  in series with inductor  $L$ .  
 $C_3$  is such that  $G \ll C_1, C_2$ .

Clapp's oscillator:

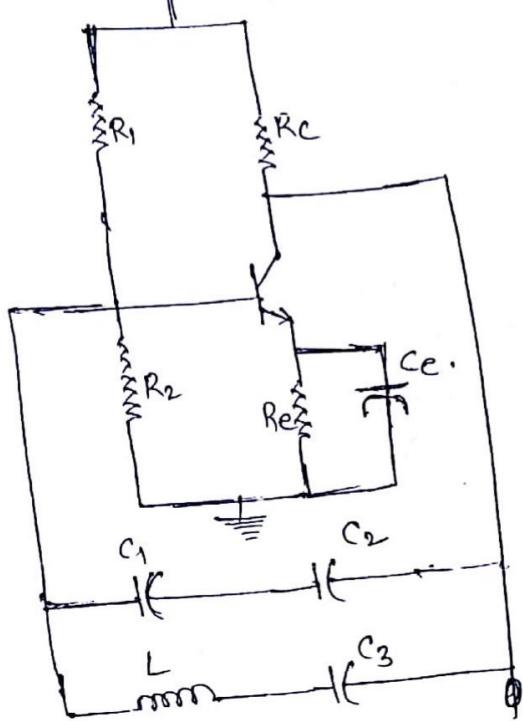

The above circuit is called ~~an~~ Clapp oscillator.  
 The CE Amplifier produces  $180^\circ$  phase shift and  
 LC tank oscillator produces another  $180^\circ$  phase shift.  
 The total phase shift is  $360^\circ$ , which satisfies the Barkhausen criteria, thus the Barkhausen angle criteria is satisfied.  
 The general equation is LC oscillator is

$$rie \{Z_1 + Z_2 + Z_3\} + Z_1 Z_2 (1 + \frac{1}{Z_3}) + Z_1 Z_3 = 0.$$

$$\text{Now } Z_1 = \frac{1}{j\omega C_1}$$

$$Z_2 = \frac{1}{j\omega C_2}$$

$$Z_3 = j\omega L + \frac{1}{j\omega C_3}$$

$$hie \left[ \frac{1}{j\omega C_1} + \frac{1}{j\omega C_2} + j\omega L + \frac{1}{j\omega C_3} \right] + \frac{1}{j\omega C_1} \cdot \frac{1}{j\omega C_2} (1+h_{fe}) - \frac{1}{j\omega C_1} \left( j\omega L + \frac{1}{j\omega C_3} \right) = 0.$$

$$\frac{hie}{j\omega} \left[ \frac{1}{C_1} + \frac{1}{C_2} + j\omega L + \frac{1}{C_3} \right] + \frac{hie}{j\omega} \left[ \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} + (j\omega)^2 L \right] + \frac{1}{(j\omega)^2} \cdot \frac{1}{C_1 C_2} (1+h_{fe}) + \frac{j\omega}{j\omega C_1} \left[ L + \frac{1}{(j\omega)^2 C_3} \right] = 0$$

$$\text{let } \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} = \frac{1}{C_{eq}},$$

$$\frac{hie}{j\omega} \left[ \frac{1}{C_{eq}} - \tilde{\omega}^2 L \right] - \frac{1}{\tilde{\omega}^2 C_2} (1+h_{fe}) + \frac{1}{C_1} \left[ L - \frac{1}{\tilde{\omega}^2 C_3} \right] = 0, \quad \text{real part}$$

Imaginary part

Equating the imaginary part on both sides.

$$\frac{hie}{\tilde{\omega}} \left[ \frac{1}{C_{eq}} - \tilde{\omega}^2 L \right] = 0,$$

$$\frac{1}{C_{eq}} - \tilde{\omega}^2 L = 0$$

$$\tilde{\omega}^2 = \frac{1}{L C_{eq}},$$

$$\tilde{\omega} = \sqrt{\frac{1}{L C_{eq}}},$$

$$\boxed{f = \frac{1}{2\pi\sqrt{L C_{eq}}}},$$

condition for sustained oscillations:

Equating the real part on both sides.

$$\frac{-1}{\tilde{\omega}^2 C_2} (1+h_{fe}) + \frac{1}{C_1} \left( L - \frac{1}{\tilde{\omega}^2 C_3} \right) = 0,$$

$$\frac{-1}{\tilde{\omega}^2 C_2} (1+h_{fe}) + \left( L - \frac{1}{\tilde{\omega}^2 C_3} \right) = 0.$$

$$\frac{-1}{\omega C_2} - \frac{h_{fe}}{\omega C_2} + L - \frac{1}{\omega C_3} = 0$$

~~Take~~ Take  $\frac{1}{\omega}$  common.

$$\frac{-1}{C_2} - \frac{1}{C_3} + \omega L - \frac{h_{fe}}{C_2} = 0$$

but  $\omega L = \frac{1}{C_{eq}}$

$$\frac{-1}{C_2} - \frac{1}{C_3} + \frac{1}{C_{eq}} - \frac{h_{fe}}{C_2} = 0$$

$$\frac{1}{C_2} - \frac{1}{C_3} + \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} - \frac{h_{fe}}{C_2} = 0$$

$$\frac{1}{C} = \frac{h_{fe}}{C_2}$$

$$h_{fe} = \frac{C_2}{C}$$

frequency  $f = \frac{1}{2\pi\sqrt{L C_{eq}}}$

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$

But  $C_3 \ll C_1, C_2$

$$\frac{1}{C_3} \gg \frac{1}{C_1}, \frac{1}{C_2}$$

$$\therefore \frac{1}{C_3} \approx \frac{1}{C_{eq}} \Rightarrow C_{eq} = C_3$$

$$f = \frac{1}{2\pi\sqrt{L C_{eq}}} \approx \frac{1}{2\pi\sqrt{L C_3}}$$

∴ the frequency of the clapp oscillator depends on the value of  $C_3$  rather than on the values of  $C_1, C_2$ .



06/03/19  
wednesday

## Crystal oscillator:-

### Piezo electric Effect:

when an electric field is applied across a piezo electric crystal mechanical vibrations are produced in a direction normal to the applied electric field.

Conversely, if mechanical stress is applied on a piezo electric crystal, electrical signal will be generated with a frequency equal to the resonant frequency of the crystal. This effect is known as piezo electric effect.

Examples of piezo electric crystals are Quartz, Rochelle salt & tourmaline.


Quartz has medium frequency stability and medium physical strength. It is easily available and is very cheap.

Rochelle salt has highest frequency stability and lowest physical strength.

Tourmaline has lowest frequency stability, but highest physical strength and it is more costly.

Quartz is more commonly used.

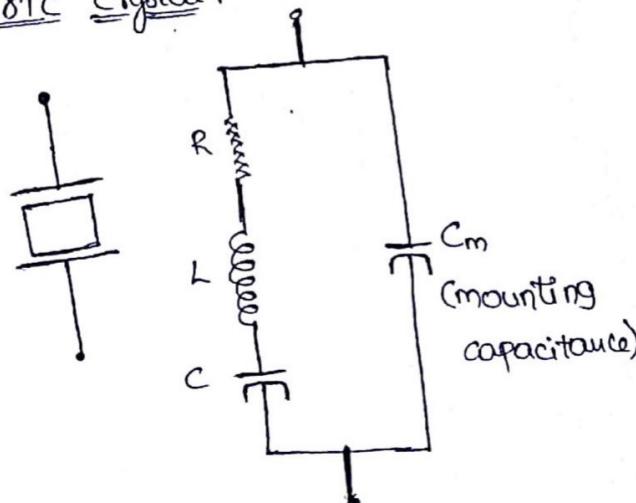Equivalent circuit of crystal oscillator (or) Equivalent circuit of Piezo electric crystal:



In the above circuit,  $R$  represents the resistance of the crystal, which is a result of friction losses of the crystal.  $L$  represents the inductance of the circuit, which is a result of moment of inertia of the crystal.  $C$  represents the capacitance of the circuit, which is a result of stiffness of the crystal.

The crystal is normally placed between two conducting plates and this results in a capacitance called the mounting capacitance.

Crystal can be operated in one of the two mode.

### 1) Fundamental Mode:-

In this mode, the crystal will be operating at a frequency equal to the fundamental resonant frequency of the crystal.

### 2) Overtone mode:-

In this mode, the crystal will be operating at a frequency which is integral multiple of the fundamental frequency.

### Resonance frequency of the crystal:-

Crystal will have two resonance frequencies.

### series Resonance frequency:-

Resonance is that condition where the impedance of the circuit is purely resistive.

∴ At series resonance the reactance of the series RLC circuit will be zero.

$$\therefore j\omega L + \frac{1}{j\omega C} = 0.$$

$$j\omega L = -\frac{1}{j\omega C}$$

$$(j\omega)^2 = \frac{-1}{LC}$$

$$\omega^2 = \frac{1}{LC}$$

$$\omega = \frac{1}{\sqrt{LC}}$$

series

This frequency is called Resonance frequency & denoted by  $\omega_s$ .

$$\omega_s = \frac{1}{\sqrt{LC}}$$

$$2\pi f_s = \frac{1}{\sqrt{LC}}$$

$$f_s = \frac{1}{2\pi\sqrt{LC}}$$

Parallel Resonance Frequency :-

In parallel resonance, the total reactance between the two electrodes of the crystal should be zero.

$$j\omega_L + \frac{1}{j\omega C} + \frac{1}{j\omega C_m} = 0$$

$$j\omega_L = -\frac{1}{j\omega} \left[ \frac{1}{C} + \frac{1}{C_m} \right]$$

$$(j\omega)_L = - \left[ \frac{1}{C} + \frac{1}{C_m} \right]$$

$$\omega_L = \left[ \frac{1}{C} + \frac{1}{C_m} \right]$$

$$\text{Let } \frac{1}{C} + \frac{1}{C_m} = \frac{1}{C_{eq}}$$

$$\omega_L = \frac{1}{C_{eq}}$$

$$\omega = \frac{1}{\sqrt{L C_{eq}}}$$

This is called Parallel resonant frequency & denoted by

$\omega_p$

$$\omega_p = \frac{1}{\sqrt{L C_{eq}}}$$

$$2\pi f_p = \frac{1}{\sqrt{L C_{eq}}}$$

$$f_p = \frac{1}{2\pi\sqrt{L C_{eq}}}$$

$$\frac{1}{C_{eq}} = \frac{1}{C} + \frac{1}{C_m}$$

But  $C_m \gg C$ ;



$$\frac{1}{C_m} \ll \frac{1}{C}$$

$$\frac{1}{C_{eq}} \approx \frac{1}{C}$$

$$C_{eq} \approx C \quad \therefore \omega_s \approx \omega_p$$

Impedance curve of the ~~sur~~ crystal (8) Impedance graph

of the crystal :-

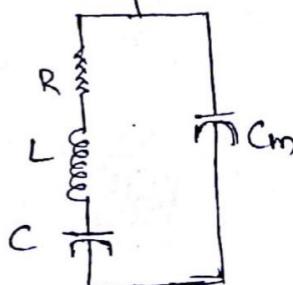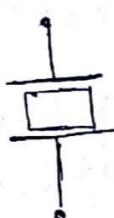

an

The impedance of the above circuit is.

$$Z = \left( R + j\omega L + \frac{1}{j\omega C} \right) \parallel \frac{1}{j\omega C_m}$$

But normally R will be very small, ignore R.

$$\therefore Z = \left( j\omega L + \frac{1}{j\omega C} \right) \parallel \frac{1}{j\omega C_m}$$

$$= \frac{\left( j\omega L + \frac{1}{j\omega C} \right) \left( \frac{1}{j\omega C_m} \right)}{j\omega L + \frac{1}{j\omega C} + \frac{1}{j\omega C_m}}$$

$$= \frac{j\omega L \cdot j\omega C + 1}{j\omega C} \cdot \frac{1}{j\omega C_m} \\ \frac{j\omega L \cdot j\omega C \cdot j\omega C_m + j\omega C_m + j\omega C}{j\omega C \cdot j\omega C_m}$$

$$= \frac{-\tilde{\omega} L C + 1}{-\tilde{\omega} L C \cdot j\omega C_m + j\omega C_m + j\omega C}$$

$$= \frac{1}{j\omega C_m} \left[ \frac{-\tilde{\omega} L C + 1}{-\tilde{\omega} L C + 1 + \frac{j\omega C}{j\omega C_m}} \right]$$

$$= \frac{1}{j\omega C_m} \left[ \frac{-\tilde{\omega} L C + 1}{-\tilde{\omega} L C + 1 + \frac{C}{C_m}} \right]$$

$$= \frac{1}{j\omega C_m} \frac{jC \left[ -\tilde{\omega} + \frac{1}{L C} \right]}{jC \left[ -\tilde{\omega} + \frac{1}{L C} + \frac{1}{C_m} \right]}$$

$$= \frac{1}{j\omega C_m} \left( \frac{-\tilde{\omega} + \frac{1}{L C}}{-\tilde{\omega} + \frac{1}{L} \left( \frac{1}{C} + \frac{1}{C_m} \right)} \right)$$

$$= \frac{1}{j\omega C_m} \left( \frac{-\tilde{\omega} + \frac{1}{L C}}{-\tilde{\omega} + \frac{1}{L C_{eq}}} \right)$$

Thi

$$= \frac{1}{j\omega C_m} \left( \frac{-\hat{\omega} + \hat{\omega}_s}{-\hat{\omega} + \hat{\omega}_p} \right)$$

$$Z = \frac{1}{j\omega C_m} \left( \frac{\hat{\omega} - \hat{\omega}_s}{\hat{\omega} - \hat{\omega}_p} \right)$$

At  $\omega = \omega_s$ ,


$$Z = 0.$$

At  $\omega = \omega_p$ ,  $Z = \infty$ .

For  $\omega < \omega_s$ , impedance is capacitive.


For  $\omega > \omega_p$ , impedance is capacitive.

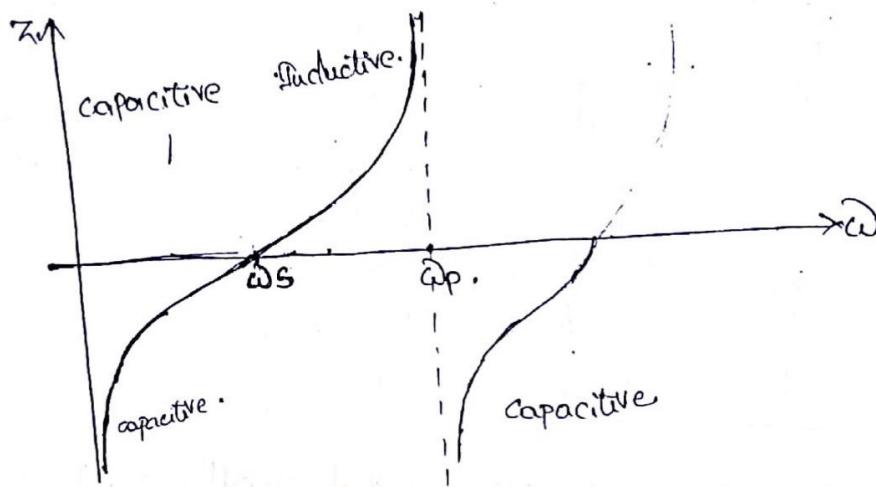For  $\omega_s < \omega < \omega_p$ , impedance is inductive.



07/03/19  
Thursday.

### Pierce crystal oscillator

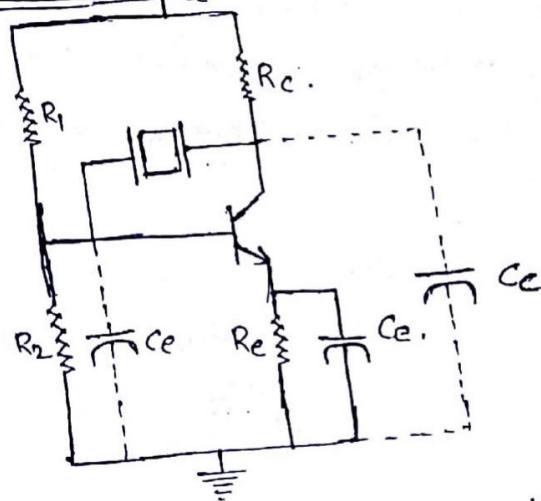

The above figure shows Pierce crystal. The circuit is similar to Colpitt's oscillator. Crystal will behave like an


inductor when operated at a frequency  $\omega$  such that  $\omega_s < \omega < \omega_p$ .

The junction capacitances across the base emitter junction and collector emitter junction will provide the required capacitance for the tank circuit.

\* The frequency of oscillation is given by the resonant frequency of the crystal.

$$f = \frac{1}{2\pi\sqrt{LC}}$$

### Miller crystal oscillator :-

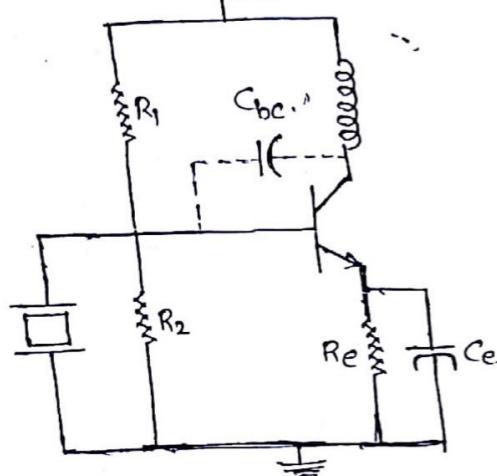

The above figure shows miller crystal oscillator, it is similar to the hartely oscillator. one of the inductors is replaced with crystal and the collector base junction capacitance provides the necessary capacitance to the tank circuit. The circuit oscillates with the resonant frequency of the crystal.

## Frequency stability of oscillator:

Frequency stability of an oscillator is a measure of its ability to maintain the required frequency as precisely as possible over as long a time possible.

The main drawback in transistor oscillator is the frequency of oscillation is not stable for a long time operation. The following are the factors that contribute to the change in frequency.

i) Due to the change in temperature, the values of the frequency determining components like resistors, inductors and capacitors will change.

ii) Due to fluctuations in power supply

iii) Due to change in climatic conditions and aging.

iv) Due to loading effects.

\* Loading effects can be minimized with the oscillator is connected to the load through an impedance matching circuit. The temperature effects may be minimized by using automatic temperature control mechanisms.

The frequency stability is defined as

$$S_\omega = \frac{d\theta}{d\omega}$$

where  $d\theta$  is the phase shift introduced for a small frequency change in the nominal frequency  $\omega_0$ .

The circuit having a larger value of  $\frac{d\theta}{d\omega}$  has more frequency stability.

Oscillators with large Q-factor are more stable.

Amongst all the available oscillators, crystal oscillators have highest frequency stability.




## Amplitude stability of oscillators:-

The amplitude of the oscillations may also drift due to temperature aging, supply fluctuations and loading effects. In case of RC oscillators, if there is any change in amplitude that can be stabilized by replacing the resistors in the bridge (feed back loop) RC network by transistors which are temperature dependent resistors.



Electrical Analogue Circuit

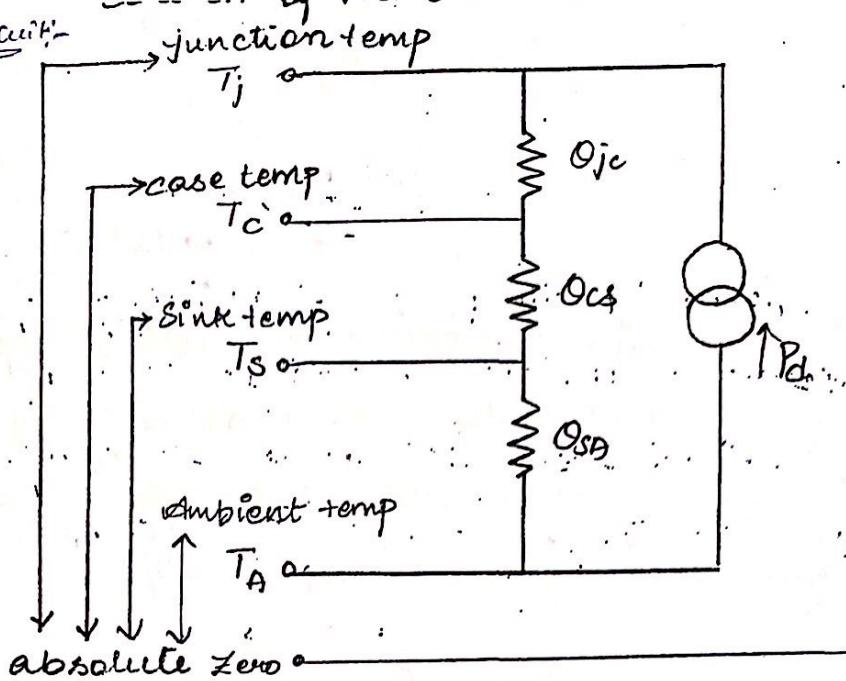

27/Q

Pb  
① Determine the junction, case & sink temperature for a power  $T^{\circ}\text{r}$  if it carries  $I_C = 1\text{Amp}$  with an average (dc) voltage of 10V. Assume  $\theta_{jc} = 5^\circ\text{C/W}$ ,  $\theta_{sa} = 4^\circ\text{C/W}$ ,  $\theta_{cs} = 1^\circ\text{C/W}$  the ambient temperature is  $T_A = 25^\circ\text{C}$

$$\text{So } I_C = 1\text{Amp}, V_{CE} = 10\text{V}, \theta_{jc} = 5^\circ\text{C/W}, \theta_{sa} = 4^\circ\text{C/W}$$

$$\theta_{cs} = 1^\circ\text{C/W}, T_A = 25^\circ\text{C}$$

$$\text{rise in temperature} \Rightarrow T_j - T_A = \theta_{ja} P_d$$

$$P_d = V_{CE} \cdot I_C$$

$$= 10\text{W}$$

$$T_s - T_A = P_d \cdot \theta_{sa}$$

$$T_s - 25 = 10(4)$$

$$T_s = 40 + 25$$

$$= 65^\circ\text{C}$$

$$T_c - T_s = \theta_{cs} P_d$$

$$T_c - 65 = 1 \times 10 \Rightarrow T_c = 75^\circ\text{C}$$

$$T_j - T_c = \theta_{jc} P_d$$

$$T_j - 75 = 5(10)$$

$$T_j = 50 + 75 = 125^\circ\text{C}$$

② Determine the power handling capacity of a 60W power transistor rated at  $25^\circ\text{C}$  if derating is required above  $25^\circ\text{C}$  at a case temperature of  $100^\circ\text{C}$ . The derating factor is  $0.2\text{W}/^\circ\text{C}$ .

$$T_0 = 25^\circ\text{C}$$

$$T_1 = 100^\circ\text{C}$$

$$P(T_0) = 60\text{W}$$

$$P(T_1) = ?$$

$$D = 0.25$$

$$P(T_1) = P(T_0) - (T_1 - T_0)(D)$$

$$P(T_1)_{\text{req}} = P(T_0) - (75)(0.25)$$

$$P(T_1) = 93.75$$

$$P(T_1) = 41.25\text{W}$$

③ A power transistor with a rated power 20W and maximum junction temp of  $150^\circ\text{C}$  is to be operated in air with an ambient temp of  $25^\circ\text{C}$ . calculate its thermal resistance b/w junction & case. for rated power handling capacity. If a heat sink is provided now with  $\theta_{SA} = 1^\circ\text{C}/\text{W}$  &  $\theta_{CS} = 2^\circ\text{C}/\text{W}$ . Determine power handling capacity of the transistor.

$$P_d = 20W \quad \theta_{SA} = 1^\circ C/W \quad | \text{ after producing heat sink.}$$

$$T_j = 150^\circ C \quad \theta_{CS} = 2^\circ C/W$$

$$T_A = 25^\circ C$$

$$\theta_{JC} = ?$$

If the case is ideal,  $T_c = T_A$ ,  $\therefore \theta_{JC} = \frac{T_j - T_c}{P_d}$

$$\theta_{JC} = \frac{T_j - T_A}{P_d} = 60.25^\circ C/W$$

$$P_d' = ?$$

$$\begin{aligned} \theta_{JA} &= \theta_{JC} + \theta_{SA} + \theta_{CS} \\ &= 60.25 + 3 \\ &= 90.25^\circ C/W \end{aligned}$$

$$T_j - T_A = \theta_{JA} P_d'$$

$$\frac{150 - 25}{90.25} = P_d'$$

$$\Rightarrow P_d' = 13.51W$$

④ State the heat sink selection criteria for a transistor operating with  $V_{CE} = 20V$ ,  $I_C = 1.5Amp$ . Given  $\theta_{JC} = 1^\circ C/W$  junction temp should not exceed  $85^\circ C$  while the ambient temp is  $25^\circ C$

So

$$V_{CE} = 20V$$

$$P_d = 30$$

$$I_C = 1.5A$$

$$\theta_{JC} = 1^\circ C/W$$

$$T_A = 25^\circ C$$

$$T_j < 85^\circ C$$

one of the specifications of heat sink is  $\theta_{CA} = \theta_{CS} + \theta_{SA}$ .

$$\Rightarrow Q_{CA} = \frac{85 - 25}{30} - 1$$

$$\Rightarrow Q_{CA} = 1^{\circ}\text{C}/\text{W}$$

$\therefore$  A sink with  $Q_{CA} = 1^{\circ}\text{C}/\text{W}$  should be selected.

(5) A series fed class A amplifier uses a supply of 40V. The AC i/p voltage results in a base current of 6mA peak. calculate (a) Q-point ( $\beta = 25$ )

(b) DC i/p power

(c) AC o/p power

(d) Efficiency


(e) Power dissipated

Sol

$$(I_B)_{max} = 6\text{mA}$$

$$V_{CC} = 40\text{V}$$

$$I_C = \beta I_B$$

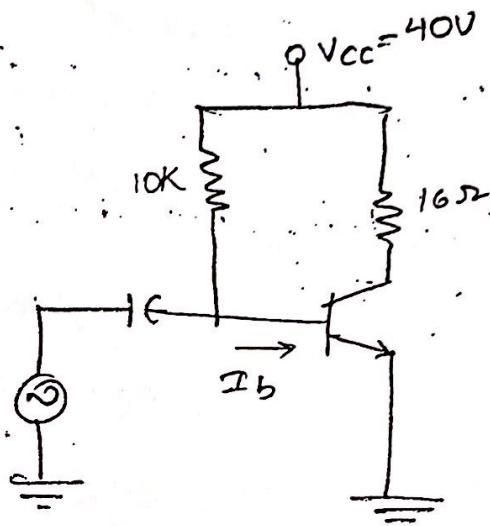

The DC equivalent ckt is


$$I_C = \beta I_B$$

$$V_{CC} = (10k)I_B + V_{BE}$$

$$I_B = \frac{V_{CE} - V_{BE}}{10k}$$

$$= \frac{40 - 0.7}{10k}$$

$$= 3.93 \text{ mA}$$

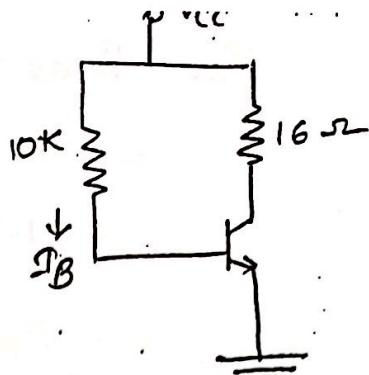

$$( \because V_{BE} = 0.7 \text{ V} )$$

class A amp

$$I_C = \beta I_B$$

$$= 25 \times 3.93 \text{ mA}$$

$$= 98.25 \text{ mA}$$

$$V_{CC} = I_C (16) + V_{CE}$$

$$V_{CE} = 40 - 98.25 \times 10 \times 16$$

$$V_{CE} = -1.572 \text{ V} + 40$$

$$\approx 38.428 \text{ V}$$

$$(a) Q \text{ point} = (V_{CE}, I_C) = (38.428, 98.25 \text{ mA})$$

$$(b) DC o/p power = V_{CC} \cdot I_C = 10 \times 98.25 \times 10^3$$

$$= 982.5 \text{ W}$$

$$(c) AC o/p power \Rightarrow P_{ac} = \frac{V_m I_m}{2} = \frac{1}{2} I_m^2 R_L$$

$$(I_C)_{max} = I_{max} = \beta (I_B)_{max}$$

$$= 25 \times 6 \text{ mA}$$

$$= 150 \text{ mA}$$

$$I_m = I_{max} - I_c$$

$$= 150 - 98.25$$

$$= 51.75 \text{ mA}$$

$$P_{ac} = \frac{1}{2} I_m^2 R_L = \frac{1}{2} (51.75 \times 10^{-3})^2 \times 16$$

$$= 0.0214 \text{ W}$$

(d) Efficiency =  $\frac{P_{ac}}{P_{dc}}$

$$= \frac{0.0214}{3.93} \times 100 = 5.44 \times 10^{-3} \times 100$$

$$= 0.54$$

(e) power dissipated =  $P_{dc} - P_{ac}$

$$= 3.93 - 0.0214$$

$$= 3.9 \text{ W}$$

\* \* \*  
 (b) A transistor amplifier with transformer coupled load produces harmonic amplitudes in the o/p as  $B_0 = 1.5 \text{ mA}$ ,  $B_1 = 120 \text{ mA}$ ,  $B_2 = 10 \text{ mA}$ ,  $B_3 = 4 \text{ mA}$ ,  $B_4 = 2 \text{ mA}$ ,  $B_5 = 1 \text{ mA}$ .

(c) Determine the % of total harmonic distortion.

(b) Assume an additional identical T/R is used to form a pushpull configuration. Use above amplitudes to find % distortion.

(a) Given  $B_0 = 1.5 \text{ mA}$ ,  $B_1 = 120 \text{ mA}$ ,  $B_2 = 10 \text{ mA}$ ,  $B_3 = 4 \text{ mA}$

$B_4 = 2 \text{ mA}$ ,  $B_5 = 1 \text{ mA}$

Total harmonic distortion

$$D = \sqrt{D_2^2 + D_3^2 + D_4^2 + D_5^2}$$

$$P_2 = \left| \frac{B_2}{B_1} \right| = \frac{10}{120} = 0.08$$

$$D_3 = \left| \frac{B_3}{B_1} \right| = 0.083$$

$$D_4 = \left| \frac{B_4}{B_1} \right| = \frac{2}{120} = 0.016$$

$$D_5 = \left| \frac{B_5}{B_1} \right| = 0.0083$$

$$D = \sqrt{D_2^2 + D_3^2 + D_4^2 + D_5^2}$$

$$D = \sqrt{(0.08)^2 + (0.083)^2 + (0.016)^2 + (0.0083)^2}$$

$$D = \sqrt{8.81744 \times 10^{-3}}$$

$$D = 0.0982$$

$$= 8.8\%$$

$$D = 91.2\%$$

c) In a pushpull configuration, even harmonics are cancelled. so we take only  $B_2 = B_4 = 0$

$$\Rightarrow D = \sqrt{D_3^2 + D_5^2}$$

$$= \sqrt{(0.083)^2 + (0.0083)^2}$$

$$\% D = 3.4\%$$

⑦ A sinusoidal signal with  $v_g = 1.75 \sin 600t$  is fed to a power amplifier. The resulting o/p current is  $I_o = 15 \sin 600t + 1.5 \sin 1200t + 0.5 \sin 2400t$ . calculate the % increase in power due to distortion.  $+1.2 \sin 1800t$

$$P = (1+D^2)P_1$$

$$P = \frac{1}{2} D^2 P_1$$

(d)

$$B_1 = 15$$

$$B_2 = 105$$

$$B_3 = 0.5 \times 10^2$$

$$B_4 = 0.5$$

$$D_2 = \left| \frac{B_2}{B_1} \right| = \frac{105}{15} = 0.1$$

$$D_3 = \left| \frac{B_3}{B_1} \right| = \frac{1.2}{15} = 0.08$$

$$D_4 = \left| \frac{B_4}{B_1} \right| = \frac{0.5}{15} = 0.03$$

$$D = \sqrt{D_2^2 + D_3^2 + D_4^2}$$

$$= \sqrt{(0.1)^2 + (0.08)^2 + (0.03)^2}$$

$$= \sqrt{0.4 \times 10^{-3}}$$

$$= 0.13$$

Excess power due to distortion

$$= \frac{P - P_1}{P_1} \times 100$$

$$= D^2 \times 100$$

$$= 1.45$$

Q) class B pushpull amplifier supplies power to a resistive load of  $12\Omega$ . The O/p T/F has a turns ratio of 8:1 & efficiency of 78.5%. Obtain (i) Max. power o/p  
(ii) Max. power dissipation in each transistor.

(iii) Max. base & collector current for each transistor.

Assume  $\beta_{FE} = 25$ ,  $V_{CC} = 20V$

so:  $R_L = 12\Omega$   
 $1:n = 8:1$   
 $\eta = 78.5\%$

(i)  $(P_C)_{max} = \frac{V_{CC}}{2R_L}$

$$R_L' = \frac{R_L}{n^2} = \frac{12}{8^2} = 12 \times 9 = 108$$

$$(P_C)_{max} = \frac{400}{2(108)} = 1.85W$$

(ii)  $P_C = P_i - P$

$$= \frac{2V_{CC}I_m}{\pi} - \frac{V_m I_m}{2}$$

$$= 2V_{CC}$$

$$(P_C)_{max} = \frac{2V_{CC}^2}{\pi^2 R_L'} = \frac{2 \times 400}{\pi^2 \times 108} = 0.75W$$

power dissipated

$$\text{by each } T/R = \frac{(P_C)_{max}}{2}$$

$$= 0.75/2$$

$$= 0.375$$

(iii)  $P_i = V_{CC} \cdot \frac{2I_m}{\pi} = 2.6$

$$I_m = \frac{P_i \cdot \pi}{2V_{CC}} = 0.204 \text{ Amp}$$

$$(P_C)_{max} = \frac{V_m I_m}{2} = \frac{V_{CC} I_m}{2} = 1.85W$$

$$\Rightarrow I_m = 0.185 \text{ Amp}$$

$$(P_c)_{\max} = \beta (I_B)_{\max}$$

$$(I_B)_{\max} = \frac{(P_c)_{\max}}{\beta}$$

$$= \frac{0.185}{25}$$

$$= 7.4 \text{ mA}$$

- ⑨ A silicon T/R operates as an ideal class B amplifier if DC current drawn from the supply is 25mA. calculate the AC power delivered to load for a load resistance of  $2k\Omega$ .

Sol

$$I_{DC} = 25 \text{ mA}$$

$$R_L = 2 \text{ k}\Omega$$

$$P_{AC} = ?$$

$$P_{AC} = V_{RMS} \cdot I_{RMS}$$

$$= (I_{RMS})^2 \cdot R_L$$

$$\left[ \because I_{RMS} = \frac{I_m}{2} \right]$$

$$= \left( \frac{I_m}{2} \right)^2 R_L$$

Half sinusoidal.

$$= k_4 I_m^2 R_L$$

$$I_{DC} = \frac{I_m}{\pi} \Rightarrow I_m = I_{DC} \times \pi$$

$$= 25 \text{ mA} \times \pi$$

$$= 78.5 \text{ mA}$$

$$P_{AC} = k_4 (78.5)^2 \times 2 \times 10^3$$

$$= 3.08 \text{ W}$$

$$V_{CC}^2 = 80 \times 32$$

$$\therefore V_{CC}^2 = 10240 \text{ Volts}$$

$$V_{CC} = 100 \text{ Volts}$$

$$V_{CC} = 50.59 \text{ Volts}$$

1/3/13

- ① A dynamic curve of a transistor amplifier is represented by  $i_C = G_1 i_b + G_2 i_b^2$ . The i/p signal to the transistor is  $I_1 \cos \omega_1 t + I_2 \cos \omega_2 t$  show that the output will contain a DC term sinusoidal signals with frequencies  $\omega_1, \omega_2, 2\omega_1, 2\omega_2, \omega_1 + \omega_2, \omega_1 - \omega_2$ .

Given,

$$i_C = G_1 i_b + G_2 i_b^2$$

The input current,  $i_b = I_1 \cos \omega_1 t + I_2 \cos \omega_2 t$

$$i_C = G_1 (I_1 \cos \omega_1 t + I_2 \cos \omega_2 t) + G_2 (I_1 \cos \omega_1 t +$$

$$I_2 \cos \omega_2 t)^2$$

$$i_C = G_1 I_1 \cos \omega_1 t + G_2 I_2 \cos \omega_2 t + G_2 I_1^2 \cos^2 \omega_1 t + G_2 I_1 I_2 \frac{\cos \omega_1}{\cos \omega_2} \cos \omega_2 t + G_2 I_2^2 \cos^2 \omega_2 t$$

$$i_c = \frac{G_2 I_1^2}{2} G_1 I_1 \cos \omega_1 t + G_1 I_2 \cos \omega_2 t + G_2 I_1^2 \left( \frac{1 + \cos 2\omega_1 t}{2} \right) + G_2 I_2 \left[ \cos(\omega_1 + \omega_2)t + \cos(\omega_1 - \omega_2)t \right]$$

$$i_c = \frac{G_2 I_1^2}{2} + \frac{G_2 I_2^2}{2} + G_1 I_1 \cos \omega_1 t + G_1 I_2 \cos \omega_2 t + G_2 I_1^2 \cos \frac{2\omega_1 t}{2} + G_2 I_2^2 \cos 2\omega_2 t + G_2 I_1 I_2 \left[ \cos(\omega_1 + \omega_2)t + \cos(\omega_1 - \omega_2)t \right]$$

$\therefore$  the O/p contains a DC term and sinusoidal signals with frequencies  $\omega_1, \omega_2, 2\omega_1, 2\omega_2, \omega_1 + \omega_2, \omega_1 - \omega_2$

- ⑫ The dynamic transfer curve for a given transistor is  $i_c^o$  (in mA) =  $50i_b^o + 1000i_b^{o^2}$  where,  $i_b^o = 10 \cos 2\pi(100t)$  mA. calculate the % of harmonic distortion.

sg Given

$$i_c^o (\text{in mA}) = 50i_b^o + 1000i_b^{o^2} \quad \textcircled{1}$$

$$i_b^o = 10 \cos 2\pi(100t) \text{ mA}$$

$$i_c^o = G_1 i_b^o + G_2 i_b^{o^2} \quad \textcircled{2}$$

comparing ① & ②

$$G_1 = 50, G_2 = 1000$$

$$\Rightarrow i_b^o = P_{Bm} \cos \omega_0 t$$

$$\Rightarrow i_c^o = G_1 P_{Bm} \cos \omega_0 t + G_2 P_{Bm}^2 \cos^2 \omega_0 t$$

$$\Rightarrow i_c^o = G_1 P_{Bm} \cos \omega_0 t + G_2 P_{Bm}^2 \left( \frac{1 + \cos 2\omega_0 t}{2} \right)$$

$$\Rightarrow i_c^o = G_1 P_{Bm} \cos \omega_0 t + \frac{G_2 P_{Bm}^2}{2} + \frac{G_2 P_{Bm}^2}{2} \cos 2\omega_0 t$$

$$B_0 = \frac{G_2 I_{BM}}{2} = \frac{1000 \text{ mA} \times (10 \text{ mA})}{2} = 0.05 \times 10^{-3}$$

$$B_1 = G_1 I_{BM} = 5 \text{ mA} \times 10 \text{ mA} \\ = 500 \times 10^{-6} = 0.5 \times 10^{-3}$$

$$B_2 = \frac{G_2 I_{BM}^2}{2} = 0.05 \times 10^{-3}$$

$$D_2 = \left| \frac{B_2}{B_1} \right| = 0.1$$

$$\Rightarrow \% D_2 = 10\%$$

(13) A silicon power transistor, operated with a heat sink having thermal resistance  $\theta_{JS} = 1.5^\circ\text{C}/\text{W}$ ,  $\theta_{JC} = 0.5^\circ\text{C}/\text{W}$ ,  $\theta_{CS} = 1.5^\circ\text{C}/\text{W}$ . The transistor has to dissipate 150 W of power at 25°C. Determine the dissipated power at 200°C.

so Given,  $\theta_{JC} = 0.5^\circ\text{C}/\text{W}$

$$\theta_{CS} = 1.5^\circ\text{C}/\text{W}$$

$$\theta_{SA} = 1.5^\circ\text{C}/\text{W}$$

$$\theta_{JA} = 0.5 + 1.5 + 1.5 = 3.5^\circ\text{C}/\text{W}$$

$$T_J = 200, T_A = 25$$

$$T_J - T_A = \theta_{JA} \cdot P_d$$

$$P_d = \frac{200 - 25}{3.5} = 50 \text{ W}$$

(14) calculate the second harmonic distortion of the o/p signal w/f of a pushpull amplifier has measured values of  $V_{CE(\min)} = 1\text{V}$ ,  $V_{CE(\max)} = 24\text{V}$  &  $V_{CEQ} = 14\text{V}$

so Given  $V_{CE(\min)} = 1\text{V}$

$$V_{CE(\max)} = 24\text{V}$$