

## Unit-1

### Power Semiconductor Devices

Power:-


The power stages are Generation, Transmission, Distribution.

Electronics:-

Solid state devices, Signal processing.

Control:-

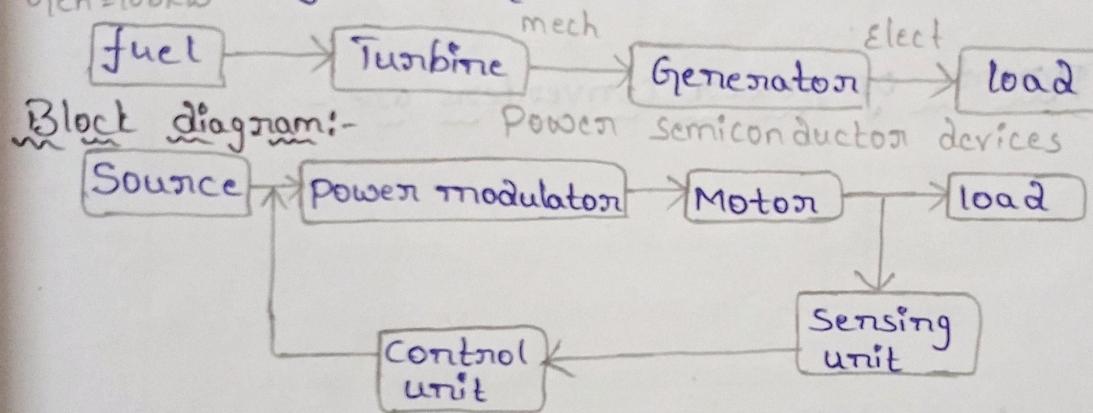- Power Gen=lookw (i) Steady state characteristics  
(ii) Dynamic characteristics.



Source:- It may be Ac or Dc.

power modulator:- It is also known as power converter which is used for Converting the source voltage to the required voltage of the motor i.e, Ac to Dc (or) Dc to Ac.

Motor:- The motor may be DC motor, induction motor, Synchronous motor, Ac series motor etc..

Sensing unit:- It senses the output of motor i.e, Speed, torque etc..

Control unit:- The control unit receives the feedback from the sensing and gives signals to the power modulator using the feedback obtained.

Load:- The load may be resistive and capacitive load.

Symbol

Types of power converters:-

- (1) AC to DC converter - Rectifier.
- (2) DC to AC converter - Inverter.
- (3) DC to DC converter - chopper.
- (4) AC to AC converter - cyclo converter.
- (5) AC regulator - [fixed frequency].

The main components of power converters are:-

- (i) SCR
- (ii) MOSFET
- (iii) IGBT

\* MOSFET:-

It is a three terminal device which is used in high power applications the 3 terminals are

\* Drain  
\* Source  
\* Gate


These are mainly classified into 2 types.

- a.) Enhancement type MOSFET
- b.) Depletion type MOSFET.


These MOSFET are again classified into

- \* N-channel MOSFET
- \* P-channel MOSFET.

Symbol of Mosfet:-

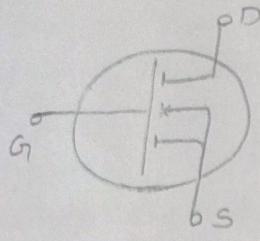


n-channel

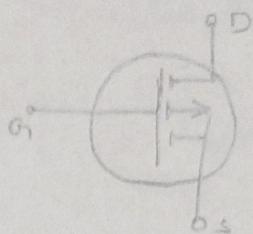

p-channel.


\* Metal oxide silicon field effect transistor (MOSFET)

Structure of Mosfet:- (construction)

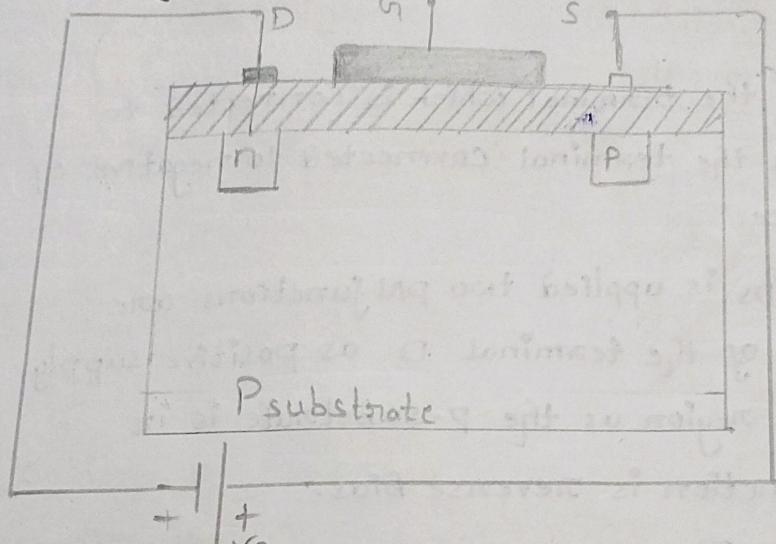


- (1) A p-type semiconductor is taken and this behaves as base for the mosfet and it is called as a substrate.
- (2) Two regions on the same side of the substrate are heavily doped with a n-type impurity as shown.
- (3) The Drain and source terminals are taken from this impurity.
- (4) Now, the entire top layer of the substrate is coated with silicon dioxide ( $\text{SiO}_2$ ) as shown. and this behaves as an insulation between the gate and substrate.
- (5) On this layer a metallic plate is placed and the gate terminal is taken from this metallic plate.
- (6) Hence, the gate is insulated from the substrate and source and drain are directly connected as shown.

### Operation of Mosfet:-

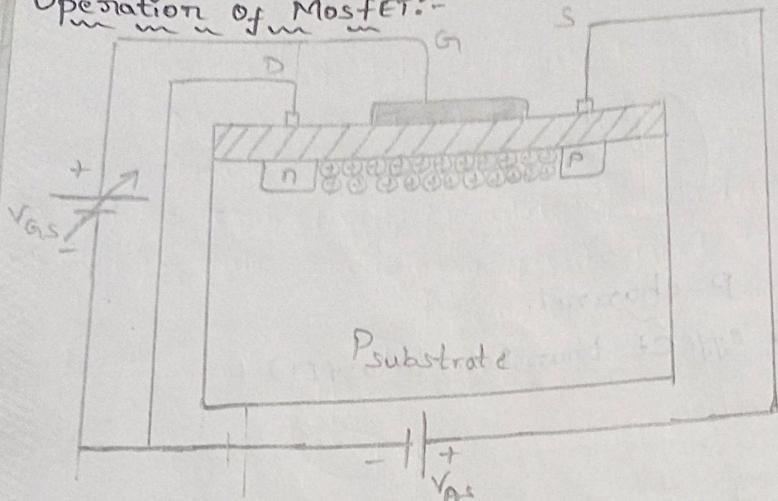

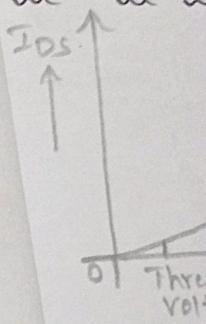the conductivity  
Due to the elec  
because between  
) If the gate ve  
the Mosfet Co  
) When the ga  
the Mosfet i  
ntrolled devi  
characteristics  
) Transfer cha



- (1) The voltage  $V_{DS}$  is applied to the terminal which is connected to positive is called drain and the terminal connected to negative of  $V_{DS}$  is called as a source.
- (2) As soon as the voltage  $V_{DS}$  is applied two p-n junctions are formed in the substrate of the terminal D as positive supply is given to the n-type region as the P-substrate is in high polarity here, the junction is reverse bias.
- (3) As the negative supply is given to the source terminal to the n-type region here the junction is forward bias.
- (4) Hence, there is no significant current flows from drain to source.
- (5) Only the minimum leakage current flows due to the minority charge carriers.
- (6) Now, the voltage is applied to the gate terminal i.e  $V_{GS}$  as the minority carriers attracted to the gate terminal and forms as a channel as shown in figure.
- (7) This channel is known as n-channel and the MOSFET is called the N-channel Mosfet.
- (8) As the gate voltage is increase number of free electrons accumulated nearer the plate gets increased. Hence,

the conductivity of the MosfET depends upon the gate voltage.


(i) Due to the Electrostatic attraction the conduction takes place between Drain and source.

(ii) If the gate voltage is greater than the threshold voltage value the MosfET comes to on state.

(iii) When the gate voltage is less than the threshold voltage value the MosfET is in off state. Hence, these device is called voltage controlled device.


### Characteristics of MosfET:-

#### (i) Transfer characteristics:-

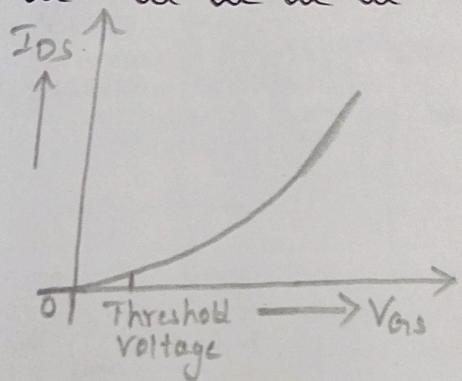
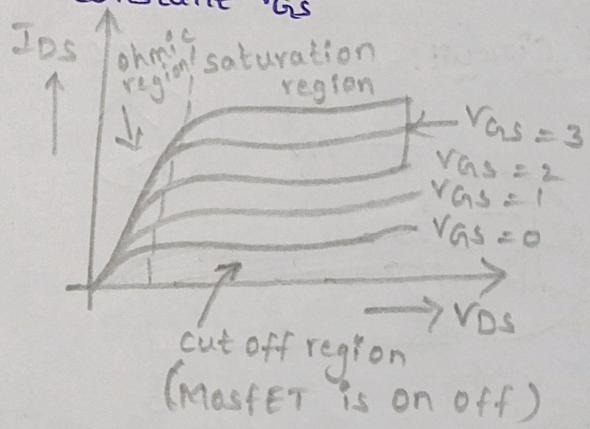
#### (ii) Output characteristics:-

drawn between  $V_{DS}$  &  $I_{DS}$  at constant  $V_{GS}$



### Applications of MosfET:-

(1) High frequency Inverters.

(2) In SMPS, Motor control applications

(3) Industrial process control.

IGBT:-


Insulated gate bi-polar Transistor

MOSIGBT - Metal Oxide Insulated gate transistor


IGT - Insulated gate Transistor

COMFET - Conductivity Modulated field effect transistor

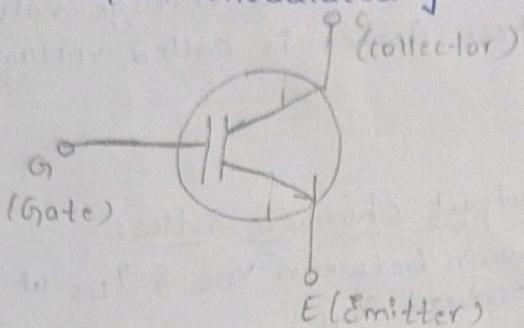GEMFET - Gain modulated field effect transistor.




Equivalent circuit:-

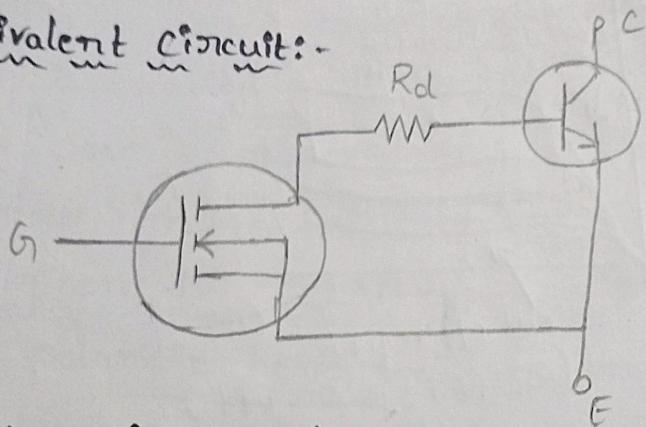


Structure (or) Construction of IGBT:

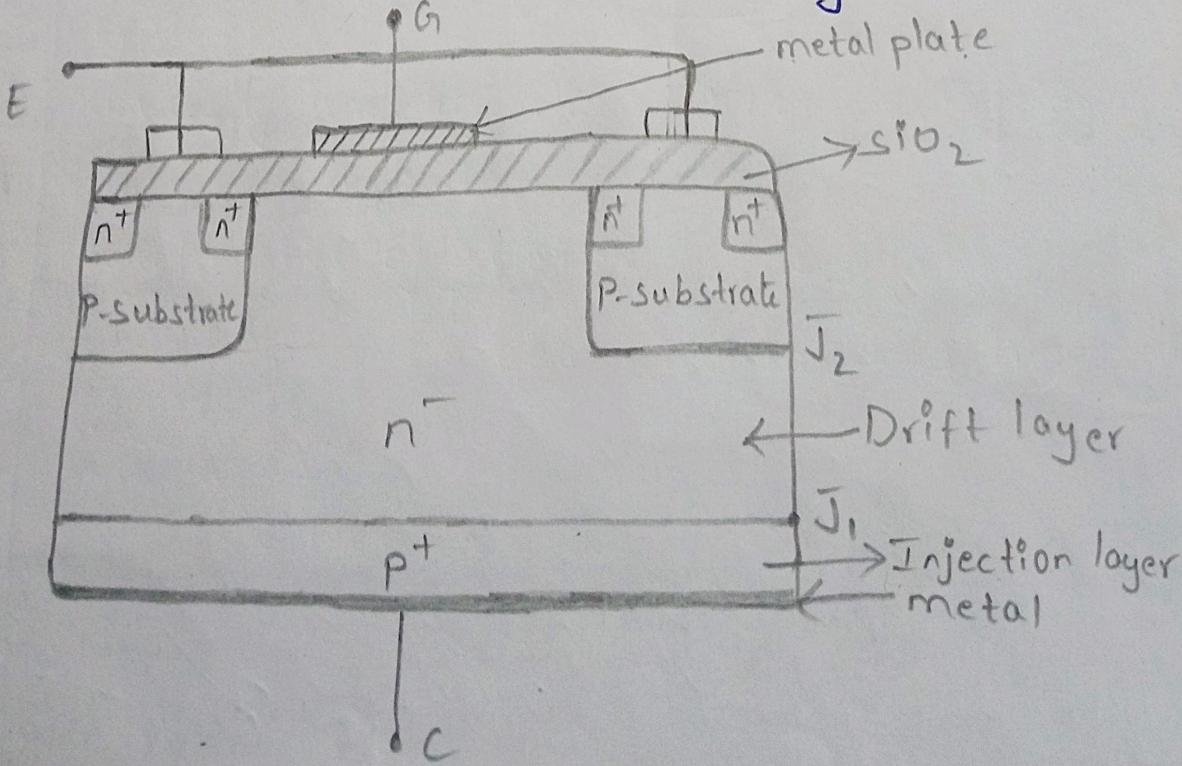- (1) It is a combination of Mosfet and BJT and it is a four layer three terminal device. It has two junctions.



- 2) The first layer is p-layer is also known as injection layer as a carriers are injected from this layer.
- 3) The second layer is drift layer it determines the break down voltage in this layer.
- 4) Next layer is similar to MOSFET where the p-substrate and n-type material is doped as shown in figure.
- 5) The silicon dioxide is Coated on the top layer and a metal plate is placed from this metal plate the gate terminal (G) is taken.
- 6) Collector terminal is taken from first layer i.e p layer and Emitter terminal is taken from the third layer which is like a MosfET.


### Operation (or) Working of IGBT:-

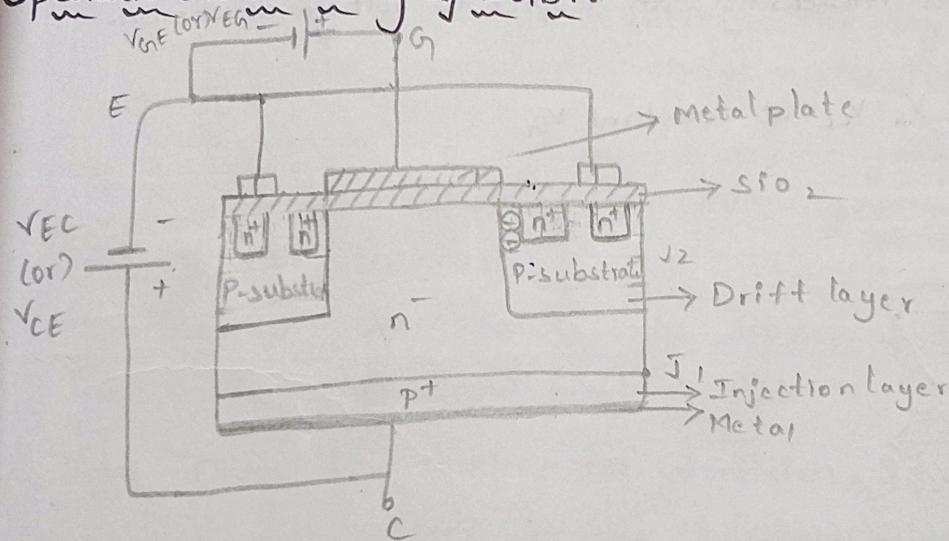

- (1) The supply voltage  $V_{cc}$  is applied between emitter and collector and gate voltage is "0" volts. At this condition junction  $J_1$  is forward bias and junction  $J_2$  is reverse bias. Hence only a leakage current due to minority charge carriers it flow through the IGBT.
- (2) When the voltage  $V_G$  is applied along with  $V_{cc}$  then a capacitance effect is forward at the gate terminal. hence all the minority charge carriers gets attracted towards the gate as shown.
- (3) Hence the conduction path is created from collector to emitter as shown. Hence the IGBT comes to ON state. So, the current  $I_c$  flows in the circuit.

Characteristics of IGBT:-


Transfer characteristics

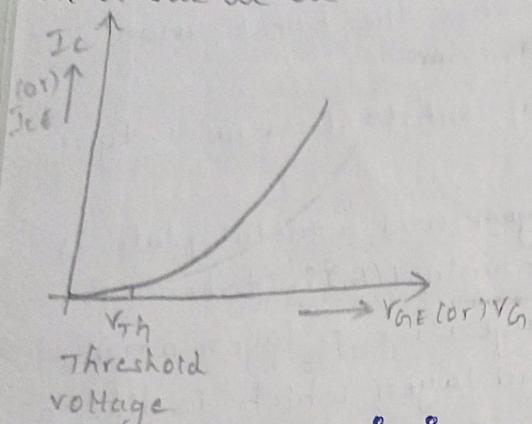

As, the gate voltage is increased from zero After the threshold value the current  $I_c$  starts increasing with respect to voltage as shown.

Output characteristics:-

$I_c$  Vs  $V_{cc}$  at constant  $V_G$

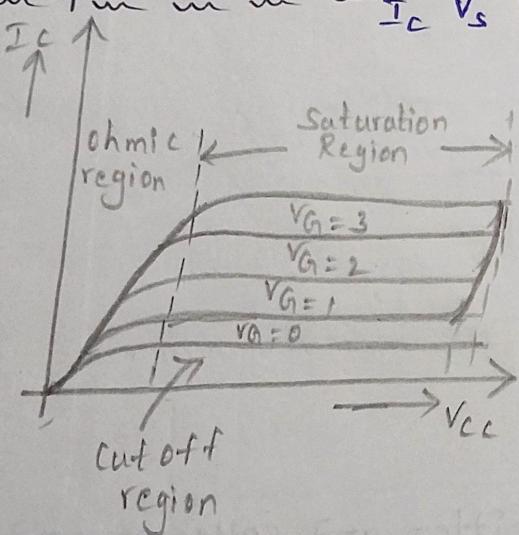


Applications of IGBT:-

Switching devices of inverters, Air conditioners, Refrigerators and Industrial motor application.

Switching characteristics of IGBT:-

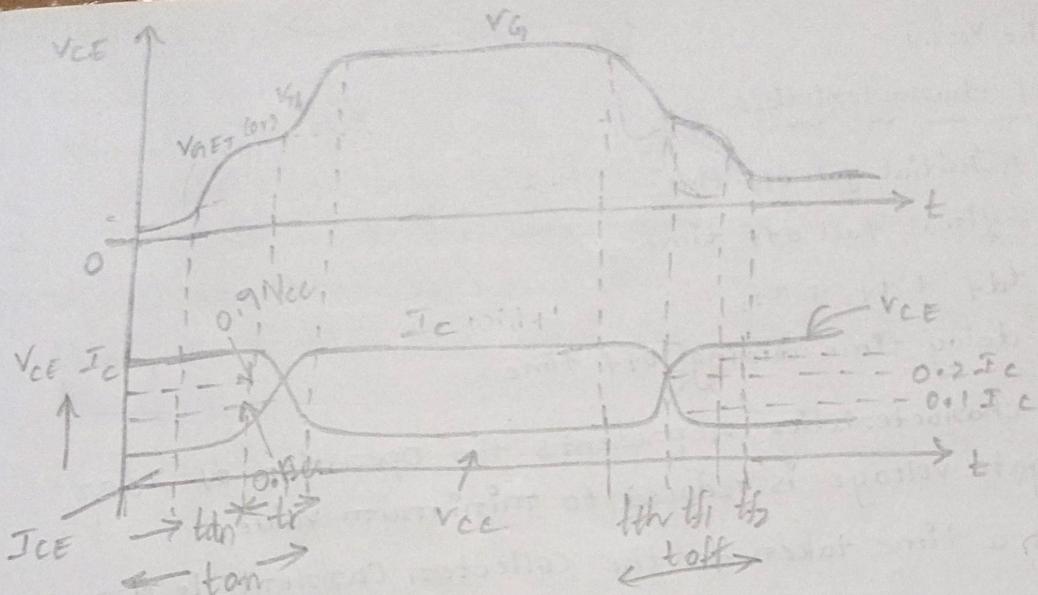\* It contains turn "on" characteristics and turn "off" characteristics



Generally during turn ON - current moves from 0 to  $\infty$   
voltage moves from 0 to  $\infty$ .

During Turn off - Current moves from  $\infty$  to 0  
Voltage moves from  $\infty$  to 0

#### Turn ON characteristics:-

- \* The turn ON characteristics represents operation of IGBT from forward blocking state to conduction state.
- \*  $t_{ON}$  - Delay time during ON condition, It is defined as when the gate voltage reaches the threshold value from minimum value it is also defined as the time taken for the collector voltage ( $V_{CE}$ ) drops from  $V_{CE}$  to  $0.9 V_{CE}$
- \* It is also defined as the time taken for the collector current to raise from  $I_{CE}$  to  $0.1 I_c$

#### Turn off characteristics:-

- \* raise time  $t_r$  it is defined as time taken for the collector voltage fall from  $0.9 V_{CE}$  to  $0.1 V_{CE}$ .
- \* And it is also defined as the rise of collector current from  $0.1 I_{CE}$  to  $I_c$  (maximum value)

- \* finally the voltage drops to very small value called as conduction

drop, i.e  $V_{CEs}$ .

\* Turn off characteristics:-

$t_{f1}$  = Initial fall off time

$t_{f2}$  = final fall off time

$t_{off} = t_{df} + t_{f1} + t_{f2}$

$t_{doff}$  = delay time during off time

Turn off characteristics represents the operation of IGBT when the gate voltage is reduced to minimum value.


$t_{df}$  - It is a time taken for the collector current to drop from  $I_c$  to  $0.9 I_c$

$t_{f1}$  - It is the time taken to drop off collector current from  $0.9 I_c$  to  $0.2 I_c$

$t_{f2}$  - It is the time taken for the collector current to reach  $0.1 I_c$  from  $0.2 I_c$ .

Here, the voltage raises to  $V_{CE}$  value.

\* Switching characteristics of MOSFET:-

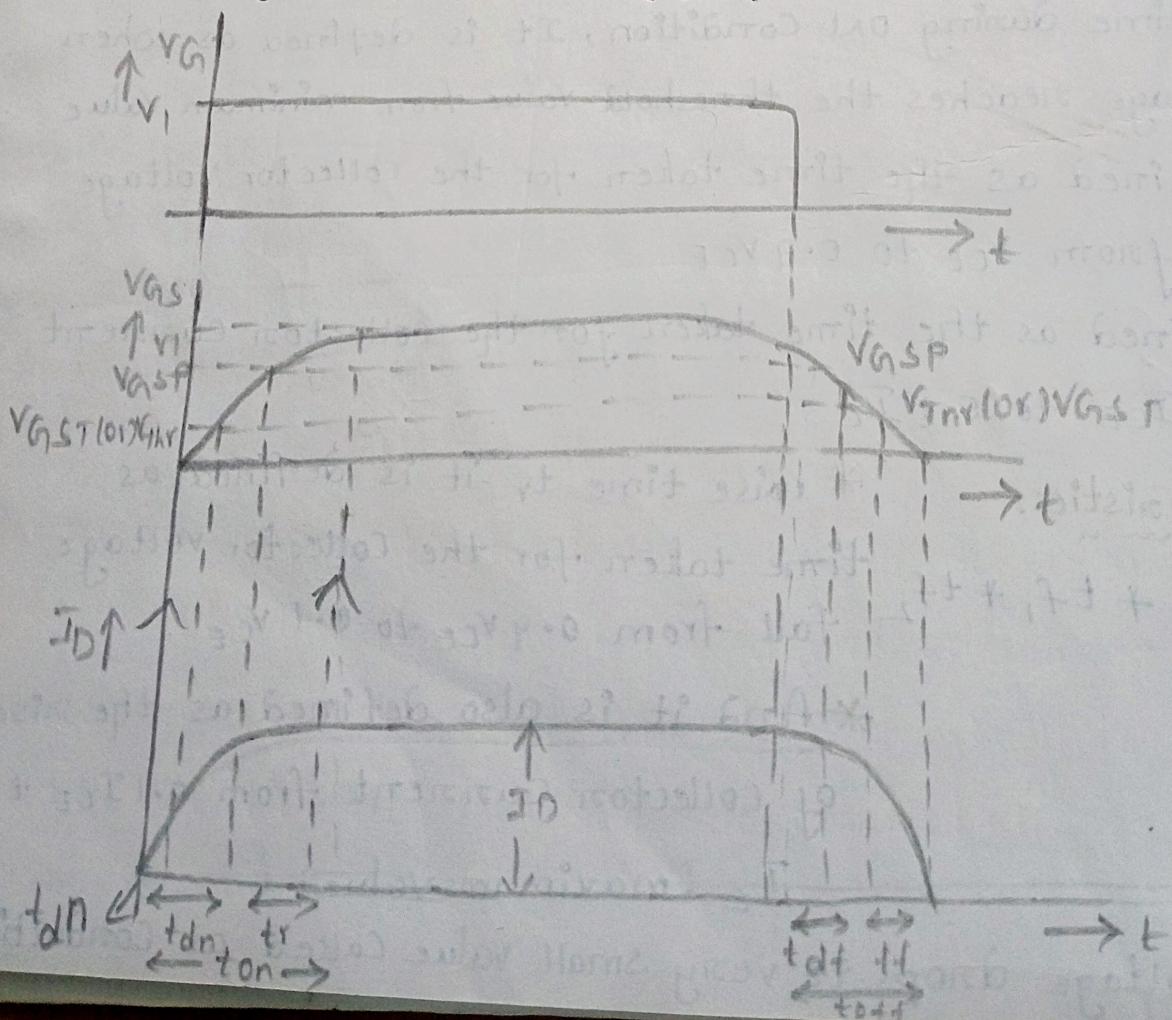

### Turn On characteristics:-

$$t_{on} = t_{dn} + t_r$$

Where,

$t_{dn}$  is the delay time during ON state.

- \* It is defined as the time taken for the rise of voltage from 0 to threshold voltage
- \* During this period no current flows in the MOSFET it is represented as  $I_{DN}$
- \*  $t_r$  is the time taken for the voltage to reach its maximum value i.e  $V_{GSP}$  (full gate source voltage)
- \* It is also defined as time taken to raise current from 0 to Maximum value  $I_D$ .

### Turn Off characteristics:-

$$t_{off} = t_{df} + t_f$$


- \*  $t_{df}$  - Delay time during OFF state

\* It is the time taken for the gate voltage to start decreasing when the gate pulse is removed.

- \*  $t_f$  is the fall time

It is the time taken for the voltage to reduce from  $V_{GSP}$  to  $V_{thr}$ . Hence, the current also starts reducing to 0 i.e  $I_D = 0$ .

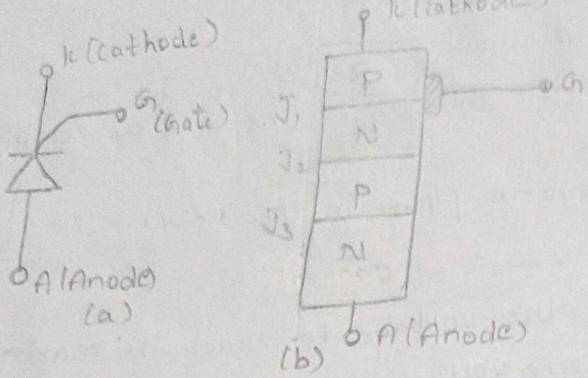\* SCR:-  
(silicon Controlled Rectifier) (or) Thyristor



forward con  
As, the  
depletion l  
x stage (hence the  
and this  
known as  
conducting  
Reverse


\* It is a four layer three terminal 3 junction device.

It operates in 3 modes they are.

- \* forward blocking mode
- \* forward conduction mode
- \* Reverse blocking mode.

forward blocking mode:

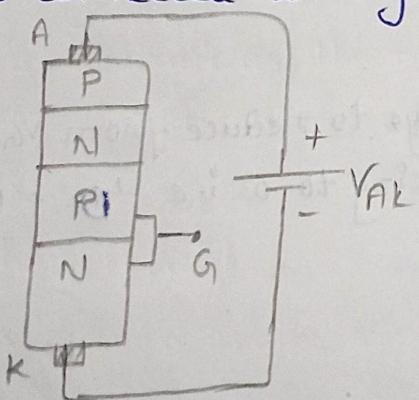In this mode anode is given positive supply and Cathode is connected to Negative Supply as shown




In this mode junction  $J_1$ ,  $J_3$  are forward bias and the junction  $J_2$  is reverse bias. Because of formation of depletion layer at the junction  $J_2$  it does not allow the flow of electrons through the device only a small leakage current flows through the circuit. This current is not sufficient the device to conduct. Hence this mode is called forward blocking mode.

\* forward conduction mode:- voltage

As, the Anode to Cathode current increases the width of the depletion layer gets reduced. If the voltage is continuously increased a stage comes where the depletion layer vanishes at junction  $J_2$ . Hence the reverse bias junction  $J_2$  breaks down at this stage and this is known as Avalanche breakdown and this mode is known as forward conduction and hence the device starts conducting.

\* Reverse blocking mode:-

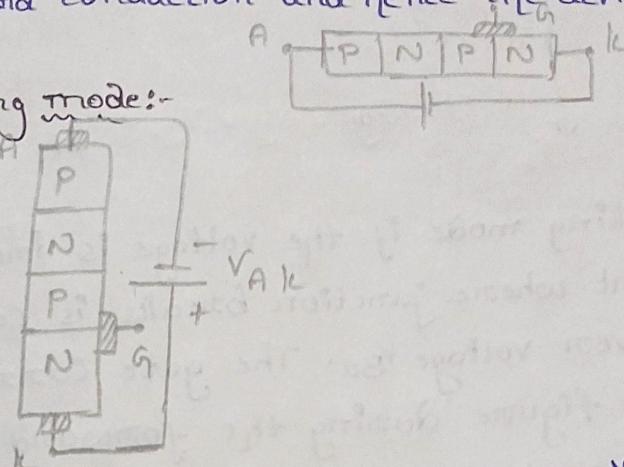

In this mode the anode is connected to negative supply and Cathode is connected to positive supply. Hence, the junction  $J_2$  is only forward bias and the junctions  $J_1$  &  $J_3$  are reverse bias. Because of this only a small amount of leakage current flows through the circuit. Hence, the device will not conduct. Hence, this mode is called reverse blocking mode.

Characteristics of SCR:-


There are two types of characteristics

They are

- \* static characteristics
- \* Dynamic characteristics

\* Static characteristics (or) VI :-

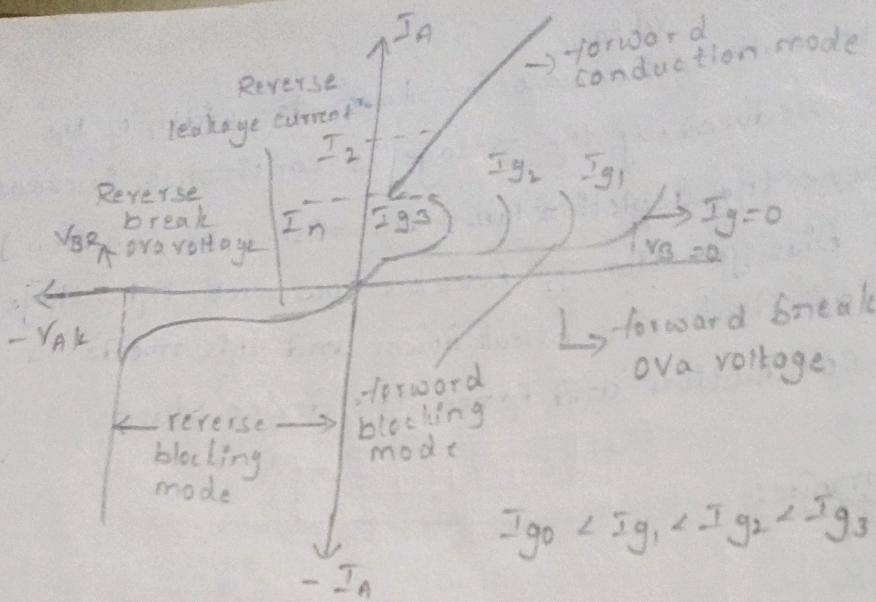In reverse blocking mode if the reverse voltage is increased continuously the point where the junction breaks is called reverse break over voltage  $V_{BR}$ . And the current starts flowing in the reverse direction as shown.



In forward blocking mode if the voltage is increased continuously the point where junction breaks is called forward break over voltage  $V_{BO}$ . The gate current is applied as shown in figure during the forward conduction mode. Hence the current starts flowing in forward direction as shown.


$I_H$  - Holding Current

It is defined as the minimum value of the current flowing through the anode below which the thyristor can not be turned ON.

$I_L$  - latching Current.

It is defined as the minimum current at which the thyristor is maintained at ON state even if the gate pulse is removed.

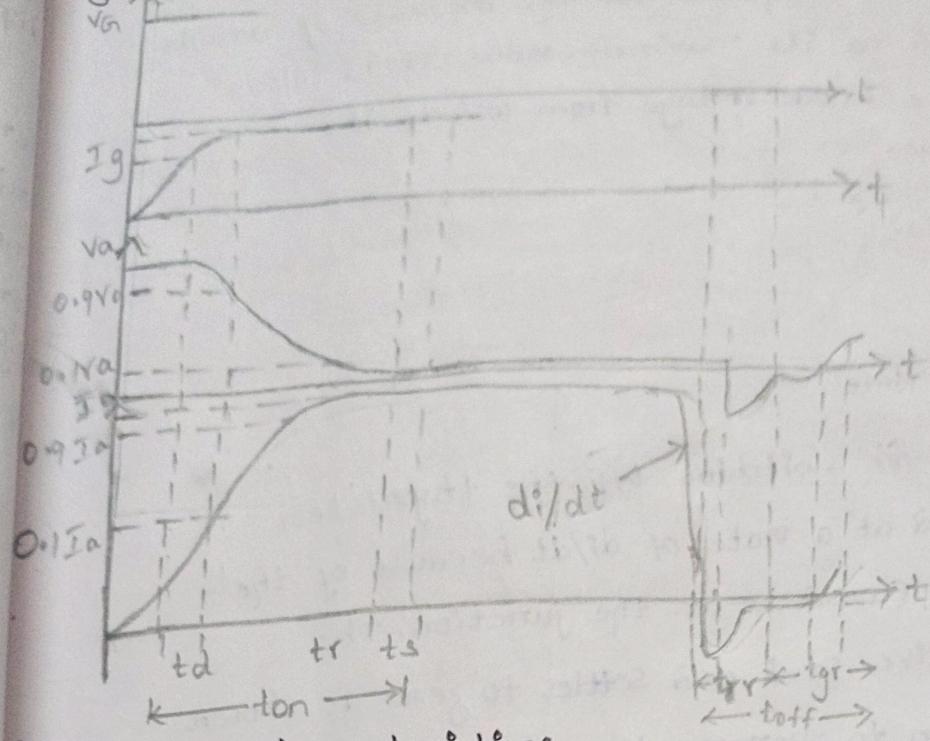Dynamic (or) switching characteristics of SCR:-



\* Turn ON characteristics:-

$$t_{ON} = t_d + t_r + t_s$$

$t_d \rightarrow$  delay time.  $t_s \rightarrow$  settling time.

$t_r \rightarrow$  rise time

delay time:-

It is the time taken by the gate current to reach its maximum value from 90% as shown in figure.

\* It is also defined as the time taken by the anode current to reach 10% as shown

\* It is also defined as the anode voltage to decrease 90% from its maximum value

\* Rise time  $t_r$

It is defined as the time required for the anode voltage to decrease to 10% of  $V_a$  as shown

It is also defined as time taken for the increased of anode current from 10% to 90% of its value.

$t_s$  (spelled on settling time):-

\* It is the time required for the increase of anode current from 90% to its maximum value. It is also defined as to reduce anode voltage from 10% to its minimum leakage value.

Turn off characteristics:-

$$T_{off} = t_{rr} + t_{gr}$$

$t_{rr}$  = Reverse Recovery time.

During this time for switching off the thyristor the current is reduced at a rate of  $dI/dt$  because of the presence of the charge carriers at the junction. The current goes to its negative peak and settles to zero as shown.

$t_{rr}$  is the time taken to remove the charge carriers at junction  $J_1 \& J_3$ . At this period the voltage spike is also occurs in negative direction as shown in figure.

$t_{gr}$  = Gate recovery time.

It is the time taken to remove the charge carriers at the junction  $J_2$ . Hence the thyristor comes to complete off state.


$t_c$  - circuit turn off time.

It is the total time of  $t_{rr}$  and  $t_{gr}$ .

\* SCR triggering Methods :-  
Turn on (or) offing


- (1) forward voltage triggering
- (2) Gate triggering
- (3) dv/dt triggering
- (4) Temperature triggering
- (5) light triggering.

\* forward voltage triggering:-

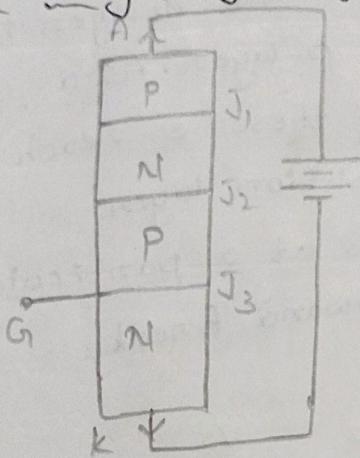


In this method anode is connected to positive terminal and Cathode is connected to negative terminal. Hence the junction J<sub>1</sub> & J<sub>3</sub> are forward bias. And a depletion layer is formed at junction J<sub>2</sub>. As the voltage is increased the width of the depletion layer reduces and it break down at some point which is called as Avalanche breakdown. Hence the junction J<sub>2</sub> allows the movement of electrons along the function. Hence the SCR comes to ON state.

Gate triggering:-

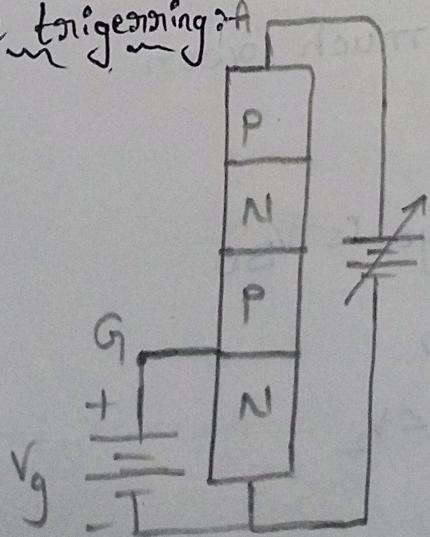

Turning on of SCR by gate triggering is simple, reliable and efficient. Thyristor with a  $V_{BO}$  (800V) higher than the nominal working voltage (400V) is chosen. This means SCR remains in off-state with normal working voltages with ( $R_g = 0$ ). When even +ve gate voltage applied AP w.r.t. cathode, the p-layer is flooded with  $e^-$  from the cathode. This is because cathode n-layer is heavily doped as compared to gate p-layer. As a thyristor is forward biased, some of these  $e^-$  reach junction  $J_2$ , as a result width of depletion layer decreases and breakdown occurs at a particular voltage which is lesser than the forward break over voltage ( $V_{BO}$ ).

Over voltage ( $V_{BO}$ )

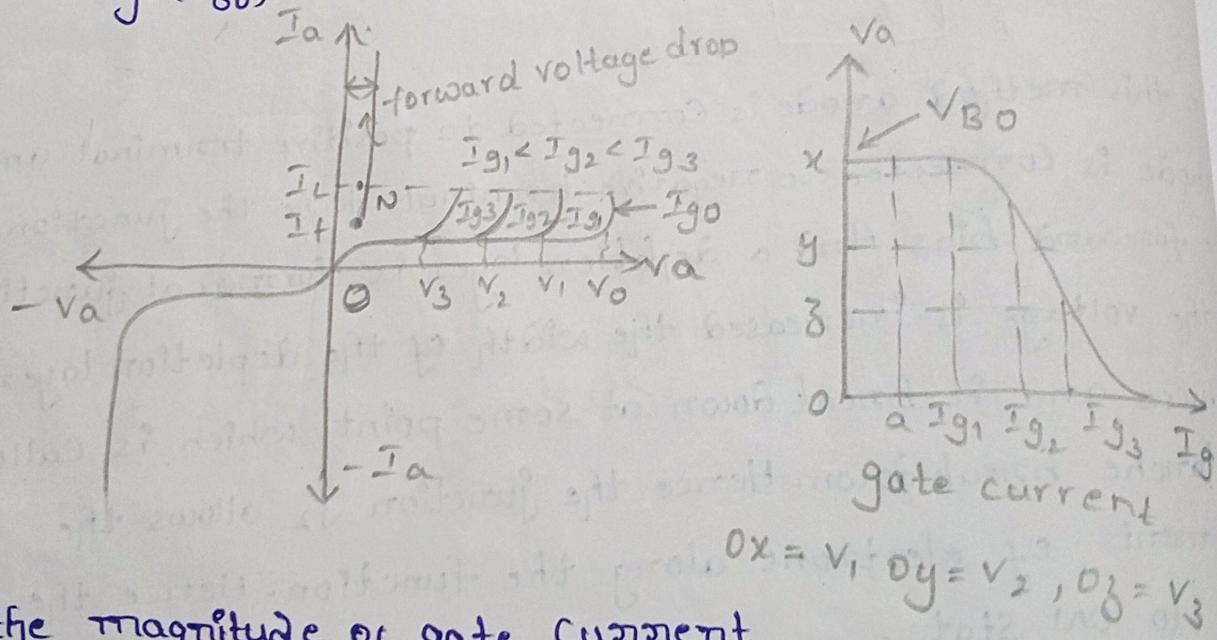

If the magnitude of gate current increases then the SCR gets turned on much lower forward voltage.

At  $I_g = 0$  forward breakover voltage is  $V_{BO}$

If at  $I_{g1}$  turn on voltage is  $V_1$  &  $V_1 < V_{BO}$

at  $I_{g2} \Rightarrow V_2$  &  $V_2 < V_1$  at  $I_{g3} \Rightarrow V_3$  &  $V_3 < V_2$

(Typical values of  $I_g$  (20-200) mA.

$\therefore I_{g3} > I_{g2} > I_{g1} > I_{go}$  then  $v_3 < v_2 < v_1 < V_{BO}$ .

This is also shown in fig.

\*  $\frac{dv}{dt}$  triggering:-

With forward voltage across A-K of SCR, the two layers  $J_1, J_3$  are forward biased &  $J_2$  is reverse biased. This reverse biased junction  $J_2$  has the characteristics of a capacitor due to space charge region (Depletion layer) at junction  $J_2$ .

If the forward voltage is suddenly applied, a charging current through junction capacitance  $C_J$  may turn ON SCR. Almost the entire voltage suddenly applied at A-K appears at junction  $J_2$  the charging current is  $i_C$  given by

$$i_C = \frac{dq}{dt} = \frac{d}{dt}(C_J V_A)$$

$$= C_J \frac{dV_A}{dt} + V_A \frac{dC_J}{dt} \approx 0$$

$$\therefore i_C = C_J \frac{dV_A}{dt}$$

Therefore if rate of rise of forward voltage ( $\frac{dV_A}{dt}$ ) is high, the charging current ( $i_C$ ) would be more if it is greater than  $I_L$  then SCR is turned ON even  $V_A$  is small.


It is the rate of change of  $V_A$  that plays the role of turning-on the SCR.

### \* Temperature triggering (Thermal triggering)

During forward blocking, most of the applied voltage appears across reverse biased junction J<sub>2</sub>. This voltage across J<sub>2</sub>, associated with leakage current, would rise temperature of this junction for semi conductor materials. If temperature then resistance at junction J<sub>2</sub> is decreases. This leads allowing of more current through J<sub>2</sub>. It is cumulative process. The depletion layer will be vanished and device gets turned-on.

The semi conductor materials having -ve temperature Co-efficient. i.e If temperature increases then resistance will be decreases.

### \* Light triggering:-

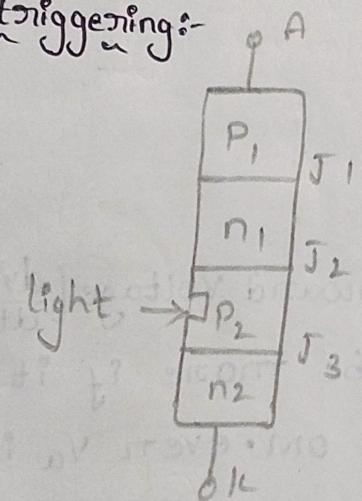

for light triggering SCR P<sub>2</sub>-layer having a provision for light : when light is irradiated on P<sub>2</sub> layer then collisions takes place at gate terminal the free charge carriers generated just to like a gate signal.

This flow of charge carriers reduce the junction J<sub>2</sub> then SCR is on.


LASCR may be triggered with a light source or with a gate signal. Sometimes a combination of both lights and gate signal LASCR's have now used in HVDC-transmission system.

#### \* SCR firing Circuits

As we have seen in above that out of various triggering methods to turn the SCR, gate triggering is the most effective and reliable method. Most of the control applications use this type of triggering because the desired instant of SCR turning is possible with gate triggering method.

#### R triggering of SCR:-

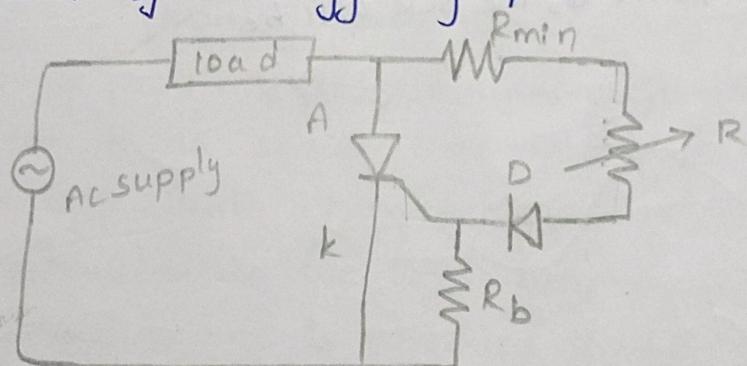(i) R triggering of SCR is one of the methods to turn ON SCR through resistive elements. fig 1 shows the circuit diagram of R triggering of SCR.



Circuit diagram for R triggering of SCR

(2) The resistance  $R_{min}$  is used to limit the gate current to its maximum value. The value of  $R_{min}$  is decided by formula


$$R_{min} \geq \frac{V_m}{I_{gmax}}$$

(3) The resistance  $R_b$  is the stabilizing resistance. The resistance ensures that minimum gate voltage is applied to SCR.

(4) The Variable Resistor  $R$  is used to trigger the thyristor  $T_1$ . When the value of  $R$  is zero.


the firing angle is minimum. The firing angle increases as the value of  $R$  increases.

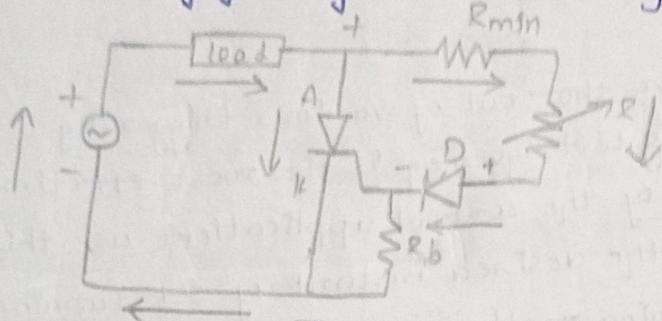- (5) figure 2 shows the operation of the circuit with the direction of flow of current during positive half cycle



Operation of the circuit having during positive half cycle

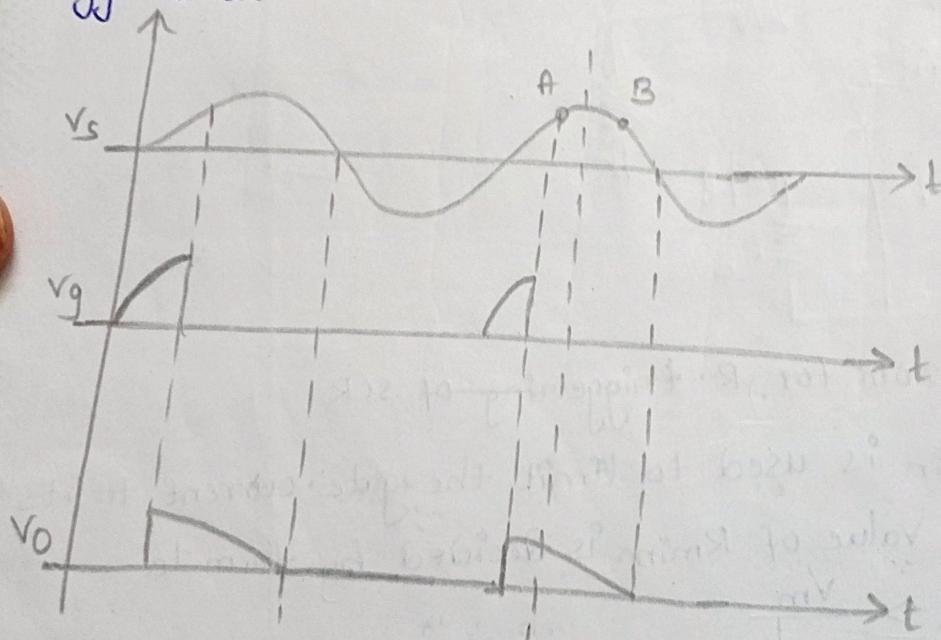
- (6) In the above waveforms it can be observed at points A and B the supply voltage is the same. Therefore, if it is desired to trigger SCR at point B, the SCR will be triggered at




Point A. In other words, triggering of SCR can be controlled only for  $90^\circ$

- (7) Hence maximum triggering angle that can be derived is  $90^\circ$ . This is one of the major drawbacks for this circuit.

\* Rc Half wave triggering of SCR

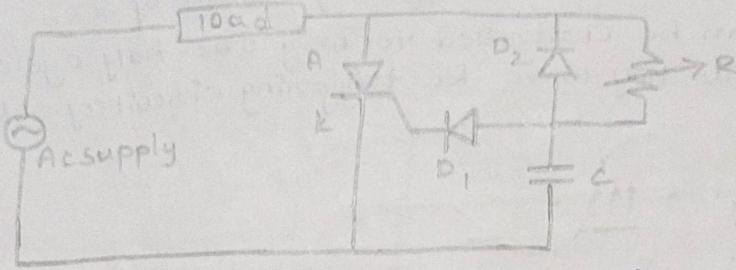


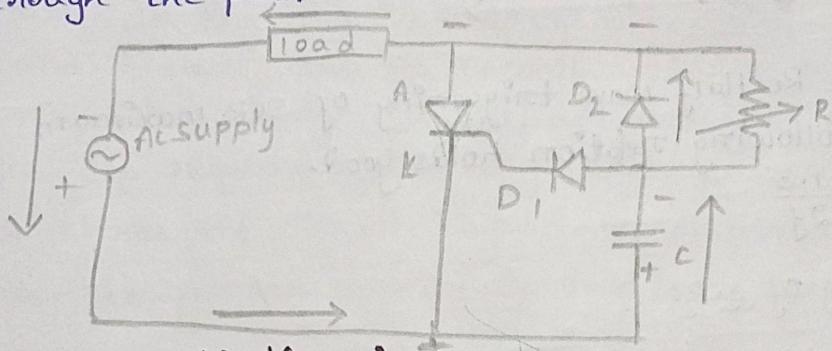(1) During the negative half cycle the capacitor charges to negative polarity through the diode  $D_2$  as shown. The flow of current is through the path indicated with the red arrow head.



(2) Working during negative half cycle.

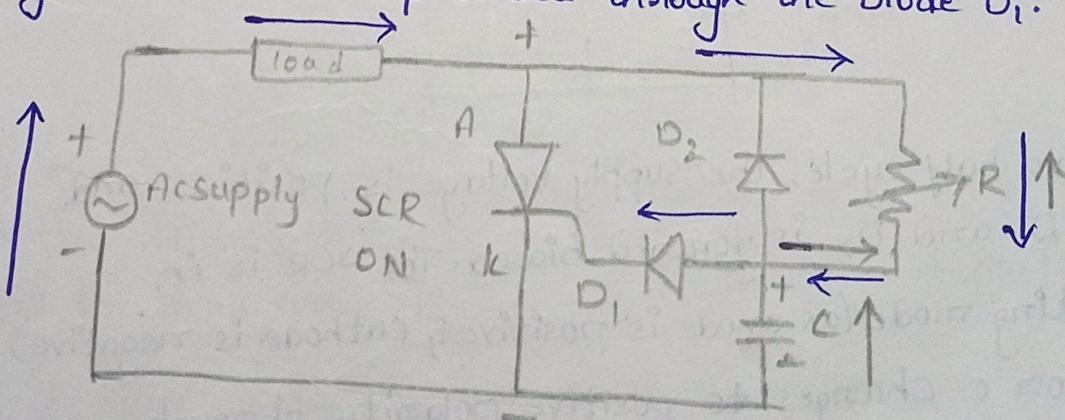(2) During positive half cycle, the capacitor discharges through the resistor  $R$  as shown. Once the energy is discharged, the capacitor starts charging to positive voltage (through the green arrow head). Once the capacitor charges to the gate voltage the gate current is provided through the Diode  $D_1$ .




Working during positive half cycle.

Diode  $D_1$  also prevents negative capacitor voltage to appear across the gate terminal of SCR. the Waveform of the RC triggering circuit of SCR. It can be observed that the SCR can be triggered for

for 180-degree range. Hence it is having much better control over the conventional R triggering circuit of SCR.

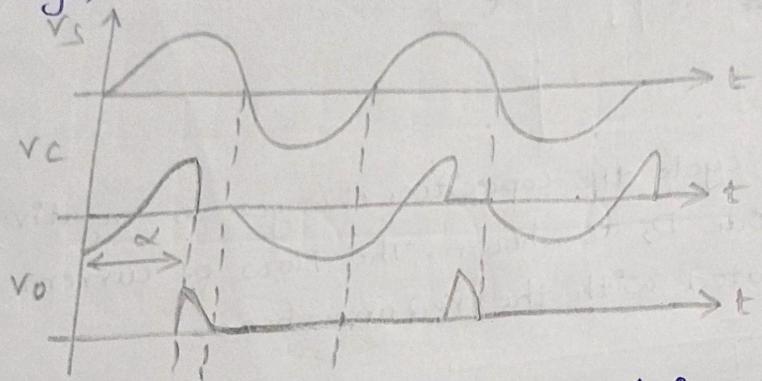
(4) Since the SCR can be controlled for only one-half cycle range, it is called as Half wave RC triggering circuit of SCR.



(5) For zero Output (i.e. RC Half wave triggering of SCR maximum firing angle), the following relation holds good.


$$RC \geq \frac{1.3}{2f}$$

\* RC full wave triggering of SCR:-

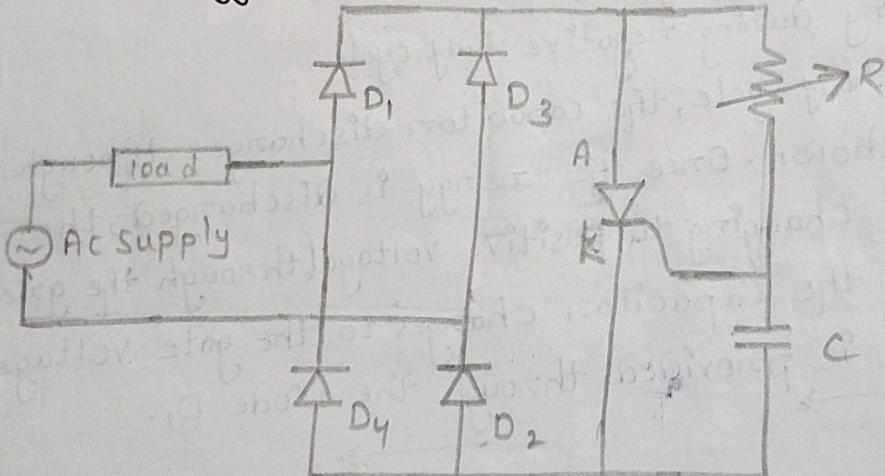

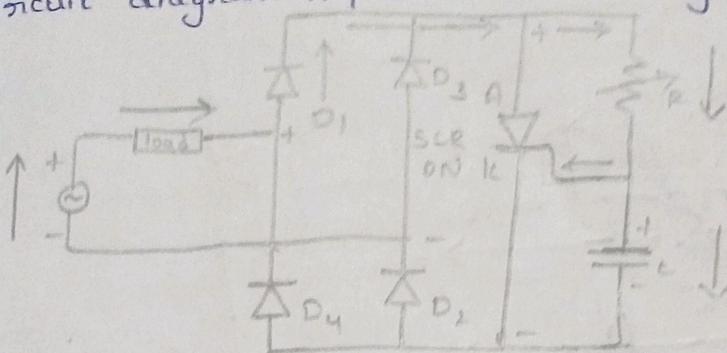
- (1) During positive half cycle, the Supply voltage is positive and consequently D<sub>1</sub> and D<sub>2</sub> is forward biased. The SCR is in forward blocking mode (as anode is positive & cathode is negative)
- (2) The capacitor C charges to positive polarity through the resistor. Once the capacitor charges to find defind the gate voltage, the capacitor supplies the required gate voltage. The SCR now moves from forward blocking

mode to forward conduction mode and turns ON. fig 2 shows the circuit diagram representation during positive half cycle.




During positive half cycle.

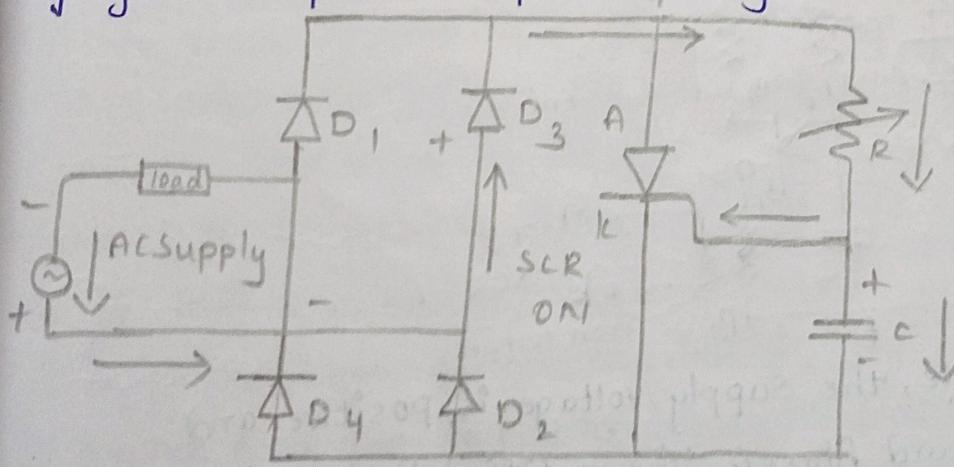- 3) Similarly, during negative half cycle the diode D<sub>3</sub> and D<sub>4</sub> are forward biased and the capacitor charges to positive voltage. Once the capacitor charges to the defined gate voltage, the capacitor supplies the required gate voltage and the SCR is turned ON.
- (q) fig 3. shows the circuit diagram representation during negative half cycle. The process repeats during both the half cycles.



During negative half cycle

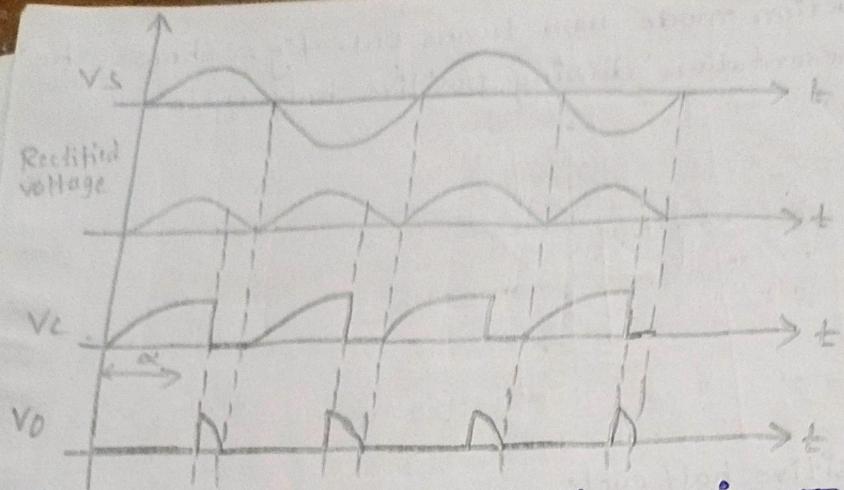- (5) from the Waveform it can be observed that the Capacitor charges to positive voltages in both the half cycle. The Capacitor voltage clamps to zero once the SCR is turned ON.
- (6) One of the major advantages with this circuit is SCR can be turned on with a firing angle between 0 to 180°. In addition, it is possible to control the SCR in both the half cycles. Hence the name RC full wave triggering of SCR.




The following relation holds for maximum firing angle,

$$R_C \geq \frac{0.0157}{2\pi f}$$


$f$  is the supply frequency in above eqn.

\* UJT triggering Circuit for SCR:-

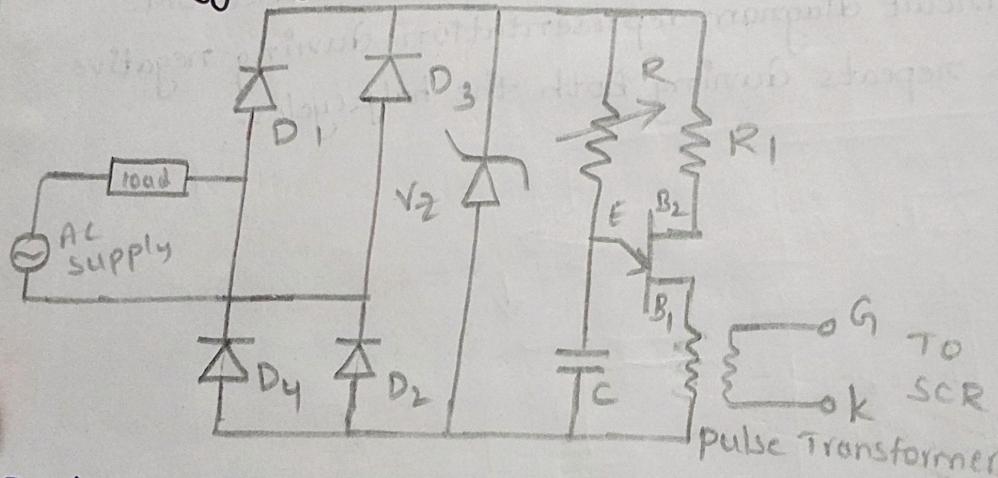


(1) During positive half cycle, the supply voltage is positive and diodes D<sub>1</sub> and D<sub>2</sub> are forward biased. The rectified voltage is clamped to zener voltage V<sub>Z</sub> through the zener diode. The capacitor starts charging to positive voltage through the resistor R as shown in fig 2.


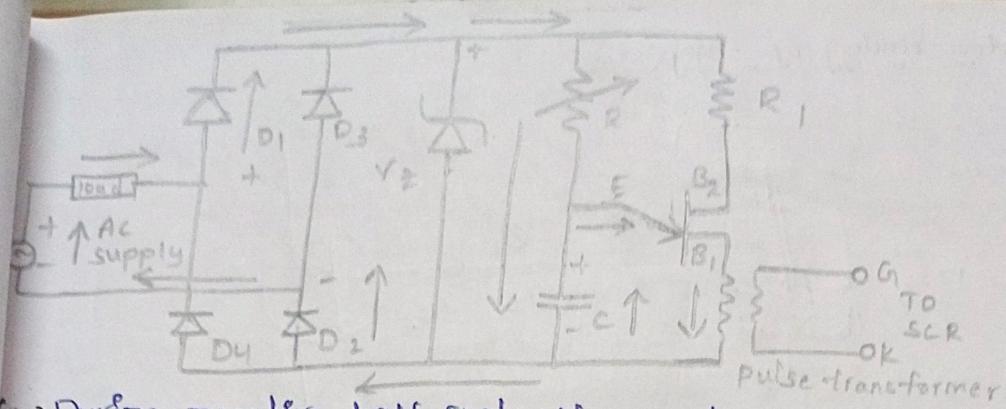
(2) Once the capacitor charges to a peak voltage say V<sub>K</sub> it triggers the UJT and starts discharging. The UJT is turned ON and it supplies excitation to the pulse transformer. The pulse transformer provides the pulse to the gate to Cathode terminal to the SCR.



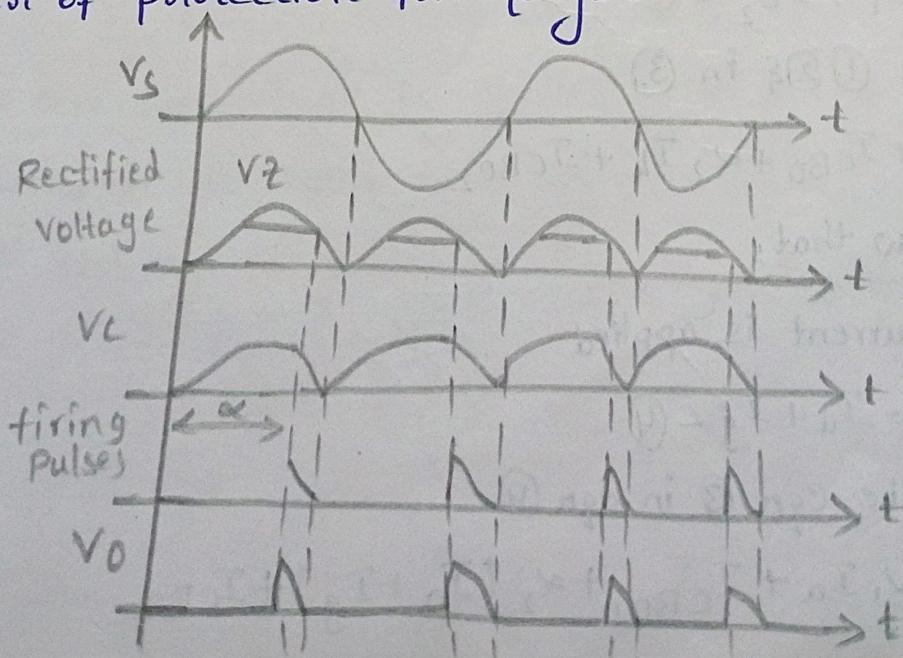- (3) During negative half cycle, the supply voltage is negative and diodes D<sub>3</sub> and D<sub>4</sub> are forward biased. The rectified voltage is clamped to zener voltage V<sub>z</sub> through the zener diode. The capacitor starts charging to positive voltage through the resistor R.
- (4) Once the capacitor charges to a peak voltage say, V<sub>k</sub> it triggers the UJT and starts discharging. The UJT is turned ON and it supplies excitation to the pulse transformer. The pulse transformer provides the pulse to the gate to cathode terminal of SCR.
- (5) This mode of working of UJT is called as relaxation oscillator. The waveforms of UJT triggering circuit for SCR. The firing angle can be controlled by designing suitable values of R & C elements.
- (6) The UJT triggering circuit has the firing angle range from 0 to 180°. One of the major advantages of this circuit is that the pulse transformer provides electrical isolation with the source and the load terminals. This adds up as an additional layer of protection for the gate terminal.



\* Two transistor analogy of Thyristor

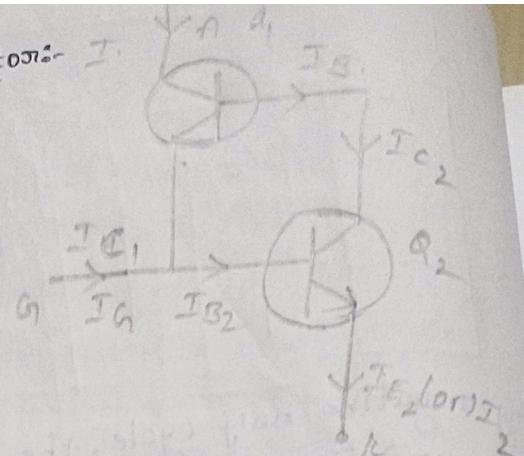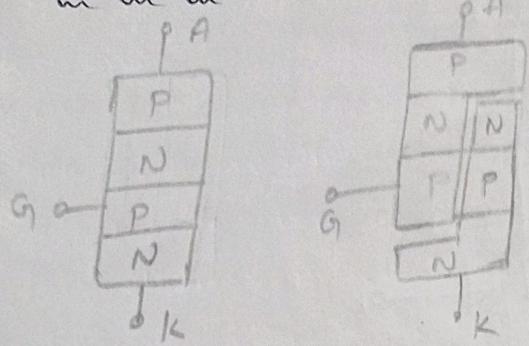

from the circuit,

$$I_a = I_{E_1}$$

$$I_{B_1} = I_{C_2}$$

$$I_{E_2} = I_k$$

We know that,

$$\text{Current Gain of transistor} = \alpha = \frac{I_C}{I_E}$$

$$I_C = \alpha I_E + I_{CB0}$$

$I_{CB0}$  is the Collector base leakage current

$$\therefore I_{C_1} = \alpha_1 I_{E_1} + I_{CB0_1}$$

$$I_{C_1} = \alpha_1 I_a + I_{CB0_1} \quad \textcircled{1}$$

$$I_{C_2} = \alpha_2 I_{E_2} + I_{CB0_2}$$

$$I_{C_2} = \alpha_2 I_k + I_{CB0_2} \quad \textcircled{2}$$

$$I_A = I_{C_1} + I_{C_2} \quad \textcircled{3}$$

Sub \textcircled{1} \textcircled{2} \& in \textcircled{3}

$$I_A = \alpha_1 I_a + I_{CB0_1} + \alpha_2 I_k + I_{CB0_2}$$

We know that,

when Gate current is applied

$$I_k = I_a + I_g \quad \textcircled{4}$$

Substitute eqn \textcircled{3} in eqn \textcircled{4}

$$I_a = \alpha_1 I_a + I_{CB0_1} + \alpha_2 (I_a + I_g) + I_{CB0_2}$$

$$I_a = \alpha_1 I_a$$

$$I_a - \alpha_1 I_a$$

$$I_{a1} - \alpha_1 - \alpha_2$$

$$I_a =$$

commutation

To turn on  
applied to the

Once the th

hyristor will  
to zero, or

The thyrist

voltage never

NO such

to force

process is

commutati

the process

In all C

ie thy

The cor

\*  $I_A <$

\* A rev

nablin

\*

\*

$$I_a = \alpha_1 I_a + I_{CBO_1} + \alpha_2 I_a + \alpha_2 I_g + I_{CBO_2}$$

$$I_a - \alpha_1 I_a - \alpha_2 I_a = I_{CBO_1} + \alpha_2 I_g + I_{CBO_2}$$

$$I_a(1 - \alpha_1 - \alpha_2) = I_{CBO_1} + \alpha_2 I_g + I_{CBO_2}$$

$$I_a = \frac{\alpha_2 I_g + I_{CBO_1} + I_{CBO_2}}{1 - (\alpha_1 + \alpha_2)}$$

Commutation - Turning off SCR:-

- (1) To turn on a thyristor, a low voltage, short duration pulse is applied to the gate
- (2) Once the thyristor is turned-on, the gate loses control and the thyristor will only turn off when the load current falls virtually to zero, or the thyristor is reverse biased
- (3) The thyristor will turn off naturally with A.c. supplies as the voltage reverses
- (4) No such reversal occurs with D.c. supplies and it is necessary to force a voltage reversal if turn-off is to occur. The process is called forced commutation.

Commutation:-

- (1) The process of turning off SCR is defined as "Commutation".
- (2) In all commutation techniques, a reverse voltage is applied across the thyristor during the turn off process.
- (3) The conditions to be satisfied in order to turn off an SCR are:
  - \*  $I_A < I_H$  (Anode Current must be less than holding current)
  - \* A reverse voltage is applied to SCR for sufficient time enabling it to recover its blocking state
  - \* Natural commutation
  - \* forced commutation.

### \* Natural commutation:-


In AC circuit, the current always passes through zero for every half cycle.

As the current passes through natural zero, a reverse voltage will simultaneously appear across the device.

This will turn off the device immediately.

This process is called as natural commutation, since no external circuit is required for this purpose.

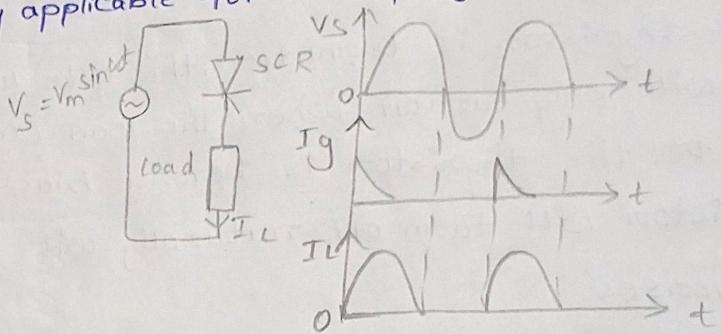This method is only applicable for AC supply.



### \* forced commutation:-

To turn off a thyristor the forward anode current should be brought to zero for sufficient time to allow the removal of charged carriers.

In case of DC circuits, the forward current should be forced to zero by means of some external circuits.

This process is called as forced commutation.


With D.C Supply, we use external circuit and active/passive components to reduce passing current's value below holding current.

The circuit involved in this procedure is called commutation circuit.

The components used are called commutating components.

\* class-A commutation:-

Working:

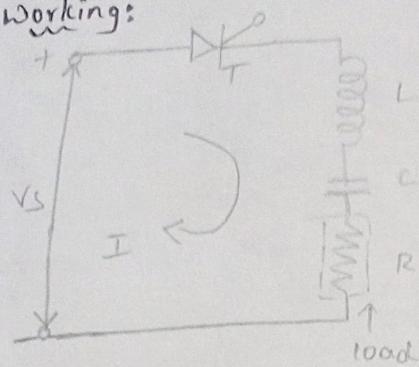

Class A commutation is also called as self-commutation or resonant commutation or load commutation


On applying an external dc gate signal, the current starts flowing through the circuit. In order to turn on the SCR in the circuit, a gate trigger pulse is required. So, simultaneously gate signal is applied that will put the thyristor in forward conduction mode

Hence, after the SCR gets on, the forward current that flows through the SCR begins to charge the capacitor. At the same time, the inductor connected in the circuit stores energy.

We know that it is the property of the inductor, that it opposes the change in current. So, once the capacitor gets charged up to the peak of the supply input, the polarity of the inductor connected in the circuit will get reversed and now the inductor will oppose any further flow of current through it.


As, the inductor does not further allow the flow of current, the output current starts to decrease and reaches zero.

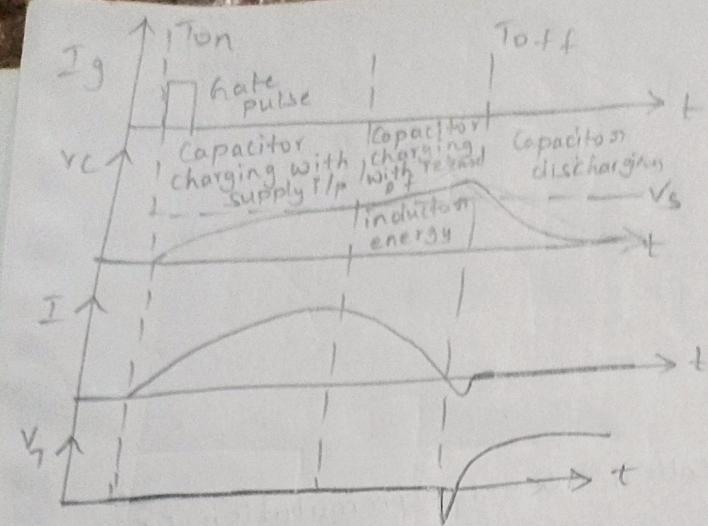This means here the commutating components make the current through the load zero and this commutes the thyristor.



\* Class - B Commutation:-

Working:-

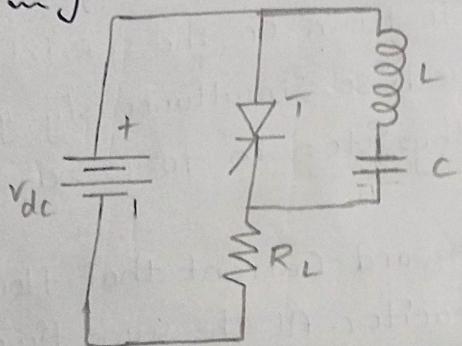

Class B commutation is also called as Resonant-pulse Commutation.


At the initial level when external i/p supply  $V_{dc}$  is provided to the circuit then this causes the capacitor to get charged. As no gate excitation is provided to the SCR thus the externally supplied i/p signal will not bring the thyristor into forward conduction mode. But due to Supply i/p, the current in the circuit flows through commuting Components L & C & the load.

This causes charging of the capacitor with the same Polarity as that of the supply i/p. The Capacitor gets charged up to the peak of supply i/p Voltage.

is, the capacitor hold the charge more, over at once comes in CR starts conduction & current flows

$V_{dc}$

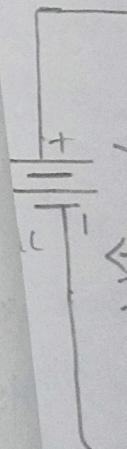
Now, once the direct exist at the gate me time to change




The note cu ho

As, the capacitor does not have a path to discharge thus it will hold the charge + $V_{dc}$

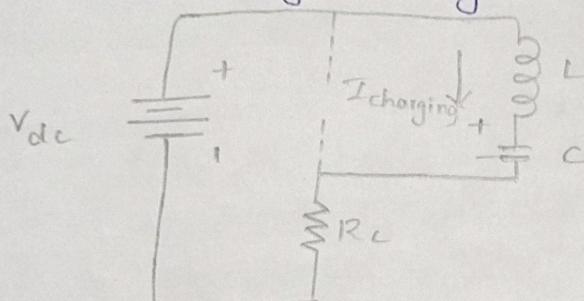
More, over at this time, if the thyristor is triggered, then the device comes in forward conduction mode. And so in this condition, SCR starts conduction and current begins to flow from the thyristor & load part of the circuit. The direction in which current flow through the thyristor takes place is shown.



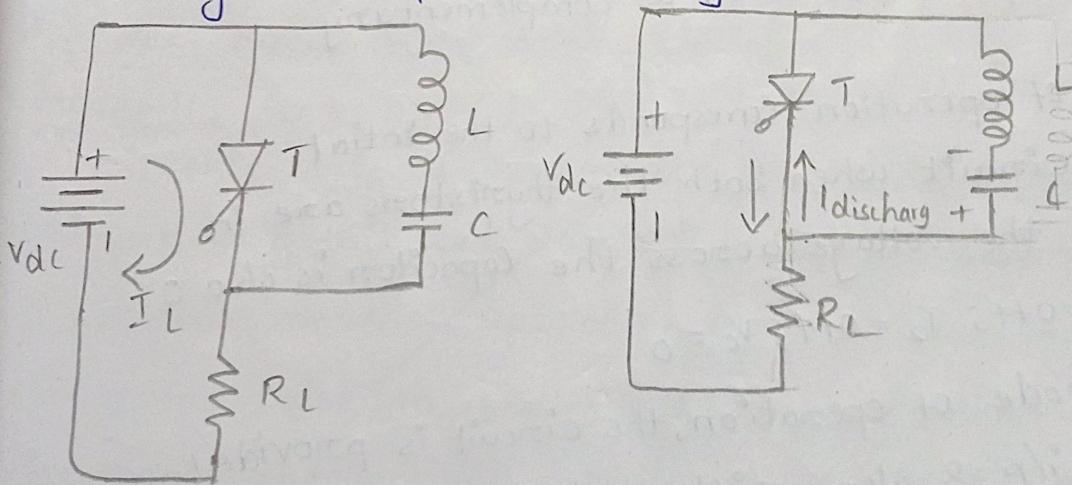Now, once the capacitor gets completely discharged then due to the direction of flow of discharging current, reverse polarity will exist at the capacitor. More simply, in the presence of supply  $V_{dc}$  and gate triggering pulse, the thyristor will be in on state & at the same time after getting discharged once, the capacitor begins to charge with opposite polarity




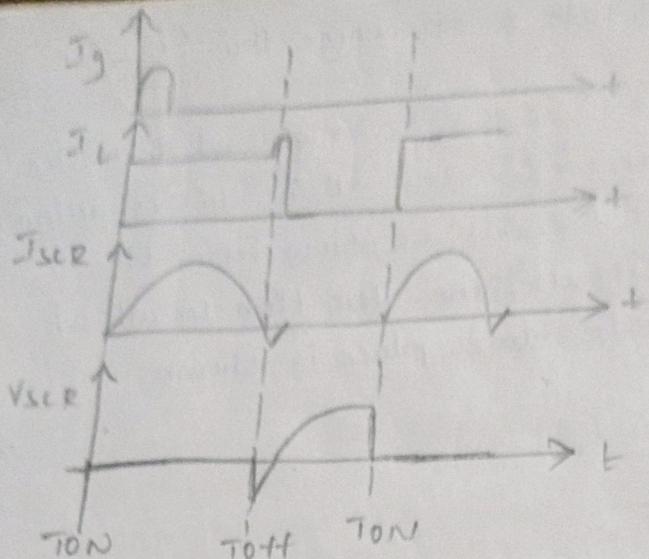This current is known as Commutating Current and is denoted by  $I_c$  & this  $I_c$  opposes the flow of  $I_L$  in given circuit. As soon as the value of  $I_c$  exceeds  $I_L$  then this makes the current flowing through the thyristor fall below the value holding current resultantly turning the thyristor off.



\* Class - C Commutation:-

Working:-

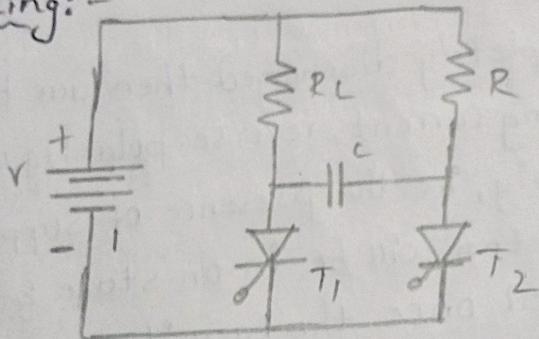


Class C commutation is also called as complementary commutation

Mode 0: This mode of operation corresponds to the initial state of the circuit when both the thyristors are in off state and so the voltage across the capacitor is also 0.

This means,  $T_1 = \text{off}$ ;  $T_2 = \text{off}$ ;  $V_C = 0$

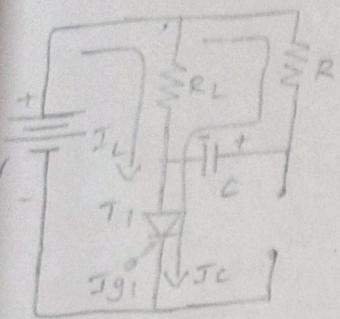Mode 1: In this mode of operation, the circuit is provided with dc supply i/p & along with that thyristor  $T_1$  is triggered with a gate signal. Due to this  $T_1$  will come in conducting state. This leads to two currents one will be the load current while the other will be charging current of capacitor to flow through the whole circuit



The load current & capacitor current are given as  $I_L = \frac{V}{R_L}$

while the charging current will be

$$I_C = \frac{V}{R}$$

Hence, the overall current that flows through SCR,  $T_1$ , will be the sum of load current & charging current. This is given as

$$I = \underline{V} + \underline{V}$$

Mode-I

Due to flow of the charging Current, the capacitor gets charged up to peak of supply i/p accordingly to the polarity as shown

However, the charging Current reduce to 0, once the Capacitor gets fully charged up to the Supply i/p, & thus the only Current that continues to flow through  $T_1$  is the load current. Even when the moment C is holding the charge,  $T_1$  continues to remain in conducting state. Hence,


$$\text{If } T_1 = \text{On}; T_2 = \text{Off}; V_C = V$$

Now, our attempt should be to commutate  $T_1$  & this is explained in next mode of operation

Mode-II

In this state of operation,  $T_2$  is provided the gate pulse that triggers it & this leads to turning off  $T_1$ . Now, the so, this mode of operation is such that by providing a triggering pulse to  $T_2$ , the path becomes short-circuited. Once this happens, the polarity of charge stored by the capacitor reverse biases the thyristor  $T_1$ .

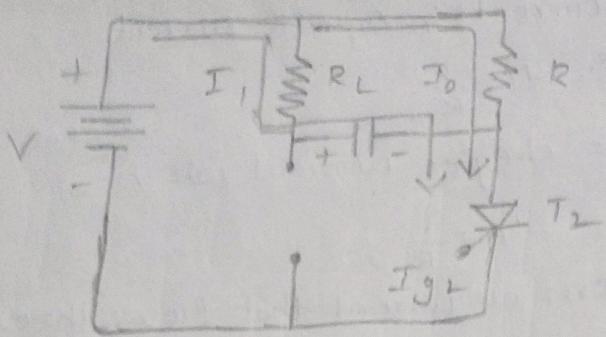This reverse biased condition leads to turning off of the thyristor  $T_1$ . So, when  $T_2$  is conducting state



Mode-II

The current flowing through  $R-T_2$  will be given as

$$I_0 = \frac{V}{R}$$

Mode-II

However, the flow of current through the capacitor again charges the capacitor but this time with reverse polarity i.e opposite to the case discussed previously

Hence, mode II operation provides,

$$\bar{T}_1 = \text{off}; T_2 = \text{on}; V_C = -V$$

See previously



Mode-III

In order to turn off  $T_2$ ,  $T_1$  is triggered using gate pulse. Once  $T_1$  starts conduction then the polarity existing across C reverse biases  $T_2$  due to which  $T_2$  stops conduction & the current flows through  $T_1$  like we have discussed in

Hence, the mode III operation will lead cause


$$\bar{T}_1 = \text{on}; \bar{T}_2 = \text{off}; V_C = V$$

Mode-III

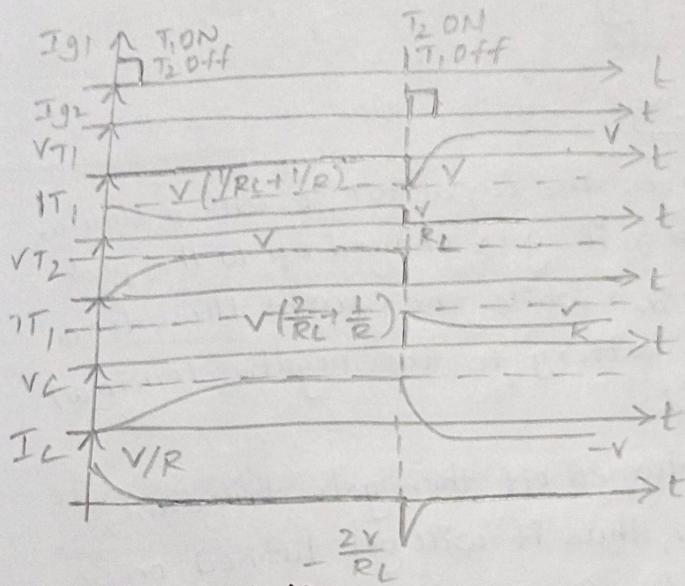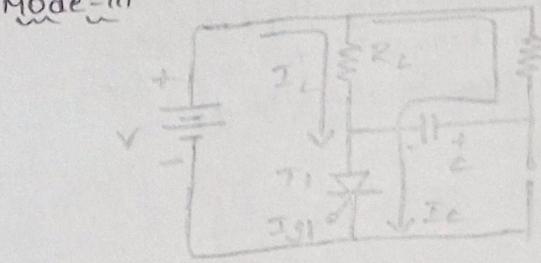

\* Class-D Commutation:-

Working:-

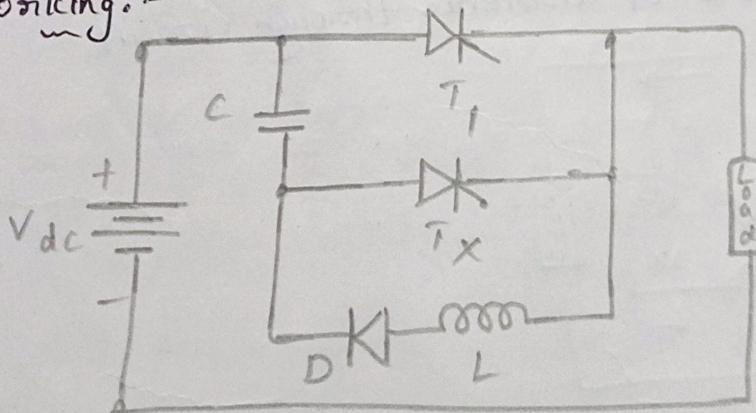


Class D commutation is also called as Impulse commutation or Voltage commutation -

Initially on applying voltage V across the circuit but in the absence of gate triggering pulse both the thyristors are in the off state.


Due to the supply i/p, the diode fig is reverse biased condition thus, no flow of current takes place through the circuit hence the voltage across the capacitor will be 0.

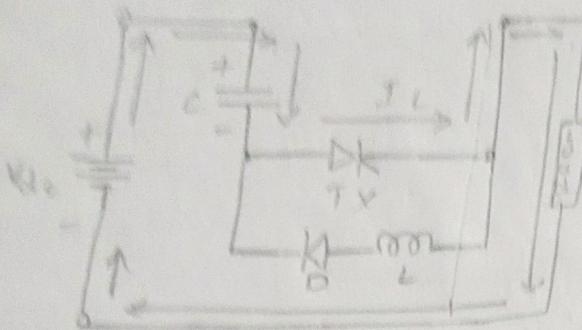Another one of two thyristors, the auxiliary thyristor is provided gate triggering pulse which brings it to conducting state, thus, the current starts to flow in the circuit.




This flow of current charges the capacitor  $C$  with a similar polarity as that of supply i/p & it gets charged up to the peak of the peak supply value i.e.  $V_{dc}$ . While the current flows from the positive terminal of the battery to the negative terminal, by passing through the load.

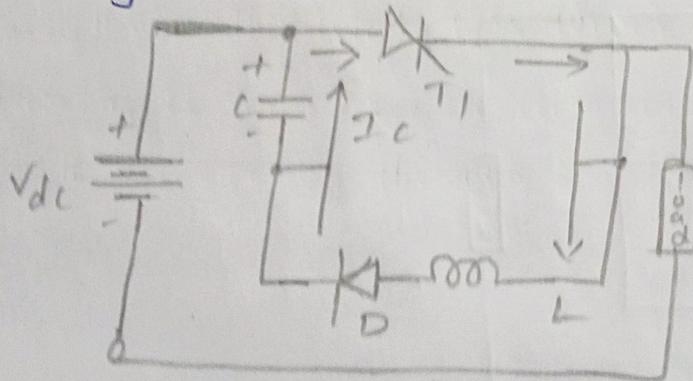Now, once  $T_1$  gets turned off then gate triggering pulse is given to thyristor  $T_1$ , thus it will get turned on under presence of supply i/p. As  $T_1$  comes into the conducting state, & the flow of currents through circuit




Now, as  $T_1$  is in conducting state & we have to commutate  $T_1$ , thus, for this we need to trigger  $T_x$  i.e. the auxiliary thyristor,  $T_x$  to a reverse biased state and this will lead to turning the thyristor off.

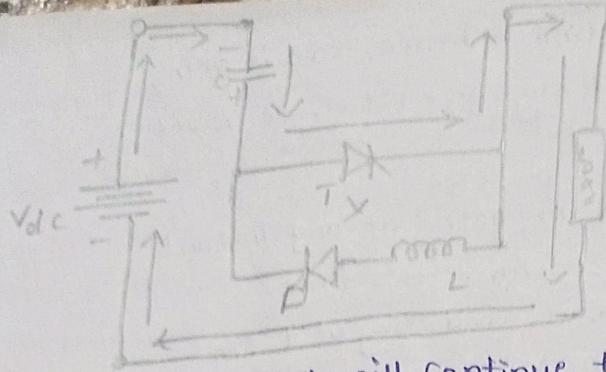
Thus, once  $T_1$  gets turned off then the current through the circuit will flow in the manner



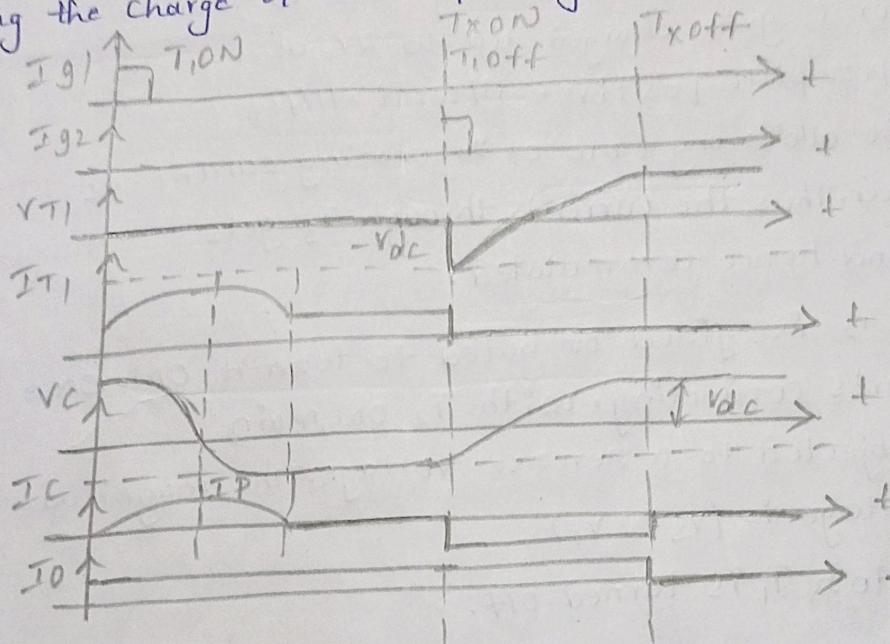And this current will continue to flow till the time the capacitor is holding the charge of reverse polarity as the supply i/p



#### \* Class - E commutation:-

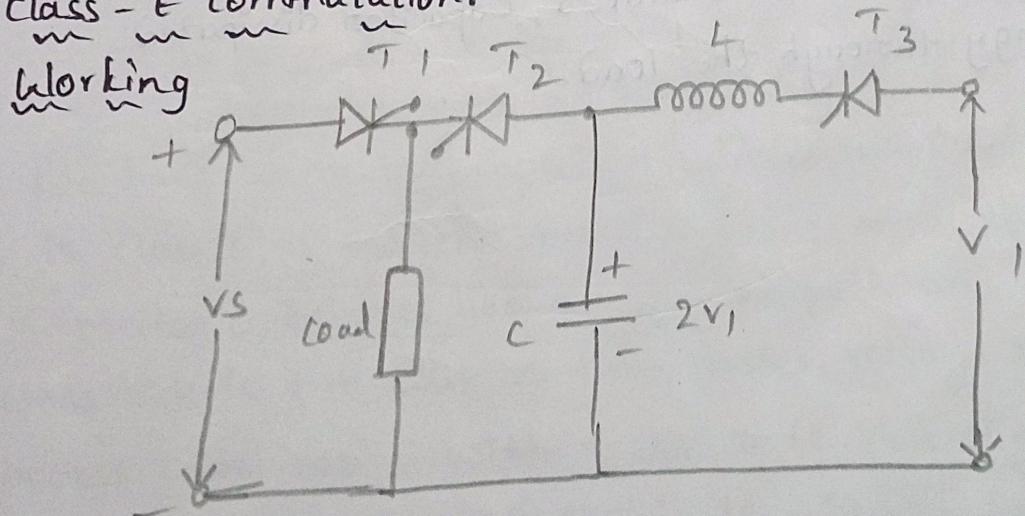

Class - E commutation is also known as External pulse commutation. This external Current pulse is obtained from a separate voltage source.

Initially thyristor  $T_1$  is conducting & hence, load is being fed by main voltage source  $V_s$  through  $V_1$ . Now, we want to turn off main SCR  $T_1$ .

For this, thyristor  $T_3$  is fired or gated at any instant of time to turn it ON. Let us assume this time to be  $t=0$  sec. Once  $T_3$  is ON, it starts conducting at  $t=0$  sec. A resonating circuit consisting of  $V_1$ ,  $L$  and  $C$  is formed and resonating current starts flowing. Due to resonating current, capacitor  $C$  gets charged up to  $2V_1$  at  $t=\pi/\sqrt{LC}$  with upper plate positive. After  $t=\pi/\sqrt{LC}$  capacitor will not allow any flow of resonating current as it is fully charged. Thus, the current through  $T_3$  gets reduced to zero and hence commutated.

Now, thyristor  $T_2$  is fired or gated to turn it ON. Once  $T_2$  is ON, it starts conducting. With  $T_2$  ON, main thyristor  $T_1$  is subjected to a reverse voltage. The magnitude of this reverse voltage is  $(V_s - 2V_1)$ .

∴ main, thyristor  $T_1$  is turned off.

After  $T_1$  is turned off or commutated, capacitor dissipates its stored energy through the load.

## \* Snubber circuit - purpose, Design and working:-


### Purpose of Snubber circuit:-

The main purpose of snubber circuit is to prevent the unwanted triggering of SCR or thyristor due to high rate of rise of voltage i.e.  $dv/dt$ . We already know that if the rate of rise of anode to cathode voltage of SCR is high then it may lead to false triggering. This is commonly known as  $dv/dt$  triggering. Thus we need to have some arrangement to protect SCR from such undesirable turning.

Application of snubber circuit. Thus it is basically  $dv/dt$  protection of SCR.
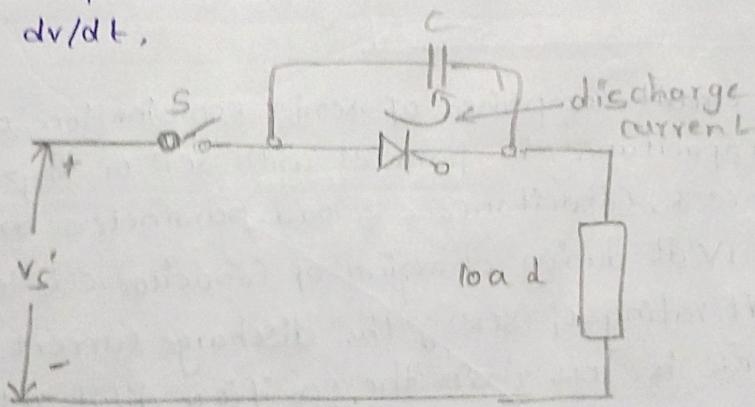
### Design and working Principle of snubber circuit:-

As we need to limit the rate of rise of anode to cathode voltage of SCR during its turn 'on' process, this means we should use a capacitor the SCR terminals. This is because a capacitor limits the rate of rise of voltage whereas an inductor limits the rate of rise of current. Thus a capacitor when connected across the SCR terminals, when limit  $dv/dt$ ,




We have connected Capacitor C in parallel with SCR. When switch S is closed, a sudden voltage appears across the circuit. Initially Capacitor C behaves like a shorted path and hence the voltage across SCR is zero. But as time passes, voltage starts building up across Capacitor C with a slow rate. Thus the rate of rise of Voltage  $dv/dt$  across SCR terminals will also be slow and less than the specified  $dv/dt$  rating of SCR.

Before SCR is fired or triggered by applying gate pulse, the Capacitor C is fully charged up to supply voltage  $V_S$ . As soon as SC

is turned on by gate pulse, this charged capacitor  $C$  discharges through SCR. Hence a current having magnitude flows in the local path formed by SCR and capacitor  $C$ . Since the value of resistance of this local path is quite small, the magnitude of discharge current will be quite higher. This will lead to high value of  $dI/dt$  which may exceed the specified  $dI/dt$  rating of SCR. In order to limit the magnitude of the discharge current, a resistor should be connected in series with the capacitor  $C$ .

Actual Snubber Circuit:- R C

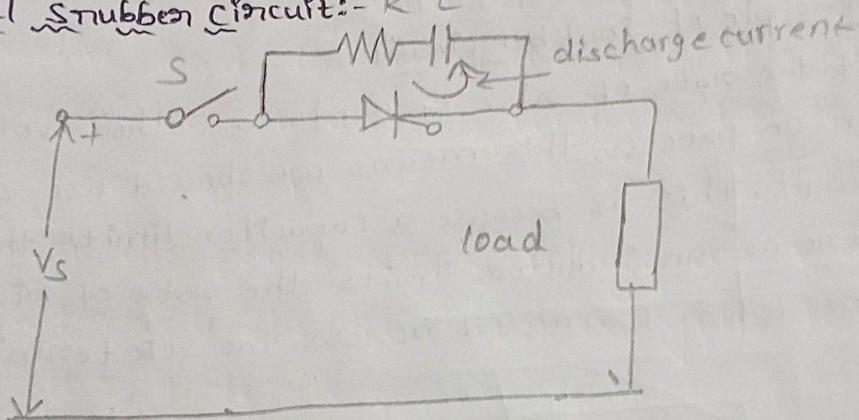

Thus a snubber circuit comprises of series combination of resistance and capacitance in parallel with SCR or thyristor. Generally, resistance  $R$ , capacitance  $C$  & load parameters are so chosen that the  $dV/dt$  during charging of capacitor  $C$  is less than the specified  $dV/dt$  rating of SCR & the discharge current at the turn on of SCR is less than the specified  $dI/dt$  rating.

Gel

Many Industrial applications make use of "controllable DC power". Examples of such applications are as follows

- (a) Steel-rolling mills, paper mills, printing presses and textile mills
- (b) Traction systems working on DC.
- (c) Electrochemical and electrometallurgical process.
- (d) magnet power supplies
- (e) portable hand tool drives
- (f) HVDC transmission

Earlier DC power was obtained from Motor-Generator (M-G) Sets or ac power was converted to DC power by means of mercury-arc rectifiers or thyristors. Now a days those are replaced with phase controlled Rectifiers.


- \* In phase-controlled rectifiers, a thyristor is turned off as ac supply voltage reverse biases it, provided anode current has fallen to a level below the holding current. The turning-off, or commutation of a thyristor by supply voltage itself is called natural (or) line commutation.
- \* therefore in phase-controlled rectifiers no need of commutation circuitry. These are less expensive and are widely used in industries where controlled DC power is required.

\*\* In the study of SCR Systems and diodes are assumed ideal switches which means that

- (i) there is no voltage drop across them
- (ii) no reverse current exists under reverse voltage conditions
- (iii) holding current is zero.

Trigger circuits are not shown in SCR ckt for convenience

\*Classification:-

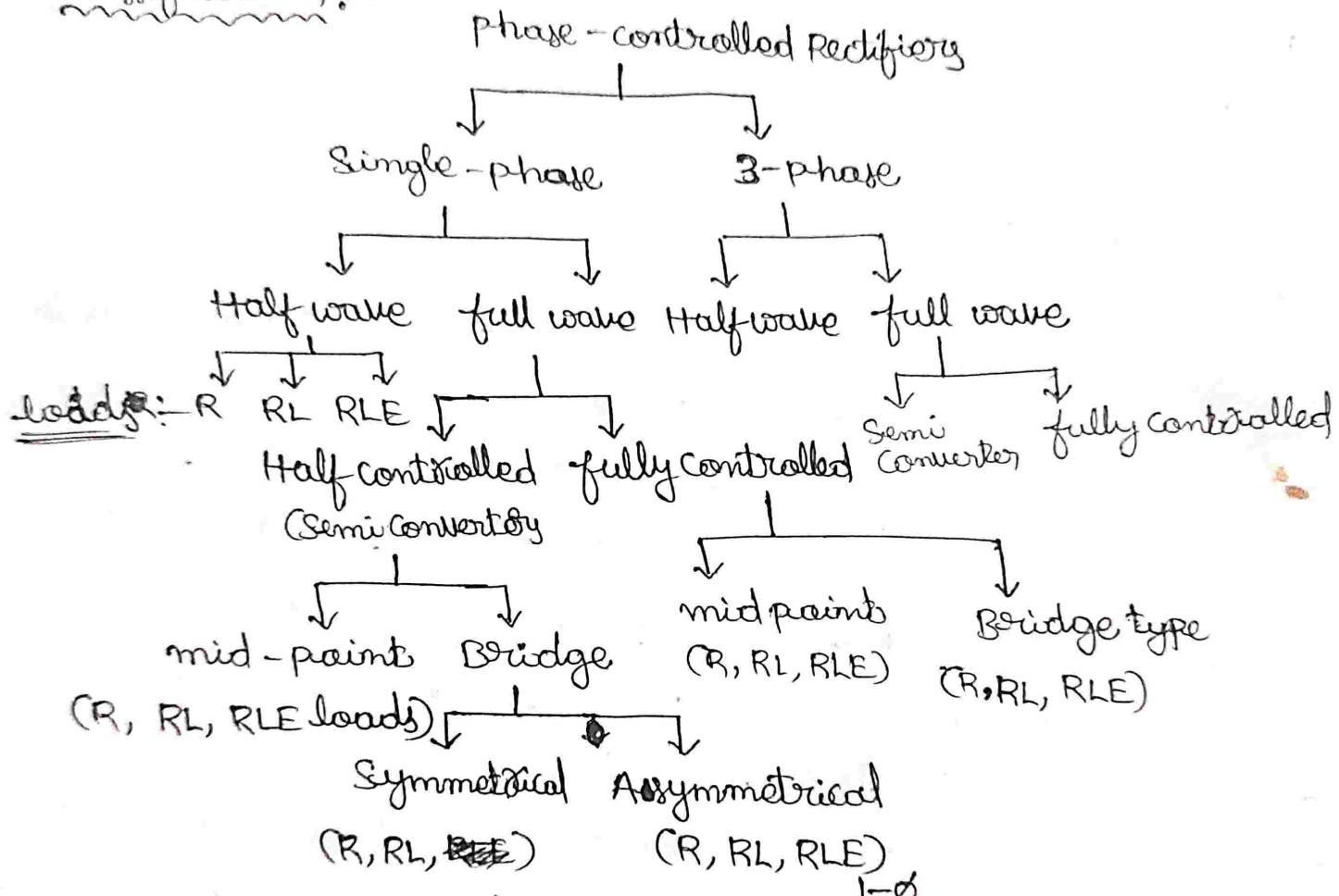

In this unit we will Study about half controlled converter

In the next unit  $\rightarrow$  we will Study about 1-phase fully controlled converters

$$V_0 = 0$$

$$I_0 = 0$$

$$V_T = V_S = V_m \sin \omega t$$

$$\text{at } \omega t = 0$$

$$V_0 = V_m \sin 0^\circ$$

$$I_0 = \frac{V_0}{R} = \frac{V_m \sin 0^\circ}{R}$$

$\alpha \leq \omega t \leq \pi$ :

$$V_0 = V_S = V_m \sin \omega t$$

$$I_0 = \frac{V_0}{R}$$

$$V_T = 0$$

at  $\omega t = \pi$  they just enter turn-off

$$V_0 = 0$$

$$V_T = V_S$$

$$I_0 = 0$$

The circuit turn-off time is given by

$$t_c = \frac{\pi}{\omega} \text{ sec} \quad (\because \omega = 2\pi f)$$

Average voltage  $V_0$  across load  $R$  is given by

$$V_0 = \frac{1}{2\pi} \int_{\alpha}^{\pi} V_m \sin \omega t d(\omega t) \quad \left[ \because V_{avg} = \frac{1}{T} \int_0^T f(t) dt \right]$$

$$V_0 = \frac{V_m}{2\pi} \left[ -\cos \omega t \right]_{\alpha}^{\pi}$$

$$V_0 = \frac{V_m}{2\pi} \left[ -\cos \pi + \cos \alpha \right]$$

$$\therefore V_0 = \frac{V_m}{2\pi} [1 + \cos \alpha]$$

The maximum value of average of  $V_0$  occurs at  $\alpha = 0^\circ$

$$V_{0m} = \frac{V_m}{2\pi} [1 + \cos 0^\circ] = \frac{V_m}{\pi}$$

$$\text{Average load current } (I_0) = \frac{V_0}{R} = \frac{V_m}{2\pi R} (1 + \cos \alpha)$$

RMS voltage of load voltage is given by

$$V_{0r} = \left[ \frac{1}{2\pi} \int_{\alpha}^{\pi} V_m^2 \sin^2 \omega t d(\omega t) \right]^{\frac{1}{2}}$$

$$V_{0r} = \left[ \frac{V_m^2}{2\pi} \int_{\alpha}^{\pi} \left( \frac{1 + \cos 2\omega t}{2} \right) d(\omega t) \right]^{\frac{1}{2}}$$

$$V_{0r} = \frac{V_m}{2\sqrt{\pi}} \left[ \pi - \alpha + \frac{\sin 2\alpha}{2} \right]$$

$$\& I_{0r} = \frac{V_{0r}}{R}$$

# Single-phase half-wave converter with R-load



The half wave converter with R-load is shown in fig.

The source voltage is

$$V_s = V_m \sin \omega t$$

An SCR can conduct only when Anode voltage is +ve and a gate signal is applied.


Thyristor blocks the current to until it is triggered at  $\omega t = \alpha$  some delay angle. Thyristor can be triggered.

then  $V_o$  varies from 0 to  $V_m \sin \alpha$  and output voltage follows the input from  $\alpha$  to  $\pi$ .

\* firing angle of a thyristor is measured from the instant it would start conducting if it were replaced by a diode. It would begin conduction at  $\omega t = 0, 2\pi, 4\pi$  etc.

\*\* firing angle may be defined as the angle measured from the instant SCR gets forward biased to the instant it is triggered.

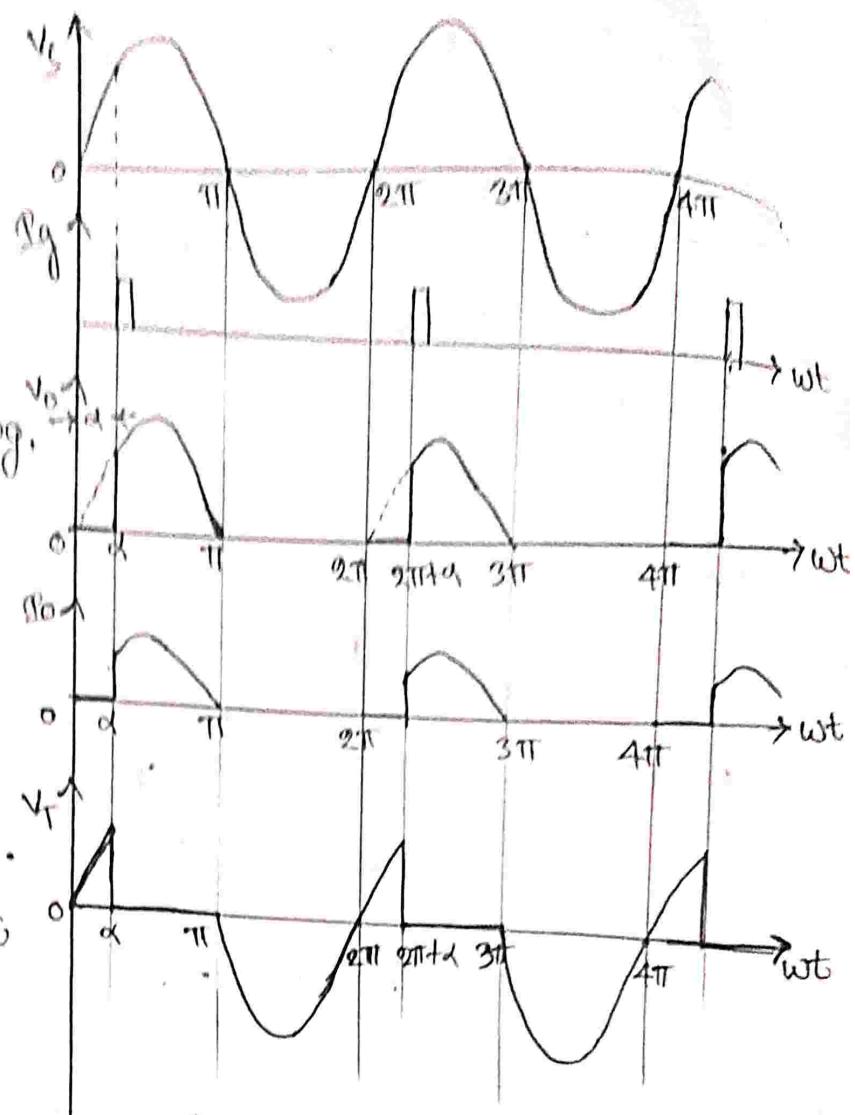once the SCR is on, load current flows until it is turned off by reversal of voltage at  $\omega t = \pi, 3\pi$  etc... At these angles load current falls to zero & Thyristor is OFF.



$$V_{0\delta} = \left[ \frac{V_m^2}{4\pi} \int_{-\alpha}^{\pi} (1 - \cos 2\omega t) d(\omega t) \right]^{\frac{1}{2}} \quad (3)$$

$$V_{0\delta} = \frac{V_m}{2\sqrt{\pi}} \left\{ \left[ \omega t - \frac{\sin 2\omega t}{2} \right]_{-\alpha}^{\pi} \right\}^{\frac{1}{2}}$$

$$V_{0\delta} = \frac{V_m}{2\sqrt{\pi}} \left\{ (\pi - \alpha) - \left[ \frac{\sin 2\pi - \sin 2\alpha}{2} \right] \right\}^{\frac{1}{2}}$$

$$\therefore V_{0\delta} = \frac{V_m}{2\sqrt{\pi}} \left[ (\pi - \alpha) + \frac{\sin 2\alpha}{2} \right]^{\frac{1}{2}}$$

The value of RMS load current  $I_{0\delta}$  is

$$I_{0\delta} = \frac{V_{0\delta}}{R}$$

$$\therefore I_{0\delta} = \frac{V_m}{2\sqrt{\pi}(R)} \left[ (\pi - \alpha) + \frac{\sin 2\alpha}{2} \right]^{\frac{1}{2}}$$

$$\text{power delivered to resistive load} = V_{0\delta} \times I_{0\delta} = \frac{V_{0\delta}^2}{R} = I_{0\delta}^2 R$$

$$\text{Input volt amperes} = V_s \times I_{0\delta}$$

$$= V_s \times \frac{V_m}{2\sqrt{\pi}} \left[ (\pi - \alpha) + \frac{\sin 2\alpha}{2} \right]^{\frac{1}{2}} \quad \left[ V_{0\delta} = \frac{V_m}{\sqrt{2}} \right]$$


$$V_s I_{0\delta} = \frac{\sqrt{2} V_s^2}{2R\sqrt{\pi}} \left[ (\pi - \alpha) + \frac{\sin 2\alpha}{2} \right]^{\frac{1}{2}} \quad \left[ \therefore V_m = \sqrt{2} V_s \right]$$

$$\text{Input power factor} = \frac{\text{power delivered to load}}{\text{input VA}}$$

$$\begin{aligned} &= \frac{\frac{V_m^2}{R(4\pi)} \left[ (\pi - \alpha) + \frac{\sin 2\alpha}{2} \right]}{\frac{V_m^2}{2\sqrt{2}R\pi} \left[ (\pi - \alpha) + \frac{\sin 2\alpha}{2} \right]^{\frac{1}{2}}} \\ &= \frac{\sqrt{2}}{2\sqrt{\pi}} \end{aligned}$$

$$\therefore \text{I/p P.F} = \frac{1}{\sqrt{2}\pi} \left[ (\pi - \alpha) + \frac{\sin 2\alpha}{2} \right]^{\frac{1}{2}}$$
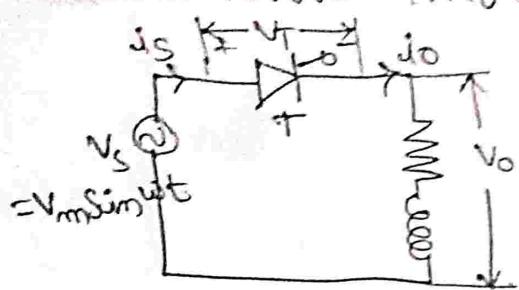
# Single-phase Half-wave circuit with RL load



$$0 \leq \omega t \leq \alpha$$

In this Interval

$$V_o = 0$$

$$I_o = 0$$

$$V_T = V_s$$

At  $\omega t = \alpha$  Thyristor T is turn-on by gating signal

$$V_o = V_m \sin \alpha$$


$I_o$  starts rising.

$\alpha \leq \omega t \leq \pi$ : O/p voltage  $V_o = V_s$  current rises gradually after some time  $I_o$  reaches maximum & then begins to decrease

At  $\omega t = \pi$   $V_o = 0$  but load current  $I_o$  is not zero because of the load inductor L. After  $\omega t = \pi$ , SCR is subjected to reverse anode voltage but it will not be turned off as load current is not less than the holding current. At some angle  $\beta > \pi$ , "o" reduced its zero and SCR is turned-off as it is already reverse biased.

After  $\omega t = \beta$ ,  $V_o = 0$  &  $I_o = 0$  At  $\omega t = 2\pi + \alpha$  SCR is triggered again,  $V_o = V_s$ .

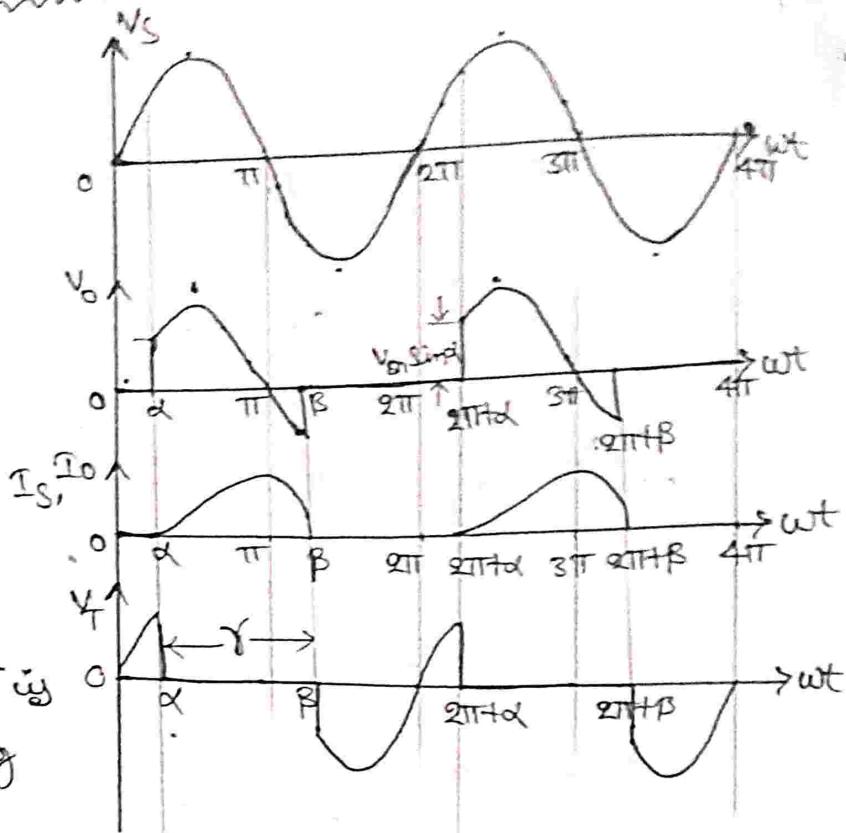Angle "β" is called the extinction angle and  $\gamma = (\beta - \alpha)$  is called the conduction angle.



Thus circuit turn-off time  $t_c$

conducting upto  $\beta \Rightarrow \omega t_c = 2\pi - \beta$

$$t_c = \frac{2\pi - \beta}{\omega}$$

Average load voltage is given by

$$\begin{aligned} V_{dc} = V_{avg} &= \frac{1}{2\pi} \int_{\alpha}^{\beta} V_m \sin \omega t d(\omega t) \\ &= \frac{V_m}{2\pi} [-\cos \omega t]_{\alpha}^{\beta} \end{aligned}$$

$$V_o = V_{avg} = \frac{V_m}{2\pi} [\cos \alpha - \cos \beta]$$

$$\text{Average load current } I_o = \frac{V_m}{2\pi R} [\cos \alpha - \cos \beta]$$

$$\begin{aligned} \text{RMS load voltage } V_{o\gamma} &= \left[ \frac{1}{2\pi} \int_{\alpha}^{\beta} (V_m \sin \omega t)^2 d(\omega t) \right]^{\frac{1}{2}} \\ &= \frac{V_m}{2\pi} \left\{ \int_{\alpha}^{\beta} (1 - \cos 2\omega t) d\omega t \right\}^{\frac{1}{2}} \end{aligned}$$


$$= \frac{V_m}{2\sqrt{\pi}} \left[ (\beta - \alpha) - \left( \frac{\sin 2\omega t}{2} \right)_{\alpha}^{\beta} \right]^{\frac{1}{2}}$$

$$\therefore V_{o\gamma} = \frac{V_m}{2\sqrt{\pi}} \left[ (\beta - \alpha) - \frac{1}{2} (\sin 2\beta - \sin 2\alpha) \right]^{\frac{1}{2}}$$

# of half-wave circuit with RL load & with freewheeling
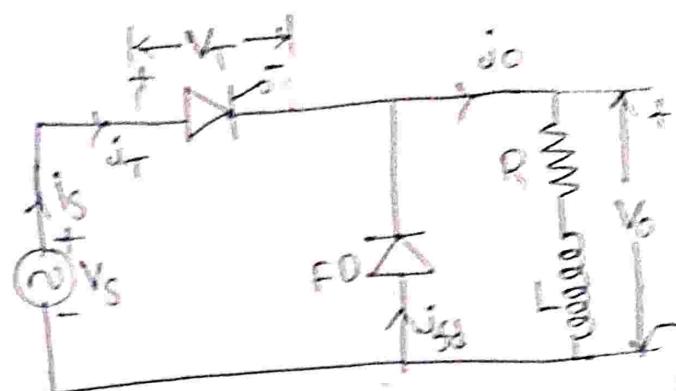
## Diode :-


1-Q half wave circuit with RL load with freewheeling diode as shown in fig.



" A freewheeling diode is also called by-pass or commutating diode.

At  $\omega t = 0$   $V_s$  is +ve,  
At some delay angle  $\alpha$ ,  
forward biased SCR  
triggered and  
Source Voltage  
appears across the  
load as  $V_0$ .

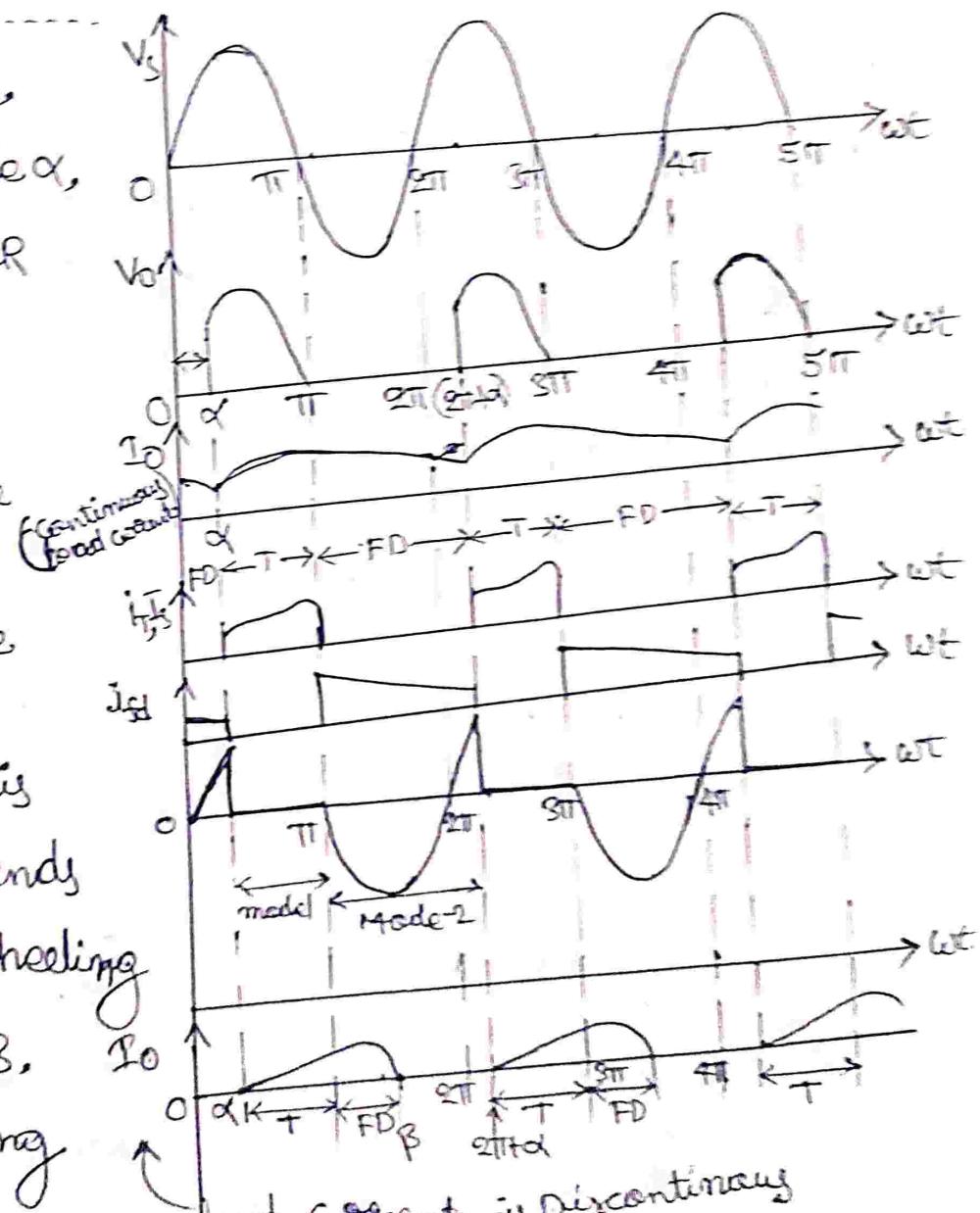At  $\omega t = \pi$  Source  
Voltage is zero  
and just after this  
instant, as  $V_s$  tends  
to reverse, Free-wheeling  
diode (FD) is F.B.  
through conducting  
SCR. as a result



Load current is discontinuous  
load current is immediately transferred from SCR to FD  
as  $V_s$  tends to reverse.

At the same time SCR is subjected to Reverse Voltage and zero current, it is turned off at  $wt = \pi$ . Ans

\* Assume that load current is continuous and  $I_0$  current does not decay to zero until the SCR is triggered again at  $(2\pi + \alpha)$ . Voltage drop across FD is taken almost zero, the load voltage  $V_0$  is therefore zero during freewheeling period.

Assume SCR is turn-off at  $wt = \pi$ , & reverse biased from  $\pi$  to  $2\pi$

$\therefore$  circuit turn-off time  $t_c = \frac{\pi}{\omega}$  Sec

$I_S$  &  $T$  are same as shown in fig

Mode 1 (Conduction)


~~OK~~  $wt \leq \pi$

$$V_0 = V_S$$

$$I_0 = \frac{V_0}{R}$$

$$V_T = V_S$$

SCR-ON

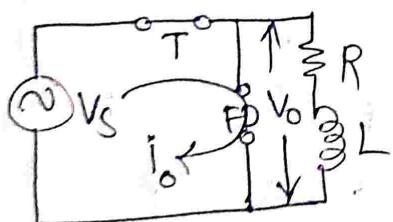

Voltage Eq.

$$V_m \sin wt = R i_0 + L \frac{di_0}{dt}$$

Sol. of above Eq.

$$i_0 = \frac{V_m}{Z} \sin(wt - \phi) + \left[ I_0 - \frac{V_m}{Z} \sin(\alpha - \phi) \right] e^{-\frac{R}{L}(t - \frac{\pi}{\omega})}$$

Mode-2 (Freewheeling)


$\pi \leq wt \leq 2\pi + \alpha$

SCR-OFF

$$V_0 = 0$$

$$I_0 = I_{fd}$$

$$V_T = V_S$$

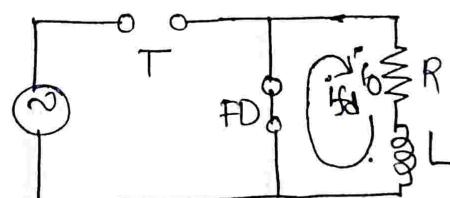

Voltage Eq.

$$0 = R i_0 + L \frac{di_0}{dt}$$

Sol. of above Eq.

$$\text{at } wt = \pi \quad i_0 = I_{01}$$

$$i_0 = I_{01} e^{-R_L(t - \frac{\pi}{\omega})}$$

Average load voltage  $V_o$  is given by

$$\begin{aligned} V_o &= \frac{1}{2\pi} \int_{\alpha}^{\pi} V_m \sin(\omega t) d(\omega t) \\ &= \frac{V_m}{2\pi} \int_{\alpha}^{\pi} \sin(\omega t) d(\omega t) \\ &= \frac{V_m}{2\pi} [\cos(\omega t)]_{\alpha}^{\pi} = \frac{V_m}{2\pi} [-\cos(\pi) + \cos(\alpha)] \end{aligned}$$

$$V_o = \frac{V_m}{2\pi} [1 + \cos(\alpha)] \rightarrow ①$$

$$\text{Average load current } I_o = \frac{V_o}{R} = \frac{V_m}{2\pi R} (1 + \cos(\alpha))$$

\* Load absorbs the power for  $\alpha$  to  $\pi$ , but for  $\pi$  to  $(2\pi + \alpha)$  energy stored in "L" is delivered to load "R" through the FD. Therefore power consumed by load is more.

∴ It can be concluded that power delivered to load for same firing angle is more when FD is used.

### \* Advantages of freewheeling Diode

- i) input P.F is improved
- ii) load current waveform is improved
- iii) as  $I_o$  is increases load performance is better
- iv) as energy stored in L is transferred to "R" during freewheeling period, overall converter "η" increases.
- v) FD prevents the load voltage " $V_o$ " from being negative.
- vi) with same firing angle the power delivered to load is increases with FD.

1-Ø half wave converter thus introduces a DC component into the supply line. This leads saturation of supply T/F and other difficulties (harmonics etc.)

This difficulties can be overcome with 1-Ø full wave circuits.

### \* Disadvantages of 1-Ø half wave converter:-

- 1-Ø half wave controlled rectifier gives
  - low DC op Voltage
  - low DC op power & lower efficiency
  - higher ripple voltage & ripple current
  - higher ripple factor
  - low Transformer utilization factor
  - Input Supply Current has a DC component, which can result in saturation of T/F core.

### < 1-Ø full wave controlled Rectifiers:-

It produces two pulse op across the load. So sometimes it is also called as "2-pulse Converter".

These are Various types

① 1-Ø full wave controlled Rectifier (Centred Tapped T/F)

② 1-Ø " " (Bridge Configuration)

ⓐ Half Controlled Bridge Converter (Semi Converter)

ⓑ Fully Controlled Bridge Converter (full Converter)


$\therefore$  1-Ø full converter:-

1-Ø fully controlled bridge circuit with R-load :-

The below fig shows, 1-Ø full wave

converter in bridge circuit with R-load.

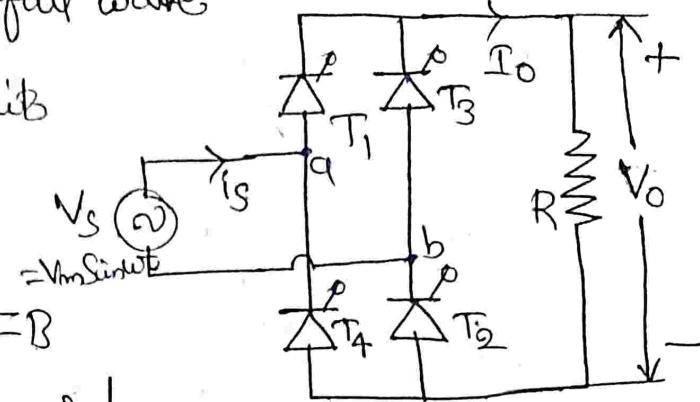During the HC  $T_1$  &  $T_2$  are FB  
but those 2-SCRs in forward  
Blocking mode.  $[0 \leq wt < \alpha, T_1 \& T_2 - OFF, V_o = I_o = 0]$



At  $wt = \alpha$ , both

$T_1$  &  $T_2$  triggered  
& turned on.

$$V_o = V_{m \sin \alpha}$$

$$I_o = V_o / R$$

$$V_{T_2} = V_{T_1} = 0$$

$\alpha \leq wt < \pi$

$T_1 \& T_2 - ON$

$$V_o = V_s$$

$$I_o = V_o / R$$

$$V_{T_1} = V_{T_2} = 0$$

at  $wt = \pi$

due to natural  
commutation

$T_1 \& T_2 - OFF$

+  $V_s - T_1 - R - T_2 - V_s$

During -ve Half Cycle  $T_3$  &  $T_4$  are in FBM

& at  $wt = \pi + \alpha$

$T_3 \& T_4$  are  
triggered & gets  
turned on.

$$V_o = V_{m \sin \alpha}$$

$$I_o = V_o / R$$

$$V_{T_3} = V_{T_4} = 0$$

$\pi + \alpha \leq wt < 2\pi$

$T_3 \& T_4 \Rightarrow ON$

$$V_o = V_s$$

$I_o - path$ !

$$V_s - T_3 - R - T_4 - V_s$$


$$V_{T_3} = V_{T_4} = 0$$

at  $wt = 2\pi$

due to  
natural  
commutation

$T_3 \& T_4$   
turned off.

\* Waveforms!

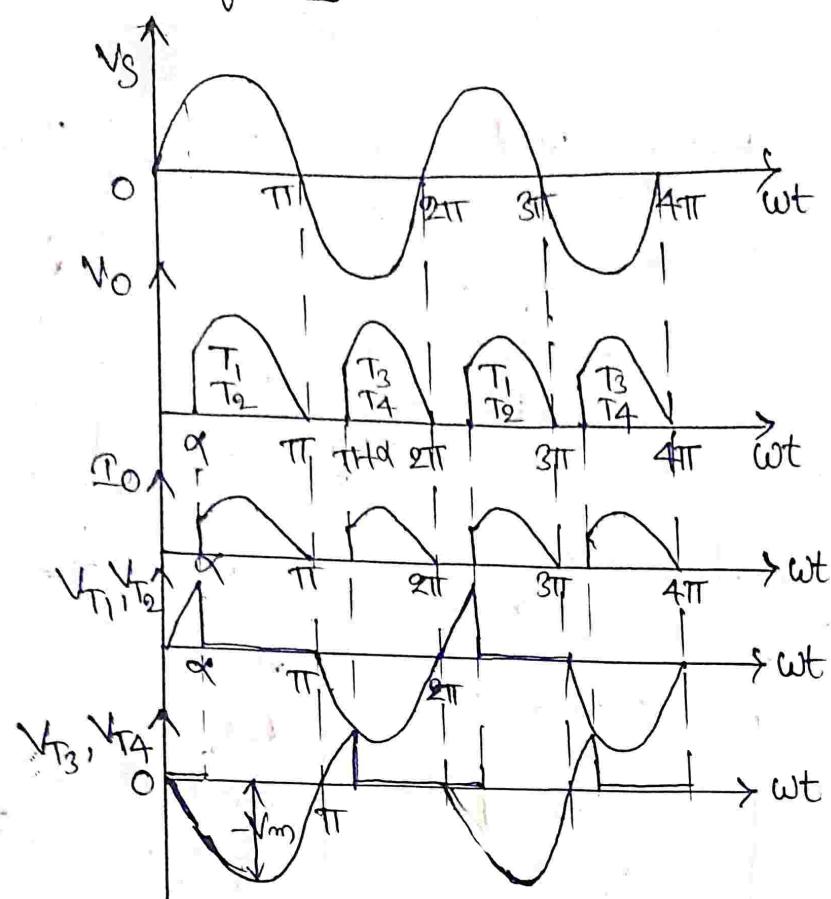

$$\text{Average O/p Voltage } V_{DC} = V_{avg} = \frac{1}{\pi} \int_{\alpha}^{\pi} V_m \sin \omega t d(\omega t)$$

$$V_{DC} = \frac{V_m}{\pi} \left[ -\cos \omega t \right]_{\alpha}^{\pi}$$

$$= \frac{V_m}{\pi} \left[ -\cos \pi + \cos \alpha \right]$$

$$V_{DC} = \frac{V_m}{\pi} [1 + \cos \alpha] \rightarrow ①$$

$$I_{DC} = \frac{V_{DC}}{R} = \frac{V_m}{\pi R} (1 + \cos \alpha) \rightarrow ②$$

RMS output voltage  $V_{rms} = \sqrt{\frac{1}{\pi} \int_{\alpha}^{\pi} (V_m \sin \omega t)^2 d(\omega t)}$

$$V_{rms} = \sqrt{\frac{V_m^2}{2\pi} \int_{\alpha}^{\pi} (1 - \cos 2\omega t) d(\omega t)}$$

$$V_{rms} = \frac{V_m}{\sqrt{2\pi}} \sqrt{(\pi - \alpha) + \frac{\sin 2\alpha}{2}} \rightarrow ③$$


# 1-φ fully controlled bridge converter with RL-load :-

The below fig shows the 1-φ 2-pulse or full converter with RL load.

$$V_{ab} = -V_{ba} = V_m \sin \omega t$$

During the H.C.  $T_1 \& T_2 \Rightarrow FB$  &  
 $T_3 \& T_4 \Rightarrow RB$

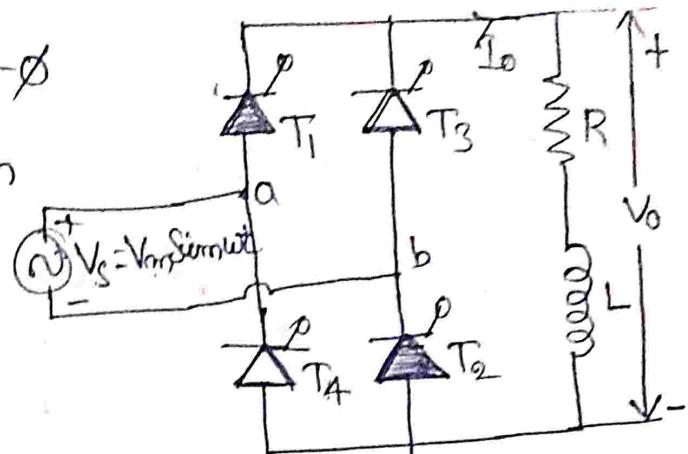During -ve H.C.  $T_3 \& T_4 \Rightarrow FB$  &  
 $T_1 \& T_2 \Rightarrow RB$ .



Assume that load inductance is larger enough and load current is being continuous. The waveforms of full converter in continuous conduction mode as follows.


① In continuous current conduction mode

$\beta \geq \pi + \alpha$ , it holds good.

$0 \leq wt < \alpha$   $T_3 \& T_4$  -on

&  $T_1 \& T_2$  are in FBM.

at  $wt = \alpha$   $T_1, T_2$  -on

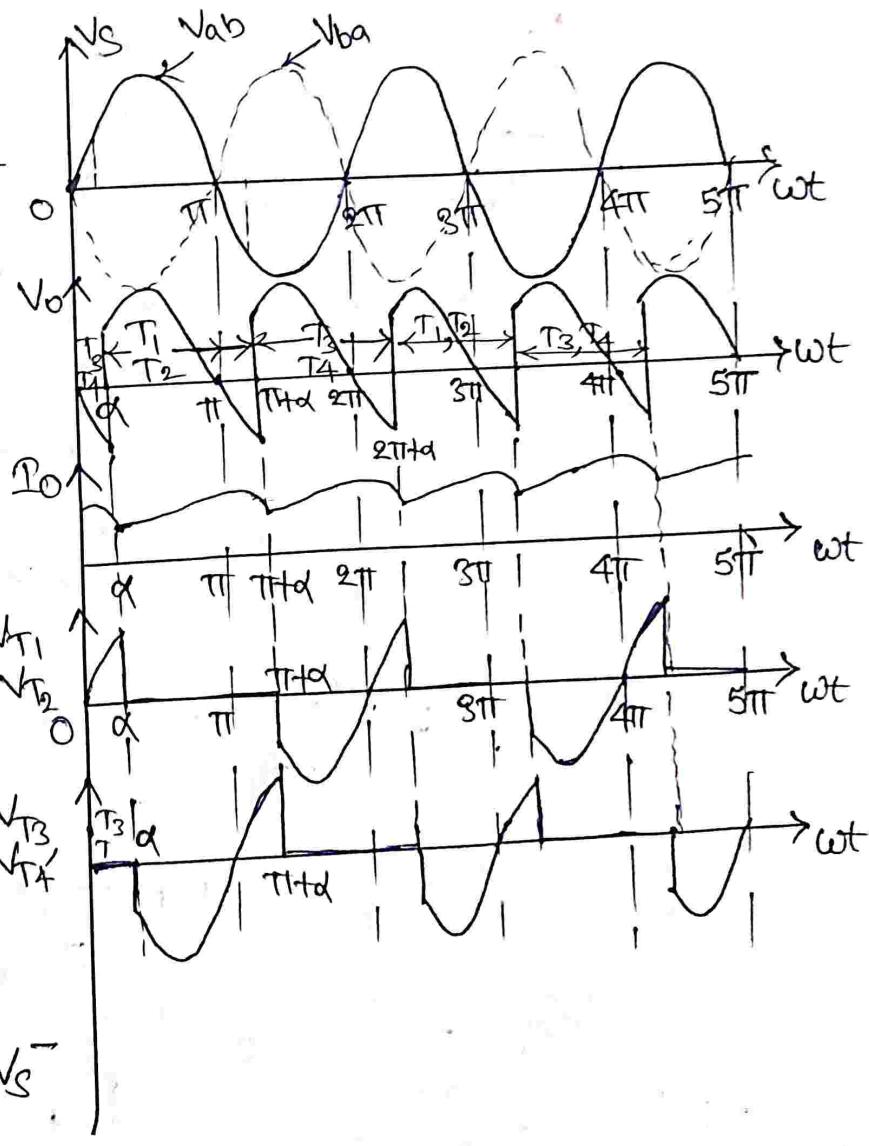

$\alpha \leq wt < \pi + \alpha$

$T_1, T_2$  -on

$T_3 \& T_4$  -off

$$V_o = V_s \quad V_{T1} = V_{T2} = 0$$

$I_o$ -path  $V_s^+ - T_1 - R - L - T_2 - V_s^-$

At  $\omega t = \pi + \alpha$   $T_1$  &  $T_2$  - turned OFF &  
 $T_3$  &  $T_4$  are gets triggered & turn-on.

$$V_o = V_S ; V_{T3} = V_{T4} = 0$$

$$\text{I}_o - \text{path} \Rightarrow V_S - T_3 - R - L - T_4 - V_S^+$$

Average o/p voltage is derived as follows

$$V_{DC} = \frac{1}{\pi} \int_{\alpha}^{\pi+\alpha} V_m \sin \omega t d(\omega t)$$

$$= \frac{V_m}{\pi} \left[ -\cos \omega t \right]_{\alpha}^{\pi+\alpha}$$

$$= \frac{V_m}{\pi} \left[ -\cos(\pi+\alpha) + \cos \alpha \right]$$

$$= \frac{V_m}{\pi} \left[ \cos \alpha + \cos \alpha \right]$$

$V_{DC} = \frac{2V_m \cos \alpha}{\pi} \rightarrow ①$

$$I_{DC} = V_{DC}/R = \frac{2V_m \cos \alpha}{\pi R} \rightarrow ②$$

Rms Value of O/p Voltage is derived as

$$V_{o rms} = \sqrt{\frac{1}{\pi} \int_{\alpha}^{\pi+\alpha} (V_m \sin \omega t)^2 d(\omega t)}$$

$$= \sqrt{\frac{V_m^2}{2\pi} \int_{\alpha}^{\pi+\alpha} (1 - \cos 2\omega t) d(\omega t)}^{\frac{1}{2}}$$

$$= \frac{V_m}{\sqrt{2\pi}} \left[ \omega t - \frac{\sin 2\omega t}{2} \right]_{\alpha}^{\pi+\alpha}^{\frac{1}{2}}$$

$$= \frac{V_m}{\sqrt{2\pi}} \left\{ (\pi + \alpha - \alpha) - \frac{(\sin(2\alpha + 2\pi) - \sin 2\alpha)}{2} \right\}^{\frac{1}{2}}$$


$$V_{o rms} = \frac{V_m}{\sqrt{2\pi}} [\sqrt{\pi}] = \frac{V_m}{\sqrt{2}} \rightarrow ③$$

$$\text{i/p P.f.} = \frac{V_{o rms}}{V_{s rms}} = 1$$

⑥ Discontinuous Current Conduction mode:-

$\beta < \pi + \alpha$ , it holds good (L is small)

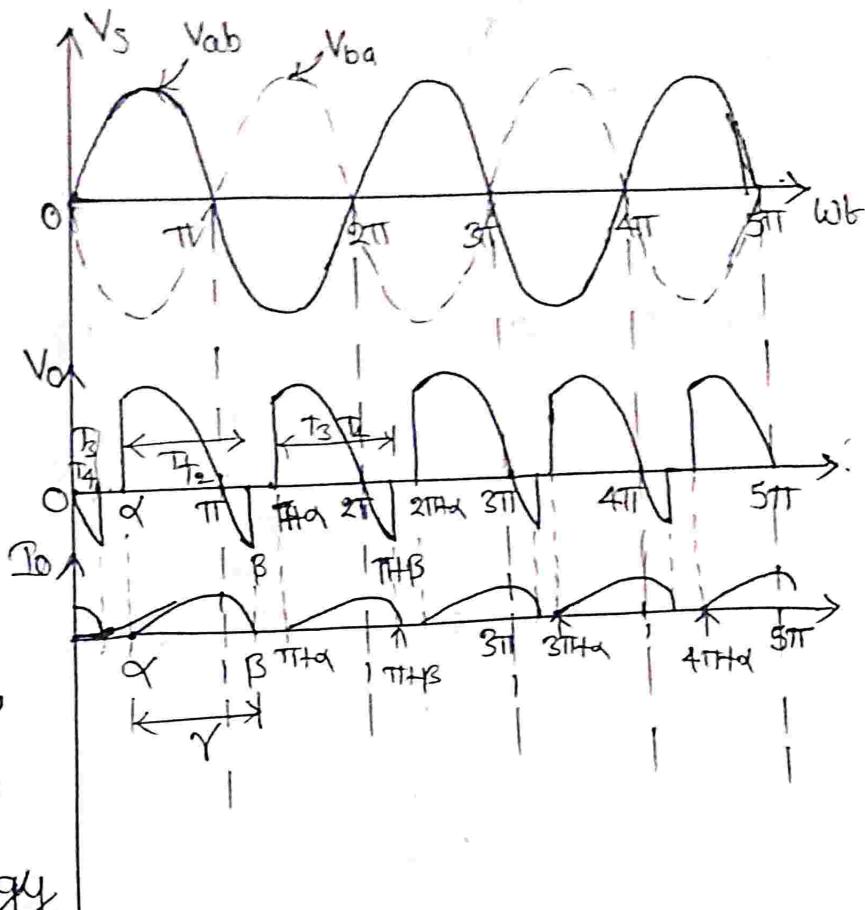In discontinuous current conduction mode load current is made to zero before the  $\pi + \alpha$  & ( $\beta < \pi + \alpha$ ) at extinction angle "B" after this instant inductor "L" will not have a sufficient energy to drive the load current.



$\therefore T_1 \& T_2$  Conducts up to  $\beta$  only

$\beta \leq wt \leq \pi + \alpha$  all the SCRs are OFF state. during this period  $V_o = 0$  &  $I_o = 0$

turn off time period of thyristors  $T_1 \& T_2, T_3 \& T_4$  are increase from  $\frac{\pi - \alpha}{\omega}$  to  $\frac{\pi + \alpha - \beta}{\omega}$ .

Average o/p Voltage is derived as

$$V_{DC} = V_{oavg} = \frac{1}{\pi} \int_{\alpha}^{\beta} V_m \sin \omega t dt$$

$$= \frac{V_m}{\pi} [-\cos \omega t]_{\alpha}^{\beta}$$

$$V_{DC} = \frac{V_m}{\pi} [-\cos\beta + \cos\alpha]$$

$$\therefore V_{DC} = \frac{V_m}{\pi} [\cos\alpha - \cos\beta]$$

$$I_{DC} = \frac{V_{DC}}{R} = \frac{V_m}{\pi R} [\cos\alpha - \cos\beta]$$

RMS value of o/p voltage is

$$V_{o rms} = \sqrt{\frac{1}{\pi} \int_{\alpha}^{\beta} (V_m \sin \omega t)^2 d(\omega t)}$$

$$= \sqrt{\frac{V_m^2}{2\pi} \int_{\alpha}^{\beta} (1 - \cos 2\omega t) d(\omega t)}$$

$$= \frac{V_m}{\sqrt{2\pi}} \sqrt{\left[ \omega t - \frac{\sin 2\omega t}{2} \right]_{\alpha}^{\beta}}$$

$$= \frac{V_m}{\sqrt{2\pi}} \left[ (\beta - \alpha) - \frac{(\sin 2\beta - \sin 2\alpha)}{2} \right]^{\frac{1}{2}}$$

$$V_{o rms} = \frac{V_m}{\sqrt{2\pi}} \left\{ (\beta - \alpha) + \frac{\sin 2\alpha - \sin 2\beta}{2} \right\}^{\frac{1}{2}}$$

$$\text{i/p p.f.} = \frac{V_{o rms}}{V_{s rms}}$$


$$\text{i/p p.f.} = \frac{1}{\sqrt{\pi}} \left\{ (\beta - \alpha) + \frac{\sin 2\alpha - \sin 2\beta}{2} \right\}^{\frac{1}{2}}$$

- \* Average thyristor current  $(I_T)_{avg} = \frac{I_{DC}}{2}$
  - \* RMS value of thyristor current  $(I_T)_{rms} = \frac{I_{o rms}}{\sqrt{2}}$
- } full converter

## -Q full converter with RLE load:-

The below fig shows the full converter with RLE-load or motor load.

$$V_{ab} = -V_{ba} = V_m \sin \omega t$$

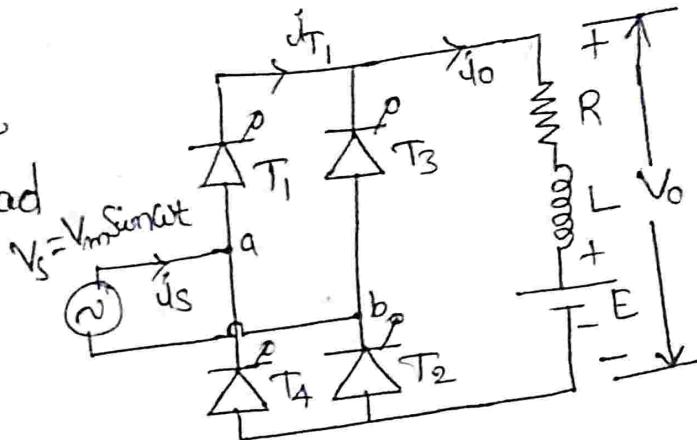

$T_1, T_2$  pair simultaneously triggered and  $\pi$  radians latter pair  $T_3, T_4$  is gated together.

Load current  $I_o$  is assumed to be continuous the waveforms as follows

at  $\omega t = \alpha$   $T_1, T_2$  triggered

$0 \leq \omega t < \alpha$   $T_1, T_2 + T_3$

$T_3, T_4$  are in conduction

at  $\omega t = \alpha$   $T_1, T_2$  are turn-on

&  $T_3, T_4$  are turned-off

with reverse voltage of

$V_m \sin \alpha$ .


$\alpha \leq \omega t \leq \pi + \alpha$   $T_1, T_2$  - on

$$V_o = V_s, I_o \text{ path}$$

$$V_s^+ - T_1 - R - L - E - T_2 - V_s^-$$

$\omega t = \pi + \alpha$   $T_3, T_4$  are gated & turned on.

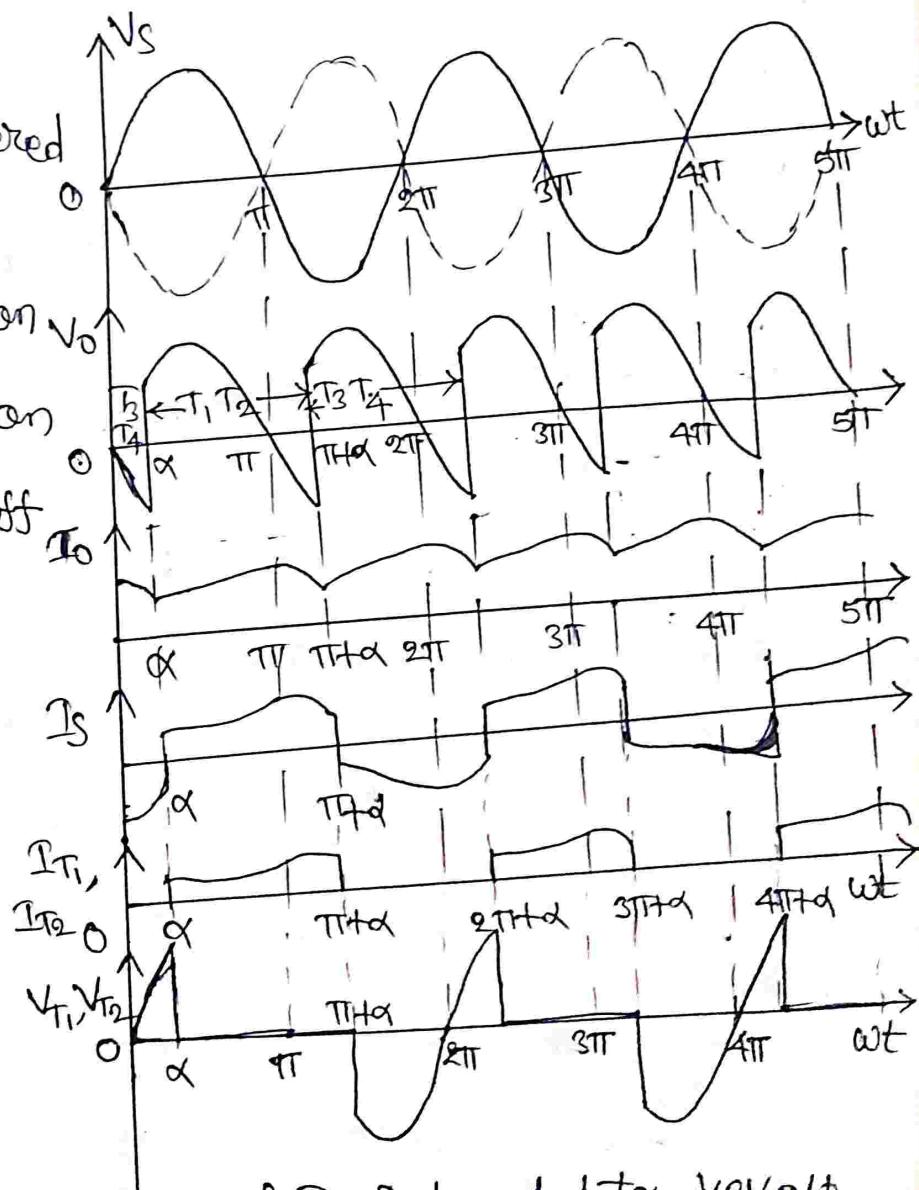& already conducting thyristors  $T_1, T_2$  subjected to -ve voltage turned-off naturally.



$\pi + \alpha \leq wt < 2\pi + \alpha$     $T_3 \& T_4$  - On    $T_1 \& T_2$  - OFF

$$V_o = V_s \quad I_o \text{ path} \quad V_s = T_3 - R - L - E - T_4 + V_s^+ \quad 5$$

Average O/P Voltage  $V_{dc} = \frac{1}{\pi} \int_{\alpha}^{\pi+\alpha} V_m \sin \omega t d(\omega t)$

$$V_{dc} = \frac{2V_m}{\pi} \cos \alpha$$

$$\therefore V_{dc} = I_{dc} R + E$$

$$I_{dc} = \left\{ \frac{2V_m}{\pi R} \cos \alpha - E \right\} / R$$


$$V_{o rms} = \frac{1}{\pi} \int_{\alpha}^{\pi+\alpha} (V_m \sin \omega t)^2 d\omega t = \frac{V_m}{\sqrt{2}}$$

### Inverter mode of operation:-

If firing angle  $\alpha > 90^\circ$ , O/P

Voltage  $V_{dc}$  is negative

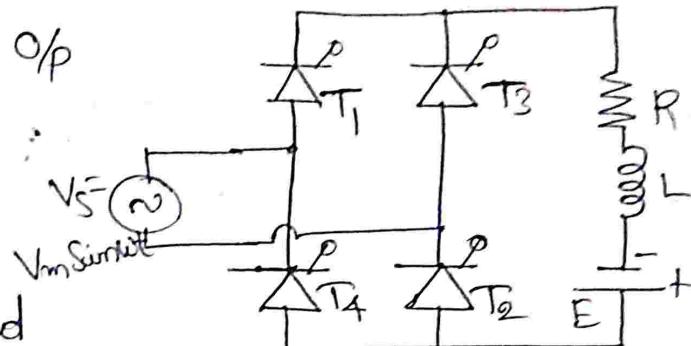As  $V_o$  is -ve, the load circuit emf  $E$  is reversed as shown in below fig.



\* With  $\alpha > 90^\circ$  then this DC source  $E$  will feed power back to AC source. This mode of operation of full converter is known as "Inverter operation".

or full converter with  $\alpha > 90^\circ$  is called line-commutated inverter.

\* The Voltage Source on the DC load side may be a battery, a photovoltaic source, a DC voltage produced by wind-generator system or counter emf of DC motor.


$0 \leq \omega t < \alpha$

$V_S$  is +ve but  
 $I_S$  is -ve,

power therefore, flows  
from DC source to  
AC source.

$\alpha \leq \omega t < \pi$

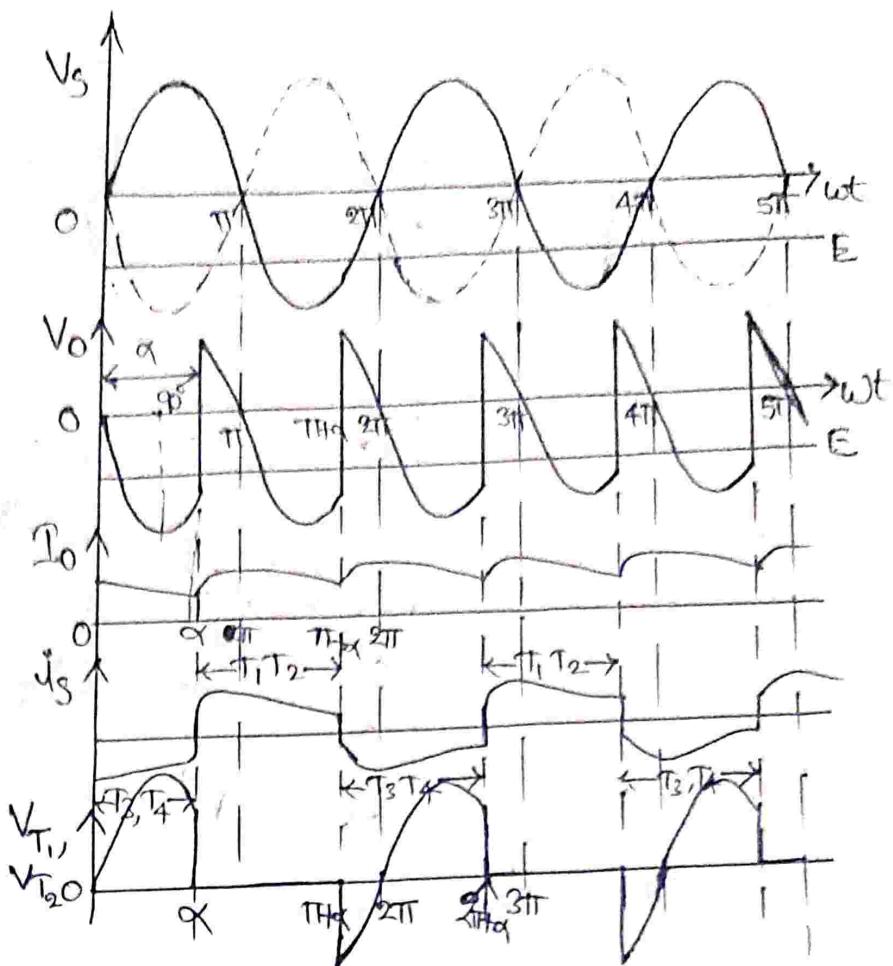both  $V_S$  &  $I_S$  are +ve,  
power therefore, flows  
from AC source to  
DC source.




But the net power flow is from DC source to AC source  
because  $(\pi - \alpha) < \alpha$  (from above fig)

\* Both in converter mode ( $0^\circ \leq \alpha \leq 90^\circ$ ) and inverter  
mode ( $90^\circ < \alpha \leq 180^\circ$ ), thyristors must be FB and  
current through SCRs must flow in same direction.  
as these are unidirectional devices.

\* 1-φ full converter with Discontinuous current :-

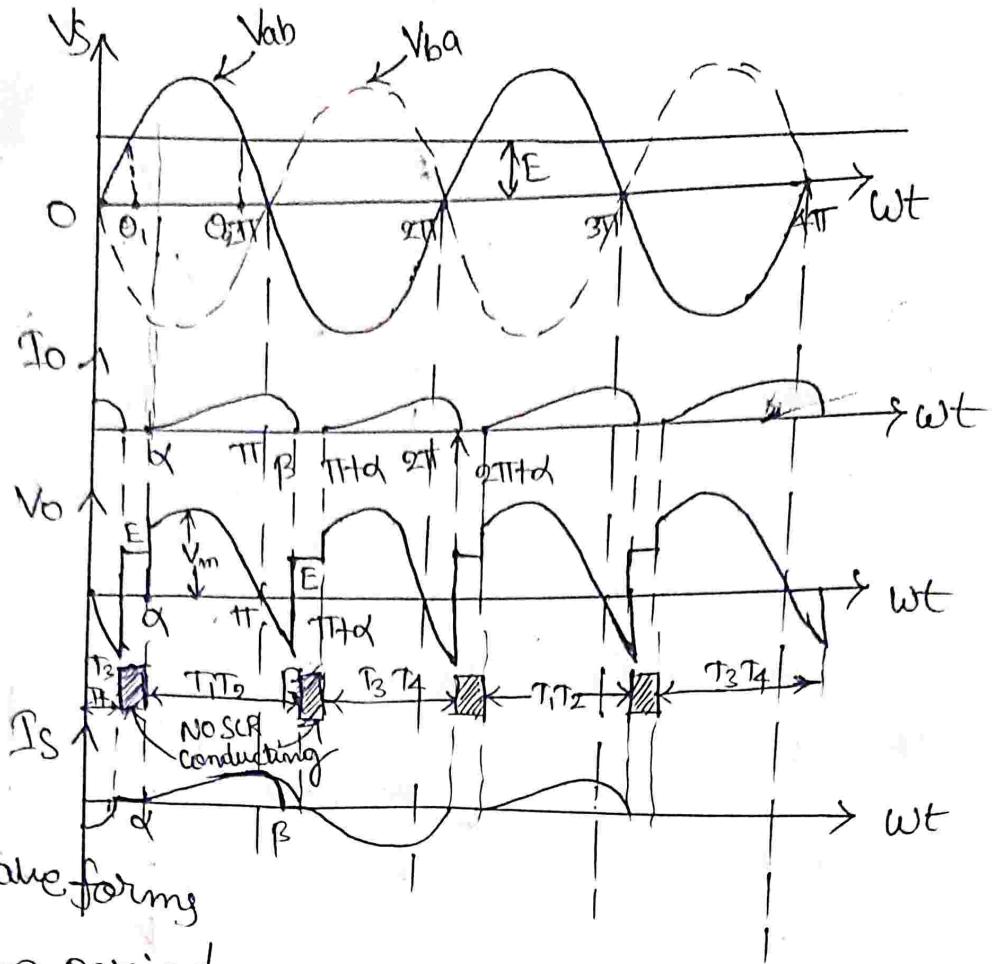The load current being discontinuous because of  
either small inductance or  $\beta < \pi + \alpha$ . or inductor  
should not have a sufficient energy to drive the  
load. During this O/P wave forms are shown below.



from above wave forming

- (i) Conduction period,  $\alpha \leq wt < \beta$   $T_1, T_2$  conduct &  $V_o = V_g$   
& also  $(\pi + \alpha) \leq wt < (\pi + \beta)$   $T_3, T_4$  conducts and  $V_o = V_g$
- (ii) Idle period  $\beta \leq wt < \pi + \alpha$ , no circuit element conducts  
and  $V_o = E$  &  $I_o = 0$

When the Supply voltage is less than the DC Voltage "E".  
in the circuits the SCRs are in reverse biasing condition. hence thyristors cannot conduct when the supply voltage less than DC Bus voltage "E".

Due to this firing angle control is limited to  
firing angle  $\theta_1$  &  $\theta_2$  as shown in wave forms

$$V_{m \sin \alpha} = E$$

$$\therefore \alpha = \sin^{-1} \left( \frac{E}{V_m} \right) = \theta_1$$

$$\therefore \theta_2 = \pi - \theta_1$$

Average O/P Voltage is derived as

$$\begin{aligned}
 V_{\text{Oavg}} &= V_{\text{DC}} = \frac{1}{\pi} \left[ \int_{\alpha}^{\beta} V_m \sin \omega t dt + \int_{\beta}^{\pi+\alpha} E d(\omega t) \right] \\
 &= \frac{1}{\pi} \left[ V_m \left[ -\cos \omega t \right]_{\alpha}^{\beta} + E \left[ \omega t \right]_{\beta}^{\pi+\alpha} \right] \\
 &= \frac{V_m}{\pi} [\cos \alpha - \cos \beta] + \frac{E}{\pi} \left[ \pi + \alpha - \beta \right] \\
 \boxed{V_{\text{Oavg}} = \frac{V_m}{\pi} [\cos \alpha - \cos \beta] + E \left[ 1 + \frac{\alpha - \beta}{\pi} \right]} \rightarrow ①
 \end{aligned}$$

for  $i_{\text{Oavg}}$ .

$$V_{\text{DC}} = i_o R + E$$

$$\boxed{i_{\text{DC}} = i_o = \frac{V_{\text{DC}} - E}{R}} \rightarrow ②$$

A rms value of output voltage is derived as

$$\begin{aligned}
 V_{\text{Orms}} &= \sqrt{\frac{1}{\pi} \int_{\alpha}^{\beta} (V_m \sin \omega t)^2 d(\omega t) + \int_{\beta}^{\pi+\alpha} E^2 d(\omega t)} \\
 &= \sqrt{\frac{V_m^2}{2\pi} \left( \left[ 1 - \cos 2\omega t \right]_{\alpha}^{\beta} \right) + \frac{E^2}{\pi} \left[ \omega t \right]_{\beta}^{\pi+\alpha}} \\
 &= \sqrt{\frac{V_m^2}{2\pi} \left[ (\beta - \alpha) + \frac{\sin 2\alpha - \sin 2\beta}{2} \right] + \frac{E^2}{\pi} \left[ \pi + \alpha - \beta \right]} \\
 V_{\text{Orms}} &= \sqrt{\frac{V_m^2}{2\pi} \left[ (\beta - \alpha) + \frac{\sin 2\alpha - \sin 2\beta}{2} \right] + E^2 \left[ 1 - \frac{\alpha - \beta}{\pi} \right]} \rightarrow ③
 \end{aligned}$$


### Effect of Source Inductance :-

If the source having some Impedance and it is taken as pure inductive, source source resistance is very less when compared to inductor.


The source inductance causes the both incoming and outgoing thyristors to conduct together.
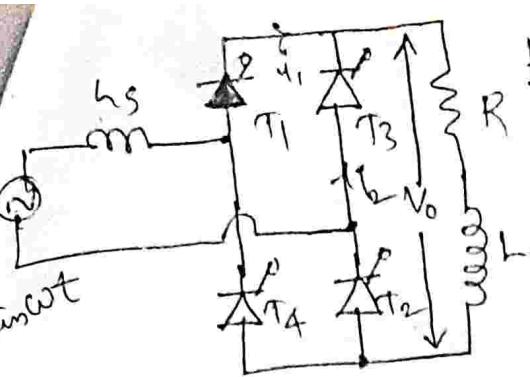
### \* Overlap angle or commutation angle $\Pi$ :-

The angular period during which both the incoming & outgoing SCRs conducting together. Due to this  
→ reduction in  $V_{avg}$ , modified performance characteristics  
→ Distorted V, I waveforms



## Effect of Source Inductance

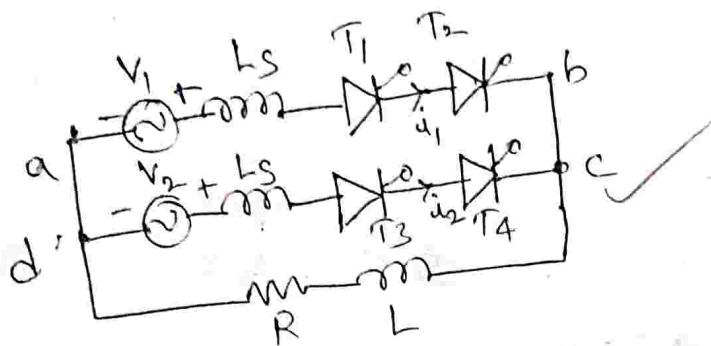

when  $T_1, T_2$  are triggered at  $\omega t = \alpha$   
commutation of  $T_3, T_4$  begins

Because of Source Inductance  $L_s$

the current through outgoing devices  $T_3, T_4$ , decreases gradually to zero from its initial value of  $I_0$ .

whereas in Incomming SCRs  $T_1, T_2$  the current builds up gradually from zero to full value of load current  $I_0$ .

During the commutation of  $T_1, T_2$  &  $T_3, T_4$  i.e. during

the overlap angle "M"

KVL for the loop abcda

$$V_1 - L_s \frac{di_1}{dt} = V_2 - L_s \frac{di_2}{dt}$$

$$V_1 - V_2 = L_s \left( \frac{di_1}{dt} - \frac{di_2}{dt} \right)$$


$$V_1 = V_m \sin \omega t \text{ then}$$

$$V_2 = -V_m \sin \omega t$$

$$\text{i.e. } L_s \left( \frac{di_1}{dt} - \frac{di_2}{dt} \right) = 2V_m \sin \omega t$$

The load current is assumed to be constant through

$$i_1 + i_2 = I_0$$

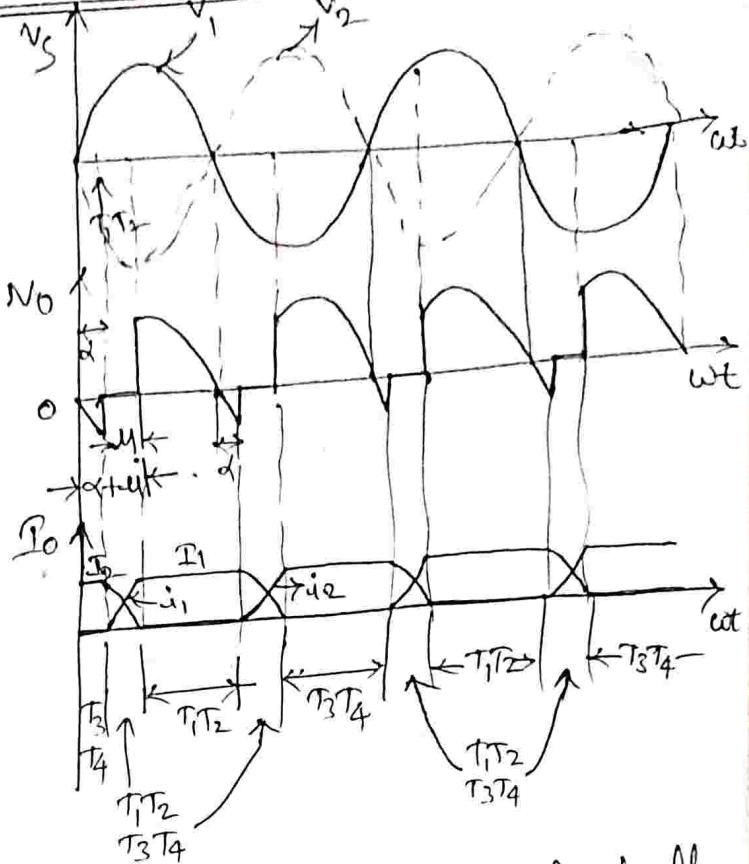

\* M - commutation angle (°)  
overlap angle

$$\frac{di_1}{dt} + \frac{di_2}{dt} = 0 \rightarrow ①$$

$$\frac{di_1}{dt} - \frac{di_2}{dt} = \frac{2V_m \sin \omega t}{L_S} \rightarrow ②$$

$$\frac{2di_1}{dt} = \frac{2V_m \sin \omega t}{L_S}$$

$$\frac{di_1}{dt} = \frac{V_m \sin \omega t}{L_S} \rightarrow ③$$

load currents through  $T_1$  &  $T_2$  at  $\omega t = \alpha$   $I_0 = i_1 = 0$

at  $\omega t = \alpha + \mu$   $i_1 = I_0$

from Eq ③

$$\int_{\alpha}^{I_0} di_1 = \frac{V_m}{L_S} \int_{\alpha/\omega}^{(\alpha+\mu)/\omega} \sin \omega t d(\omega t)$$

$$I_0 = \frac{V_m}{\omega L_S} [\cos \alpha - \cos (\alpha + \mu)] \rightarrow ④$$

$V_o = 0$  from  $\omega t = \alpha$  to  $\omega t = \alpha + \mu$

$$\begin{aligned} V_{dc} = V_{oavg} &= \frac{1}{\pi} \int_{\alpha+\mu}^{\pi+\alpha} V_m \sin \omega t d(\omega t) \\ &= \frac{V_m}{\pi} [\cos \omega t]_{\alpha+\mu}^{\pi+\alpha} \end{aligned}$$

$$V_o = \frac{V_m}{\pi} [\cos \alpha + \cos (\alpha + \mu)]$$

from Eq ④

$$\frac{T_0 \omega L_S}{V_m} = \cos \alpha - \cos (\alpha + \mu)$$

$$\cos (\alpha + \mu) = \cos \alpha - \frac{\omega L_S T_0}{V_m} \rightarrow ⑤$$

Substitute Eq. ⑤ in  $\underline{V_o}$  then

$$V_o = \frac{V_m}{\pi} [\cos \alpha + \cos \alpha - \frac{\omega L_S T_0}{V_m}]$$

$$* V_o = \frac{2V_m}{\pi} \cos \alpha - \frac{\omega L_S T_0}{\pi} * \rightarrow ⑥$$

from Eq (4)

$$I_0 = \frac{V_m}{\omega L_s} [\cos \alpha - \cos(\alpha + \mu)]$$

$$\frac{I_0 \omega L_s}{V_m} + \cos(\alpha + \mu) = \cos \alpha$$


Sub "cos \alpha" in Eq (6) then

$$V_o = \frac{2V_m}{\pi} \left[ \frac{\omega L_s I_0}{V_m} + \cos(\alpha + \mu) \right] - \frac{\omega L_s I_0}{\pi}$$

$$= \frac{2 \omega L_s}{\pi} I_0 + \frac{2V_m}{\pi} \cos(\alpha + \mu) - \frac{\omega L_s I_0}{\pi}$$

\*  $V_o = \frac{2V_m}{\pi} \cos(\alpha + \mu) + \frac{\omega L_s}{\pi} I_0$  \*

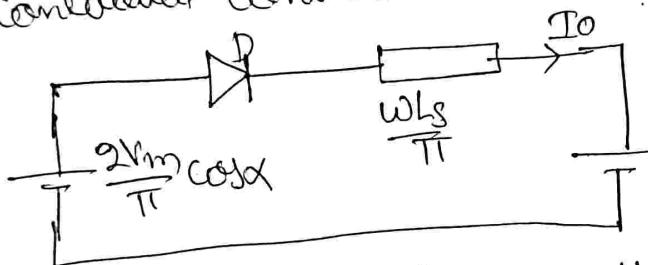from Eq (6) A DC Equivalent circuit for two-pulse 1-φ fully controlled converter can be drawn as



\* Diode "D" indicates that load current is unidirectional.


In 1-φ full converter as long as  $\mu < \pi$

$$V_o = \frac{2V_m}{\pi} \cos \alpha - \frac{\omega L_s I_0}{\pi} = \frac{2V_m}{\pi} \cos \alpha - 2f L_s I_0$$

when  $\mu = \pi$  the load will be permanently short circuited by SCR, and o/p voltage will be zero. because the overlap angle, all SCR's will be conducting

$$V_o = \frac{V_m}{\pi} (\cos \alpha + \cos(\alpha + \mu)) = \frac{V_m}{\pi} (\cos \alpha + \cos(\pi + \alpha))$$

$\underset{= 0}{\cancel{\cos \alpha}}$

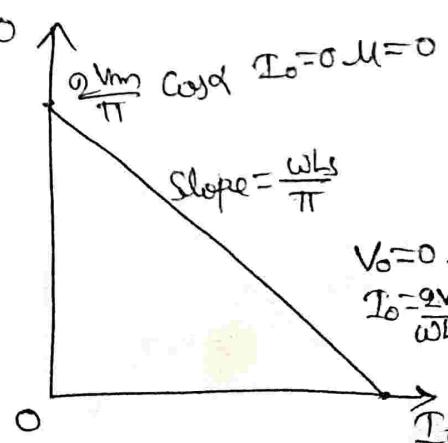

If  $\alpha = 0$  o/p voltage can be controlled over  $\mu < \alpha < 180^\circ$  and also max. firing angle can be "180° - \mu".

Harmonic factor or Total Harmonic Distortion  
HF or THD is defined as follows

$$HF = THD = \sqrt{\left(\frac{1}{CDF}\right)^2 - 1}$$

CDF = Current Distortion factor =  $\frac{I_{S1}}{I_S}$   
where

$I_{S1}$  - RMS value of fundamental current

$I_S$  - RMS value of total i/p current

$$\therefore THD = \sqrt{\left(\frac{I_S}{I_{S1}}\right)^2 - 1}$$

$$* \boxed{i/p P.F = CDF \times DDF} *$$

$$i/p P.F = \frac{I_{S1}}{I_S} \times \cos \alpha$$

## Performance factors of Line commutated Converters

### Input Displacement angle ( $\phi$ ) :-

It is defined as the angular displacement b/w the fundamental component of the a.c line current and the associated line to neutral voltage.

The fundamental component is either in phase or lags behind the voltage by an angle which depends upon the fixing angle

### ② Input Displacement factor ( $\cos\phi$ ) :-

The Input Displacement factor  $\cos\phi$ , is defined as the cosine of the input displacement angle or " $\cos\alpha$ ".

### ③ Input power Factor (PF) :-

The input P.f is defined as the ratio of the total mean input power to the total RMS input VA (volt Amperes). Since only the fundamental component contributes the mean input power,

$$\text{The P.f may be defined as} = \frac{V_1 I_1 \cos\phi}{V_{s\text{rms}} I_{s\text{rms}}}$$

where  $V_1 = V_{s\text{rms}}$

$I_1$  - fundamental component of Supply current

$\phi$  - Displacement angle

$$\therefore \text{Input P.f} = \frac{\text{power delivered to load}}{\text{Input VA}}$$

### ④ DC Voltage Ratio ( $\gamma$ )

It is defined as the ratio of the mean DC terminal voltage at a given fixing angle  $\alpha$ , to the max. possible D.C terminal voltage (i.e  $V_o$  at  $\alpha=0$ )

## ⑤ Input current distortion Factor:-

The Distortion factor of the current in a given input line is defined as ratio of the RMS amplitude of the fundamental component, to the total RMS amplitude.

## ⑥ Input Harmonic factor ( $I_H$ ):-

The input Harmonic factor is defined as the ratio of the total harmonic content to the fundamental Component

$$I_H = \frac{\sqrt{I_{\text{rms}}^2 - I_1^2}}{I_1}$$

## ⑦ Form factor:-(FF)

It is defined as the ratio of output RMS voltage to the DC voltage.

$$\text{form factor of voltage} = \frac{V_{\text{rms}}}{V_{\text{DC}}} \quad (\text{or}) \quad \frac{V_{\text{rms}}}{V_{\text{avg}}}$$

$$\text{Form factor of current} = \frac{I_{\text{rms}}}{I_{\text{dc}}} \quad (\text{or}) \quad \frac{I_{\text{rms}}}{I_{\text{avg}}}$$

## ⑧ Voltage Ripple factor:-( $K_V$ )

It is Defined as the ratio of the net harmonic content of the o/p voltage to the average o/p voltage

$$K_V = \sqrt{\frac{V_{\text{rms}}^2 - V_{\text{dc}}^2}{V_{\text{dc}}^2}} \Rightarrow \sqrt{\left(\frac{V_{\text{rms}}}{V_{\text{avg}}}\right)^2 - \frac{V_{\text{avg}}^2}{V_{\text{avg}}^2}}$$

$$\therefore K_V = \sqrt{(F.F)_{\text{voltage}}^2 - 1}$$

## ⑨ Current Ripple factor ( $K_I$ ):- It is defined as the ratio of net harmonic content of o/p current to the average output current

$$K_I = \frac{\sqrt{I_{\text{rms}}^2 - I_{\text{dc}}^2}}{I_{\text{dc}}} \quad (\text{or}) \quad K_I = \sqrt{(F.F)_{\text{current}}^2 - 1}$$

## True power Input ( $P_T$ ):-

It can be defined as

$P_T = \text{RMS line voltage} \times \text{RMS fundamental component}$   
of current  $\times$  Displacement factor

$$P_T = V_{\text{rms}} \times I_1 \times \cos \alpha$$

## ⑪ Reactive power Input:-

$$Q_T = V_{\text{rms}} \times I_1 \sin \alpha$$

## ⑫ Rectification efficiency :- ( $\eta$ )

It is defined as the ratio of DC power delivered to the load to Total ac input power.

$$\text{i.e. Rectification efficiency } \eta = \frac{P_{\text{dc}}}{P_{\text{ac}}} \quad \left. \begin{array}{l} \text{As } P_{\text{ac}} \text{ is AC output power } \\ \text{power } \frac{V_{\text{rms}}^2}{R} \end{array} \right\}$$

## ⑬ peak Inverse voltage (PIV)

Source.  
the maximum possible reverse voltage which is subjected to the SCRs in Reverse bias condition to turn-off it naturally by the source

for mid point configuration (M-2)  $\Rightarrow PIV = 2V_m$   
Bridge "  $PIV = V_m$

## ⑭ Transformer utilization factor (TUF):-

If  $V_s, I_s$  are the RMS voltage and RMS currents of the Secondary winding of input Transformer. Then TUF

is defined as

$$TUF = \frac{P_{\text{dc}}}{V_{S_{\text{rms}}} I_{S_{\text{rms}}}} = \frac{V_{\text{odc}} I_{\text{odc}}}{V_{S_{\text{rms}}} I_{S_{\text{rms}}}}$$

$$\therefore TUF = \frac{P_{\text{dc}}}{\text{VA rating of T/F}}$$

- ① A  $1\phi$  T/F with secondary voltage of 230V  $f=50\text{Hz}$ , delivers power to load  $R=10\Omega$  through half wave contd. rectifier ckt for a fixing angle delay of  $60^\circ$  Determine  
 (i) Rectifier efficiency (ii) form factor (iii) voltage ripple factor  
 (iv) T/F utilization factor (TUF) (v) PIV of Thyristor.

$$V_S \text{ rms} = 230V$$

$$V_m = V_S \text{ rms} \times \sqrt{2} = 230 \times \sqrt{2}$$

$$= 325.26 \text{ V}$$



$$R = 10\Omega$$

$$\alpha = 60^\circ$$

$$V_{dc} = \frac{V_m}{2\pi} (1 + \cos \alpha)$$

$$= \frac{230 \times \sqrt{2}}{2\pi} (1 + \cos 60^\circ)$$
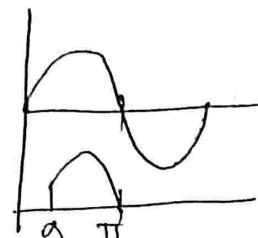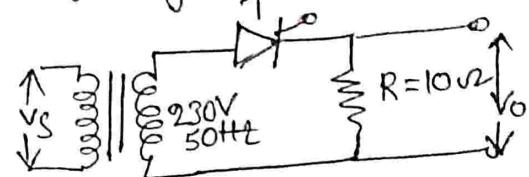
$$V_{dc} = \frac{2\pi}{77.65} \text{ V}$$



$$V_o = \frac{V_m}{2\pi} (1 + \cos \alpha)$$

(i) Rectifier efficiency =  $\frac{P_{dc}}{P_{ac}} = \frac{V_{dc} \times I_{dc}}{V_{S \text{ rms}} \times I_{S \text{ rms}}}$

$$I_{dc} = \frac{V_{dc}}{R} = \frac{77.65}{10} = 7.765 \text{ A}$$

$$I_{S \text{ rms}} = \frac{V_{S \text{ rms}}}{R} = \frac{V_m}{R \cdot 2\sqrt{\pi}} \left\{ (\pi - \alpha) + \frac{\sin 2\alpha}{2} \right\}^{\frac{1}{2}}$$

$$= \frac{230 \times \sqrt{2}}{10 \times 2 \times \sqrt{\pi}} \sqrt{\left\{ (\pi - \frac{\pi}{3}) + \frac{\sin (2 \times 60^\circ)}{2} \right\}^2}$$

$$I_{S \text{ rms}} = 14.58 \text{ A} \quad \& \quad I_{S \text{ rms}} = I_{S \text{ rms}}$$

$$\text{Rectifier efficiency } (\eta) = \frac{77.65 \times 7.765}{(I_{S \text{ rms}}^2 R)} \times 100 = \frac{603.18}{2127.89}$$

$$\eta = 28.33 \%$$

~~Q.E.D.~~  
Contd.

$$\text{Form factor} = \frac{V_{\text{rms}}}{V_{\text{dc}}} = \frac{145.8}{77.65} = 1.877$$

(iii) Voltage Ripple factor  $k_V = \sqrt{(T^2 - 1)}$

$$= \sqrt{(1.877)^2 - 1}$$

$$= \underline{1.589}$$

(iv) TUF =  $\frac{P_{\text{DC}}}{V_S I_S} = \frac{V_{\text{dc}} I_{\text{dc}}}{V_{S\text{ rms}} \times I_{S\text{ rms}}} = \frac{77.65 \times 7.765}{145.8 \times 14.58}$

~~Ans~~

$$\text{TUF} = 0.2836$$

(v) PIV = peak reverse voltage on Secondary Side of i/p TA  
 $= V_m = 230 \times \sqrt{2} = \underline{325.26} \text{ V}$

(2012)

Ans to Q1 E1

Set-2  
 Q. A/B  
 ③ A 1-φ fully controlled bridge circuit is used for obtaining a regulated DC o/p voltage. The RMS value of the ac i/p voltage is 230V. and the firing angle is  $\alpha = \frac{\pi}{3} = 60^\circ$ , so that the load current is 4A calculate  
 (i) The DC o/p voltage  
 (ii) Active and Reactive power i/p.

$$V_{S\text{ rms}} = 230V$$

$$I_o = 4A$$

$$\alpha = \frac{\pi}{3} = 60^\circ$$

$$(i) V_{dc} = \frac{2V_m}{\pi} \cos \alpha$$


$$V_{dc} = \frac{2 \times 230 \times \sqrt{2}}{\pi} \cos 60^\circ = 103.54V$$

$$\text{given } I_{dc} = 4A = \frac{V_{dc}}{R}$$

$$R = \frac{V_{dc}}{I_{dc}} = 25.89\Omega$$

$$\begin{aligned}
 \text{Active power input } P_i &= \frac{2V_m}{\pi} I_{dc} \cos \alpha \\
 &= \frac{2 \times 230 \times \sqrt{2}}{\pi} \times 4 \times \cos 60^\circ
 \end{aligned}$$

$$P_i = 414.145W$$

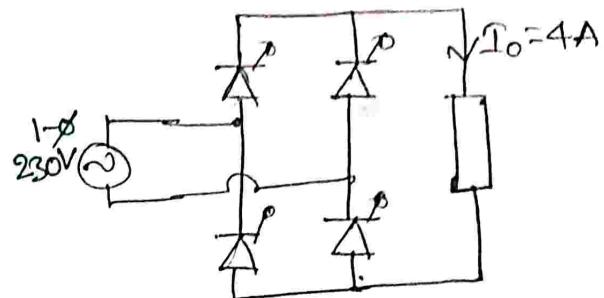

## Reactive power input $Q_i$

$$Q_i = \frac{2V_m}{\pi} I_{dc} \sin \alpha$$

$$= \frac{2 \times \sqrt{2} \times 230 \times 4 \times \sin 60^\circ}{\pi}$$

$$Q_i = 717.32 \text{ VARS}$$

Set 3 (2012)  
Q - 3(b)

- ④ A 230V, 50Hz one pulse SCR controlled converter is triggered at a firing angle of  $40^\circ$  and the load current extinguishes at an angle of  $210^\circ$ . Find the circuit turn-off time,  $V_o$  and  $I_o$  for  $R=5\Omega$  &  $L=2\text{mH}$

$$V_{\text{rms}} = 230V, f = 50\text{Hz}$$

$$\alpha = 40^\circ$$

$$\beta = 210^\circ$$

$$(i) T_{off} = ?$$

$$\omega t_{off} = 2\pi - \beta$$


$$t_{off} = \frac{2\pi - \beta}{\omega} = \frac{2\pi - 2.10 \times \frac{\pi}{180}}{2 \times 50\pi}$$

$$T_{off} = \frac{(2\pi - 1.167\pi)}{2\pi \times 50} = 8.33 \text{ mSec}$$

$$(ii) V_o = \frac{V_m}{2\pi} (\cos \alpha - \cos \beta)$$

$$V_o = \frac{230 \times \sqrt{2}}{2 \times \pi} (\cos 40^\circ - \cos 210^\circ) = 84.48 \text{ V}$$
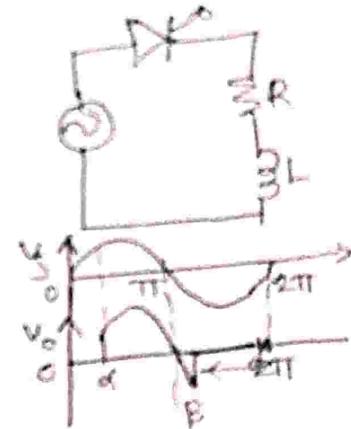
$$I_o = \frac{V_o}{R} = \frac{84.48}{5} = 16.89 \text{ A}$$



$$V_o = \frac{V_m}{2\pi} \int_{\alpha}^{\beta} \sin \omega t dt$$

$$= \frac{2}{\pi} V_m (\cos \alpha - \cos \beta)$$

Set 3 (2012)  
Q - A (b) 1-Ø full converter is made to deliver a constant load current. for  $\alpha = 0^\circ$ ,  $M = 15^\circ$ . calculate the overlap angle when fixing angle is (i)  $30^\circ$  (ii)  $45^\circ$  & (iii)  $60^\circ$

$$\alpha = 0^\circ \quad M = 15^\circ$$

$$I_0 = \frac{V_m}{\omega L_s} [\cos \alpha - \cos(\alpha + M)]$$

Let  $M_1$  be the overlap angle for fixing angle  $\alpha_1$ ,

$$\text{i.e } \alpha_1 = 0 \quad M = 15^\circ$$

$$\frac{V_m}{\omega L_s} [\cos \alpha - \cos(\alpha + M)] = \frac{V_m}{\omega L_s} [\cos \alpha_1 - \cos(\alpha_1 + M_1)]$$

$$\cos 0^\circ - \cos(0 + 15^\circ) = \cos \alpha_1 - \cos(\alpha_1 + M_1)$$

$$0.934 = \cos \alpha_1 - \cos(\alpha_1 + M_1)$$

$$\boxed{\cos(\alpha_1 + M_1) = \cos \alpha_1 - 0.934}$$

i) at  $\alpha = 30^\circ$

$$\cos(30^\circ + M_1) = \cos 30^\circ - 0.934$$

$$\cos(30^\circ + M_1) = 0.832$$

$$30^\circ + M_1 = 33.69^\circ$$

$$\boxed{M_1 = 3.69^\circ}$$

ii) at  $\alpha = 45^\circ$

$$\cos(45^\circ + M_1) = \cos 45^\circ - 0.934$$

$$45^\circ + M_1 = \cos^{-1}(0.673)$$

$$M_1 = 47.7 - 45^\circ$$

$$* \boxed{M_1 = 2.7^\circ} *$$

iii) at  $\alpha = 60^\circ$

$$\cos(60^\circ + M_1) = \cos 60^\circ - 0.934 = 0.466$$

$$M_1 = 62.22^\circ - 60^\circ$$

$$* \boxed{M_1 = 2.22^\circ} *$$

A 1-Φ half wave controlled rectifier with  $R = 10\Omega$  is supplied from 230V, 50Hz supply. Assume  $V_{rms}$  voltage is 50% of max. possible  $V_{rms}$  voltage. Determine  
 ①. firing angle ②. average DC op voltage ③. average  $V_{rms}$  current of SCR.

Sol: - Given data

$$V_S V_{rms} = 230V$$

$$V_m = V_S V_{rms} \times \sqrt{2}$$

$$= 230 \times \sqrt{2} = 325.27 V$$

$$R = 10\Omega$$

$$V_{rms} = \frac{(V_{rms})_{max}}{2}$$

*AT Q. 2*

$$= \frac{V_m}{2\sqrt{\pi}} \sqrt{(\pi - \alpha) + \frac{\sin 2\alpha}{2}}$$

$(V_{rms})_{max}$  at  $\alpha = 0$

$$\therefore (V_{rms})_{max} = \frac{V_m}{2\sqrt{\pi}} \sqrt{\pi + \frac{\sin 0}{2}} = \frac{V_m}{2}$$

$$\therefore \left( \frac{V_m}{2} \right) / 2 = \frac{V_m}{2\sqrt{\pi}} \sqrt{(\pi - \alpha) + \frac{\sin 2\alpha}{2}}$$


$$\left( \frac{\sqrt{\pi}}{2} \right)^2 = (\pi - \alpha) + \frac{\sin 2\alpha}{2}$$

$$\frac{\pi}{4} = \pi - \alpha + \frac{\sin 2\alpha}{2}$$

$$\alpha = \pi - \frac{\pi}{4} + \frac{\sin 2\alpha}{2}$$

$$\alpha = \frac{3\pi}{4} + \frac{\sin 2\alpha}{2}$$

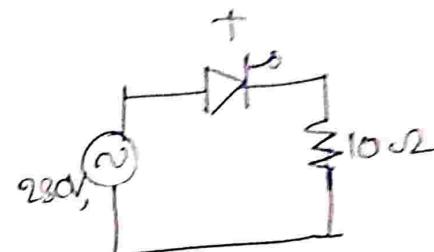Solution is  $\alpha = 114^\circ$  \* trial & error method



(ii) average DC o/p voltage

$$V_{DC} = \frac{V_m}{2\pi} (1 + \cos \alpha) = \frac{325.27}{2\pi} (1 + \cos 114^\circ)$$

$$V_{DC} = 30.71 \text{ V}$$

$$I_{DC} = \frac{V_{DC}}{R} = \frac{30.71}{10} = 3.071 \text{ A}$$

(iii)  $I_{Tavg} = I_{DCavg} = 3.071 \text{ A}$

$$I_{TRms} = \frac{V_{Orms}}{2}$$

$$V_{Orms} = \left( \frac{V_m}{2} \right) \sqrt{2} = \frac{325.27}{2} \sqrt{2} = (162.635) \text{ V}$$

$$I_{Orms} = \frac{162.635}{20} = 8.131 \text{ A}$$

$$I_{TRms} = I_{Orms} = 8.131 \text{ A}$$

---

(x) A  $\frac{1}{2}$  half wave controlled rectifier with  $R = 10\Omega$  is supplied from 230V, 50Hz supply, if the average load current is 10A, determine (i) firing angle, (ii) average DC O/p voltage (iii) rms voltage & current of SCR.

Sol: - given data

$$V_{S\text{rms}} = 230V$$

$$V_m = 230 \times \sqrt{2} = 325.27V$$

$$R = 10\Omega$$

$$I_{DC\text{ avg}} = 10A$$

$$10 = \frac{V_m}{2\pi R} (1 + \cos\alpha)$$

$$\frac{10 \times 2\pi \times 10}{325.27} = 1 + \cos\alpha$$

$$\cos\alpha = 1.9316 - 1$$

$$\alpha = \cos^{-1}(0.9316)$$

$$\boxed{\alpha = 21.31^\circ}$$

(ii) average O/p voltage  $V_{DC} = I_{DC} \times R$   
 $= 100V$

(iii)  $V_{T\text{rms}}$  is difficult to find?  $\therefore V_{O\text{rms}} =$

$$V_{O\text{rms}} = \frac{V_m}{2\sqrt{2}\pi} \sqrt{(\pi - \alpha) + \frac{\sin 2\alpha}{2}}$$

$$= \frac{325.27}{2 \times \sqrt{2}\pi} \sqrt{\left(\pi - 21.31 \times \frac{\pi}{180}\right)} + \frac{\sin 2 \times 21.31}{2}$$

$$= 91.756 \times 1.763$$

$$\boxed{V_{O\text{rms}} = 161.766V}$$

$$\boxed{I_{T\text{rms}} = I_{O\text{rms}} = 16.176A}$$

③ A 1-φ 230V, 1kW heater is connected across a 1-φ, 50Hz supply through an SCR. For the firing angle of  $45^\circ$  &  $90^\circ$ , find the power absorbed by heater element.

Sol:  $V_{\text{rms}} = 230\text{V}$   $V_m = 230 \times \sqrt{2}$   
at  $\alpha = 45^\circ$   $= 325.27\text{V}$

$$V_{DC} = \frac{V_m}{2\pi} (1 + \cos \alpha)$$

$$= \frac{325.27}{2\pi} (1 + \cos 45^\circ)$$

$$V_{DC} = 88.374\text{V}$$

$$P = I^2 R = \frac{V^2}{R}$$

$$V_{\text{rms}} = \frac{V_m}{2\sqrt{\pi}} \sqrt{(\pi - \alpha) + \frac{\sin 2\alpha}{2}}$$

$$= \frac{325.27}{2\sqrt{\pi}} \sqrt{(\pi - \pi/4) + \frac{\sin 90^\circ}{2}}$$

$$V_{\text{rms}} = 155.072\text{V}$$

we know that  $\frac{V_{\text{rms}}^2}{R} = P$

$$\frac{(230)^2}{R} = 1000\text{W}$$

$$R = \frac{(230)^2}{1000} = 52.9\Omega$$

$\therefore$  power consumed by heater at  $\alpha = 45^\circ$  is  $= \frac{V_{\text{rms}}^2}{R}$


$$\frac{(155.072)^2}{52.9} = 454.58\text{W}$$

at  $\alpha = 90^\circ$

$$V_{\text{rms}} = \frac{325.27}{2\sqrt{\pi}} \sqrt{(\pi - \pi/2) + \frac{\sin 180^\circ}{2}} = 0$$

$$V_{\text{rms}} = \frac{325.27}{2\sqrt{\pi}} \times \sqrt{\frac{\pi}{2}} = 115.0\text{V}$$

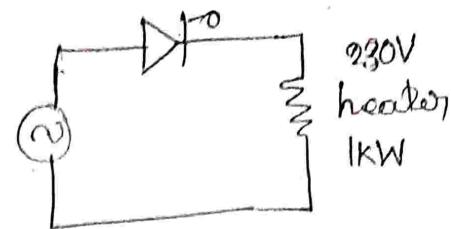power consumed by heater element  $= \frac{(115)^2}{52.9} = 250\text{W}$



Ques:- 1- $\phi$  full-convertor feeds power to RLE load with  $R=6\Omega$ ,  $L=6mH$  and  $E=60V$ . The ac source voltage is 230V, 50Hz. for continuous conduction, find the average value of load current for a firing angle delay of  $50^\circ$

In case one of the four SCR's gets open circuited due to a fault, find new value of o/p voltage and indicate the conduction of various SCR's (To continuous)

Sol:- 1- $\phi$  full-convertor with RLE load

$$V_{S\text{ rms}} = 230V, f = 50\text{Hz}$$

$$V_m = 230\sqrt{2} V$$

$$\alpha = 50^\circ$$

$$R = 6\Omega$$

$$L = 6mH$$

$$E = 60V$$

$$V_{DC} = \frac{2V_m}{\pi} \cos \alpha$$

$$= \frac{2 \times 230 \sqrt{2}}{\pi} \cos 50^\circ$$

$$V_{DC} = 133.084V$$

$$I_o = \frac{V_{DC} - E}{R} = \frac{133.084 - 60}{6}$$

$$\therefore I_o = 12.181A$$

due to fault let  $T_3$  gets damaged & it is open then


$$V_o = \frac{1}{2\pi} \int_{\alpha}^{\pi+\alpha} V_m \sin \omega t d(\omega t)$$

$$= \frac{V_m \cos \alpha}{\pi}$$

$$V_o = \frac{\sqrt{2} \times 230 \cos 50^\circ}{\pi} = 66.542V$$

$$I_o = \frac{66.542 - 60}{6} = 1.0903A.$$

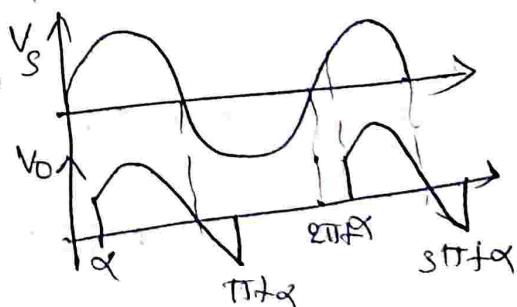$\therefore$  Load current reduced drastically.



⑤ A 1- $\phi$ -full-Converter, connected to 230V, 50Hz source, is feeding a load  $R = 10\Omega$  in series with a large inductance that makes current ripple free. For a firing angle of 45°, calculate the I/p and o/p performance parameters of this converter.

$$V_0 = \frac{2V_m \cos \alpha}{\pi} = \frac{2\sqrt{2} \times 230}{\pi} \cos 45^\circ$$

$$V_{DC} = 146.423V$$

$$I_{DC} = \frac{V_{DC}}{R} = \frac{146.423}{10} = 14.64A$$

$$V_{S\text{rms}} = \frac{V_m}{\sqrt{2}} = V_s = 230V$$

for Ripple free current  $I_{0\gamma} = I_0 = 14.64A$

$$\begin{aligned} P_{DC} &= V_{DC} I_{DC} = 146.423 \times 14.6423 \\ &= 2143.97W \end{aligned}$$

$$\underline{I_{S\text{rms}} = I_0 = I_{0\gamma} = 14.64A}$$

$$\begin{aligned} P_{AC} &= V_{0\gamma} \times I_{0\gamma} = 230 \times 14.6423 \\ &= 3367.73W \end{aligned}$$

$$\text{Rectification } \eta = \frac{P_{DC}}{P_{AC}} = \frac{2143.97}{3367.73} = 0.6366 = 63.66\%$$

$$\text{form factor } FF = \frac{V_{0\gamma}}{V_{DC}} = \frac{230}{146.423} = 1.5708$$

$$\begin{aligned} NRF &= \sqrt{FF^2 - 1} = \sqrt{(1.5708)^2 - 1} \\ &= 1.2114 \end{aligned}$$

Fundamental Component of  $I_S$

$$\boxed{\left( I_{S1} \right) = \frac{2\sqrt{2}}{\pi} \times I_{DC}}$$

$$\begin{aligned} * &= \frac{2\sqrt{2}}{\pi} \times 14.6423 \\ &= 13.183A \end{aligned}$$

$$DF = \cos \alpha = \cos 45^\circ = 0.707$$

$$CDF = \frac{I_{S1}}{I_S} = \frac{13.183}{14.6423} = 0.90032$$

$$HF = THD = \sqrt{\left(\frac{1}{CDF}\right)^2 - 1}$$

$$= \sqrt{\left(\frac{1}{0.90032}\right)^2 - 1}$$

$$\boxed{HF = THD = 0.4834}$$

$$\text{Active power} = V_{DC} \cdot I_{DC} = 2143.97W$$

$$\text{Reactive power} = \frac{2V_m}{\pi} I_{DC} \sin \alpha$$

$$= \frac{2 \times 230 \times \sqrt{2}}{\pi} \times 14.6423 \times \sin 45^\circ$$

$$= 2143.963 \text{ VARs}$$

Input P.F = CDF X DF

$$= 0.90032 \times 0.707$$

$$= 0.63653 \text{ lagging}$$

parameter	full converter	Semi converter
Current Displacement factor (CDF) = $\frac{I_{S1}}{I_S}$	$\frac{2\sqrt{2}}{\pi}$	$\frac{2\sqrt{2} \cos \frac{\alpha}{2}}{\sqrt{\pi(\pi-\alpha)}}$
Harmonic factor (HF) or (THD)-Total harmonic distortion	$THD = \sqrt{\frac{1}{CDF^2} - 1}$	$THD = \sqrt{\frac{\pi(\pi-\alpha)}{8 \cos^2 \frac{\alpha}{2}}} - 1$
Input P.F = CDF X DF	$i/p Pf = \frac{2\sqrt{2}}{\pi} \cos \alpha$	$i/p Pf = \sqrt{\frac{2}{\pi(\pi-\alpha)}} \times (H \cos \alpha)$

- ⑥ A  $\text{H}\phi$  Semi converter with free-wheeling Diode action. The load is operated from a 120V, 60Hz supply. The load current with an average value of  $I_a$  is continuous with negligible ripple content. If the firing angle is  $\pi/3$ , calculate ① HF of ip current ② Displacement factor ③ the input power factor.

Sol- given Data  $V_{S\text{rms}} = 120\text{V}$  | Let  $R = 10\Omega$

$$V_m = 120\sqrt{2}$$

$$\alpha = \frac{\pi}{3} = 60^\circ$$

$$V_{DC} = \frac{V_m(1 + \cos\alpha)}{\pi} = \frac{\sqrt{2} \times 120}{\pi} (1 + \cos\frac{\pi}{3})$$

$$V_{DC} = 81.03\text{V}$$

$$I_{DC} = 8.103\text{A}$$

by neglecting Ripple Voltage or current

$$I_{S\text{rms}} = I_{DC} = 8.103\text{A}$$

$$CDF = \frac{2\sqrt{2} \cos\frac{\alpha}{2}}{\sqrt{\pi(\pi-\alpha)}} = \frac{2\sqrt{2} \cos 30^\circ}{\sqrt{\pi(\pi-\pi/3)}}$$

$$CDF = 0.955$$

① ip current Harmonic factor =  $\sqrt{\left(\frac{1}{CDF}\right)^2 - 1} = \sqrt{\left(\frac{1}{0.955}\right)^2 - 1}$

$$THD = HF = 0.3108$$

② Displacement factor =  $\cos\frac{\alpha}{2} = \cos 30^\circ = 0.866$

③ ip power factor =  $CDF \times DF$   
 $= 0.955 \times 0.866$   
 $= 0.827$


The explanation for waveforms in the above fig. reveals the phase angle relation b/w line voltages leads phase voltages by an angle  $30^\circ$

Let  $V_a, V_b, V_c$  are phase voltages &  $-V_a, -V_b, -V_c$  are corresponding negative phase voltages. & line voltages are  $V_{ab}, V_{bc}, V_{ca}, V_{ba}, V_{cb}$  &  $V_{ac}$ .

$$\begin{array}{ll} \text{Let } V_a = V_{mp} \angle 0^\circ & -V_a = V_{mp} \angle -180^\circ \\ V_b = V_{mp} \angle -120^\circ & -V_b = V_{mp} \angle -300^\circ \\ V_c = V_{mp} \angle -240^\circ & -V_c = V_{mp} \angle 60^\circ \end{array}$$

Line voltages can be related as

$$\begin{aligned} V_{ab} &= V_a - V_b = V_{mp} \angle 0^\circ - V_{mp} \angle -120^\circ \\ &= V_{mp} [\sin \omega t - \sin(\omega t - 120^\circ)] \\ &= V_{mp} 2 \cos\left(\frac{\omega t + \omega t - 120^\circ}{2}\right) \times \\ &\quad \sin\left(\frac{\omega t - \omega t + 120^\circ}{2}\right), \\ &= 2V_{mp} \cos(60^\circ) \sin 60^\circ V_{ab} \\ &= 2V_{mp} \sin(\omega t - 60 + 90^\circ) \times \frac{\sqrt{3}}{2} \\ &= \sqrt{3} V_{mp} \sin(\omega t + 30^\circ) \end{aligned}$$

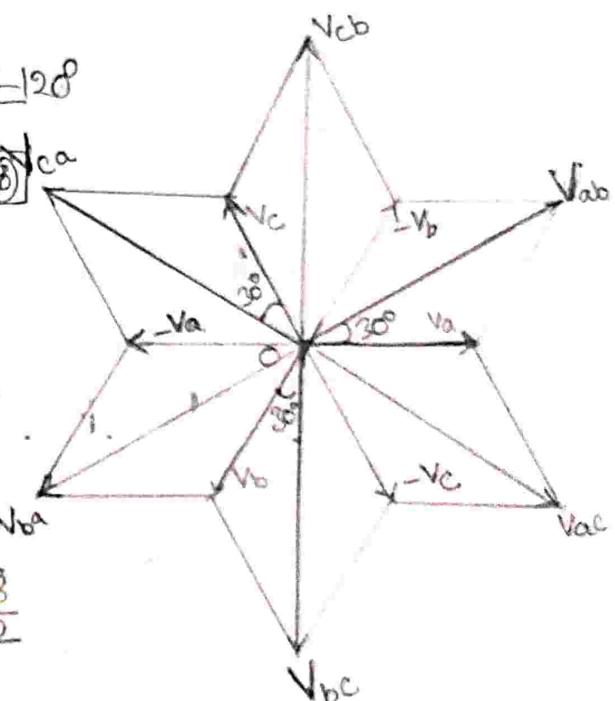

$$\{\sin C - \sin D = 2 \cos\left(\frac{C+D}{2}\right) \sin\left(\frac{C-D}{2}\right)\}$$

$$V_{ab} = V_{mp} \sin(\omega t + 30^\circ) \quad ; \quad \text{where } V_{ml} = \sqrt{3} V_{mp}$$

$$V_{ab} = V_{ml} \angle 30^\circ = \sqrt{3} V_{mp} \angle 30^\circ$$

$$\begin{aligned} V_{bc} &= \sqrt{3} V_{mp} \angle 90^\circ & V_{ba} &= \sqrt{3} V_{mp} \angle -150^\circ \\ V_{ca} &= \sqrt{3} V_{mp} \angle -210^\circ & V_{cb} &= \sqrt{3} V_{mp} \angle 150^\circ \\ V_{ac} &= \sqrt{3} V_{mp} \angle 30^\circ & V_{bc} &= \sqrt{3} V_{mp} \angle -30^\circ \end{aligned}$$

If you

# \* Three phase line commutated Converters \*


In general 3- $\phi$  4-Y Transformer is employed for delivering power to 3- $\phi$  converters. All three-phase controlled converters use line commutation for the turning -off of SCRs.

3- $\phi$  thyristor converters may be classified as under

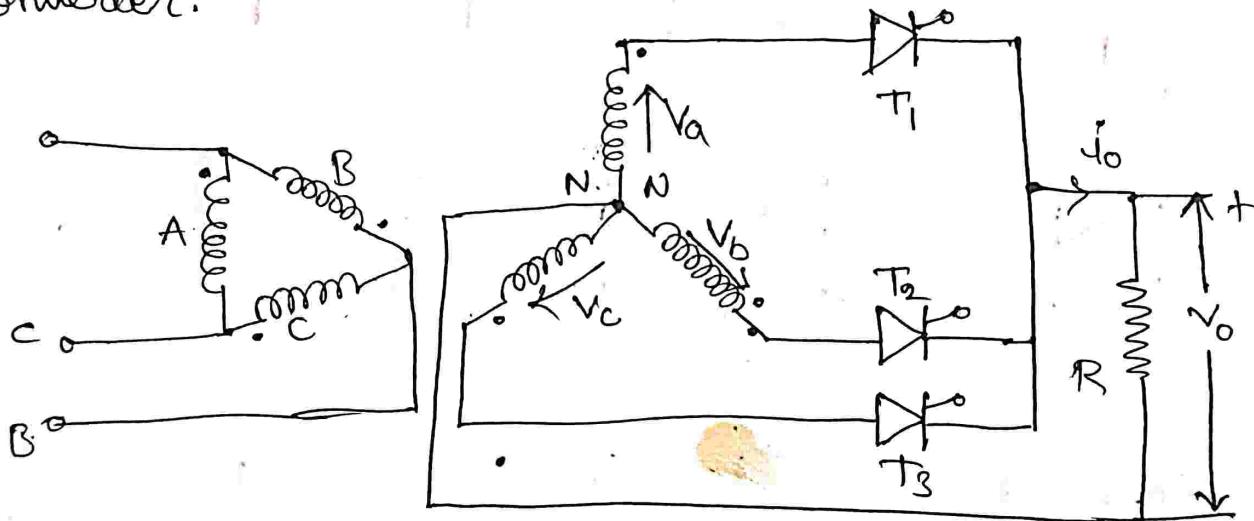- (a) 3-pulse converters
- (b) 6-pulse converters
- (c) twelve-pulse converters

3- $\phi$  Half-wave controlled converter (with R-load):-

It is also called 3- $\phi$  3-pulse converter or 3- $\phi$  M-3 converter.



The above fig. shows the circuit diagram for 3- $\phi$  Half wave (3-pulse M-3) converter with R-load.

If firing angle is zero degrees, SCR T<sub>1</sub> would be conducting from  $\omega t = 30^\circ$  to  $150^\circ$ , T<sub>2</sub> from  $150^\circ$  to  $270^\circ$  and T<sub>3</sub> from  $\omega t = 270^\circ$  to  $390^\circ$  and so on.

each thyristor conducts for  $\frac{360^\circ}{3\text{-pulses}} = 120^\circ$


fixing angle  $\alpha < 30^\circ$ :

The o/p voltage wave form  $V_o$  for  $\alpha < 30^\circ$

$T_1$  conducts from  $\omega t = 30^\circ + \alpha$  to  $\omega t = 150^\circ + \alpha$ .

$T_2$  " "  $\omega t = 150^\circ + \alpha$  to  $\omega t = 270^\circ + \alpha$

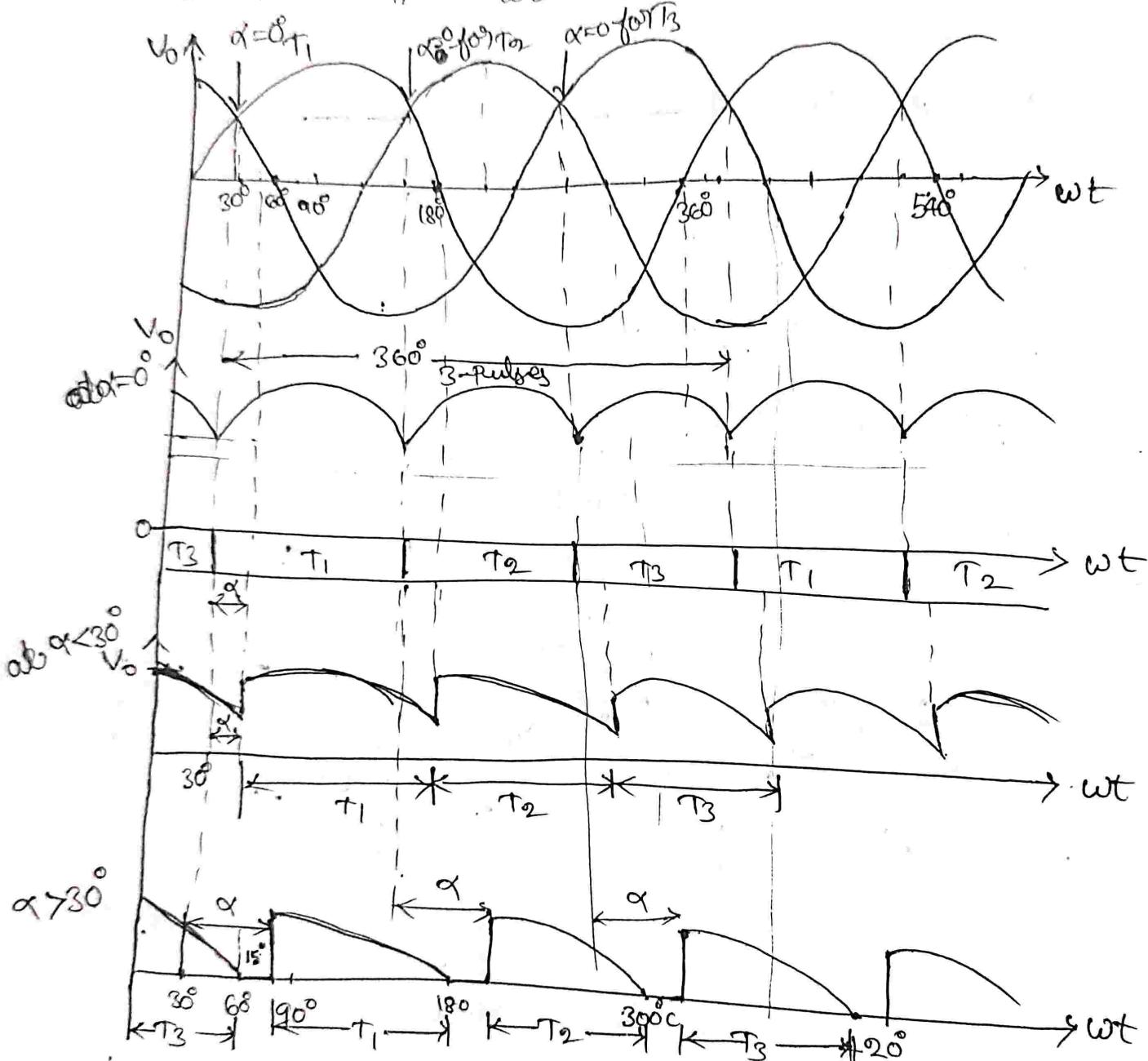$T_3$  " "  $\omega t = 270^\circ + \alpha$  to  $\omega t = 390^\circ + \alpha$  ---



from the o/p voltage wave forms for  $\alpha < 30^\circ$

$$\text{average o/p voltage } V_o = \frac{3}{2\pi} \int_{\alpha + \pi/6}^{\alpha + 5\pi/6} V_{mp} \sin \omega t \, d(\omega t)$$

$$= \frac{3V_{mp}}{2\pi} \left[ -\cos \omega t \right]_{\alpha + \pi/6}^{\alpha + 5\pi/6}$$

$$V_o = \frac{3V_{mp}}{2\pi} [\cos(\alpha + \pi/6) - \cos(\alpha + 5\pi/6)]$$

$$V_o = \frac{3\sqrt{3}}{2\pi} V_{mp} \cos \alpha$$

$V_{mp}$  = maximum value of phase (Line-neutral) voltage

$V_{ml}$  = max. value of line voltage =  $\sqrt{3} \cdot V_{mp}$

$\alpha$  = firing-angle delay

$$\therefore V_o = \frac{3V_{ml}}{2\pi} \cos \alpha$$

$$\text{Average load current } I_o = \frac{V_o}{R} = \frac{3V_{ml}}{2\pi R} \cos \alpha$$

RMS value of o/p load voltage is.

$$V_{o rms} = \left[ \frac{3}{2\pi} \int_{\alpha + \pi/6}^{\alpha + 5\pi/6} V_{mp}^2 \sin^2 \omega t d(\omega t) \right]^{\frac{1}{2}}$$

$$V_{o rms}^2 = \frac{3V_{mp}^2}{4\pi} \int_{\alpha + \pi/6}^{\alpha + 5\pi/6} (1 - \cos 2\omega t) d\omega t$$

$$= \frac{3V_{mp}^2}{4\pi} \left[ \omega t - \frac{\sin 2\omega t}{2} \right]_{\alpha + \pi/6}^{\alpha + 5\pi/6}$$

$$= \frac{3V_{mp}^2}{4\pi} \left[ \frac{2\pi}{3} + \frac{\sqrt{3}}{2} \cos 2\alpha \right]$$

$$V_{o rms} = V_{mp} \sqrt{\left[ \frac{1}{2} + \frac{3\sqrt{3}}{8\pi} \cos 2\alpha \right]}$$

$$= \sqrt{3} V_{mp} \left[ \frac{1}{6} + \frac{\sqrt{3}}{8\pi} \cos 2\alpha \right]^{\frac{1}{2}}$$

$$V_{o rms} = V_{ml} \left[ \frac{1}{6} + \frac{\sqrt{3}}{8\pi} \cos 2\alpha \right]^{\frac{1}{2}}$$

$$\text{Rms load current } I_{o rms} = \frac{V_{o rms}}{R} = \frac{V_{ml}}{R} \left[ \frac{1}{6} + \frac{\sqrt{3}}{8\pi} \cos 2\alpha \right]^{\frac{1}{2}}$$

for  $\alpha > 30^\circ$ :

Half wave

T<sub>1</sub> conducts from  $30^\circ + \alpha$  to  $180^\circ$

T<sub>2</sub> "  $150^\circ + \alpha$  to  $300^\circ$

T<sub>3</sub> "  $270^\circ + \alpha$  to  $420^\circ$

at wt =  $180^\circ$  current flows through T<sub>1</sub> is reaches to

∴ T<sub>1</sub> is turned off at wt =  $180^\circ$

it conducts for  $150^\circ - \alpha$  only

Average o/p voltage is given by

$$V_o = \frac{3}{2\pi} \int_{\alpha + \pi/6}^{\pi} V_{mp} \sin(\omega t) d(\omega t)$$

$$* \boxed{N_o = \frac{3V_{mp}}{2\pi} [1 + \cos(\alpha + 30^\circ)]} *$$

Rms value of o/p voltage  $V_{o rms} = \left[ \frac{3}{2\pi} \int_{\alpha + \pi/6}^{\pi} V_{mp}^2 \sin^2(\omega t) d(\omega t) \right]^{1/2}$

$$V_{o rms} = \frac{\sqrt{3}V_{mp}}{2\sqrt{\pi}} \left[ \left( \frac{5\pi}{6} - \alpha \right) + \frac{1}{2} \sin(2\alpha + \pi/3) \right]^{1/2}$$

$$\boxed{V_{o rms} = \frac{V_{mp}}{2\sqrt{\pi}} \left[ \left( \frac{5\pi}{6} - \alpha \right) + \frac{1}{2} \sin(2\alpha + \pi/3) \right]^{1/2}}$$


$$I_o = \frac{V_o}{R}$$

$$P_{o rms} = \frac{V_{o rms}}{R}$$

or

$$\boxed{V_{o rms} = \sqrt{3}V_{mp} \left[ \frac{5}{24} - \frac{\alpha}{4\pi} + \frac{1}{8\pi} \sin(2\alpha + \pi/3) \right]^{1/2}}$$
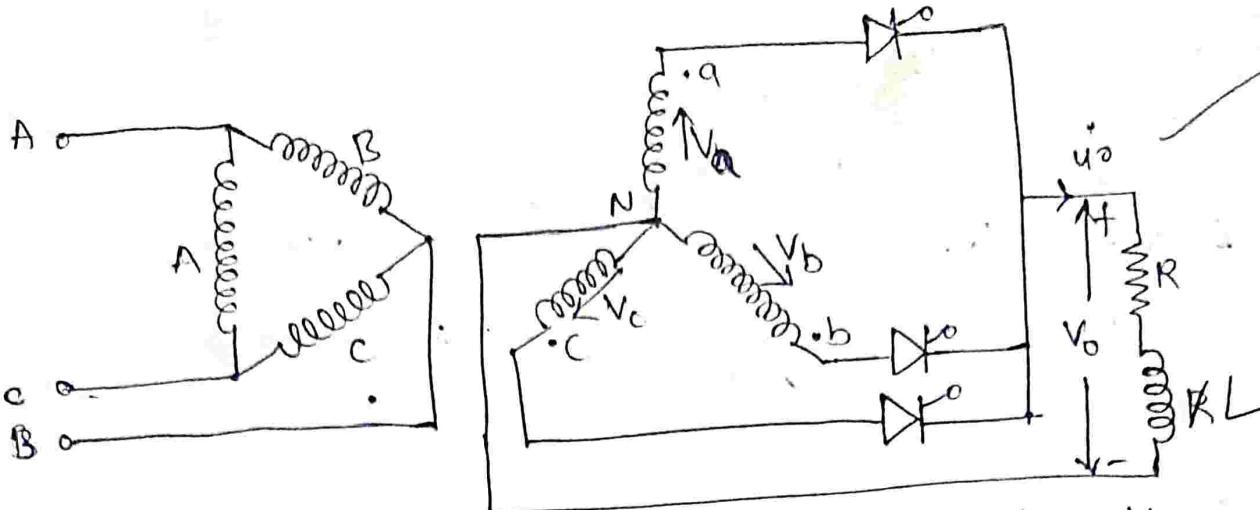
## Half wave Converter with RL load:- (3-phase)



The above fig. Shows the 3- $\phi$  M-3 converter with RL load  
for  $\alpha < 30^\circ$  o/p voltages waveforms are similar to the R-load as discussed above  
for firing angles range of  $30^\circ < \alpha < 90^\circ$  and  $90^\circ < \alpha < 180^\circ$

this converter behaves differently

$30^\circ < \alpha < 90^\circ$  :- at  $\alpha = 90^\circ V_{o\text{avg}} = 0$

$T_1$  - conducts from  $30^\circ + \alpha$  to  $150^\circ + \alpha$ ,  $T_2$  from  $150^\circ + \alpha$  to  $270^\circ + \alpha$ ,  $T_3$  from  $270^\circ + \alpha$  to  $390^\circ + \alpha$ . Thus each SCR Conducts for  $120^\circ$  for fixing angle  $\alpha = 45^\circ$

$T_1$  conducts from  $75^\circ$  to  $195^\circ$ ,  $T_2$  -  $195^\circ$  to  $315^\circ$   $T_3$   $315^\circ$  to  $435^\circ$ .

at  $wt = \pi$   $V_o = 0$  but SCR  $T_1$  current  $i_{T_1}$  is not zero because of RL-load. Therefore,  $T_1$  would be continue conducting beyond  $wt = \pi$   $V_o = V_a$  goes to  $-ve$ .

When  $T_2$  is turn-on at  $wt = 150^\circ + \alpha$  load current shifts from  $T_1$  to  $T_2$  &  $T_1$  gets turn-off.

$T_2$  conducts for  $120^\circ$  thereafter  $T_3$  for  $120^\circ$  then  $T_1$ , etc -- the average value of o/p voltage is same as R-load

$$V_o = \frac{3V_m d}{2\pi} \cos \alpha$$



$$V_{o\text{rms}} = V_m \left[ \frac{1}{6} + \frac{\sqrt{3}}{8\pi} \cos 2\alpha \right]^{\frac{1}{2}}$$

$$I_o = \frac{V_o}{R}$$

$$I_{o\text{rms}} = \frac{V_{o\text{rms}}}{R}$$

$$30^\circ < \alpha < 90^\circ$$

$$\text{at } \alpha = 45^\circ$$

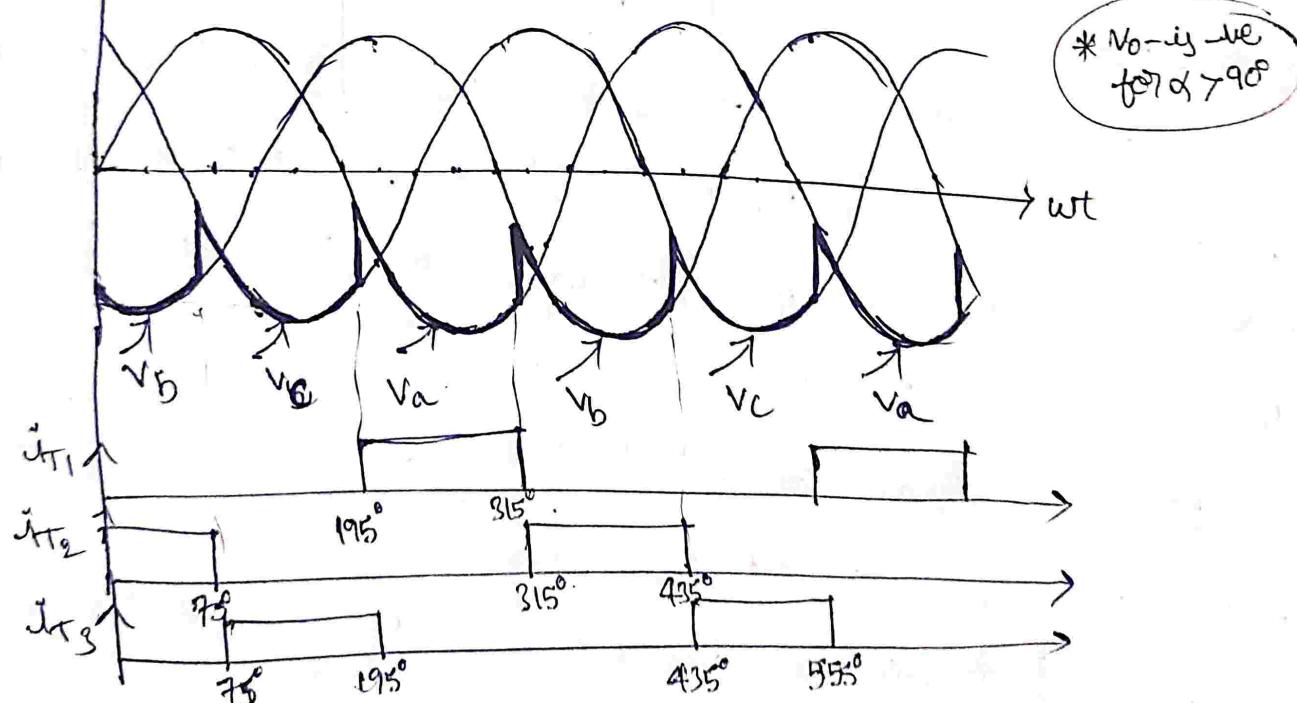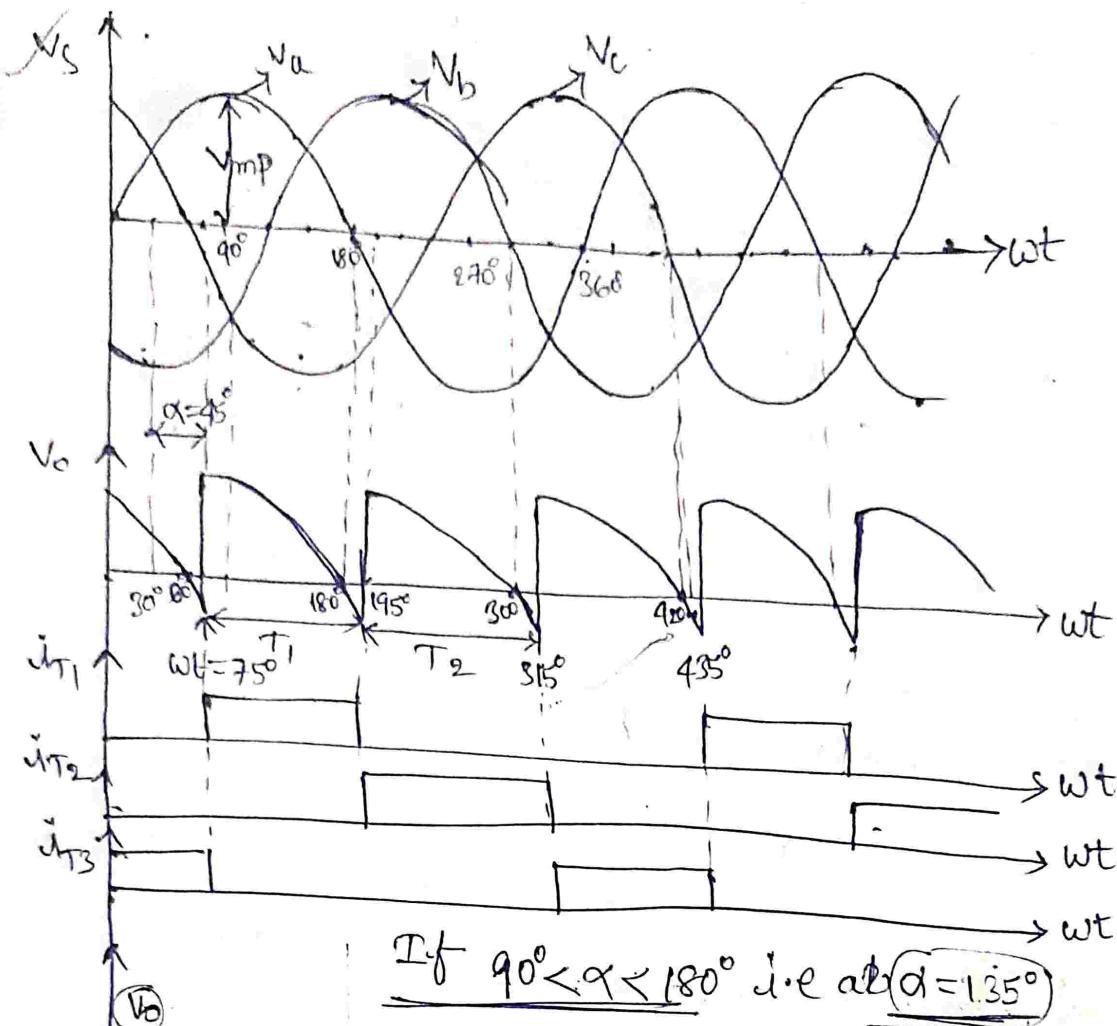


$$I_m = I_a + I_b + I_c = I_o \text{ (load current)}$$

$$I_a = I_b = I_c = I_o / \sqrt{3}$$

Sec. of T/R is connected in zigzag as a result core flux, core losses & temp ↑ are unaffected.

## THREE PHASE FULLY CONTROLLED BRIDGE CONVERTER With Resistive Load

Three-phase fully controlled bridge rectifier with resistive load is shown in Fig. 6.44. For six-pulse operation, each SCR has to be fired twice in its conduction cycle, that is firing intervals should be  $60^\circ$ . As shown in Fig. 6.43 (b), there are six line to line phasors, each having a maximum conduction angle of  $60^\circ$ . The output voltage waveform for different values of ' $\alpha$ ', i.e.  $\alpha = 0^\circ, 30^\circ, 60^\circ, 90^\circ$  and  $120^\circ$  are shown in Fig. 6.45 (a).

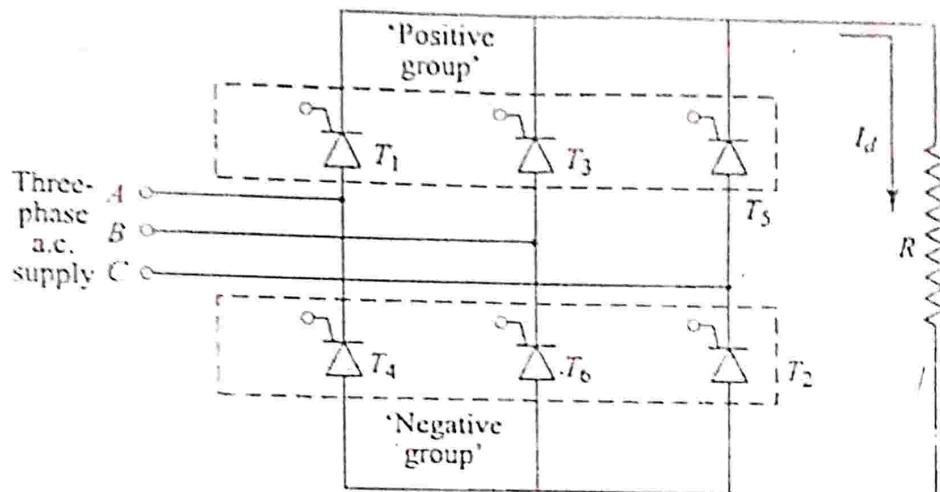

**Fig. 6.44** 3-phase fully controlled bridge rectifier with resistive load

The defining equations for phase and line voltages are:

$$\begin{aligned}
 E_{AN} &= \underline{E_m} \sin(\omega t) & E_{BC} &= \sqrt{3} \underline{E_m} \sin(\omega t - 90^\circ) \\
 E_{BN} &= \underline{E_m} \sin(\omega t - 120^\circ) & E_{BA} &= \sqrt{3} \underline{E_m} \sin(\omega t - 150^\circ) \\
 E_{CN} &= \underline{E_m} \sin(\omega t + 120^\circ) & E_{CA} &= \sqrt{3} \underline{E_m} \sin(\omega t + 150^\circ) \\
 E_{AB} &= \sqrt{3} \underline{E_m} \sin(\omega t + 30^\circ) & E_{CB} &= \sqrt{3} \underline{E_m} \sin(\omega t + 90^\circ) \\
 E_{AC} &= \sqrt{3} \underline{E_m} \sin(\omega t - 30^\circ)
 \end{aligned}$$


The following points can be noted from Fig. 6.45 (a).

- (i) The output voltage waveform for any value of ' $\alpha$ ' is a six pulse wave with a ripple frequency of 300 Hz.
- (ii) *Continuous conduction mode* ( $0 \leq \alpha \leq \pi/3$ ) When the phasor (A-B) is allowed to conduct at ' $\alpha$ ' between zero to  $\pi/3$ , it continues to conduct by  $60^\circ$  when the phasor (A-C) is fired. The conduction is shifted from SCR  $T_1$  to SCR  $T_3$ .  $T_6$  is commutated off by the reverse-voltage of phase C and B across it. The phasor (A-C) conducts after another  $60^\circ$  after which it is replaced by phasor (B-C) when phase B voltage assumes greater value than C or A. Hence, load current is continuous for ' $\alpha$ ' between 0 to  $\pi/3$ .

(iii) *Discontinuous conduction mode:* ( $\pi/3 \leq \alpha \leq 2\pi/3$ ) When  $\pi/3 \leq \alpha \leq 2\pi/3$ , the phasor (A-B) conducts upto an angle  $\pi$  after which both the thyristors  $T_1$  and  $T_6$  are commutated off because phase B becomes positive with respect to phase C and after  $60^\circ$ , when  $T_2$  and  $T_5$  are fired, phase (A-C) conducts also upto angle  $\pi$ , hence load current remains zero from angle  $\pi$  to the next firing pulse and becomes discontinuous, therefore, the fully-controlled bridge circuit produces a ripple frequency of six times the supply frequency at all trigger angles.

(iv) For  $\alpha = 120^\circ$ , the output voltage is zero and hence  $\alpha_{\max} = 120^\circ (2\pi/3)$ .

### Output Voltage Wave Forms: (R- Load)

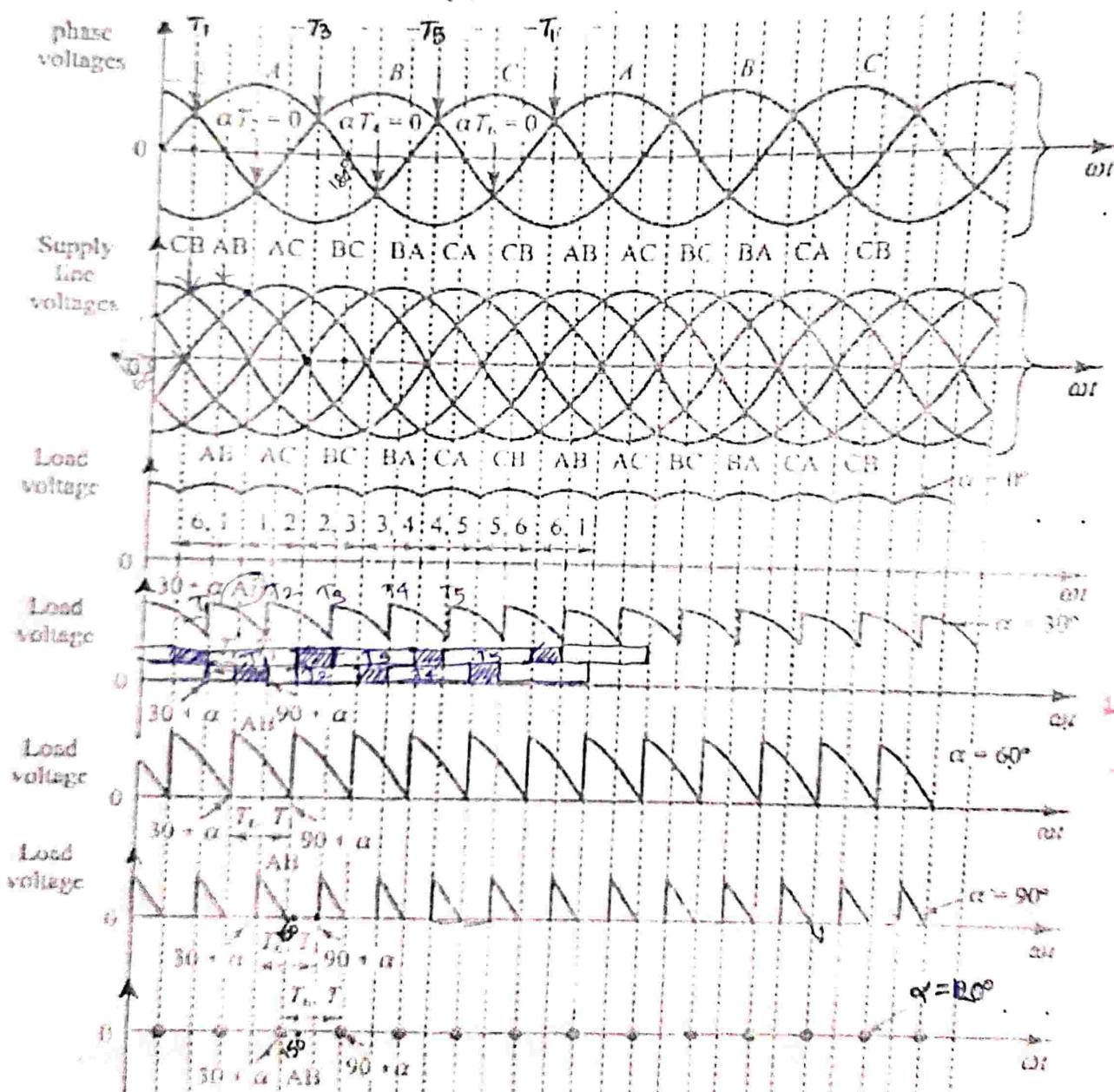

The voltage and current relations for both the modes can be derived as follows:

**(a) Continuous Conduction Mode:** ( $\alpha < 60^\circ$ ) The general equation for the average load voltage is given by

$$E_{dc} = \frac{1}{2\pi} \int_0^{2\pi} E_{AB}(\omega t) \cdot d(\omega t)$$

Now for  $\alpha < 60^\circ$ , and from Fig. 6.45 (a), we can write

$$E_{dc} = 6 \times \frac{1}{2\pi} \int_{\frac{\pi}{6} + \alpha}^{\frac{\pi}{2} + \alpha} E_{AB}(\omega t) \cdot d(\omega t)$$

where the line-to-line-voltage  $E_{AB}$  is given by:

$$E_{AB} = \sqrt{3} E_m \sin(\omega t + \pi/6) \quad (6.48)$$

$$\begin{aligned} \therefore E_{dc} &= \frac{3}{\pi} \int_{\frac{\pi}{6} + \alpha}^{\frac{\pi}{2} + \alpha} \sqrt{3} E_m \sin(\omega t + \pi/6) d(\omega t) = \frac{3\sqrt{3} E_m}{\pi} \int_{\frac{\pi}{3} + \alpha}^{\frac{2\pi}{3} + \alpha} \sin(\omega t) \cdot d\omega t \\ &= \frac{3\sqrt{3} E_m}{\pi} (\cos \omega t) \Big|_{\frac{\pi}{3} + \alpha}^{\frac{2\pi}{3} + \alpha} = \frac{3\sqrt{3} E_m}{\pi} [\cos(\pi/3 + \alpha) - \cos(2\pi/3 + \alpha)] \\ &= \frac{3\sqrt{3} E_m}{\pi} [\cos(\pi/3 + \alpha) + \cos(\pi/3 - \alpha)] \\ &= \frac{3\sqrt{3} E_m}{\pi} (2 \cdot \cos(\pi/3) \cdot \cos \alpha) = \frac{3\sqrt{3} E_m}{\pi} \cos \alpha \end{aligned} \quad (6.49 \text{ (a)})$$

Average load current:

$$I_{dc} = \frac{3\sqrt{3} E_m}{\pi \cdot R} \cos \alpha \quad (6.49 \text{ (b)})$$

**(b) Discontinuous Conduction Mode ( $\alpha > 60^\circ$ )**

From Fig. 6.45(a),

$$E_{dc} = 6 \times \frac{1}{2\pi} \int_{\pi/6 + \alpha}^{\pi/2} \sqrt{3} E_m \sin\left(\omega t + \frac{\pi}{6}\right) d(\omega t) = \frac{3\sqrt{3} E_m}{\pi} \int_{\pi/3 + \alpha}^{\pi/2} \sin(\omega t) d\omega t$$

CCM:  $\alpha < 60^\circ$

Derivation of RMS Voltage

$$V_{\text{rms}} = \left\{ \frac{3}{\pi} \int_{-\pi/6}^{\pi/2} (V_{AB})^2 dt \right\}^{1/2}$$

$$= \left\{ \frac{3}{\pi} \int_{-\pi/6}^{\pi/2} [\sqrt{3} V_{\text{mp}} \sin(\omega t + \pi/6)]^2 dt \right\}^{1/2}$$

$$= \left\{ \frac{3}{\pi} \times (\sqrt{3} V_{\text{mp}})^2 \int_{-\pi/6}^{\pi/2} \sin^2(\omega t) dt \right\}^{1/2}$$

$$V_{\text{rms}}^2 = \frac{9V_{\text{mp}}^2}{\pi} \int_{-\pi/6}^{\pi/2} \left[ 1 - \frac{\cos 2\omega t}{2} \right] dt$$

$$V_{\text{rms}}^2 = \frac{9V_{\text{mp}}^2}{2\pi} \left[ \omega t - \frac{\sin 2\omega t}{2} \right]_{-\pi/6}^{\pi/2}$$

$$= \frac{9V_{\text{mp}}^2}{2\pi} \left[ \frac{\pi}{3} - \frac{\pi}{3} - \frac{1}{2} [\sin(4\pi/3 + 2\alpha) - \sin(2\pi/3 + 2\alpha)] \right]$$

$$= \frac{9V_{\text{mp}}^2}{2} \left[ \frac{1}{3} - \frac{1}{2\pi} \left[ -\frac{\sqrt{3}}{2} \cos 2\alpha + \left(\frac{1}{2}\right) \sin 2\alpha - \left(\frac{\sqrt{3}}{2} \cos 2\alpha + \left(\frac{1}{2}\right) \sin 2\alpha \right) \right] \right]$$

$$V_{\text{rms}}^2 = \frac{9V_{\text{mp}}^2}{2} \left[ \frac{1}{3} + \frac{1}{2\pi} \sqrt{3} \cos 2\alpha \right]$$

\*  $V_{\text{rms}} = \frac{3V_{\text{mp}}}{\sqrt{2}} \sqrt{\left( \frac{1}{3} + \frac{\sqrt{3}}{2\pi} \cos 2\alpha \right)}$  \*

\* Or  
 $V_{\text{rms}} = \frac{3V_{\text{mp}}}{2} \left[ \frac{1}{3} + \frac{\sqrt{3}}{\pi} \cos 2\alpha \right]^{1/2}$

$$= \frac{3\sqrt{3} E_m}{\pi} (\cos \omega t)_{\pi/3+\alpha}^{\pi/3} = \frac{3\sqrt{3} E_m}{\pi} [1 + \cos(\alpha + \pi/3)] \quad (6.50)$$

For  $\alpha_{\max}$ ,  $E_{dc} = 0$ ,  $\therefore \frac{3\sqrt{3} E_m}{\pi} [1 + \cos(\alpha + \pi/3)] = 0$

Hence,  $\alpha_{\max} = 120^\circ$

Average load current:

$$I_d = \frac{3\sqrt{3} E_m}{\pi R} [1 + \cos(\alpha + \pi/3)] \quad (6.51)$$

**Detailed Waveforms (Operation) with R-Load for  $\alpha = 30^\circ$**  Figure 6.45(b) shows the detailed waveforms for output voltage, output current, supply current, SCR current and voltage with  $\alpha = 30^\circ$ . From these waveforms, following points can be noted:

- (i) Output voltage and current waveforms are six pulse with ripple frequency of 300 Hz.
- (ii) For  $\alpha \leq 60^\circ$ , the supply current waveforms are of  $120^\circ$  in each half cycle and for  $\alpha > 60^\circ$  (not shown in figure) it is less than  $120^\circ$ , i.e.  $(180^\circ - \alpha)$  in each half-cycle.
- (iii) For  $\alpha \leq 60^\circ$ , the SCR waveform is  $120^\circ$  wide and for  $\alpha > 60^\circ$ , it is  $(180^\circ - \alpha)^\circ$  wide.
- (iv) PIV rating of SCR is  $\sqrt{3} E_m$ .

### RMS Voltage Derivation in DCM operation ( $\alpha \geq 60^\circ$ )

$$V_{rms}^2 = \frac{1}{\pi/3} \int_{\pi/6+\alpha}^{5\pi/6} [\sqrt{3} V_{mp} \sin(\omega t + \pi/6)]^2 d\omega t$$

$$= \frac{3}{\pi} (\sqrt{3} V_{mp})^2 \int_{\pi/3+\alpha}^{\pi} \sin^2(\omega t) d\omega t$$

$$= \frac{9 V_{mp}^2}{\pi} \int_{\pi/3+\alpha}^{\pi} \left(1 - \frac{\cos 2\omega t}{2}\right) d\omega t$$

$$= \frac{9 V_{mp}^2}{2\pi} \left[ \omega t - \frac{\sin 2\omega t}{2} \right]_{\pi/3+\alpha}^{\pi}$$

$$V_{0rms}^2 = \frac{9V_{mp}^2}{2\pi} \left\{ (\pi - \pi/3 - \alpha) - \frac{1}{2} \left( \sin 2\pi \right)^0 - \sin \left( \frac{2\pi}{3} + 2\alpha \right) \right\}$$

$$V_{0rms}^2 = \frac{9V_{mp}^2}{2\pi} \left\{ \left( \frac{2\pi}{3} - \alpha \right) - \frac{1}{2} \left[ -\sqrt{3}/2 \cos 2\alpha - (-1/2) \sin 2\alpha \right] \right\}$$

$$V_{0rms} = \frac{3V_{mp}}{\sqrt{2}} \left\{ \left( \frac{2}{3} - \frac{\alpha}{\pi} \right) + \frac{1}{4} \left[ \sqrt{3} \cos 2\alpha - \sin 2\alpha \right] \right\}^{1/2}$$

or

$$\therefore V_{0rms} = 3V_{mp} \left\{ \left( \frac{1}{6} - \frac{\alpha}{4\pi} + \frac{\sqrt{3}}{16} \cos 2\alpha - \frac{1}{16} \sin 2\alpha \right) \right\}^{1/2}$$

Ques. No. 1  
A 3-φ full converter is connected to load

① Resistance of  $5\Omega$ , It is supplied from a  $220V, 50Hz$  ac Supply, If the firing angle  $\alpha = 30^\circ$

Determine (i) Average output voltage and current  
(ii) RMS output voltage and current.

given Data:-

3-φ full converter with R-load  
 $R = 5\Omega, \alpha = 30^\circ$

$$V_{mp} = \frac{V_{ml}}{\sqrt{3}} = V_{Lrms} = 220V$$

$$V_{ml} = V_{Lrms} \times \sqrt{2} = 220 \times \sqrt{2}$$

$$V_{mp} = \frac{220 \times \sqrt{2}}{\sqrt{3}} = 179.63V$$

①  $V_{DC} = \frac{3\sqrt{3} V_{mp}}{\pi} \cos \alpha = \frac{3\sqrt{3} \times 179.63}{\pi} \cos 30^\circ$

$$V_{DC} = 257.3V$$

$$I_{DC} = \frac{V_{DC}}{R} = 51.46A$$

②  $V_{0rms} = \frac{3V_{mp}}{2} \left[ \frac{2}{3} + \frac{\sqrt{3}}{\pi} \cos 2\alpha \right]^{\frac{1}{2}}$

$$= \frac{3 \times 179.63}{2} \left[ \frac{2}{3} + \frac{\sqrt{3}}{\pi} \cos 60^\circ \right]^{\frac{1}{2}}$$

$$V_{0rms} = 264.56V$$

$$I_{0rms} = \frac{V_{0rms}}{R} = \frac{264.56}{5} = 52.91A$$

② Set 2 Question  
2018

3-Ø half wave controlled rectifier with R load &  
triggered at  $\alpha = 60^\circ$ , supplied from 3-Ø 220V, 50Hz  
ac Supply. Determine ① DC output voltage and current  
② RMS output voltage and current. ( $R = 10\Omega$ )

Sol:-

$$V_L = 220V$$

$$V_{mfp} = 220 \times \sqrt{2}$$

$$V_{mp} = \frac{220 \times \sqrt{2}}{\sqrt{3}} = 179.63V$$

$$\alpha = 60^\circ \text{ & } R = 10\Omega$$

$$\textcircled{i} \quad V_{dc} = \frac{3\sqrt{3} V_{mp} \cos \alpha}{2\pi} = \frac{3\sqrt{3} \times 179.63}{2\pi} \times \cos 60^\circ$$

$$\boxed{V_{dc} = 74.27V}$$

$$I_{dc} = \frac{V_{dc}}{R} = \frac{74.27}{10} = 7.427A$$

$$\textcircled{ii} \quad V_{rms} = \sqrt{3} V_{mp} \left[ \frac{1}{6} + \frac{\sqrt{3}}{8\pi} \cos 2\alpha \right]^{\frac{1}{2}}$$

$$= \sqrt{3} \times 179.63 \left[ \frac{1}{6} + \frac{\sqrt{3}}{8\pi} \cos(120^\circ) \right]^{\frac{1}{2}}$$

$$\boxed{V_{rms} = 113.13V}$$

$$I_{rms} = \frac{V_{rms}}{R} = \frac{113.13}{10}$$

$$\boxed{I_{rms} = 11.313A}$$

R-1b  
 2019 SSB-2  
 Q 4(b)

A 3-φ full converter is connected to a ~~resistive~~<sup>F</sup> load of  $10\Omega$ . If the firing angle of SCR is  $\alpha = 45^\circ$  and it feeds 4kW power to a resistive load determine the amplitude of maximum line input voltage.

Sol:-

given data

$$R = 10\Omega, \alpha = 45^\circ$$

$$P = 4\text{KW} \quad V_{m,l} = ?$$

$\alpha < 60^\circ \therefore$  It is operated in CCM.

$$V_{o,\text{rms}} = \frac{\sqrt{3} V_{m,p}}{2} \left[ \frac{2}{3} + \frac{\sqrt{3}}{\pi} \cos 2\alpha \right]^{\frac{1}{2}} \rightarrow ①$$

$$V_{o,\text{rms}} = \sqrt{P \cdot R} = \sqrt{4 \times 10^3 \times 10} = 200\text{V}$$

$$200 = \frac{\sqrt{3} V_{m,l}}{2} \left[ \frac{2}{3} + \frac{\sqrt{3}}{\pi} \cos 90^\circ \right]^{\frac{1}{2}} \quad (\because V_{m,l} = \sqrt{3} V_{m,p})$$

$$200 = \frac{\sqrt{3} V_{m,l}}{2} \sqrt{\frac{2}{3}}$$

$$\therefore V_{m,l} = 200 \sqrt{2} = 282.8\text{V}$$

$$\boxed{\therefore V_{m,l} = 282.8\text{V}}$$

A6  
A 3-phase half-wave converter is supplying a load with a continuous constant current of 40A over a firing angle from 0° to 75°. What will be the power dissipated by the load at these limiting values of firing angle? The supply voltage is 415V (line)

Sol:- In 3-φ half wave converter ccm operation for R-load ( $0-30^\circ$ ) only.

Here ( $0-75^\circ$ ) load current is continuous and constant then, the load is (RL or RLE) type.


$$\text{In CCM: } V_o = \frac{3V_{mp}}{2\pi} \cos \alpha \quad V_{rms} = \sqrt{3}V_{mp} \left[ \frac{1}{6} + \frac{\sqrt{3}}{8\pi} \cos 2\alpha \right]^{\frac{1}{2}}$$

$$V_{rms} = 415V$$

$$V_{mp} = \frac{415\sqrt{2}}{\sqrt{3}} \quad & \quad V_{mp} = \frac{415\sqrt{2}}{= 586.89}$$

At  $\alpha = 0^\circ$
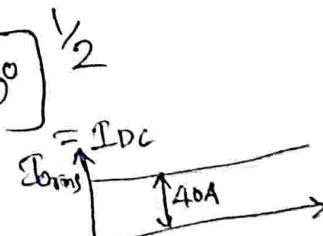
$$V_{rms} = 586.89 \left[ \frac{1}{6} + \frac{\sqrt{3}}{8\pi} \cos 0^\circ \right]^{\frac{1}{2}}$$



$$V_{rms} = 284.86V$$

given  $I_{DC} = I_{rms} = 40A$  ( $\because$  current is continuous & constant)

$\therefore$  Power delivered to the load at  $\alpha = 0^\circ = V_{rms} I_{rms}$

$$P_{\alpha=0^\circ} = 284.86 \times 40 = 9954.4W$$

$$P_{\alpha=0^\circ} = 9.9544kW$$

At

fixing angle  $\alpha = 75^\circ$

$$V_{rms} = V_m \cdot \left[ \frac{1}{6} + \frac{\sqrt{3}}{8\pi} \cos 2\alpha \right]^{\frac{1}{2}}$$

$$\approx 586.89 \left[ \frac{1}{6} + \frac{\sqrt{3}}{8\pi} \cos(2 \times 75^\circ) \right]^{\frac{1}{2}}$$

$$V_{rms} = 191.96 V$$

power dissipated to the load  $\leq V_{rms} I_{rms}$   
at  $\alpha = 75^\circ$

$$= 191.96 \times 40$$

$$= 7678.4$$

$$P = 7.6784 \text{ KW}$$

~~R1b (2019)  
Set 3 AB  
Q 46~~  
3-φ full converter fed by 230V, 50Hz, 3-phase supply. The average load current is 25A and the load is highly inductive. For fixing angle of 60° find RMS, average and peak currents through SCR's

Sol:- For highly inductive load load current is continuous and constant ( $\alpha = 60^\circ$ )  $I_{DC} = I_{avg} = 25A$

$$\text{i) Average current through SCR}' = I_{TA} = \frac{I_{DC}}{3} = \frac{25}{3} = 8.33A$$

$$I_{TA} = 8.33A$$

$$\text{ii) RMS current through SCR}' = I_{T_{rms}} = \frac{I_{rms}}{\sqrt{3}} = \frac{25}{\sqrt{3}}$$

$$I_{T_{rms}} = 14.43A$$

$$\text{iii) Peak current flowing through SCR}' = I_{rms} \times \sqrt{2}$$

$$= 14.43 \times \sqrt{2} = 20.4A$$

A 3- $\phi$  three pulse controlled rectifier with free wheeling Diode  $D_F$  is fed from a 3- $\phi$ , 400V, 50Hz. AC Supply and it is connected with a constant current load of 90A at fixing angle of  $\alpha = 45^\circ$ . Calculate DC output voltage, rms output voltage, Average and RMS currents of freewheeling Diode.

given Data:-

3-phase 3-pulse converter

$$V_{L\text{rms}} = 400V$$

$$\alpha = 45^\circ$$

$$I_{DC} = 90A$$

$D_F$  is present in circuit means

load is "(RL)". or RLE load.

$$\alpha = 45^\circ (\geq 30^\circ)$$




$$(a) V_{DC} = \frac{3V_{mp}}{2\pi} [1 + \cos(\alpha + 30^\circ)]$$

$$V_{mp} = 400 \sqrt{\frac{2}{3}} =$$

$$V_{mp} = 326.6V$$

$$\frac{\pi}{3} = 60^\circ, 30^\circ = \frac{\pi}{6}, 15^\circ = \frac{\pi}{12}$$
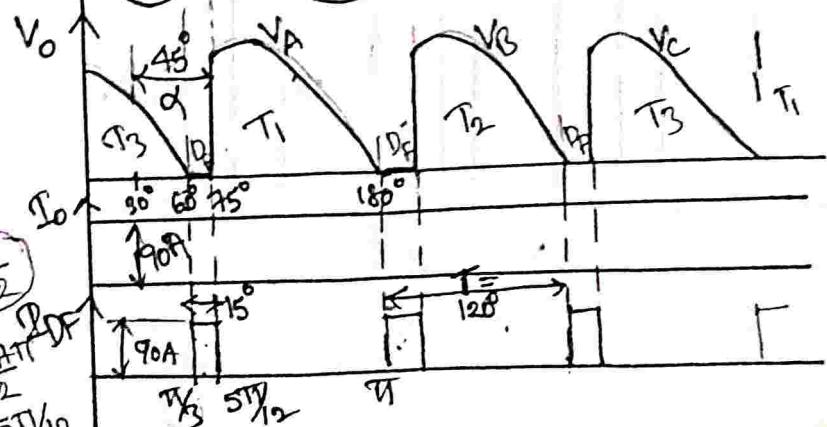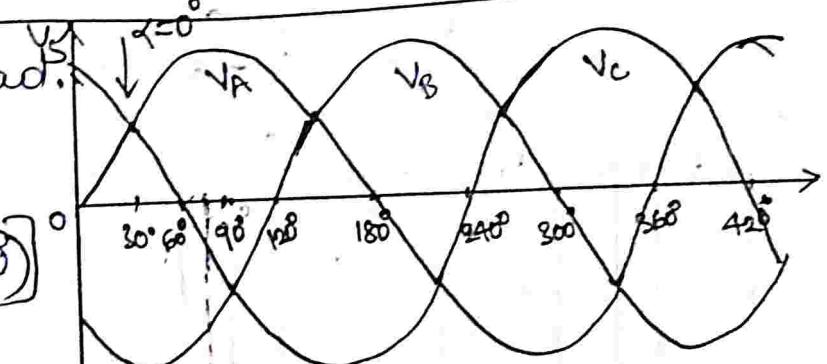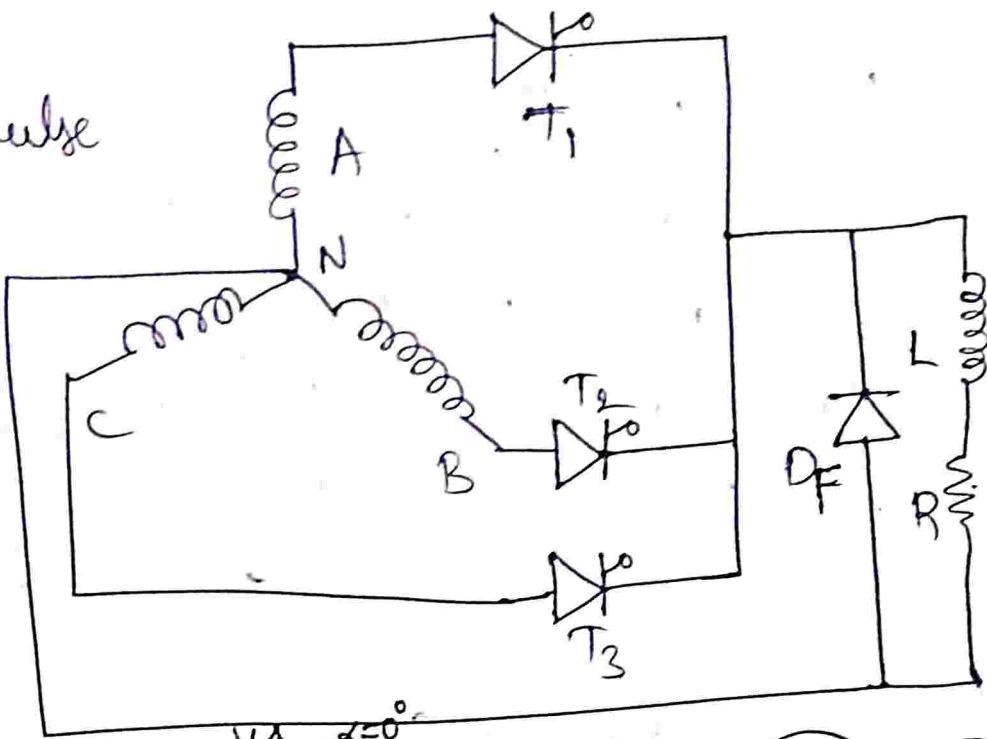
$$75^\circ = T_1 + \frac{\pi}{12} = \frac{4\pi/12 - 2\pi/12}{12} = 5\pi/12$$



$$V_{DC} = \frac{3 \times 326.6}{2\pi} (1 + \cos(45^\circ + 30^\circ))$$

$$\boxed{V_{DC} = 196.3 V}$$

$$\begin{aligned} \textcircled{b} \quad V_{rms} &= \sqrt{3} V_{mp} \left[ \frac{5}{24} - \frac{\alpha}{4\pi} + \frac{1}{8\pi} \sin(3\alpha + \pi/3) \right]^{\frac{1}{2}} \\ &= \sqrt{3} \times (400 \sqrt{\frac{2}{3}}) \left[ \frac{5}{24} - \left( \frac{\pi/4}{4\pi} \right) + \frac{1}{8\pi} \sin(90^\circ + 60^\circ) \right]^{\frac{1}{2}} \end{aligned}$$

$$\boxed{V_{rms} = 230.29 V}$$

\textcircled{c} Average free wheeling Diode currents

$$\text{periodicity } T = 120^\circ = 2\pi/3$$

$$I_{DF\ avg} = \frac{1}{2\pi/3} \int_{\pi/3}^{5\pi/12} I_{DC} dt = \frac{3I_{DC}}{2\pi} \left[ \omega t \right]_{\pi/3}^{5\pi/12}$$

$$= \frac{3I_{DC}}{2\pi} \left[ \frac{5\pi}{12} - \frac{\pi}{3} \right] = \frac{3I_{DC}}{2\pi} \left[ \frac{\pi}{12} \right]$$

$$I_{DF\ avg} = \frac{90}{8} = 11.25 A$$

\textcircled{d} RMS value of free wheeling Diode current =  $I_{D rms}$

$$\begin{aligned} I_{D rms} &= \left\{ \frac{3}{2\pi} \int_{\pi/3}^{5\pi/12} (I_{DC})^2 dt \right\}^{\frac{1}{2}} = \left\{ \frac{3(I_{DC})^2}{2\pi} \left[ \omega t \right]_{\pi/3}^{5\pi/12} \right\}^{\frac{1}{2}} \\ &= \sqrt{\frac{3I_{DC}^2}{2\pi} \left( \frac{\pi}{12} \right)} = \frac{I_{DC}}{2\sqrt{2}} = \frac{90}{2\sqrt{2}} \end{aligned}$$

$$\boxed{I_{D rms} = 31.82 A}$$

## DUAL CONVERTER

**Dual converter**, the name itself says two converters. One will perform as a rectifier and the other will perform as an inverter. Here, two full converters are arranged in anti-parallel pattern and linked to the same DC load. These converters can provide four quadrant operations. The basic block diagram is shown below figure-1.

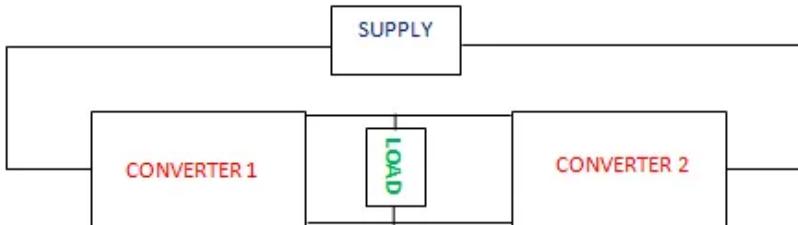


Figure 1

### Modes of Operation of Dual Converter


There are two functional modes: Non-circulating current mode and circulating mode.

#### Non Circulating Current Mode

- Only one converter will perform at a time. So there is no circulating current between the converters.
- During the converter 1 operation, firing angle ( $\alpha_1$ ) will be  $0 < \alpha_1 < 90^\circ$ ;  $V_{dc}$  and  $I_{dc}$  are positive.
- During the converter 2 operation, firing angle ( $\alpha_2$ ) will be  $0 < \alpha_2 < 90^\circ$ ;  $V_{dc}$  and  $I_{dc}$  are negative.

Let say converter-1 acts as a rectifier and supplying the load current. At this instant, converter-2 is blocked by removing the firing angle. For inversion operation, converter-1 is blocked and converter-2 is supplying the load current. The pulses to the converter-2 are applied after a delay time to avoid circulating currents. The delay time is around **10 to 20 msec**.

#### Circulating Current Mode

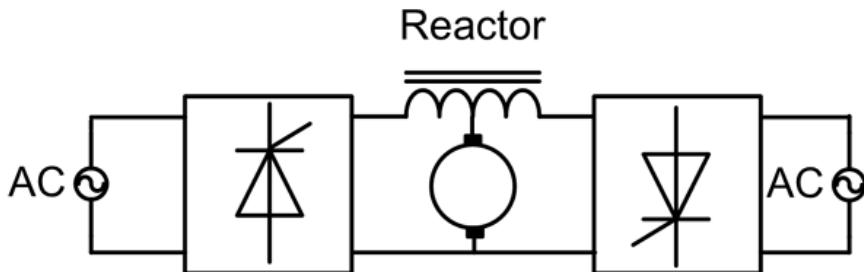

Two converters will be in the ON condition at the same time. So circulating current is present. A **current limiting reactor** is connected between the DC terminals of both converters. The firing angle of the converters is regulated by a control circuit. So, the DC voltages of both converters are equal in magnitude and opposite in polarity. This makes possible to drive current in reverse direction through the load. This makes the minimum amount of circulating current flow through the reactor.

- Average output voltage of Single-phase converter =  $2V_m \cos\alpha / \pi$
- Average output voltage of Three-phase converter =  $3V_m \cos\alpha / \pi$

- For converter 1, the average output voltage,  $V_{01} = V_{max} \cos \alpha_1$
- For converter 2, the average output voltage,  $V_{02} = V_{max} \cos \alpha_2$
- The Output voltage is given by,


$$V_0 = V_{01} = -V_{02}$$

$$V_{max} \cos \alpha_1 = -V_{max} \cos \alpha_2$$

$$\cos \alpha_1 = \cos(180^\circ - \alpha_2) \text{ or } \cos \alpha_2 = \cos(180^\circ + \alpha_1)$$

$$\alpha_1 + \alpha_2 = 180^\circ \text{ And } \alpha_1 - \alpha_2 = 180^\circ$$

- The firing angles are adjusted such that  $(\alpha_1 + \alpha_2) = 180^\circ$ .
- Converter 1 performs as a controlled rectifier when firing angle be  $0 < \alpha_1 < 90^\circ$  and Converter 2 performs as an inverter when the firing angle be  $90^\circ < \alpha_2 < 180^\circ$ . In this condition,  $V_{dc}$  and  $I_{dc}$  are positive.
- Converter 1 performs as an inverter when firing angle be  $90^\circ < \alpha_1 < 180^\circ$  and Converter 2 performs as a controlled rectifier when the firing angle be  $0 < \alpha_2 < 90^\circ$  In this condition,  $V_{dc}$  and  $I_{dc}$  are negative.
- The four quadrant operation is shown below.

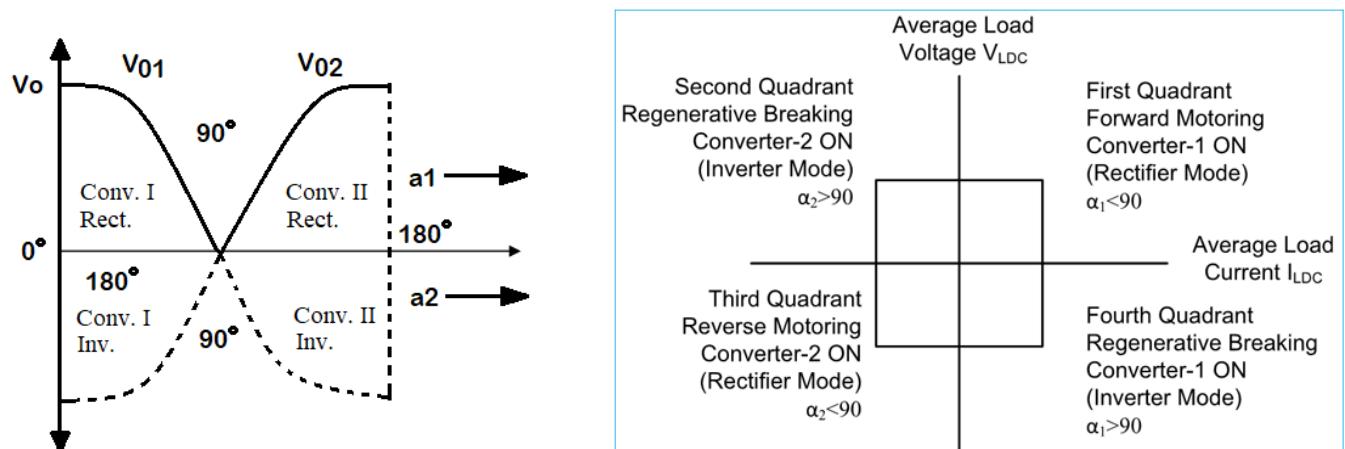

**The advantage of this scheme** is that we can get smooth operation of the converter at the time of inversion. Time response of the scheme is very fast. The normal delay period is 10 to 20 msec in the case of circulating current free operation is eliminated.

**The disadvantage of this scheme** is that, the size and cost of reactor high. Because of the circulating current, the power factor and efficiency are low. To handle the circulating current, the thyristors with high current ratings are required.

### Types of Dual Converters



They are of two types of Dual converters:

- Single-phase dual converter
- Three-phase dual converter.

According to the type of load, single-phase and three-phase dual converters are used.

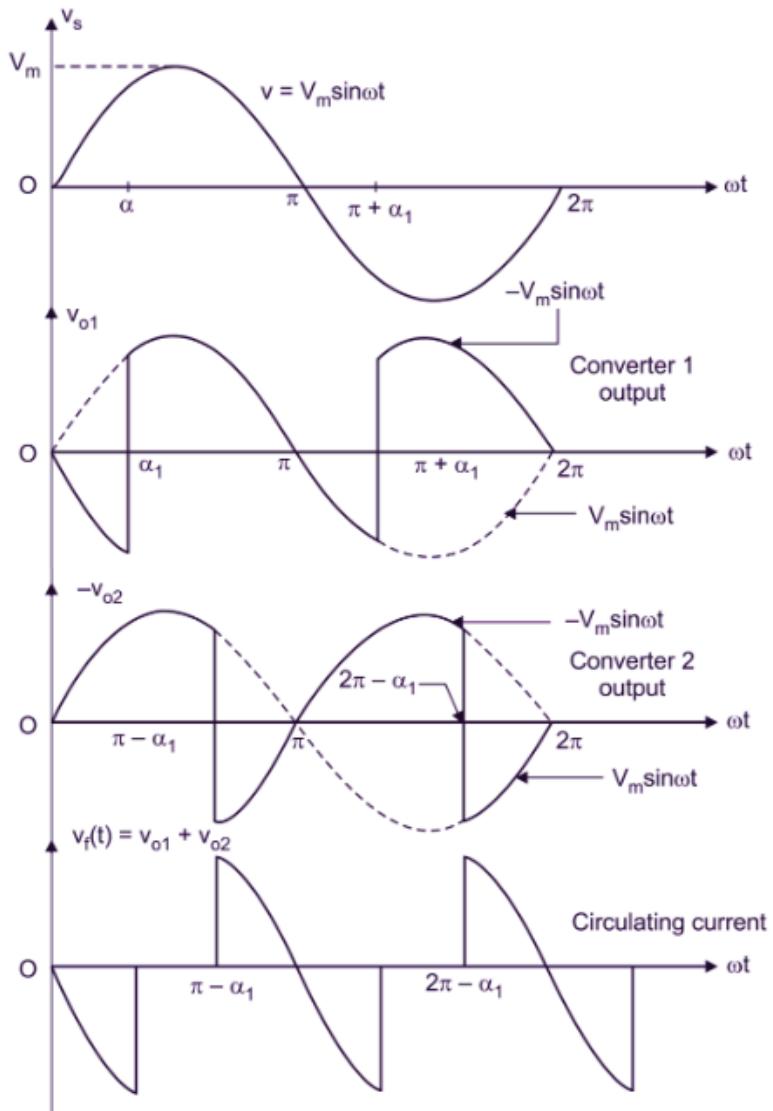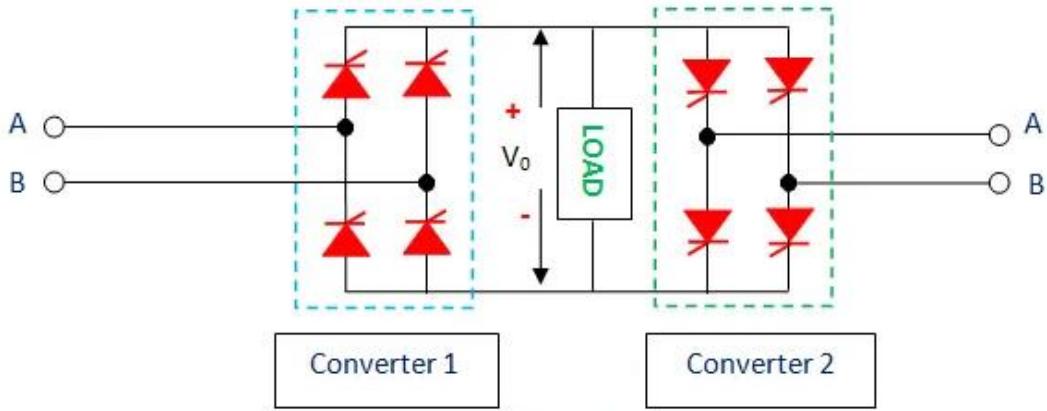
## Single Phase Dual Converter

Consider, a single phase dual converter with non-circulating mode of operation. The input is given to the converter 1 which converts the AC to DC by the method of rectification. It is then given to the load after filtering. Then, this DC is provided to the converter 2 as input. This converter performs as inverter and converts this DC to AC. Thus, we get AC as output.


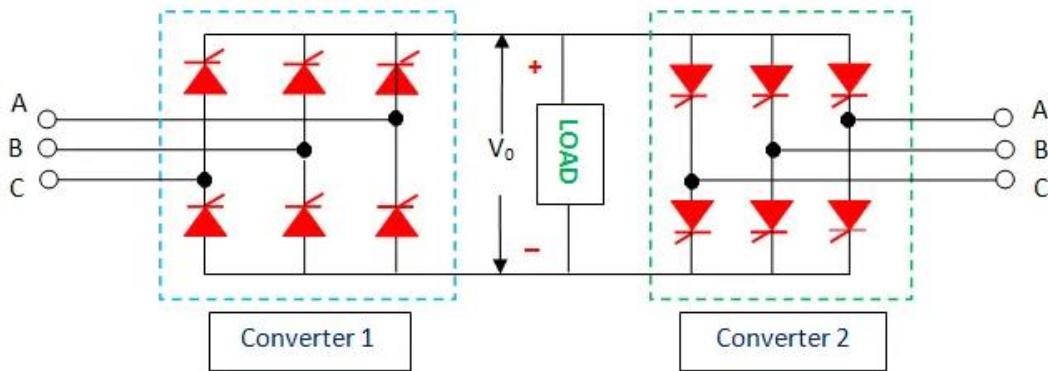
### Three Phase Dual Converter

Here, three-phase rectifier and three-phase inverter are used. The processes are similar to single-phase dual converter. The three-phase rectifier will do the conversion of the three-phase AC supply to the DC. This DC is filtered and given to the input of the second converter. It will do the DC to AC conversion and the output that we get is the three-phase AC. Applications where the output is up to 2 megawatts. The circuit is shown below.



### Application of Dual Converter

- Direction and speed control of DC motors.
- Applicable wherever the reversible DC is required.
- Industrial variable speed DC drives.

### Differences between circulating and Non-circulating current modes:


S. No	With Circulating Current	Without Circulating Current
1.	Reactors are required to limit the circulating current. These reactors may be costly and bulky and consume lot of power.	Reactors are not required for normal operation but sometimes may have to be used to make the load current continuous.
2.	Losses increase due to circulating current and hence efficiency decreases.	Efficiency is higher.
3.	The converter current is due to presence of circulating current.	Converter current can be discontinuous.
4.	Less response time, therefore fast response.	Response time is more so slow response.
5.	Transfer characteristics are linear.	Transfer characteristics are nonlinear due to discontinuous current.
6.	The fault circulating current, due to undesired firing of converters is limited by the current reactor.	Simultaneous firing of both the converter due to faulty signals will create a short circuit condition.
7.	The converter current is higher than the load current, due to circulating current.	The converter current is the same as output current.

## Unit-III

# Chopper | DC to DC Converter

**DC to DC converter** is very much needed nowadays as many industrial applications are dependent upon DC voltage source. The performance of these applications will be improved if we use a variable DC supply. It will help to improve controllability of the equipments also. Examples of such applications are subway cars, trolley buses, battery operated vehicles etc. We can control and vary a constant DC voltage with the help of a **chopper**.

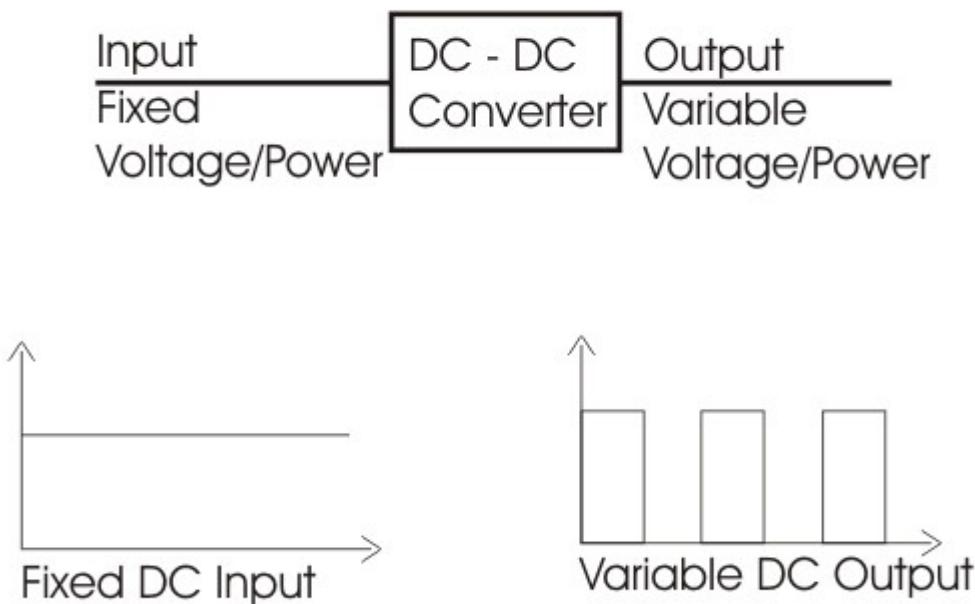Chopper is a basically static power electronics device which converts fixed DC voltage/power to variable DC voltage or power. It is nothing but a high speed switch which connects and disconnects the load from source at a high rate to get variable or chopped voltage at the output.



**Chopper** can increase or decrease the DC voltage level at its opposite

side. So, chopper serves the same purpose in DC circuit transfers in case of ac circuit. So it is also known as DC transformer.

## Devices used in Chopper

Low power application: GTO, IGBT, Power BJT, Power MOSFET etc.

High power application: Thyristor or SCR.


These devices are represented as a switch in a dotted box for simplicity.

When it is closed current can flow in the direction of arrow only.

## Operation of Step Down Chopper with Resistive Load

When CH is ON,  $V_o = V_s$

When CH is OFF,  $V_o = 0$

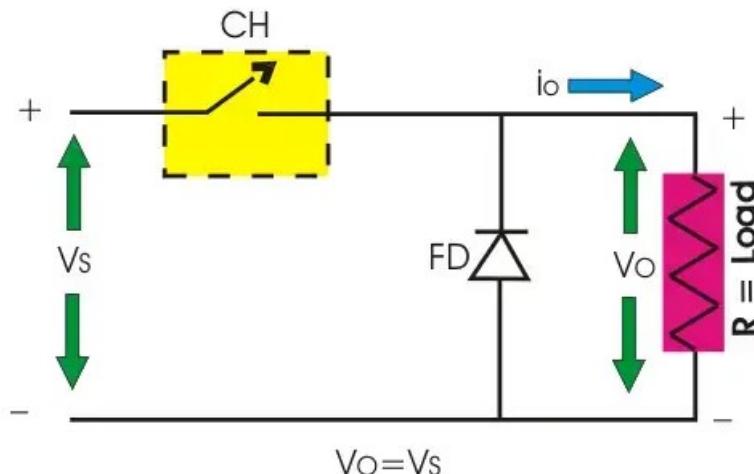

$$\text{Average output voltage } V_o = \frac{1}{T} \int_0^{T_{ON}} V_s dt = \frac{V_s T_{ON}}{T} = DV_s$$

Where, D is duty cycle =  $T_{ON}/T$ .


$T_{ON}$  can be varied from 0 to T, so  $0 \leq D \leq 1$ . Hence output voltage  $V_o$  can be varied from 0 to  $V_s$ .

$$\text{RMS output voltage } V_{or} = \sqrt{\frac{1}{T} \int_0^{T_{ON}} V_s^2 dt} = V_s \sqrt{\frac{T_{ON}}{T}} = \sqrt{D} V_s$$

$$\text{Therefore, Effective input resistance } R_i = \frac{V_s}{T_{avg}} = \frac{V_s}{DV_s/R} = \frac{R}{D}$$

So, we can conclude that output voltage is always less than the input

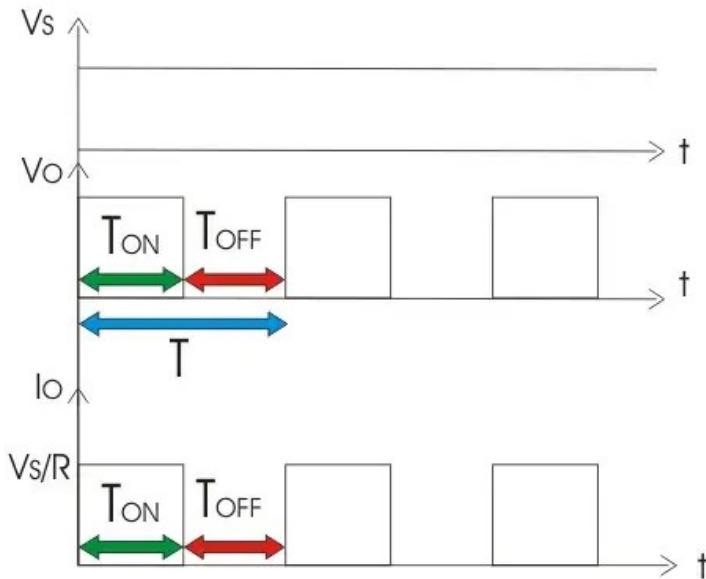voltage and hence the name step down chopper is justified. The output voltage and current waveform of step down chopper with resistive load is shown below.



## Operation Of Step Down Chopper with Inductive Load

When CH is ON,  $V_o = V_s$


When CH is OFF,  $V_o = 0$

### During ON time of Chopper

$$V_s = V_L + V_o \Rightarrow V_L = V_s - V_o \Rightarrow L \frac{di}{dt} = V_s - V_o \Rightarrow L \frac{\Delta I}{T_{ON}} = V_s - V_o$$

Therefore, peak to peak load current,
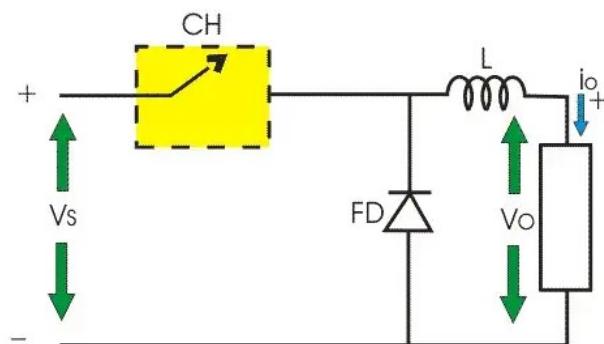
$$\Delta I = \frac{V_s - V_o}{L} T_{ON} \dots \dots \dots (i)$$



## **During OFF Time of Chopper**

If inductance value of L is very large, so load current will be continuous in nature. When CH is OFF inductor reverses its polarity and discharges. This current freewheels through diode FD.

$$\text{Therefore, } L \frac{di}{dt} = V_o$$

$$L \frac{\Delta I}{T_{OFF}} = V_o \Rightarrow \Delta I = V_o \frac{T_{OFF}}{L} \dots\dots\dots(ii)$$

By equating (i) and (ii)

$$\frac{V_s - V_o}{L} T_{ON} = \frac{V_o}{L} T_{OFF}$$

$$\frac{V_s - V_o}{V_o} = \frac{T_{OFF}}{T_{ON}}$$


$$\frac{V_s}{V_o} = \frac{T_{ON} - T_{OFF}}{T_{ON}}$$

$$\text{Therefore, } V_o = \frac{T_{ON}}{T} V_s = DV_s$$

So, from (i) we get,


$$\begin{aligned} \Delta I &= \frac{V_s - DV_s}{L} DT \left[ \text{Since, } D = \frac{T_{ON}}{T} \right] \\ &= \frac{V_s(1 - D)D}{L_f} \left[ f = \frac{1}{T} = \text{Chopping Frequency} \right] \end{aligned}$$

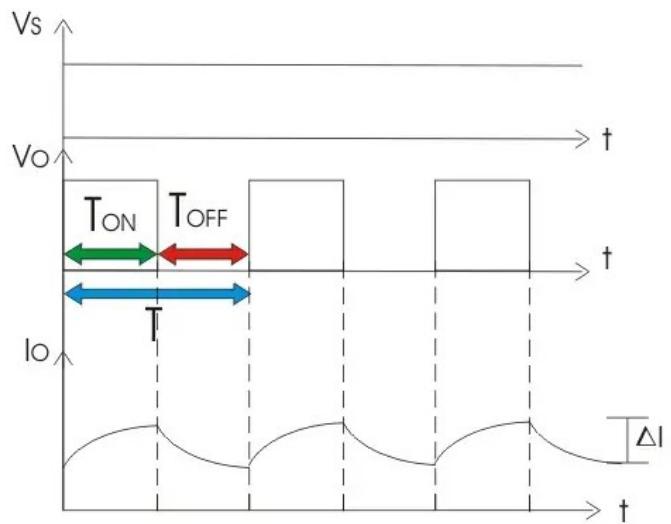
The output voltage and current waveform of step down chopper with inductive load is shown below


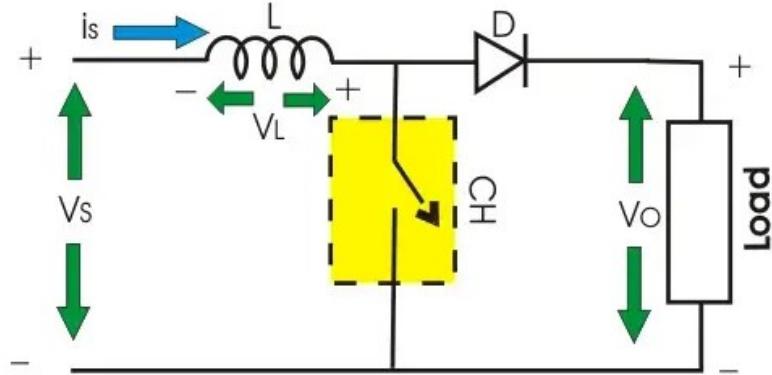
## 2) Step up Chopper or Boost Converter :


Step up chopper or boost converter is used to increase the input voltage level of its output side. Its circuit diagram and waveforms are shown below in figure.



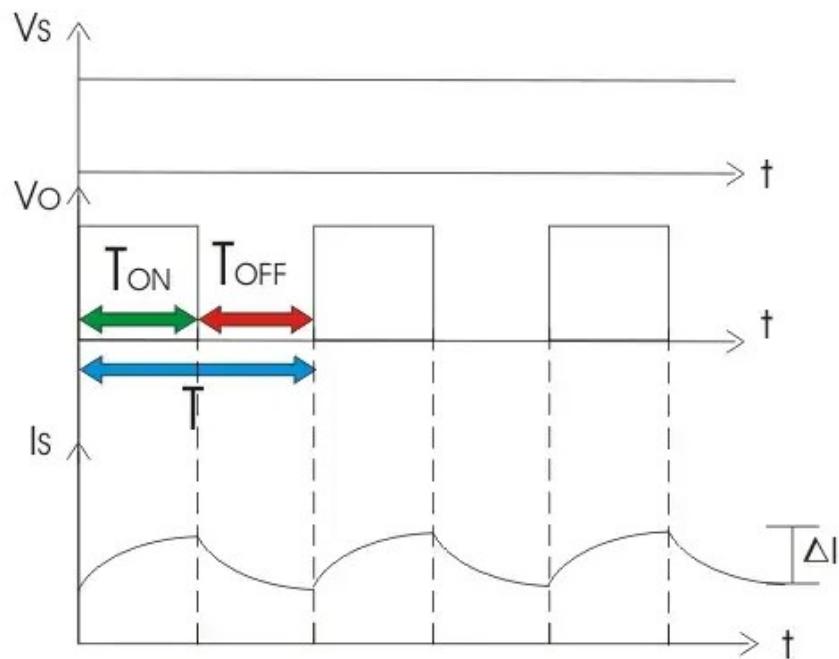

## Operation of Step up Chopper

When CH is ON it short circuits the load. Hence output voltage during  $T_{ON}$  is zero. During this period inductor gets charged. So,  $V_s = V_L$
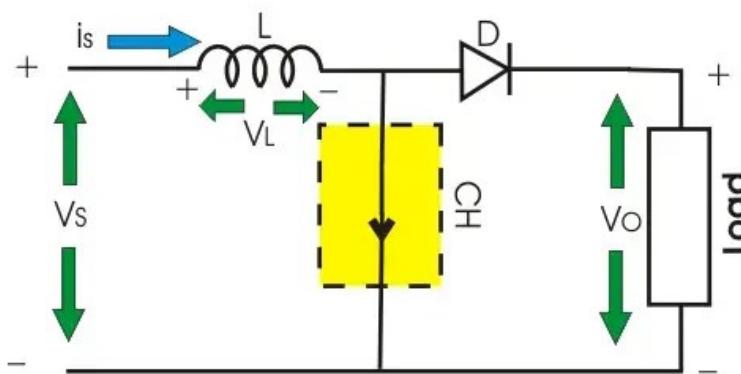
$$L \frac{di}{dt} = V_s \Rightarrow \frac{\Delta I}{T_{ON}} = \frac{V_s}{L} \Rightarrow \Delta I = \frac{V_s}{L} T_{ON} \dots \text{(iii)}$$


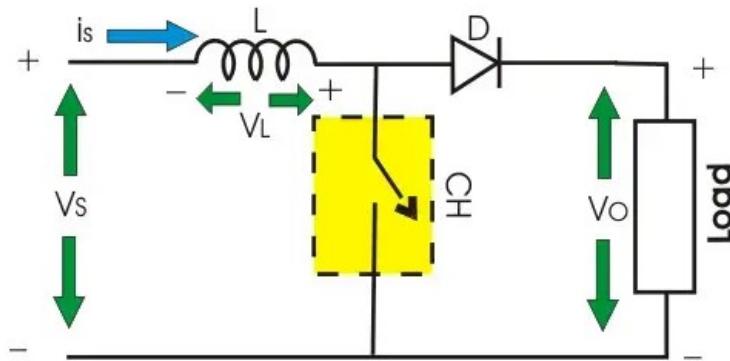
Where,  $\Delta I$  is the peak to peak inductor current.

When CH is OFF inductor L discharges through the load. So, we will get

summation of both source voltage  $V_s$  and inductor Voltage  $V_L$  as output voltage, i.e.

$$V_o = V_s + V_L \Rightarrow V_L = V_o - V_s \Rightarrow L \frac{di}{dt} = V_o - V_s$$

$$\Rightarrow L \frac{\Delta I}{T_{OFF}} = V_o - V_s \Rightarrow \Delta I = \frac{V_o - V_s}{L} T_{OFF} \dots \dots (iv)$$



Now, by equating (iii) and (iv),

$$\frac{V_s}{L} T_{ON} = \frac{V_o - V_s}{L} T_{OFF} \Rightarrow V_s (T_{ON} + T_{OFF}) = V_o T_{OFF}$$

$$\Rightarrow V_o = \frac{T V_s}{T_{OFF}} = \frac{V_s}{(T - T_{ON})/T}$$


$$\text{Therefore, average output voltage, } V_o = \frac{V_s}{1 - D}$$

As we can vary TON from 0 to T, so  $0 \leq D \leq 1$ . Hence  $V_o$  can be varied from  $V_s$  to  $\infty$ . It is clear that output voltage is always greater than the input voltage and hence it boost up or increase the voltage level.

## Buck-Boost Converter or Step Up Step Down Converter

With the help of Buck-Boost converter we can increase or decrease the input voltage level at its output side as per our requirement. The circuit

diagram of this converter is shown below.

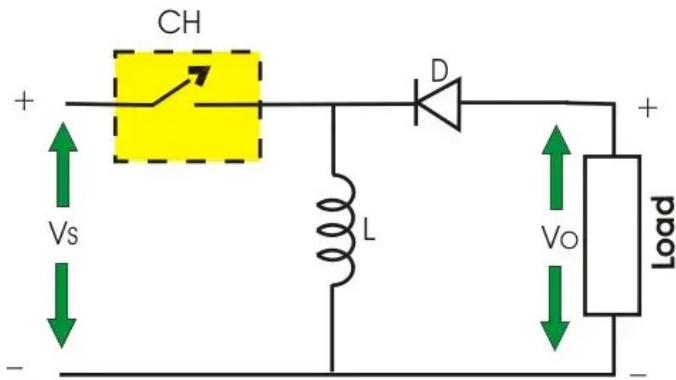

## Operation of Buck-Boost Converter

When CH is ON source voltage will be applied across inductor L and it will be charged.

So  $V_L = V_s$

$$L \frac{di}{dt} = V_s \Rightarrow \Delta I = \frac{V_s}{L} T_{ON}$$

$$\Rightarrow \Delta I = \frac{V_s}{L} T \frac{T_{ON}}{T}$$

$$\Delta I = \frac{DV_s}{Lf} \left[ \text{Since, } \frac{T_{ON}}{T} = D \text{ and } \frac{1}{T} = f = \text{Chopping Frequency} \right] \dots \dots (v)$$

When chopper is OFF inductor L reverses its polarity and discharges through load and diode, So.

$$V_o = -V_L$$

$$L \frac{di}{dt} = -V_o \Rightarrow L \frac{\Delta I}{T_{OFF}} = -V_o \Rightarrow |\Delta I| = -\frac{V_o}{L} T_{OFF} \dots \dots (vi)$$

By evaluating (v) and (vi) we get,

$$\frac{DV_s}{fL} = -\frac{V_o}{L} T_{OFF} \Rightarrow DV_s = -V_o T_{OFF} f$$

$$DV_s = -V_o \frac{T - T_{ON}}{T} = -V_o \left(1 - \frac{T_{ON}}{T}\right) \Rightarrow V_o = -\frac{DV_s}{1 - D}$$

$$\left[ \text{Since, } D = \frac{T_{ON}}{T} = \frac{T - T_{OFF}}{T} \right]$$

Taking magnitude we get,

$$V_o = \frac{DV_s}{1 - D}$$

D can be varied from 0 to one.

When, D = 0; V<sub>o</sub> = 0

When D = 0.5, V<sub>o</sub> = VS

When, D = 1, V<sub>o</sub> =  $\infty$

Hence, in the interval  $0 \leq D \leq 0.5$ , output voltage varies in the range  $0 \leq V_o \leq V_s$  and we get step down or Buck operation.

Whereas, in the interval  $0.5 \leq D \leq 1$ , output voltage varies in the range  $V_s \leq V_o \leq \infty$  and we get step up or Boost operation.